



Buck Regulator Architectures

4.1 Overview



Buck-Switching Converters





Synchronous

Non-Synchronous


(Internal-FET) Regulators

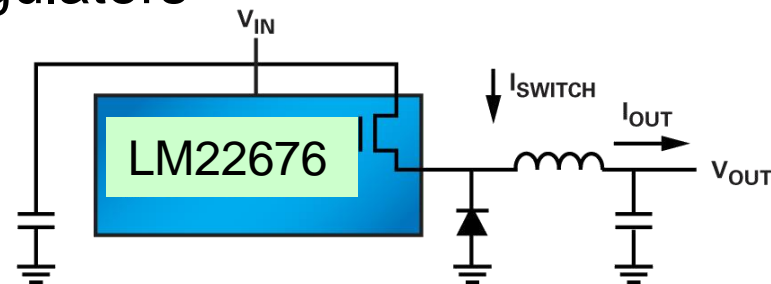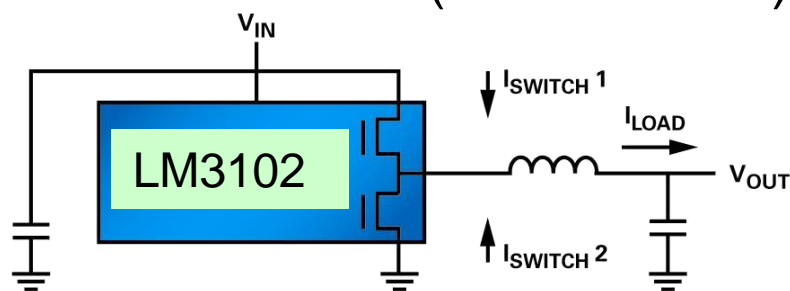


(External-FET) Controllers

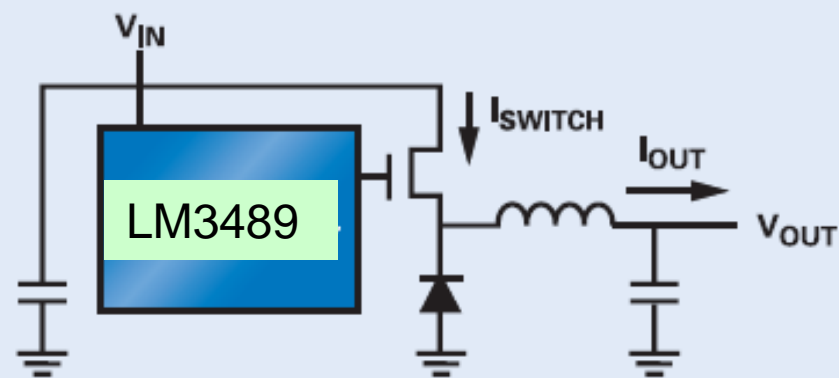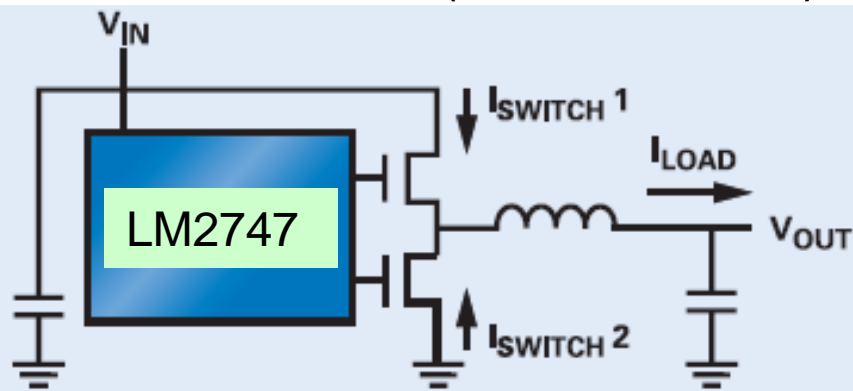

Non-Synchronous Buck Converters

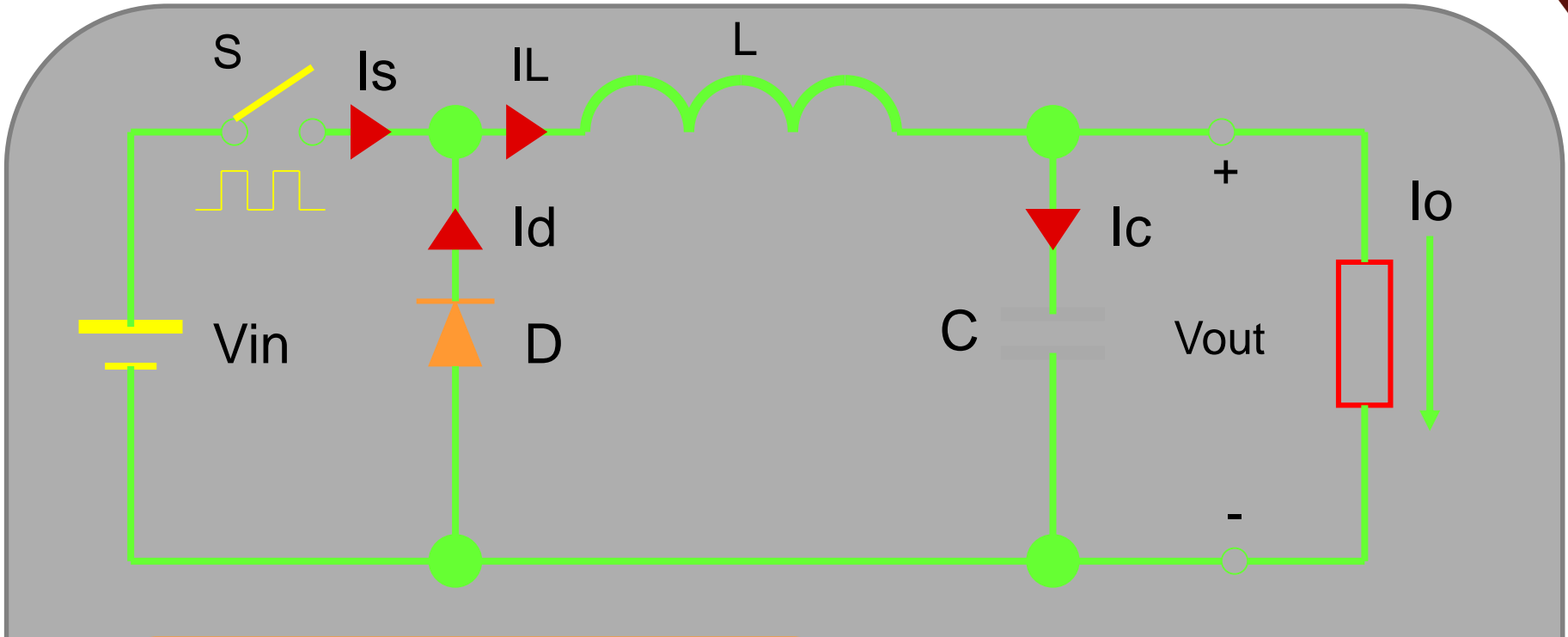
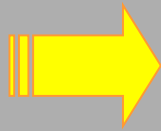
$$\Delta I_{L, Ton} = \Delta I_{L, Toff}$$
$$\Delta I_{L, Ton} = (V_{in} - V_{out}) * T_{on} / L$$
$$\Delta I_{L, Toff} = -V_{out} * T_{off} / L$$




$$V_{out} = D * V_{in}$$
$$D = T_{on} / (T_{off} + T_{on})$$

Buck Topology: Current and Voltage Waveforms



Input current

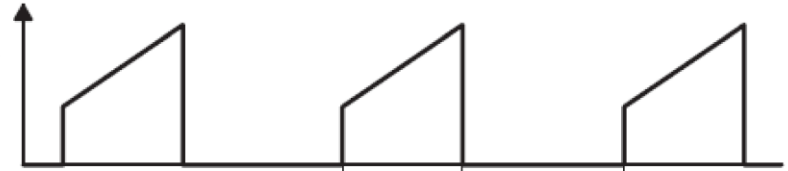


Low side switch or diode



Output and Inductor




Switch

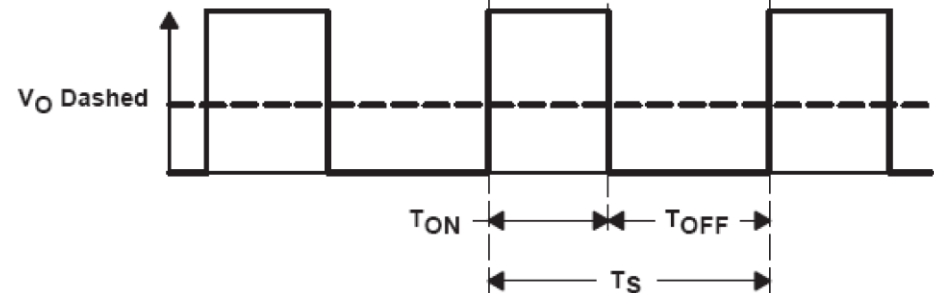


Light-Load Operation: CCM and DCM



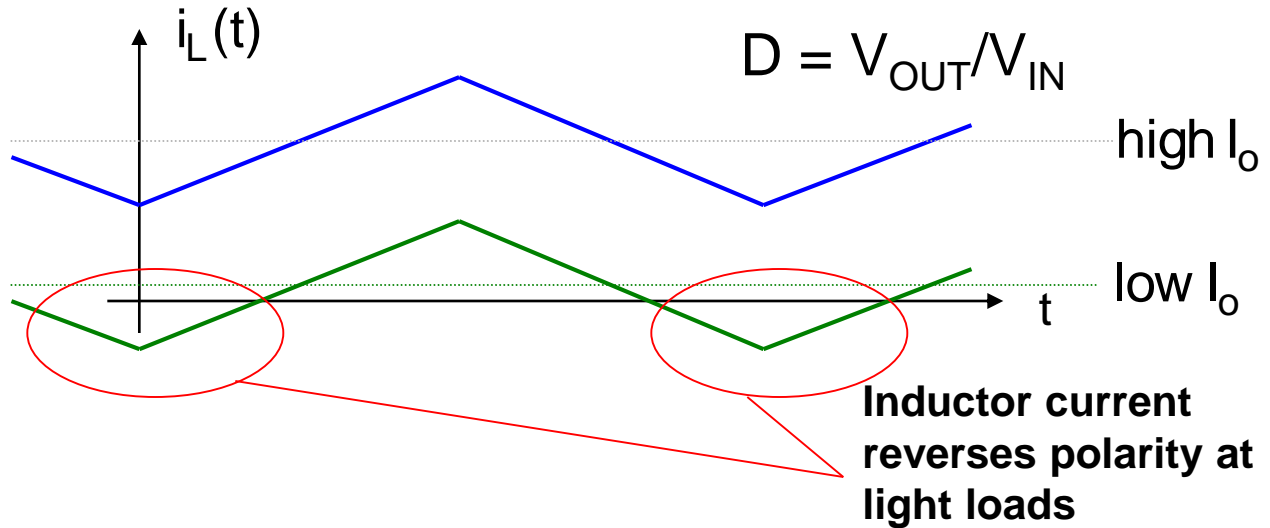Full Synchronous
Mode. Stays in
Continuous
Conduction Mode
(CCM)



Diode or
Diode Emulation

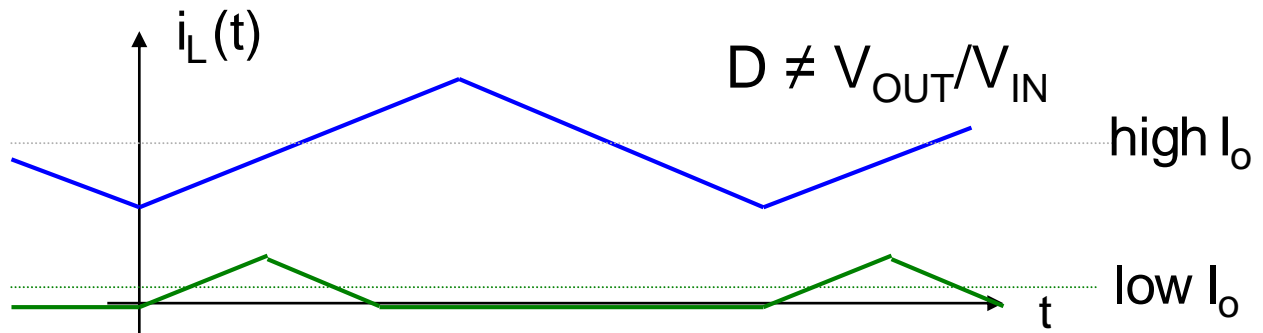


Inductor current drops to zero before the end of the cycle: “Discontinuous Conduction Mode” (DCM)


Cross Conduction with Synchronous Buck



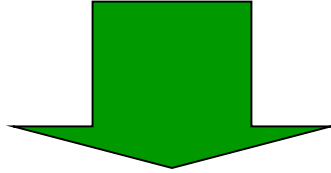- Direct Connection between V_{IN} and Ground



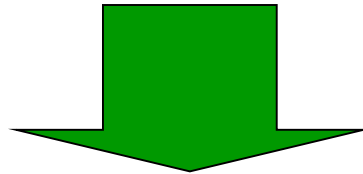- High – Side and Low – Side must not be in ON state at the same time



- A time in which both MOSFET are Turned OFF is required:
DEAD - TIME

DEAD – TIME



- **FIXED DEAD – TIME**
 - Fixed time between Turn-OFF and Turn-ON
 - No flexibility in MOSFET choice
- **ADAPTATIVE DEAD – TIME**
 - High-Side turns ON only if LS is OFF and vice versa
 - Full flexibility in MOSFET choice
- It is necessary to detect the Turn-OFF of both MOSFET



Control Mode

- Voltage Mode Control (VMC)
- Current Mode Control (CMC)
 - Peak Current Mode Control (PCMC)
 - Valley Current Mode Control (VCMC)
 - Average Current Mode Control (ACMC)
- Hysteretic Mode Control (HMC)

Voltage Mode Control Advantages and Disadvantages



- Advantages
 - Stable modulation/less sensitive to noise
 - Single feedback path
 - Can work over a wide range of duty cycles
- Disadvantages
 - Loop gain proportional to V_{IN}
 - LC double pole often drives Type III compensation
 - CCM and DCM differences - a compensation challenge
 - Slow response to input voltage changes
 - Current limiting must be done separately

Current Mode Control Advantages and Disadvantages



- Advantages
 - Power plant gain offers a single-pole roll-off
 - Line rejection
 - Cycle-by-cycle current limiting protection
 - Current sharing
- Disadvantages
 - Noise
 - Minimum ON-time
 - Sense resistor

Hysteretic Mode Control Advantages and Disadvantages



- Advantages
 - Ultra fast transient response (preferred to use in power hungry load)
 - No phase compensation required; In other words, Hysteretic Mode is a kind of large signal control
- Disadvantages
 - Noise Jitter susceptible
 - Very layout sensitive
 - Large switching frequency variation; Minimum ripple requirement



Thank you!