

# **Over Current Protection Alternatives**

## **Motor Current Control With INA240**

**MHRS-Current Sensing Team**

**Dan Harmon, Automotive & Communications Marketing**

**Sept-2016**

# Agenda


- 5 mins – Current & Power Measurement Introduction
- 20 mins – Over Current Protection: Circuits & Techniques
  - » Discrete vs. Integrated
  - » Dedicated / Analog Output / Multiple ALERTs
  - » Power Monitors
- 25 mins – Motor Current Control With INA240
  - » Introduction to Motor Current Sensing
  - » INA240 Performance Competitive Study

# Current & Power Measurement use cases

Solutions customers seek



Real-time overcurrent  
protection (OCP)

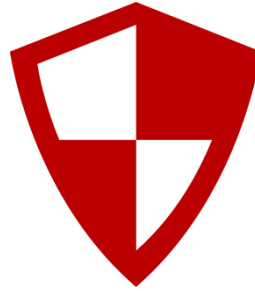


Current and power  
monitoring for system  
optimization



Current measurement for  
closed loop circuits
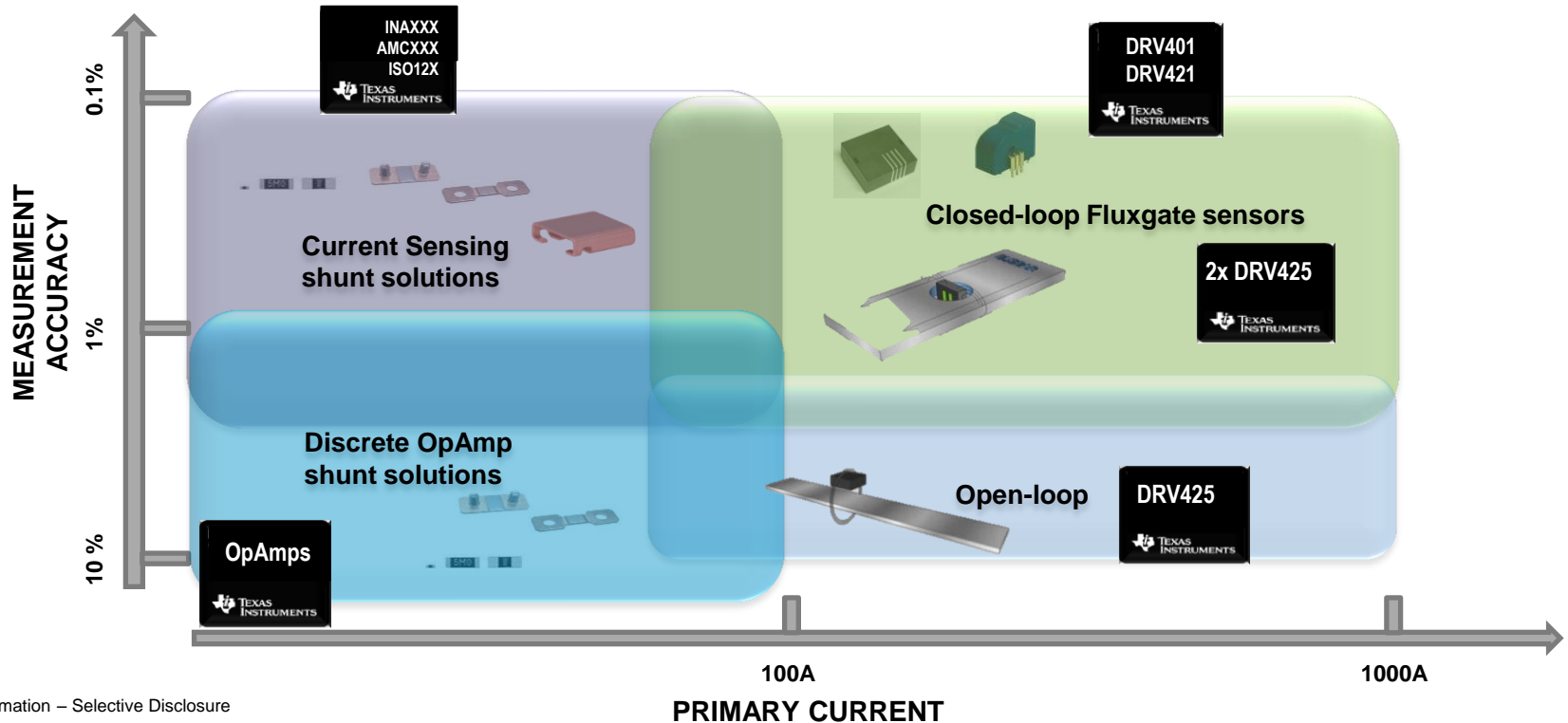
# TI's wide range of Current Sensing solutions



# Overcurrent Protection Alternatives

The strengths and challenges of the various overcurrent protection alternatives

# Why is overcurrent protection important?



- Overcurrent protection is the most basic form of current monitoring
- Historically, OCP has been managed by measuring the system's **temperature**.
  - Temperature typically is a lagging indicator.
  - The increase in system temperature normally is a result of increased current flow.
  - Measuring the current allows the system integrator to manage the thermals in their systems more efficiently and anticipate problems instead of reacting to potential issues.
- System thermal management has become more critical as two trends work against each other in modern electronic systems: driving **higher performance** in **smaller form factors**.

# Fuses for overcurrent protection



- Using a fuse is the most common overcurrent implementation, “after the fact”.
- The sole purpose is to open in the event of an extended over-current condition
  - Very simple
  - Effective in protecting the system from gross, over-current events
- Challenges to overcome:
  - Offers protection for a single event
    - The fuse is destroyed by the over-current event while protecting the remainder of the system
    - For the system to become functional again, the fuse must be replaced
      - This could involve rework at the board level to remove and replace the blown fuse
  - Typically requires that the current significantly exceed (4 times or more) the rating of the fuse in order for a quick open to occur
    - Difficult to predict the precise over-current level at which the fuse will open; requires more margin to be built into the protection scheme.
  - Does not provide information on the system’s actual operating conditions.
- It is better to protect “before the fact”, what are the alternatives?
  - The next several slides will try to picture the very condensed history of the evolution of current protection with active circuits.
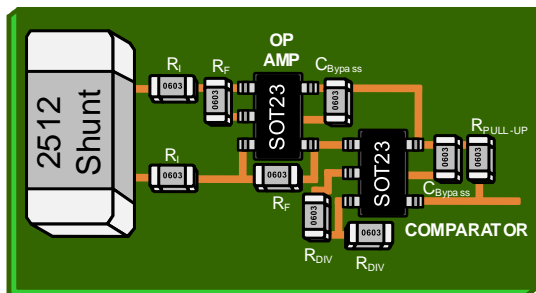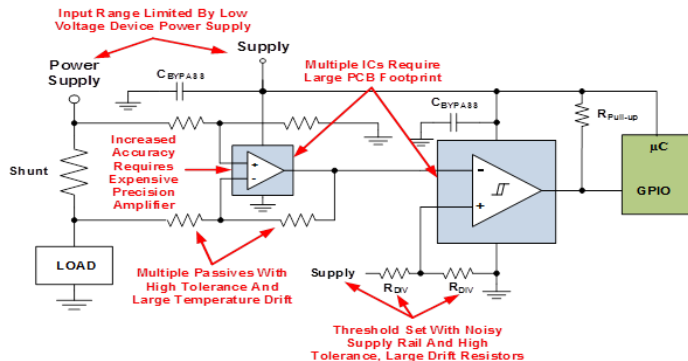
# Classic Op-amp & Comparator Implementation





Op Amp +  
Comparator  
OCP

- Strengths:
  - Possibly the lowest cost to implement
  - Fastest response time with high-speed amp and fast comparator
  - Offers both overcurrent detection and current monitoring
  - Second source alternatives
- Challenges:
  - ACCURACY & SPEED cost money!
    - Temperature drift
  - Typically Low-side only
    - High-side limited to op-amp supply rail
  - Board Space / Component Count


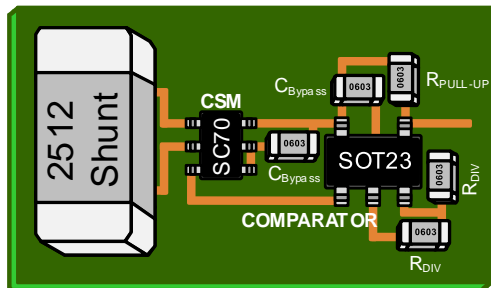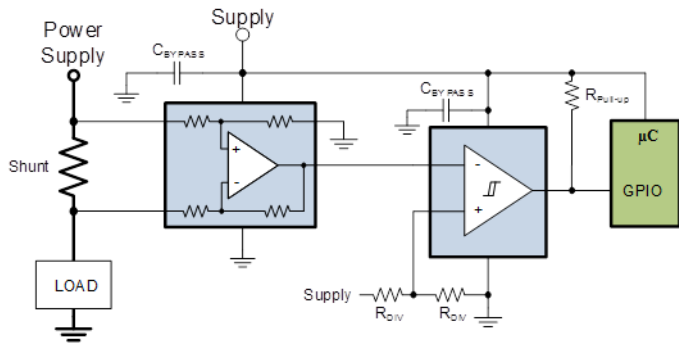
# Current Sense Amplifier & Comparator Implementation




CSM +  
Comparator  
OCP

- Strengths:
  - More accurate current measurement than typical op-amp implementation
    - Smaller shunt enabled by lower  $V_{\text{OFFSET}}$  lowers power consumption
  - Fast response time with fast comparator
  - Offers both overcurrent detection and current monitoring
  - Comparator second source alternatives
- Challenges:
  - For comparator function:
    - ACCURACY costs money!
      - Temperature drift on comparator
    - SPEED costs money!
  - Board Space / Component Count

# Overcurrent Alert Only Implementation

## - INA300 Current-Sense Comparator

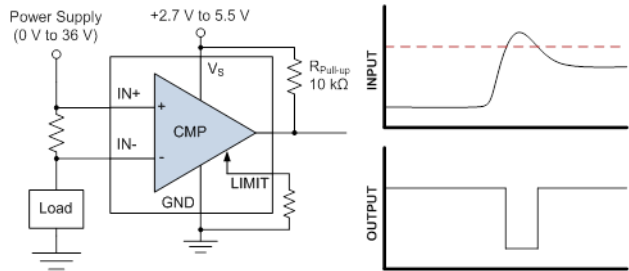


- Strengths:

- Simplest implementation with only a single external threshold setting resistor required and no additional design considerations
- High-side or low-side capable
- 70% smaller footprint versus op-amp and comparator implementation
- Miniaturization of Over-Current Detection enables rethinking system level management via subsystem monitoring
  - Utilization & efficiency: Only use those portions of the system that are needed & are enabled
  - Localized Fault Identification
  - Offload event detection: Operates independently and only wakes system controller when needed

- Challenges:




- ALERT only – no actual current information supplied to system

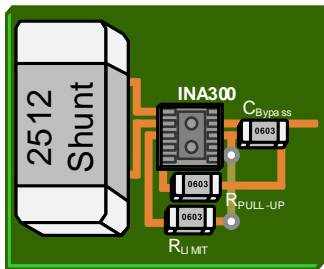

INA300
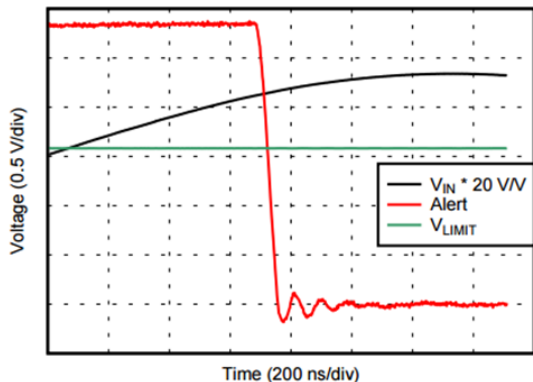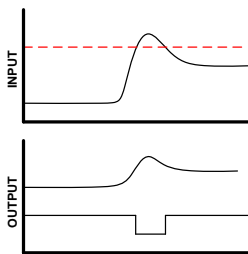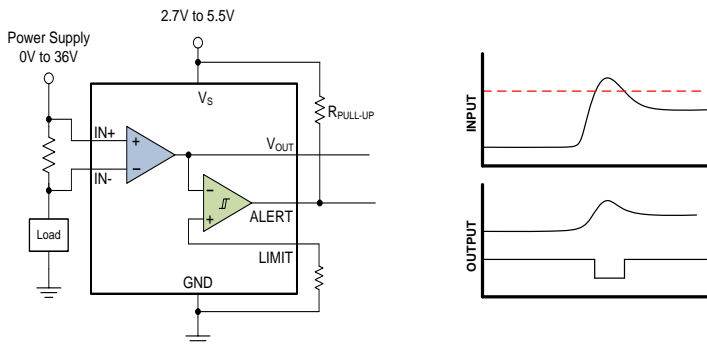
# Overcurrent Alert w/ Analog Output Implementation

- INA301 high-speed, precision current sense amplifier with integrated comparator



**Total Propagation Delay**



## • Strengths:

- Offers both overcurrent detection and current monitoring
- High-side or low-side capable
- Simple implementation with only a single external component required
- Fast response time
  - INA301 @ 1 $\mu$ s (0.6 $\mu$ s Typ)

## • Challenges:

- Design needs to comprehend current range, over-current limit, and following stage input range.
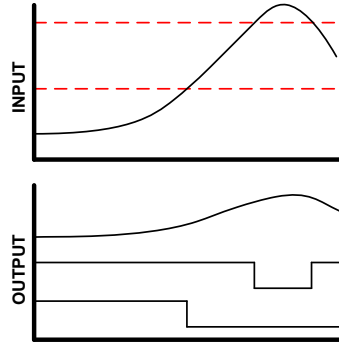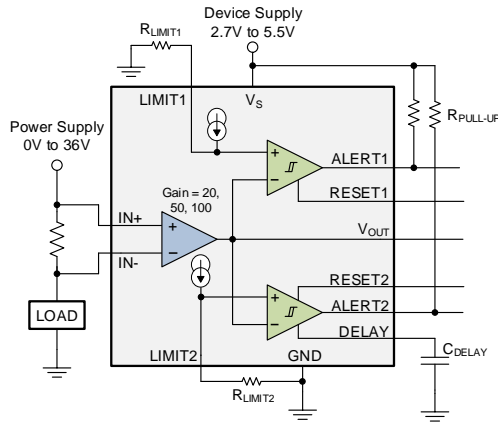
# Multi-Level Overcurrent Alert w/ Analog Output Implementation



## • INA302

- High/Low-Side, Bi-Directional, Zero-Drift Current Sense Amplifier with Multi-Alert High-Speed Comparators
- In development, sample in 3Q2016



## • Strengths:

- Offers both overcurrent detection and current monitoring
- Dual ALERTS - enables system implementation flexibility such as WARNING and SHUTDOWN
- High-side or low-side capable
- Simple implementation with only a single external component required per comparator
- Fast response time
  - INA302 @ 1 $\mu$ s

## • Challenges:

- Design needs to comprehend current range, over-current limit, and following stage input range
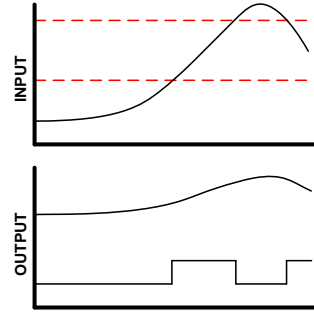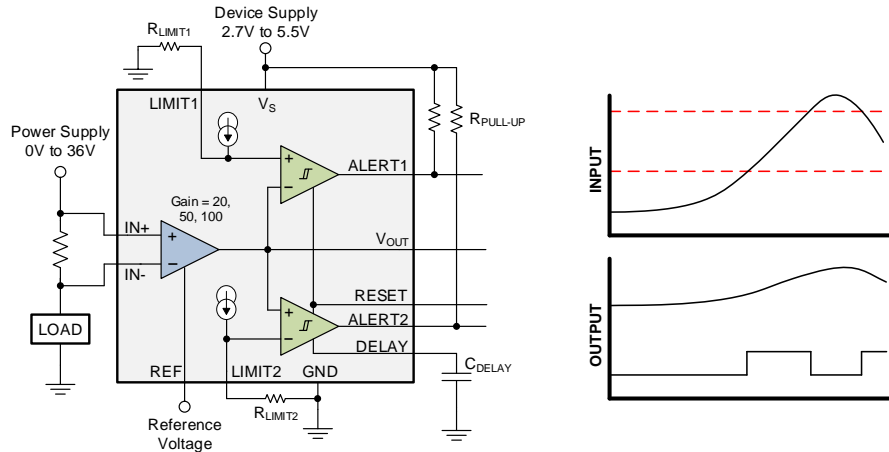
# Windowed Multi-Level Overcurrent Alert w/ Analog Output Implementation



## • INA303

- High/Low-Side, Bi-Directional, Zero-Drift Current Sense Amplifier with High-Speed Window Comparator
- In development, sample in 3Q2016

## • Strengths:



- Offers both overcurrent detection and current monitoring
- Window ALERTS enables bi-directional current measurement or both OVER and UNDER current detection
- Simple implementation with only a single external component required per comparator
- Fast response time
  - INA303 @ 1 $\mu$ s

## • Challenges:



- Design needs to comprehend current range, over-current limit, and following stage input range

# Over-Current Detection Topologies – A summary



## INA300: Overcurrent Alert Only

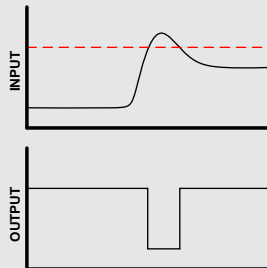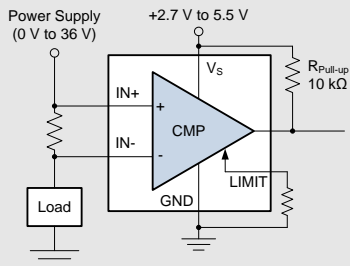

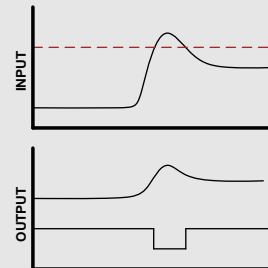
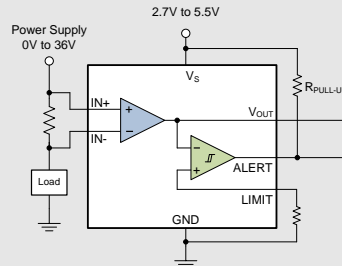
## INA301: Overcurrent Alert w/ Analog Output


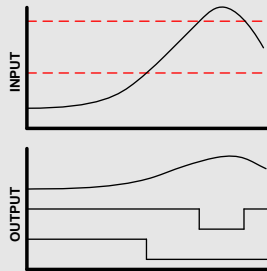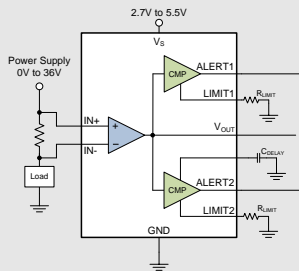
## INA302: Multi-Level Overcurrent Alert w/ Analog Output


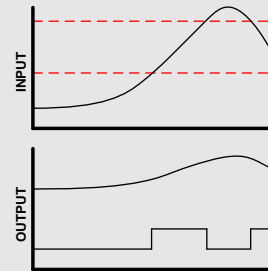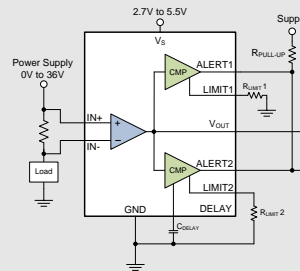
## INA303: Windowed Multi-Level Overcurrent Alert w/ Analog Output



# Over-current Protection Roadmap


## Production or Past PPR

- **INA300 QFN/MSOP - Now**
- **INA301 MSOP – Now**
- **INA301-Q1 – Now**
- INA300-Q1- MSOP – 8/16
- INA302 – sample 9/16
- INA303 – sample 9/16

## Planned for 2017

- INA302-Q1/INA303-Q1
- INA380/INA2380/INA4380
  - INAx180 + comparator/ch – 1,2,4 ch
- INA380/INA2380/INA4380-Q1
- INA311/INA312/INA313
  - INA240 + INA302/3 Comparator – 3 SKUs
- INA311/INA312/INA313-Q1

# Digital Power Monitor Implementation

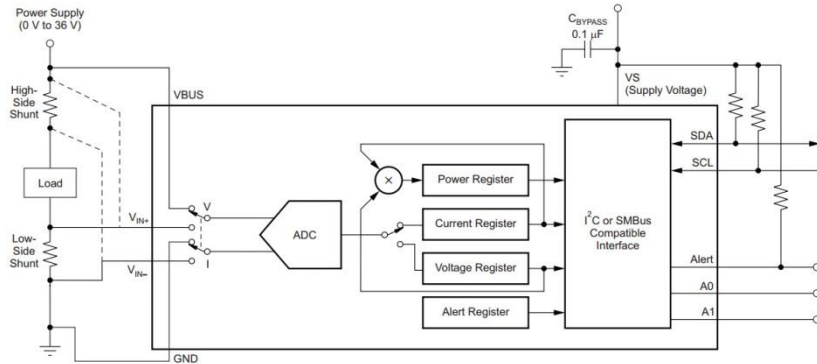

- INA226
- INA231
- INA219
- INA220

- Strengths:
  - Offers both overcurrent detection and current monitoring
    - Additionally, offers bus voltage and power monitoring
  - Flexible, Programmable ALERT settings:
    - Over/Under Current
    - Over/Under Bus Voltage
    - Over Power
  - Low-side or High-side Capable
  - Programmable conversion time
- Challenges:
  - Response time can be slower due to digitization



# Over-current Protection via Power Monitor Roadmap

## Production or Past PPR

- **INA219 MSOP - Now**
- **INA220 MSOP - Now**
- **INA220-Q1 MSOP - Now**
- **INA226 MSOP - Now**
- **INA226-Q1 MSOP - Now**
- **INA230 QFN - Now**
- **INA231 WCSP – Now**
- **LMP92064 xxx - Now**
- **INA3221 QFN - Now**

## Planned for 2017

- INA226 WCSP
- INA230 MSOP
- INA230-Q1 MSOP
- 1.8v INA3221
- INAx<sub>xxx</sub> – HV INA226

# OCP TI Design - Automotive Precision eFuse TI Design #: TIDA-00795

## Features/Benefits

Current limit: up to 30A (scalable to >100A)

Accuracy <3%

Response time: max 15 $\mu$ s (configurable)

Reverse polarity protection

Configurable delay time to accommodate inrush current for 10 $\mu$ s, 50 $\mu$ s & 100 $\mu$ s based on application

Power off resettable fuse

## Target Applications


- Automotive eFuse Box
- Body Control Module
- High-side smart switch
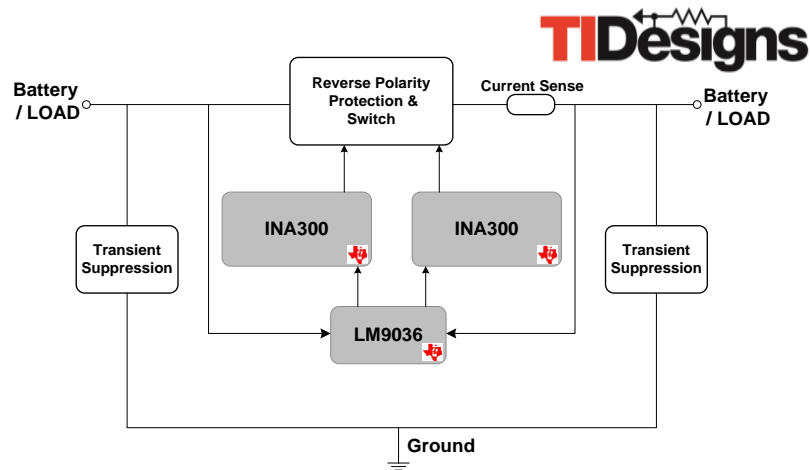
## Tools & Resources



TI Information – Selective Disclosure

- [TIDA-00795](#)
- [Design Guide](#)
- [Design Files](#): Schematics, BOM, Gerbers, and more
- [Devices](#):
  - INA300-Q1
  - LM9036




# Motor Control / Solenoid / Induction loads Current Monitoring

Why, where, and the strengths and challenges of each of the options.

# Motor Current Sensing - Discrete vs. Integrated:



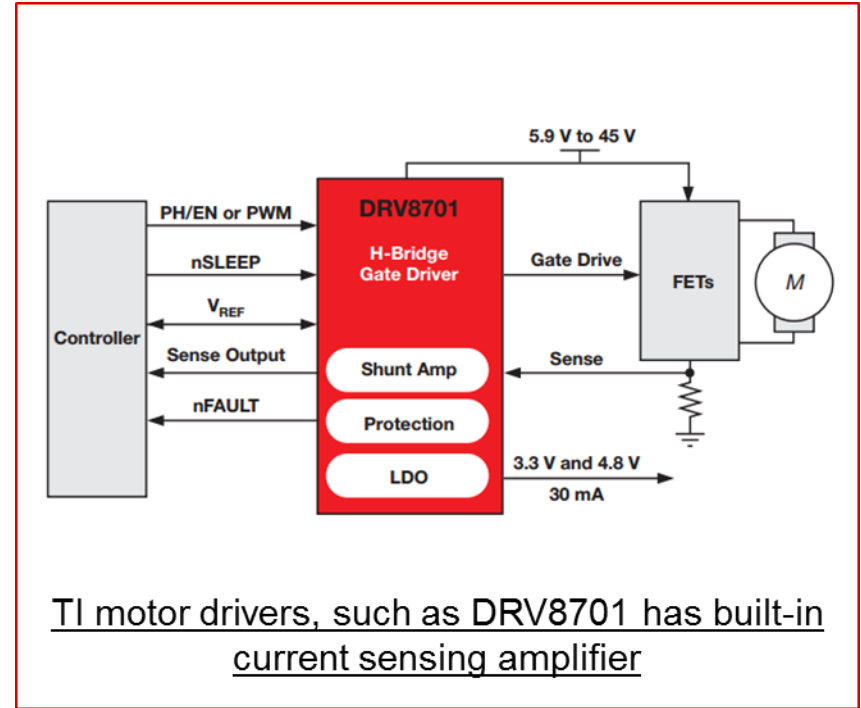
## - Why do I need separate Current sensor(s) anyway?

- Many motor drivers, such as DRV series have built-in current sensors.
- Trade off between cost and performance:
  - Driver integrated current sensor
    - Limited performance
    - No additional cost, great if adequate for the job!
  - Discrete Current Sensor
    - Can be optimized considering topology, performance and cost
    - TI offers a broad portfolio of dedicated Current Sensors, including Current Shunt Monitors (CSM) to address whichever sensing topology you choose!



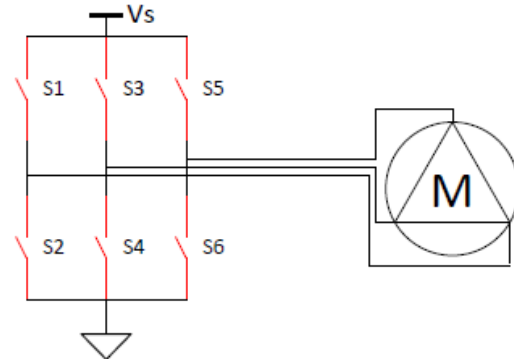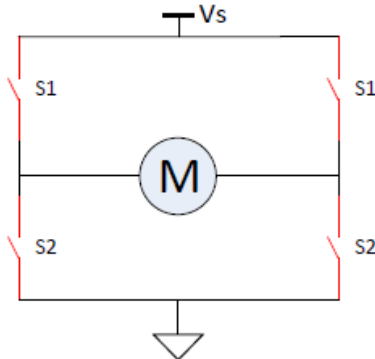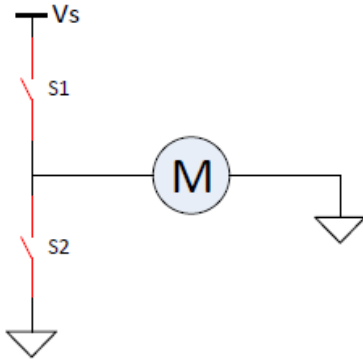
# DC Motor Driver Topologies(with variations)

- Half bridge
  - Brushed DC motor;
  - Three modes: Run, Coasting and Breaking
- H bridge
  - Brushed DC motor
  - Four modes: Run, Reverse, Coasting and Breaking
- 3 Phase
  - BLDC motor – electrically commutated.
  - Four modes: Run, Reverse, Coasting and Breaking


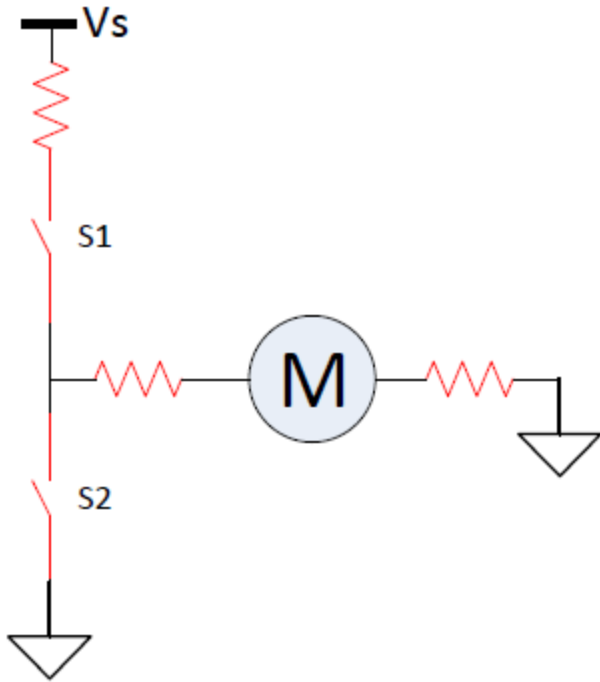
# Half bridge & H-Bridge Motor Control Current Monitoring Options



- Current information is used in:
  - Current is directly related (proportional) to torque
  - Speed/Torque control
  - Safety - guard against short circuit, stalled motor and used to monitor the general health of the motor
- Current sensing techniques in motor control
  - Noninvasive
    - Current transformer:  $\frac{I_1}{I_2} = \frac{N_2}{N_1}$
    - Hall sensor
  - Resistor based current sensing
    - High side
    - Low side
    - In-line

# Resistor based motor current sensing techniques – pros and cons


- Low side

- Advantages

- Low common mode voltage
- Low voltage Amp possible

- Disadvantages

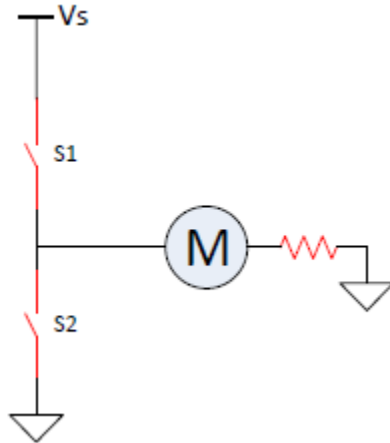- Ground variation
- Unable to detect fault
- Driver current does not necessarily equal to motor phase current




- High side

- Advantages

- Stable Common mode voltage
- Fault detection

- Disadvantages

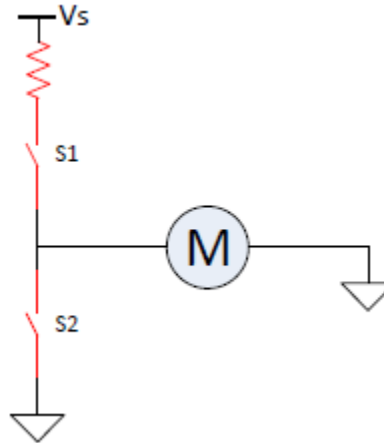- Stable but high  $V_{cm}$
- Driver current does not necessarily equal to motor phase current




- In-line

- Advantages


- True motor phase current

- Disadvantages

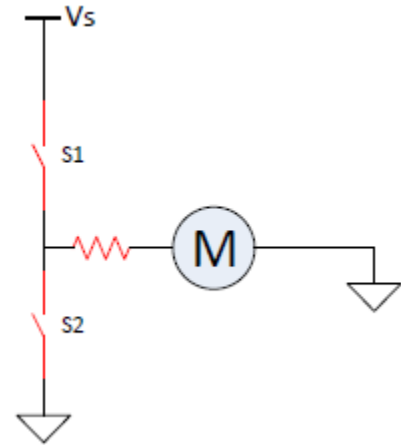- PWM common mode voltage
- Sensing amp must have good DC and AC CMRR


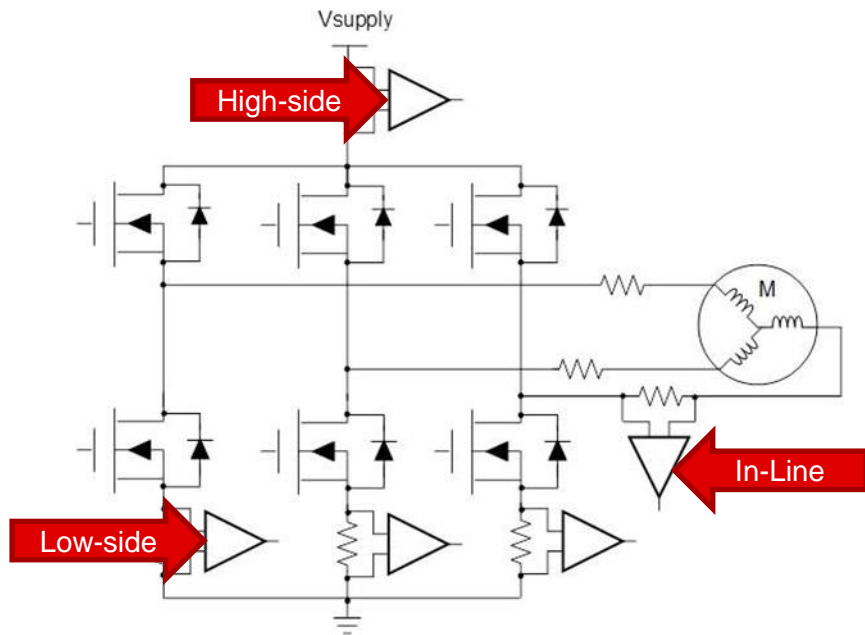
# 3Phase Motor Control Current Monitoring Options





- Three choices
  - Low side (DC link or separate driver leg measurement )
  - High side(including DC link, or separate driver leg measurement )
  - In line
- Why do we measure current in motor control?
  - Torque and speed control (two-loop)
  - Safety
  - Could be used for rotor position sensing in sensorless BLDC, replacing Hall sensors or BEMF sensing


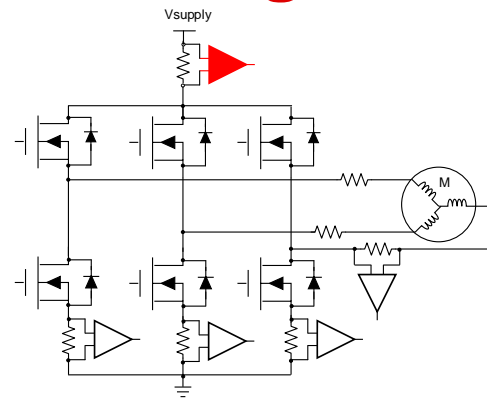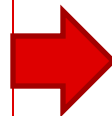
# High-side & Low-side Motor Current Monitoring



- High-side (DC link or bridge)

- Stable  $V_{cm}$  😊
- High voltage  $I_{sense}$  Amp 😞
- Driver current does not always equal to phase current 😞



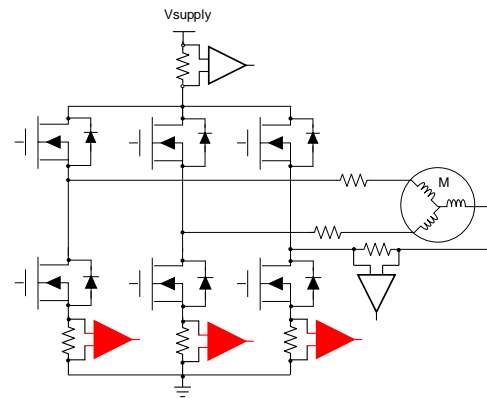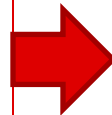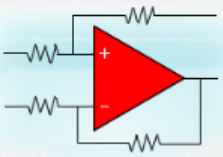

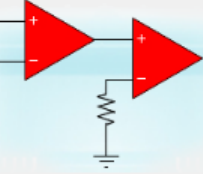
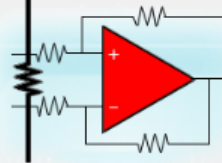
- Low-side (DC link or bridge)

- Low  $V_{cm}$  😊
- Low voltage  $I_{sense}$  Amp 😊
- Driver current does not always equal to phase current 😞
- Ground variation 😞




# Conventional High-side or Low-side sensing: – What Does TI have to offer?

- TI's broad CSM portfolio for sure can offer you one device for either High or Low side current sensing:
- <http://www.ti.com/lscs/ti/amplifiers-linear/current-sense-amplifiers-overview.page>

Analog Output	Digital Output	Comparator Output	Integrated Shunt
			
<p>Integrate the full analog signal processing and provide a voltage or current output</p> <p><a href="#">Explore products &gt;</a></p>	<p>Integrate the full signal conditioning path and utilize a standard 2-wire digital interface</p> <p><a href="#">Explore products &gt;</a></p>	<p>Provides a simple ALERT signal when the load current exceeds a threshold.</p> <p><a href="#">Explore products &gt;</a></p>	<p>Offers a low-drift, precision integrated sense element.</p> <p><a href="#">Explore products &gt;</a></p>
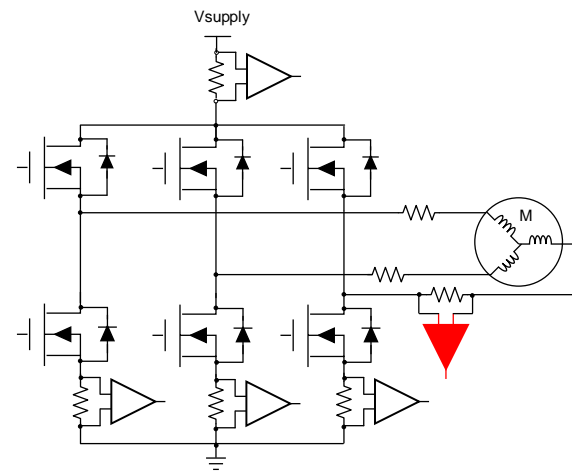
# In-line 3phase Motor Current Monitoring

- True phase current at all times, NO guess work 😊
- PWM Common Mode voltage seen by I<sub>sense</sub> Amp 😞
- High voltage combined with high dV/dT poses steep challenge to I-sense Amp 😞
- Availability of suitable Current Sensors limits the adoption of this topology.



## Signal's Frequency Contents:

- The differential signal (useful information) is relatively narrow-band, and small;
- The CM PWM signal (not useful) is wide-band and BIG.


## An ideal inline sensor:

- Amplifies only differential signal; "blind" to Common Mode signal.


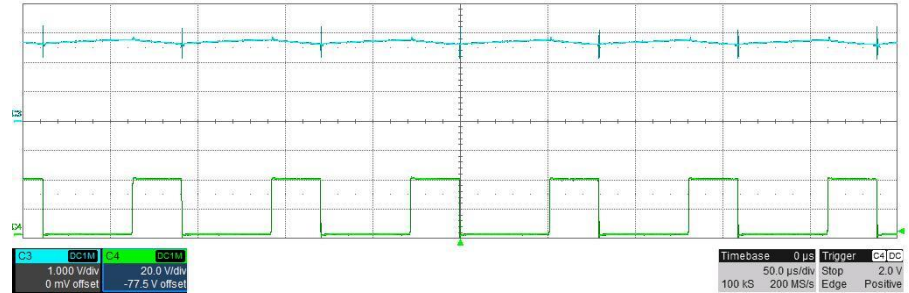
# Why Is Inline Current Measurement Challenging?

– The tale of a competitor... it is not a trivial task!

This is how the phase current should look like



This is how this competitor looks like

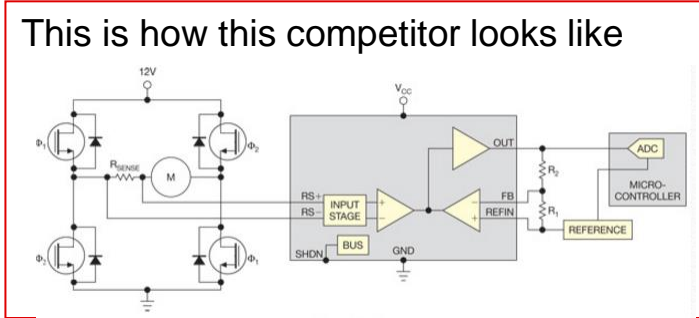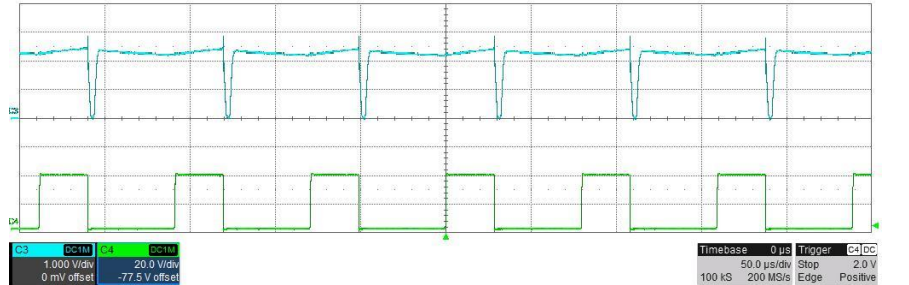

Competitor Paper: <http://www.edn.com/design/analog/4369564/Monitor-PWM-load-current-with-a-high-side-current-sense-amplifier>

TI Information – Selective Disclosure


# How Does INA240 Solve the Problem?

## Novel Architecture:

- Chopper amplifier achieves exceptionally accurate Gain; zero  $V_{os}$ ; zero Drift over temperature.
- In-package E-trim achieves superior resistor matching, resulting in excellent DC CMRR of better than 120dB.
- Minimizing coupling - Chopper amplifier without conventional feedforward path for improved AC CMRR performance, better than 90dB @50KHz
- Fully differential signal path further suppresses CM signal
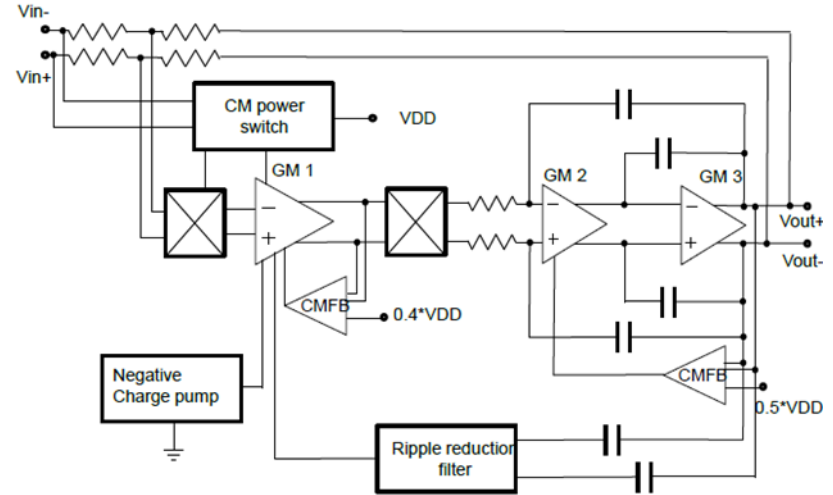
## Small signal bandwidth 150KHz@G100

- Exceptional settling, capable of PWM of 100KHz.
- Most motor drivers work in 20-40KHz range.



INA240 Input Stage

# INA240

## Features/Benefits

- Fast-transient common-mode voltage input filtering
- High AC CMRR: 90 dB @ 50 kHz

Allows for in-line motor and solenoid/actuator current sensing

High Accuracy, High-speed performance


- $V_{OS} = 100 \mu\text{V}$  &  $V_{OS} \text{ Drift} = 0.3 \mu\text{V}/^\circ\text{C}$
- Gain Error = 0.25% & Gain Error Drift = 10 ppm/ $^\circ\text{C}$
- 100 kHz Bandwidth (Gain = 100)

Enables precise current measurement under harsh motor environments

Wide common-mode input voltage range: -4 V to 80 V

Allows for motor supply voltages as high as 48 V and inductive kick-back


## Tools & Resources

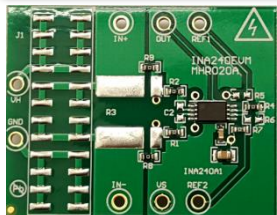

- INA240EVM
- User's Guide
- TINA-SPIICE Model
- INA240 Datasheet
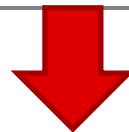
## Target Applications

- Motor control
- Solenoid / Valve Control
- Power Delivery Systems
- Telecomm Equipment
- Pressure Regulator





TI Information – Selective Disclosure

# Performance With Fast Edge, CM Step Input –

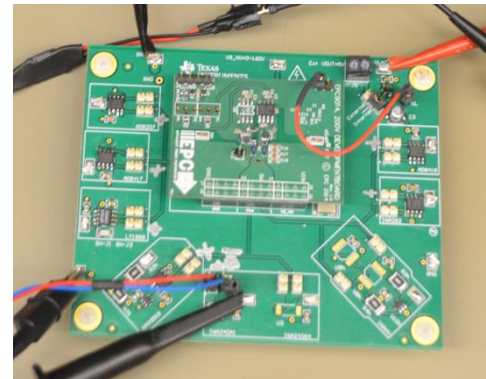
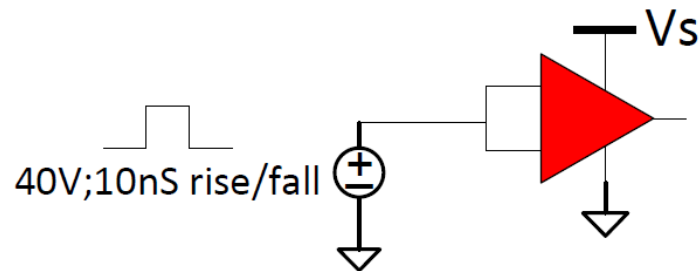
## How does INA240 compare with competition?

- Common Mode input voltage
  - INA240 can survive 100V/10nS
  - Some competitors claim ABS MAX of 65V
  - In our test a step of 50V/10nS often blows the competitor parts up
  - That is why we settled on 40V/10nS step for this study
- INA240 and other competitor devices are tested
- The inputs of the DUT are shorted together
- The same CM input voltage is fed to one device at a time.
- An ideal inline sensor:
  - Should reject CM input completely.
  - The sensor output should show no disturbances at all.


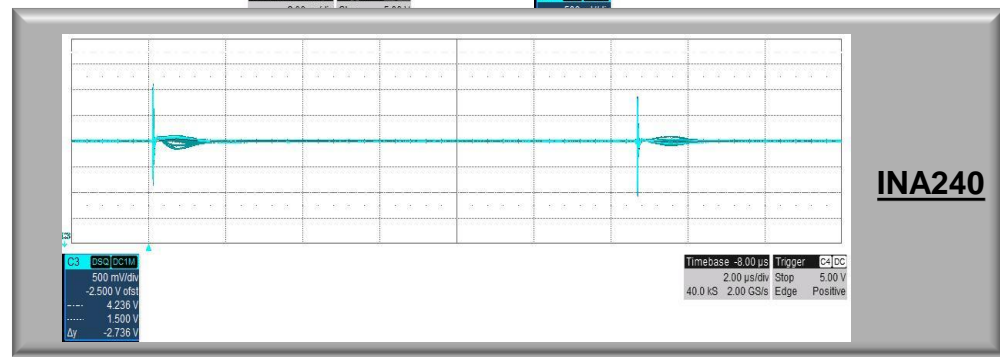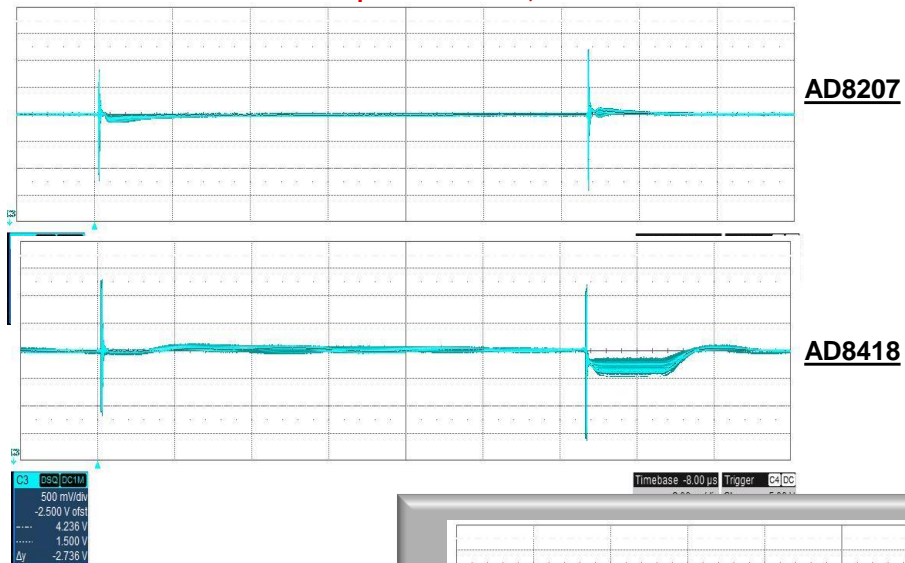
# Common Mode Step Rejection Performance Comparison

- Common Mode Input of 40V; rise time 10nS.







# Performance As Inline Sensor –

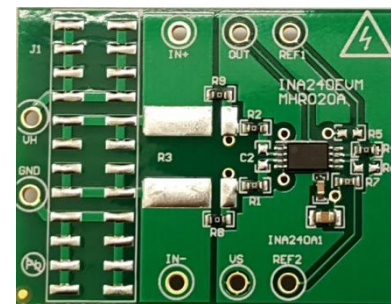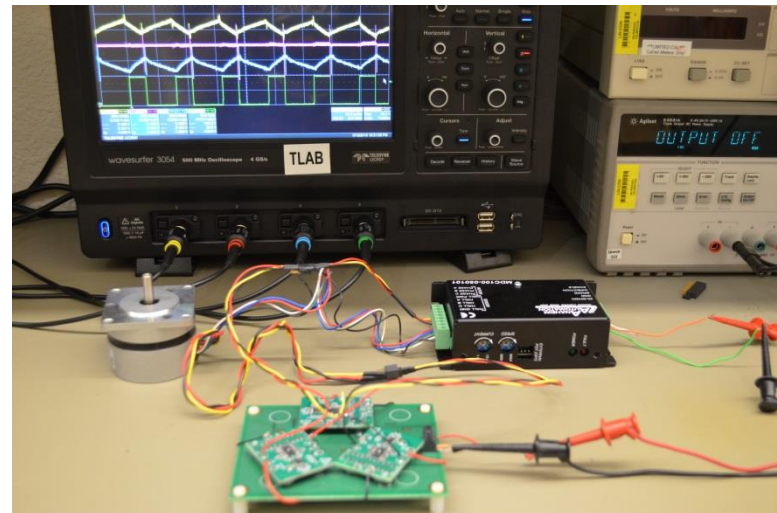
## How does INA240 perform?

- Three (3) INA240, each in one of the 3 phases
- **INA240EVM** is perfect for this task with its versatility
  - sense resistor footprint provided;
  - configurable output reference for bi-directional output;
  - configurable input source and filtering.
- The INA240's are inserted between the motor and controller




# Test Results – INA240 as inline sensor

FULL SPEED

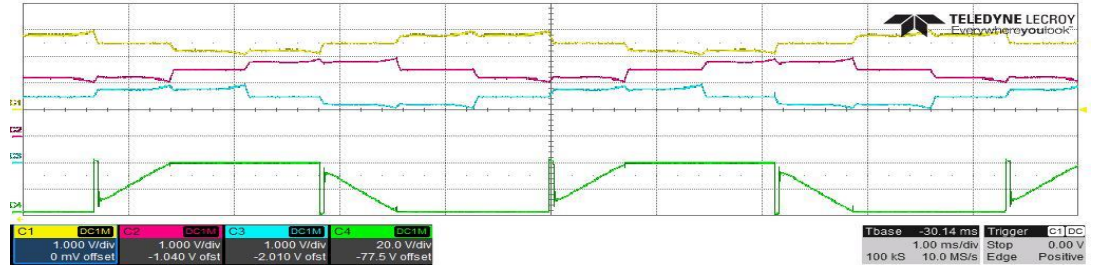


LOW SPEED

(BEMF  $\propto$  Motor Speed)

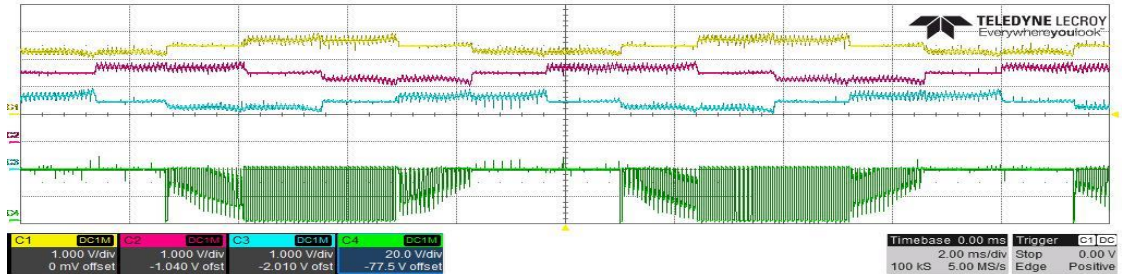


LOW SPEED  
(Zoom in)

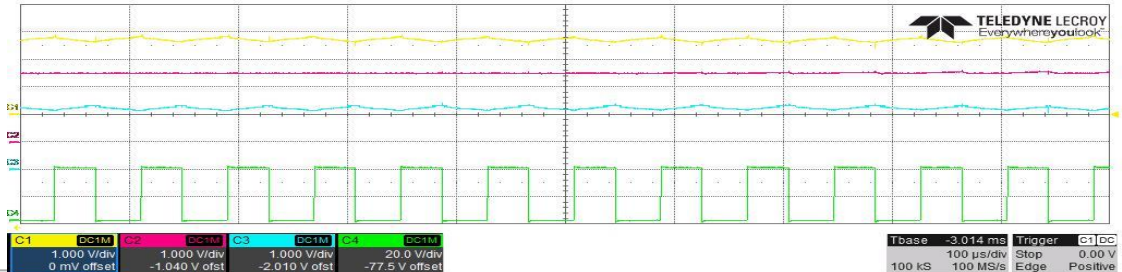




# Performance As Inline Sensor –
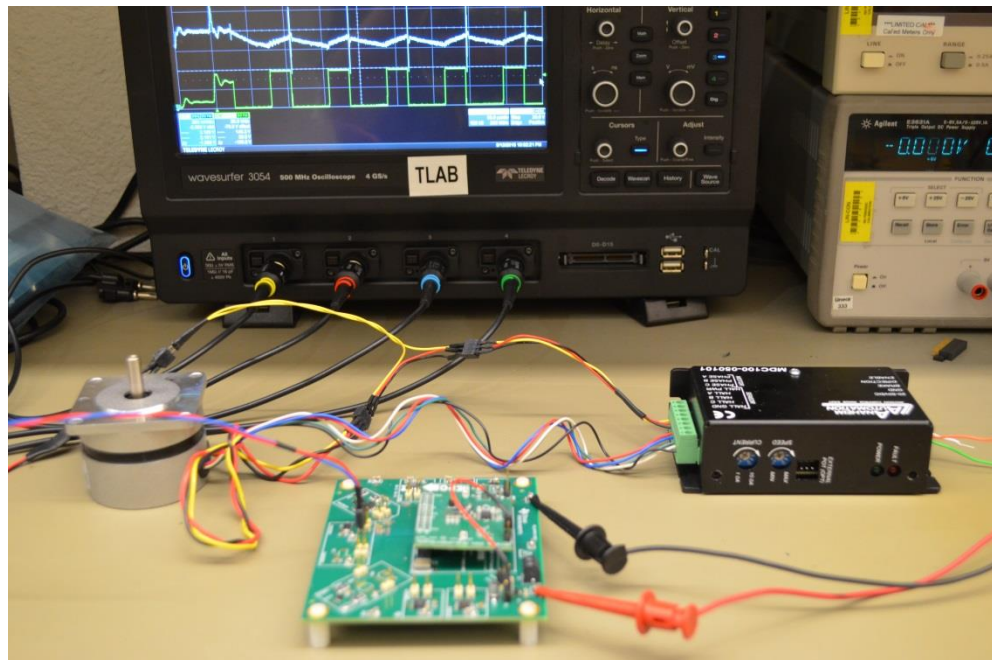
## How does INA240 compare with competition?

- PWM 40V/100nS
- Differential voltage developed across  $R_{sense}$  due to current flow
- The total input voltage is composed of a small differential voltage and a PWM CM voltage
- The same input voltage is fed to INA240 and other competitor parts
- A good inline sensor should:
  - Have excellent AC CMRR - small overshoot at transitions
  - Settles quickly after step transition
  - Other subtle criteria such as DC CMRR, accuracy that are not easy to tell visually



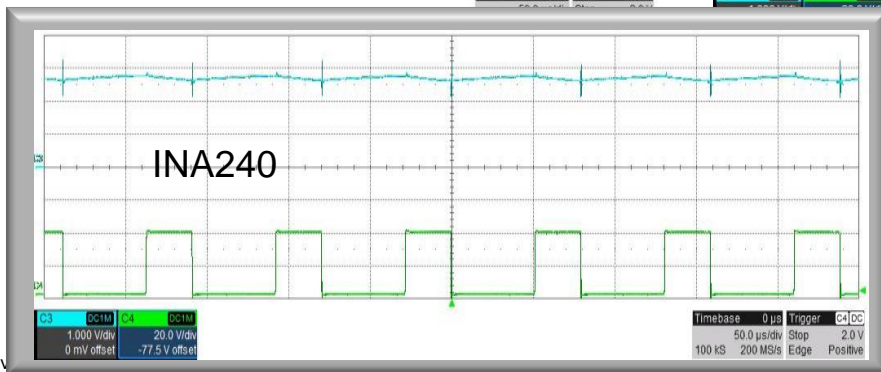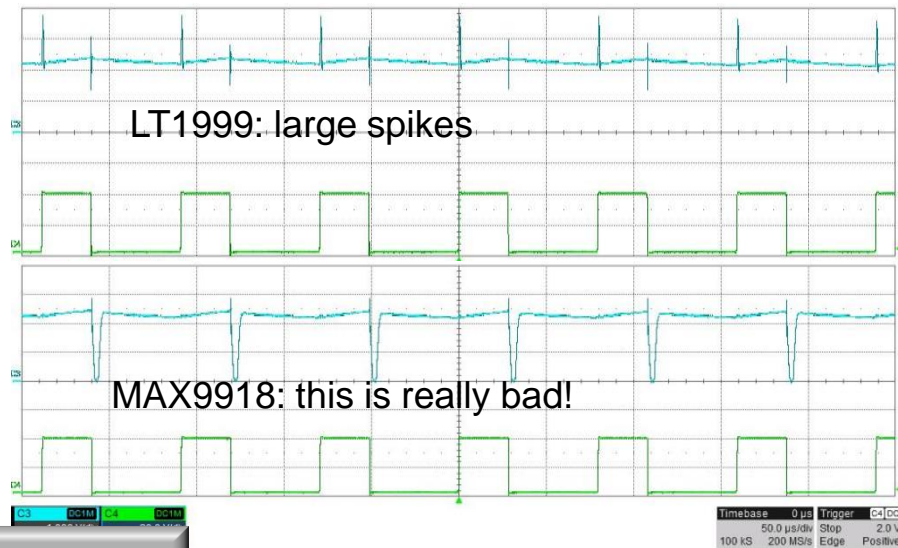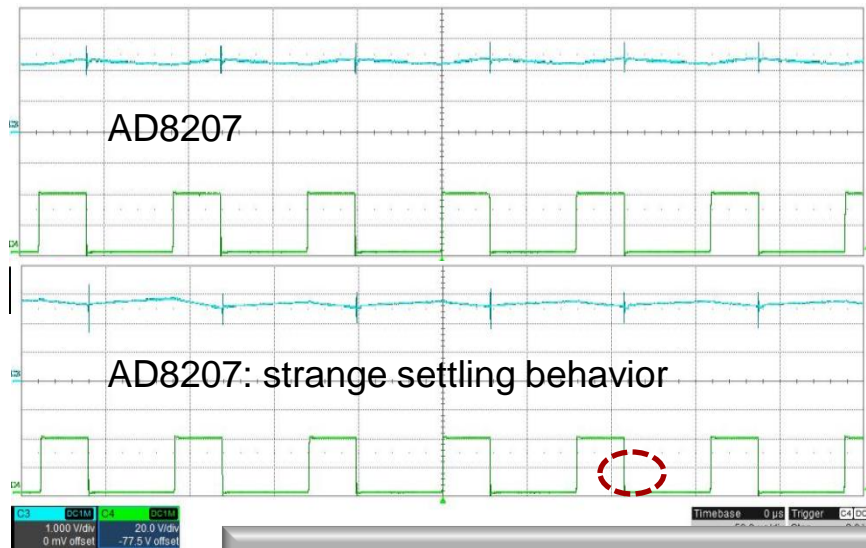Test Results –inline sensor comparative study: Left Column top to bottom: **AD8207** **AD8417(G=60)** **AD8418** **MAX9918**; Right Column top to bottom: **LT1999** **INA282(G=50)** **INA240**. Scale 1V/Div for all.



- Compared with AD8207, **INA240 wins** by:
  - ✓ Settling faster
  - ✓ Higher Abs Max CM voltage 100V (**AD8207 claims 65V**)
  - ✓ Survivability at high dV/dT – 100V/10nS (**AD8207 often blows up with 50V/10nS CM step**)

TI Information – Selectiv

# Summary

**INA240** offers best in class performance for motor inline current sensing:

- Exceptional accuracy
- -4V to 80V specified CM operation
- Unparalleled High dV/dT survivability
- Superior DC and AC common mode rejection
- Fast settling