




Current-Feedback Amplifiers – Part 2

TIPL 2012

TI Precision Labs: High-Speed Operational Amplifiers


Prepared and Presented by Samir Cherian

Slew-rate Limitation of VFB

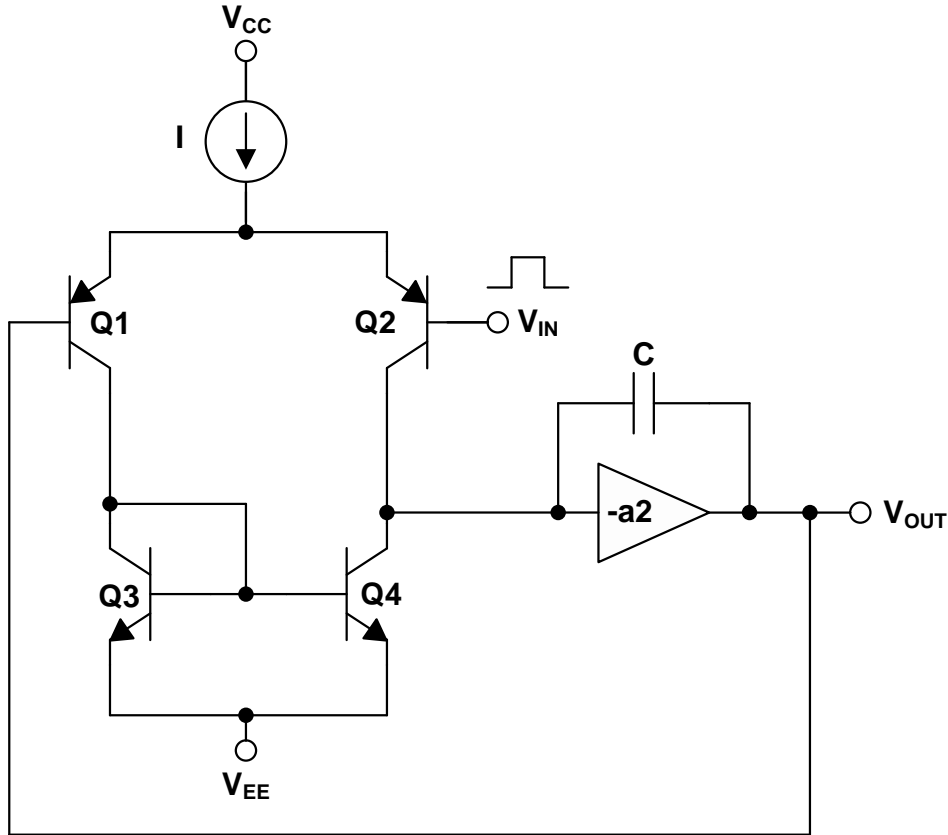

- If $I = 100\mu\text{A}$ and $C = 10\text{pF}$, then,
Slew Rate = $100\mu\text{A}/10\text{pF} = 10\text{V} / \mu\text{s}$

Slew Rate Enhancement with CFB

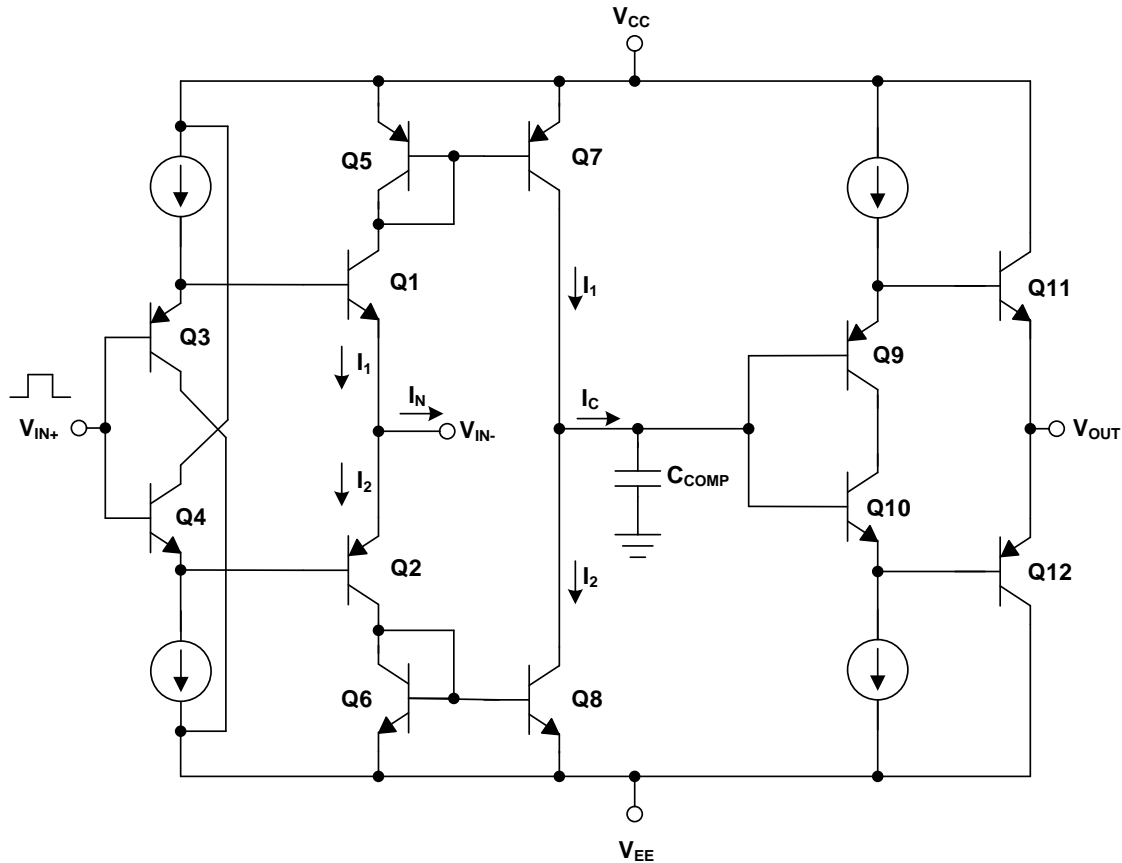


$$I_N = I_1 - I_2$$


$$I_N = I_C$$

Slew Rate VFB vs CFB

VFB

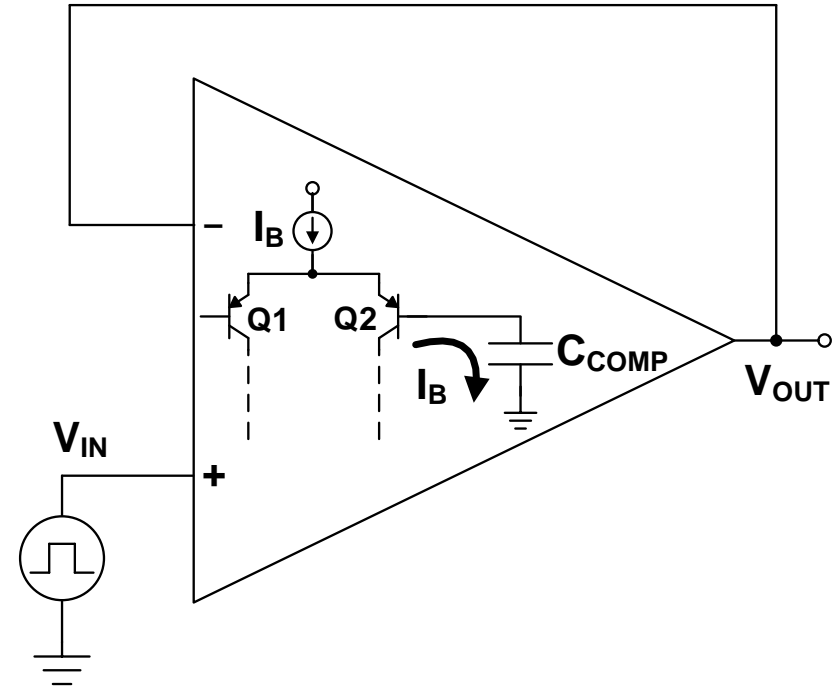

CFB

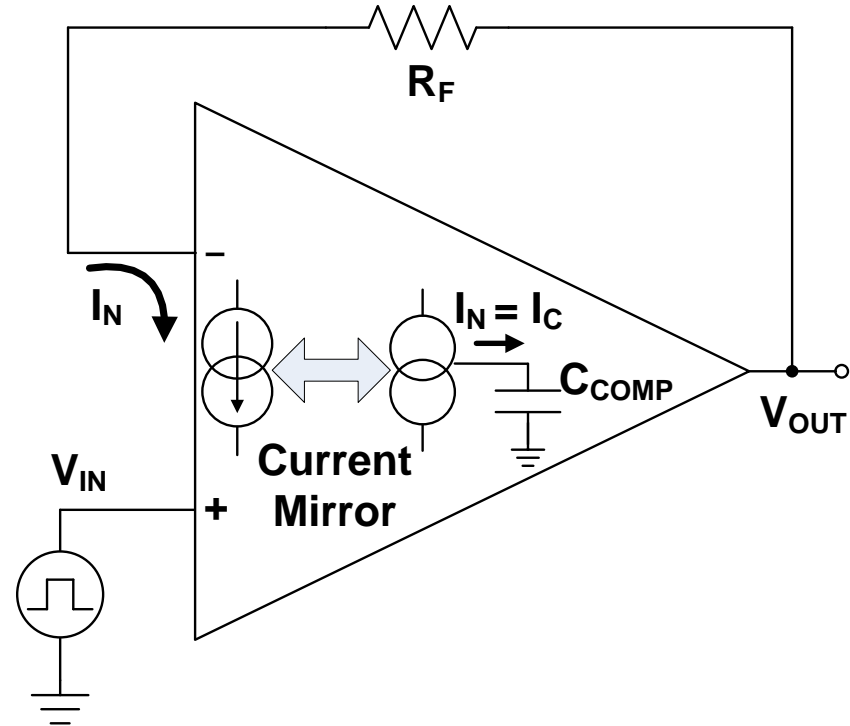

Slew Rate: VFB vs CFB

Current Feedback


Device	Slew Rate (V/ μ s)	I_Q (mA)
OPA683	210	0.79
OPA684	820	1.7
OPA691	2100	5.1
OPA695	4300	12.9
THS3001	6300	6.6
THS3061	7000	8.3
THS3091	7300	9.5

Voltage Feedback

Device	Slew Rate (V/ μ s)	I_Q (mA)
THS4281	35	0.8
LMH6619	57	1.45
OPA820	240	5.6
OPA846	625	12.6
OPA637	100	7
THS4051	240	8.5
THS4631	1000	11.5

Products in bold text are high-voltage op-amps with max. supply >24V


Low-Power CFB Amplifier Designs

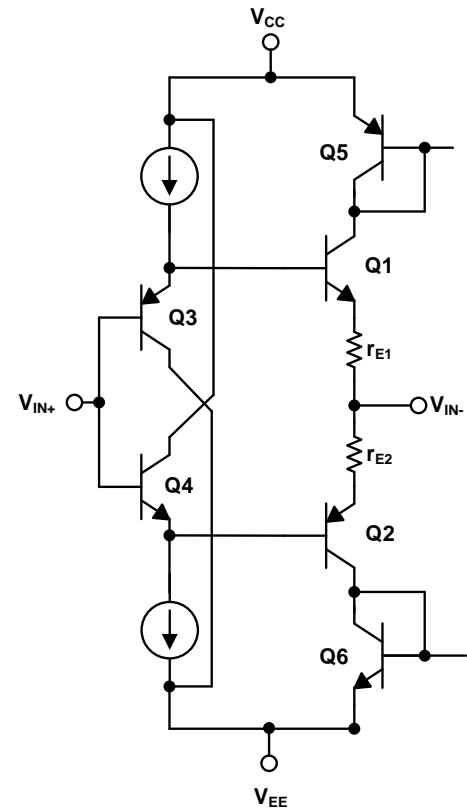

$$r_E = \frac{V_T}{I_E}$$



r_E = Emitter Resistance
 V_T = Thermal Voltage
 I_E = Emitter Current
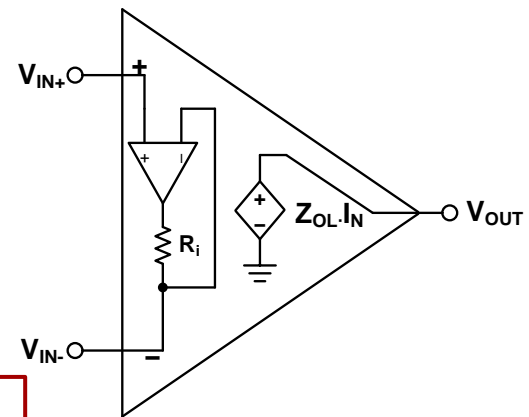
$$\text{Feedback Transimpedance} = (R_F + R_i \times \text{NoiseGain})$$



Specification	OPA691 (Open Loop Buffer)	OPA683 (Closed Loop Buffer)
Quiescent Current, I_Q	5.1 mA	0.82 mA
Inverting Input Resistance, R_i	35 Ω	4.5 Ω

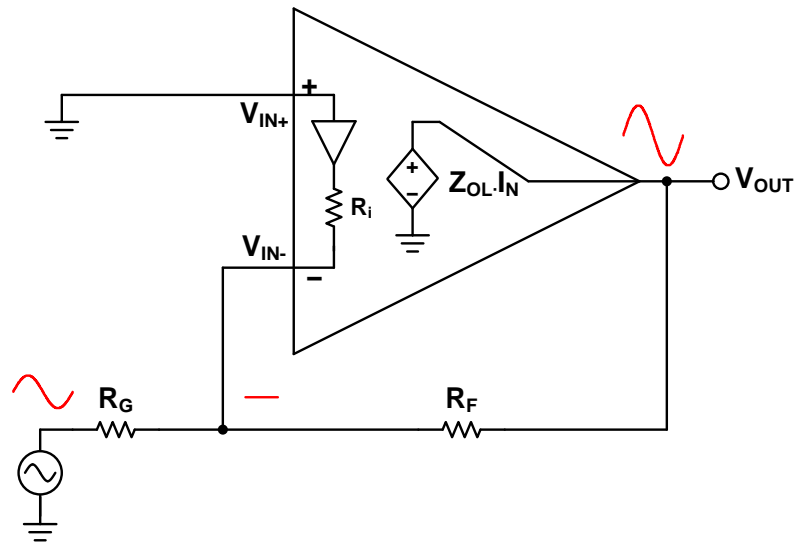
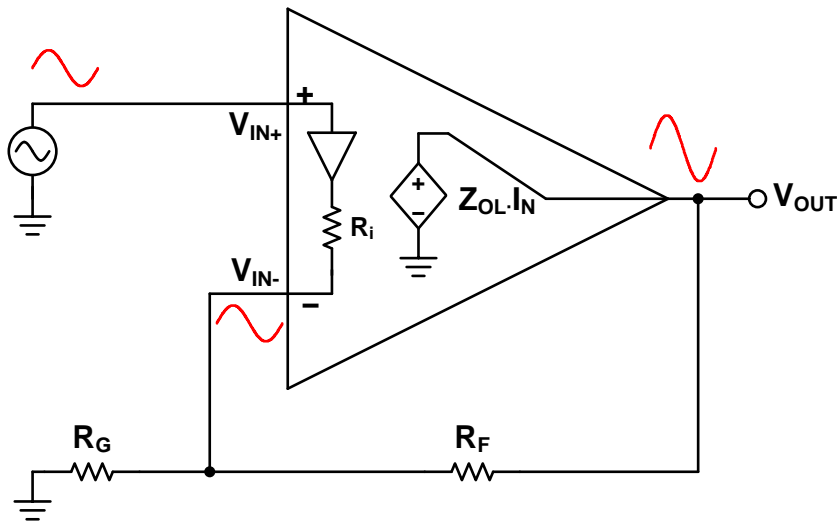
Noninverting versus Inverting Configuration



Slew rate (25% to 75% level)	$G = 2$, $V_O = 10\text{-V step}$, $R_F = 1.21\text{ k}\Omega$	$T_A = 25^\circ\text{C}$	5000	V/ μs
	$G = 5$, $V_O = 20\text{-V step}$, $R_F = 1\text{ k}\Omega$	$T_A = 25^\circ\text{C}$	7300	

$$\text{Slew Rate} = 8V_{\text{PEAK}} \cdot 2\pi \cdot 100\text{MHz} = 5025\text{V} / \mu\text{sec}$$

CFB Noise Analysis

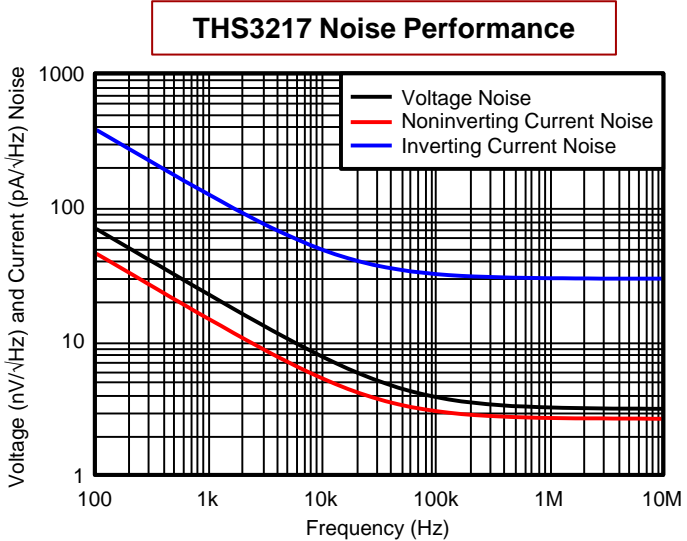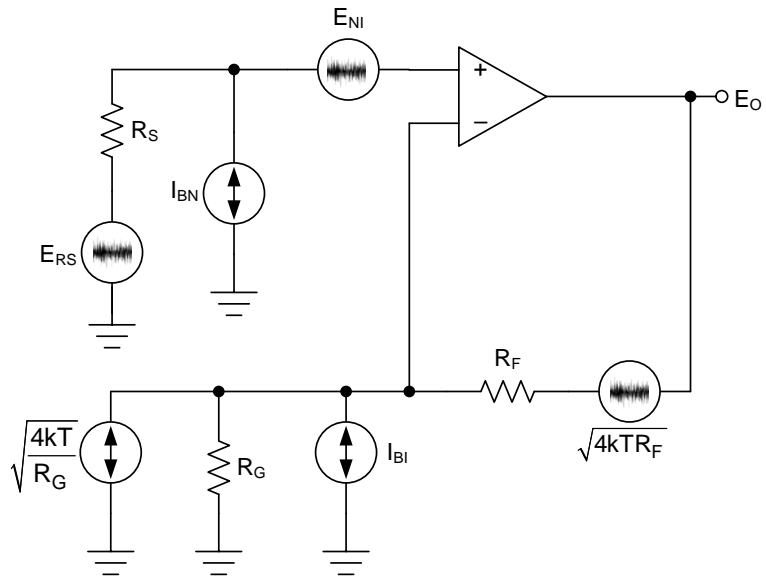

E_{NI} = Amplifier Voltage Noise


i_{BN} = Noninverting Current Noise

i_{BI} = Inverting Current Noise

G_N = Noise Gain = $(1 + R_F/R_G)$

$$E_0 = \sqrt{(E_{NI}^2 + (i_{BN}R_S)^2 + 4kTR_S)G_N^2 + (i_{BI}R_F)^2 + 4kTR_FG_N}$$

Input Bias Current and Current Noise

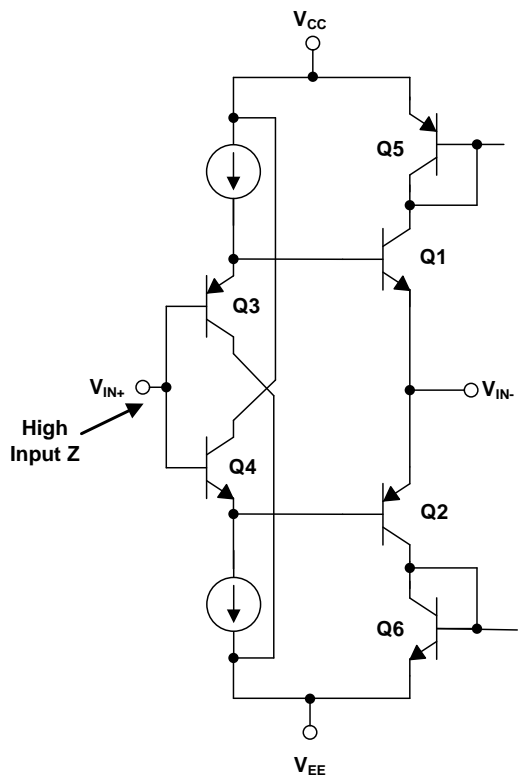

Specification	THS4271 (VFA)	OPA695 (CFA)	Units
I _B , Non-inverting Bias Current	6	±13	μA
I _B , Inverting Bias Current		±20	μA
I _{BOS} , Bias Current Offset	±1	20	μA
Non-inverting Bias Current Noise	3	18	pA/√Hz
Inverting Bias Current Noise		22	pA/√Hz

Summary Comparison

Parameters	VFA	CFA
DC Accuracy	Good	Poor
Output Swing	Many rail-to-rail output options	Larger headroom needed for output
Distortion	Better low-frequency distortion	Better high-frequency distortion
Slew Rate	Limited slew rate	Very high slew rate facilitating high full-power bandwidth
Bandwidth	Bandwidth varies with gain	Almost constant bandwidth over gain
Gain Stability	Restriction on the minimum stable gain for decompensated amplifiers	Stable across gains if feedback transimpedance is kept constant
Noise	Low input-referred voltage and current noise	Higher input-referred current noise (unequal for inverting and non-inverting inputs)
Typical Applications	<ul style="list-style-type: none">- Applications requiring DC precision- Pulse-oriented application- High-speed and precise ADC interface- Transimpedance	<ul style="list-style-type: none">- DAC interface- Output drivers- High-speed ADC interface- Sallen-Key filters.



Thanks for your time and please
take the quiz!

Current Feedback Amplifiers - 2

Exercises

TI Precision Labs: High-Speed Operational Amplifiers

Prepared and Presented by Samir Cherian

Current Feedback Amplifier – Quiz 2


- (1) A CFB amplifier has a small-signal bandwidth of 1 GHz in $G=1$ configuration and a slew-rate of $1000 \text{ V}/\mu\text{s}$. What is its slew rate in $G=2$?
- a) $500 \text{ V}/\mu\text{s}$
 - b) $2000 \text{ V}/\mu\text{s}$
 - c) Insufficient information provided
 - d) $1000 \text{ V}/\mu\text{s}$

(2) An application requires faithful reproduction of a $5V_{PP}$, 100 MHz signal. What is the minimum slew rate of the amplifier that will meet this specifications?

- a) 785 V/ μ s
- b) 1570 V/ μ s
- c) 3140 V/ μ s
- d) None of the above

(3) How would you find a current feedback amplifier in the Texas Instruments product portfolio with slew-rate between 7000V/ μ s and 8000V/ μ s. Search on www.ti.com.

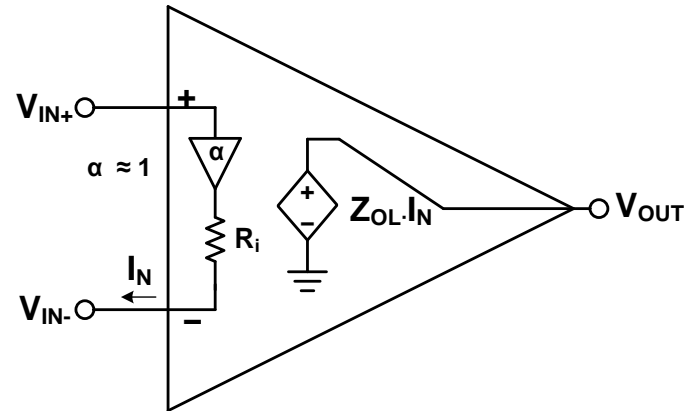- (4) This next problem is a little advanced and requires the use of TINA-TI. Use TINA simulations on the THS3091 at $\pm 15V$ supplies and determine its
- Z_{OL} (Open loop transimpedance) vs frequency
 - Inverting input resistance R_i .
 - Input Buffer Gain, α . (We assumed so far that the buffer gain $\alpha = 1$, however in a real world amplifier $\alpha < 1$)



Answers

(1) A CFB amplifier has a small-signal bandwidth (SSBW) of 1 GHz in $G=1$ configuration and a slew-rate of $1000 \text{ V}/\mu\text{s}$. What is its slew rate in $G=2$?

d) $1000 \text{ V}/\mu\text{s}$

Answer: To the 1st order Slew rate (SR) does not depend on the gain configuration irrespective of the amplifier configuration (CFB or VFB) as long as $\text{SSBW} \gg \text{SR}$. However when the SSBW approaches SR then the overall large-signal response of the amplifier will depend on both SSBW and Slew Rate.

(2) An application requires faithful reproduction of a $5V_{PP}$, 100 MHz signal. What is the minimum slew rate of the amplifier that will meet this specifications?

b) 1570 V/ μ s

Answer: Use the formula, $SR = f_{MAX} \cdot 2\pi \cdot V_{PEAK}$

Where, $f_{MAX} = 100$ MHz and $V_{PEAK} = 1/2 \cdot V_{PP} = 2.5V$, which results in a minimum slew rate of 1570 V/ μ s.

Note that there will be significant distortion at the f_{MAX} frequency. For improved linearity performance select an amplifier with slew rate 2x-3x greater than the calculated slew rate.

(3) How would you find a current feedback amplifier in the Texas Instruments product portfolio with slew-rate between $7000\text{V}/\mu\text{s}$ and $8000\text{V}/\mu\text{s}$. Search on

www.ti.com.

Select "Amplifiers"

The screenshot shows the Texas Instruments website interface. At the top, there is a navigation bar with the TI logo, the text "TEXAS INSTRUMENTS", a search bar, and links for "Login / Register". Below this is a secondary navigation bar with categories: "Products", "Applications & designs", "Tools & software", "Support & training", "Sample & buy", and "About TI". A main banner features a "Data concentrator reference design for smaller AMI networks reduces infrastructure cost" with an image of a circuit board and a list of features. Below the banner is a horizontal menu with "Products" highlighted. A dropdown menu is open under "Products", with "Amplifiers" circled in green. To the right, a "WEBENCH® Designer" tool is visible, showing power supply requirements: V_{in} (14.0 to 22.0 V), V_{out} (3.3 V), I_{out} (2.0 A), and Ambient Temp (30 °C). The URL at the bottom left is www.ti.com/lids/ti/amplifiers/amplifiers-overview.page.

Amplifier ICs | Overview | X

www.ti.com/lscs/ti/amplifiers/amplifiers-overview.page

TEXAS INSTRUMENTS

Everything Search

Login / Register

Products Applications & designs Tools & software Support & training Sample & buy About TI

History Cart English myTI

TI Home > Amplifiers

Amplifiers

Product Tree

- Operational Amplifiers (Op Amps) (1437)
- Precision Op Amps (821)
- High-Speed Op Amps (≥ 50 MHz) (319)**
- General-Purpose Op Amps (300)
- Ultra-Low-Power Op Amps ($\leq 250 \mu\text{A}$) (269)
- Audio Op Amps (58)
- Fully Differential Amplifiers (58)
- Power Op Amps (68)
- Comparators (177)
- Instrumentation Amplifiers (44)
- Current Sense Amplifiers (67)
 - Current Sense Amplifiers Analog Output (47)
 - Current Sense Amplifiers with

Overview Cross reference

Amplify your system

Amplifiers for any need: From ultra-high performance to cost-optimized and everything in between

Operational amplifiers (op amps) Large portfolio spanning high speed, precision, audio and general purpose Learn more >	Comparators Diverse offering with wide supply ranges, low supply currents and fast rise/fall times Learn more >	Instrumentation amplifiers High gain accuracy, DC precision and great CMRR for a wide range of applications Learn more >
Current sense amplifiers	Programmable and variable gain amplifiers (PGA/VGA)	Special function amplifiers

www.ti.com/lscs/ti/amplifiers/op-amps/high-speed-op-amps-overview.page

Select "High-Speed Op Amps (≥ 50 MHz)"

High-Speed Op Amps | [www.ti.com/lstds/ti/amplifiers/op-amps/high-speed-op-amps-overview.page](#) [Login / Register](#)

TEXAS INSTRUMENTS Everything ▾ Search

Products Applications & designs Tools & software Support & training Sample & buy About TI History Cart English myTI

TI Home > Amplifiers > Operational Amplifiers (Op Amps) > High-Speed Op Amps (>=50MHz)

Amplifiers


Product Tree

- Operational Amplifiers (Op Amps) (1437)
 - Precision Op Amps (821)
 - High-Speed Op Amps (>=50MHz) (319)**
 - General-Purpose Op Amps (300)
 - Ultra-Low-Power Op Amps (<=250uA) (269)
 - Audio Op Amps (58)
 - Fully Differential Amplifiers (58)
 - Power Op Amps (68)
- Comparators (177)
- Instrumentation Amplifiers (44)
- Current Sense Amplifiers (67)
 - Current Sense Amplifiers Analog Output (47)
 - Current Sense Amplifiers with Comparator (12)

Overview **Products** Applications [E2E software](#) [Technical documents](#) [Support & training](#) [Cross reference](#)

High-speed op amps to accelerate your design

Industry's broadest and highest-performance portfolio to meet all of your system need




Find products

Combining high-performance with easy product selection

Find products by:

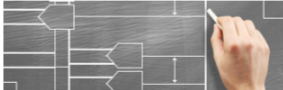- Voltage FB
- JFET/CMOS
- Current FB
- Rail-to-rail
- Fully
- DSL line driver




Learn & design

Explore TI's high speed amplifier technical content

Featured technical documents:

- Designing for low distortion with high-speed op amps
- Noise analysis for high speed op amps



Get support

Search TI's E2E™ Community to find answers

Featured forum posts:

- Front end transimpedance amplifier for low capacitance APD
- Stability of differential opamp with gain

Select "Products" tab

High-Speed Op Amps | [www.ti.com/lscs/ti/amplifiers/op-amps/high-speed-op-amps-products.page#p89=Current FB](#)

Products Applications & designs Tools & software Support & training Sample & buy About TI History Cart English myTI

TI Home > Amplifiers > Operational Amplifiers (Op Amps) > High-Speed Op Amps (>=50MHz)

Amplifiers

Overview **Products** Applications Tools & software Technical documents Support & training Cross reference

Products for High-Speed Op Amps (>=50MHz)

Hide filters

Reset 83 matching parts out of 319 total parts

Architecture

CMOS

Current FB

DSL Line Driver

FET

Fully Differential

Variable Gain (Ana)

Variable Gain (Dig)

83 total parts

Number of Channels (#)

≥ 1 ≤ 4

83 total parts

Part Number	Architecture	Number of Channels (#)	Total Supply Voltage (Min) (+5V=5, +/-5V=10)	Total Supply Voltage (Max) (+5V=5, +/-5V=10)	BW Acl (MHz)	Acl, min spec gain (V/V)	Slew Rate (Typ) (V/us)	Vn at Flatband (Typ) (nV/rtHz)	Iq per Channel (Typ) (mA)	Vos (Offset Voltage @ 25°C) (Max) (mV)	Rail-to-Rail	Additional Features	Rating	Operating Temperature Range (C)	Package Group
BUF602 - High Speed, Closed Loop Buffer	Current FB	1	2.8	12.6	1000	1	8000	4.8		30	No	N/A	Catalog	-45 to 85	SOIC, SC23
THS3091 - Single-High-Voltage, Low Distortion, Current-Feedback Operational Amplifier	Bipolar, Current FB	1	10	30	235	1	7300	2	9.5	3	No	N/A	Catalog	-40 to 85	SO PowerPA, SOIC
THS3095 - Single-High-Voltage, Low Distortion, Current-Feedback Operational Amplifier with Power-down	Bipolar, Current FB	1	10	30	235	1	7300	2	9.5	3	No	Shutdown	Catalog	-40 to 85	SO PowerPA, SOIC
THS3062 - High-Voltage, High Slew-Rate Current Feedback Amplifier	Bipolar, Current FB	2	10	30	300	1	7000	2.6	8.3	3.5	No	N/A	Catalog	-40 to 85	MSOP- PowerPA, SO PowerPA, SOIC

1


Select "Current FB" under Architecture to limit product search to only Current Feedback Amplifiers

2



Double click on "Slew Rate" to sort the amplifiers in ascending or descending order of slew rate

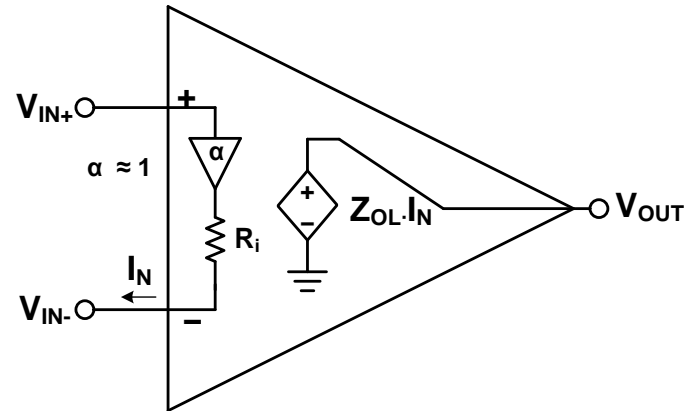- (4) This next problem is a little advanced and requires the use of TINA-TI. Use TINA simulations on the THS3091 at $\pm 15V$ supplies and determine its
- Z_{OL} (Open loop transimpedance) vs frequency..
 - Inverting input resistance R_i .
 - Input Buffer Gain, α . (We assumed so far that the buffer gain $\alpha = 1$, however in a real world amplifier $\alpha < 1$)



The TINA circuits and results are shown in the subsequent slides.



Z_{OL} - Since we are measuring open-loop transimpedance (Z_{OL}), we use a current source stimulus (IG1) and measure the output voltage (V_{out}), $Z_{OL} = V_{out}/IG1$. The 1kF input capacitor and 1kH feedback inductor represent the traditional circuit used to break the amplifier loop. The 1G Ω resistor is needed to provide a current path for the source @ Dc. An AC response simulation directly results in the amplifier Z_{OL} .

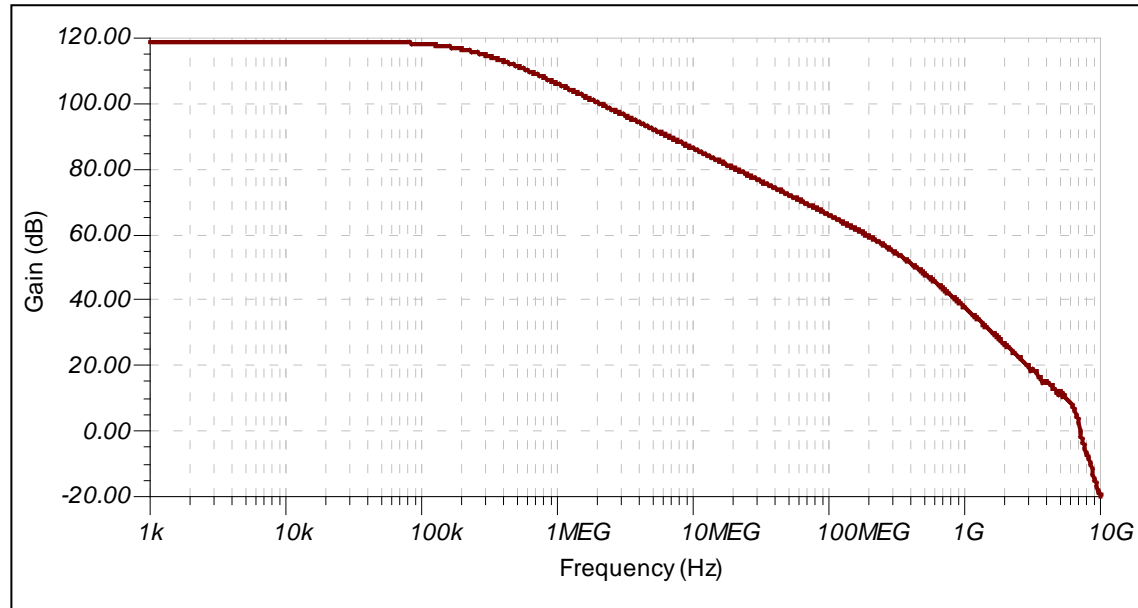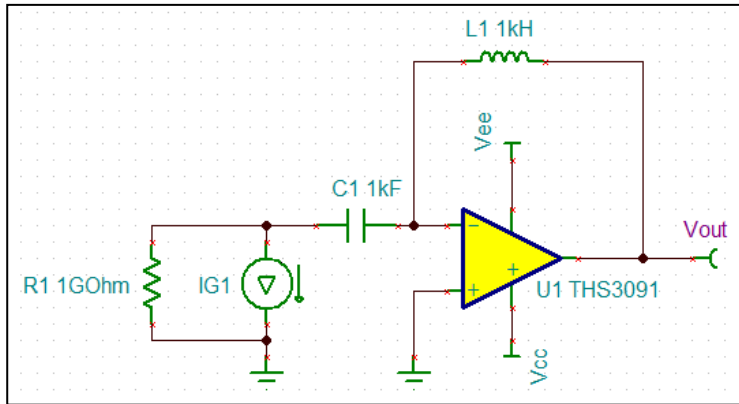

R_i - When measuring R_i we will continue to use the open loop configuration as before, however the output signal is now measured at the inverting input (Z_{IN}). Since the noninverting input is grounded the signal at the inverting input is $I_{IN} \cdot R_i$. The output does not depend on the buffer gain since the noninverting pin is at GND. An AC response simulation directly gives R_i . The output of 32.87dB corresponds to $R_i = 44\Omega$

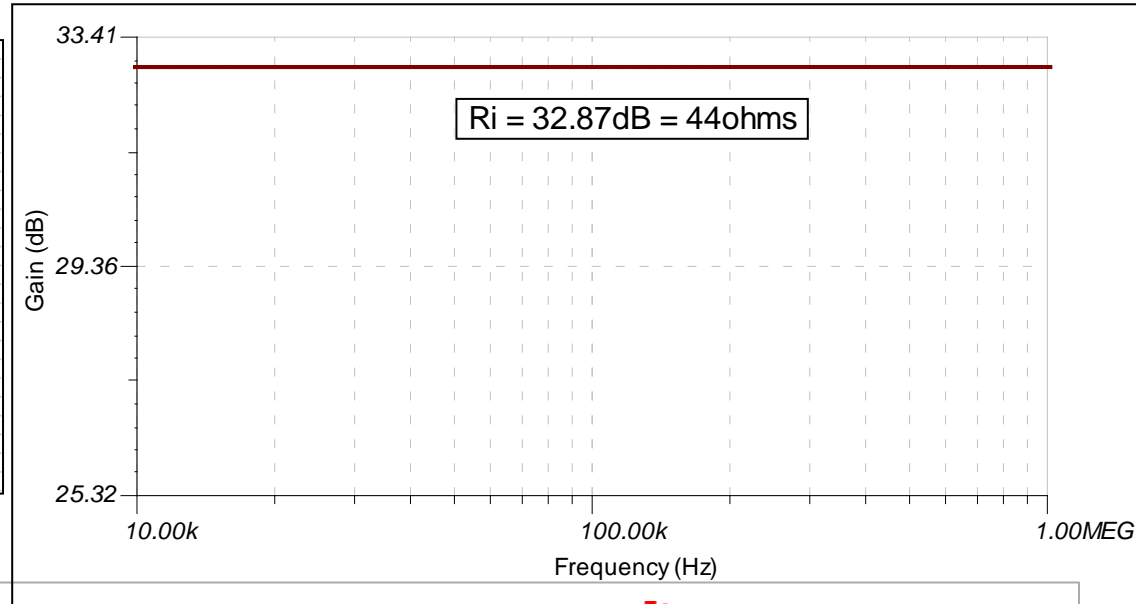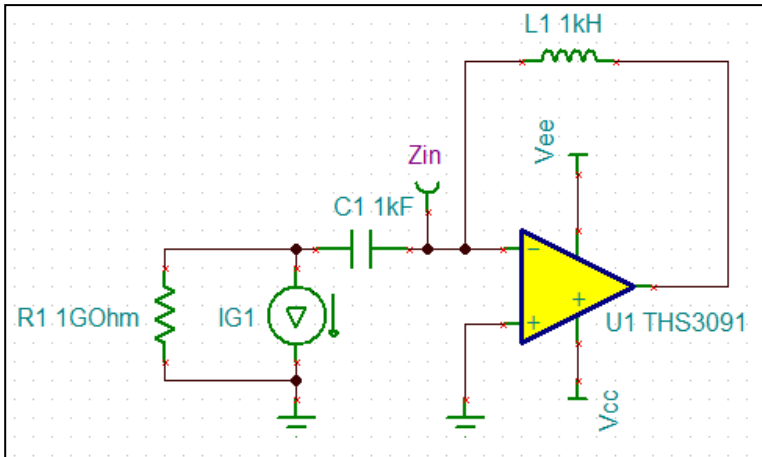


α - So far we have assumed $\alpha=1$, however practically α is slightly less than 1 and is usually an error source in a CFB op amp. In the previous tests the noninverting input was grounded in order to eliminate the effects of α . Here the input signal (VG1) is applied directly to the noninverting input.

The test circuit and the math is shown below. The value of R_i is known from the previous test. The SPICE circuit and results are shown on the next slide



$$\frac{\alpha \cdot V_{IN} - V_{TEST}}{R_i} = I_N$$
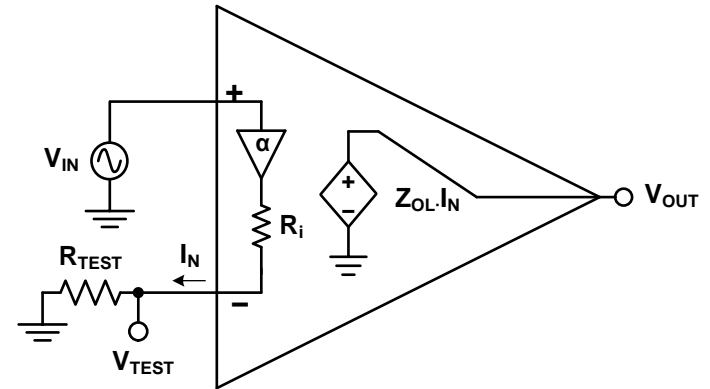
$$\Rightarrow \alpha = \frac{I_N}{V_{IN}} \cdot R_i + \frac{V_{TEST}}{V_{IN}}$$





An AC simulation on the circuit shown below will directly give I_N/V_{IN} and V_{TEST}/V_{IN} which can help α using the equations on the previous slide. $R_i = 44 \Omega$ from the earlier test. R_{TEST} can be chosen to be any value. It provides a signal path to GND for the error current I_N . The 1GH inductor puts the THS3091 in open-loop configuration.
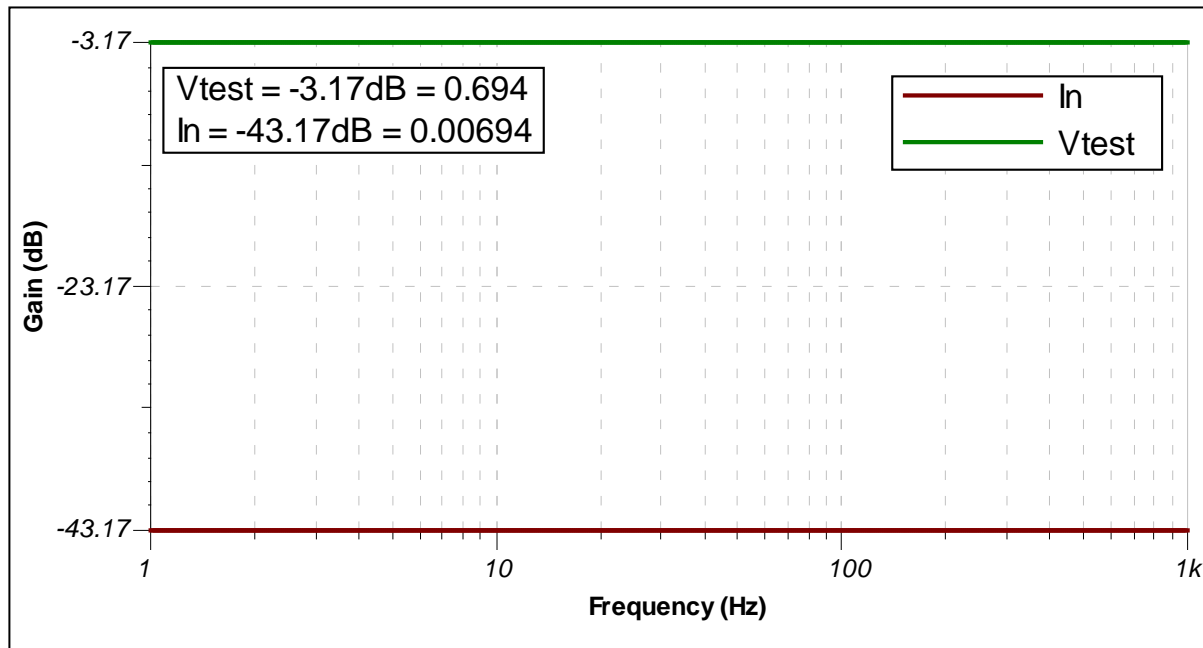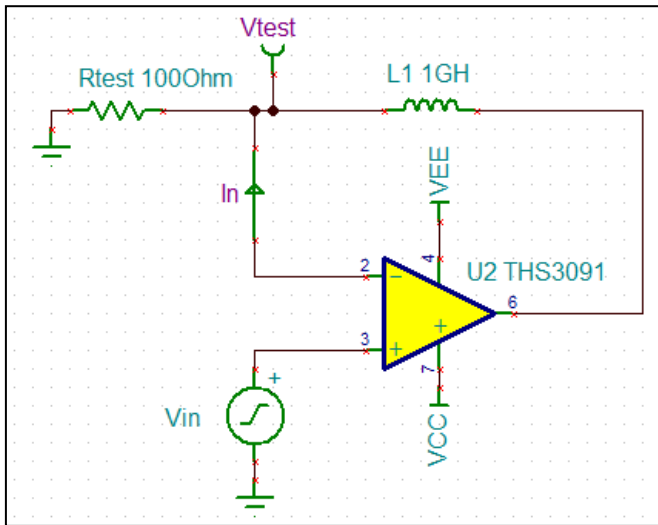
$$\alpha = 0.00694 \cdot 44 + 0.694 = 0.999$$





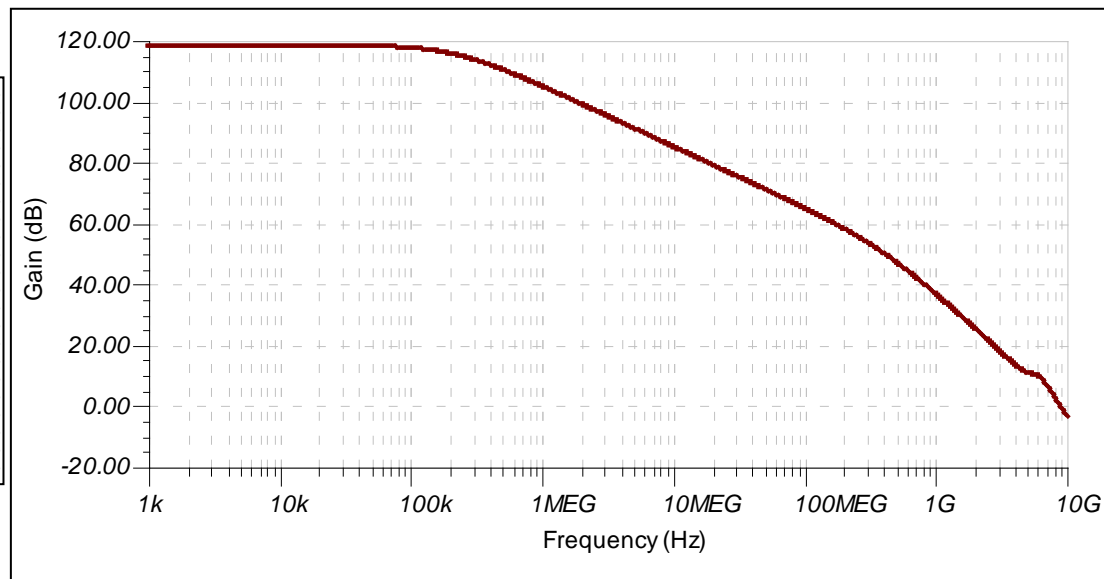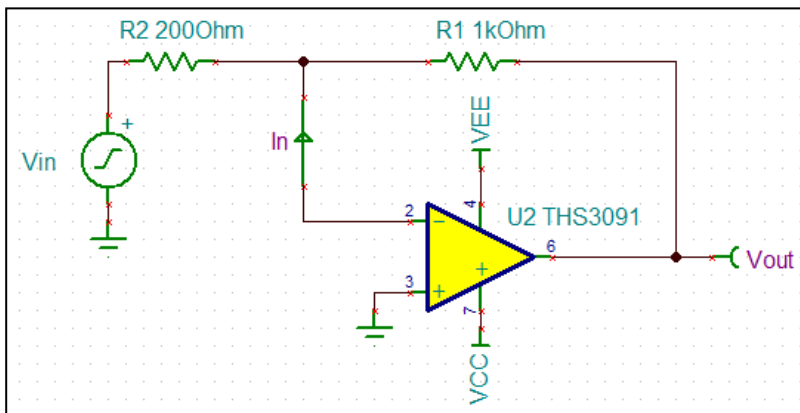So far we used the open-loop configuration to measure the parameters, however a closed-loop config. may also be used. The Z_{OL} closed loop test is shown below. Use the test circuit shown below and use the post-processor feature where $Z_{OL} = V_{OUT}/I_N$. Note that in a closed-loop system the amplifiers closed-loop output impedance will affect the results at the higher frequencies.



The circuit to measure R_i and the simulated results are shown below. I have focused on the low frequency region. Again the post processor feature in TINA is used where $R_i = Z_{IN}/I_N$.
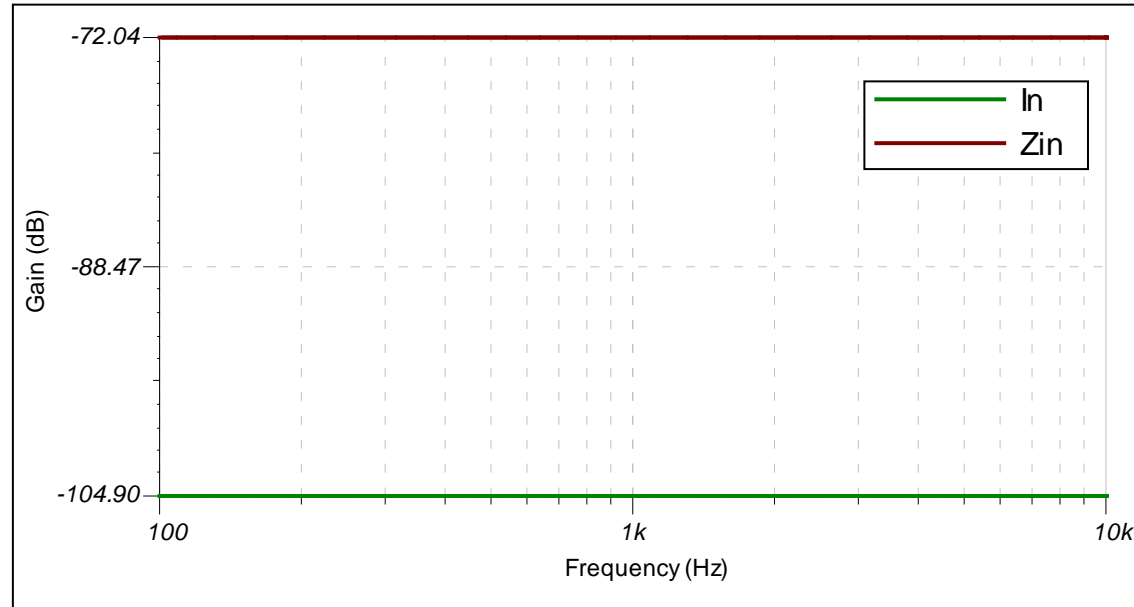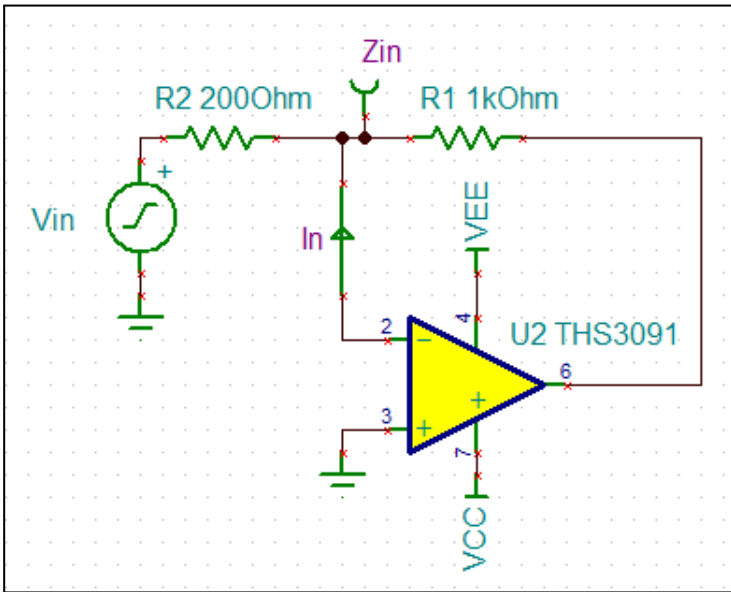
$$R_i = \frac{Z_{IN}}{I_N} = -72.04 - (-104.9) = 32.86\text{dB}\Omega = 43.95\Omega$$



I will leave the calculation of α in a closed-loop configuration as a reader exercise. For more support on current feedback amplifiers contact us on the E2E support forums:

http://e2e.ti.com/support/amplifiers/high_speed_amplifiers/