

SAR ADC Input Types



TIPL 4003

TI Precision Labs – ADCs



Created by Art Kay

Presented by Peggy Liska


Single Ended

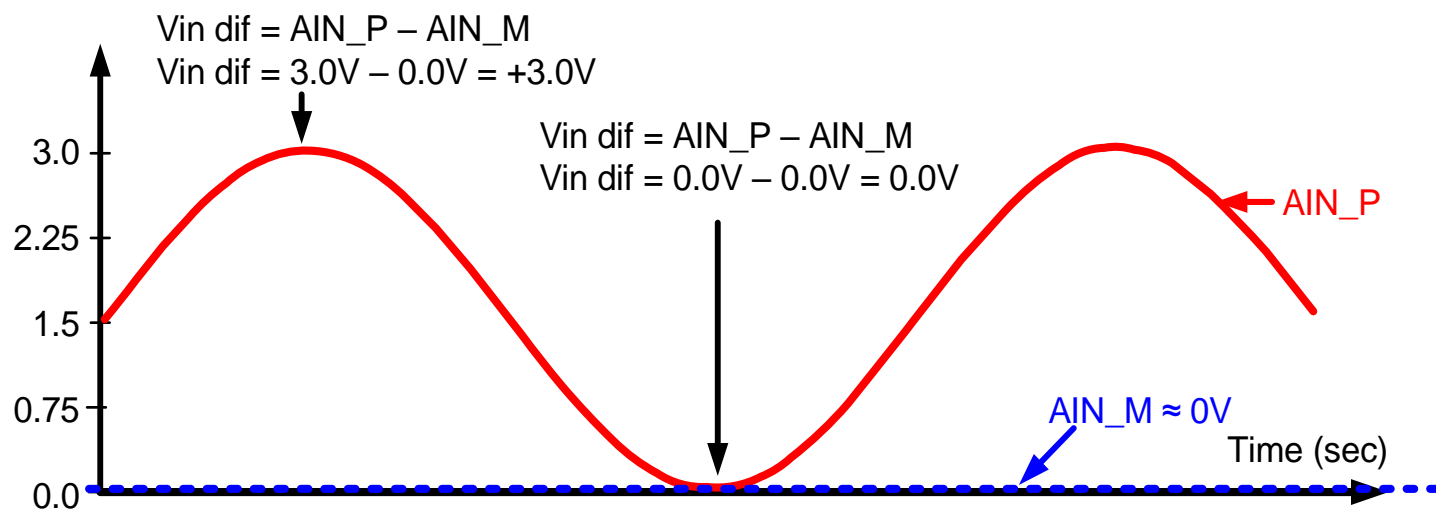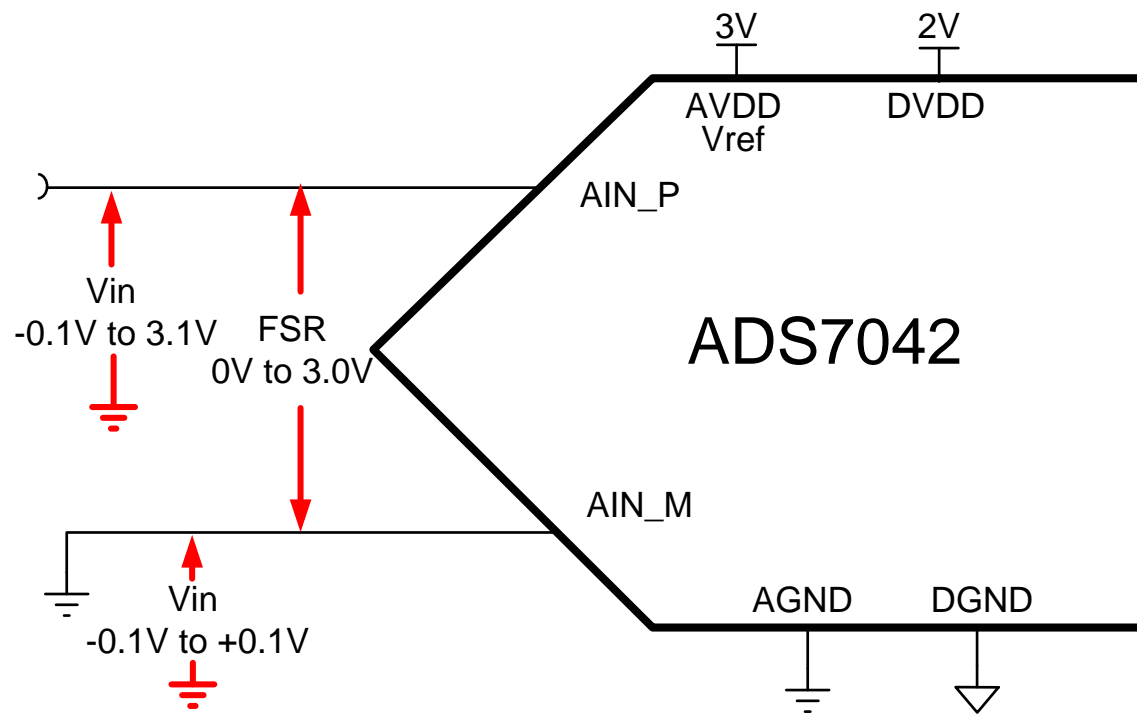

Pseudo-differential

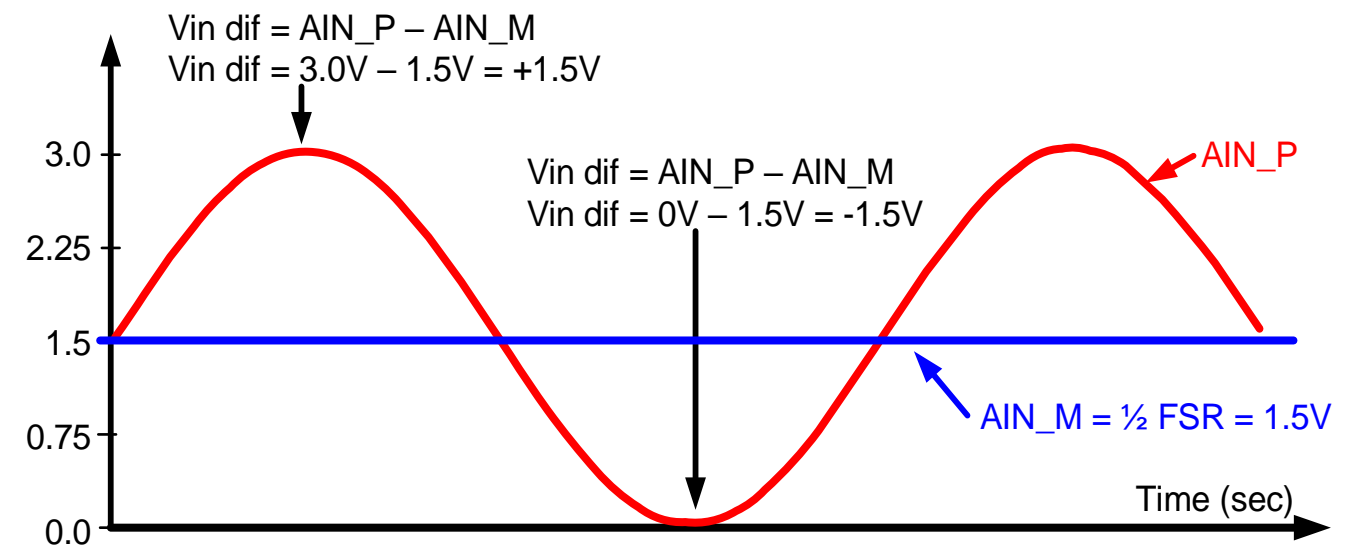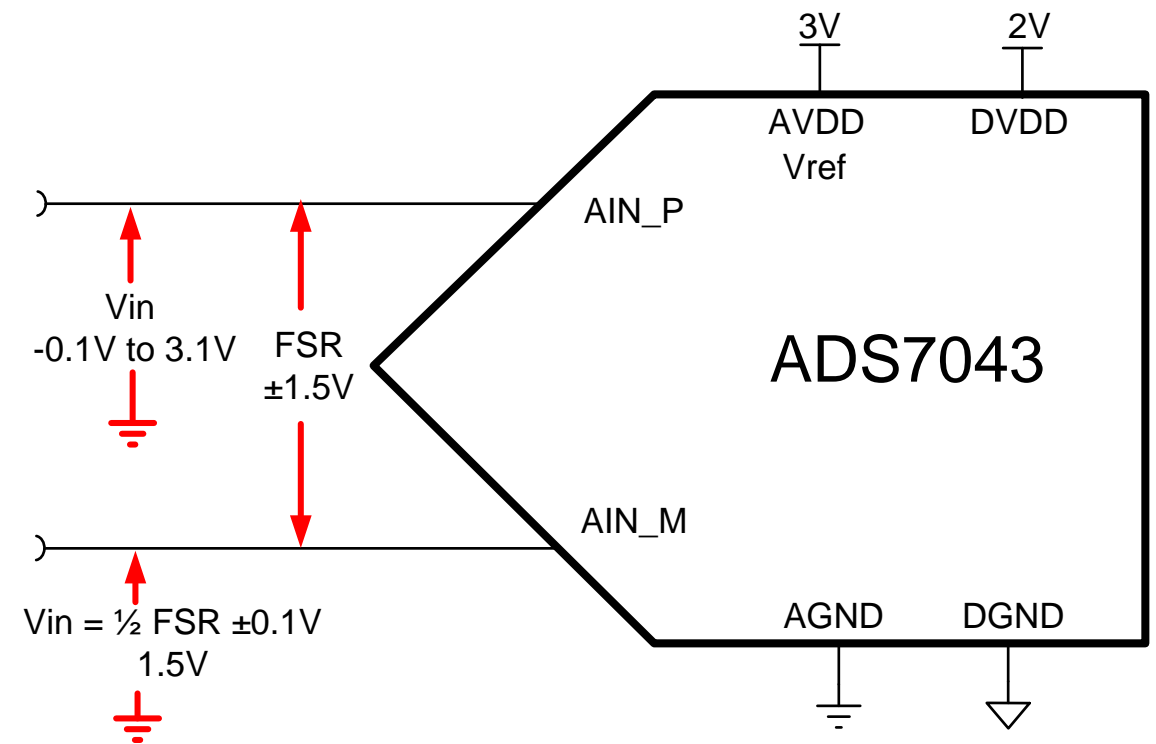


ADC Input Swing and Common Mode

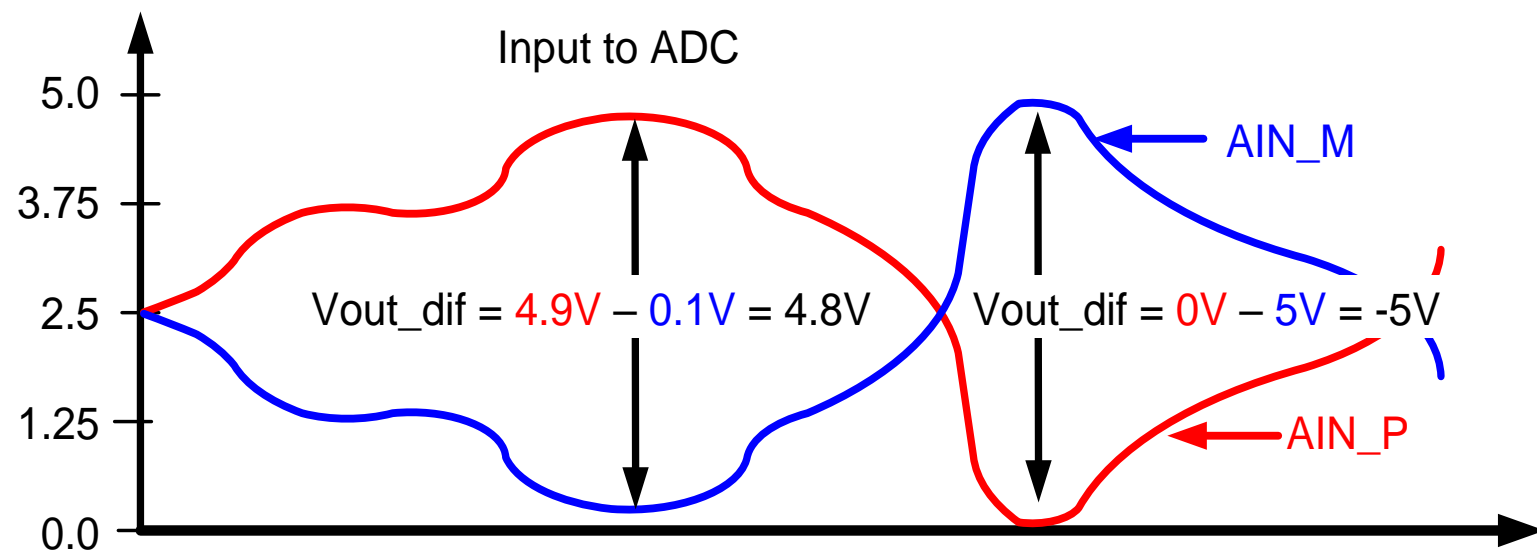

$$V_{dif} = AIN_P - AIN_M$$

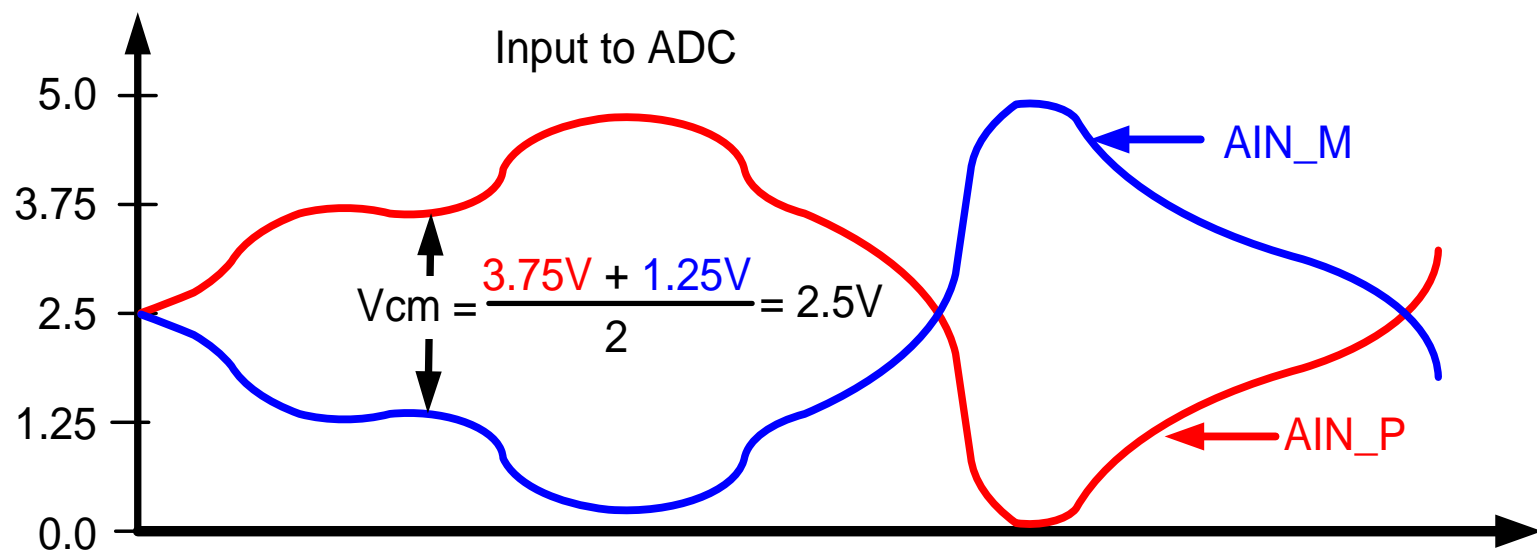- Differential of $\pm 5V$ (10Vpp)
- Single ended equivalent 0V to 5V (5Vpp)
- Double the range of single ended
- Negative differential output can occur when absolute output voltage of each output is positive (unipolar single supply)






$$V_{cm} = \frac{AIN_P + AIN_M}{2}$$

- In this example common mode is always 2.5V

Fully Differential Input

PARAMETER 9110	MIN	TYP	MAX	UNIT
ANALOG INPUT				
Full-scale input voltage span	-Vref		Vref	
Absolute Input voltage range	AIN_P to GND	-0.1	Vref + 0.1	V
	AIN_M to GND	-0.1	Vref + 0.1	
Common-mode voltage range (AIN_P + AIN_M)/2	(Vref/2)-0.1	Vref/2	(Vref/2)+0.1	


Vcm must be constant at Vref/2

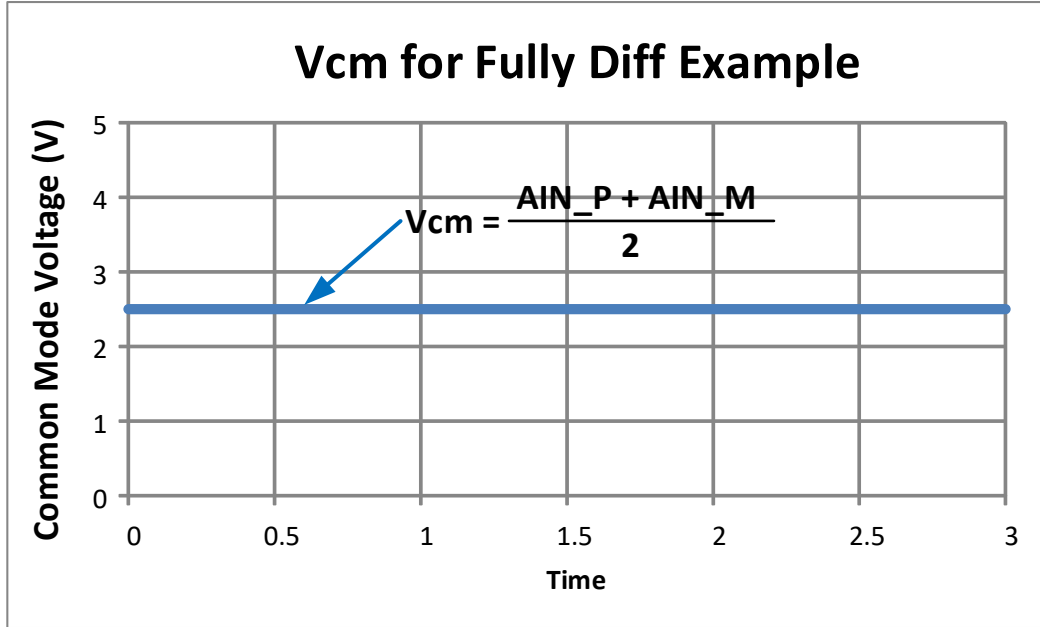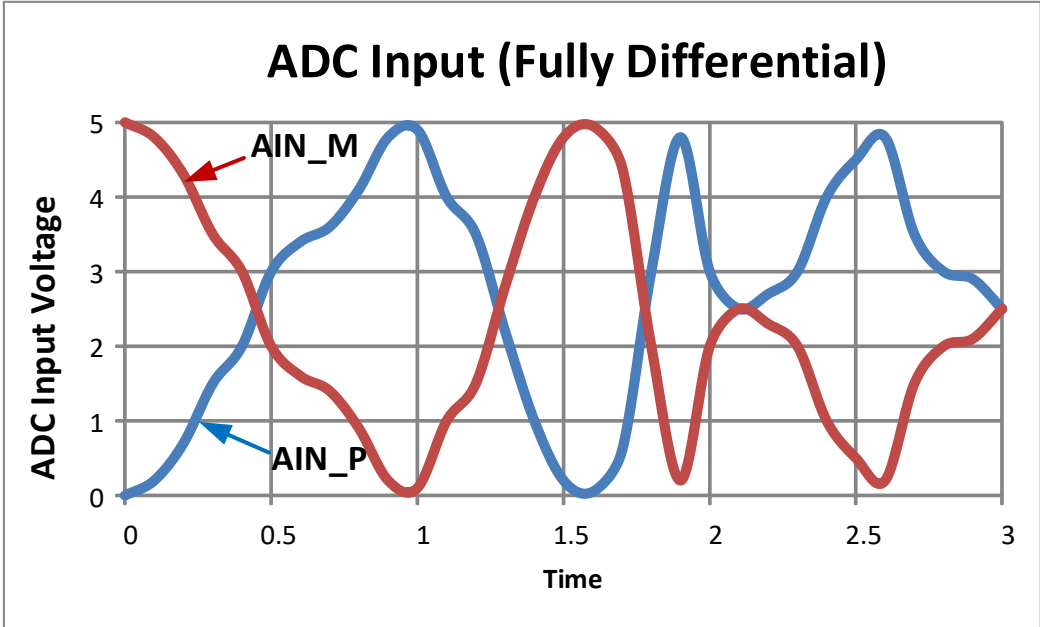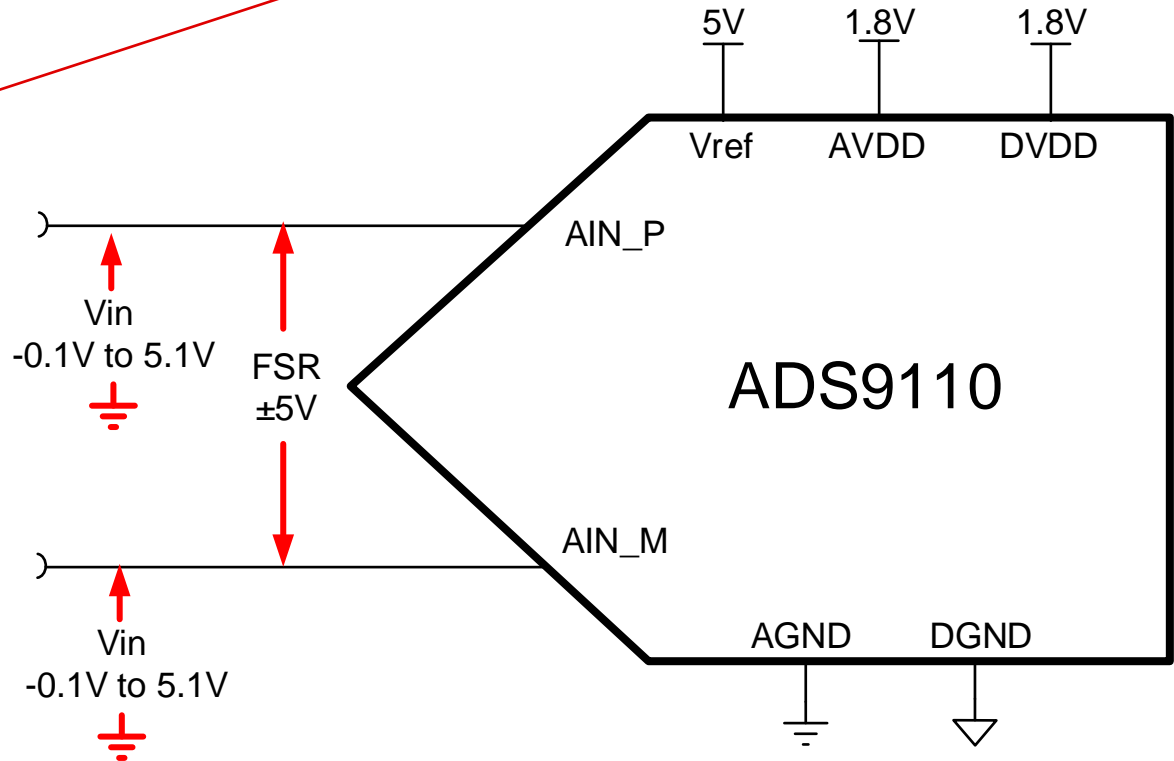


True Differential Input

PARAMETER ADS8881	MIN	TYP	MAX	UNIT
ANALOG INPUT				
Full-scale input voltage span	-Vref		Vref	
Absolute Input voltage range	AIN_P to GND	-0.1	Vref + 0.1	V
	AIN_M to GND	-0.1	Vref + 0.1	
Common-mode voltage range (AIN_P + AIN_M)/2	0.0	Vref/2	Vref	


Vcm has a wide voltage range.

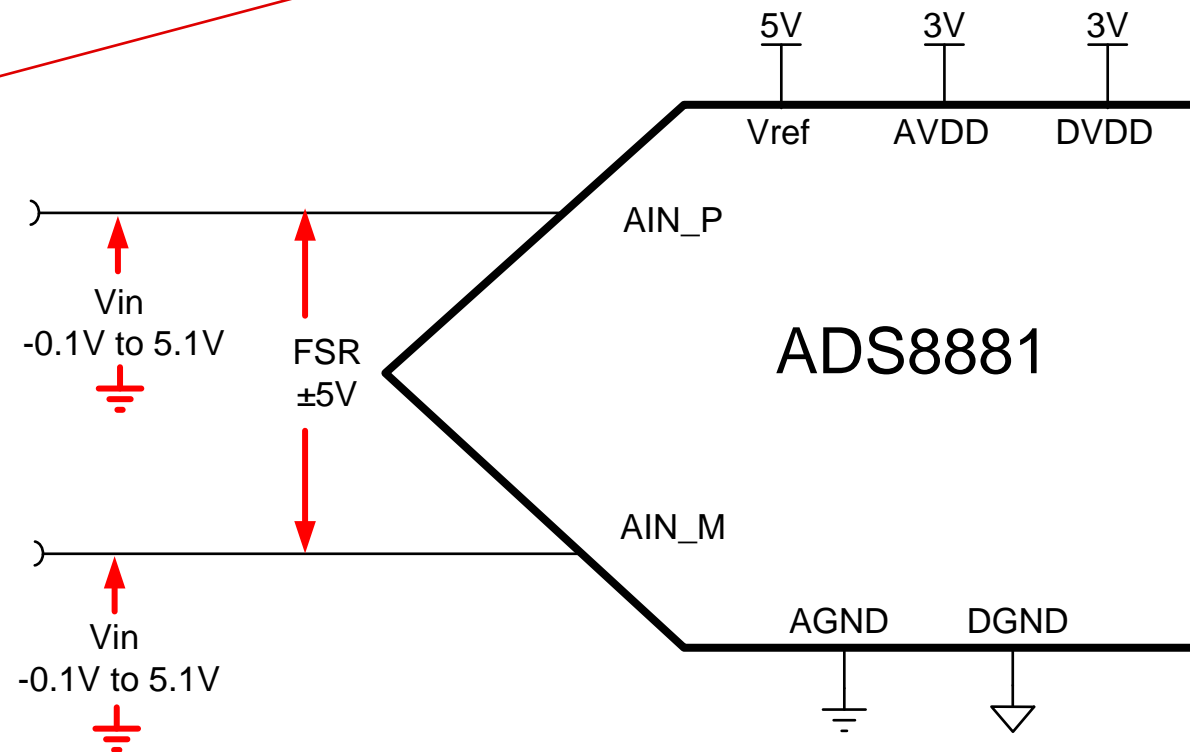

ADC Input Voltages (True Differential)

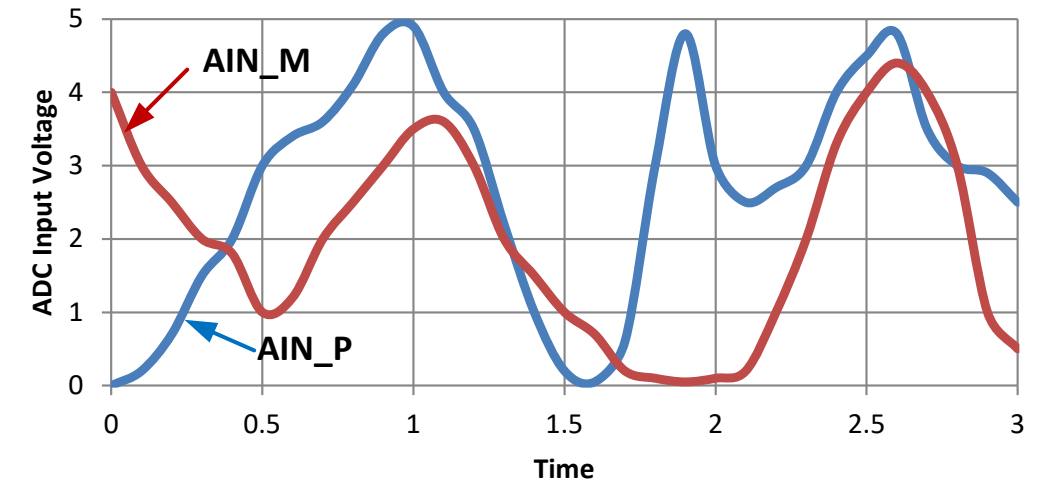


Vcm for True Diff Example

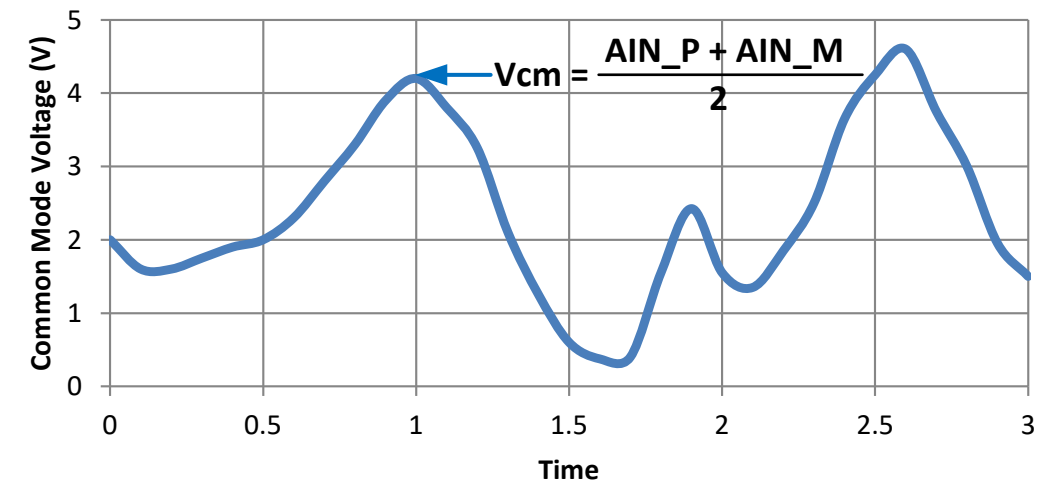


Summary of ADC input types

Input Type	Vref	Ain_P	Ain_M	Vcm	FSR	Example 16 Bit Output
Single Ended	5V	0V to 5V	GND (+/- 100mV)	n/a	0V to 5V	0000 = 0V FFFF = FSR = 5V
Pseudo Differential	5V	0V to 5V	Set ½ * Range (2.5V)	n/a	-2.5V to +2.5V	8000 = -2.5V 7FFF = +2.5V
Fully Differential	5V	0V to 5V	0V to 5V	Set ½ * Range (2.5V)	-5V to +5V	8000 = -5V 7FFF = +5V
True Differential	5V	0V to 5V	0V to 5V	Can vary from -FS to +FS	-5V to +5V	8000 = -5V 7FFF = +5V

Unipolar vs Bipolar

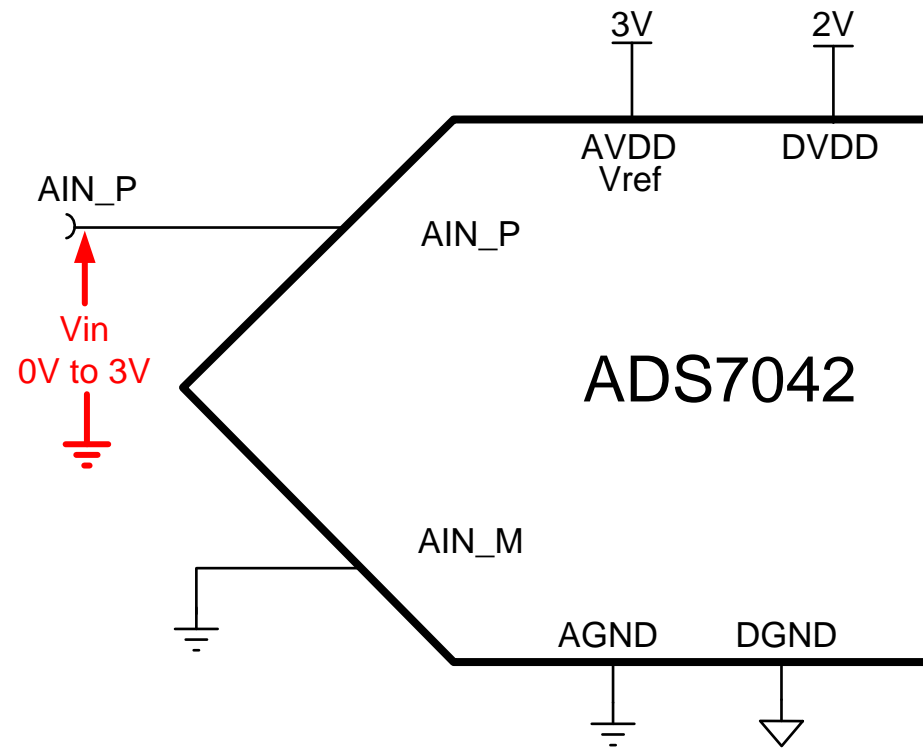


Unipolar Input

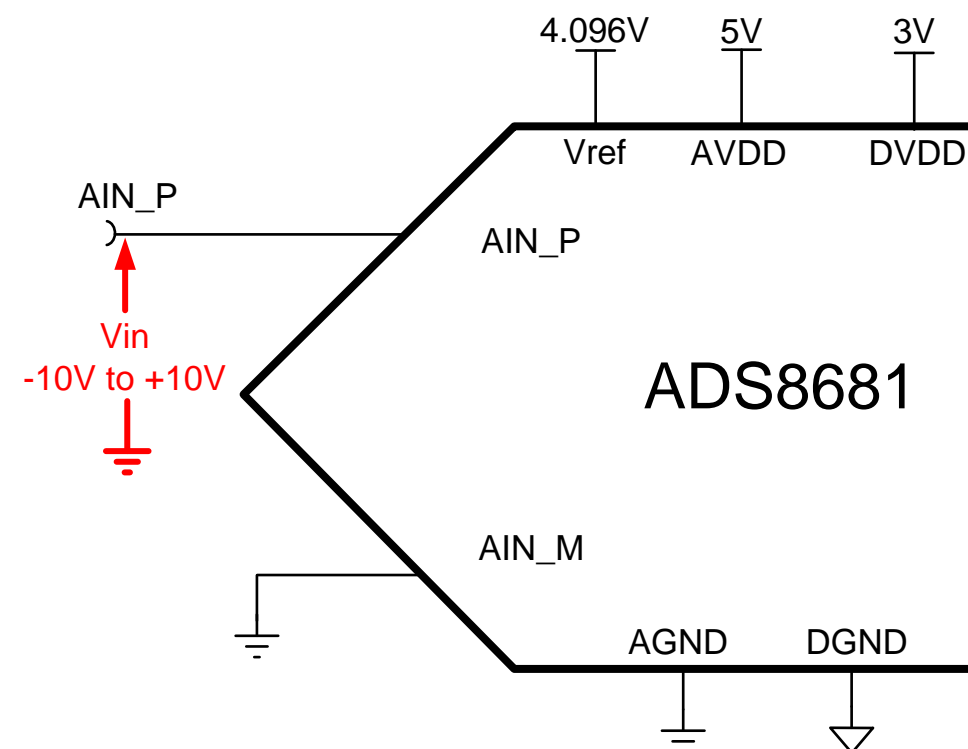

Bipolar Input


Unipolar with Differential Input

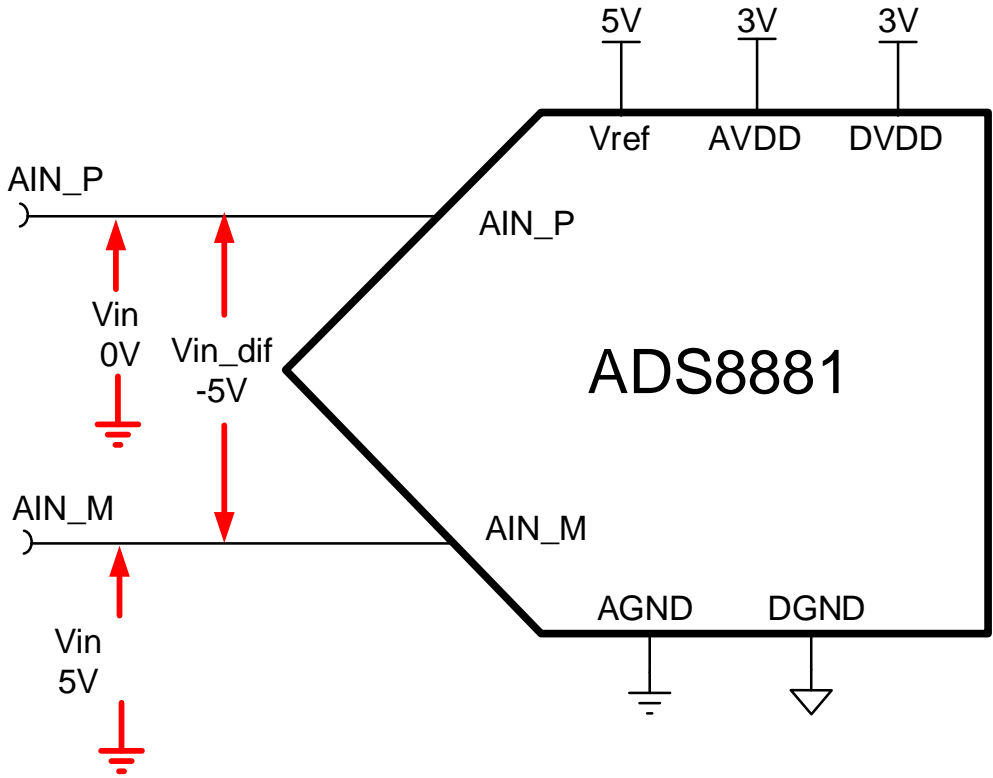

Negative Full Scale Input

$$V_{in_dif} = AIN_P - AIN_M$$

$$V_{in_dif} = 0V - 5V = -5V$$

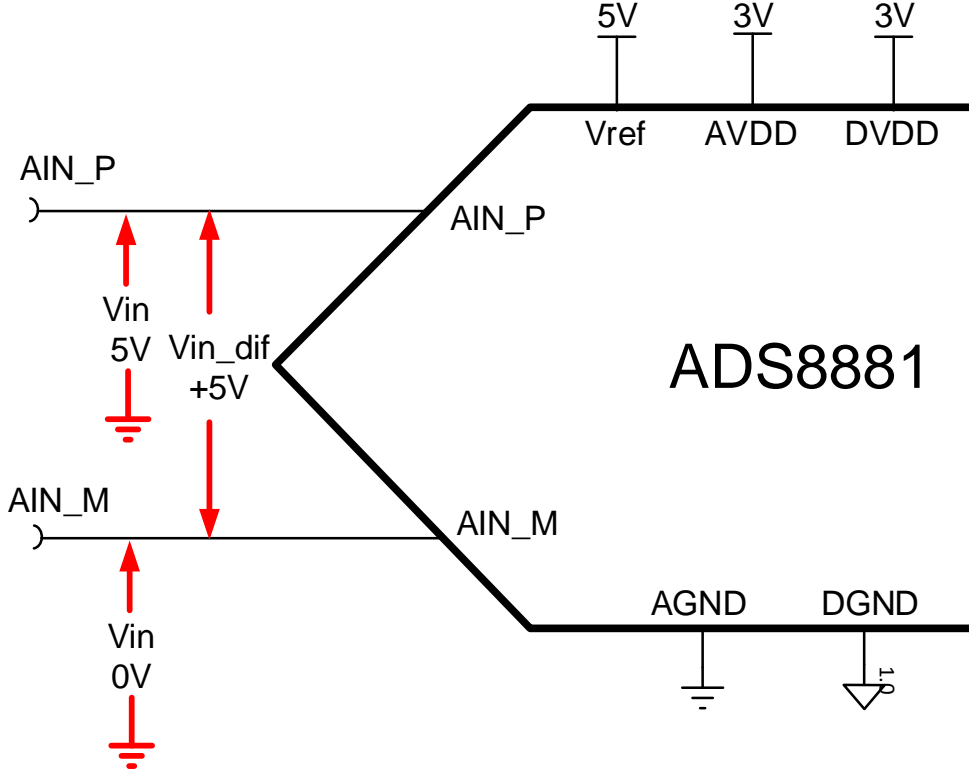


Positive Full Scale Input

$$V_{in_dif} = AIN_P - AIN_M$$


$$V_{in_dif} = 5V - 0V = +5V$$

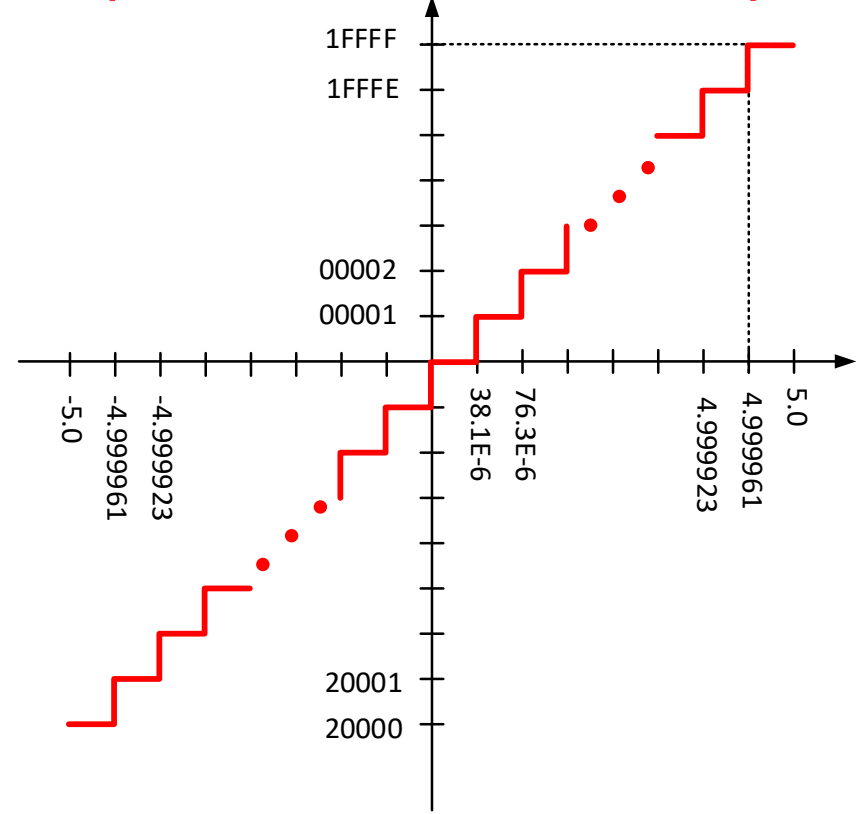Transfer Function:
Unipolar with Differential Inputs




Input Impedance: Resistive vs. Switched Capacitor

Switched Capacitor Input

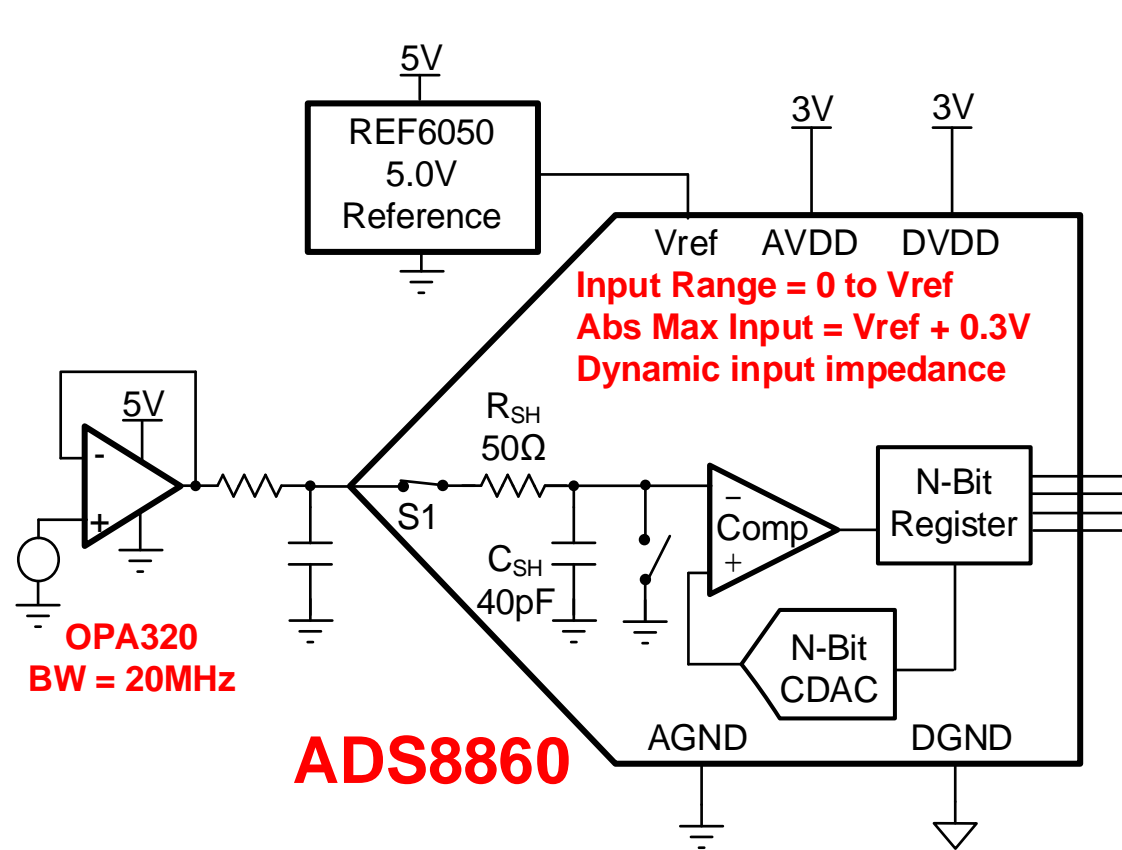

- Wide bandwidth external amp required
- Dynamic input impedance
- Input voltage range set by reference

Resistive, High Voltage, PGA input

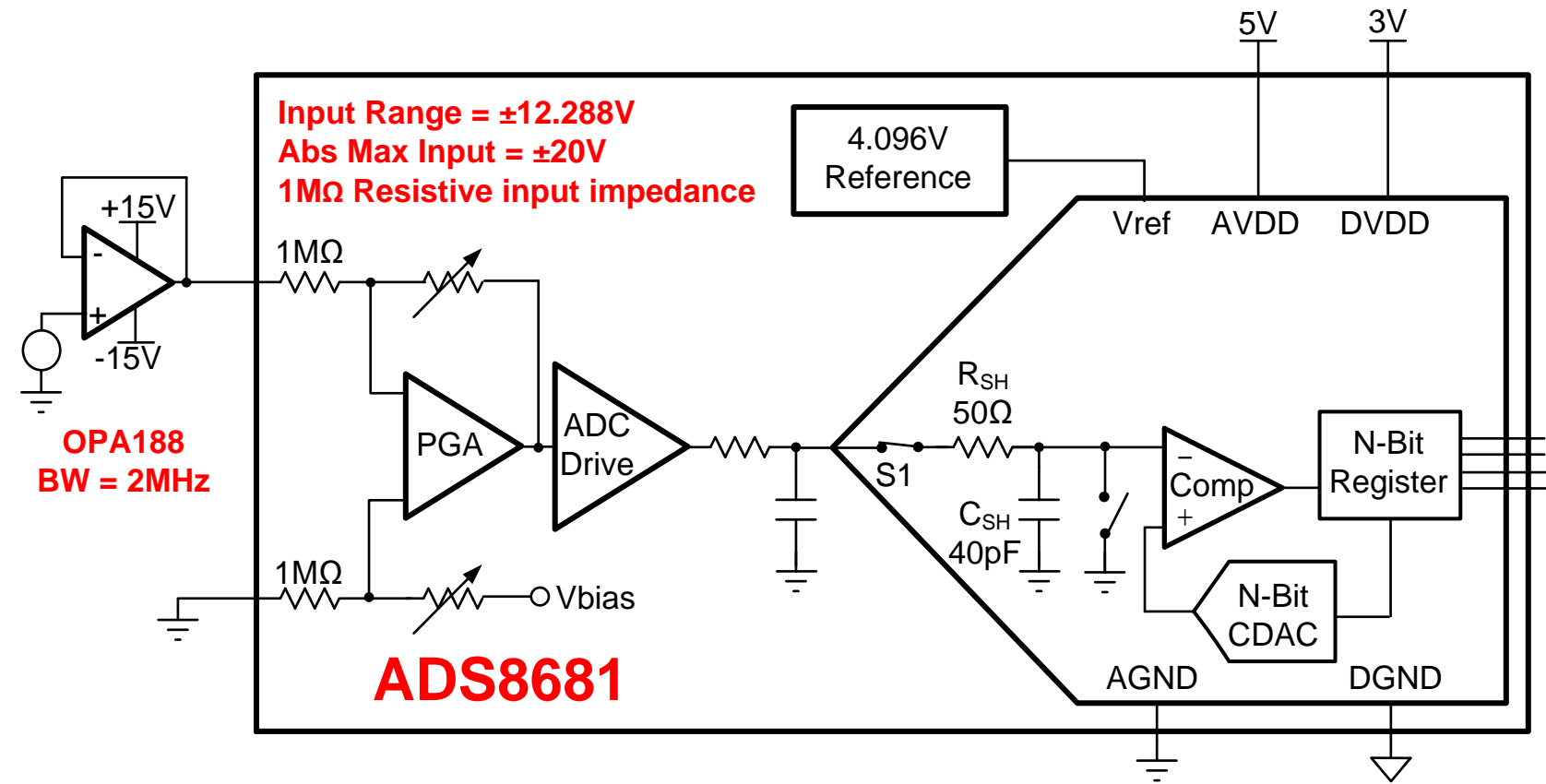

- External amplifier bandwidth not critical
- Internal PGA, ADC driver, and reference
- High voltage input (±12.288V) with 5V supply

Thanks for your time!
Please try the quiz.

Quiz: SAR ADC Input Types


TIPL 4003

TI Precision Labs – SAR

Created by Art Kay



Quiz: SAR ADC Input Types

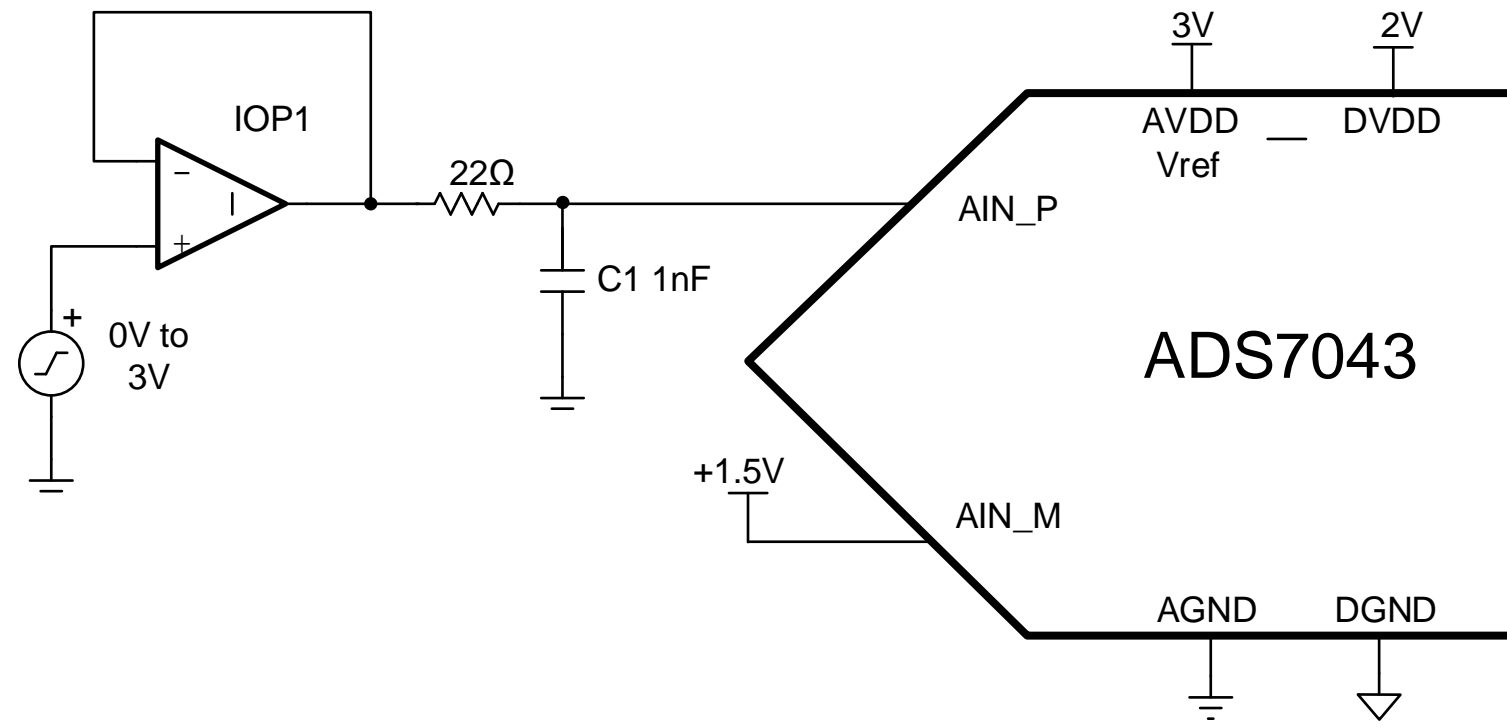1. The circuit in the figure below is a _____.
 - a. Single ended ADC.
 - b. Pseudo-differential ADC.
 - c. Fully Differential ADC.
 - d. True Differential ADC.





Quiz: SAR ADC Input Types

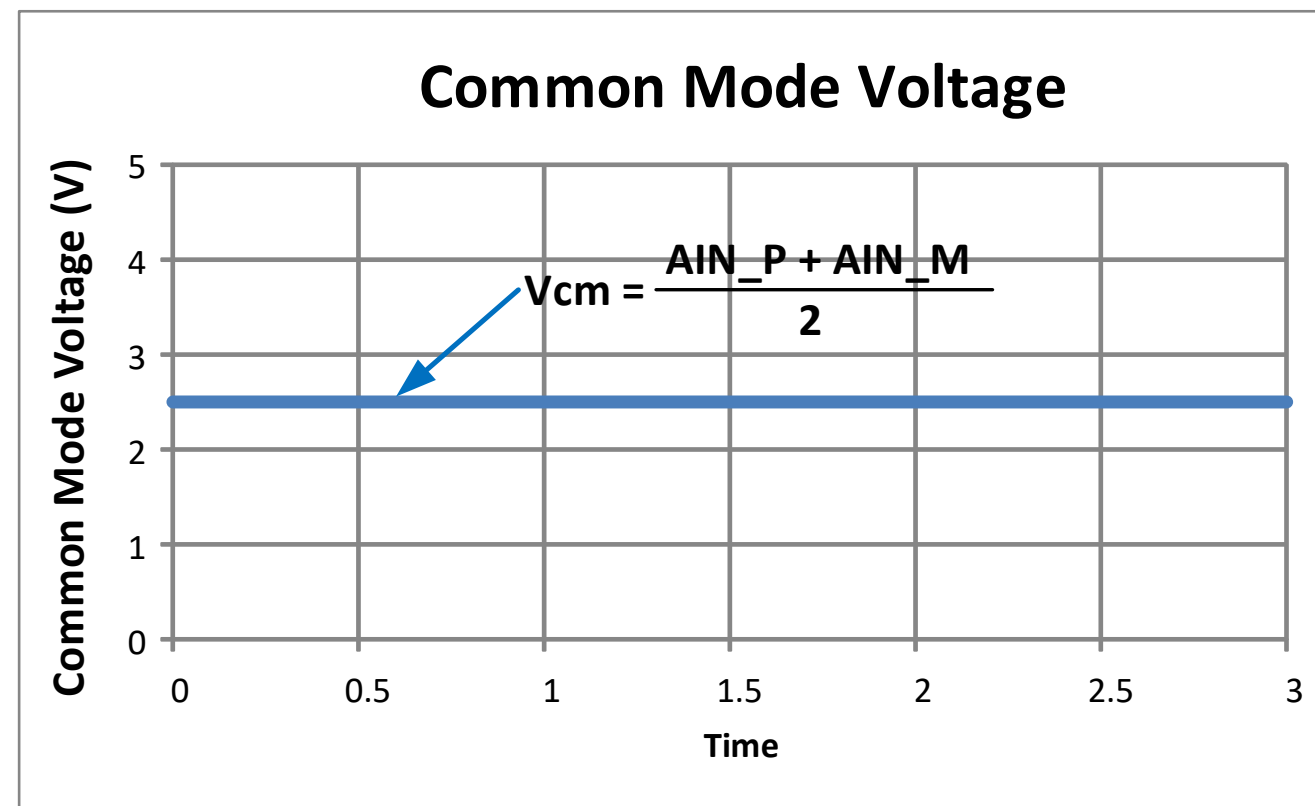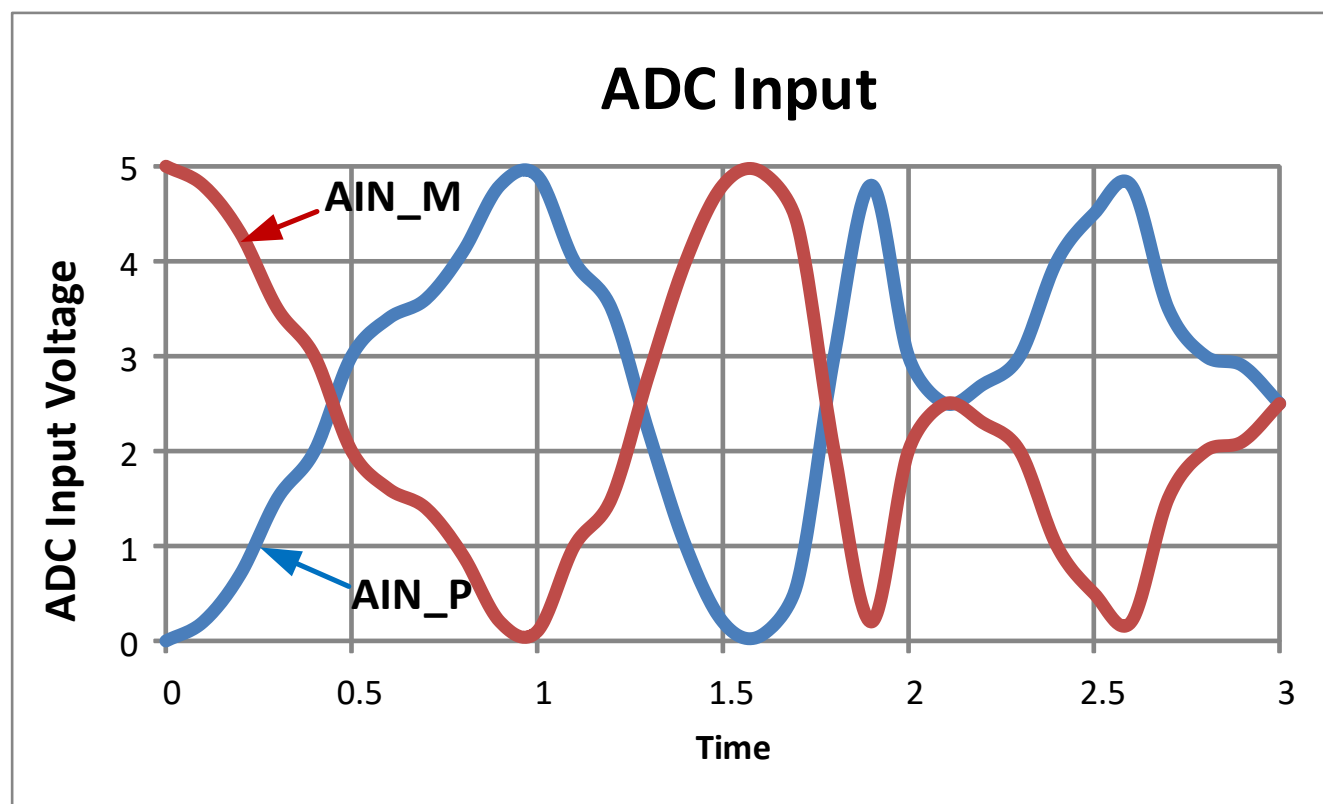2. (T/F) The signal below can be directly applied to an ADC with a fully differential input.
- a. True.
 - b. False.



Quiz: SAR ADC Input Types

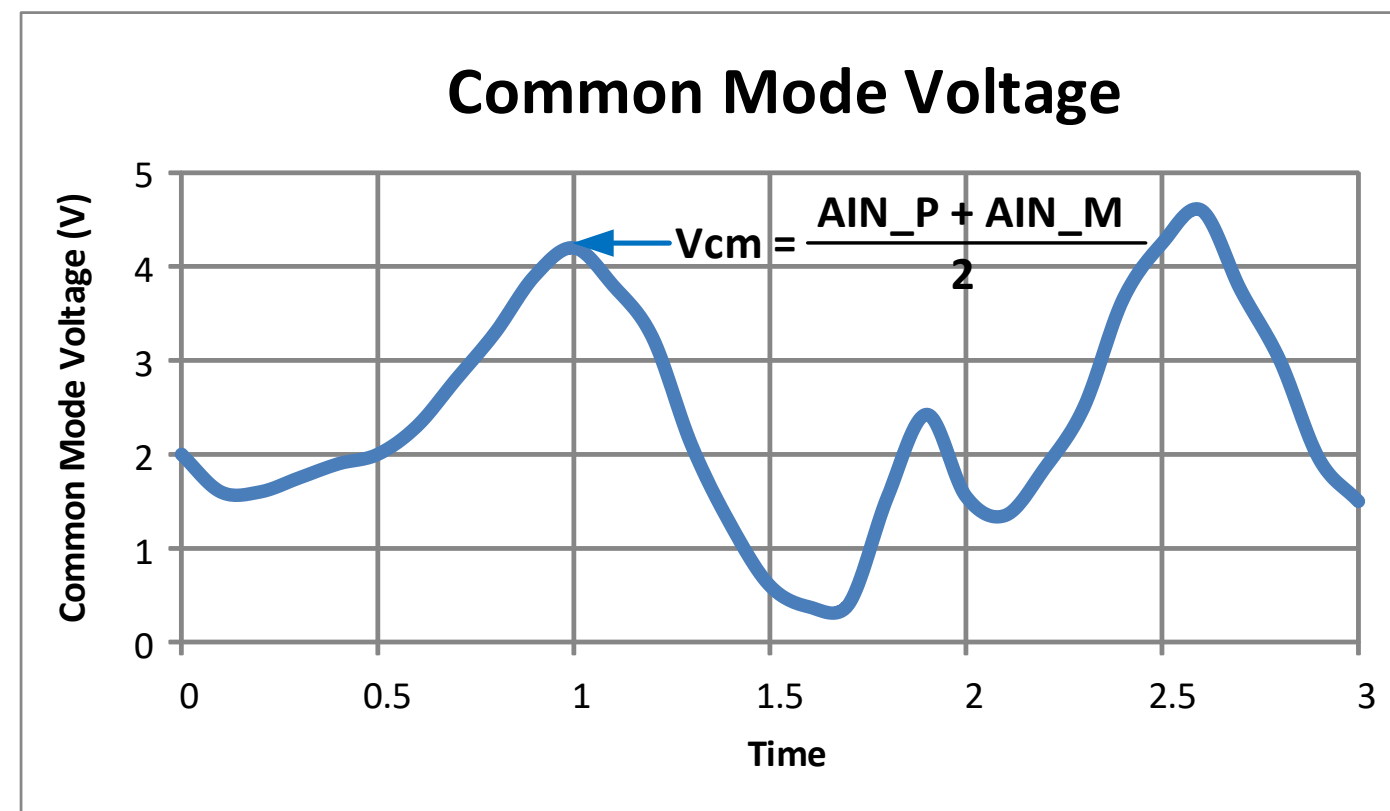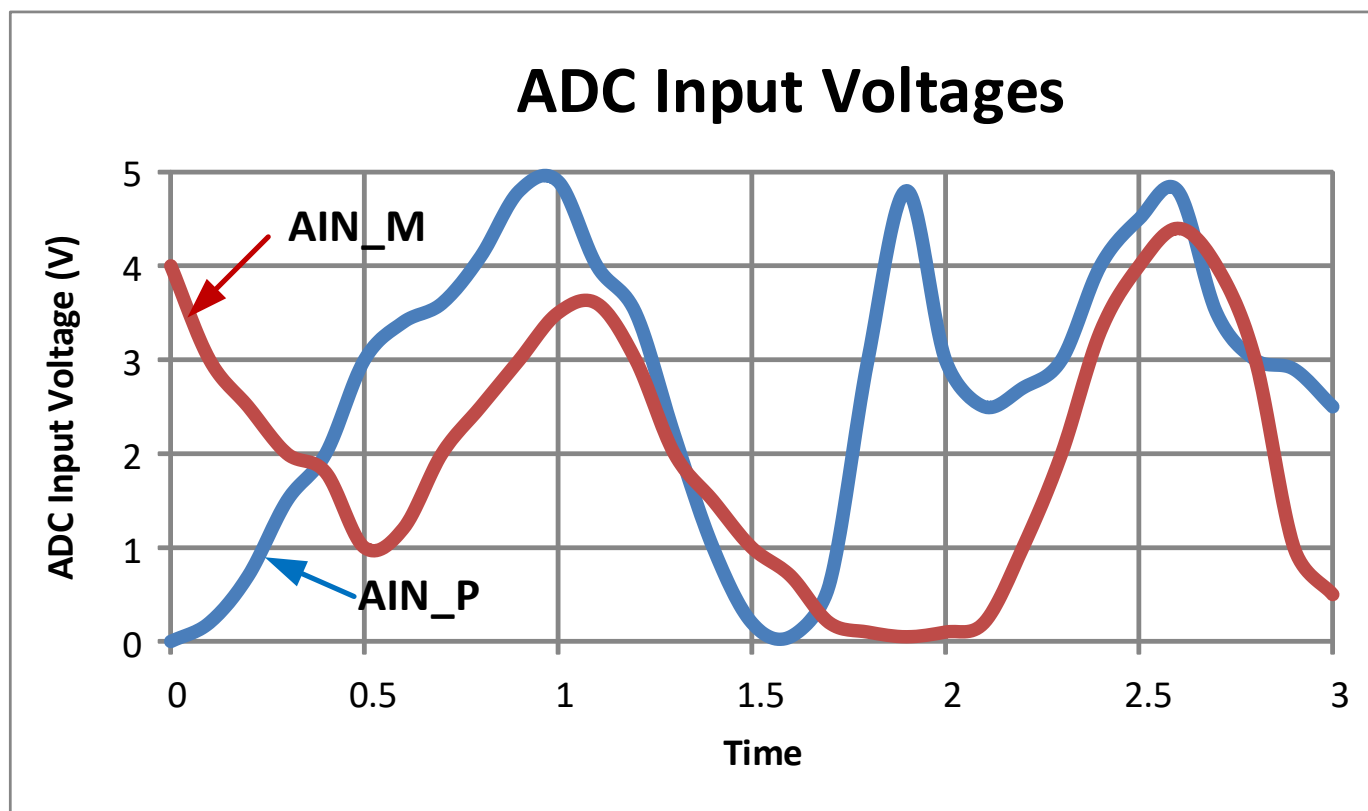3. (T/F) The signal below can be directly applied to an ADC with a fully differential input.
- a. True.
 - b. False.




Quiz: SAR ADC Input Types

4. Which type of ADC would require a wide bandwidth amplifier and a RC charge bucket filter?
 - a. A high voltage SAR with an internal PGA.
 - b. A switched capacitor input SAR ADC.


5. (T/F) In general, a fully differential input has double the range of a single ended input assuming the same reference voltage.
 - a. True.
 - b. False.

Quiz: SAR ADC Input Types

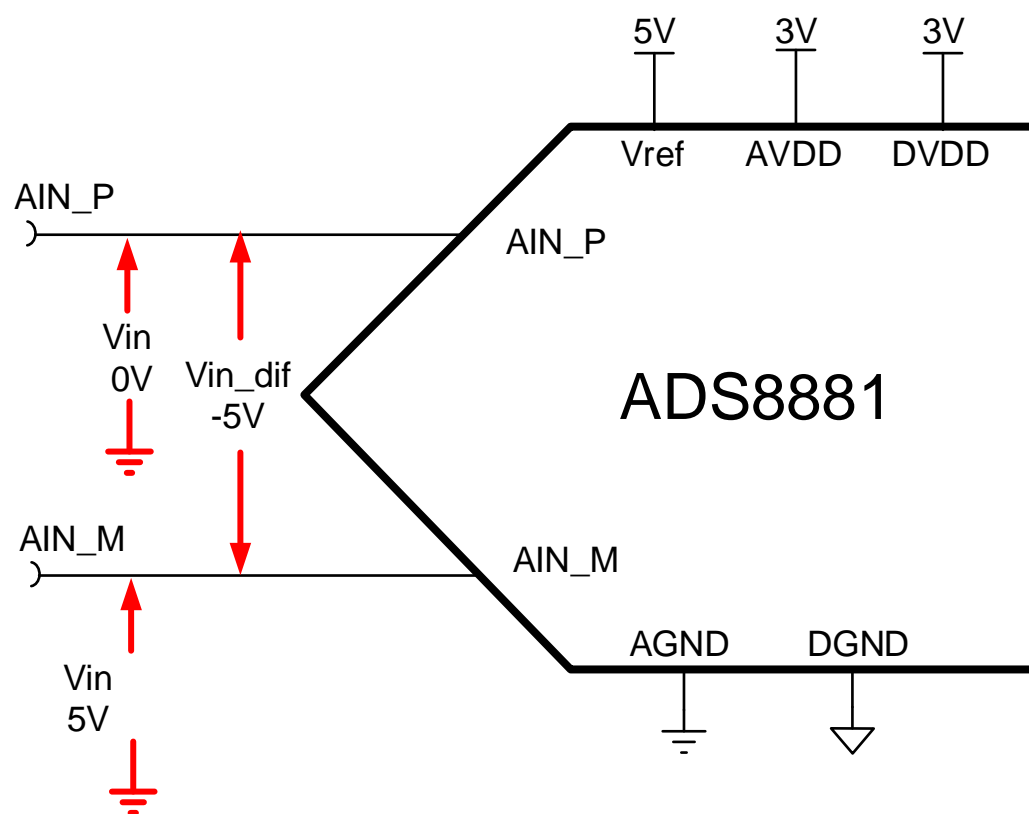6. The circuit in the figure below has a ____.
- a. Unipolar, differential input.
 - b. Bipolar, differential input.



Negative Full Scale Input

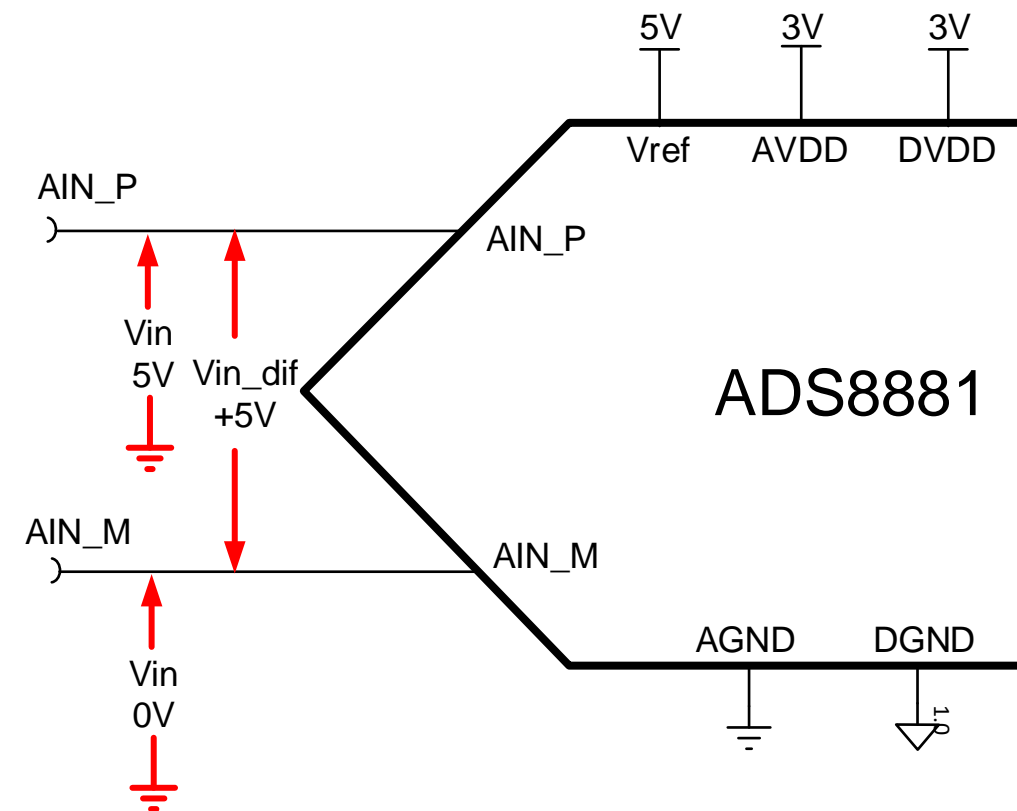


Positive Full Scale Input

Solutions



Solutions Quiz: SAR ADC Input Types

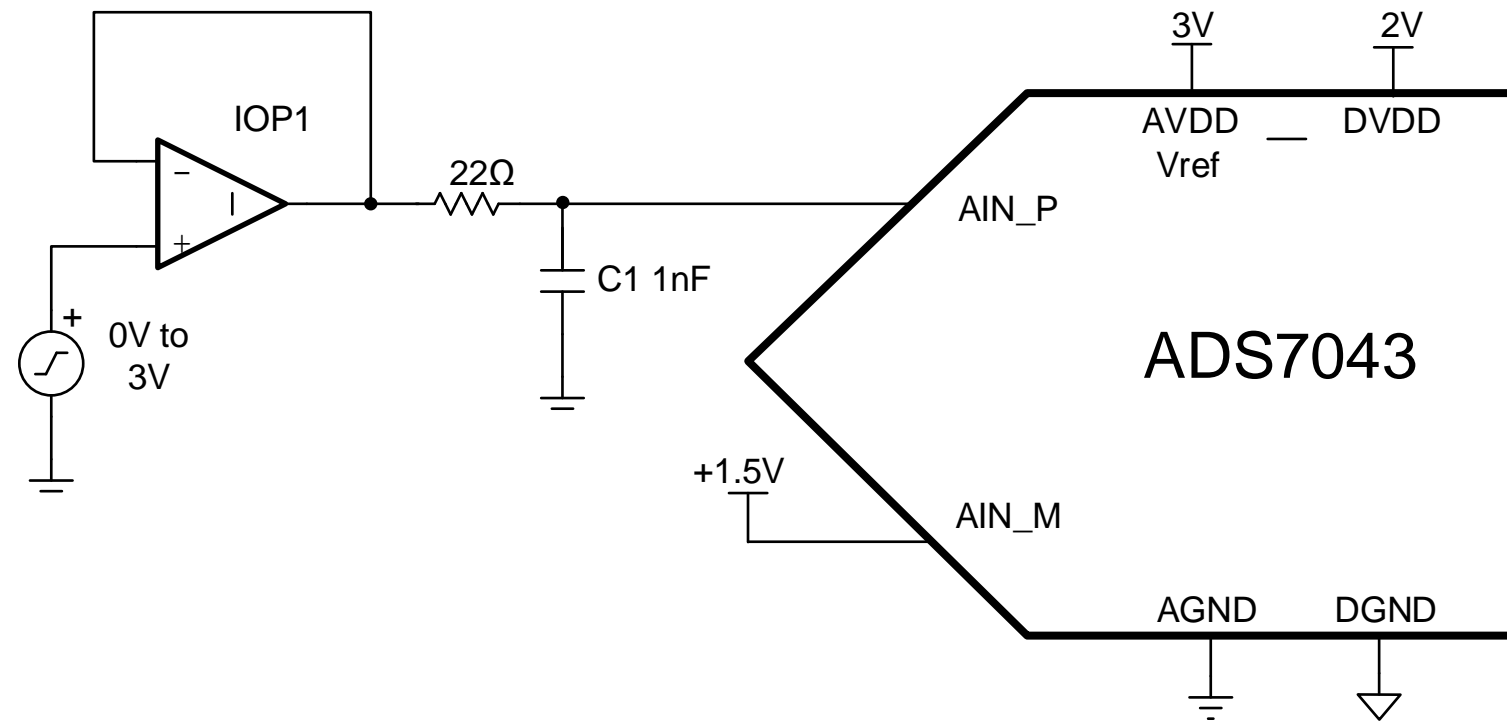1. The circuit in the figure below is a _____.
 - a. Single ended ADC.
 - b. Pseudo-differential ADC.**
 - c. Fully Differential ADC.
 - d. True Differential ADC.





Solutions Quiz: SAR ADC Input Types

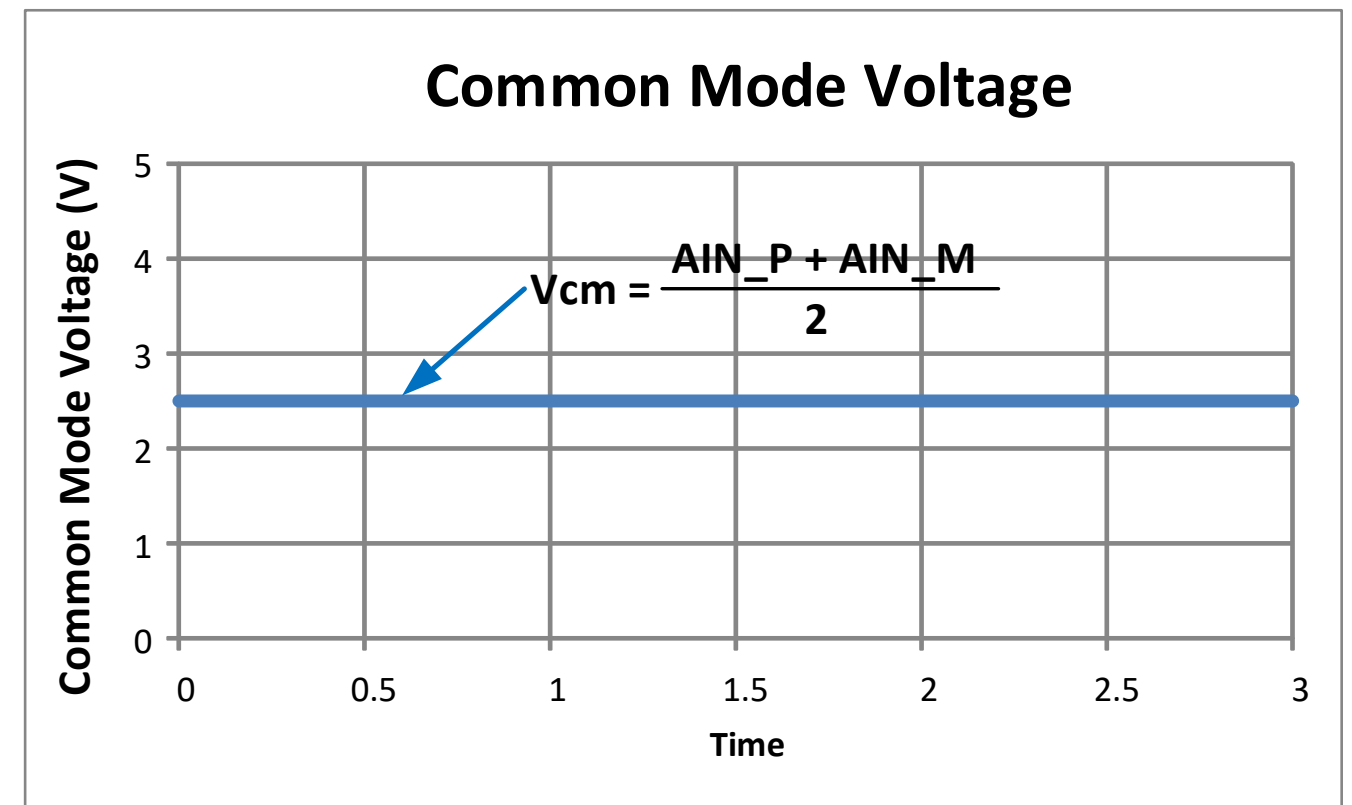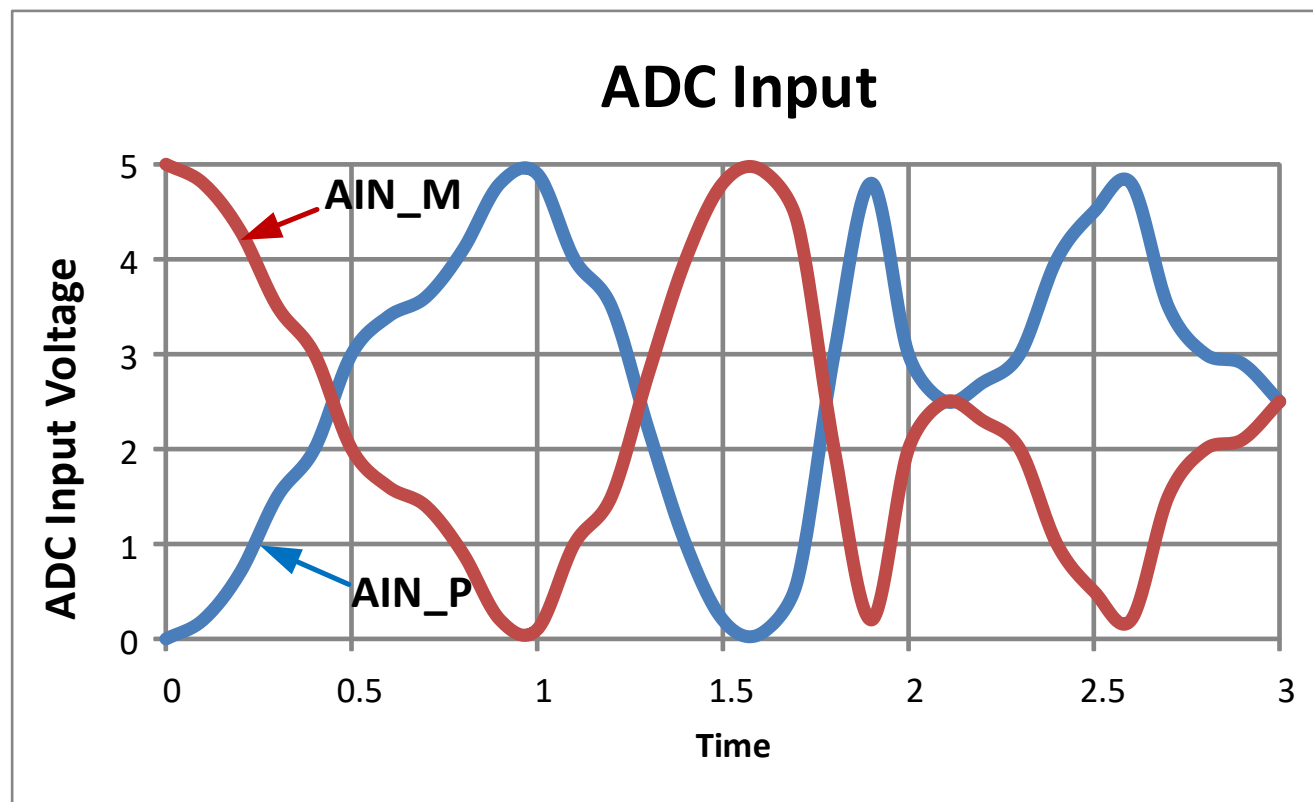2. (T/F) The signal below can be directly applied to an ADC with a fully differential input.
- a. True.
 - b. False.



Solutions Quiz: SAR ADC Input Types

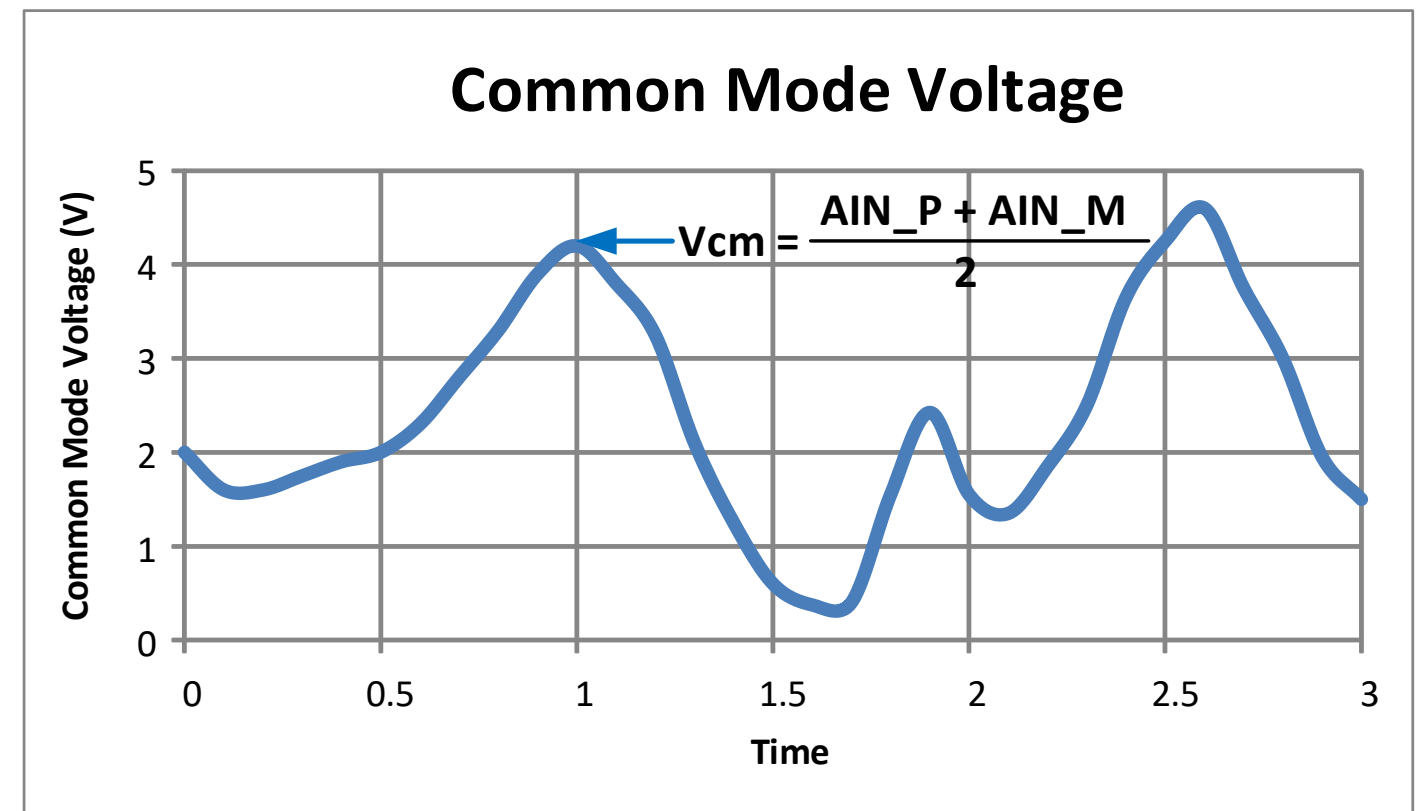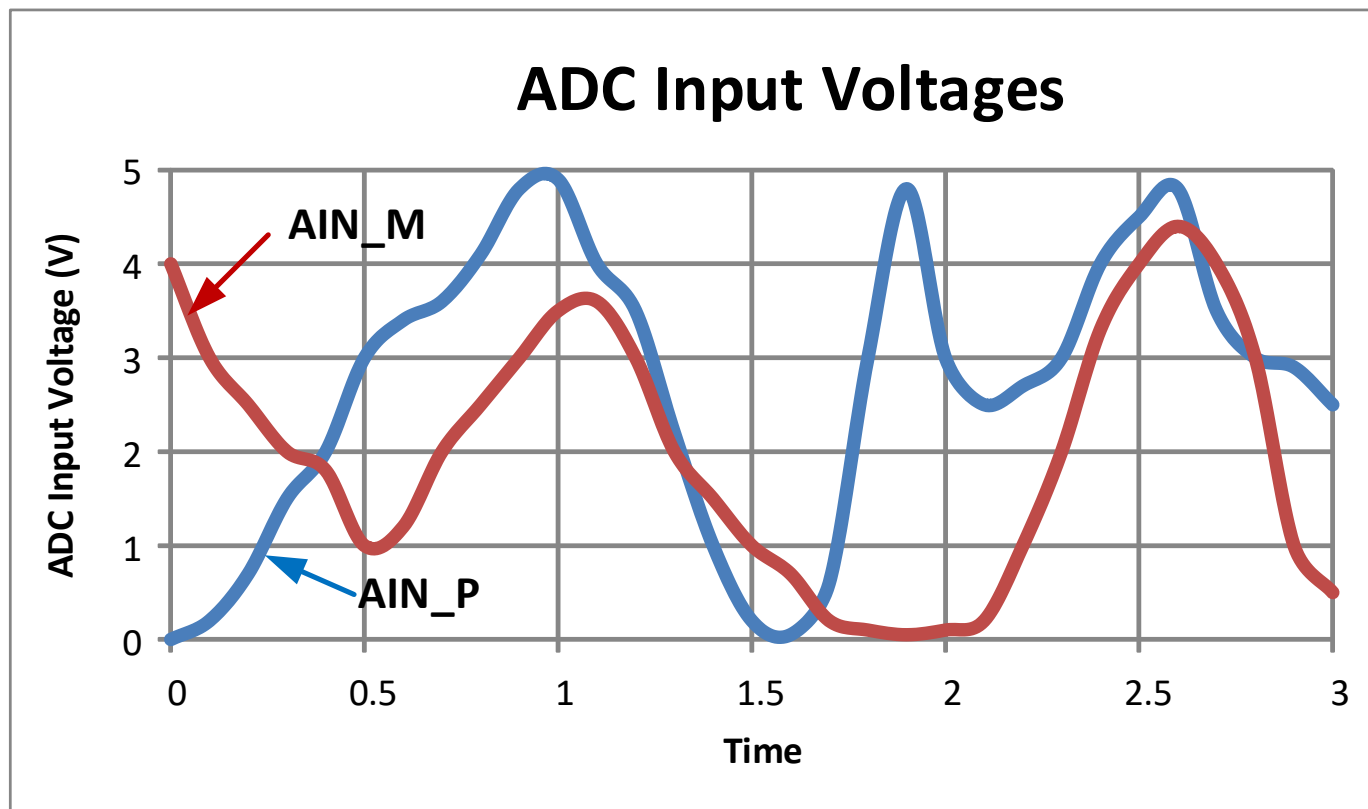3. (T/F) The signal below can be directly applied to an ADC with a fully differential input.
- a. True.
 - b. False.**



Solutions Quiz: SAR ADC Input Types

4. Which type of ADC would require a wide bandwidth amplifier and a RC charge bucket filter?
 - a. A high voltage SAR with an internal PGA.
 - b. A switched capacitor input SAR ADC.**


5. (T/F) In general, a fully differential input has double the range of a single ended input assuming the same reference voltage.
 - a. True.**
 - b. False.

Solutions Quiz: SAR ADC Input Types


6. The circuit in the figure below has a _____.

a. **Unipolar, differential input.**

b. Bipolar, differential input.

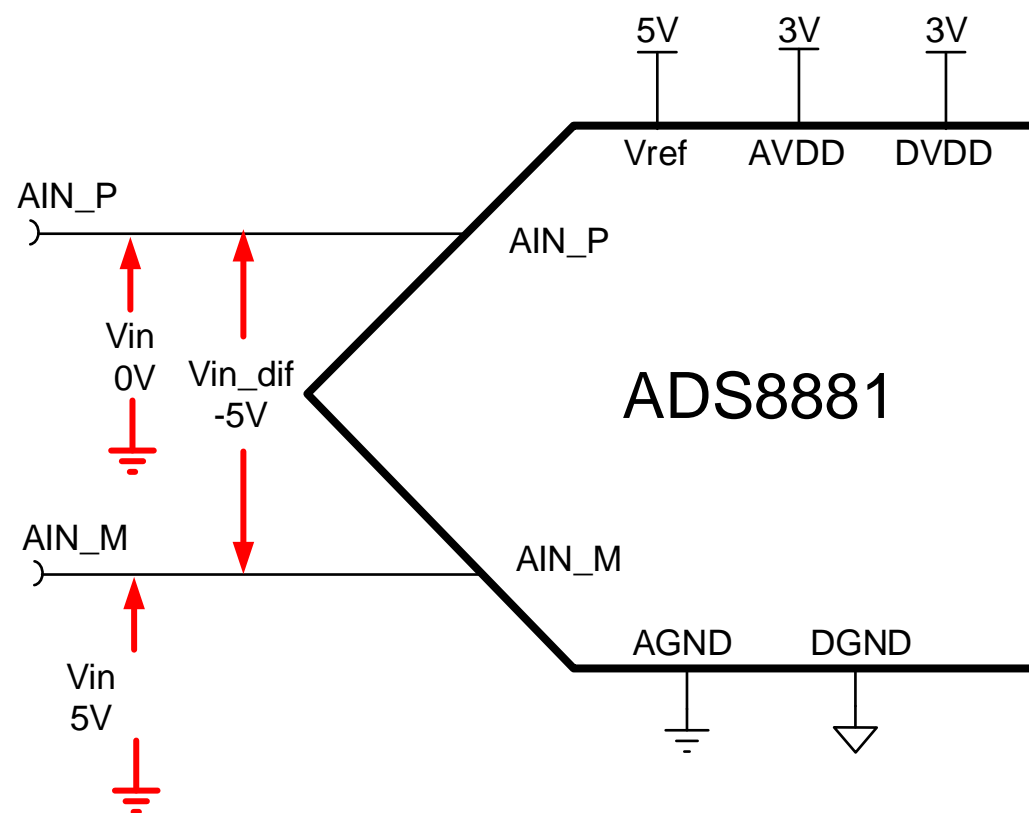

Negative Full Scale Input

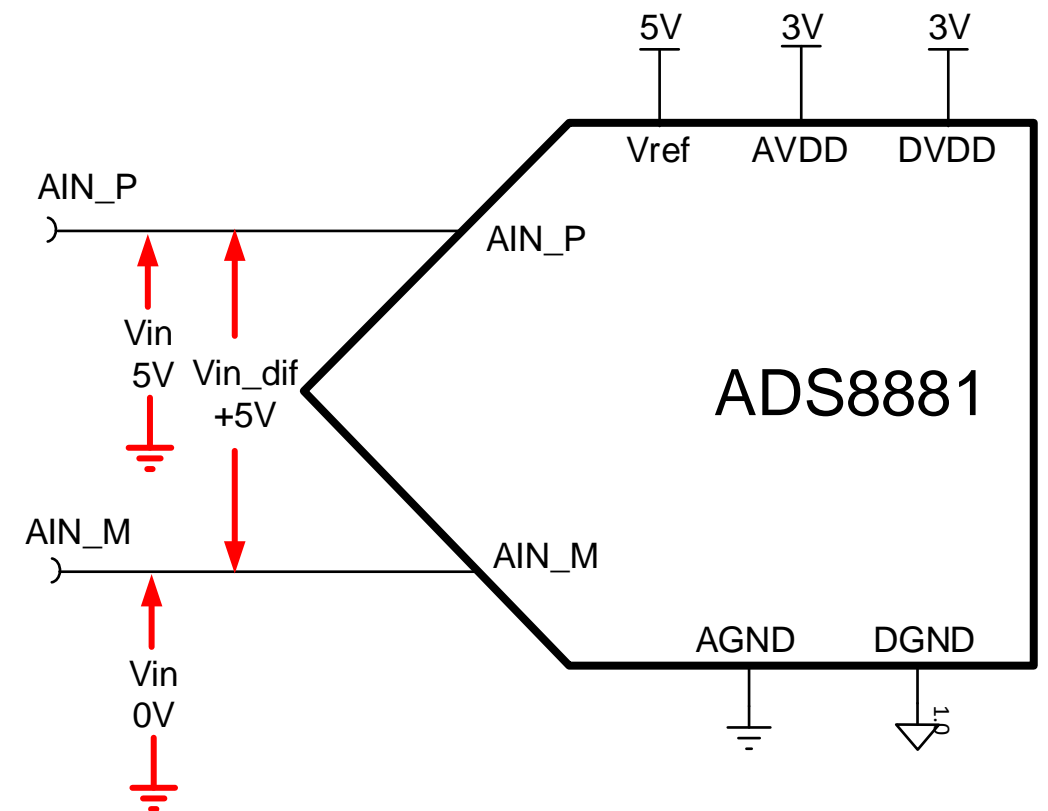

Positive Full Scale Input