

High **VOLT** Interactive

Where power supply design meets collaboration

How to protect SiC MOSFETs... the best way!


Gangyao Wang

What will I get out of this session?

- What are SiC MOSFET advantages compared with Si MOSFET and IGBT
- Different short circuit current sensing and protection methods
- How to safely turn off MOSFET under short circuit


- Relevant part numbers:
 - UCC2152x
 - ISO585X
- Relevant reference designs:
 - TIDA-01604&5
 - ISO5852SDWEVM-017
 - TIDA-00917
- Relevant applications:
 - Solar Inverter, HEV/EV Traction Inverter, EV On-Board Charger, Charging Pile

SiC MOSFET Application Positioning

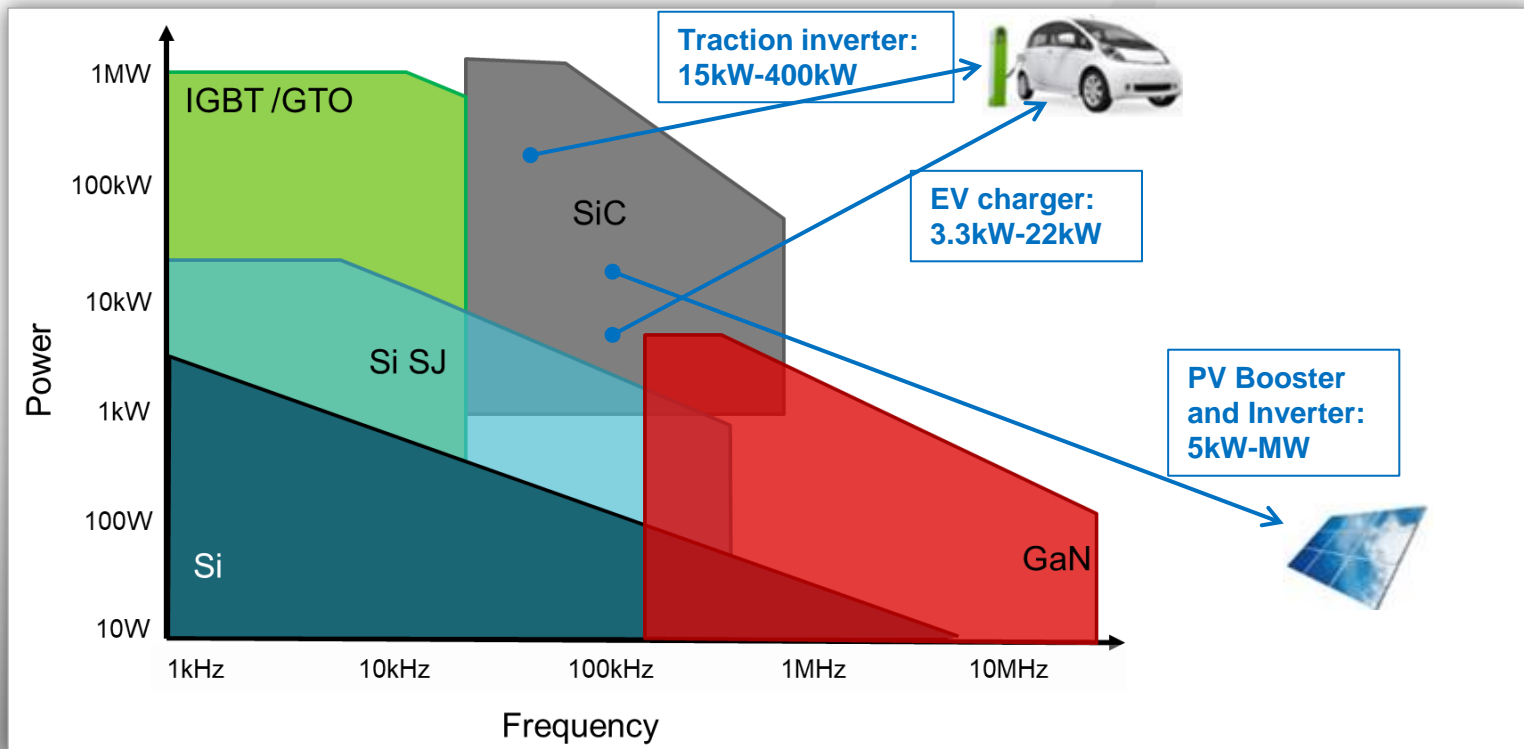


SiC MOSFET Advantages over Si MOSFET

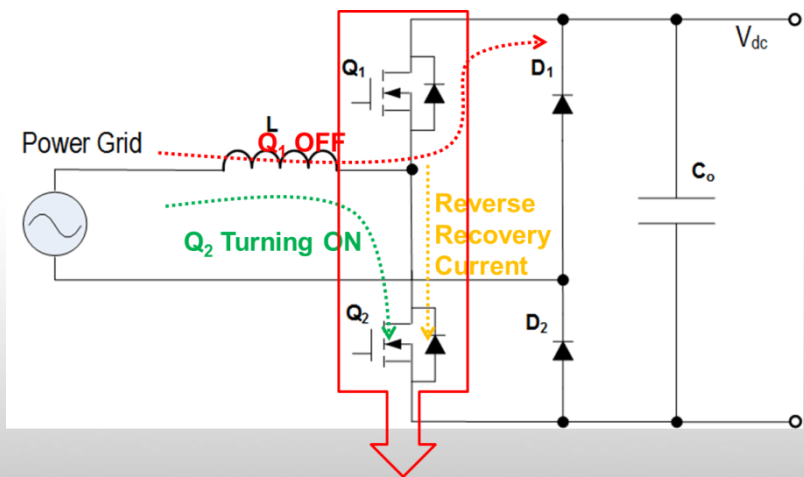- 1) Lower specific $R_{ds(on)}$ especially for $>650V$ devices;
- 2) Low body diode reverse recovery.






Use SiC , GaN devices or Si IGBT!

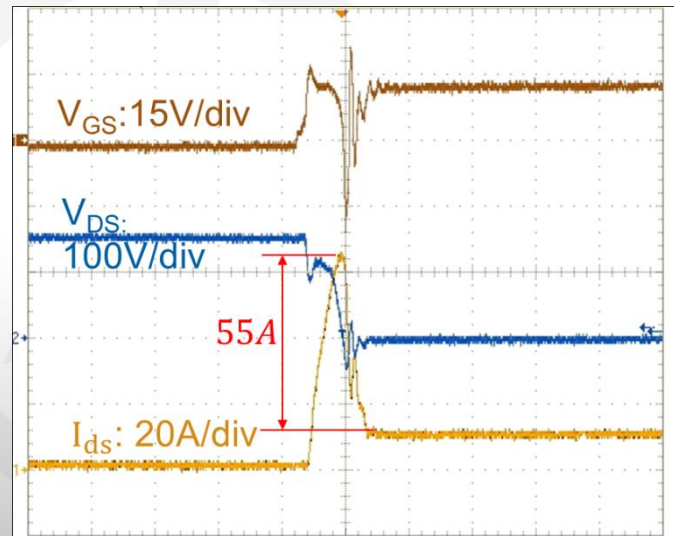

SJ-MOSFET Reverse Recovery at $V_{dd}=150V$, $I_{dd}=10A$

SiC MOSFET Advantages over Si IGBT: Conduction

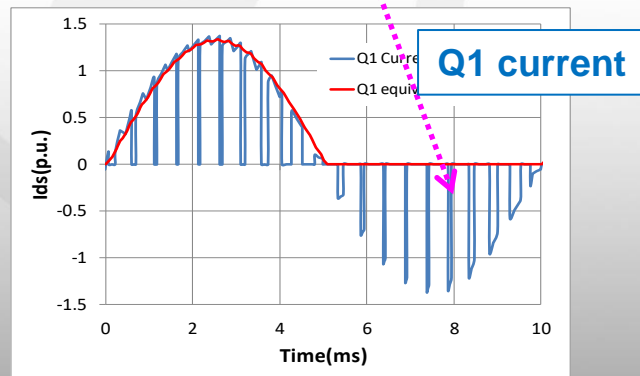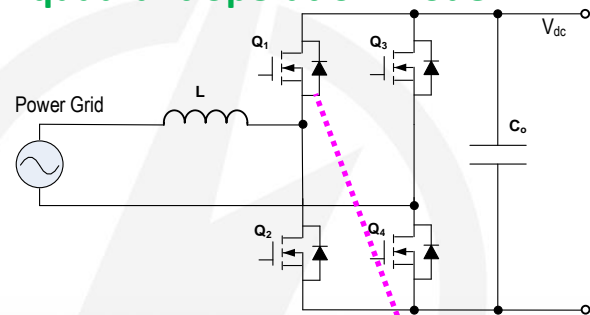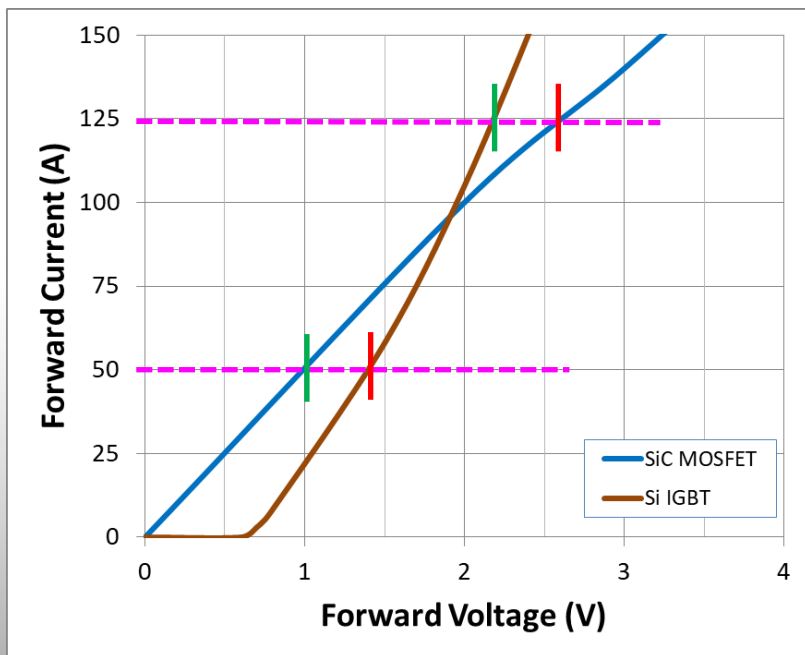1) No 0.5-1.0V knee voltage; 2) Has “body diode”; 3) 3rd quadrant operation mode.



SiC MOSFET Advantages over Si IGBT: Switching

❑ Low switching loss:


MOSFET (unipolar) vs IGBT (bipolar)- fundamental difference;

❑ Switch loss less increase at elevated temperatures:

For 1000V SiC MOSFET, $E_{sw}@25^{\circ}\text{C} = E_{sw}@150^{\circ}\text{C}$



❑ Low reverse recovery for the body diode:

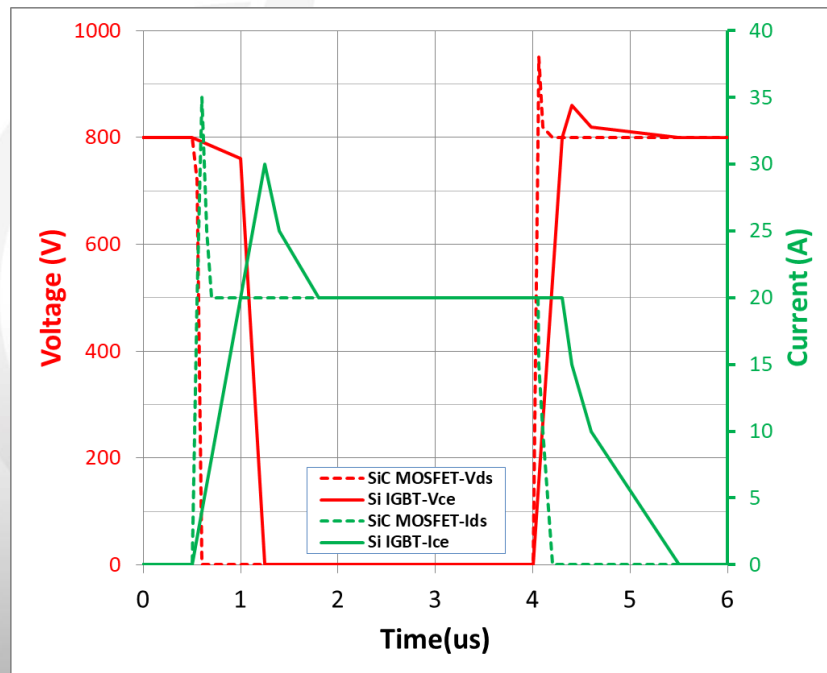Silicon PiN diode has significant reverse recovery which has reverse recovery loss and also adds more turn on loss.




Typical switching waveforms

Overcurrent/Short Circuit Fault

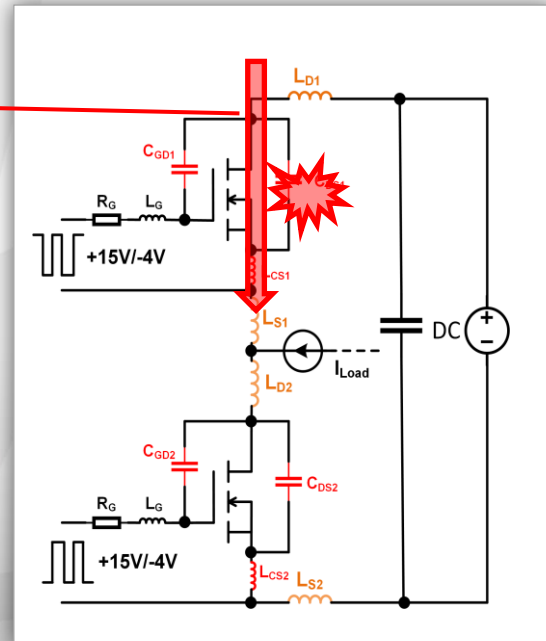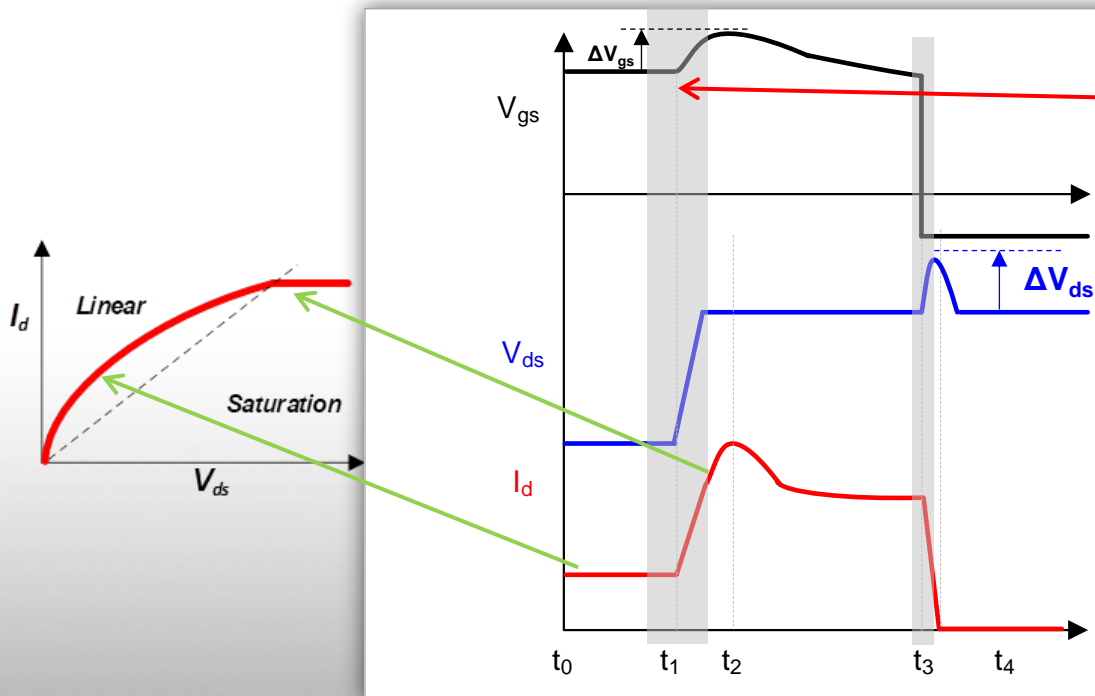

Short circuit happens at t_1 :

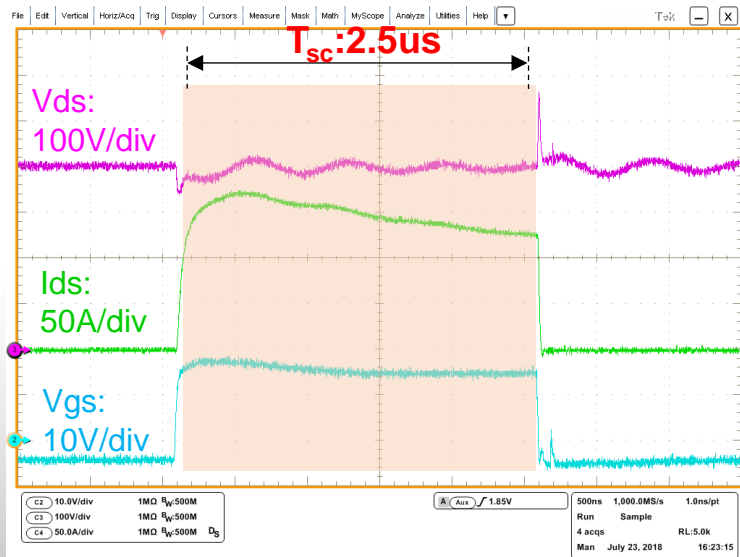
Overcurrent/Short Circuit Fault Mechanism: **Thermal limitation**



- The short circuit withstand time t_{sc} is determined by the **critical energy**
 - minimal dissipated energy leading to device failure for one short circuit pulse

$$E_c = \int_{t_1}^{t_3} V_{ds} \cdot I_d \cdot dt$$
 - V_{ds} is the DC link voltage, I_d will be the device saturation current.
- SiC MOSFET short circuit withstand time is shorter than IGBT due to smaller chip size, less thermal capacity.

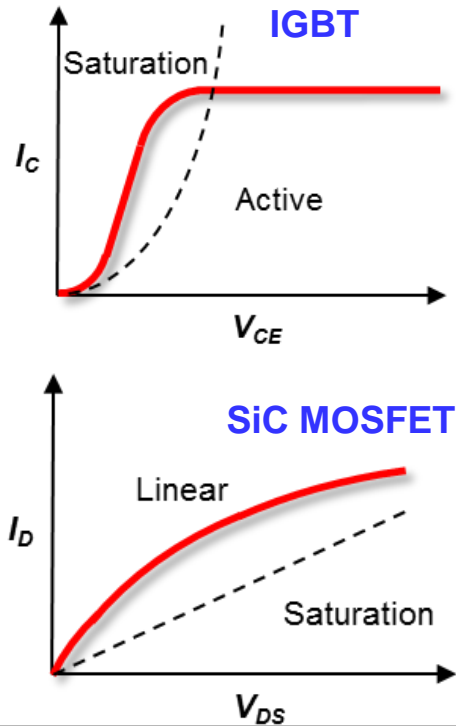Overcurrent/Short Circuit Fault Mechanism: **Thermal limitation**





- **IGBT self-limits the current increase with lower saturation current**
 - shape transient from saturation region to active region, collector current is limited to a constant value in active region
- **SiC MOSFET has large linear region with high saturation current**
 - In the case of SiC, I_d continues to increase with increase in V_{ds} , eventually resulting in faster breakdown
- **For same rated current & voltage, IGBT reaches active region for significantly lower VCE as compared to SiC MOSFET**

Question: From thermal limitation point of view, what is the typical SiC MOSFET short circuit withstand time (for example 1200V MOSFET in TO247 package used for 800V dc bus)?

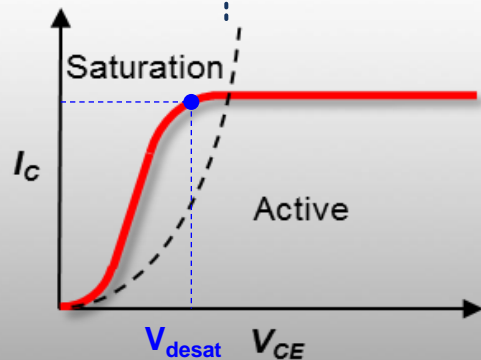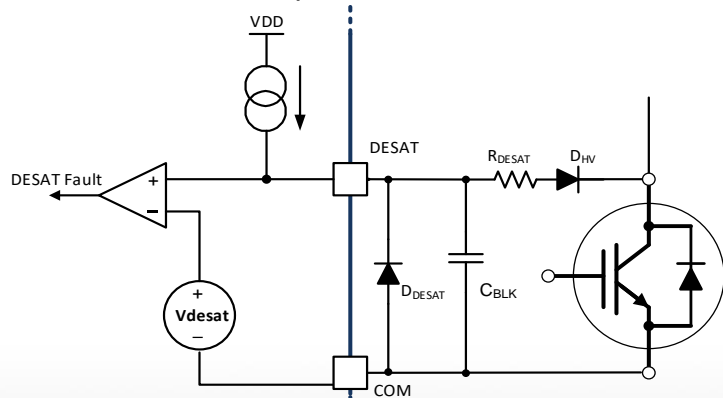- A) <1us
- B) 1-3us
- C) 3-10us
- D) >10us

Answer: B) 1-3us (under typical V_{ds} and recommended V_{gs} conditions)

Overcurrent/Short Circuit Protection Method: **DESAT**



- Desaturation circuit detects the V_{ds} of MOSFET or V_{ce} of IGBT, protection is triggered when detected voltage is above pre-set reference voltage
- Blanking time is needed to prevent false trigger during switching turn on transients


$$t_{DS_BLK} = \frac{V_{DESAT} \times C_{BLK}}{I_{CHG}}$$

- Real detection voltage on the device terminals is lower than pre-set reference voltage

$$V_{DS_DET} = V_{desat} - V_{D_{HV}} - I_{desat} \times R_{desat}$$


- DESAT threshold voltage varies between different devices due to the output characteristics, especially IGBT and SiC MOSFET

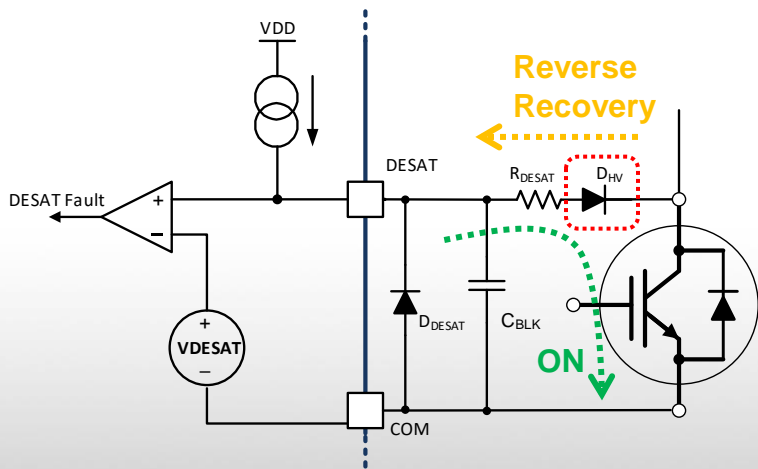Overcurrent/Short Circuit Protection Method: **DESAT**




- Advantages
 - Simple circuits
 - low loss
 - Programmable protection time
- Challenges of DESAT protection method
 - High voltage fast reverse recovery diodes add cost
 - Multiple high voltage diodes are needed to share blocking voltage for above 1200V applications
 - Blanking time makes the protection time too long for SiC MOSFET
 - Parallel diode D_{desat} is needed to prevent the negative voltage on DESAT pin
 - Indirect current sensing can be challenging for SiC MOSFET

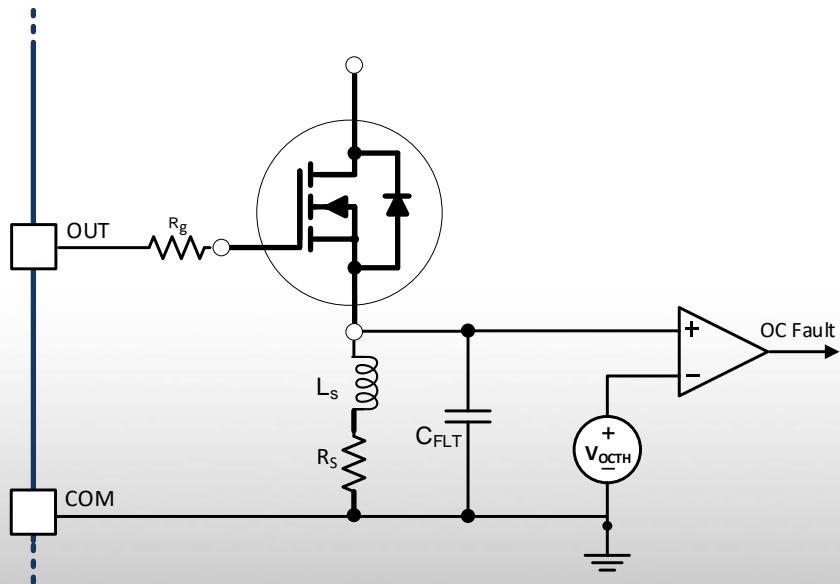Overcurrent/Short Circuit Protection Method: **Shunt Resistor**




- **Advantages**
 - Accurate for both AC and DC
 - Fast protection speed
 - Low cost
- **Challenges of shunt resistor**
 - High power loss in high power applications
 - Weak noise immunity due to gate loop noise caused by parasitic inductance of shunt resistor and PCB trace

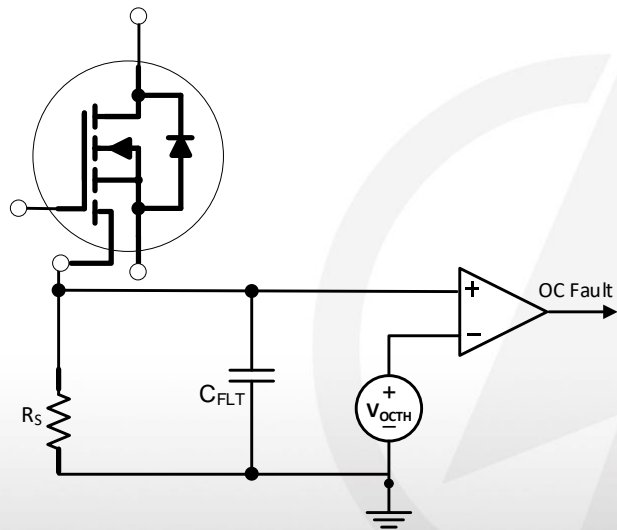Overcurrent/Short Circuit Protection Method: SenseFET / Current Mirror



- SenseFET / Current mirror is used to scale down main current, tens of mV voltage is measured on sense resistor
- Accuracy is determined by current scaling circuit and sensing resistor
- More commonly used in automotive applications

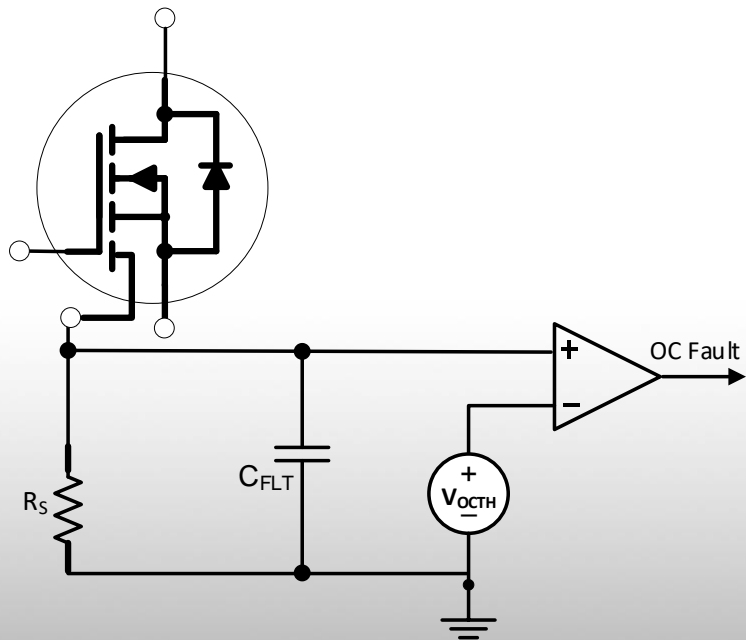Overcurrent/Short Circuit Protection Method: **SenseFET / Current Mirror**





- Advantages
 - Fastest protection speed
 - Accurate for both AC and DC
- Challenges of SenseFET / Current mirror
 - Module needs to be customized to integrate SenseFET / Current mirror
 - Higher cost

Overcurrent/Short Circuit Protection Method: Comparison

Method	DESAT	Shunt Resistor	SenseFET / Current Mirror
Response time	Slow	Fast	Fast
Accuracy	Good for IGBT; Medium for SiC MOSFET	High, depends on shunt quality 3% without calibration, 1% with calibration	Medium, depends on scaling accuracy and external resistor selection
Losses	Negligible	High and depends on R_s value	Low
Cost	Medium	Low	High



- Shunt Resistor method is not desired for high power applications due to high loss;
- SenseFET/Current Mirror works best for SiC MOSFET for its low noise and fast speed, but senseFET is not always available;
- Desat method works good for IGBT, but may have limitations for SiC MOSFET, especially for the drivers designed fro IGBT.

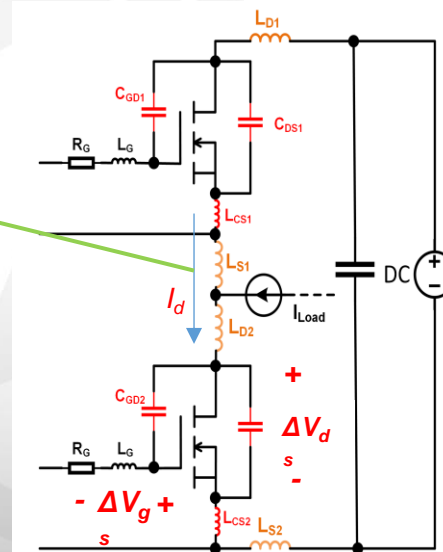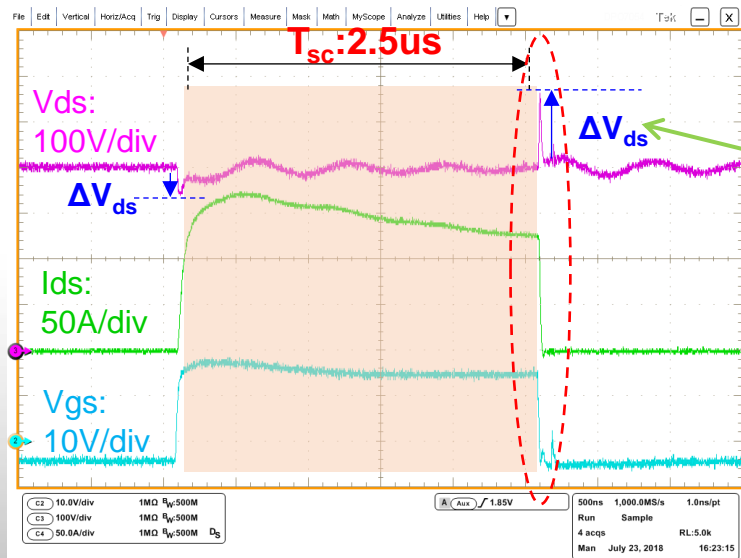Overcurrent/Short Circuit Safe Turn-off: **Avalanche limitation**



- Voltage and avalanche limit:** Device avalanche can be caused by the overshoot voltage on V_{ds}

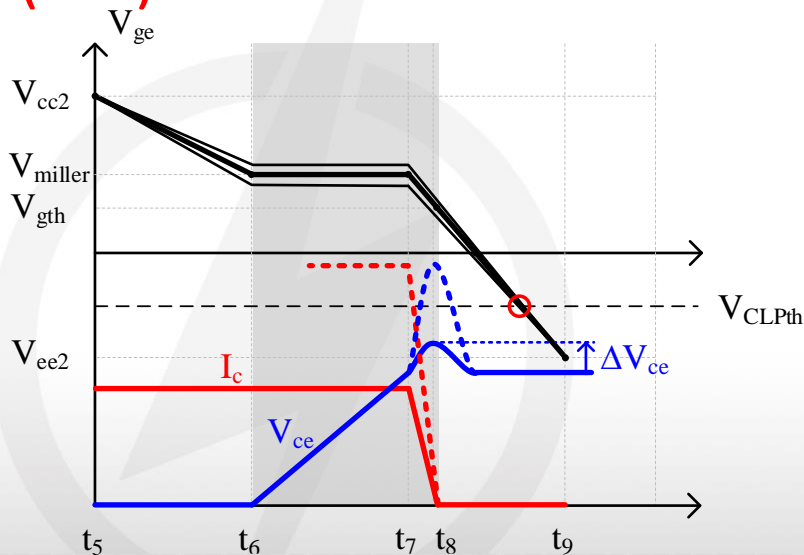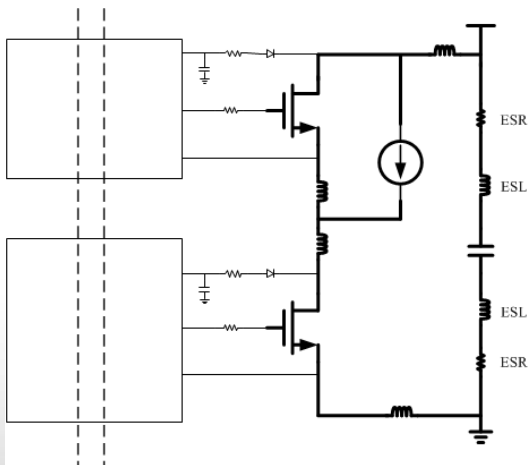SiC MOSFET Protection: **Soft Turn-Off (STO) & 2L Turn-Off**





- There are parasitic inductances in the power loop.
- Parasitic inductances together with di/dt cause voltage spikes.
- **The di/dt rate is much higher under short circuit fault** that a preventive turn-off measure needs to be taken in order to limit the loop inductance induced voltage spike.
- Effectively, there are two ways to slow down the turn-off process: reduce di or extend dt .


Short-Circuit Protection: **Hardware Validation**

Evaluation Hardware

Schematic for Double-Pulse Test Setup

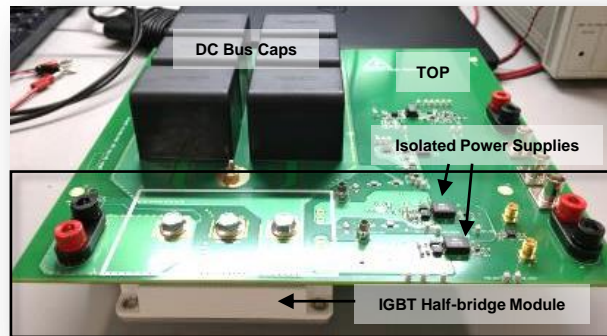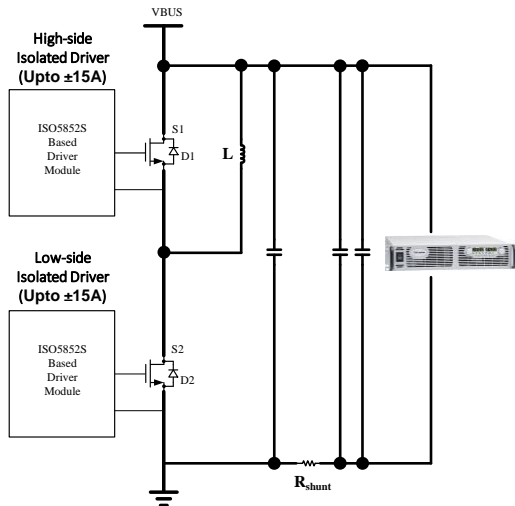


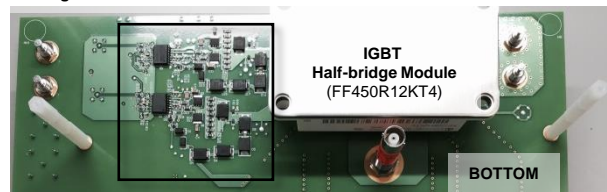Isolated Half-bridge Drive Stage
using ISO5852S-Q1 + 15A Buffer Driver




Short Circuit Protection for SiC MOSFETs: **with or without Soft turn-off**

VDS(100V/div), IC(1kA/div),
VGS(10V/div)

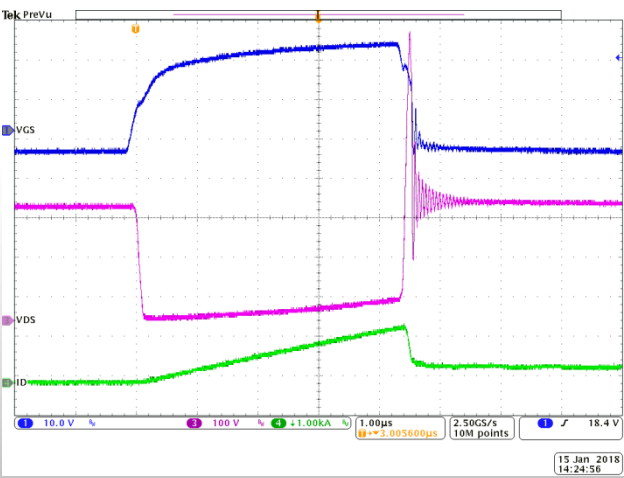


Hard Turn-off

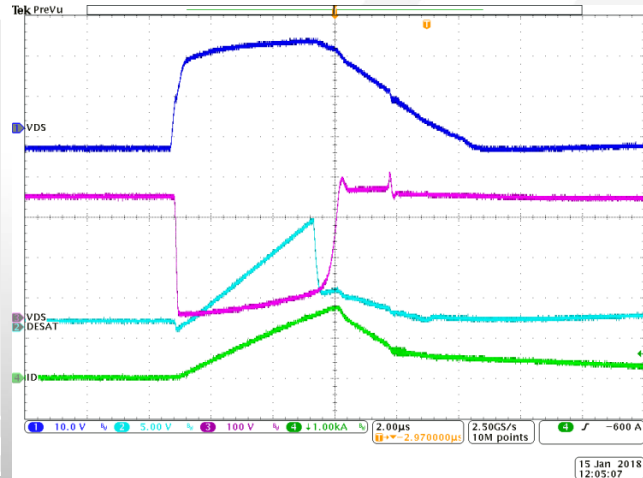VDS(100V/div), IC(1kA/div),
VGS(10V/div), VDESAT(5V/div)



Soft Turn-off for Hard SC

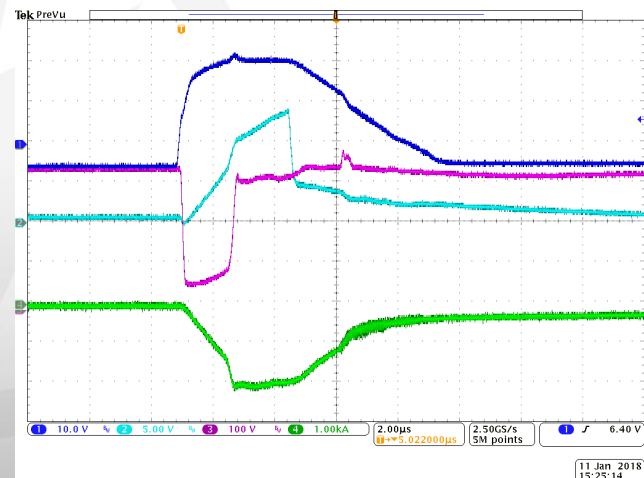VDS(100V/div), IC(1kA/div),
VGS(10V/div), VDESAT(5V/div)



Soft Turn-off for SC under Load

Summary and key takeaways

- ❑ SiC MOSFET has superior performance than Si IGBTs for both conduction and switching;
- ❑ There are mainly three methods for the fault current sensing and then protection, sense FET is good for SiC MOSFETs but cost is high;
- ❑ De-sat method used for Si IGBT needs to be re-designed for SiC MOSFETs;
- ❑ Soft/two level turn off is also desired for turning off SiC MOSFET under short circuit.