

EOS and ESD on ADC

TI Precision Labs – ADCs

Presented by Alex Smith

Prepared by Dale Li

ESD vs. EOS – What's the Difference?

ESD

- Electrostatic discharge
- Short duration event (1-100ns)
- High voltage (kV)
- Fast edges
- Both “in-circuit” and “out-of-circuit”


EOS

- Electrical overstress
- Longer duration event
 - Milliseconds or more
 - Can be continuous
- Lower voltage
 - May be just beyond absolute maximum ratings
- “In-circuit” event only

EOS from Fault or Overdriven


Fault Conditions

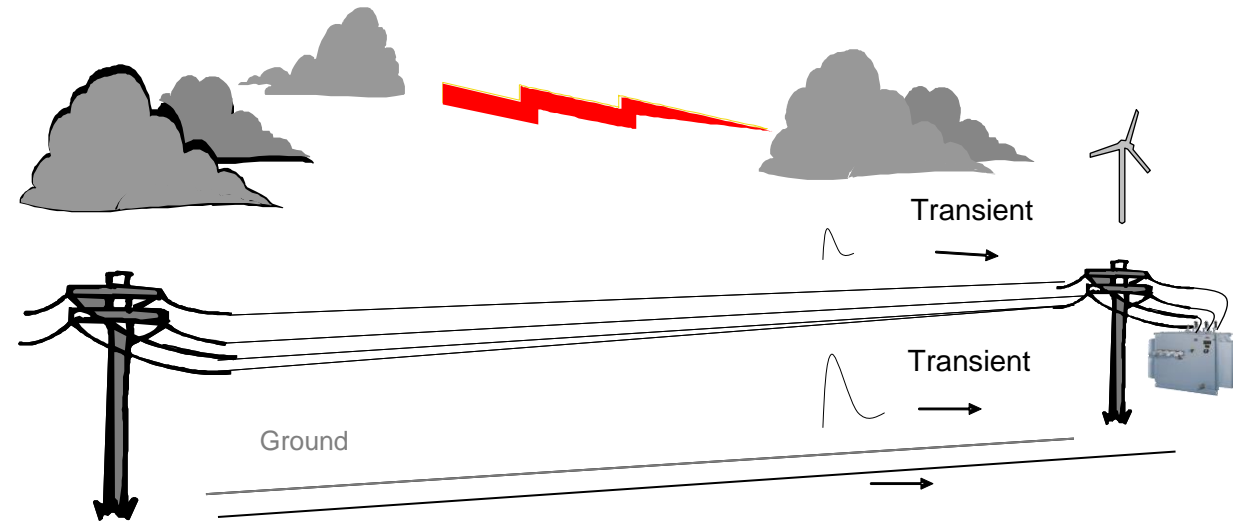- ✓ Harsh electrical environment
- ✓ High voltage circuit in the system
- ✓ Improper power up sequencing
- ✓ Hot-swap connection and disconnection
- ✓ Loss of power supply but input signal is applied
- ✓ Apply bipolar signal to unipolar input ADC
- ✓ Miswiring
- ✓ Other conditions violating the absolute maximum specifications




Internal Clamp/Protection on Data Converters


1. Input Steering diodes:

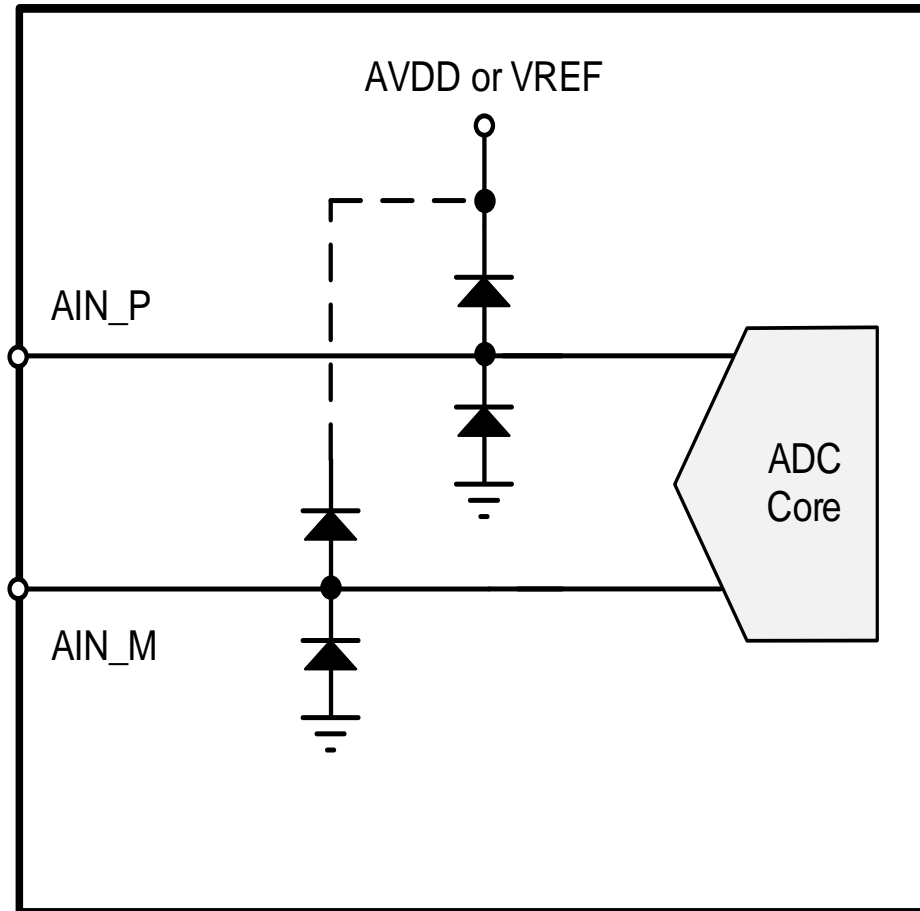

2. Back-to-Back Zener diode:

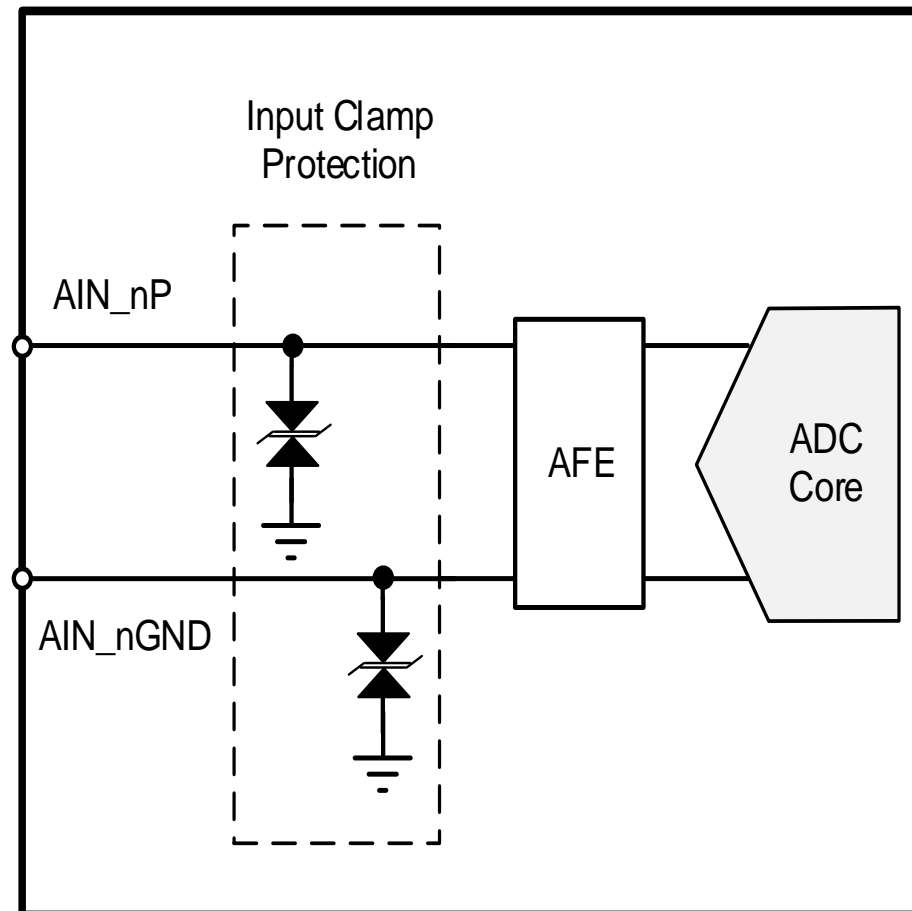


3. SCR-Based input:

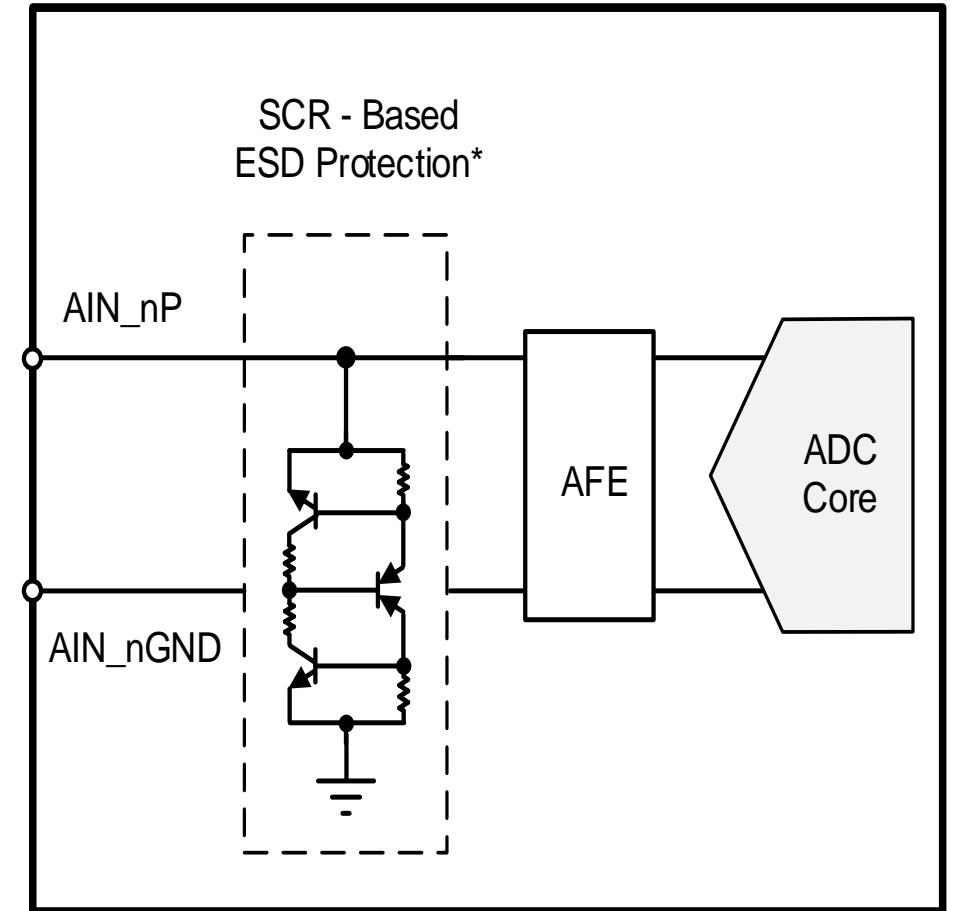



*Bi-directional SCR example

SCR-Based ESD Structure and Latch-up

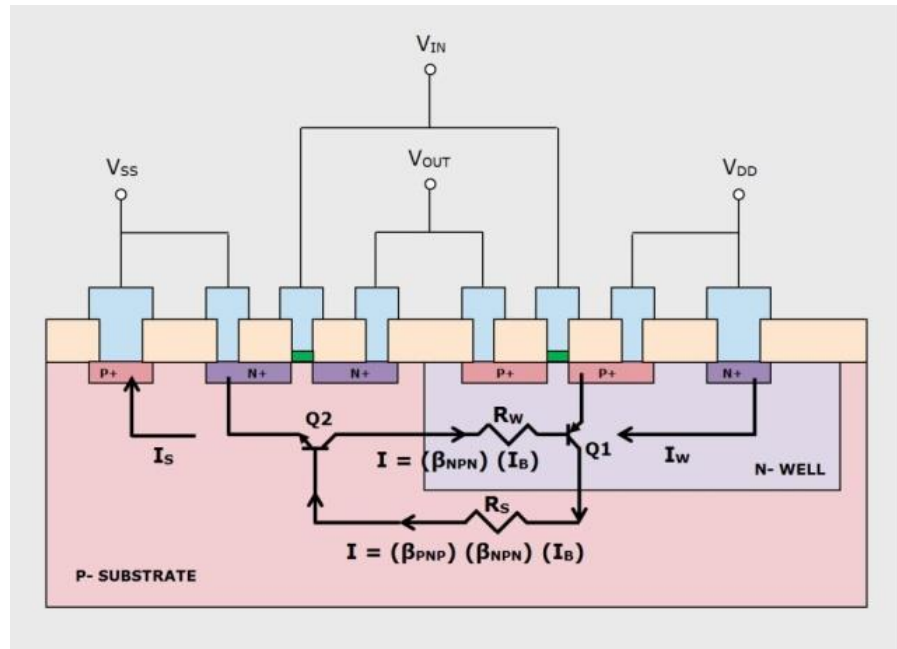


Cross section of typical SCR design structure

Equivalent circuit of SCR

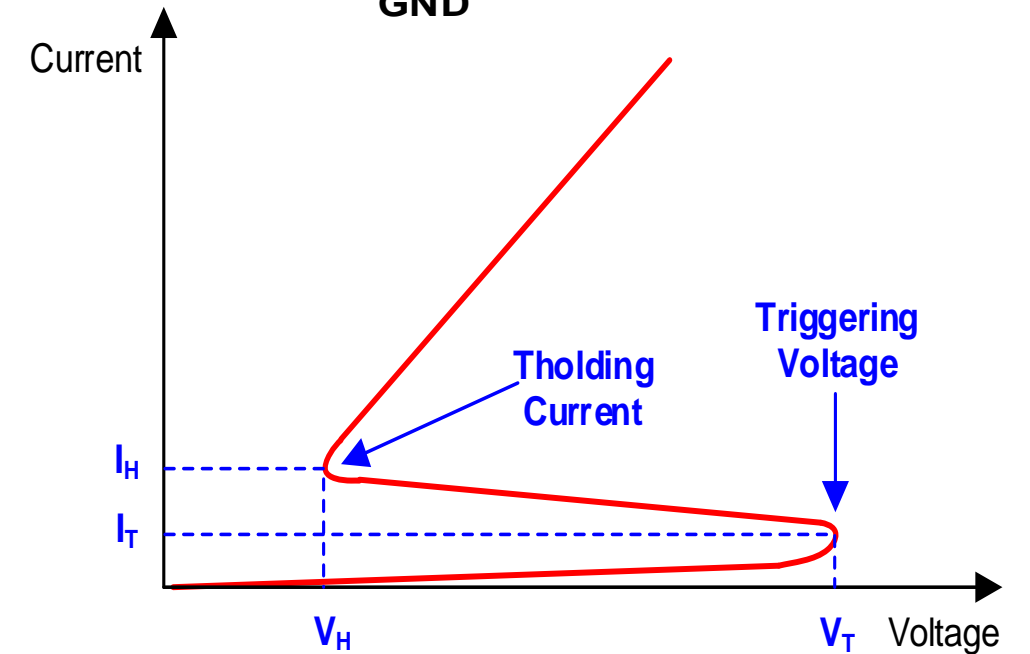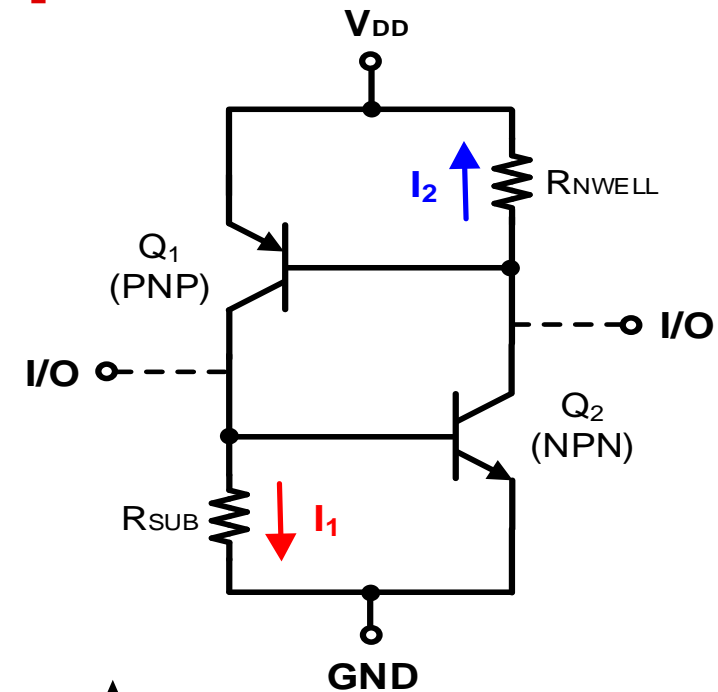

- **SCR** (silicon controlled rectifier) is a parasitic structure. Overshoot and undershoot outside the normal operating voltage and current levels can cause Latch-up and damage the device.
- **Trigger Latch-up:**
 - ✓ Applied voltage > V_H and applied current > I_H
- **Terminate Latch-up state:**
 - ✓ A latch-up remains even after applied signal has been removed and requires a **power supply shut down** to remove the low impedance path.

Why use SCR-Based ESD protection

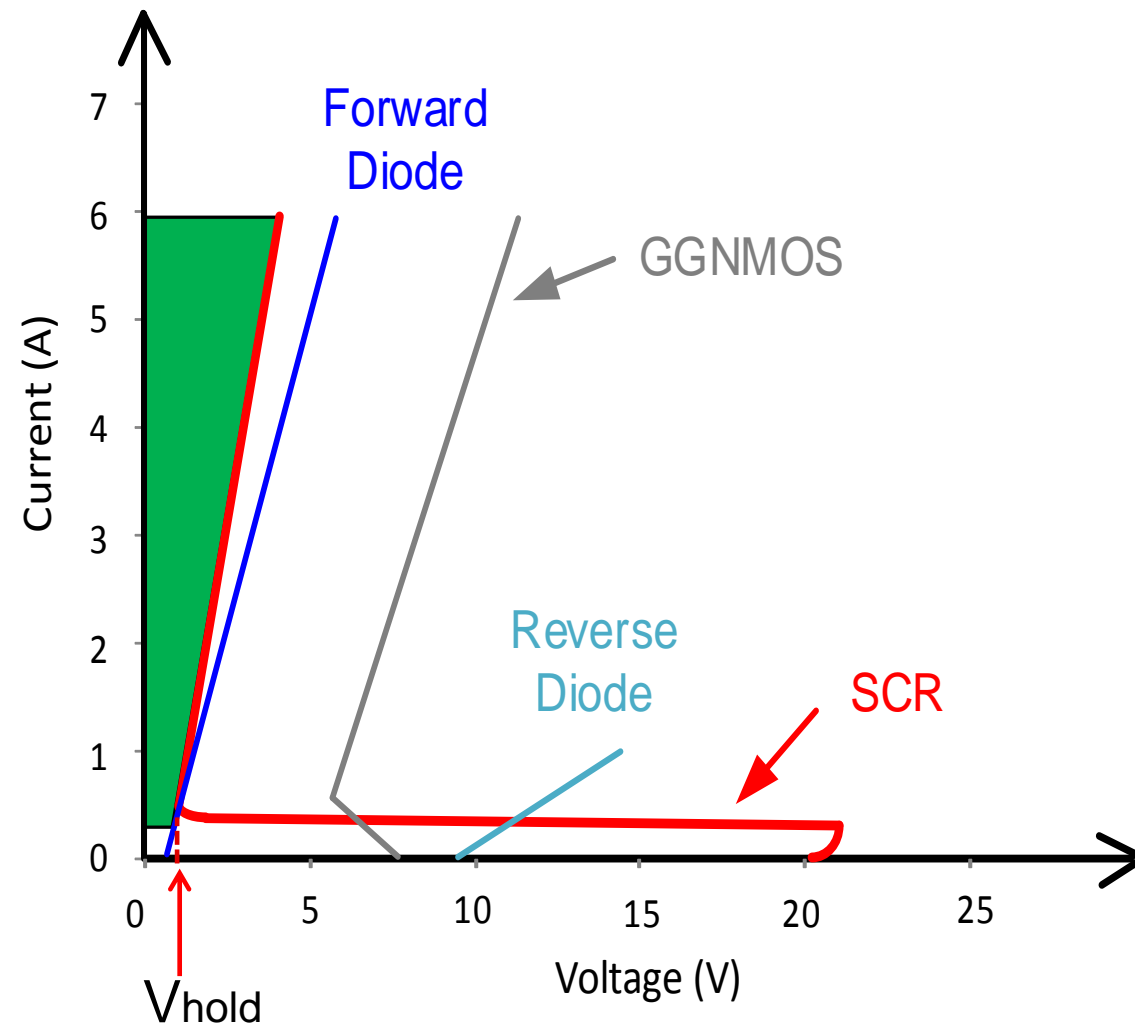


- Input Signal Voltage > Power Supply.
- SCR is used as effective input ESD protection element to sustain a higher ESD level within a smaller layout area because:
 - Lower holding voltage
 - Significantly lower power dissipation
 - Robust ESD protection


* Electrostatic Discharge Protection Circuit for High-Speed Mixed-Signal Circuits by Hossein Sarbishaei.

Input Diode to REF/AVDD

ADS8860 Input Stage


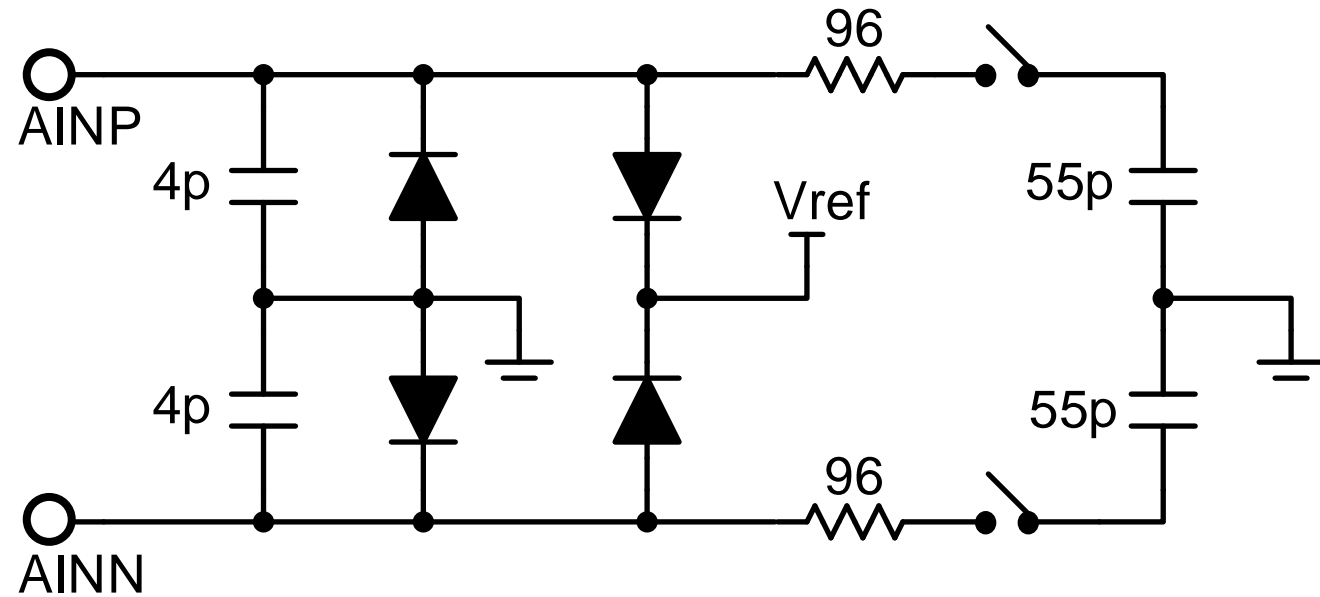


ADS9224R Input Stage

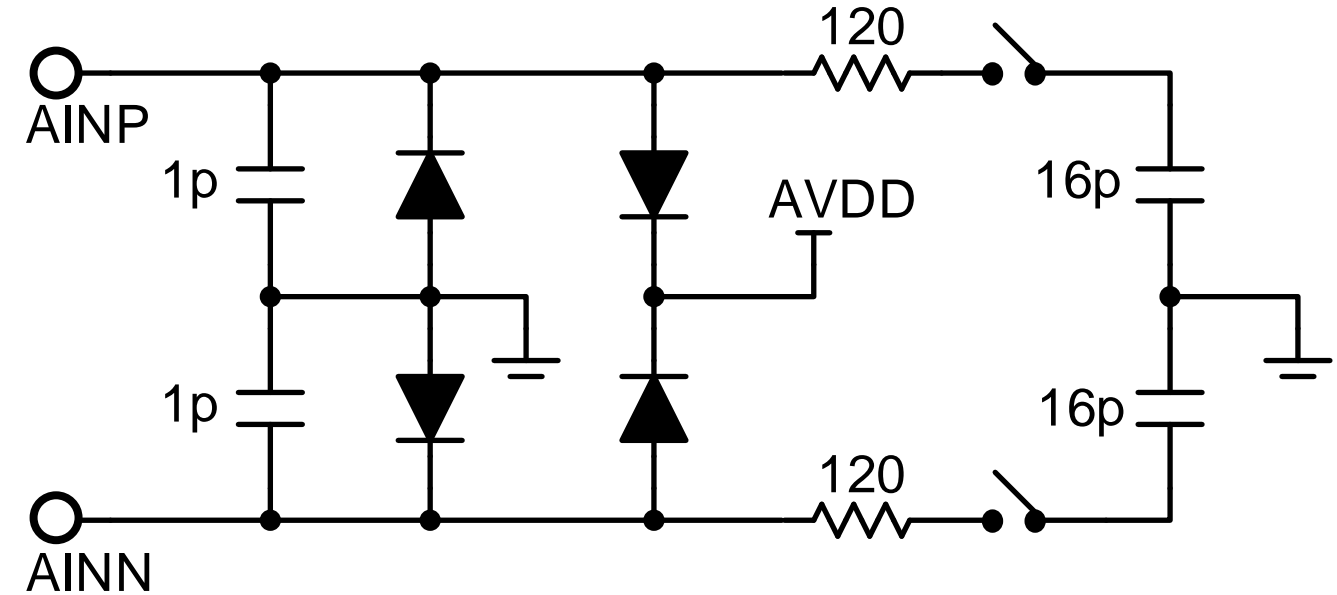

- Internal diodes are connected to REF: ADS8860, ADS9110, ADS8900B...
- Internal diodes are connected to AVDD: ADS9224R, ADS8168...
- Absolute Maximum Input Range:
 - Analog input voltage is limited to -0.3V to REF+0.3V (or AVDD+0.3V)
 - Input current is generally limited to -10mA to 10mA

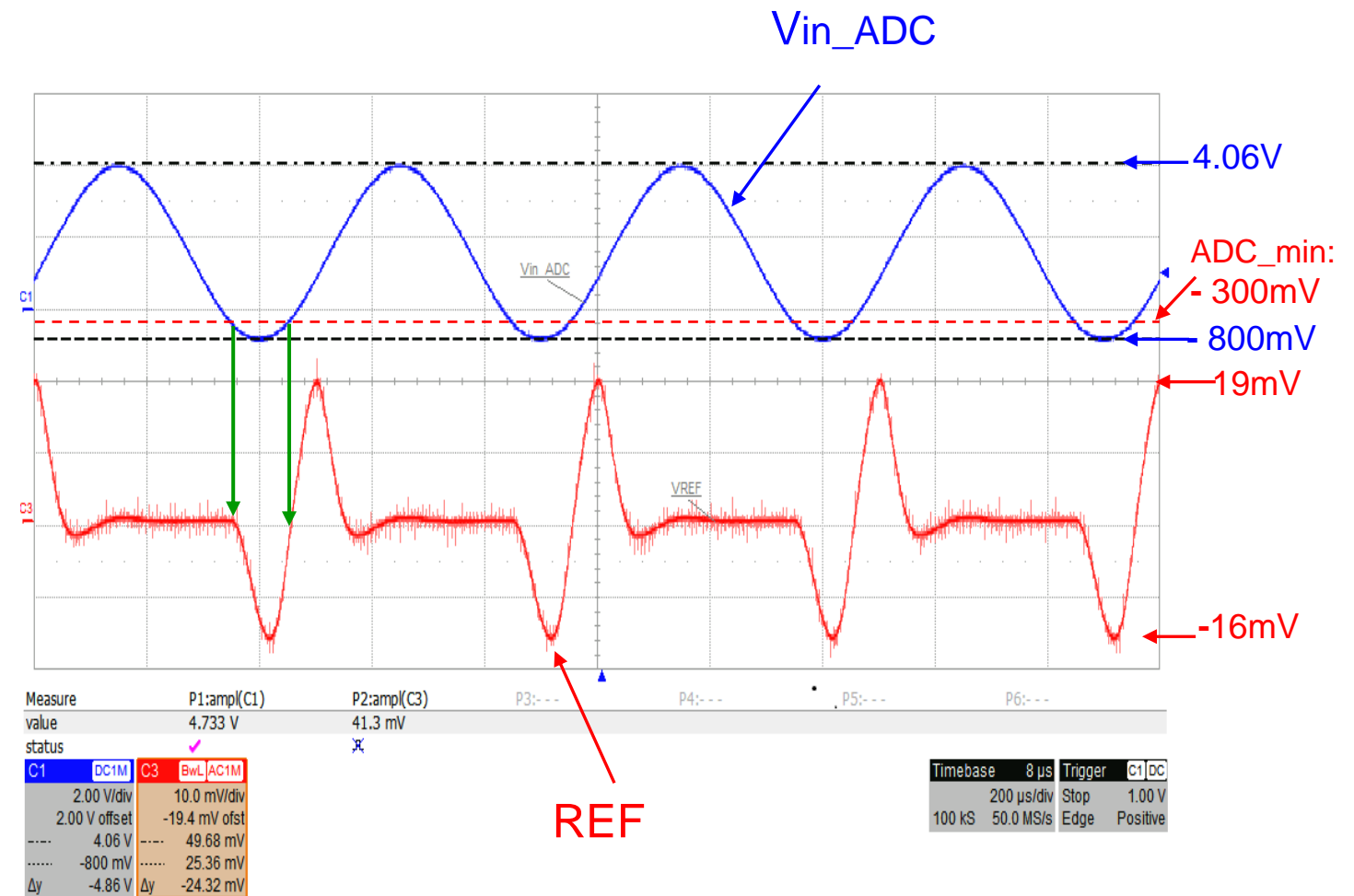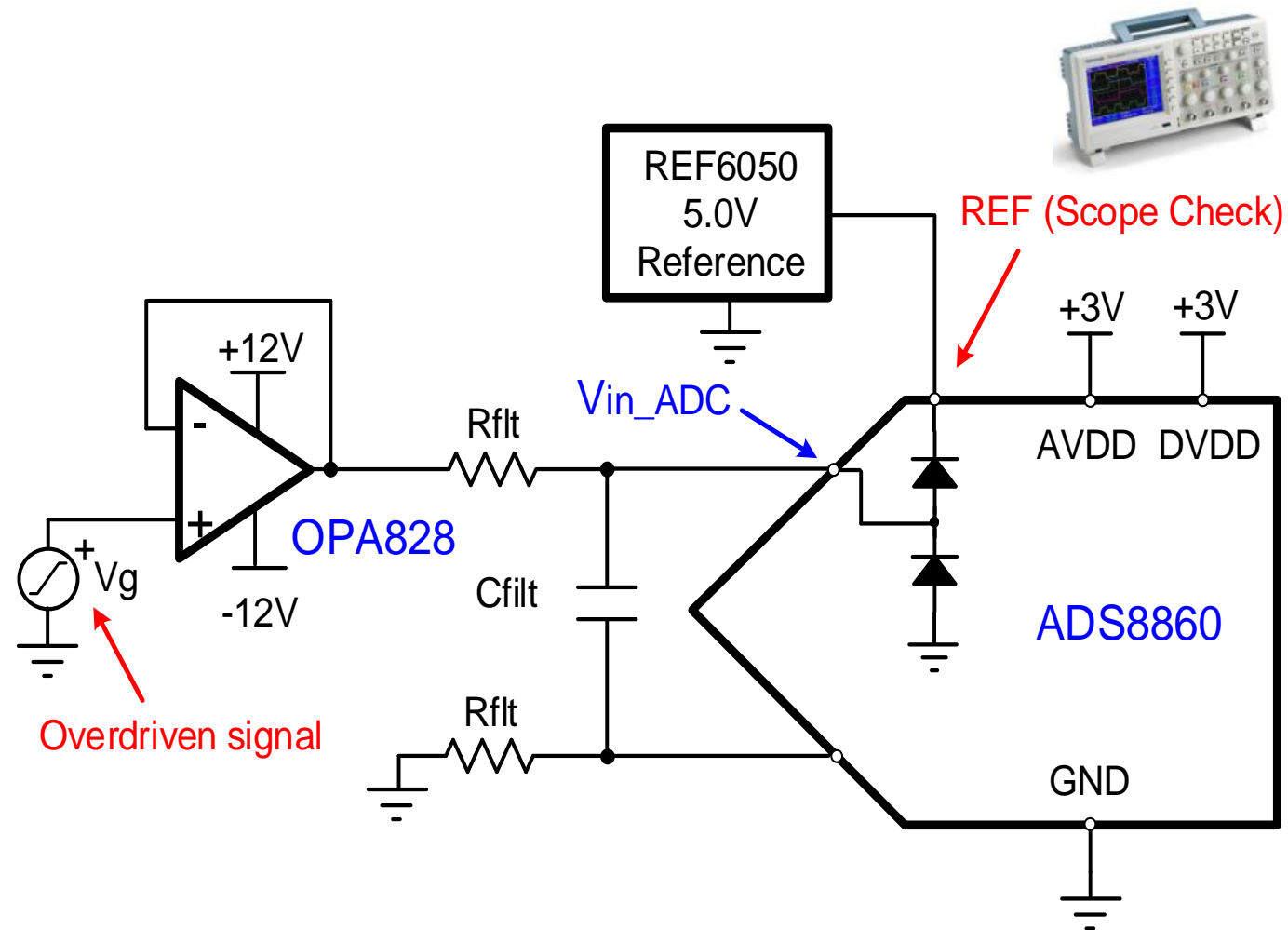
Input ESD Diode turns on and Impacts Voltage Reference




- When input signal is overdriven, a disturbance is found on REF signal (or AVDD) which can degrade the performance if the REF (or AVDD) is shared.
- The higher overdriven signal, the worse disturbance impact.

Input Protection on ADC with AFE

ADS8588S Input Stage:

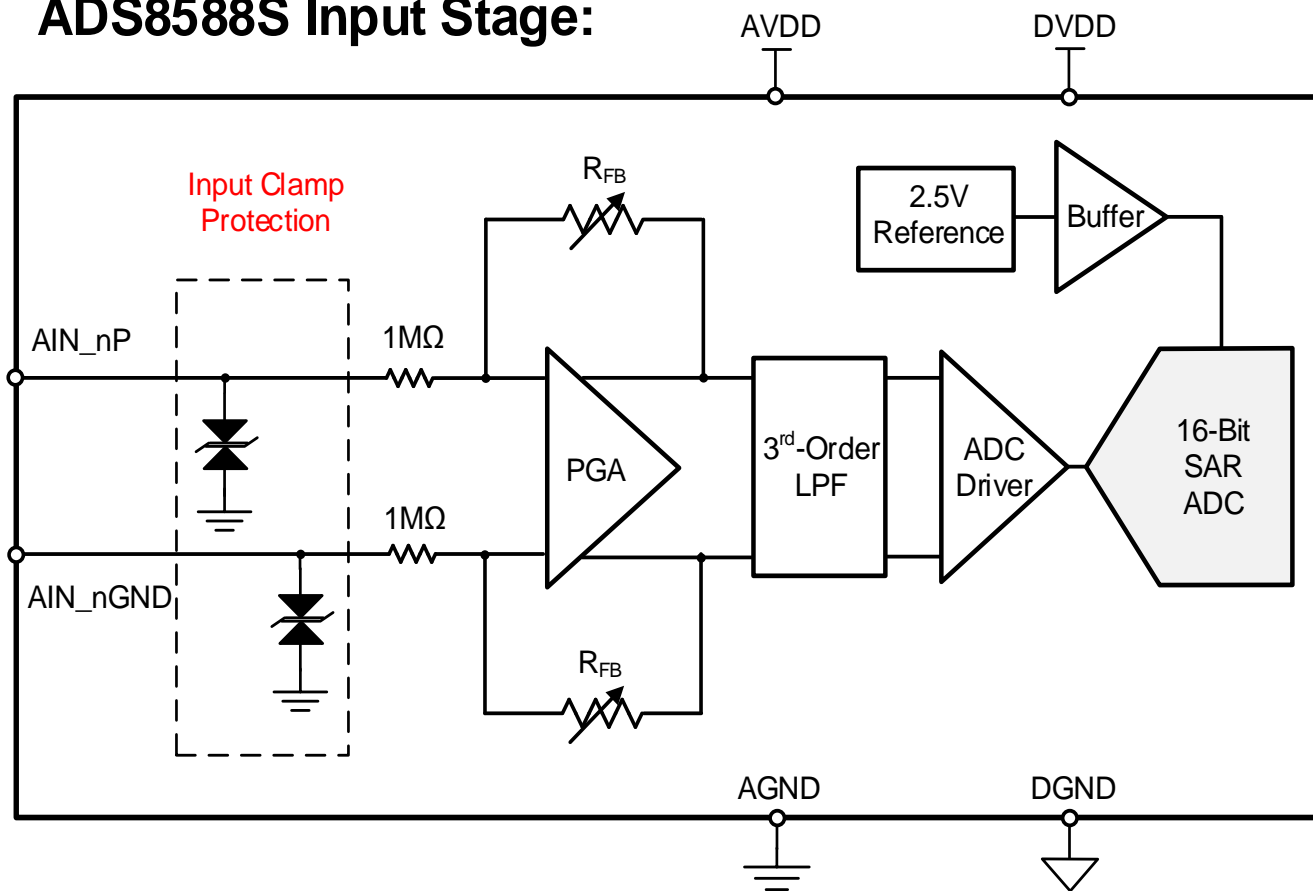

ADS8688/81 Input Stage:

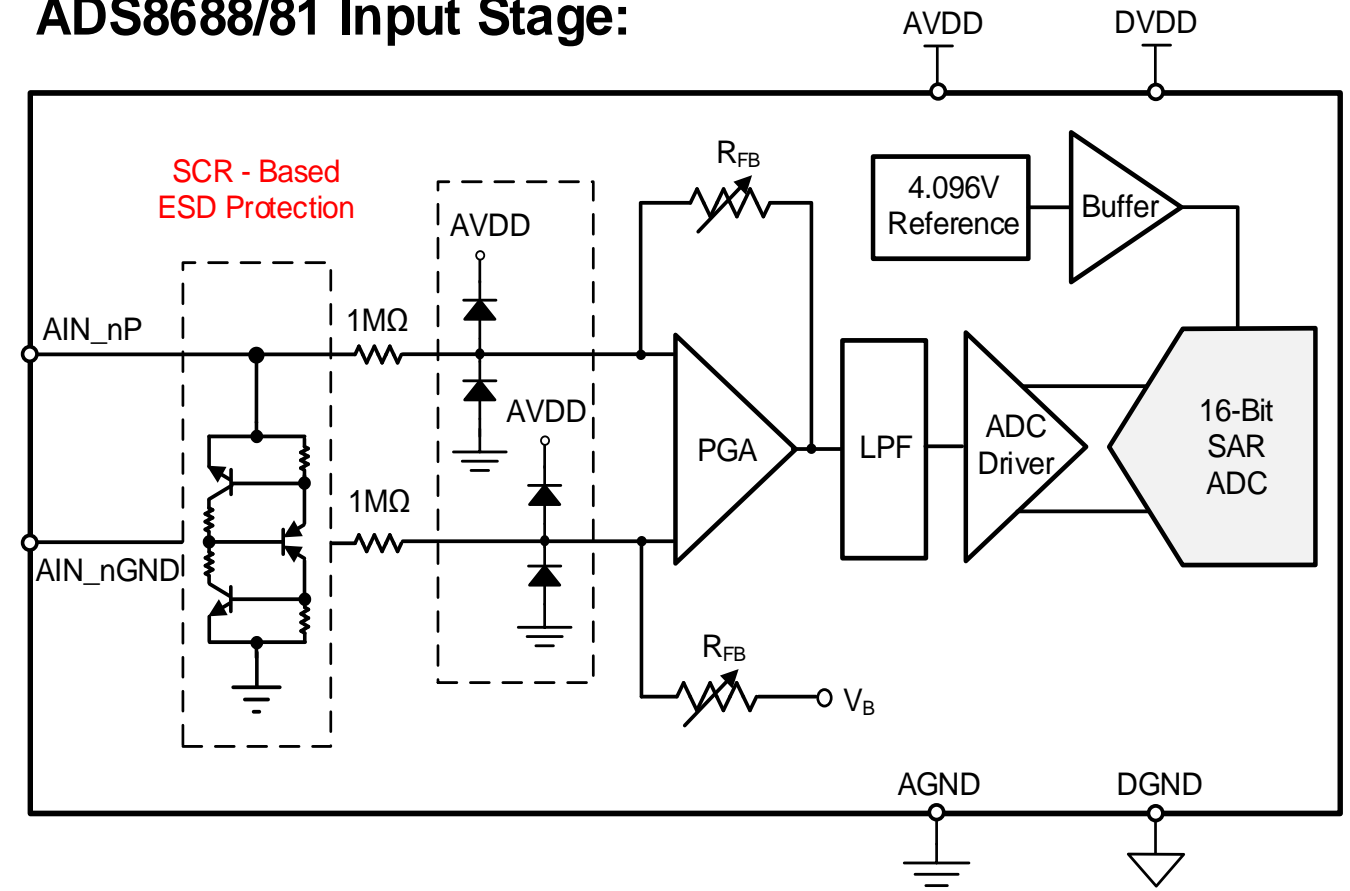


- Typically 5V supply voltage and $\pm 12V$ input range, so ESD diode to supply will not work
- Clamp is implemented with back-to-back Zener diodes or SCR input.
- ABS MAX Input voltage limit: $\pm 15V$ on ADS8588S, and $\pm 20V$ on ADS8681/8688
- ABS MAX Input current Max Limit = $\pm 10mA$

Thanks for your time!
Please try the quiz.

Questions: EOS and ESD on ADC

1. For the circuit shown below, what kind of internal ESD structure is **NOT** practical?

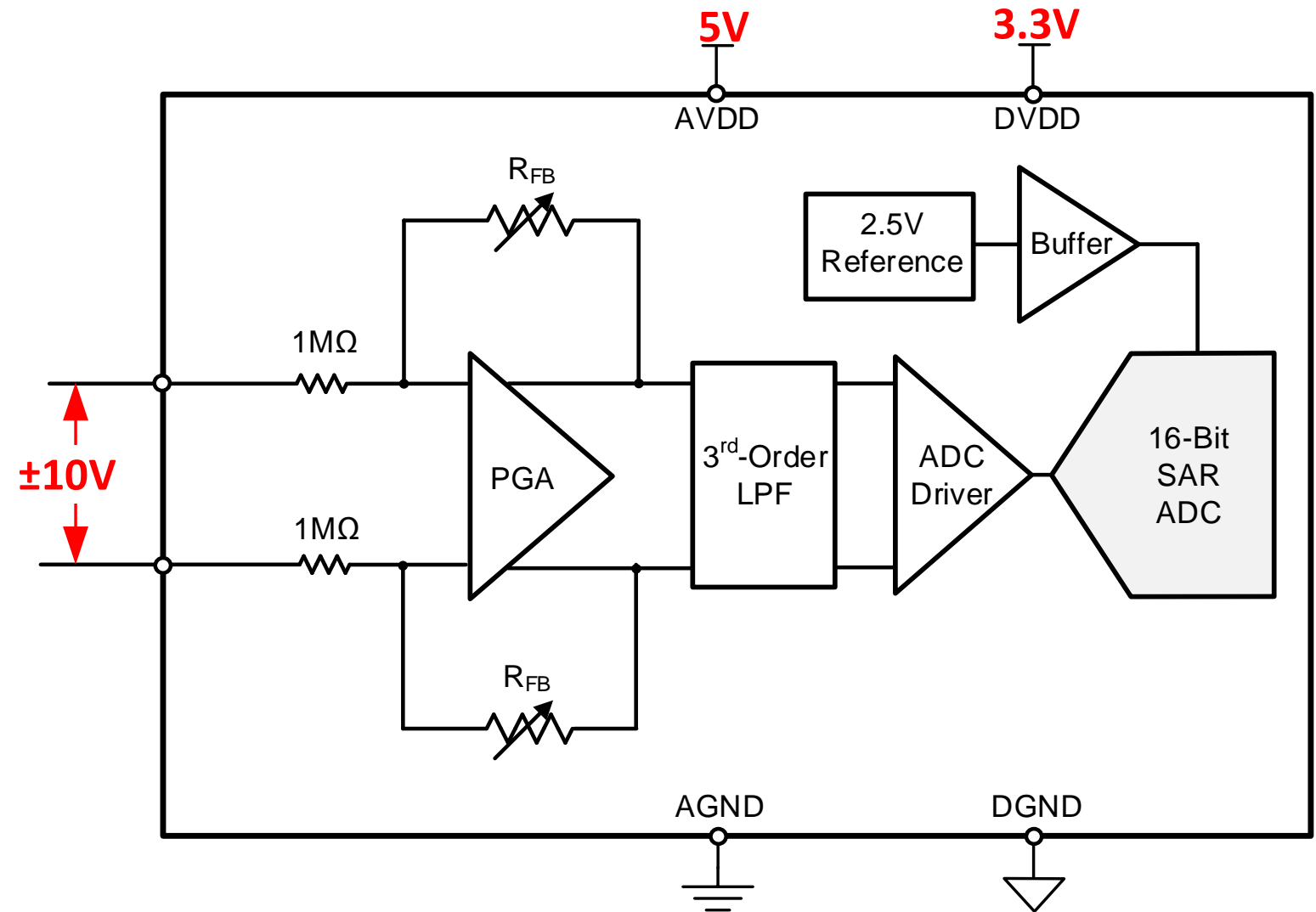- a. Input ESD steering diodes
- b. Back-to-back Zener diodes
- c. SCR type ESD structure



Questions: EOS and ESD on ADC


2. (T/F) The internal ESD protection structures are designed primarily to protect the device during assembly and test (i.e. out of circuit events).
 - a. True
 - b. False

3. Which type of ESD structure will trigger on and remain on until power is cycled?
 - a. Input ESD steering diodes
 - b. Back-to-back Zener diodes
 - c. SCR type ESD structure

Questions: EOS and ESD on ADC

4. Which of the following does **NOT** apply to ESD?
- a. High voltage (kV)
 - b. Fast edges
 - c. Long duration event of milliseconds or more.
 - d. Both “in-circuit” and “out-of-circuit”

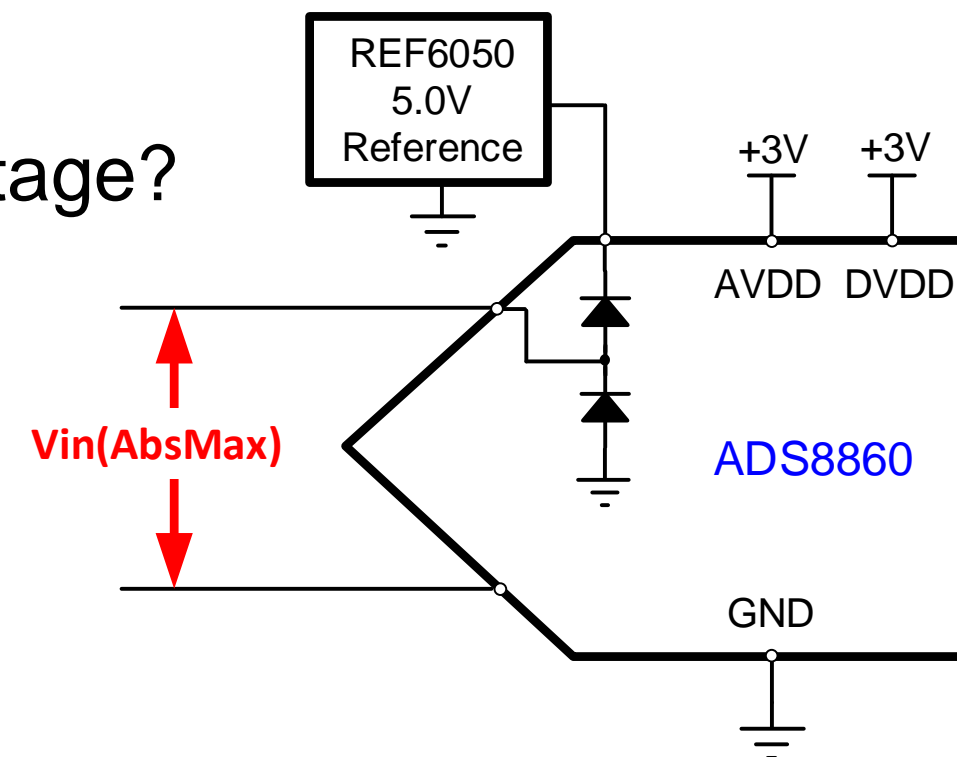5. For the circuit below, what is the maximum input voltage?
- a. 5.0V
 - b. 5.3V
 - c. 7V
 - d. 12V



Thanks for your time!



© Copyright 2019 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)

