

Linear OPAMP Characterization: Common Mode Rejection Ratio


Presented by: Joseph Serritella

Prepared by: Joseph Serritella, Daryl Hiser, Ray Ochotorena, Mark Irwin

OPAMP verification

OPAMP electrical characterization:

- Characterizing the electrical behavior of an integrated circuit is critical during application troubleshooting
 - Non-conformances can be identified by comprehending device-level characteristics in addition to system performance
- OPAMP electrical characterization series will review the following topics:
 - Voltage offset (V_{OS})
 - V_{CM} / **Common Mode Rejection Ratio (CMRR)**
 - Power Supply Rejection ratio (PSRR)
 - Output swing
 - Quiescent current
 - Open loop gain (A_{OL})

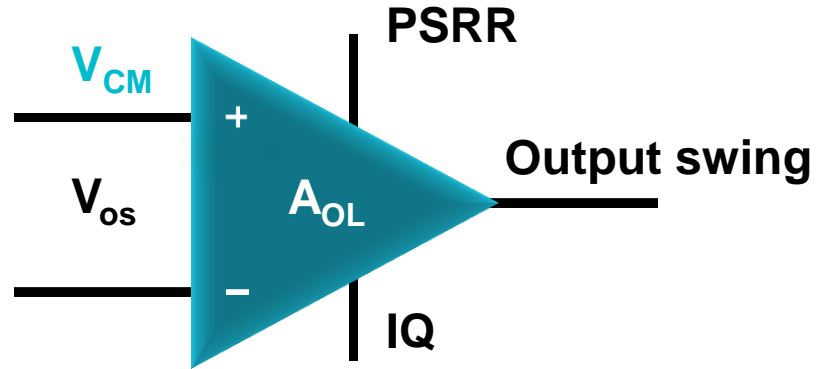

Prerequisites

Electrical characterization: CMRR

- Common mode rejection ratio measurements methods are reviewed
- Following prerequisites are recommended prior to proceeding though the handbook

Prerequisites:

TI-Precision Labs (TIPL) courses:

CMRR: TIPL - Op Amps: Common Mode Rejection

ti.com/training-opamps-vos

Pocket reference:

Training: Analog Engineer's Pocket Reference

ti.com/analogrefguide

Application handbook:

A-B-A: Board Level Troubleshooting

ti.com/board-level-troubleshooting

Simulation tools:

Simulations are presented within the handbook. It is recommended to install TINA-TI

TINA-TI can be downloaded for free on ti.com: <http://www.ti.com/tool/tina-ti>

OPAMP test loops

Overview:

- Analyzing datasheet parameters may appear a daunting task!
- Multiple parameters can be derived easily from offset (V_{OS}).
 - PSRR, CMRR, and AOL can be calculated by monitoring shifts


False Summing Junction (FSJ):

- Accurate VOS measurements can be obtained through test loops
 - **Benefits:**
 - Simplistic
 - Stable
 - Small
 - **Disadvantages:**
 - Feedback resistor load in parallel with other added loads
 - Loop drive function of DUT V_{OS}
- Majority of DC parameters determined with 4 resistors!

Measuring VOS:

- **VOS:** differential input voltage required to force output to mid-supply
 - best measured at the summing junction (V_{SJ})
- **Output control voltage (VOC):** Calibrate the out voltage to zero volts
 - Know as offset correction factor (derived from Kirchhoff's Voltage Law):
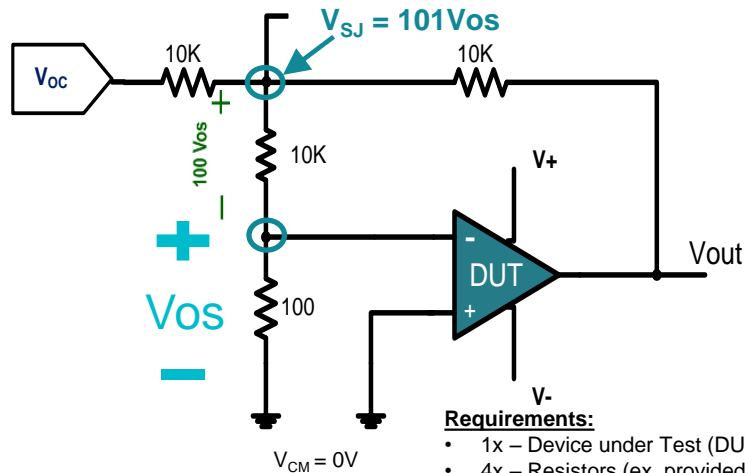
$$V_{OC} = -(V_{OUT} + VOS(302)) + 2V_{CM}$$



Requirements:

- 1x – Device under Test (DUT)
- 4x – Resistors (ex. provided)
 - Resistor values can be varied depending on device

Example:

- $V_+ = +10V$
- $V_- = -10V$
- $V_{OUT} = 0V$
- $V_{OC} = 0V$ (ideal opamp)

Results:


- $V_{SJ} = 1.01mV$
- $1.01mV = (101)V_{OS} = V_{SJ}$
 $10\mu V = V_{OS}$

Common mode rejection ratio - OPA192

Measurement preparation:

- **CMRR**: Change in V_{OS} divided by the V_{CM} change
- Review data sheet test conditions prior to evaluating **CMRR**
 - V_{CM} range of a complementary input AMP has three operation regions
 - **pMos** , **nMos** , and the **transition region**
 - Measuring CMRR in the **transition region** may impact the result

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT	
INPUT VOLTAGE						
V_{CM}	Common-mode voltage range	(V-) - 0.1		(V+) + 0.1	V	
CMRR	Common-mode rejection ratio	(V-) - 0.1 V < V_{CM} < (V+) - 3 V		94	110	dB
			$T_A = -40^{\circ}\text{C}$ to $+125^{\circ}\text{C}$	90	104	
		(V+) - 1.5 V < V_{CM} < (V+)		100	120	
			$T_A = -40^{\circ}\text{C}$ to $+125^{\circ}\text{C}$	84	100	
	(V+) - 3 V < V_{CM} < (V+) - 1.5 V	See <i>Typical Characteristics</i>				

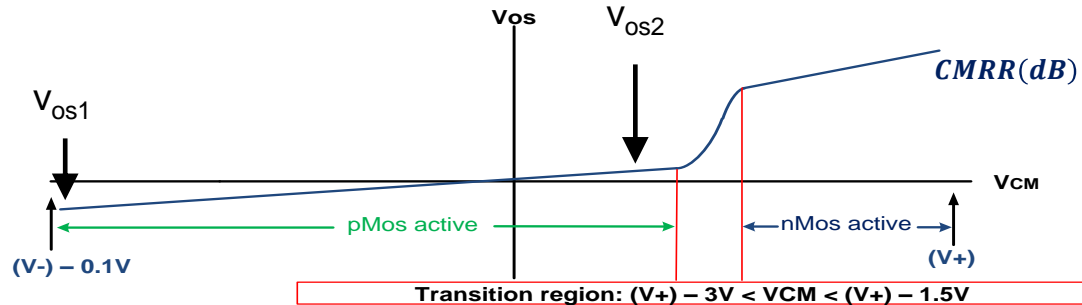

$$CMRR\left(\frac{V}{V}\right) = \left(\left|\frac{\Delta V_{OS}}{\Delta V_{CM}}\right|\right)$$


$$CMRR(dB) = -20 \times LOG\left(CMRR\left(\frac{V}{V}\right)\right)$$

Figure 4: V_{CM} versus V_{OS} graph highlighting operating regions

Common mode rejection ratio

Bench setup and measurements:

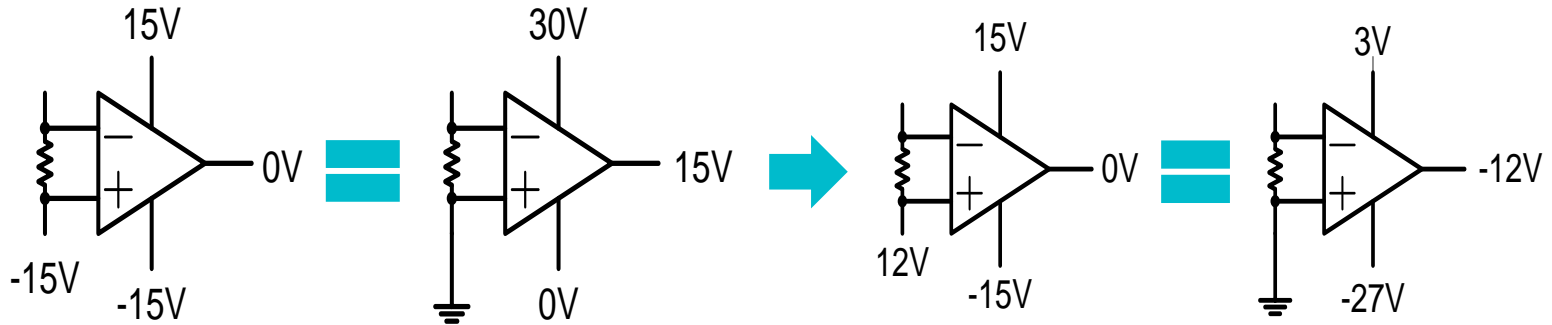- Shifting supplies & output is equivalent to moving V_{CM}



Offset voltage (1):

- DUT:** OPA192IDGK
- $V_+ = +30V$
- $V_- = 0V$
- $V_{OUT1} = 15V$
- $V_{CM1} = -15V$

Offset voltage (2):

- DUT:** OPA192IDGK
- $V_+ = +3V$
- $V_- = -27V$
- $V_{OUT2} = -12V$
- $V_{CM2} = 12V$

Use the offset correction factor equation to accurately set V_{out}