

High **VOLT** Interactive

Where power supply design meets collaboration

隔離式開極驅動器概論


張巍, 系統工程師
德州儀器


What will you get out of this session?

❑ **PURPOSES:**


- ❖ What are the gate driver application
 - ❖ What are the differences: low-side, high-side and low-side, and isolated gate driver?
 - ❖ How to maximize the gate driver performance – from basic to details
 - Parasitics in the gate driver
 - Hard/soft switching
 - High dV/dt and di/dt
 - Isolated gate driver
- Part numbers mentioned:
 - Low side:** UCC27511A, UCC27524A
 - H-/L- Side:** UCC27282, LMG1210, UCC27710
 - Isolated:** UCC21540, UCC23513, UCC21710,
 - Relevant End Equipment:
 - Telecom, servers, solar inverters, motor drive, EV/HEV, UPS

Where are gate driver ICs used?

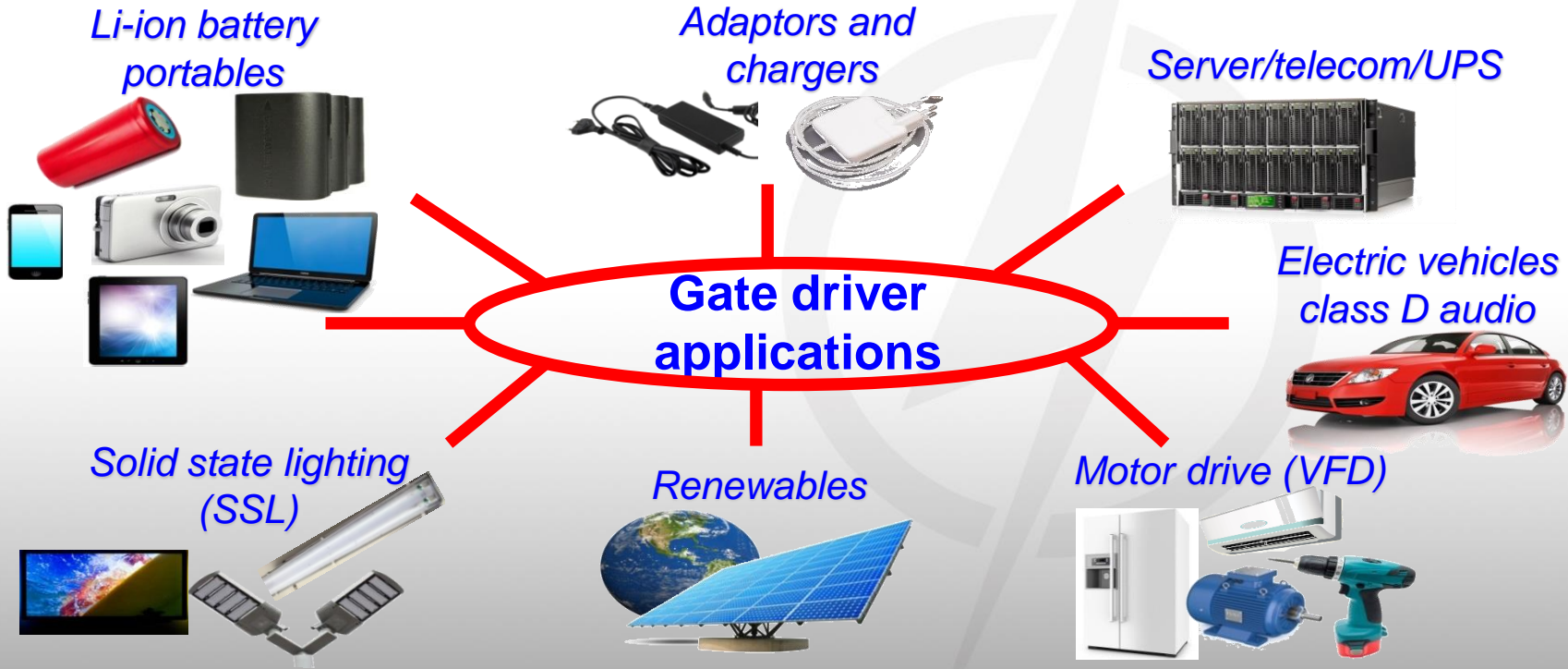


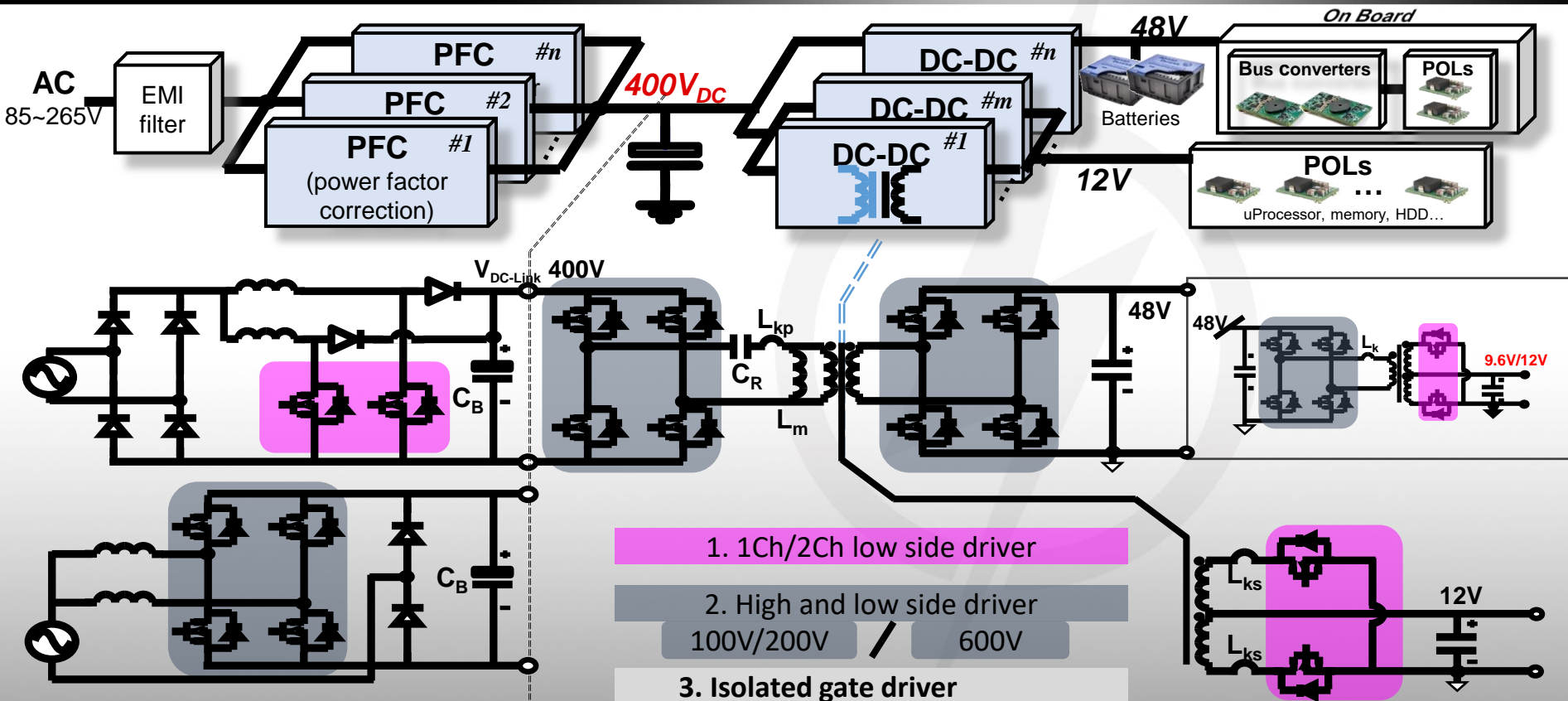


Si-MOSFET

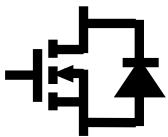



IGBT

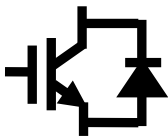

SiC-MOSFET

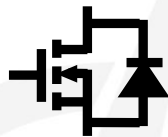

GaN

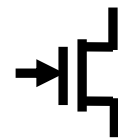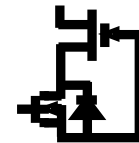

Nom-ON

Nom-OFF

Voltage ratings

20~650V

≥650V

≥650V

≤650V

Optimal V_{GS}

0~15V

-10~15V

-5~20V

-5~10V

-4~6V

Max.limit

(±20V)

(±20V)


(-10~25V)

(±18V)

(-10~7V)


Si-MOSFET

10V

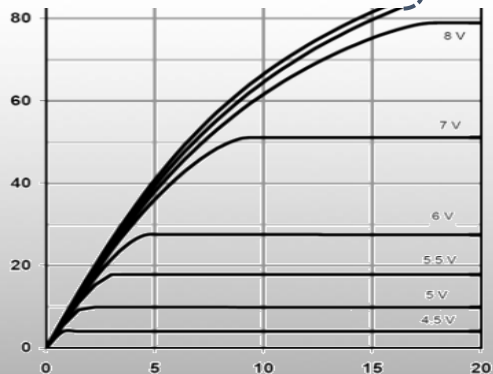


IGBT

12V

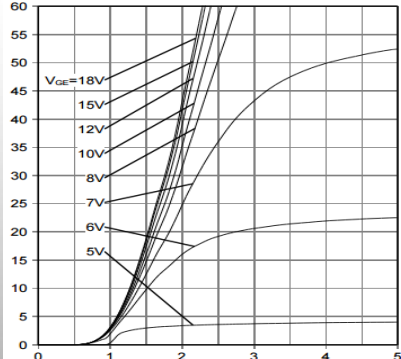


SiC-MOSFET

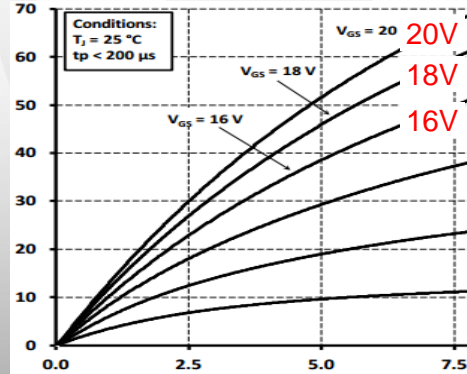


GaN

5V

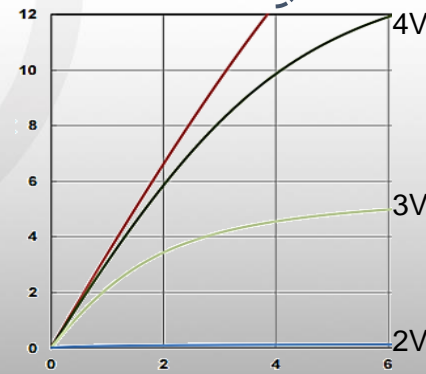


- I-V curves are from datasheets of Infineon, Fairchild, ST, Wolfspeed, EPC

Si-MOSFET

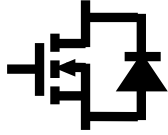


IGBT

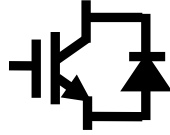


SiC-MOSFET






GaN

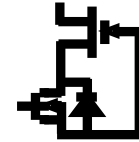


Nom-ON

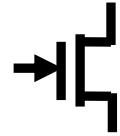

Nom-OFF

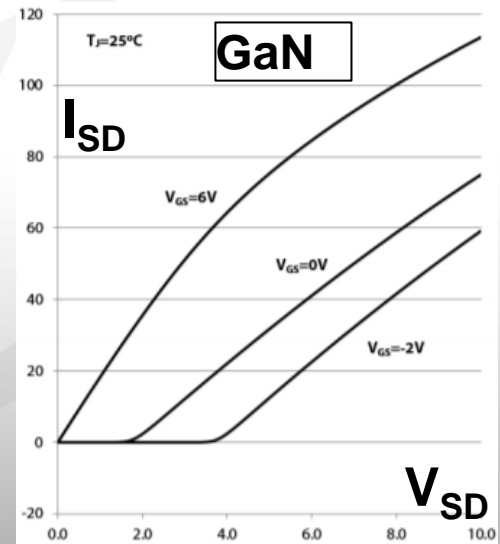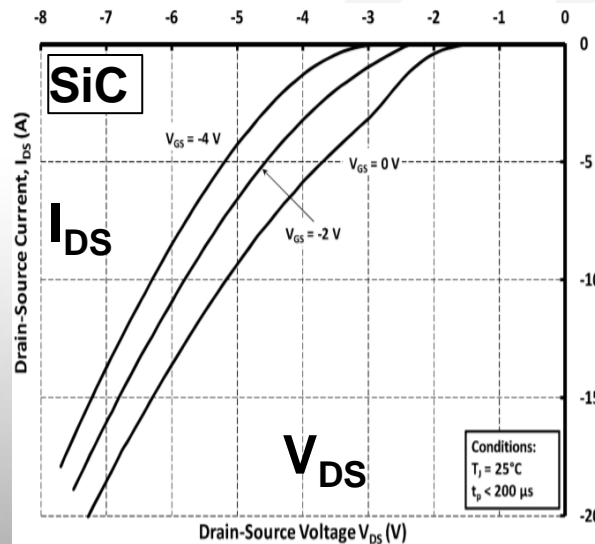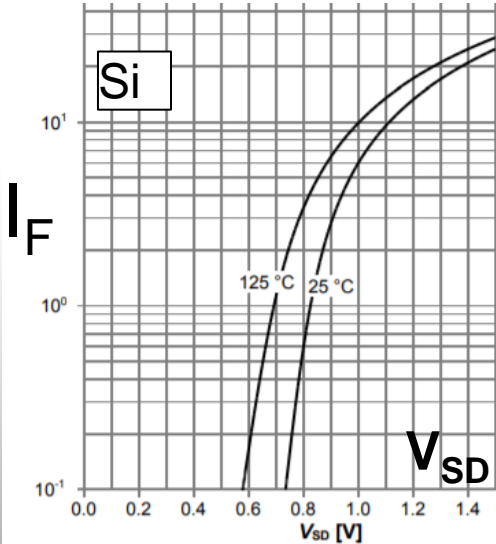


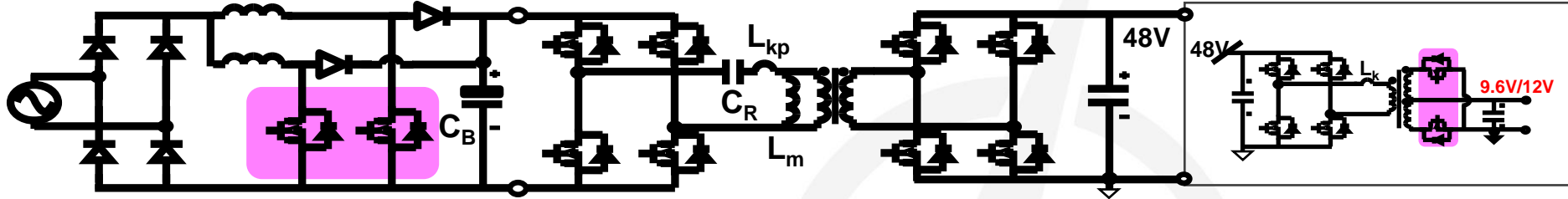

Level shift circuit + NPN/PNP totem pole

3.3V/5V
PWM signal from
microcontroller or
DSP

Micro/DSP

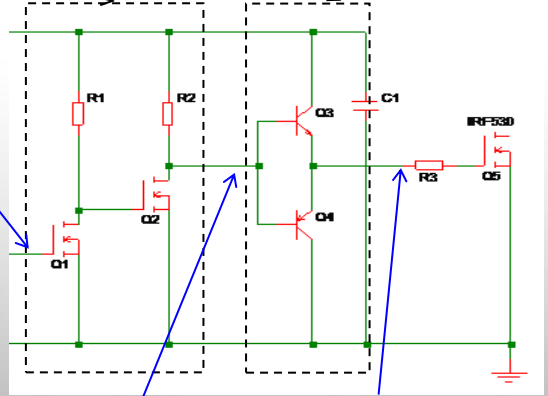

Level shifted
12V signal

12V with high peak
source/sink current




Now

- Reduces BOM component count
- Reduces PCB space
- Protects from spurious signals during power up (such as UVLO)
- Improves reliability




- UCC27511A - Single
- UCC27524A - Dual
- UCC27531 - SiC or IGBT

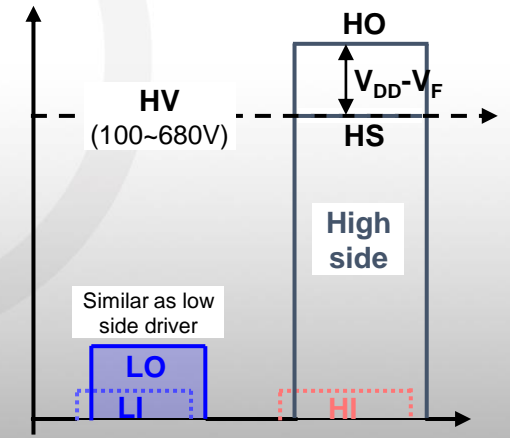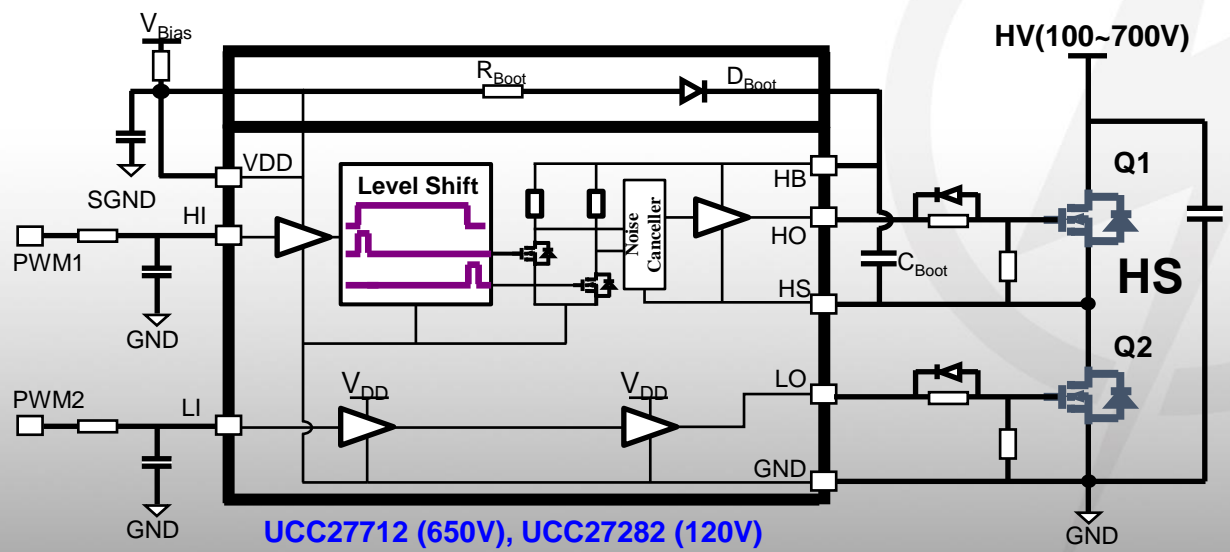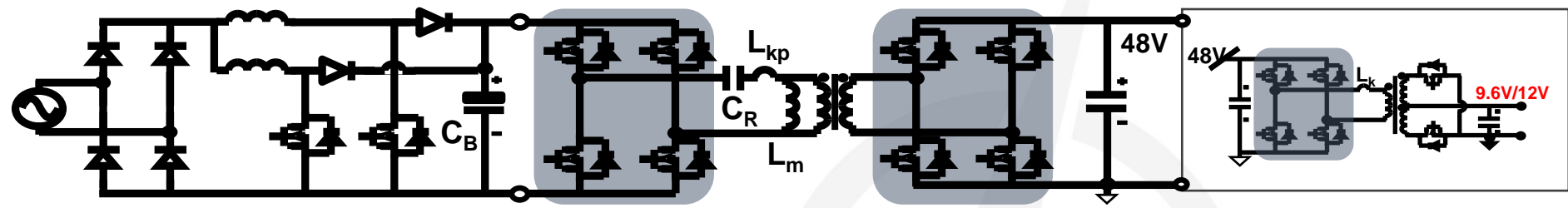
High **VOLT** Interactive How does a Half-Bridge Driver Operate?



Si-MOSFET

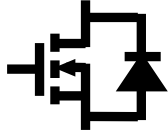


IGBT

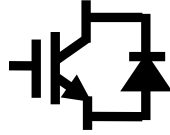


SiC-MOSFET






GaN

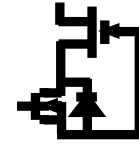


Nom-ON

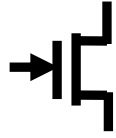

Nom-OFF

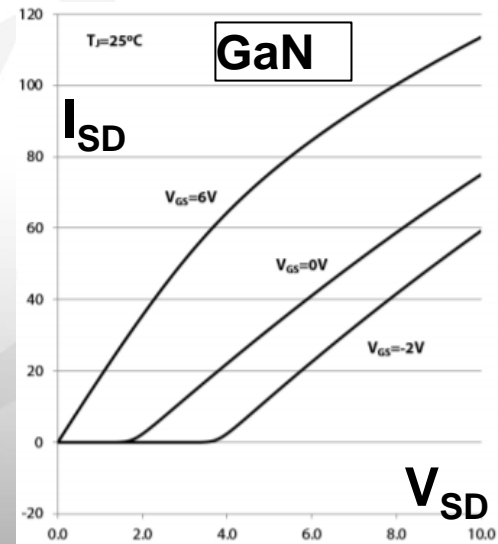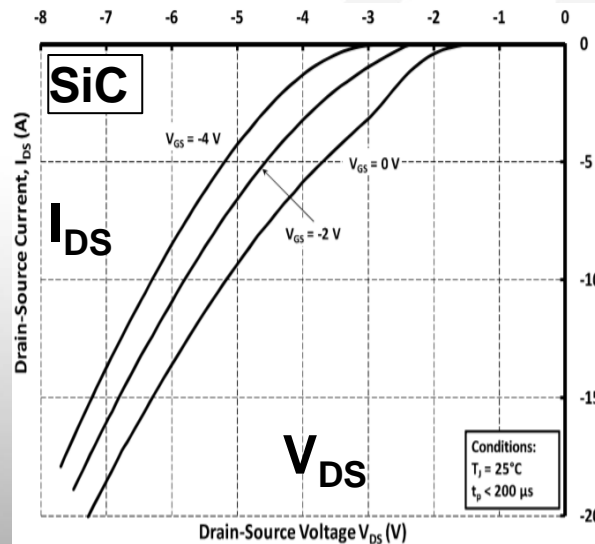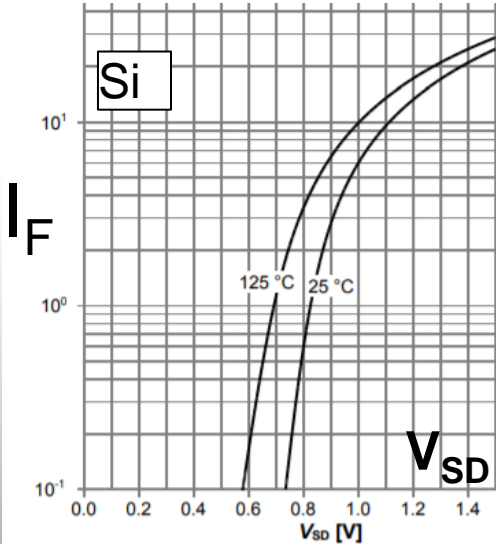


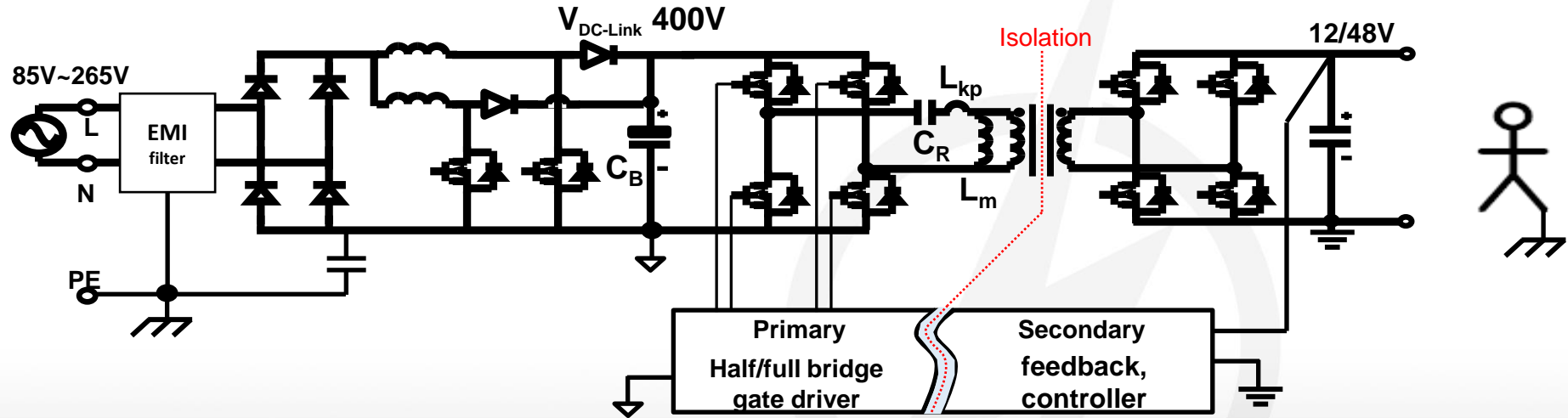


IEC 60950-1 ed. 2.0, Table 5B

Working voltage V, peak or DC	Test voltage for electric strength based on peak working voltage		
	Functional Isolation (V_{RMS})	Basic Isolation (V_{RMS})	Reinforced Isolation (V_{RMS})
≤ 210	1000	1000	1500
≤ 420	1500	1500	3000

Isolation	Definition	Featured Drivers
<u>Functional</u>	Isolation that is necessary only for the <u>correct functioning</u> of the equipment	UCC21220A, UCC21222
<u>Basic</u>	Isolation to provide <u>basic protection against electric shock</u>	UCC21220A, UCC21222
<u>Reinforced</u>	<u>Single Isolation system</u> that provides a degree of protection against electric shock equivalent to DOUBLE isolation under the conditions specified in this standard	UCC21540, UCC21520

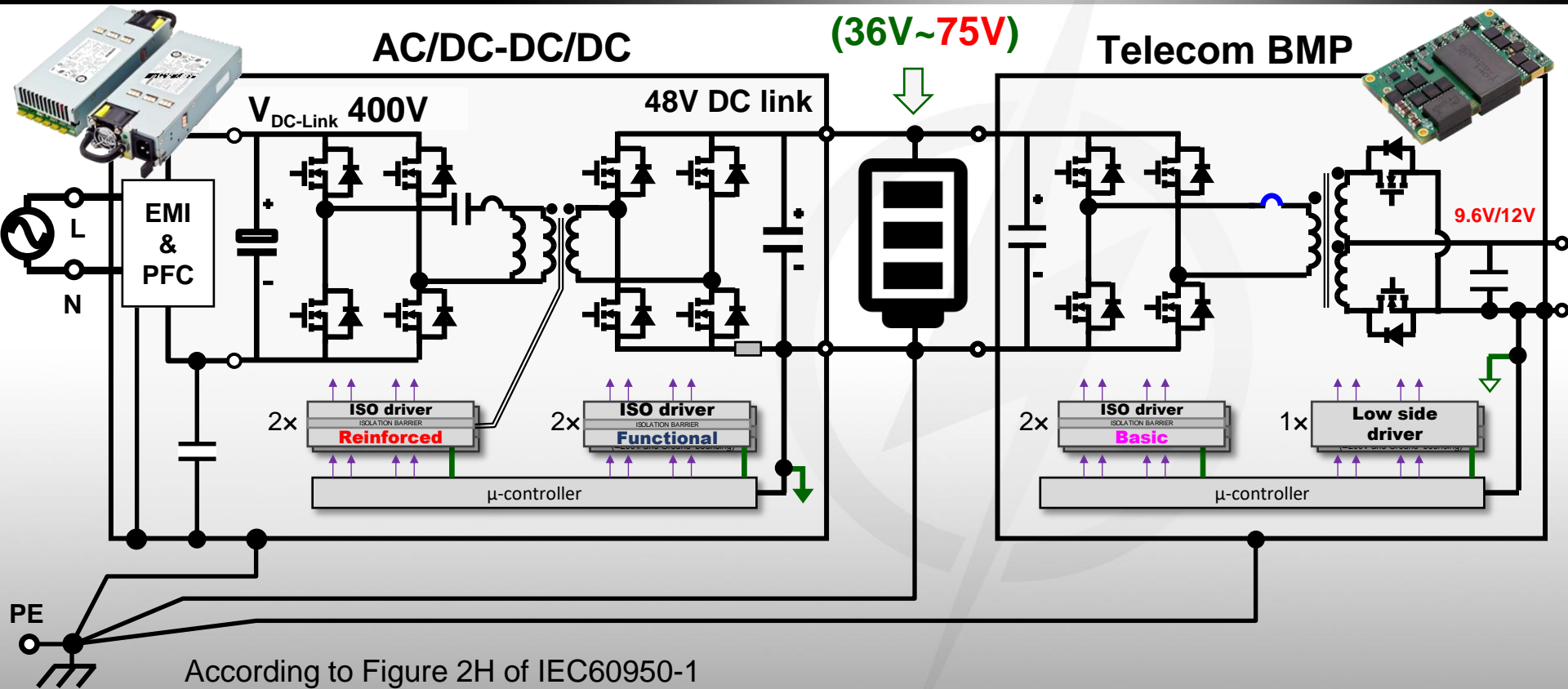


According to Figure 2H of IEC60950-1

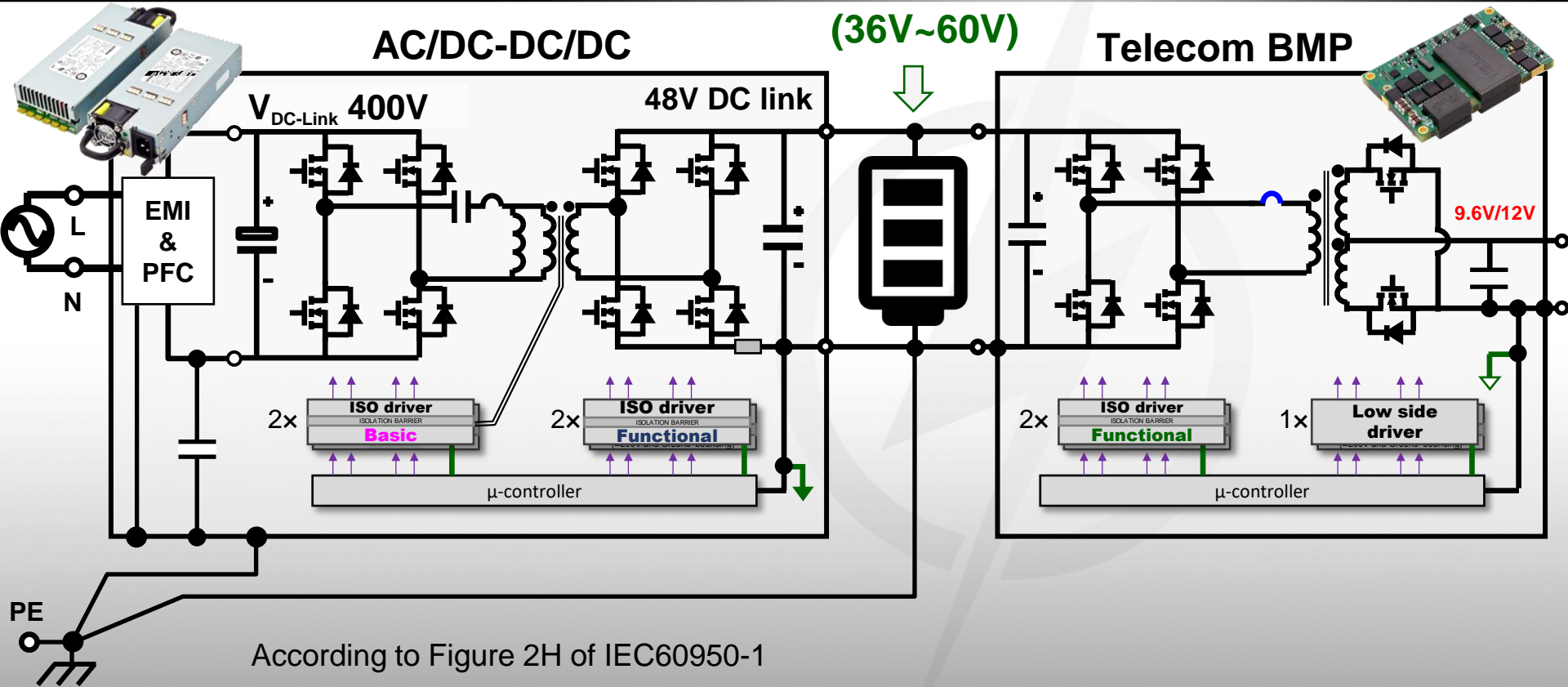


According to Figure 2H of IEC60950-1

TYPE A

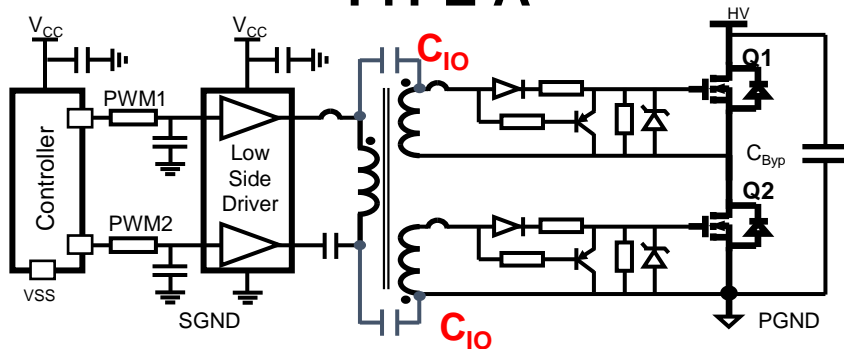


TYPE B

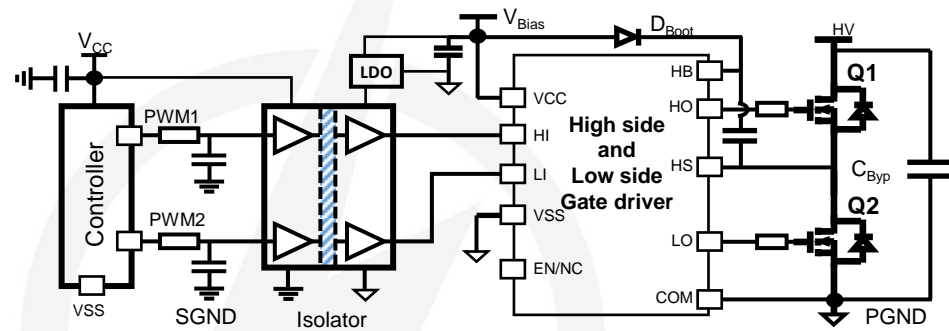


	Type A	Type B
T_{Prop}	$\approx 20\text{ns}$	$\approx 100\text{ns}$
Bias power	NO	Yes
C_{IO}	$\geq 10\text{pF}$	$< 1\text{pF}$
Parasitics	Large (L_{LK})	Very small
Overshoot	Large	Small
Size	Bulky	Small

TYPE A

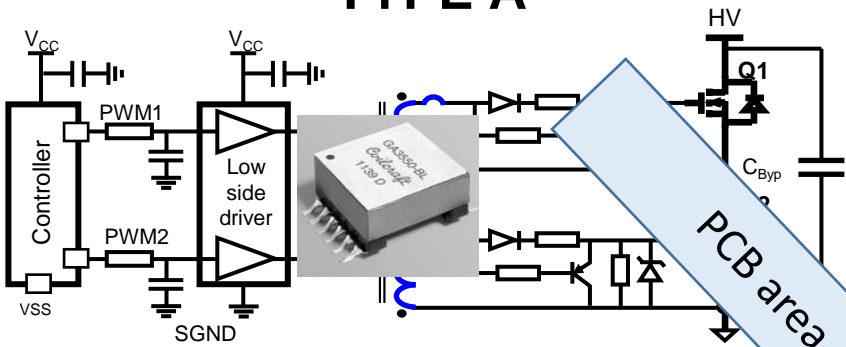

TYPE B

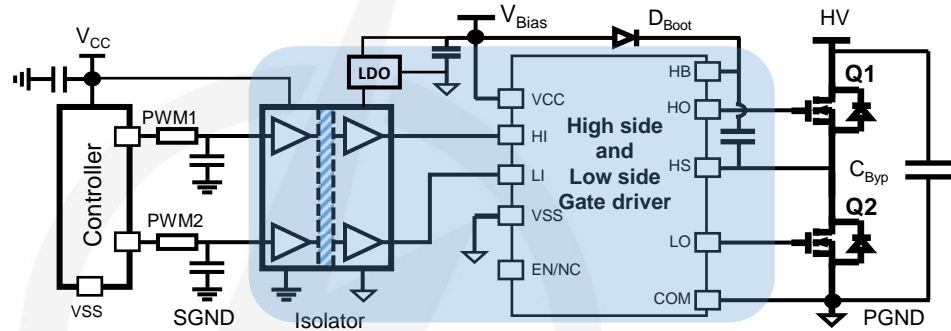

PCB area reduction - 76%

TYPE C: ISO driver

- ❖ CMTI > 100V/ns
- ❖ 5kVrms reinforced isolation

T_{Prop} : 19ns typ.
 Match./ T_{PWD} < 5ns


❖ **110mm²**

		W (mm)	L (mm)	H (mm)	Area (mm ²)	
Type A	UCC27324	5	6.2	1.75	31	5
	GA3550-BL	17.4	24.13	10	420	4200
SUM					451	4254

Type B	ISO7520C	10.5	10.6	2.65	111.3	295
	UCC27714	8.75	6.2	1.75	54.25	95
	MURS360	8.1	6.1	2.4	49.41	119
SUM					215	509

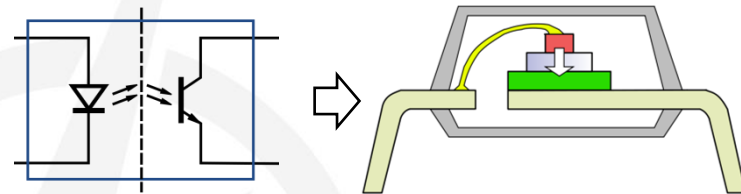
- A) Optocoupler

- Signal transfer between two isolated circuits using light – LED + phototransistor, ~1970s



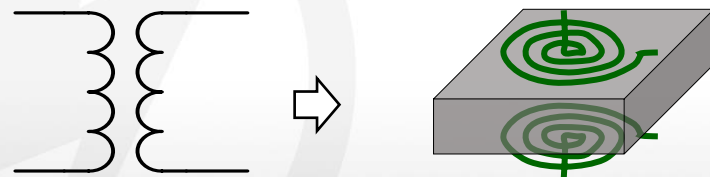
- B) Transformer

- Integrated micro-transformer and electronic circuitry, ~2001




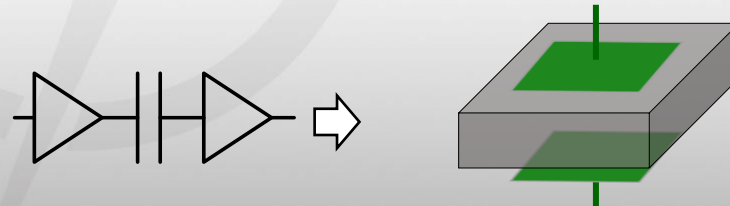- C) Capacitor


- Signal transmission through capacitive isolation with on-off-keying (OOK) modulation, ~2004



TI Reinforced Isolation Technology

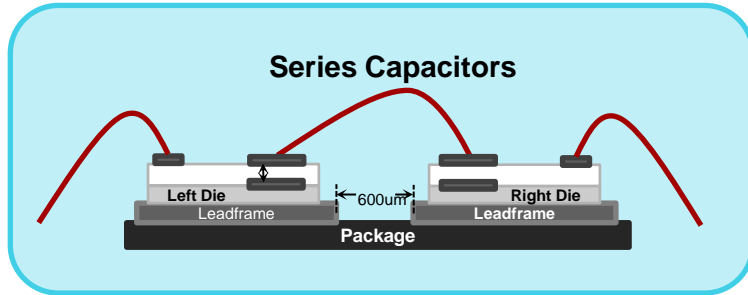


UCC2x52x, UCC2154x,
UCC2351x

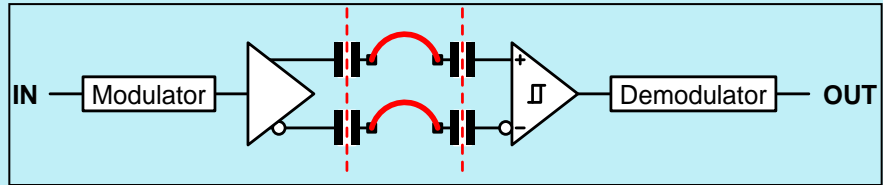

- Reinforced Isolation is realized by thick SiO_2 capacitors combined in series
 - Each channel uses high voltage isolation capacitors on both die
- Combined Isolation capacitor thickness is $>21\mu\text{m}$
- 12.8kV surge voltage, 8kVpeak transient over-voltage, 1.5kVrms working voltage

Foundation of Quality – Qualification & Reliability

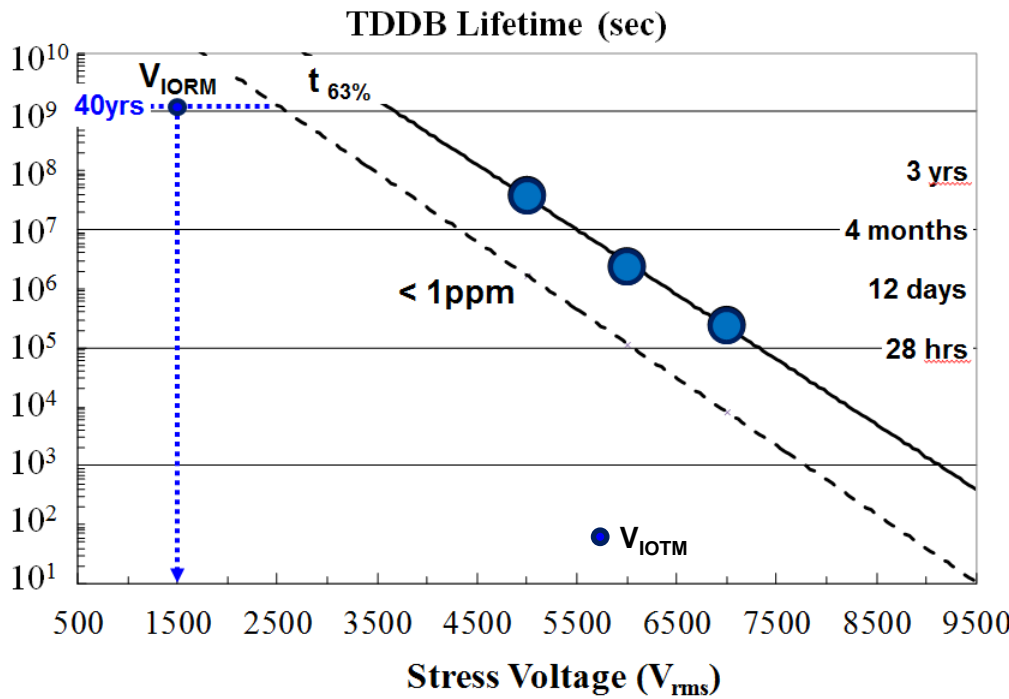- The main Isolation electrical lifetime test is TDDB: **Qualification Test**
 - Standard methodology for determining the lifetime of a dielectric as a function of Voltage



- *TDDB is accelerated lifetime testing of the isolation barrier*
 - Weibull statistics at each voltage
- *First technology to certify to VDE 0884-11*

Foundation of Quality – SiO₂ Insulation

TI **Capacitive Isolation** uses SiO₂ as the Isolation Dielectric.

- SiO₂ advantages compared to competing HV isolative material are: **reliability** and **dielectric strength**


Insulator Materials	Dielectric Strength, 1 sec	Dielectric Strength, 40yr reliability
Air	~1 Vrms/um	
Epoxies	~20 Vrms/um	
Silica filled Mold compounds	~100 Vrms/um	
Polyimide	~300 Vrms/um	~20 Vrms/um
SiO ₂	~500 Vrms/um	~100 Vrms/um

Table 1: Commonly used materials for High-Voltage isolation (SiO₂ has the highest dielectric strength and best reliability)

Dielectric Thickness (SiO₂) Fabrication Process Control & Monitor:

- **Repeatability** and **Reproducibility** – SiO₂ thickness monitored using two methods:
 - Oxide thickness sample measured in the wafer fab for each of the layers of the dielectric stack
 - Tox by capacitance measurement on test structures on every production wafer after fabrication
- Thickness is tracked on all wafers for each fabrication lot as required by UL standard

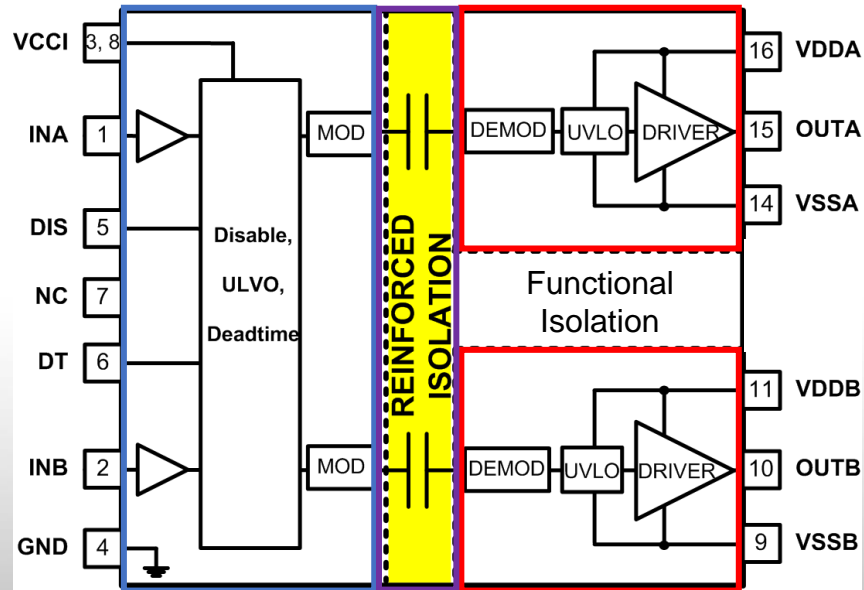UCC21220A, UCC21540: 2-ch. Isolated Gate Driver




Input Die – takes inputs from μ Controller, modulates and transmits across isolation barrier using on-off-keying

SiO₂ Capacitors – provides high voltage basic or reinforced isolation, with excellent noise immunity and lifetime

Output Die – demodulates signal and drives outputs on or off depending on logic inputs

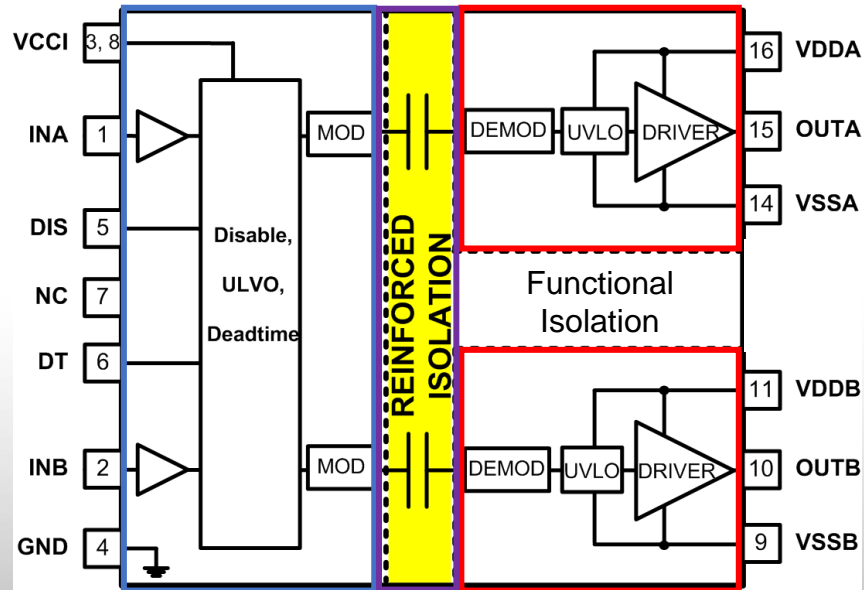UCC21220A, UCC21540: 2-ch. Isolated Gate Driver



- 6A/4A sink/source
- 28ns propagation delay
- >100V/ns CMTI
- Up to 3~5V input range and 6~18V wide output voltage range
- Programmable overlap, and interlock/delay time from 0ns~5 μ s
- Output fail safe low with active pull down
- UVLO options: 5V, 8V
- 3.0kV, 5.7kV basic/functional and reinforced isolation
- Pin-2-pin compatible to industry standard
- UL, VDE, CQC certified

Features & Integration

Reinforced

Functional / Basic

ISO=5.7kV

ISO585x/ISO545x

WV=2.1kV

• **Single IGBT driver with protection**

- DeSAT, clamp, fault output, UVLO OK
- 2.5A source/5A sink
- CMTI = 100V/ns
- 76ns prop delay (typ)
- Vdd=15-30V
- **16-pin SOIC (8mm)**
- AUTO

ISO=5.7kV

UCC2152x/A/C

WV=1.4kV

ISO=5.7kV

WV=2.1kV

• **Dual driver**

- 4A source/6A sink
- CMTI > 100V/ns
- 19ns prop delay (typ)
- 5ns match (max)
- VCC=3-18V & Vdd=9-25V
- **16-pin SOIC (8mm)**
- **OPTIONS:**
 - 5, 8, 12V UVLO
 - EN or DIS
 - Dual IN or PWM
 - AUTO

UCC21530-Q1

ISO=5.7kV

WV=2.1kV

- 12V UVLO
- **AUTO**

- **16-pin SOIC DWK (8mm) w/ 3.3mm HS to LS (missing pins)**

UCC21540

ISO=5.0kV

WV=1.4kV

• **Dual driver**

- 4A source/6A sink OR 2A/3A
- Pin-to-pin with 21520
- 5V or 8V UVLO
- **VCC=3-5.5V**
- **5KVrms Viso**
- 16-pin SOIC (8mm) DW or DWK (missing pins)

ISO=5.0kV

WV=2.1kV

UCC5310MC UCC5390EC UCC5320SC

- 1A, 2A & 10A
- **8-pin SOIC (8mm)**

UCC2x225/A

ISO=2.5kV

WV=790V

- **Dual driver**
- 4A source/6A sink
- CMTI > 100V/ns
- 19ns prop delay (typ) w/ 5ns match (max)
- PWM (UCC20x) or dual input (UCC21x) w/disable
- 5V or 8V UVLO
- **13-pin LGA (5x5mm)**

ISO=3kV

WV=990V

UCC5390SC/EC UCC5350MC

- **10A source/10A sink**
- **M = Miller clamp**

UCC5320SC/EC UCC5310MC

- **Single driver (12V UVLO)**
- 2A source/2A sink
- M = Miller clamp (5310)
- S = Split output
- VCC=3-15V & Vdd=10-33V
- **8-pin SOIC (4mm)**

UCC5350SB

- **Single driver (8V UVLO)**
- 3KVrms Viso
- 8.5A source/10A sink
- VCC=3-15V & Vdd=10-33V
- **8-pin SOIC (4mm)**

ISO=3.0kV

WV=990V

UCC21220/A UCC21222-Q1

- **Dual driver**
- 5V or 8V UVLO, DIS
- Dead-time (DT)
- 4A source/6A sink
- VCC=3-5.5V & Vdd= 4.8-18V
- 25ns prop delay (typ)
- **16-pin SOIC (4mm)**
- **AUTO**

End Equipment:



- Server PSU → PFC, SR
- Telecom Rectifiers → PFC, SR
- Brick Power Modules
- Solar Inverter & Solar Optimizers
- Motor Drives & Robotics

End Equipment:

- Server PSU → Isolated DC/DC
- Telecom Rectifiers → Isolated DC/DC
- Industrial AC-DC
- Solar Inverters
- AC Motor Drives

Time

Main Differences UCC21520 & UCC21540

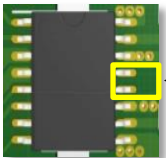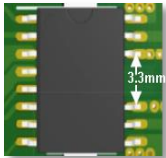Parameter	UCC21520	UCC21540	Comments
VCCI/VDD AbsMax	20V _{CCI} /30V _{DD}	6V _{CCI} /20V _{DD}	UCC21540 – MOSFET
Output UVLO	5V, 8V, 12V	5V and 8V	
Pin 5 Functionality	DISABLE	DISABLE	UCC21540 – P2P w/ UCC21520
Driver-to-Driver Spacing	2mm	2mm & 3.3mm	3.3mm enables higher bus voltage safety standards
Propagation Delay	19ns typical	28ns typical	Allow accurate switching and fastest response - higher power density enabling smaller solutions
VDDA/VDDDB UVLO startup delay	50μs typical	23μs typical	Easy synchronization between high side and low side
PCB modifications to accommodate for >600V DC Bus Voltage Applications	<p>External coating on pins 12-13 (NC) to increase driver-to-driver working voltage</p>  <p>Need Conformal Coating on System PCB for HV isolation</p>	<p>No changes required</p>  <p>No coating required</p>	<p>UCC21540 enables:</p> <ul style="list-style-type: none"> Lower cost MOSFET Solution No special coating required Higher system reliability
Automotive Grade	AEC-Q100 available	N/A	

UCC23513 Specifications

4A, 5kV_{RMS}, Opto-Compatible Input Gate Driver in Stretched SO-6

Overview

UCC23513 is a 4A, 5kV_{RMS} opto-compatible gate driver available in stretched SO-6. Using capacitive isolation technology to simulate opto-isolation, this solution is more robust, longer-lasting, and exhibits exemplary propagation delay and Common Mode Transient Integrity specifications. With UCC23513, TI is providing customers with a pin-to-pin replacement for opto-isolated gate drivers to offer a better performing and longer-lasting solution that requires minimal effort to design in.


Features

- Opto-compatible input, isolated Gate driver for IGBT/MOSFET/SiCs
- SiO₂ based capacitive isolation technology
- **Pin compatible, drop-in upgrade for ACPL-W341, W346, TLP5752**
- 4A peak output drive current
- 35V max output drive ($V_{CC} - V_{EE}$)
- SO6 (6 pin wide lead, smt), NiPdAu lead finish, material group I
- > 8.5mm Cr & Clr; 5kV_{RMS} reinforced isolation
- **105ns propagation delay with 25ns part-to-part delay matching**
- **100 kV/us Common Mode Transient Integrity (CMTI)**
- 12V Under Voltage Lockout (UVLO)
- Input stage can be reverse-biased for interlock
- **Wide operating temperature range (Tj): -40°C to 150°C**

Benefits

- **Higher common mode transient integrity**
- **Smaller propagation delay and tighter part-to-part delay matching**
- Lower pulse width distortion
- Higher reliability, resistant to temperature and aging
- No long term aging of input stage
- Very tight tolerance of cap oxide since oxide is a controlled fab process
- **Long lifetime (> 40 yrs)**
- Less variation in forward current due to tighter V_F


<http://www.ti.com/product/UCC23513>

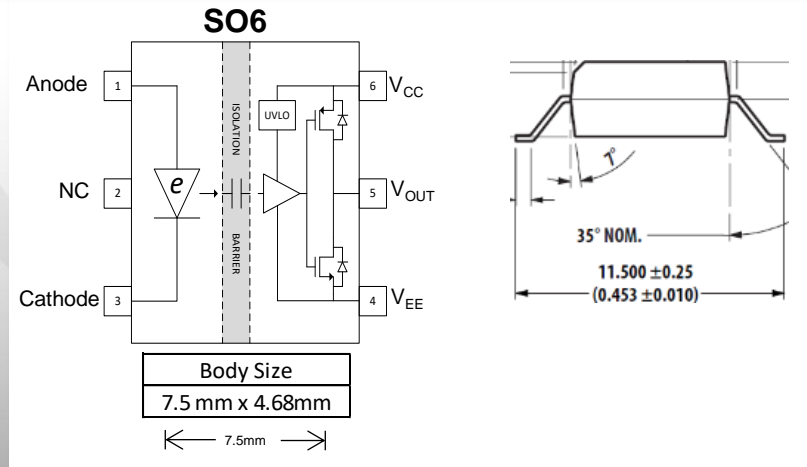

New Features in UCC217XX	Key System Challenge Solved ...		System Benefits
	IGBT	SiC	
±10A peak drive strength (throughout drive voltage range)	>10kW systems use discrete buffers (e.g., NPN+PNP) to increase drive strength: Reliability, drive supply & cost challenges		<ul style="list-style-type: none"> Higher System Reliability + Higher Efficiency Lower System Cost + Smaller PCB Area
>150V/ns CMTI (Min)	(Typically <50V/ns)	SiC switches fast to reduce switching loss	<ul style="list-style-type: none"> Enhanced System Robustness Higher System Efficiency
200ns Over-Current Detection + 650ns Isolated Fault Reporting	Programmable DESAT threshold voltage	SiC has <3μs short-circuit capability	<ul style="list-style-type: none"> Fast System Protection Enhanced System Robustness
2-Level Turn OFF (Option)	Significantly reduced V_{CE} / V_{DS} Overshoot during System Shutdown		<ul style="list-style-type: none"> Safe System Shutdown Enhanced System Robustness Improved Switch Lifetime
Integrated Isolated Accurate Analog-to-PWM Sensor	Eliminate all discrete components used for bus voltage sensing / switch temperature sensing / sec-to-primary feedback / isolated alarm / ...		<ul style="list-style-type: none"> Lower System Cost Smaller PCB Area
VEE UVLO (Option)	Eliminate discrete circuitry for VEE monitoring (voltage sensor + isolator)		<ul style="list-style-type: none"> Lower System Cost Smaller PCB Area
External Miller Clamp (Option)	More effective technique than internal miller clamp for high-power switch modules		<ul style="list-style-type: none"> Enhanced System Robustness Lower System Noise (Ringing + EM)
Standard SOIC-16 DW Package	Small package size, 1mm pad pitch, pin-to-pin compatibility with better specs		<ul style="list-style-type: none"> Lower System Cost Smaller PCB Area

UCC21710

 : AEC-Q100

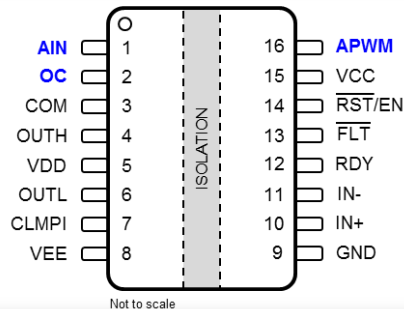

Fast (200ns) Over-Current Detection:


- Important for fast switch protection, especially SiC MOSFETs
- Allows for flexible DESAT threshold setting for SiC MOSFET or IGBT
- Applicable to IGBT modules with SenseFET

Internal Miller Clamp: Suited for lower power levels (<50kW) or tighter layouts (driver to switch)

Soft Turn-OFF: Preferred method for safe shutdown of SiC or IGBT switch

UCC21732 / 36

 : AEC-Q100

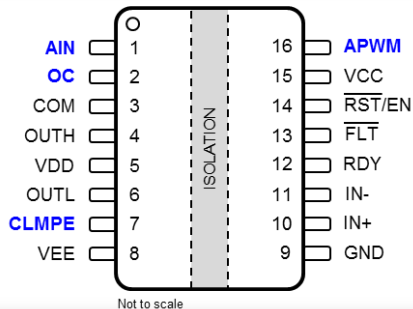

Fast (200ns) Over-Current Detection:


- Important for fast switch protection, especially SiC MOSFETs
- Allows for flexible DESAT threshold setting for SiC MOSFET or IGBT
- Applicable to IGBT modules with SenseFET

External Miller Clamp: Ideal for high-power IGBT/SiC modules (reduce clamp-to-gate parasitics)

2-Level Turn-OFF: Preferred for high-power modules for higher power applications

UCC21750

 : AEC-Q100

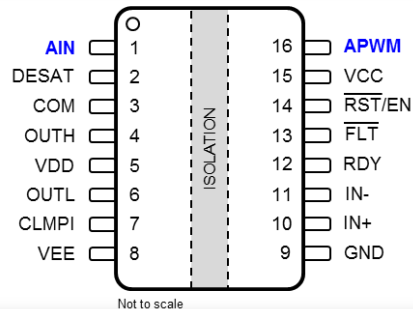

Standard 9V DESAT:

- Exactly what typical IGBTs need (same specs as ISO58XX)
- 9V DESAT might be high for SiC MOSFETs (depends on SiC MOSFET supplier)


Internal Miller Clamp: Suited for lower power levels (<50kW) or tighter layouts (driver to switch)

Soft Turn-OFF: Preferred method for safe shutdown of IGBT or SiC switch

[NOTE: Pins in Black have same pin locations as in ISO5852S or ISO5452. Pin in Blue are new pin definitions.]


[Disclaimer: Specs, features & pinouts subject to change without prior notice.]

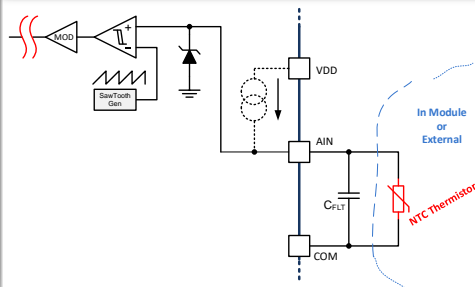Isolated Switch Temperature Sensing: **NTC/PTC**




- AIN Range: 0.5V to 4.5V
- AIN Bandwidth: 50kHz
- APWM: 90% to 10%
- APWM Frequency: 400kHz
- AIN-APWM Accuracy:
 - $\pm 1\%$: System-level cal.
 - $\pm 3\%$: Without cal.
- I_{AIN} : 0.2mA ($\pm 3\%$)

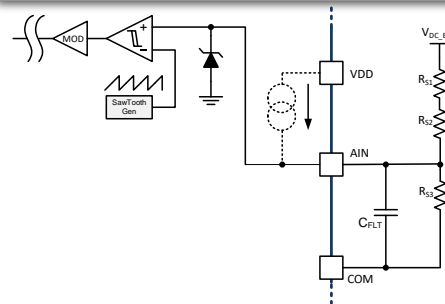Isolated Analog Signal Sensing: **HV Bus / Power Supply / ...**




- HV Bus Sensing
- Secondary-to-Primary Bus Voltage Feedback
- Driver-side Supply Voltage Monitoring (Redundant / Additional UVLO)

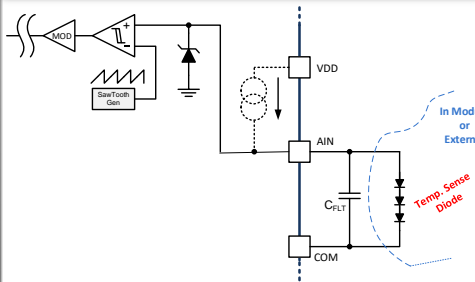Isolated Switch Temperature Sensing: **Thermal Diode**




- Switch Over-temperature Detection: System Protection
- System performance optimization based on Switch Temperature Sensing
- Switch temp-cycling / lifetime monitoring

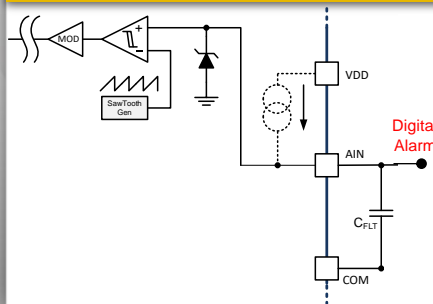Isolated Digital Signal: **Alarm / Shutdown**



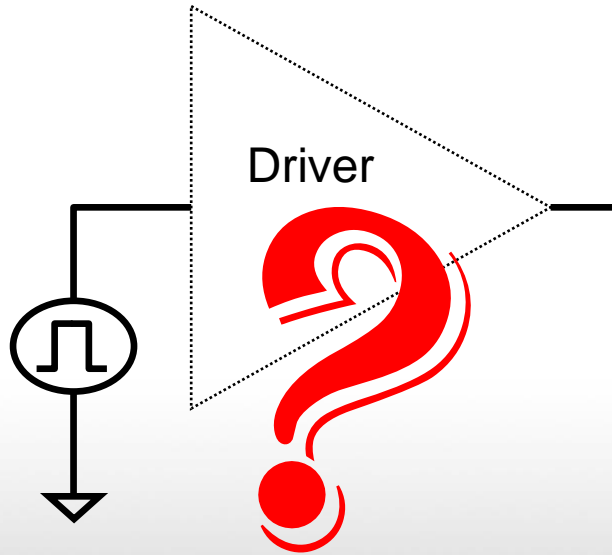
- Digital Alarm
- Emergency Shutdown signal



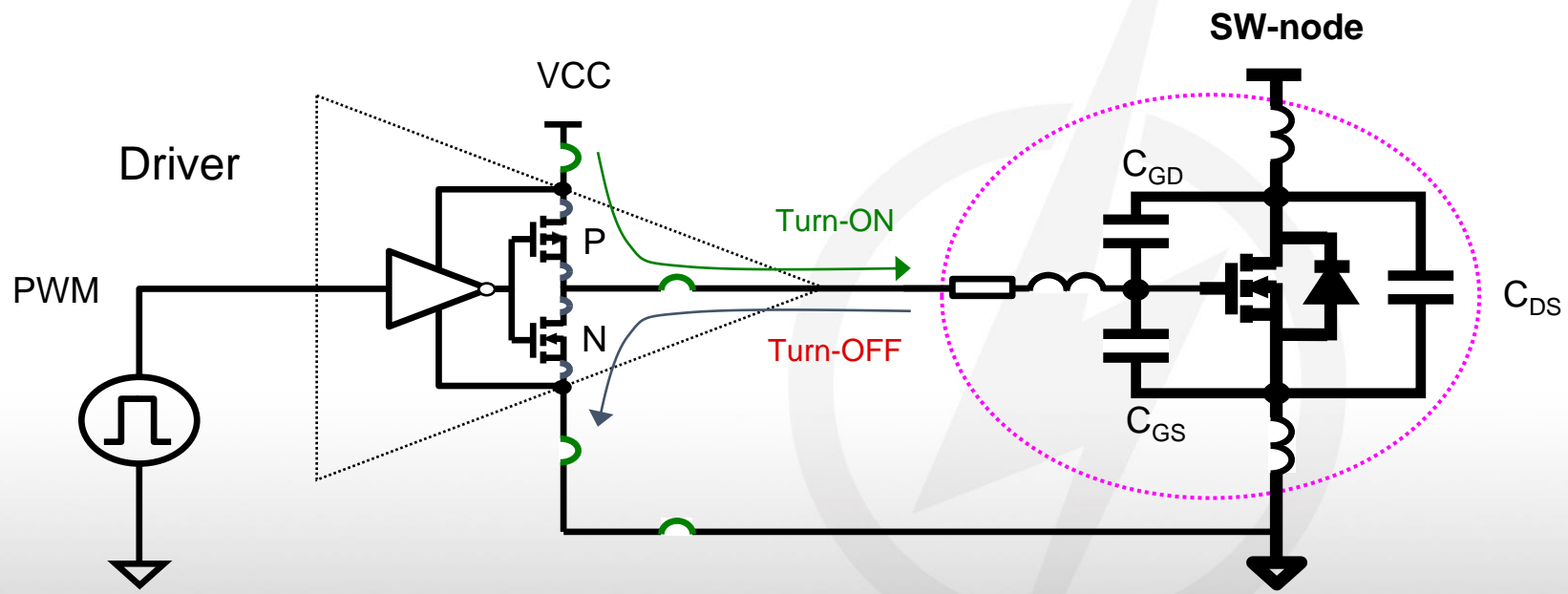1. Parasitics in gate driver?
2. Common mode transient immunity(CMTI), dv/dt and di/dt through parasitics L and C?
3. Gate driver soft/hard switching difference?
4. Strong gate driver and MOSFET nonlinear C_{oss} ?
5. Power supply for isolated gate driver in UPS, server and Telecom system

Gate driver deep dive

Very critical role in converter efficiency and reliability




$$C_{ISS} = C_{GS} + C_{GD}$$


$$C_{RSS} = C_{GD}$$

$$C_{OSS} = C_{GD} + C_{DS}$$

Turn-ON

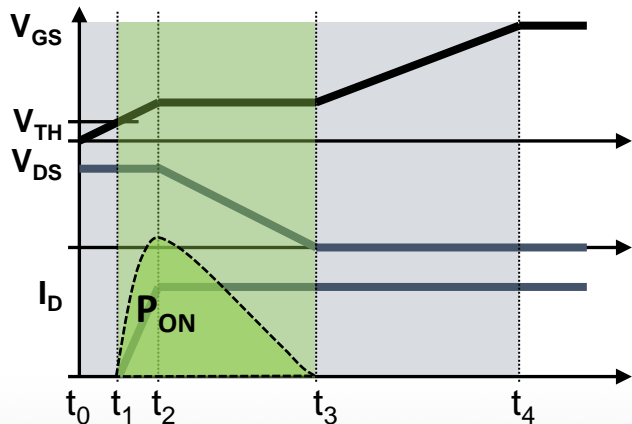

Turn-OFF



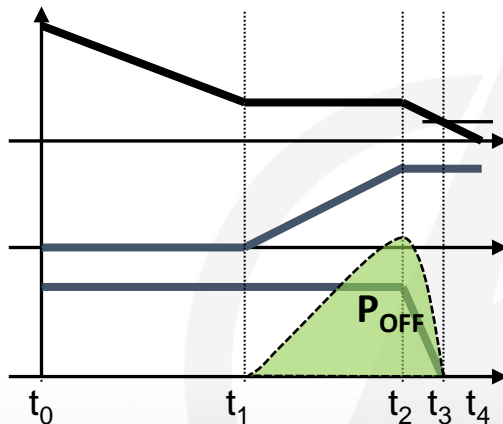



Switching on loss

$$\int_{t_1}^{t_3} V_{DS}(t) \cdot I_D(t) dt + E_{OSS}$$



$$t_{1\sim3} \propto \frac{1}{I_{Drv}}$$

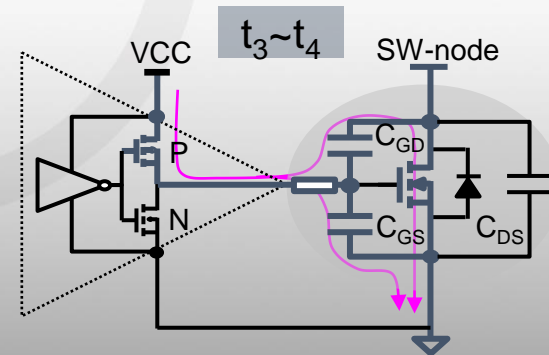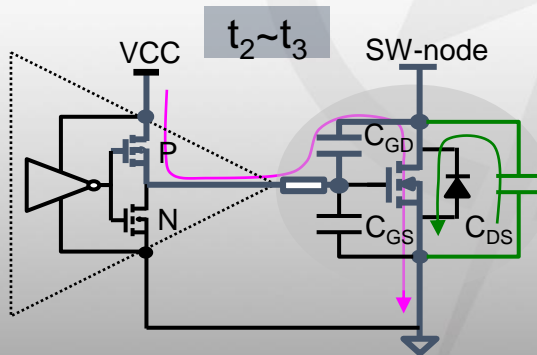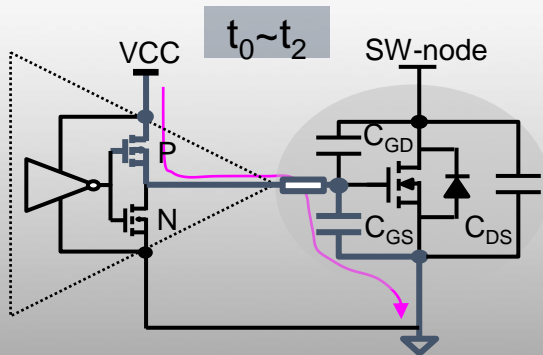Stronger driver \rightarrow lower switching loss





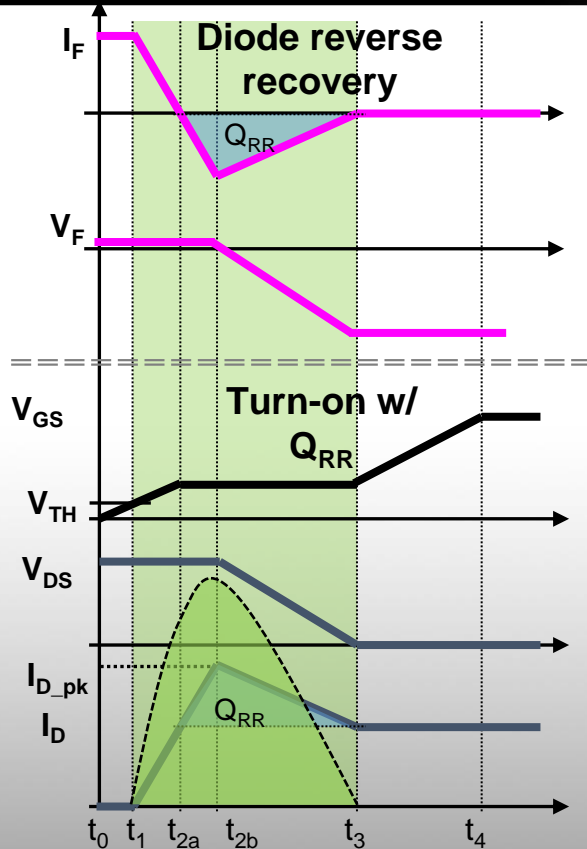


SJ-MOSFET

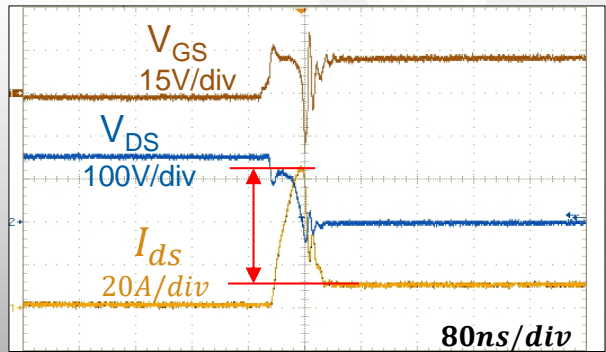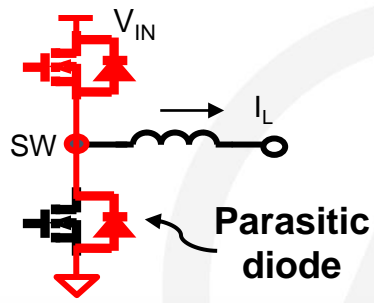


IGBT

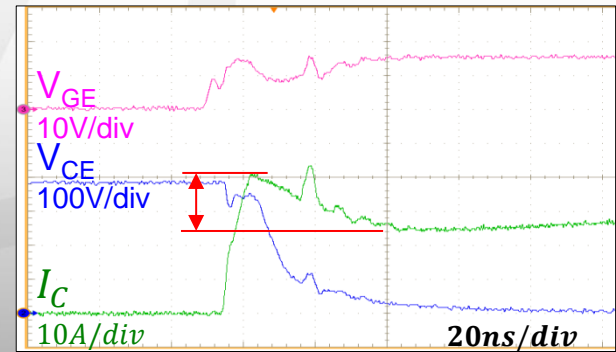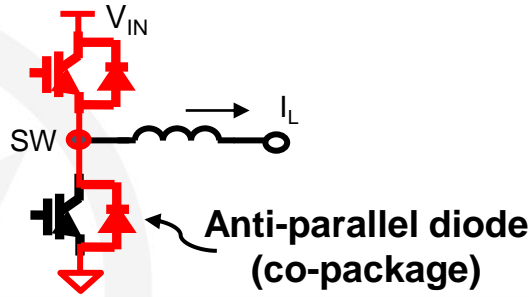






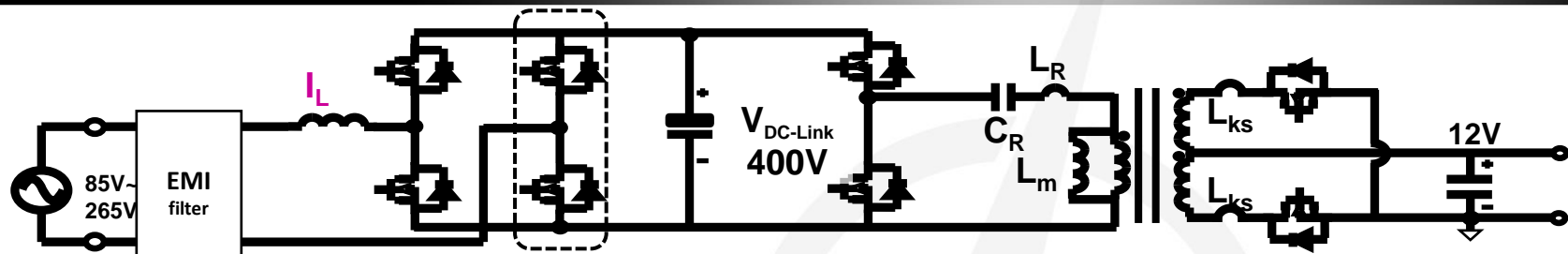




CRM totem pole PFC

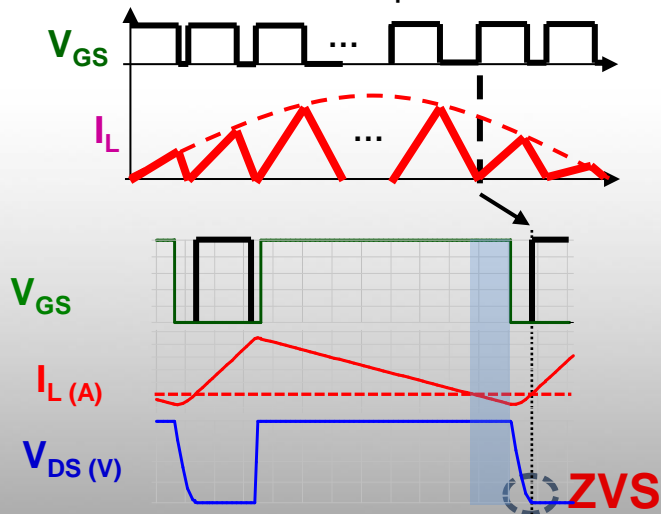

LLC converter + center-tap rectifier


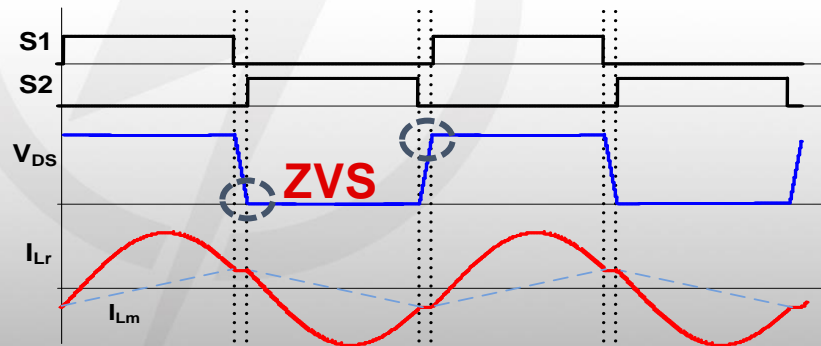


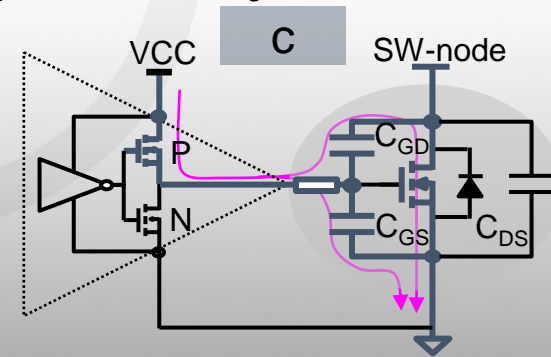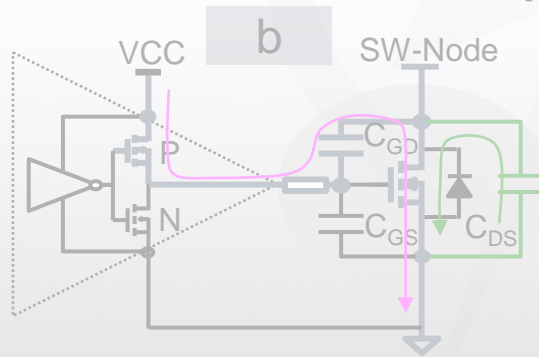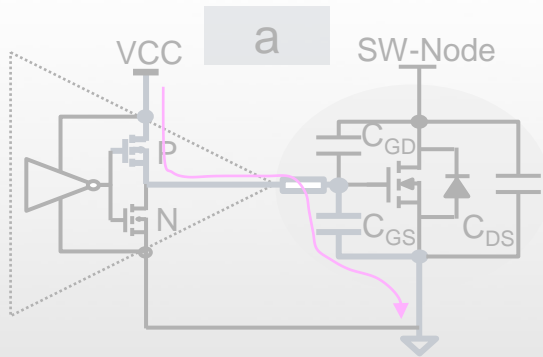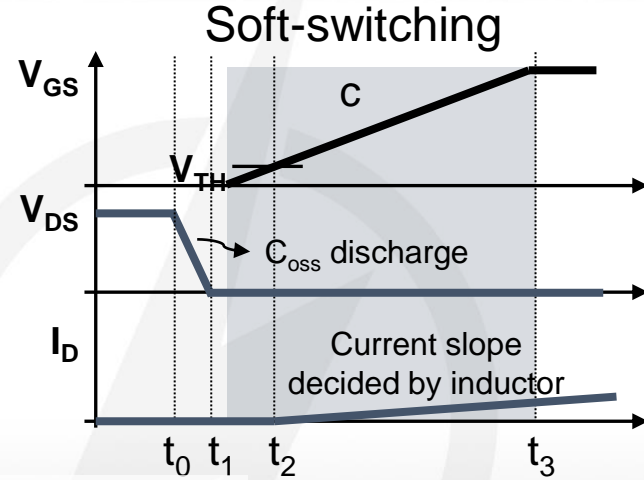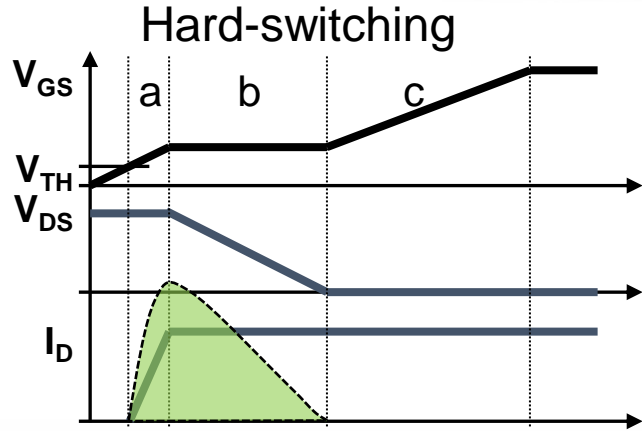

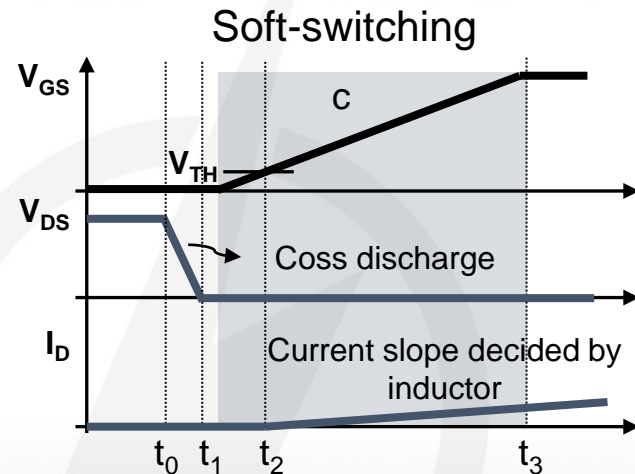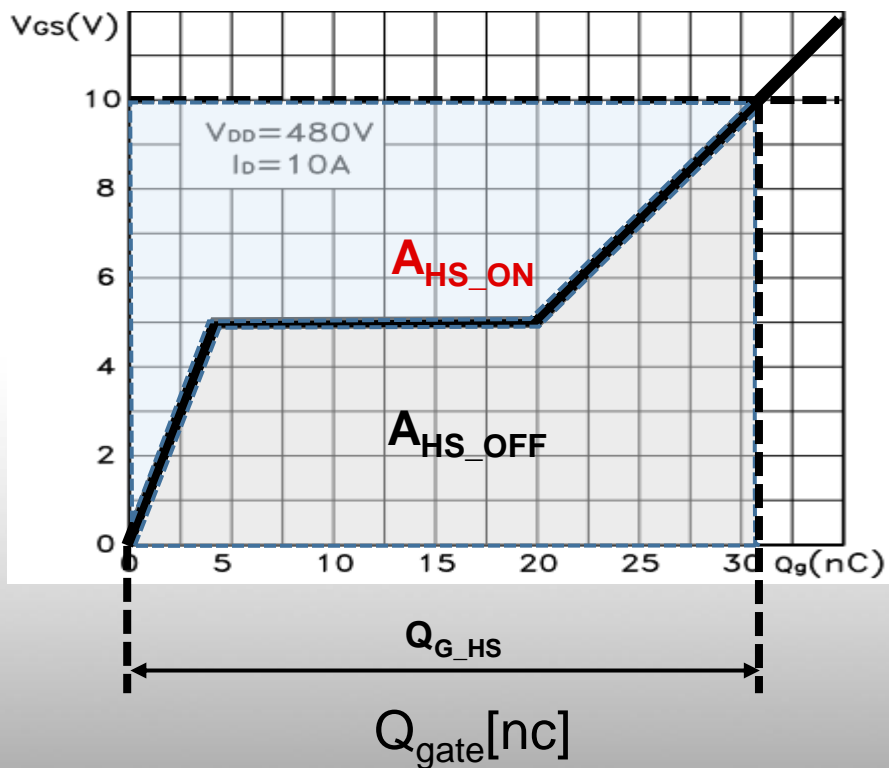

$$E_{G_HS} = A_{HS_ON} + A_{HS_OFF} = V_{GS} \cdot Q_{G_HS}$$





$$P_{GateDrv} = E_G \cdot f_{SW}$$

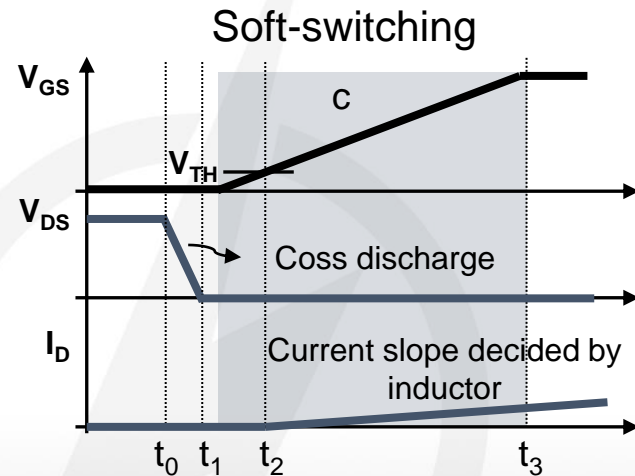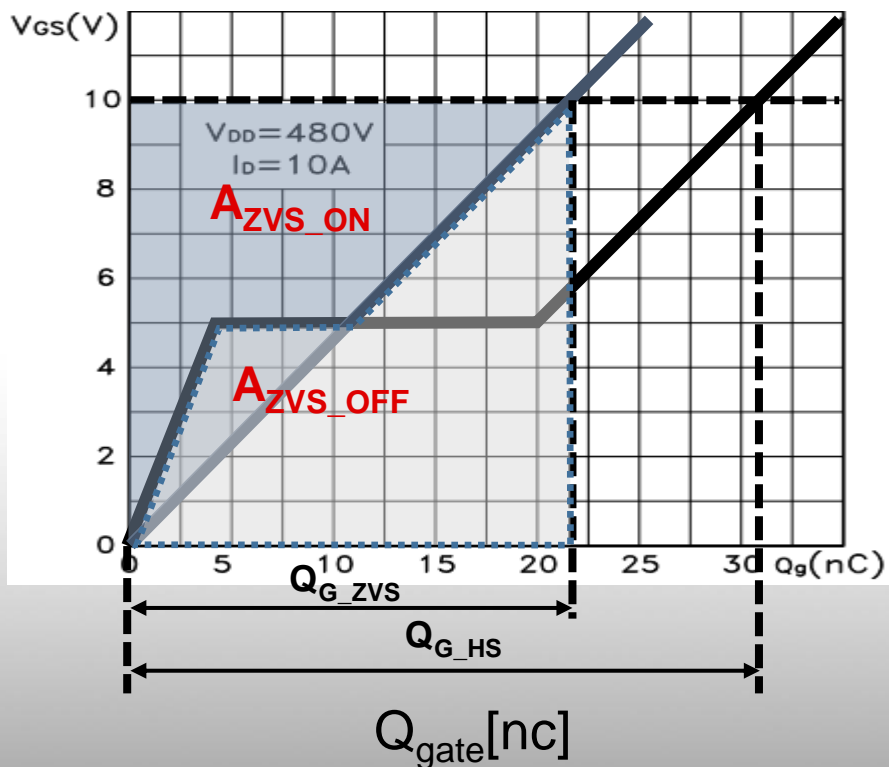

$$E_{G_HS} = A_{HS_ON} + A_{HS_OFF} = V_{GS} \cdot Q_{G_HS}$$

$$E_{G_ZVS} = A_{ZVS_ON} + A_{ZVS_OFF} \approx V_{GS} \cdot Q_{G_ZVS}$$


$$P_{GateDrv} = E_G \cdot f_{sw}$$

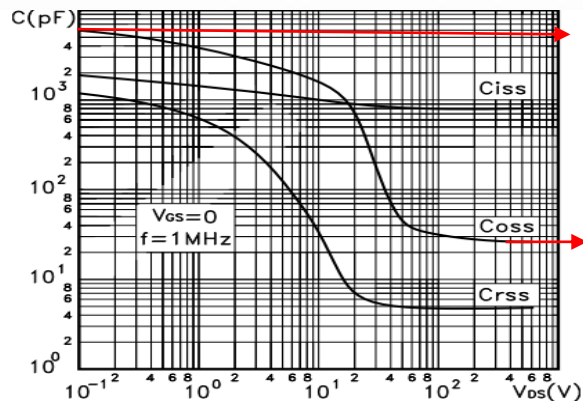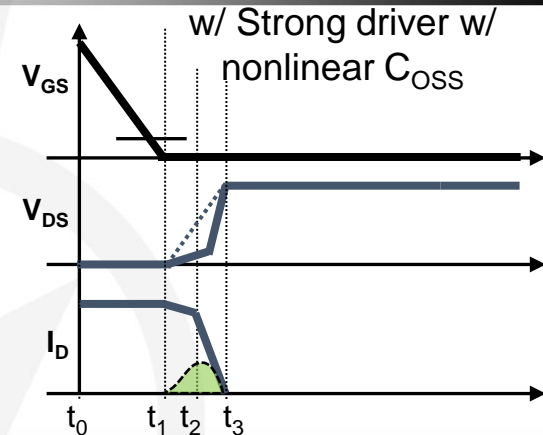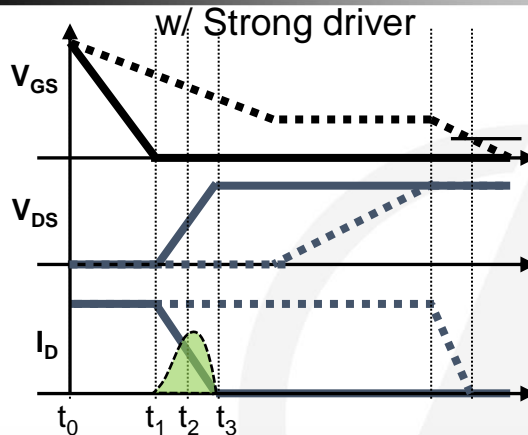
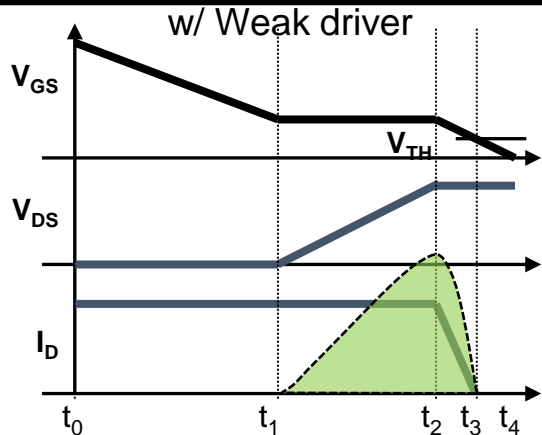


$C_{OSS}(0V)$
 $=6nF$

$C_{OSS}(400V)$
 $<30pF$


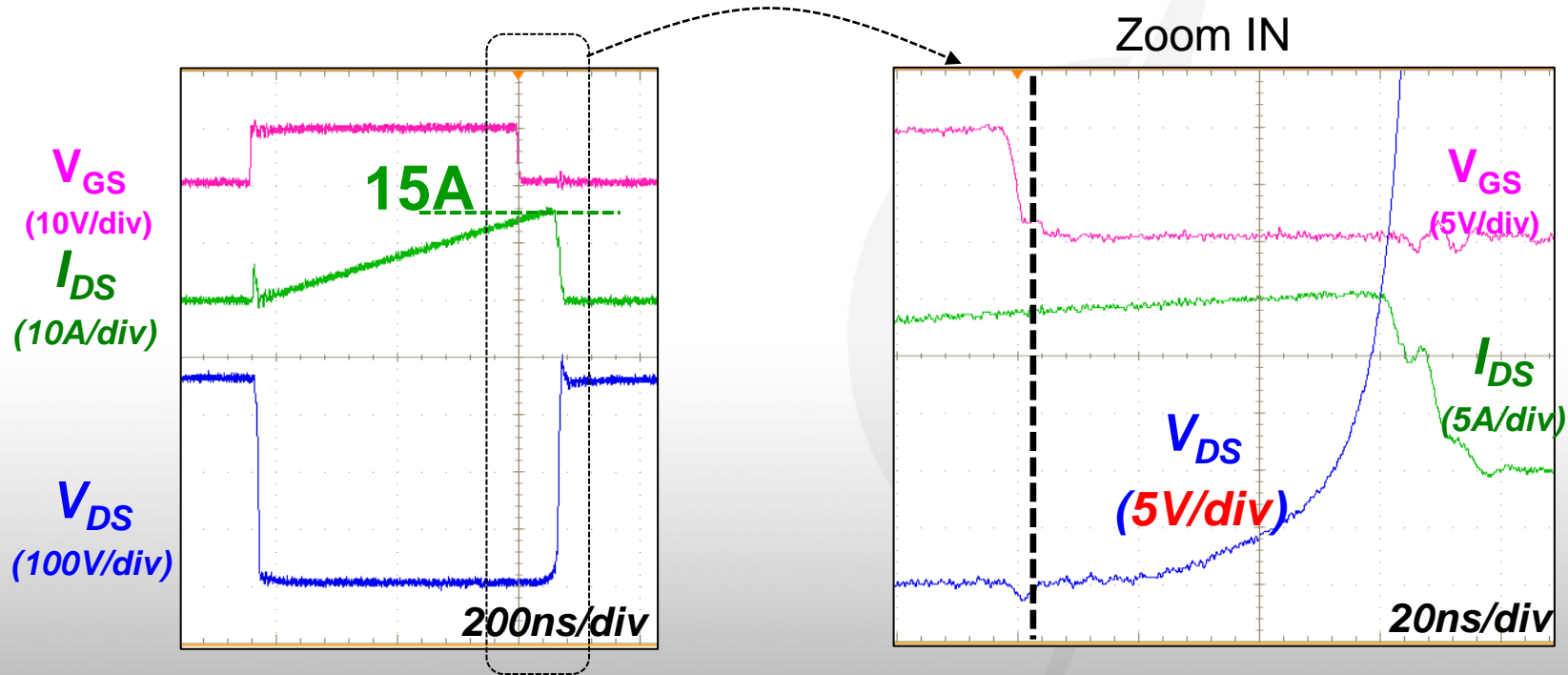
- Switching behavior is not controlled by gate current, but by C_{OSS} and load current
- Large C_{OSS} at low voltage performs as natural snubber
- Small C_{OSS} at high voltage shortens V-I overlap
- Fast dv/dt and di/dt , other bad things





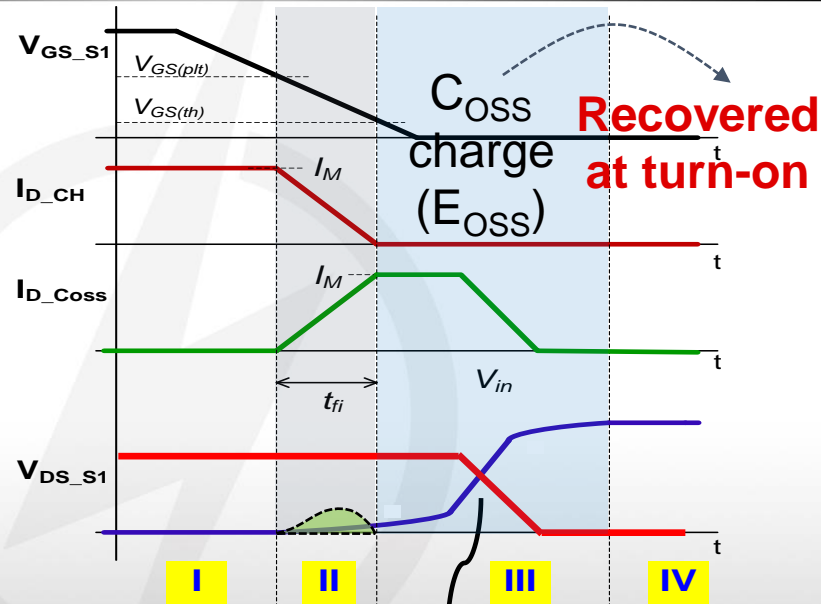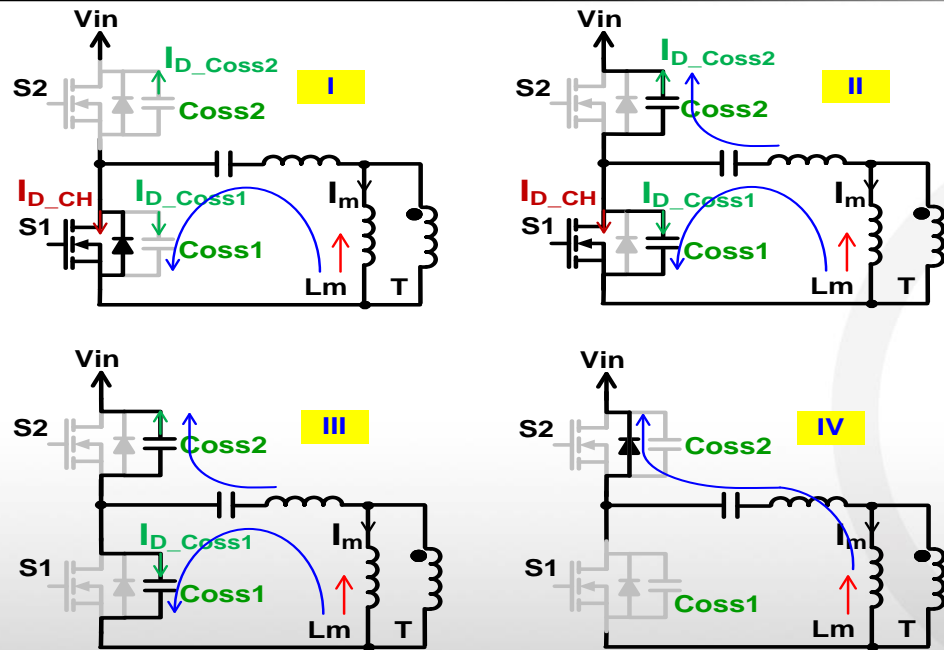


In period II, $V_{DS_S1} \ll V_{DS_S2}$; $C_{oss1} \gg C_{oss2}$
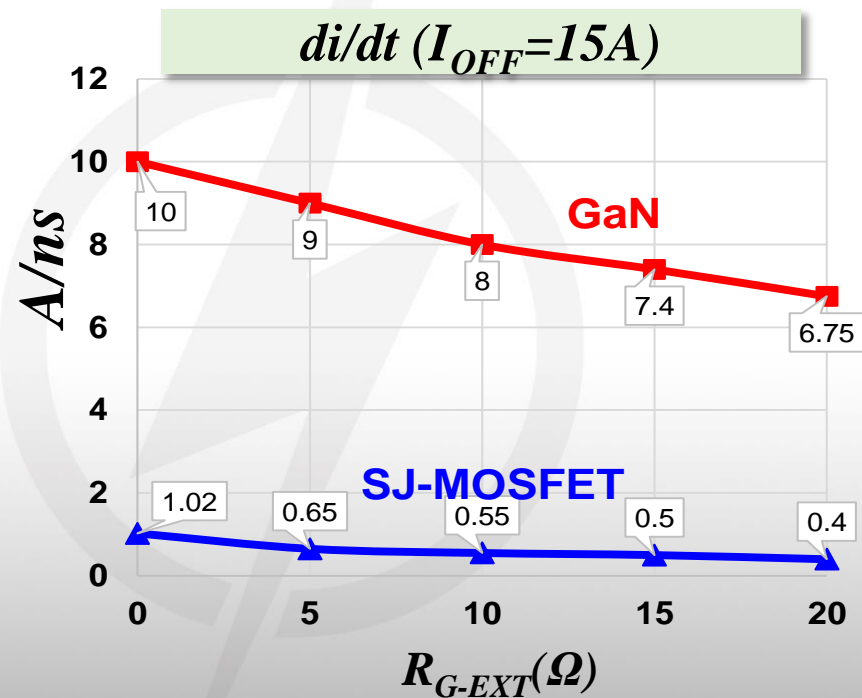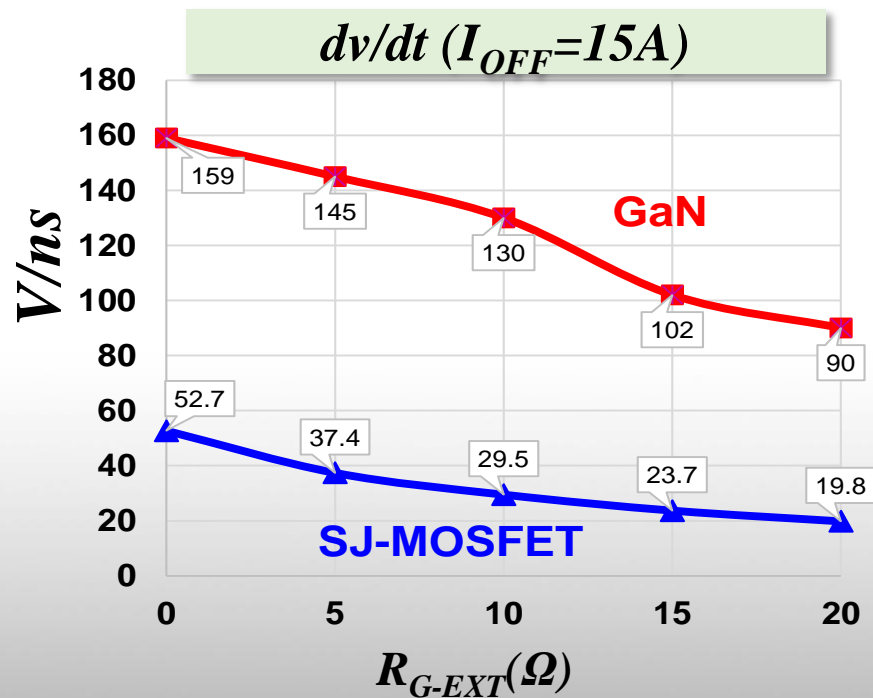
$$I_{D_Coss} = I_{D_Coss1} + I_{D_Coss2} \approx I_{D_Coss1}$$



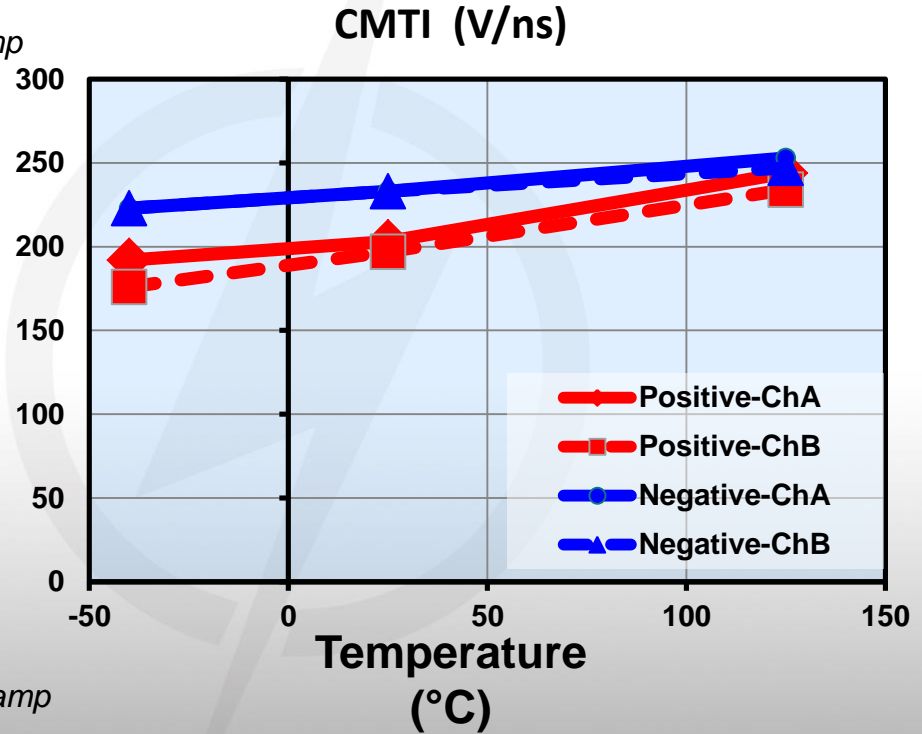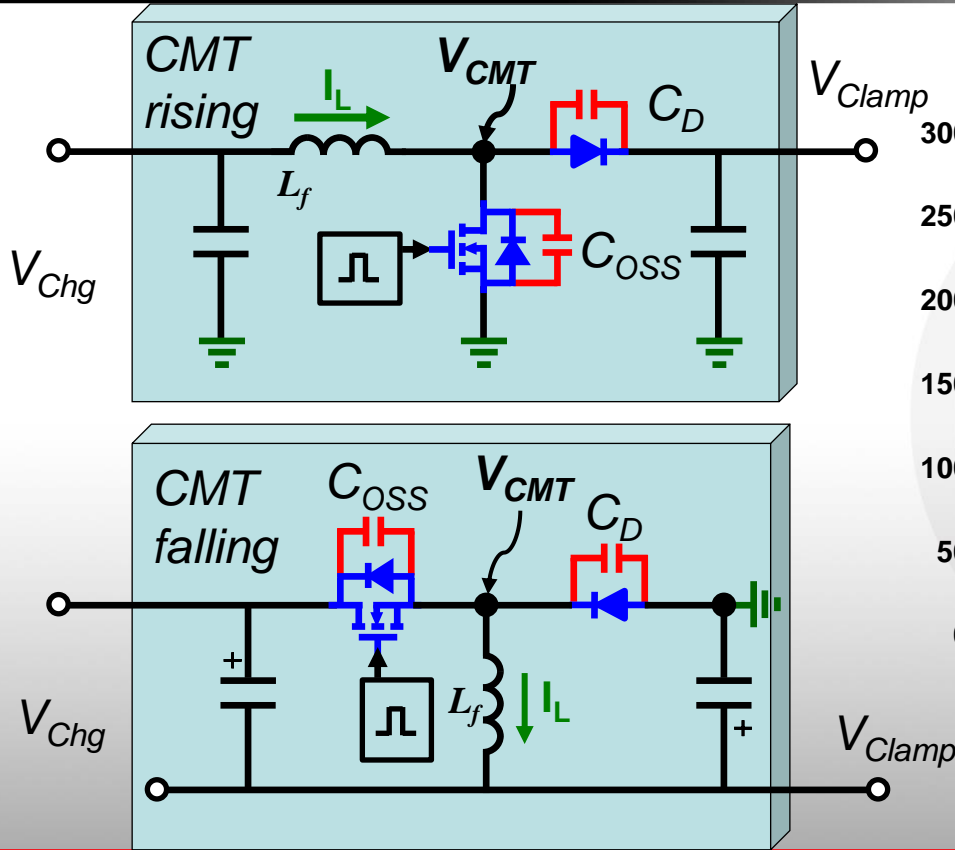

Gate Drivers

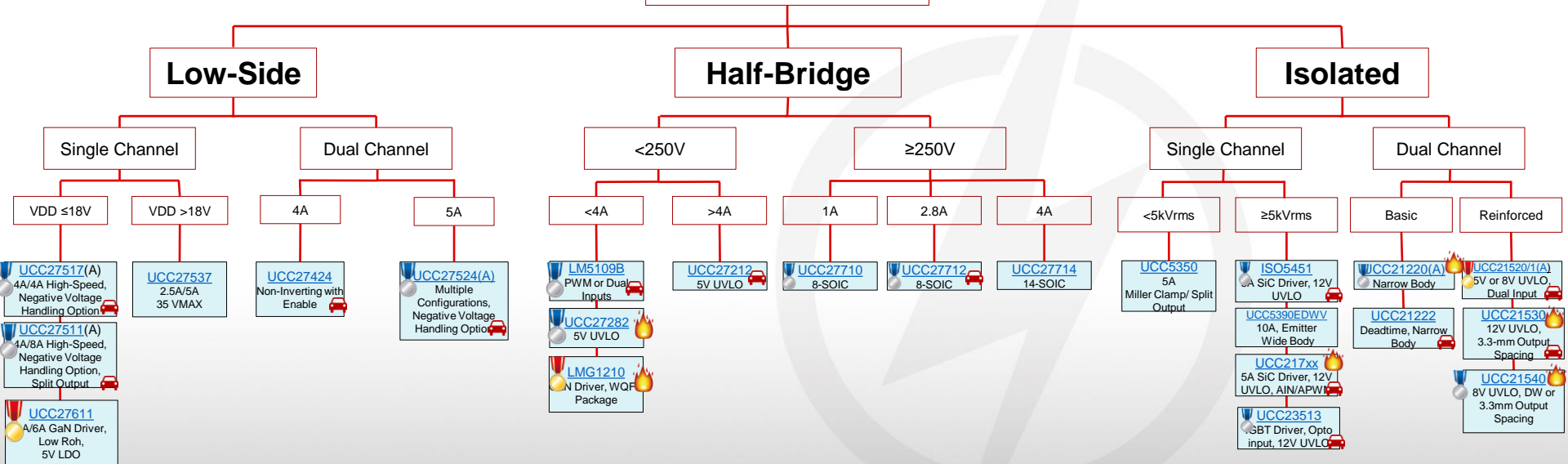

	AEC-Q100 Qualified		Cost-Competitive Part
	RTM'd/APL'd in last 4 Quarters		Premium Part

Production

- ❑ Gate driver fundamentals and in-system consideration
- ❑ Low side, high- and low side, isolated gate driver
- ❑ Parasitics in gate driver?
- ❑ Gate driver soft/hard switching difference?
- ❑ Strong gate driver and MOSFET nonlinear C_{oss} ?
- ❑ Common mode transient immunity(CMTI), dV/dt and di/dt through parasitics
- ❑ Power supply for isolated gate driver in UPS, server and Telecom

➤ **Sample TI's New Isolated Gate Drivers:**

- ✓ **UCC21540:** <http://www.ti.com/product/UCC21540/samplebuy>
- ✓ **UCC21220A:** <http://www.ti.com/product/UCC21220A/samplebuy>
- ✓ **UCC21710-Q1:** <http://www.ti.com/product/UCC21710-Q1/samplebuy>
- ✓ **UCC23513:** <http://www.ti.com/product/UCC23513/samplebuy>

*Thank
You*

