

***Input protection introduction:
Hot-swap/eFuse/Power switch/Oring***

Analog FAE : Redick Lee



Agenda


- *Hot-swap*
- *Power switch*
- *eFuse*
- *Oring*




Why Protection Devices?

- High Availability Systems
 - Cannot be shutdown
 - Redundancy, No single point of failure
 - Live maintenance
- Who uses High Availability Machines
 - Follow the money
 - Stock markets, Amazon
 - Mission Critical
 - Air traffic control, Google
- User Expectation


Hot Insertion without a Hot-Swap

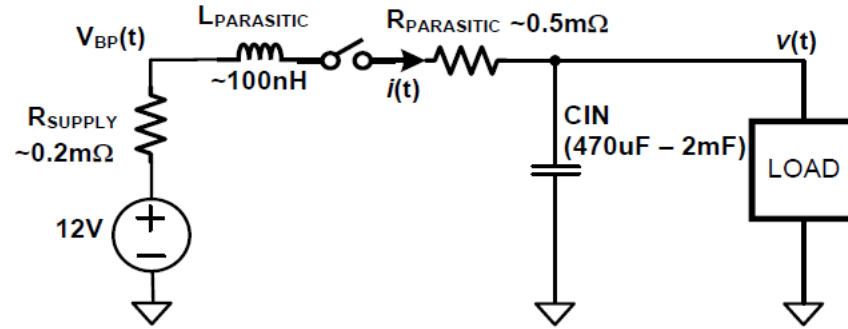

Contact Current Waveform

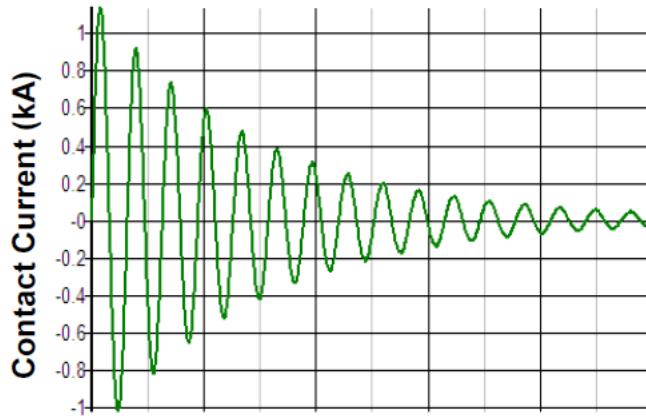

Load Voltage Waveform

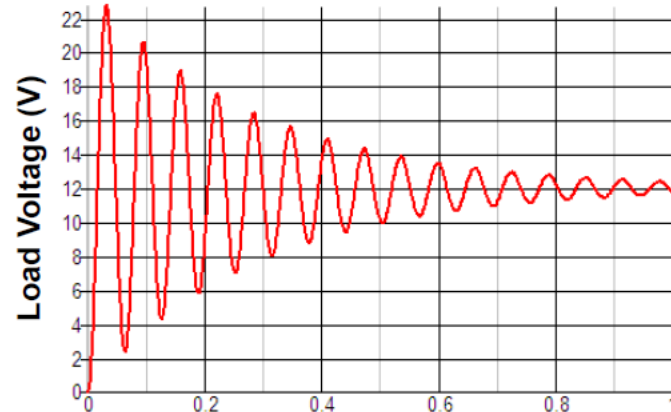


What Problems are Addressed by Protection Circuits?

- Inrush Currents
- Damage
 - Connector Pins
 - Board Etch
 - Components
- Disrupt The Backplane Voltage
 - Backplane voltage droop can shutdown the system

SUPPLY



CONNECTORS

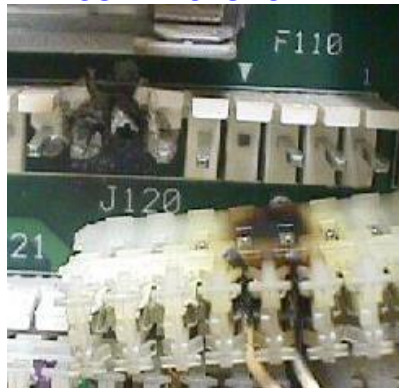

POWER FET



LOAD




What Problems are Addressed by Protection Circuits?


- Manage Power-on
 - Power Limit
 - dv/dt
 - di/dt
- Shutdown
 - Over Voltage
 - Under Voltage
 - Current Overload
 - Load Shorted
 - Latchoff
 - Re-try

Components of a Protection Circuit

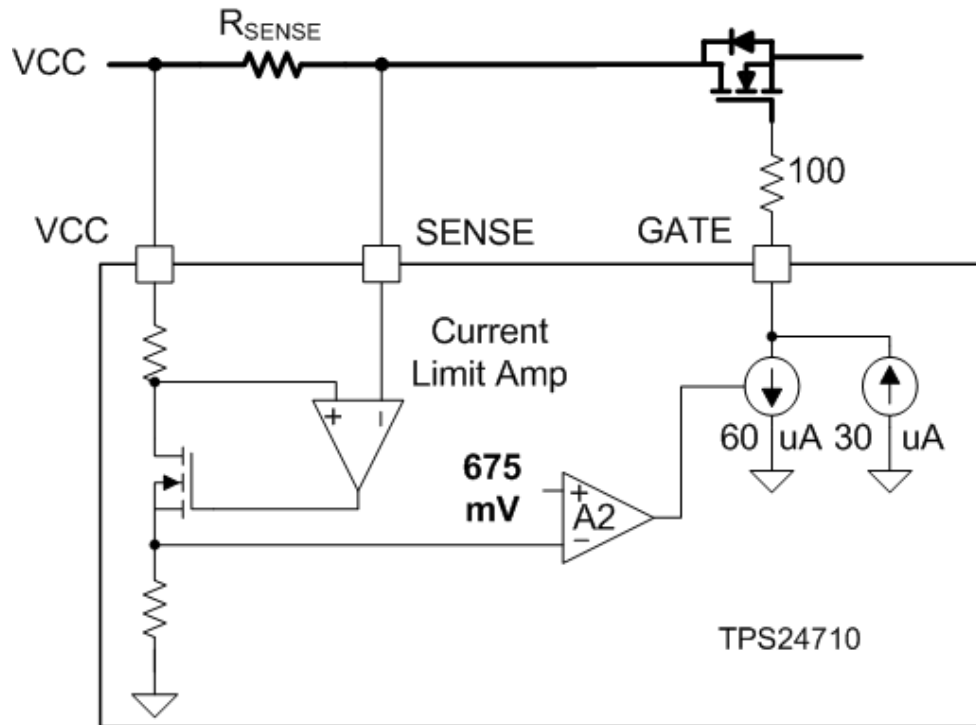- MOSFET
 - Pass element controls flow of current to the output
- Sense Resistor
 - A few milliohm resistor senses current
- Controller
 - Reads the current sense
 - Operates the MOSFET
- Over-load
- Fast Turn Off



What is circuit protection?

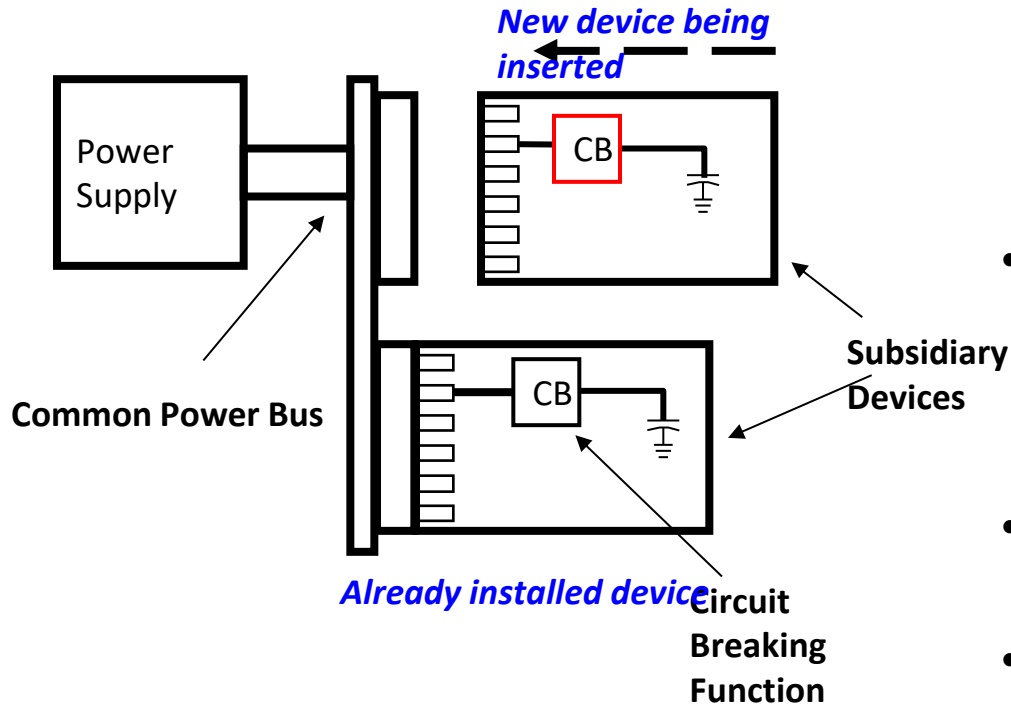

- Without circuit protection, current inrush to a subsidiary device during live insertion is limited by the ESR of the capacitor's DC contact resistance.
 - Typically over **80 Amps** for a 3A board or device!
- Without a Circuit Breaker / inrush-limiter there will be a logic glitch or an over designed power supply
- Circuit Breaker Limits Current Inrush and load to less than 4A (or some preset level)


Hot Swap: Power Glitch Issues

Without a Circuit Breaker, current is limited by the ESR of the capacitor's DC contact resistance.

- Typically over 80 Amps for a 3A board!

Without a Circuit Breaker there will be a logic glitch or an over designed power supply

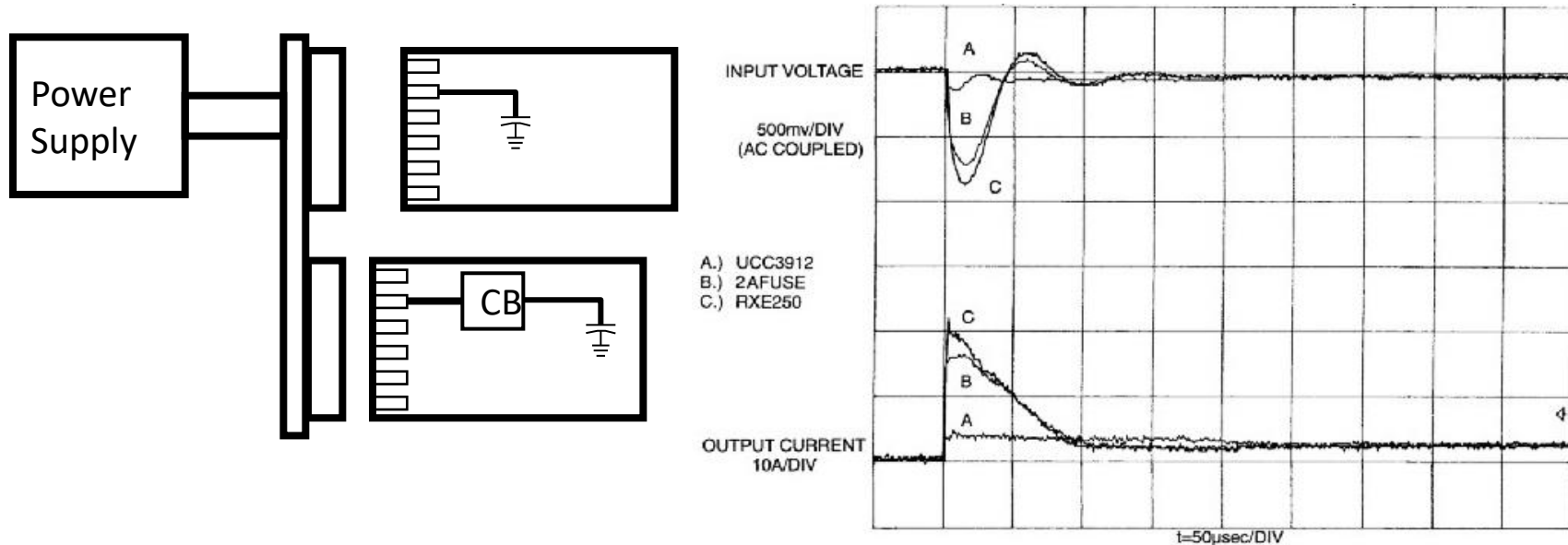Circuit Breaker Limits Current Inrush and load to less than 4A




Circuit-breaking vs. Current-limiting

Circuit-breaking

- Time limit above fault current threshold exceeded
- Short-circuit event (instant)

FET gate driven OFF


- No Conduction

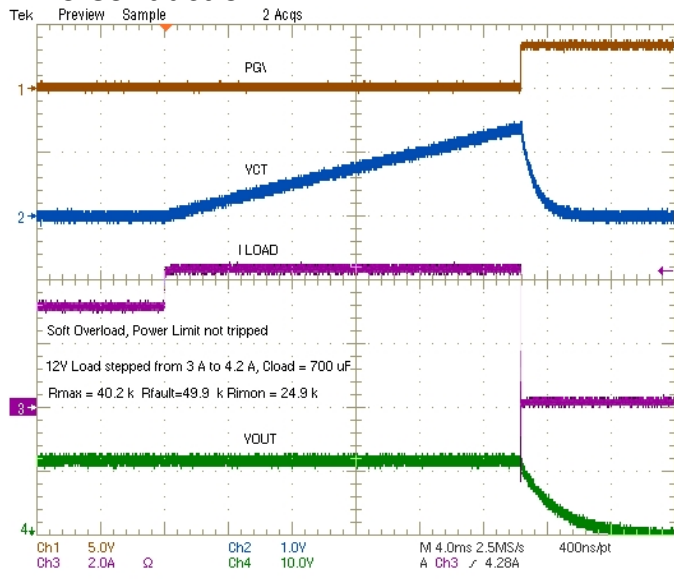

TPS2420 going from 3A to 4.2A, Fault timer limit reached

Current-limiting

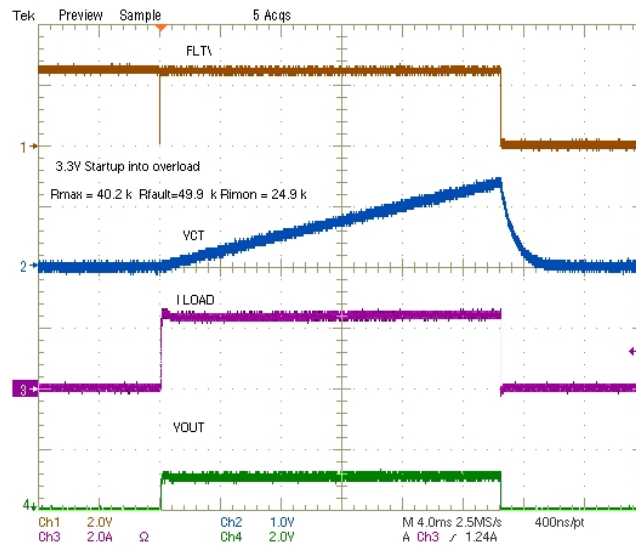- Current-limit threshold exceed
- Gate drive ramps down
 - Current-limited to desired level
 - Output voltage may droop



TPS2420 3V startup into overload – current-limited.
(Circuit not disconnected until Ct limit reached.)

Fault Timers

Hot swap managers must allow enough time for the fault condition on startup to charge bypass capacitors.

Retry Duty cycles are typically 2 - 3 % on fault conditions for auto reset parts.

External FET versions may have an additional Power Limit adjustment to reduce the duty cycle.

Latch off parts are used on systems where faults should not occur

Fault times are adjusted by the Ct capacitor

Ct calculation requires knowledge of the load

- Bypass capacitance
- Load Current


$$\text{Fault time} = 27.8 * 10^3 * C_t$$

$$C_{out} (\text{max}) = (I_{\text{max}} - I_{\text{load}}) * \left(\frac{28 * 10^3 * C_t}{V_{\text{out}}} \right)$$

$$\left(\frac{28 * 10^3 * C_t}{V_{\text{out}}} \right)$$

After Fault Timeout

1. RETRY OPTION

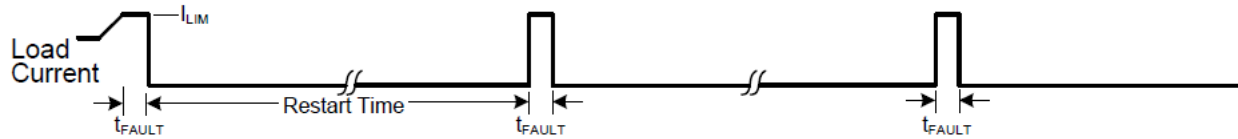


Restart time is typically several seconds

→ set by the timing capacitor C_T

→ circuit will continue to attempt restarts until the fault is removed

2. LATCH-OFF OPTION

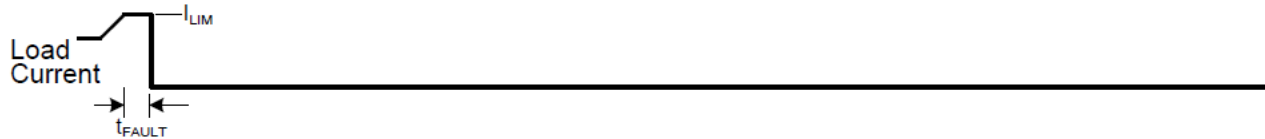


The circuit is restarted by:

→ cycling the input voltage off-on, or


→ by momentarily grounding the UVLO pin

Timer Cap Function – Fault Retry Delay

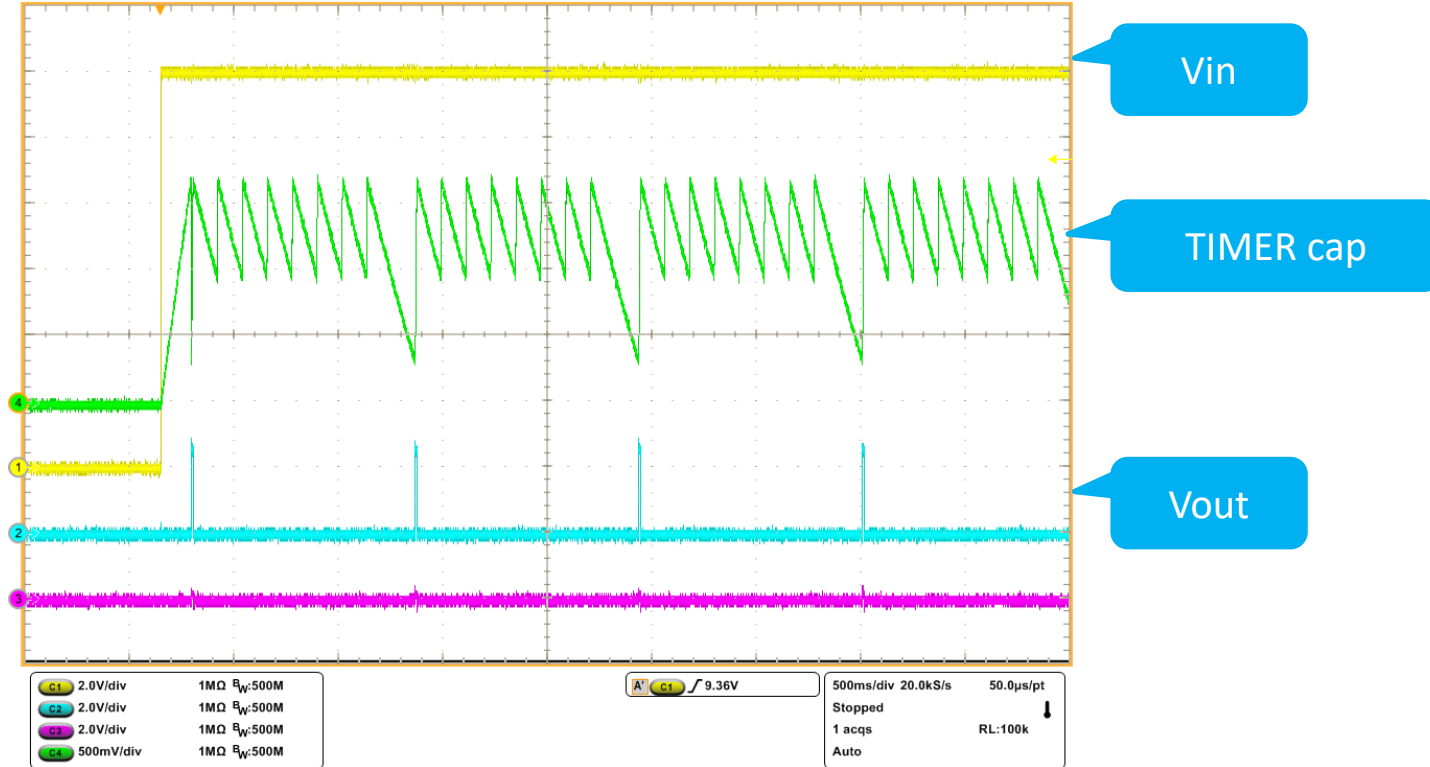


The hiccup time allows adequate cooling of pass MOSFET

Idealized Typical Startup Waveforms

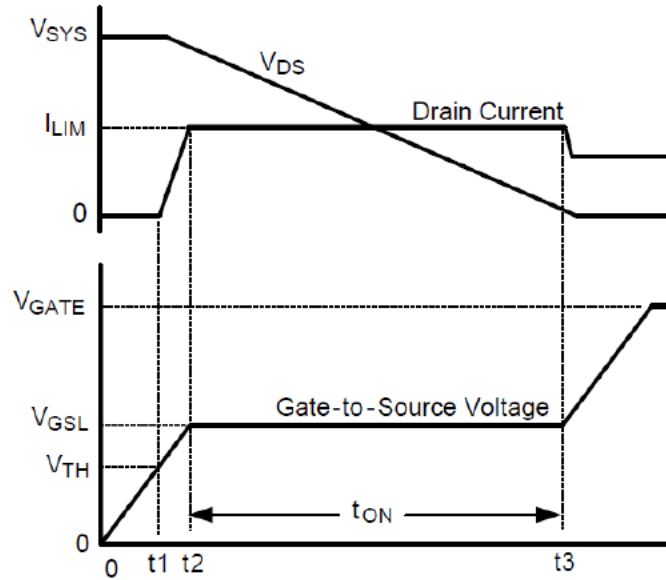

a) Current Limit Only

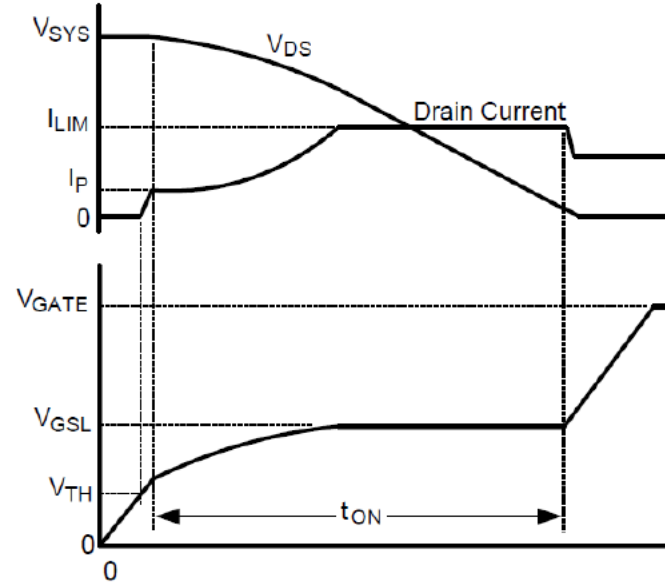


b) Power Limit and Current Limit

Common Design Errors SOA of FET Too Small

- **SOA = Safe Operating Area**
 - SOA Chart – Every FET has one
 - Defines Bounds of FET Operation
 - V_{DS_MAX} = Vertical Limit
 - I_{D_MAX} = Horizontal Limit
 - $R_{DS(on)}$ limits I_D at lower voltages
 - **Theoretical** $P_{MAX} = 3000\text{ W}$
- **Fault Time Is Critical**
 - Longer Fault time means bigger FET
 - Shorter Fault Time allows higher peak power
- **Most Stressful FET Events**
 - Startup into short
 - Shorted load while under full load

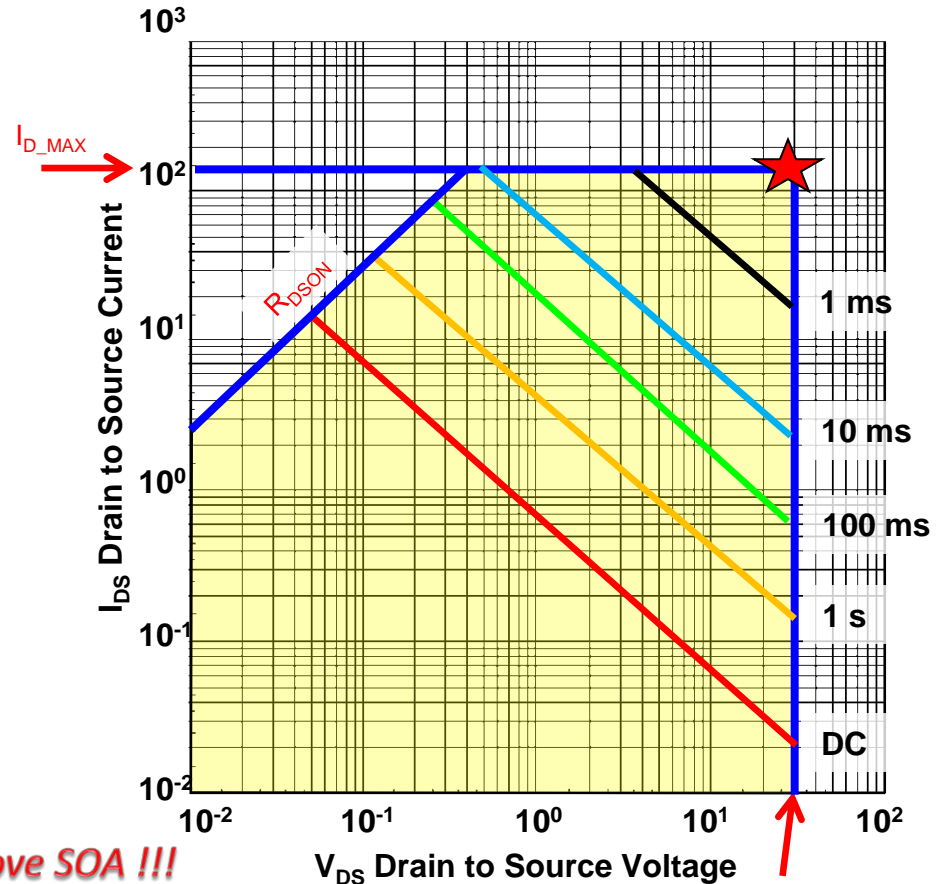Putting FETs in parallel does NOT improve SOA !!!



Common Design Errors

SOA of FET Too Small -

Example - 12 V, 50 A Server


- Without Power Limiting

- $P_{MAX} = I_{LIMIT} \times V_{SUPPLY} = 600 \text{ W}$
- $T_{SOA_MAX} = \sim 800 \text{ us}$

- With Power Limiting

- $P_{MAX_LIMITED} = 50 \text{ W}$
- As V_{DS} increases I_{LIMIT} is reduced
- $T_{SOA_MAX} = 10 \text{ ms}$
- Smaller FET can be used
- @ 50 A will start limiting when $V_{DS} > 1\text{V}$

- Common Error to Pick FET Too Small

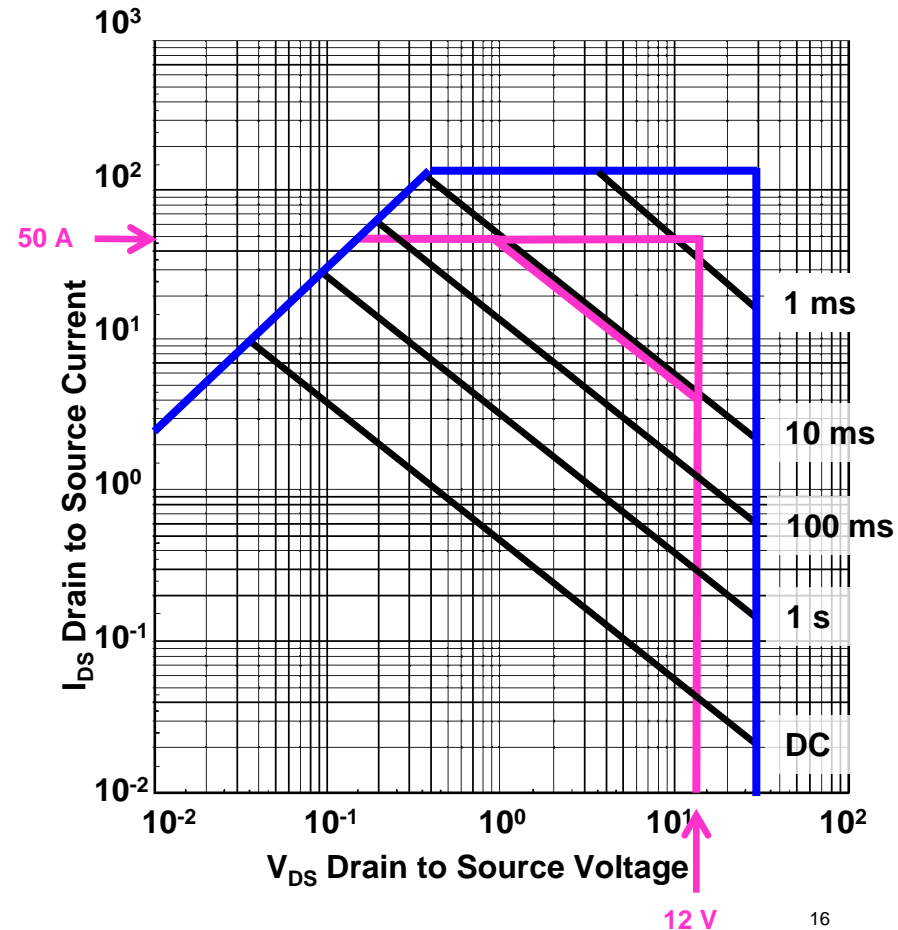

Common Design Errors Inadequate Transient Protection


- All wires are inductive
- Inductance stores energy
- When the FET turns off, voltage spikes occur

$$E = \frac{LI^2}{2}$$

$$V = L \frac{di}{dt} \quad \frac{di}{dt} \Rightarrow \infty$$


Positive Spikes at Input to Switch/FET

Negative Spikes at Output of Switch/FET

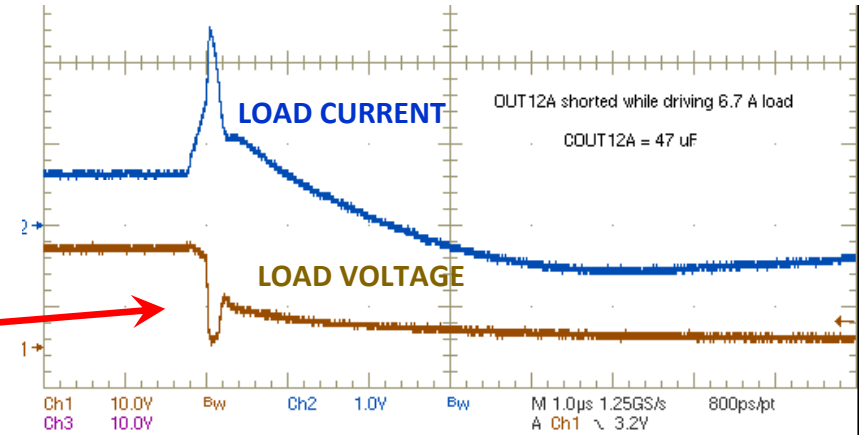


Common Design Errors Inadequate Transient Protection

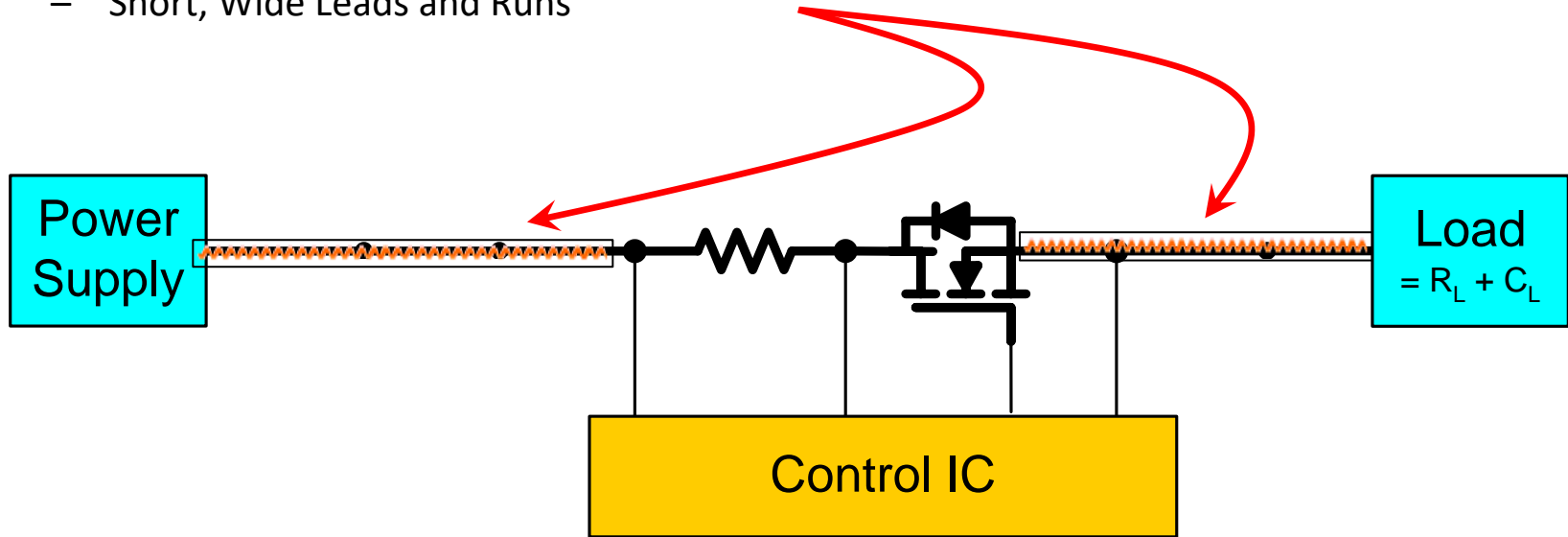- To squelch inductive spikes from supply / load leads
 - Caps and/or TVS at UUT Input to clamp positive spike
 - Schottky Clamp across output to clamp negative spike
 - Short, Wide Leads and Runs



Potential Causes for Device Damage

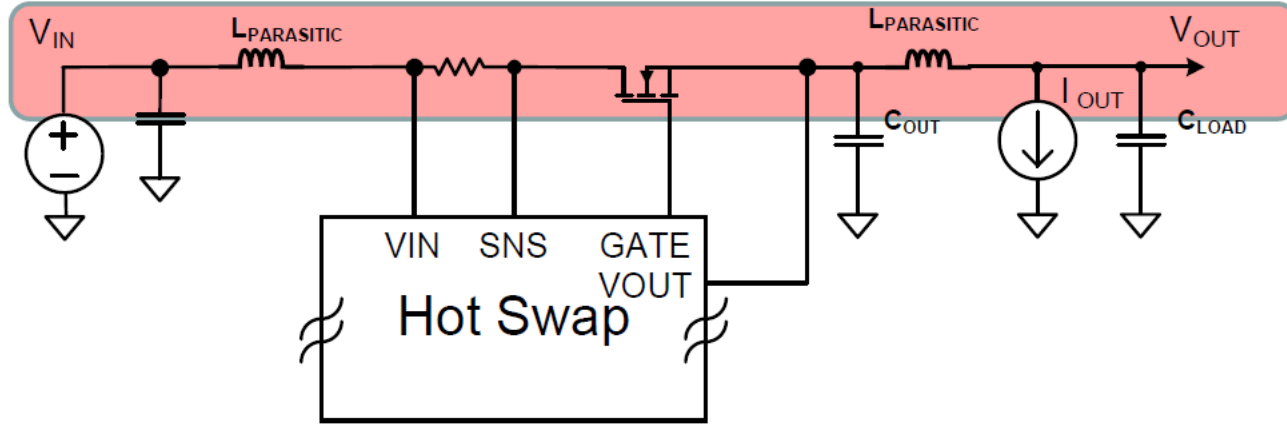


- Parasitic Inductance on the Input and Output of a hot-swap can be detrimental to the reliability and performance of the hot-swap, especially when high currents are involved.
- By understanding the effects of these inductances, measures can be taken to insure robust operation.

Potential Causes for Device Damage

Input Supply Surge During a Fault

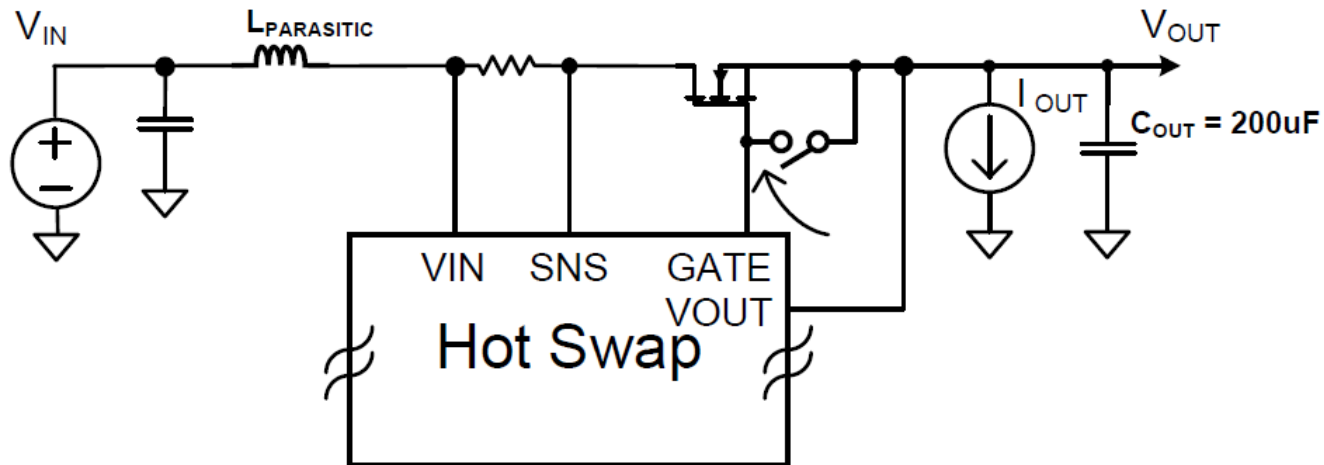
- The classic voltage supply inductive surge problem can cause over-voltages on the input of a hot swap
- Consider the following circuit. It is designed to simulate a circuit-breaker condition on a hot swap.



Input Supply Surge

BEFORE THE GATE IS SHORTED TO V_{OUT}

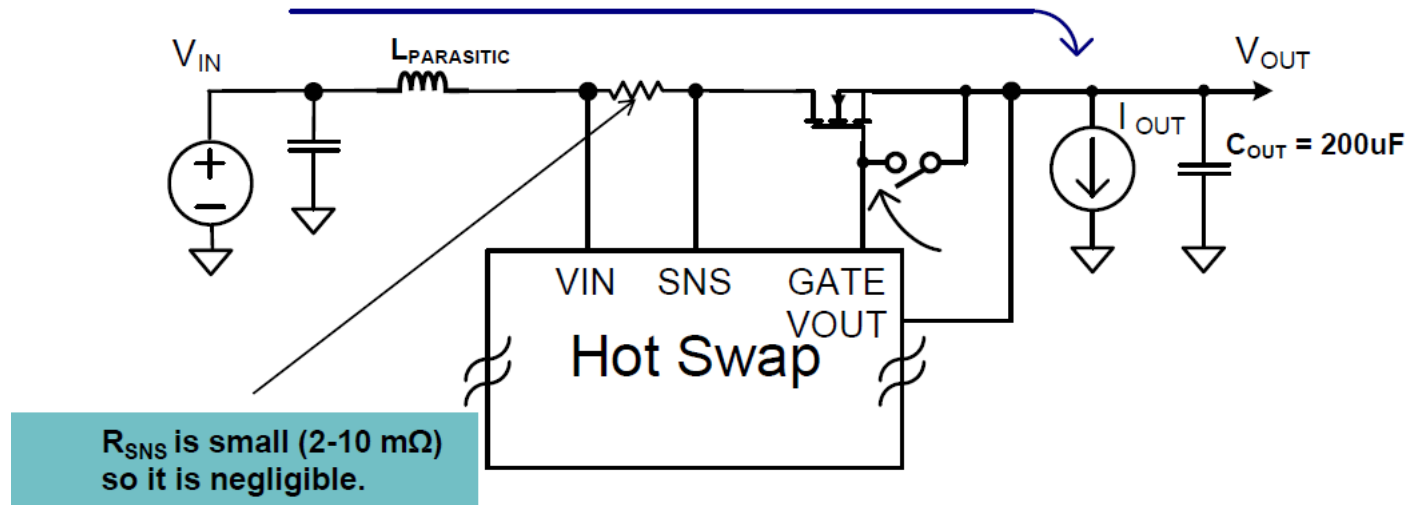
→ I_{OUT} runs continuously through the pass FET, and $L_{PARASITIC}$




Input Supply Surge

AFTER THE GATE IS SHORTED TO VOUT

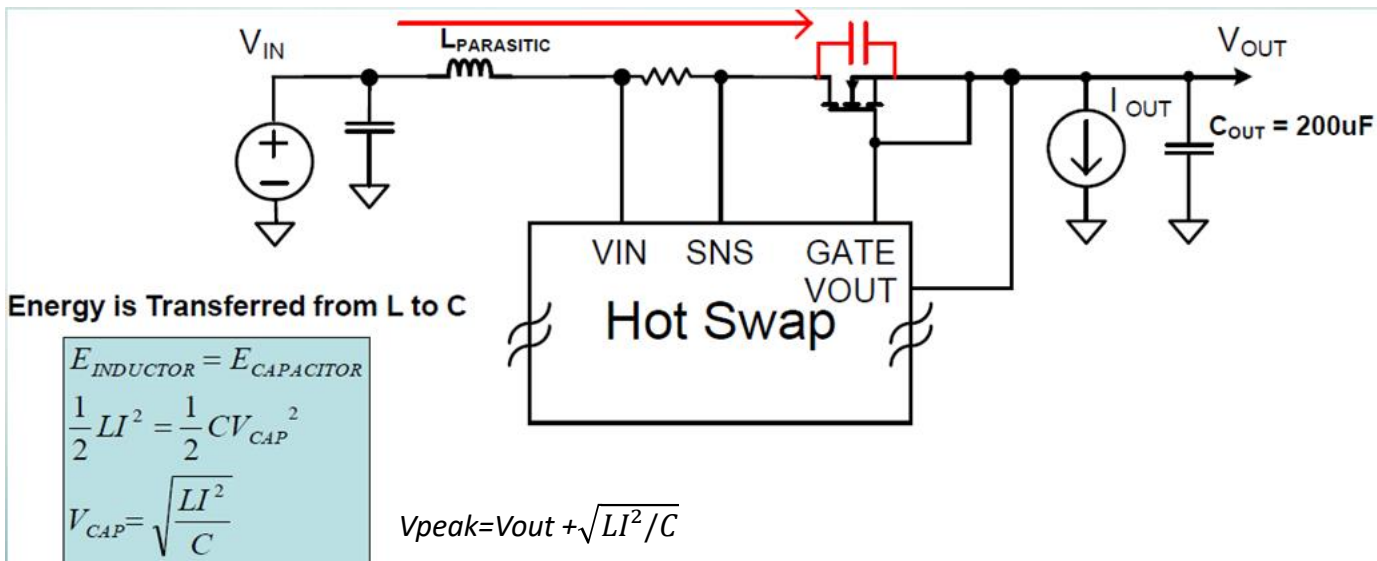- The pass FET stops conducting, and the current in L_{PARASITIC} charges the pass FET capacitance across the FET.



Input Supply Surge During Test

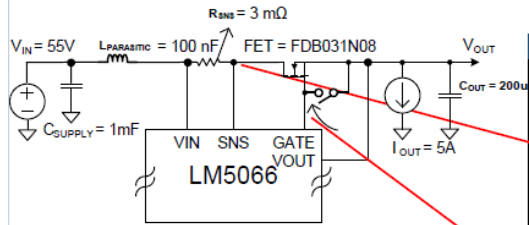

$V_{PEAK} = 104.8\text{ V}$
This is greater than ABS MAX!

Theoretical Calculation

$$V_{peak} = V_{out} + \sqrt{\frac{LI^2}{C}}$$

$$V_{peak} = V_{out} + \sqrt{\frac{100\text{ nH} \times 5^2}{1000\text{ pF}}}$$

$$= 105V$$



Key TVS Specifications

| Part Number (Uni) | Part Number (Bi) | Marking | | Stand off Voltage V_R (Volts) | Voltage V_{max} (Volts) @ I_T | | Current I_T (mA) | Clamping voltage V_C @ I_{pp} (V) | Peak Pulse Current I_{pp} (A) | Reverse Leakage I_R @ V_R (μ A) | Agency Approval |
|-------------------|------------------|---------|-----|---------------------------------|-----------------------------------|------|--------------------|---------------------------------------|---------------------------------|--|-----------------|
| | | UNI | BI | | MIN | MAX | | | | | |
| SMDJ5.0A | SMDJ5.0CA | RDE | DDE | 5.0 | 6.40 | 7.00 | 10 | 9.2 | 326.1 | 800 | X |


1. Ensure VBR is equal to or above max DC operating level
2. Ensure VC(max) at circuit breaker setpoint is less than the pass MOSFET & hot swap controller voltage ratings
3. Higher power rating TVS devices have a sharper knee characteristic

Note: $PPP = VC(max) * IPP$

Recommended TVS components:

12V rail: Littelfuse 5.0SMDJ15A


\pm 48V rail: Littelfuse 5.0SMDJ60A

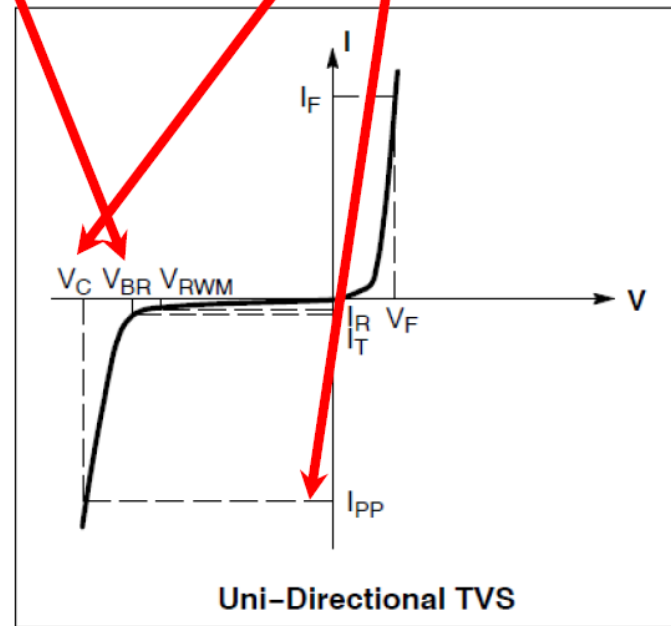

Causes for FET damage


Possible Causes

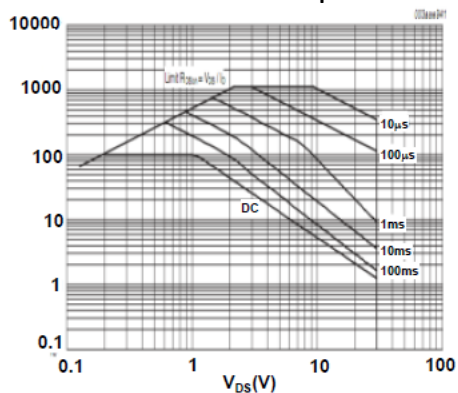- Improper Power Limit Setting or FET Selection.
- Start with 50% derating for desired SOA time
- Improper Timing Capacitor Selection
- Set timer to be 20% below desired SOA timeout
- Improper Clamping of input/output Voltage
- Excessive FET temperature (SOA is for TC=25C)
- Check RDSON and Package, RthJC
- Monitor FET temperature with remote Diode(LM25066)




PSMN1R0-30YLC

TI Information – Selective Disclosure

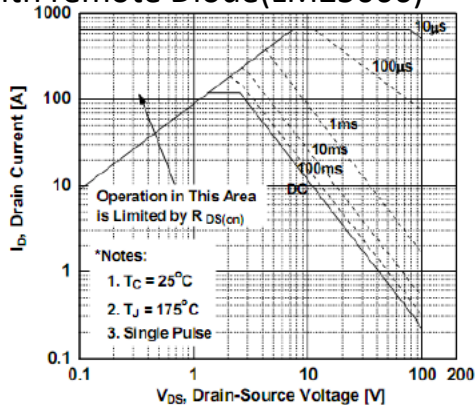

FDB047N10 100V

IR DirectFETs are not recommended.

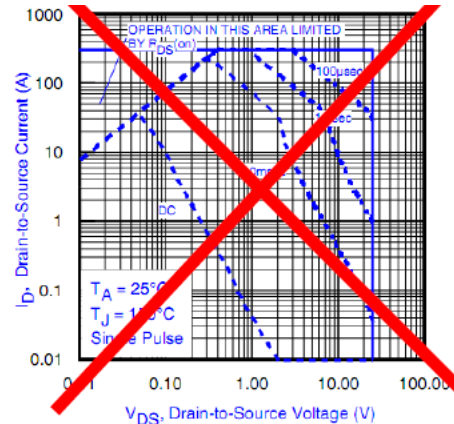

IRF6798 (BAD)

Building Blocks for your Design

Load Switch & eFuse



Load Switches

- Power savings and simplify power sequencing
- Protects against inrush current with integrated soft start



eFuses

- Protects against over-voltage, over-current and inrush events.
- Saves board space
- Increases reliability - UL/IEC recognized



Smart High-side Switches

- Increases short-circuit reliability with selectable current limit
- Improves diagnostics with high accuracy current sensing.

Signal Chain



Signal Switches

- Resolves constrained I/O and address conflict
- Improves signal integrity



I²C Solutions

- Isolates signals & simplifies board routing
- Low-power/high-speed technology
- Low-noise audio and THD performance



Voltage Level Translators

Bridges I/O voltage domains between MCU/MPU and peripherals with:

- Low voltage support (down to 0.8V)
- Compact packaging

Circuit Protection



High Performance TVS Diodes

- Protects system from damaging external transients (ESD, EFT, Surge)
- Protects high speed interfaces and sensitive end equipment



Integrated ESD Protection


- All-in-one protection for many popular interfaces like USB and HDMI
 - ESD, EMI, Current Limit Switch, OVP
- USB Type-C Short-to-VBUS protection for CC/SBU



Automotive ESD Protection

- AEC-Q100, AEC-Q101
- Short-to-Battery/Ground
- Over Current Protection

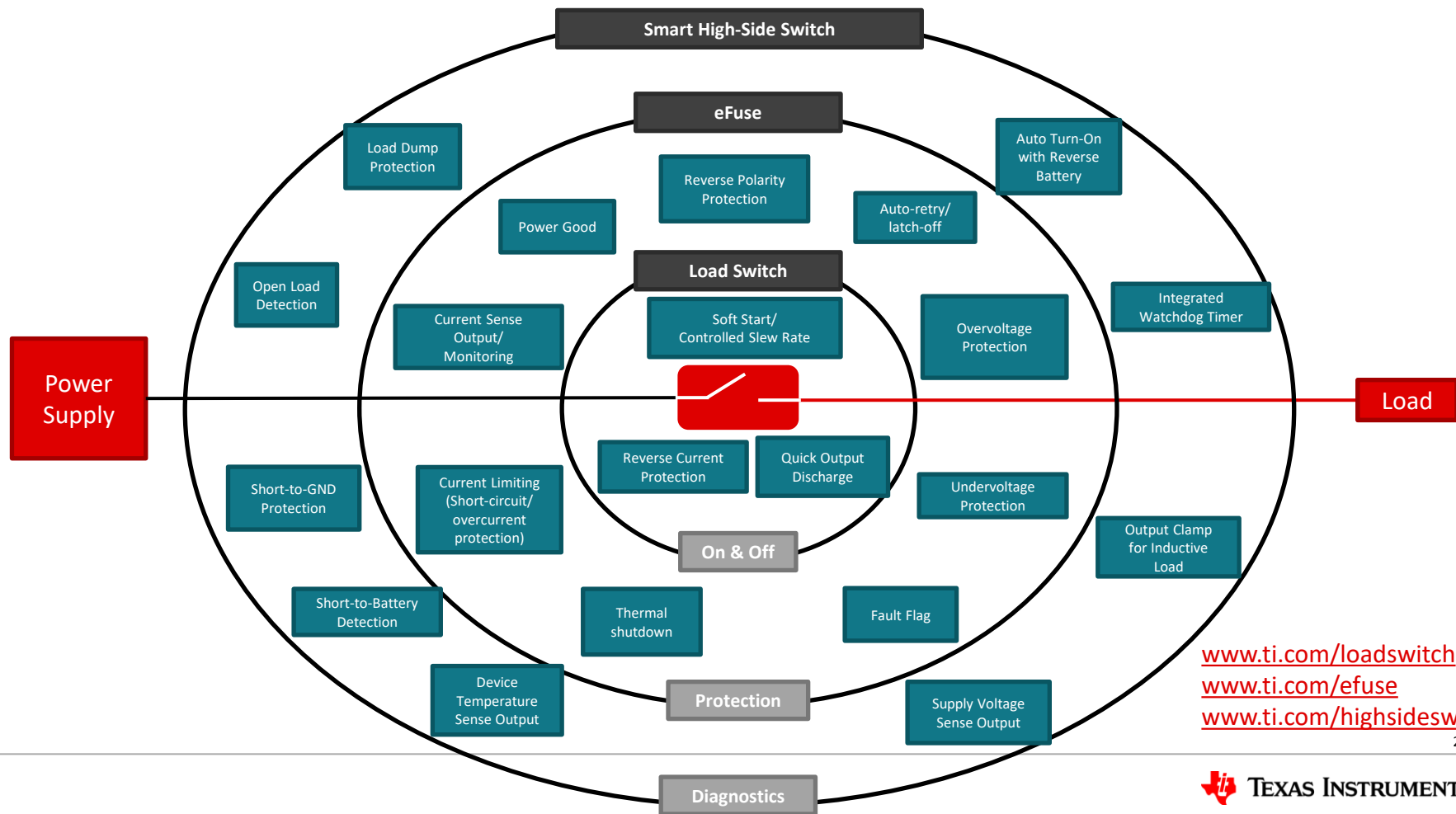Load Switch, eFuse & Smart High-Side Switch



www.ti.com/loadswitch
www.ti.com/efuse
www.ti.com/highsideswitch

Load Switch, eFuse & Smart High-Side Switch

Load Switches

Power Distribution & Savings

Benefits

- Extends battery life
- Simplifies power sequencing
- Mitigates inrush current damage
- Saves space & reduces solution size

Parameters

- **Ron:** 4 - 435 m Ω
- **Vin:** 0.65 - 6.0 V
- **I_{max}:** up to 15 A
- **Size:** down to 0.64 mm²
- **Package:** WCSP, SOT-23, SON, QFN

Applications



www.ti.com/LoadSwitch

eFuses

Power Protection

Benefits

- Protects against under/over-voltage, over-current, and inrush events
- Maximizes equipment uptime & reduces maintenance costs
- Prevents failure during hot-plugging, hot-swapping & transient events
- Faster time to market – UL recognized

Parameters

- **Ron:** 3 – 150 m Ω
- **Vin:** 2.5 – 55 V
- **I_{max}:** up to 12 A
- **Size:** down to 9 mm²
- **Package:** SON, QFN, SOIC, TSSOP

Applications



www.ti.com/eFuse

Smart High-Side Switches

Diagnostics & Protection

Benefits

- Increased reliability against short-circuit
- Accurate, real-time load diagnostics
- Robust solutions withstands automotive requirements – AEC-Q100/ISO

Parameters

- **Ron:** 4 m Ω – 1 Ω
- **Vin:** 3 - 40 V
- **I_{max}:** up to 90 A
- **Size:** down to 32 mm²
- **Package:** HTSSOP (PWP)

Applications




www.ti.com/HighSideSwitch

Load Switch Overview

- **Extend battery life** by reducing standby leakage current. Turn off unused subsystems w/load switches: WiFi/BT, LCD, SD Card
- **Save space** and reduce solution size by integrating discrete circuitry into a load switch (2+ FETs w/Resistors & Capacitors)
- **Simplify power sequencing** by implementing point of load control with load switches. Power on/off each rail with GPIO
- **Mitigate inrush current damage** to the system with integrated “Soft Start” slew rate /rise time control.


Replace these 7+ components...

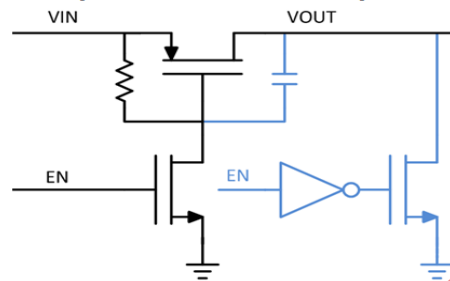

With this 1 device:



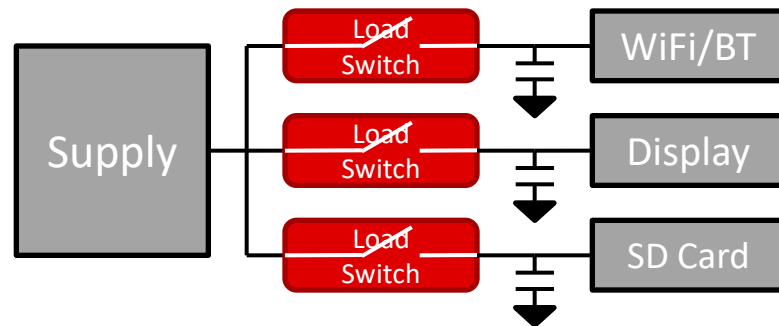Smaller, less components, more features, easier design!




Manage power distribution for subsystems

| Load Switch | Features |
|-----------------|---|
| TPS22975 | 5.7V, 6A, 16mΩ, Adjustable Soft Start/ Rise Time (CT), Quick Output Discharge (QOD), Thermal Shutdown, QFN-8 pkg (0.5mm pitch) |
| TPS22990 | 5.5V, 10A, 3.9mΩ, Adjustable Soft Start/ Rise Time (CT), Quick Output Discharge (QOD), Integrated Power Good (PG), QFN-10 |
| TPS22918 | 5.5V, 2A, 52mΩ, Adj. Soft Start/ Rise Time (CT), Configurable Quick Output Discharge (QOD), leaded SOT23-6pin, AEC-Q100 Available |
| TPS22915 | 5.5V, 2A, 38mΩ, Fixed Soft Start/ Rise Time, Optional Quick Output Discharge (QOD), 0.78mm x 0.78mm WCSP-4 (0.4mm pitch) |
| TPS22976 | 5.7V, 6A, 2-channel, 16mΩ, Adjustable Soft Start/ Rise Time per channel (CT1 & CT2), QOD, Thermal Shutdown, QFN-14 package |

What Is A Load Switch?

Load Switch

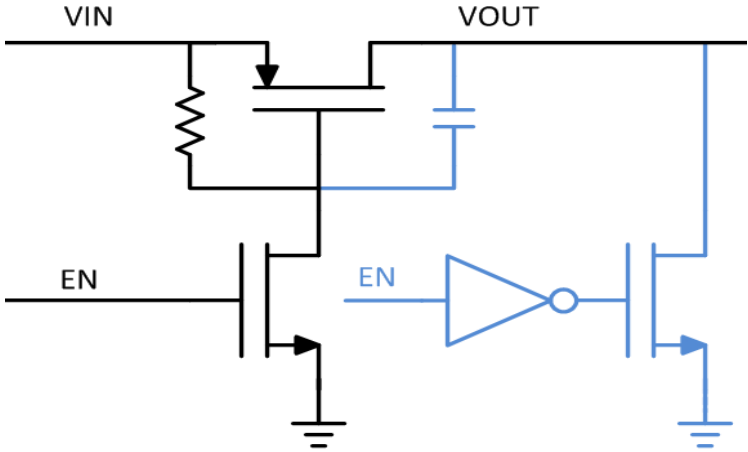Load switches are electronic relays used to turn on/off power supply rails.



Space Savings


Reduced Inrush Current

Extended Battery Life

Broad Portfolio


eFuse Overview

- **Integrated FET & current sense** an active circuit protection device that commonly replaces fuses and Polyfuse/PTC
- **Prevents failure** during hot-plug/swap by protecting against under/over-voltage, over-current, and inrush events
- **Save Space** and reduced solution size by integrating discrete protection circuitry
- **Faster Time to Market** and increased reliability through UL/IEC recognition

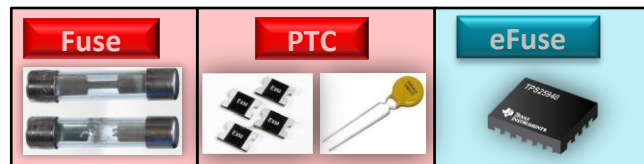

| | | | |
|----------------------|----------------------------------|--|--|
| After Fault: | ✗ Broken after fault | ✓ Auto-retry | ✓ Auto-retry; latch off |
| Reliability: | ✗ Must be replaced | ✗ R_{ON} increases after fault | ✓ Not damaged by fault |
| Time to trip: | ✗ Slow trip (s/ms) | ✗ Slow trip (ms) | ✓ Fast trip (<1.5 us) |
| Accuracy: | ✗ Needs time to heat up and melt | ✗ Current limit depends on ambient temp. | ✓ Up to $\pm 2\%$ current limit accuracy |

| eFuse | Features |
|-----------------|--|
| TPS2660x | 60V, 2A, 150mΩ, ILIM, CT pin, RCB, ISNS, RPP, OVP HTSSOP |
| TPS25940/2/4 | 18V, 5.2A, 42mΩ, ILIM, CT pin, RCB, ISNS, OVP, QFN |
| TPS25921A/L | 18V, 1.6A, 87mΩ, ILIM, CT pin, OVP, SOIC |
| TPS25925x/6x | 18V, 5A, 30mΩ, ILIM, CT pin, OVC, SON |
| TPS25923x/4x/7x | 18V, 5A, 28mΩ, ILIM, CT pin, OVC, BFET, SON |

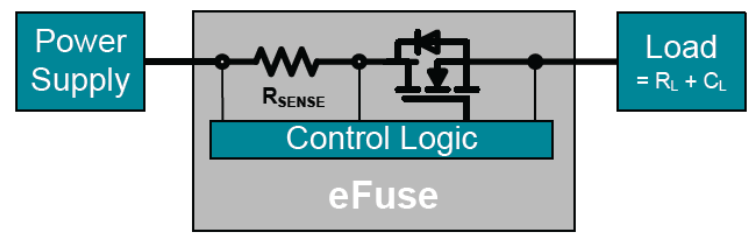


Highly Integrated Protection Features

What Is An eFuse?

eFuse

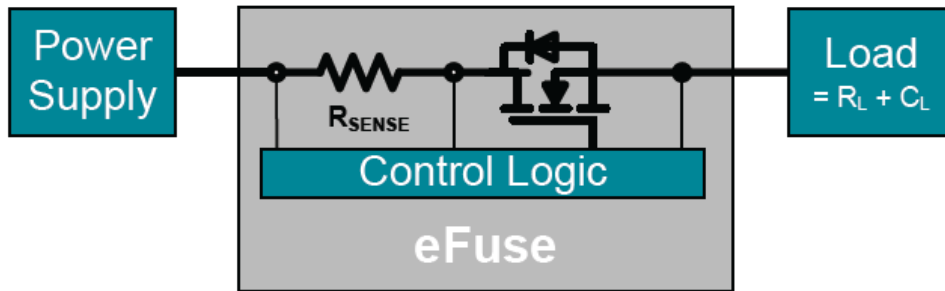An active circuit protection device with an integrated FET to control load current



Integrated Advanced Circuit Protection


Stable, Reliable Current Limit & Short Circuit

Reduced Inrush Current

UL Recognition: 60950 & 2367

33

Integration

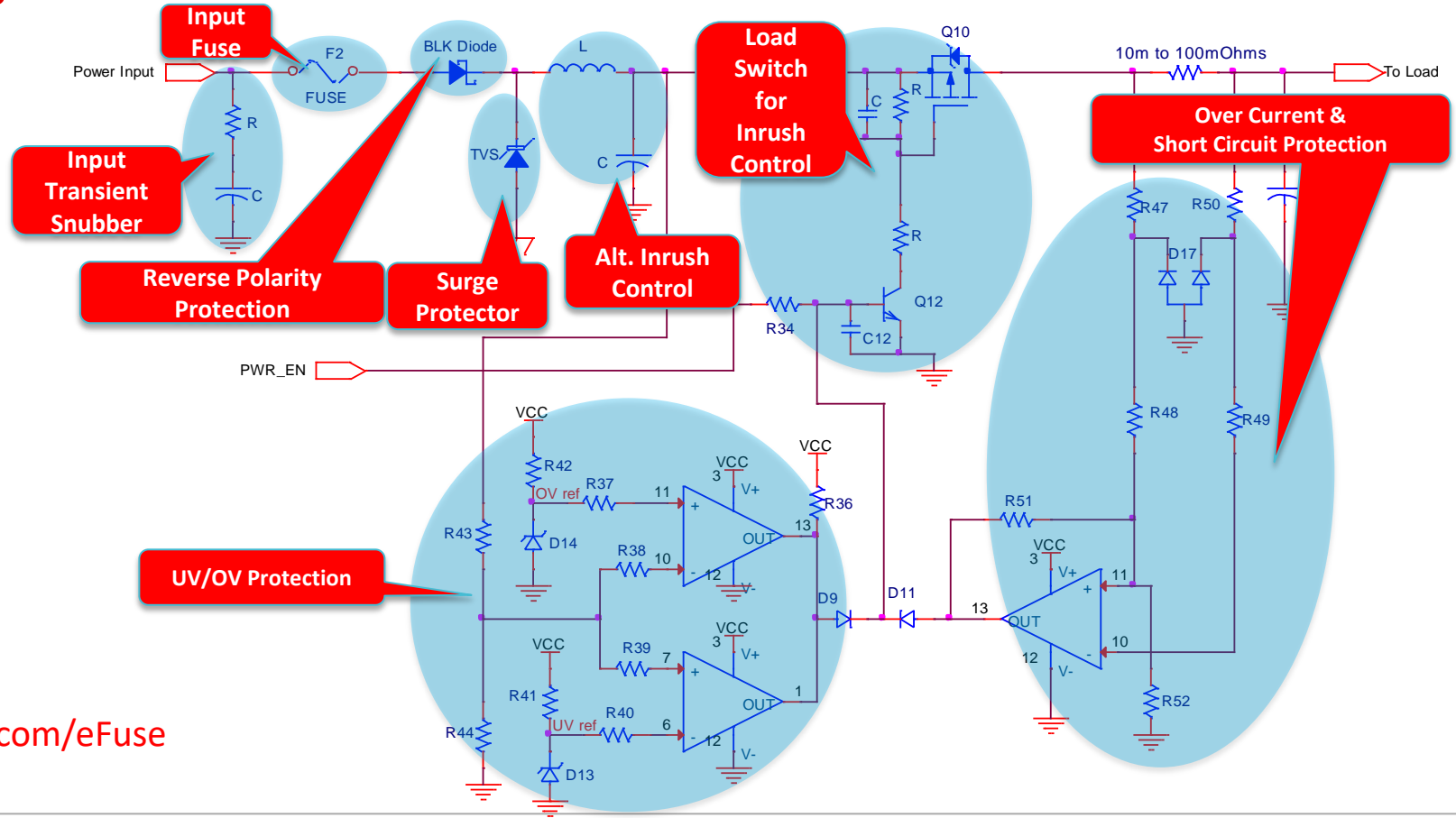

ti.com/eFuse

eFuse Features

Adjustable Current Limit, Inrush

- ✓ More flexibility in System design

Short Circuit protection

- ✓ Very fast (<200nS) Robust protection of system during short circuit situations

Over & Under Voltage protection

- ✓ Programmable OVP & UVLO help eliminates supervisory circuits


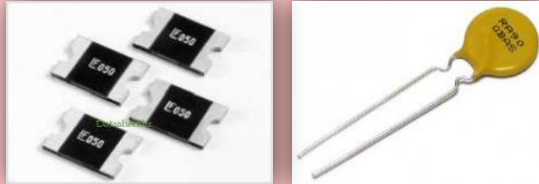
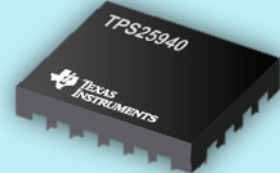
Reverse Current & I/P Voltage Protection

- ✓ Protects against miswiring {Reverse polarity i/P}
- ✓ Reserves holdup capacitor charge during power failure (Last Gasp)
- ✓ Addresses Power Muxing system challenges

Status output pins

- ✓ PG signal provides sequencing in the application
- ✓ Fault intelligence provided to the micro controller etc
- ✓ Real Time Analog Load current monitor

eFuse vs. Fuse vs. PTC

| | <div style="text-align: center; background-color: red; color: white; padding: 5px; margin-bottom: 5px;">Fuse</div>  | <div style="text-align: center; background-color: red; color: white; padding: 5px; margin-bottom: 5px;">PTC</div>  | <div style="text-align: center; background-color: teal; color: white; padding: 5px; margin-bottom: 5px;">eFuse</div>  |
|----------------------|---|---|---|
| After Fault: | ✗ Broken after fault | ✓ Auto-retry | ✓ Auto-retry; latch off |
| Reliability: | ✗ Must be replaced | ✗ R_{ON} increases after fault | ✓ Not damaged by fault |
| Time to trip: | ✗ Slow trip (s/ms) | ✗ Slow trip (ms) | ✓ Fast trip (<1.5 us) |
| Accuracy: | ✗ Needs time to heat up and melt | ✗ Current limit depends on ambient temperature | ✓ Up to $\pm 2\%$ current limit accuracy |

For More Information On eFuses & Load Switches:


Please visit: ti.com/efuse & ti.com/loadswitch

App Notes

- [Basics of Load Switch](#)
- [Fundamentals of On-Resistance in Load Switches](#)
- [Achieve 20A Circuit Protection and space Efficiency using Paralleled eFuses](#)
- [The TPS2660simplifies Surge and Power Fail Protection Circuit in PLC Systems](#)
- [Soft Startup of Brushless DC Fan with TPS25924 eFuses](#)

The logo for TI Designs, featuring the letters 'TI' in red and 'Designs' in black, with a circuit symbol above the 'i'.A red arrow pointing to the right with the text 'Application Notes' in white.A dark teal arrow pointing to the right with the text 'Training Video' in white.An icon representing the TI E2E Community, showing two stylized human figures in white speech bubbles on a teal background, with the text 'TI E2E™ Community' below.A dark grey arrow pointing to the right with the text 'Blogs' in white.

System Protection & Management Options

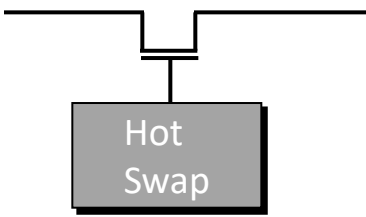


A schematic diagram showing a MOSFET circuit for hot swapping. A MOSFET is connected to a power source, and a load is connected to its drain. The MOSFET is labeled "Hot Swap".

Hot Swap

Inrush Current and Fault Protection

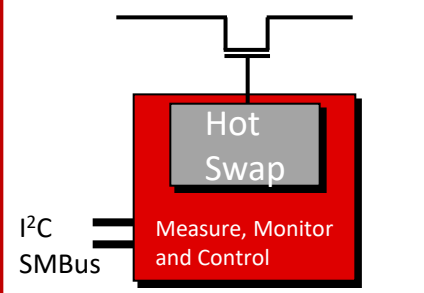- Highly reliable hot swap cores
- Power limiting protects MOSFETs



A schematic diagram showing a hot swap core with digital management. The core is labeled "Hot Swap" and "Measure, Monitor and Control". It is connected to an I²C/SMBus interface.


Hot Swap

Measure, Monitor and Control

I²C
SMBus

I²C/SMBus System Management

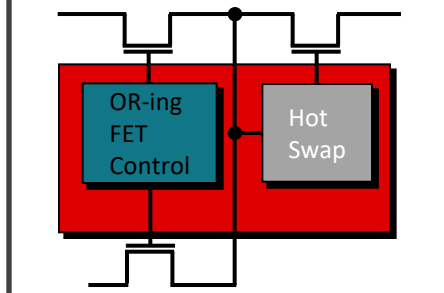- Integration of hot swap and digital system power management for system diagnostics
- PMBus support



A schematic diagram showing a multi-function hot swap core. The core is labeled "OR-ing FET Control" and "Hot Swap". It is connected to a power source and a load.

OR-ing FET Control

Hot Swap


Multi-function Integration

- Integration of key analog cores for additional PCB area savings

ORing Control (Linear v. Hysteretic)


Linear Control

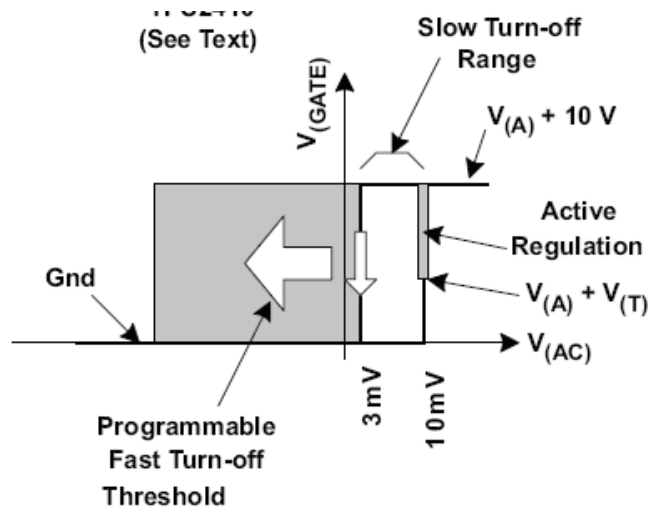- Regulates V_{AC} to 10 mV
- Reverse current less likely
- May not like reactive loads





Hysteretic Control

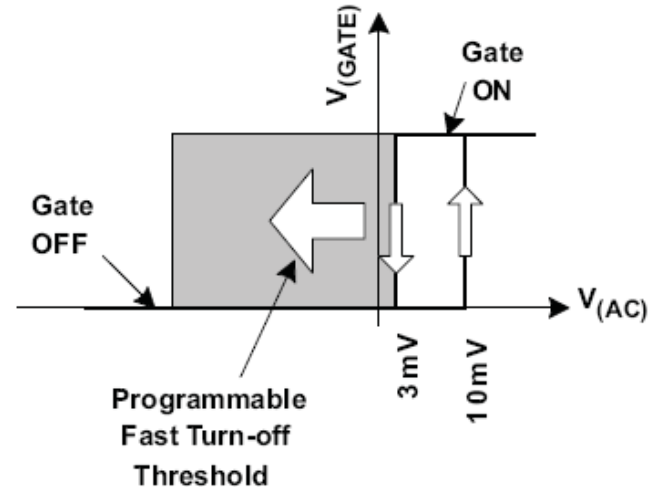- FET on if $V_{AC} > 10\text{ mV}$
- FET off if $V_{AC} < 3\text{ mV}$
- Fast off if V_{AC} goes negative
- Less sensitive to reactive loads
- Suceptible to light load oscillation



Hotswap/ORing Controller Combos

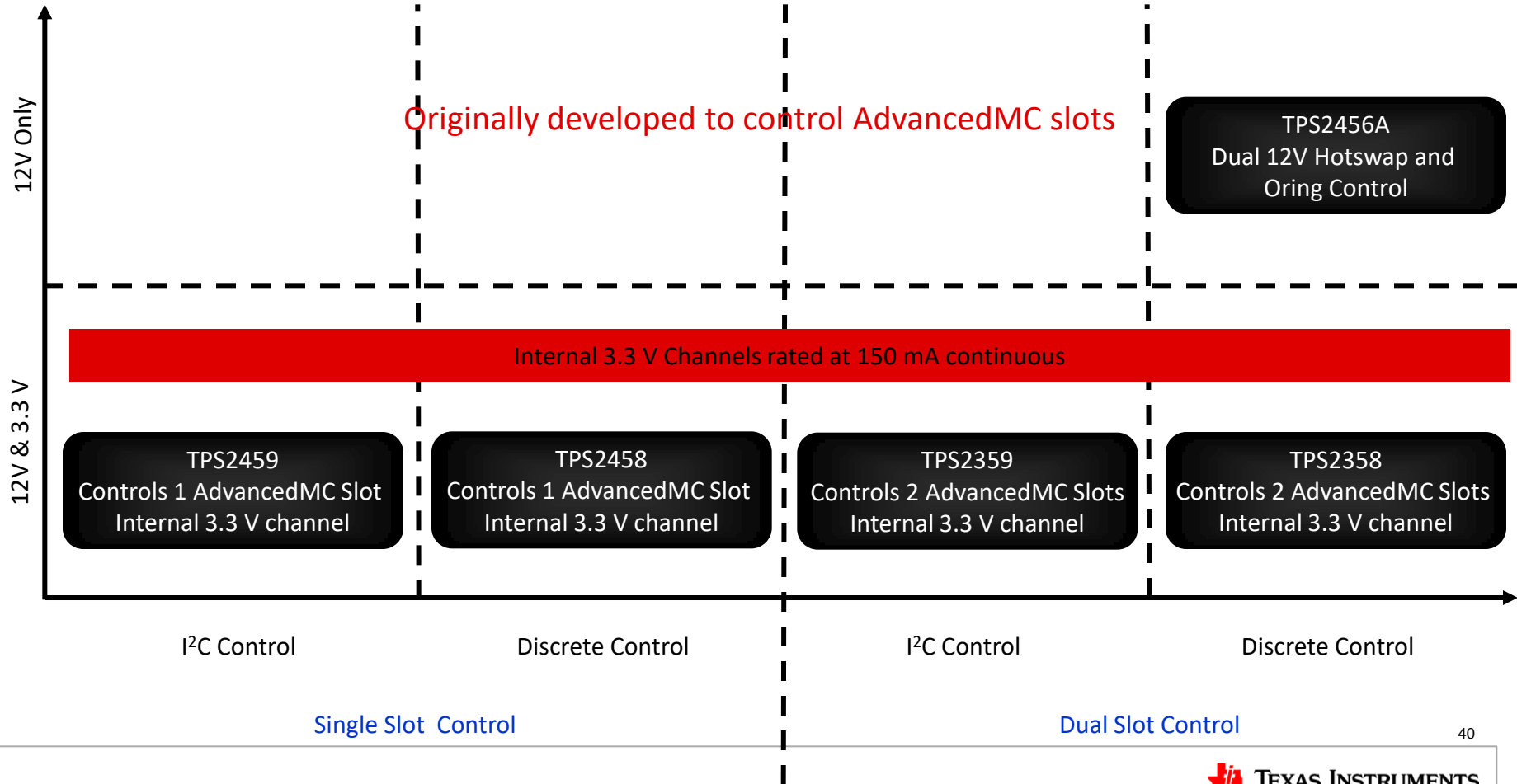

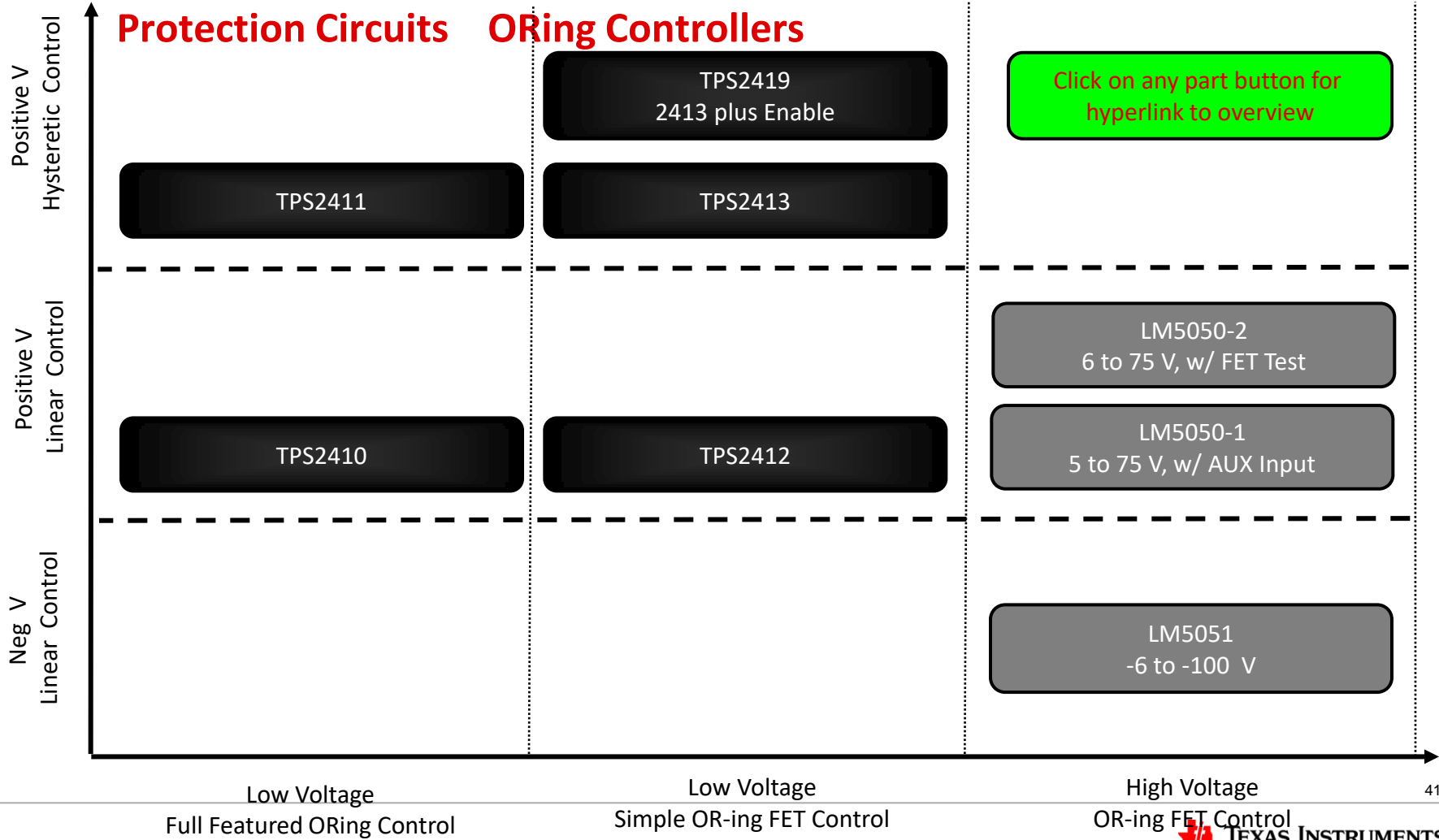

Positive ORing Controller Device Comparison

| PART | V _{OPERATING} | Package | AUX Input | FET Test | Control Type | I _{GATE} uA | V _{TH} FAST SHUTOFF mV | |
|----------|------------------------|---------------|-----------|----------|--------------|----------------------|---------------------------------|------------|
| LM5051 | -6 to 100 | SOIC8 | No | Yes | Linear | 280 - 950 | -45 | |
| LM5050-1 | 5 to 75 | TSOT23-6 Thin | Yes (VS) | No | Linear | 12 - 41 | -28 | |
| LM5050-2 | 6 to 75 | | No | Yes | | | | |
| TPS2410 | 0.8 – 16.5 | TSSOP14 | Yes (VDD) | Yes | Linear | 290 | Adjustable -3 to -200 | |
| TPS2411 | | | | Yes | Hysteretic | | | |
| TPS2412 | | TSSOP8 | | No | No | | | Linear |
| TPS2413 | | | | No | | | | Hysteretic |
| TPS2419 | | | | | | | | No |

Thank you.