

PLC Analog Output and Transmitter Introduction: 4-20mA Iout/0-10V Vout

PLC 類比輸出和傳送器介紹： 4-20mA Iout / 0-10V Vout

TI Analog FAE – Edward Lee

Edward.lee@ti.com


Agenda

- Overview
 - Where/how are analog outputs used in industrial automation?
 - What are the standard configurations for analog outputs?
- Designing 3-wire Transmitters
 - Theory of Operation
 - Design Examples
- Designing 2-wire Transmitters
 - Theory of Operation
 - Design Examples
- Designing Protection Solutions
 - How does a device get damaged?
 - How do customers test for industrial transient immunity?
 - How do I stop these transients from damaging my design?

Overview

Where are analog outputs used in Industrial Automation? What do they look like?

Industrial Automation Overview

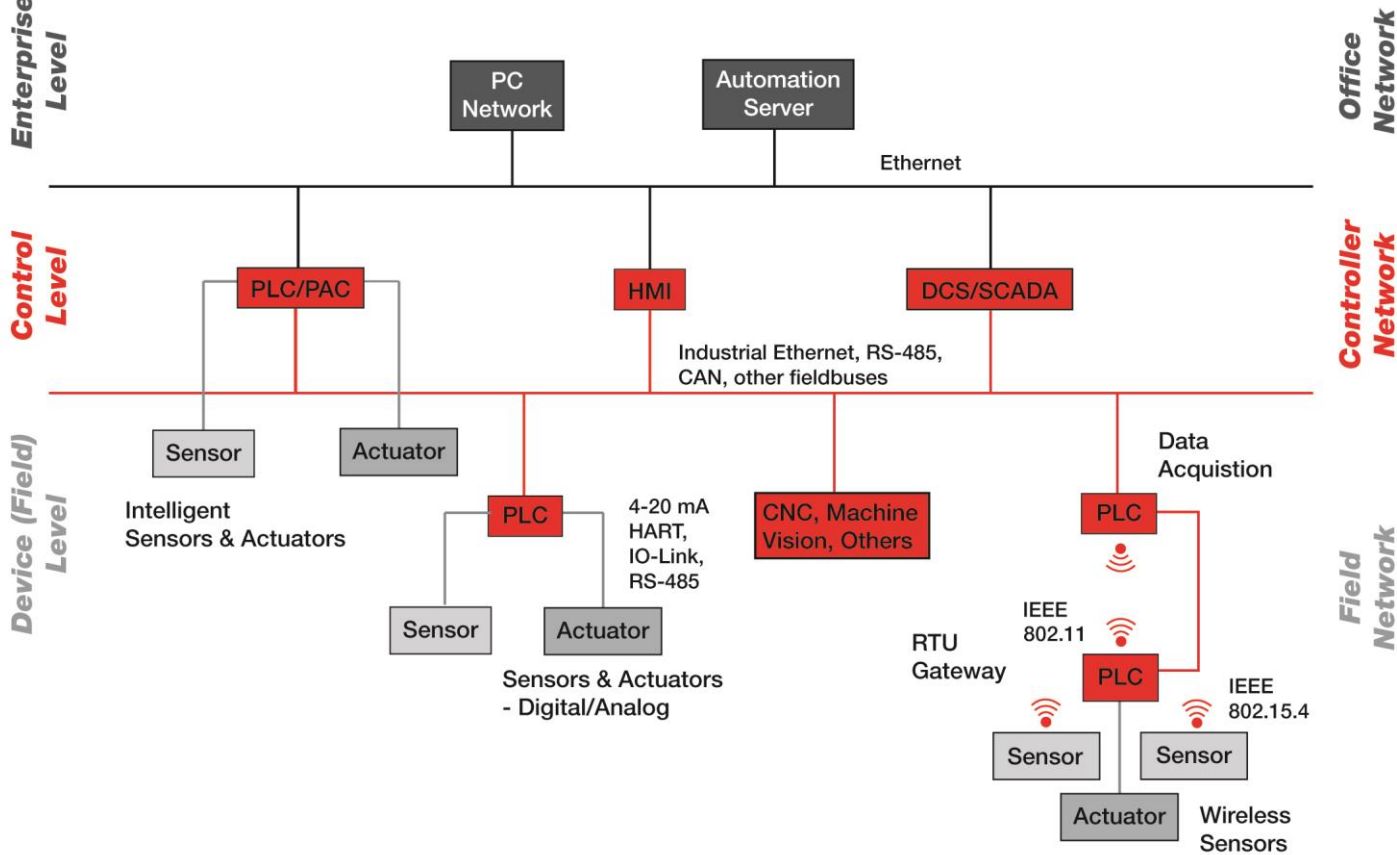


How are Analog Outputs used in Industrial Automation?

- Programmable Logic Controllers
 - Analog output modules that control something placed in the field
 - Communication, valve position, position of linear actuator, etc.
 - Analog output module is powered by PLC back-plane
 - Primarily 3-wire systems




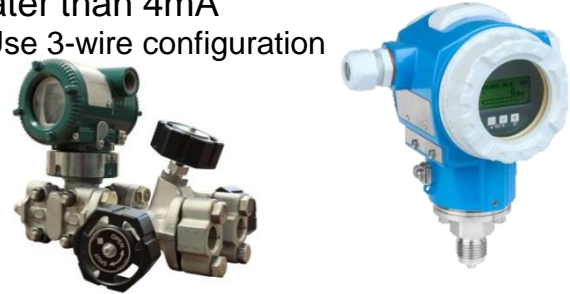- Field Elements
 - Analog outputs paired with sensors, placed remotely in the field
 - Comprise a majority of the market for industrial analog outputs
 - Most often 2-wire, or loop-powered, 4-20mA sensor transmitters
 - Some transmitter current requirements are greater than 4mA
 - Use 3-wire configuration




- Is isolation required? Why? Is isolation provided by the receiver or the transmitter?
 - There are isolated variants of 2-wire and 3-wire analog outputs
 - Power isolation, at least, is implied in all 4-wire analog outputs

4-20mA Overview

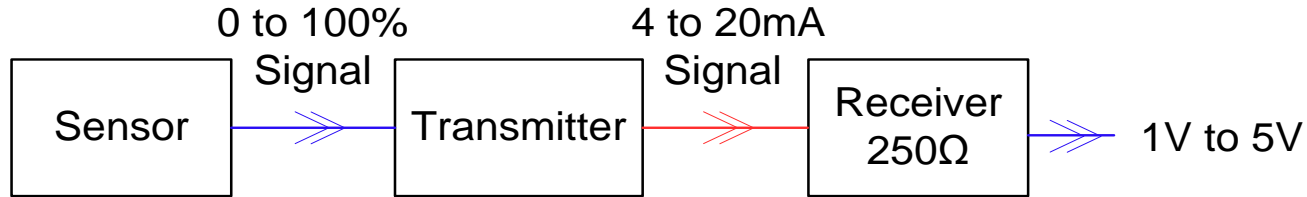

- 4mA represents 0% input level
 - Allows up to 4mA to power external input circuitry
 - 4mA zero level allows under-scale settings and fault detection
- 20mA represents 100% input level
 - Provides sufficient current to power electromechanical devices
 - Over-scale can also be used to detect fault conditions


Example of AO application

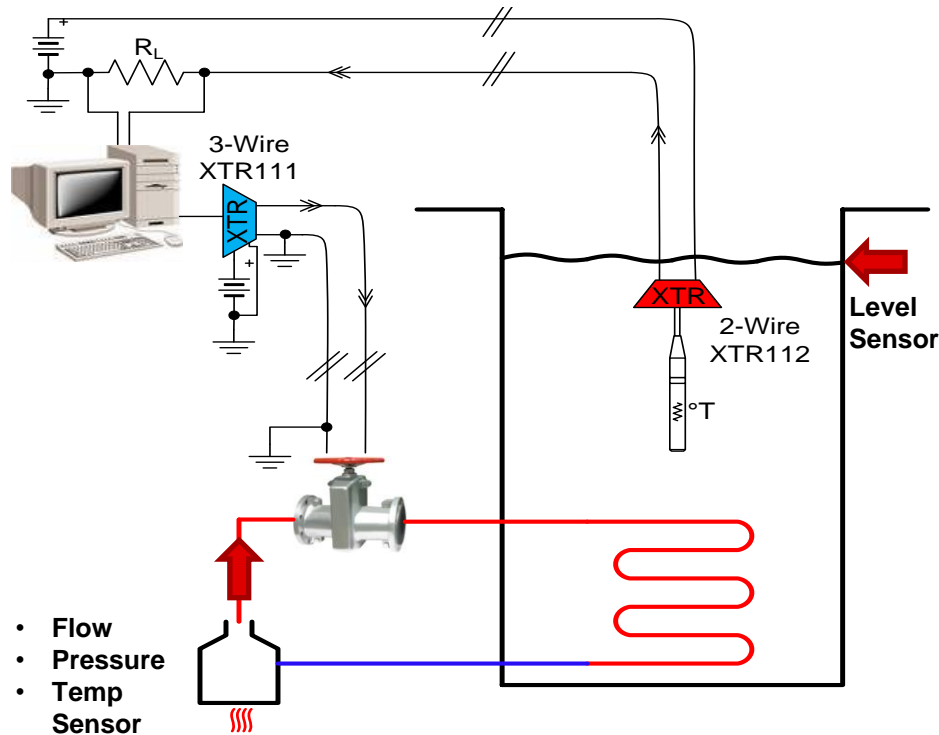


- 2-Wire Transmitter
 - Submersible temperature sensor
 - Remote location prevents local power supply
 - Sends data back to control station
- 3-Wire Transmitter
 - Sends control signal to element at remote location
 - Local power supply is available

2-wire Configuration

ANSI/ISA-50.1-1982 Illustration

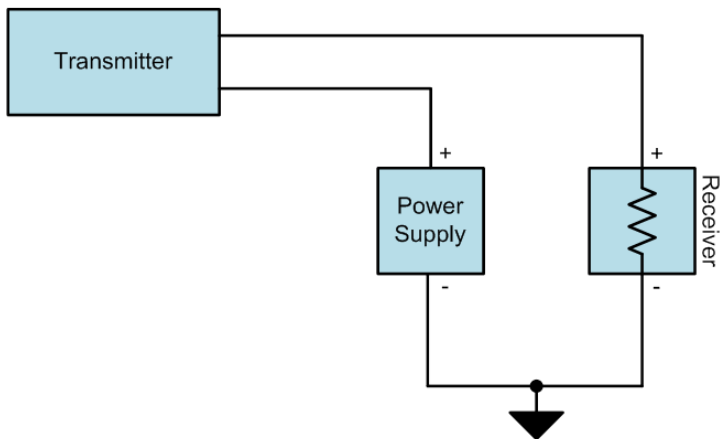


Practical Illustration

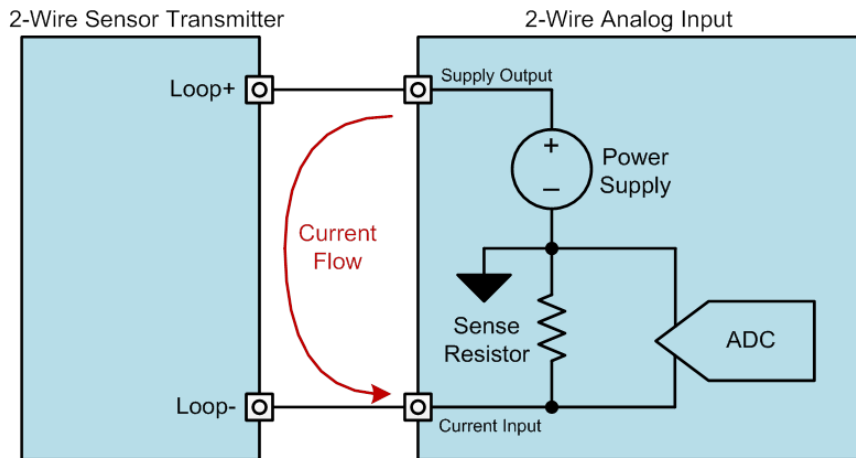


- Supply, transmitter, and receiver are in series – power & signal are in the same loop
- Transmitter communicates with receiver through return current (4-20mA)
- Transmitter must be powered on $\leq 4\text{mA}$ of supply current
- Long cable lengths between supply and transmitter, transmitter and receiver, and large sense resistors can reduce voltage available for transmitter

2-wire Isolation

Non-Isolated

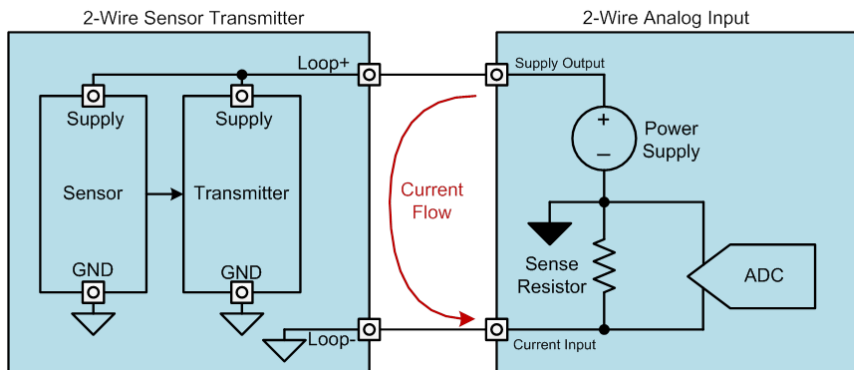


Input-Isolated

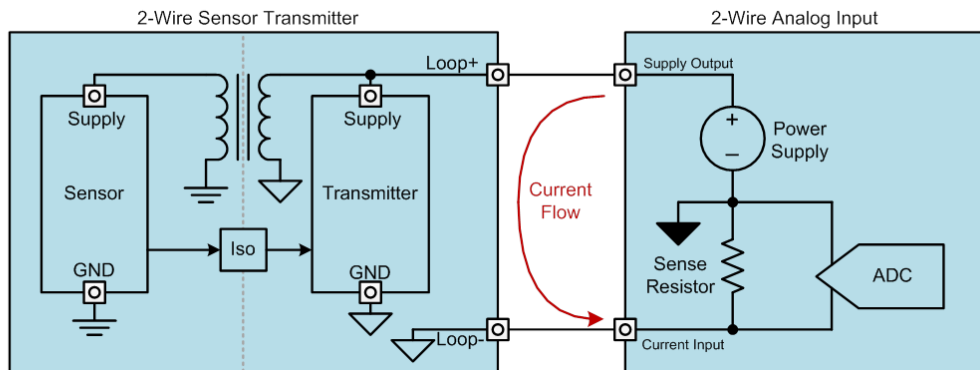


3-wire Configuration


ANSI/ISA-50.1-1982 Illustration

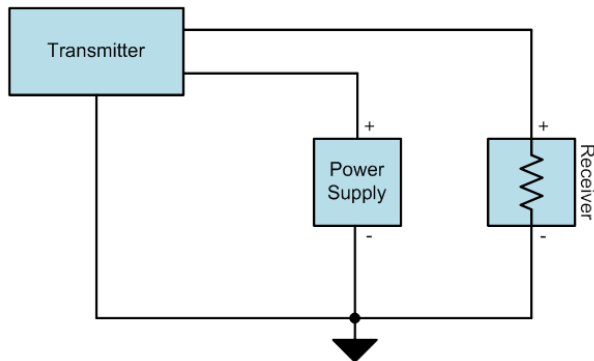

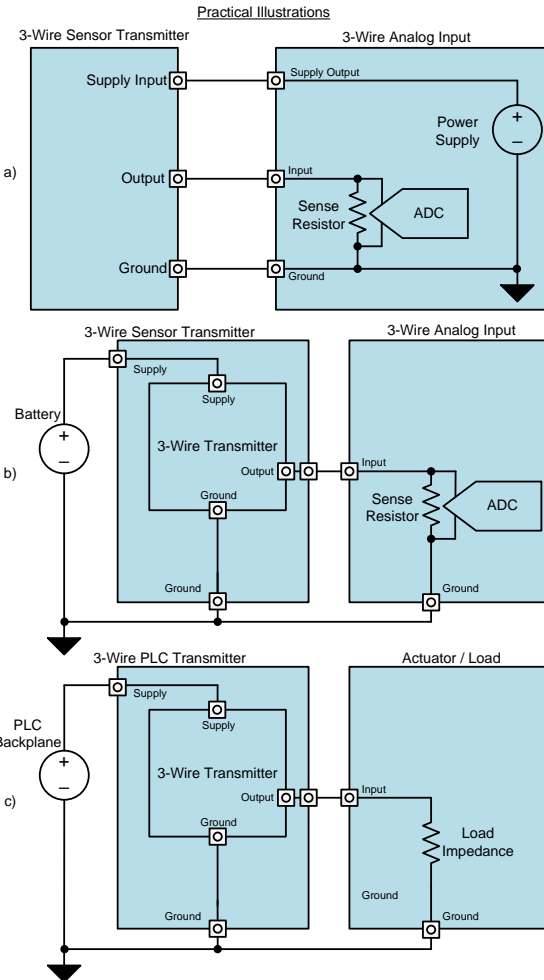
- Transmitter has separate loops for power and for analog output
 - Output current can reach 0mA
- Grouping of power supply, transmitter, and receiver may vary
 - a) >4mA supply current available for transmitter
 - b) Similar to a) but with local supply to remove cable impedance voltage drop
 - c) Typical implementation for PLC transmitter, battery from b) replaced by PLC backplane




3-wire Isolation

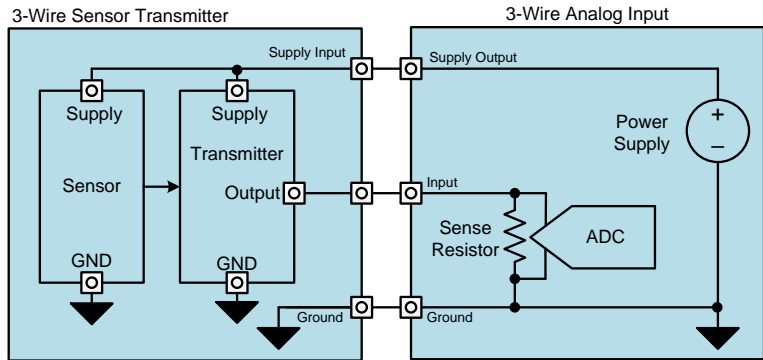

Non-Isolated

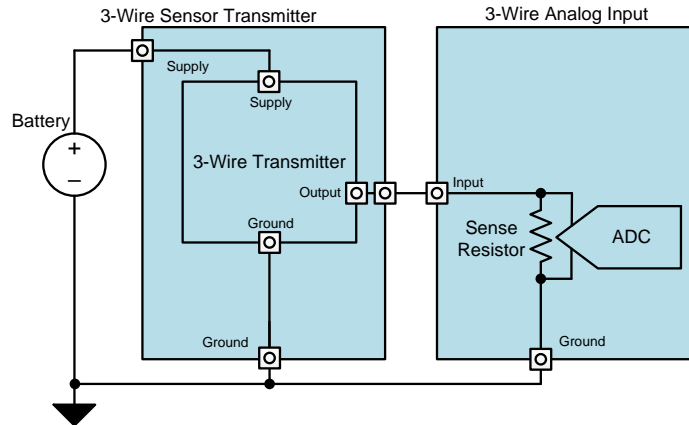


Input-Isolated

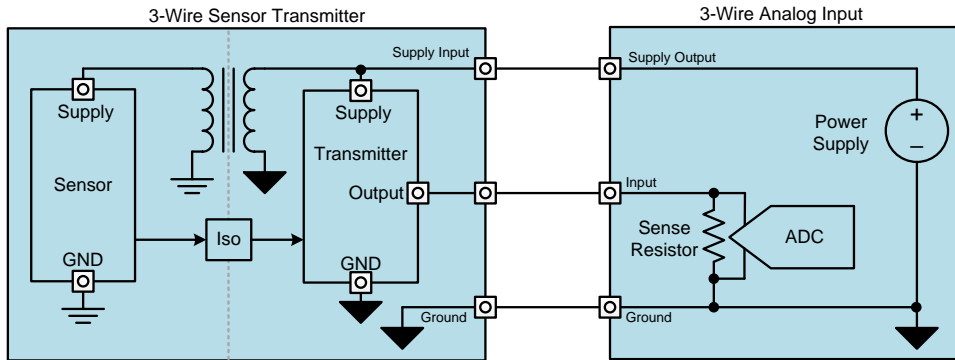


4-wire Configuration & Isolation


ANSI/ISA-50.1-1982 Illustration

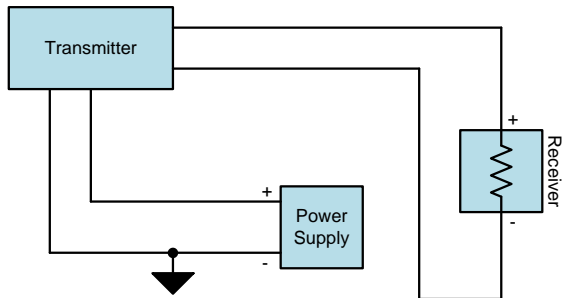


Power-Isolated

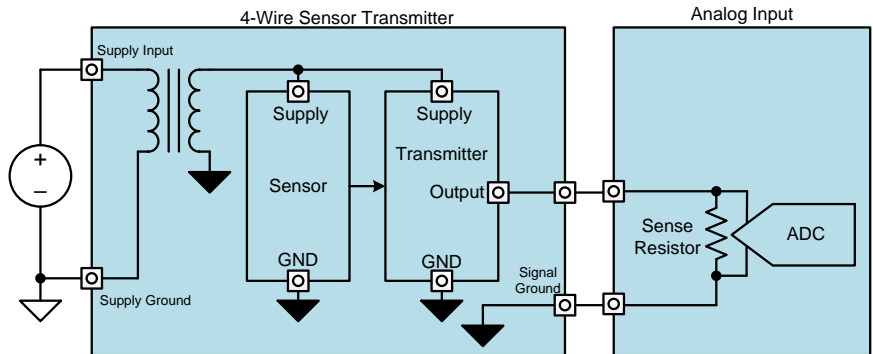

Output-Isolated

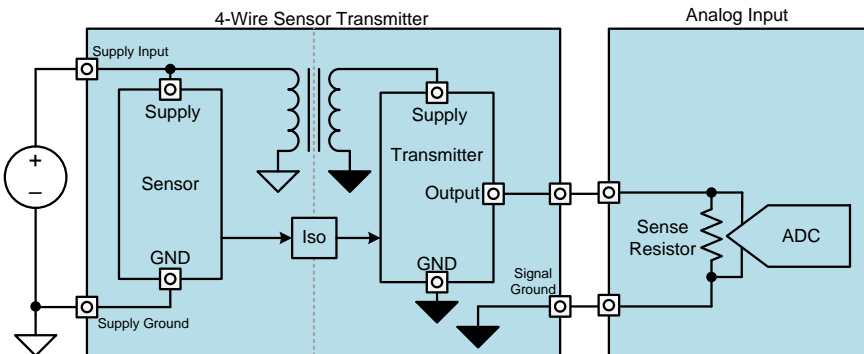


Fully-Isolated

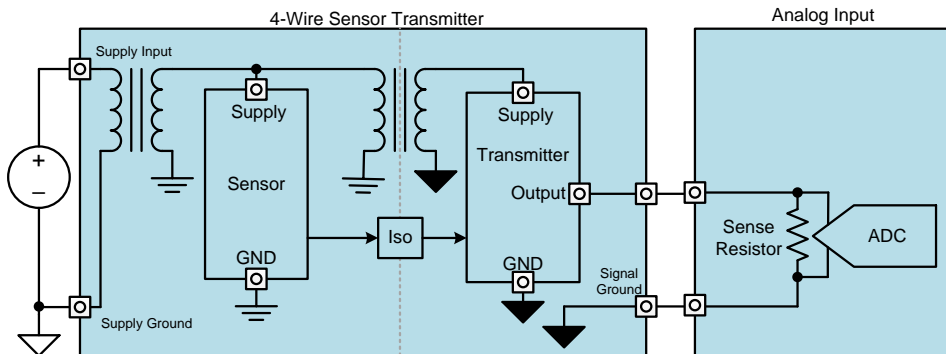


Designing 3-wire Transmitters

Theory of Operation & Design Examples

Current Output: Theory of Operation

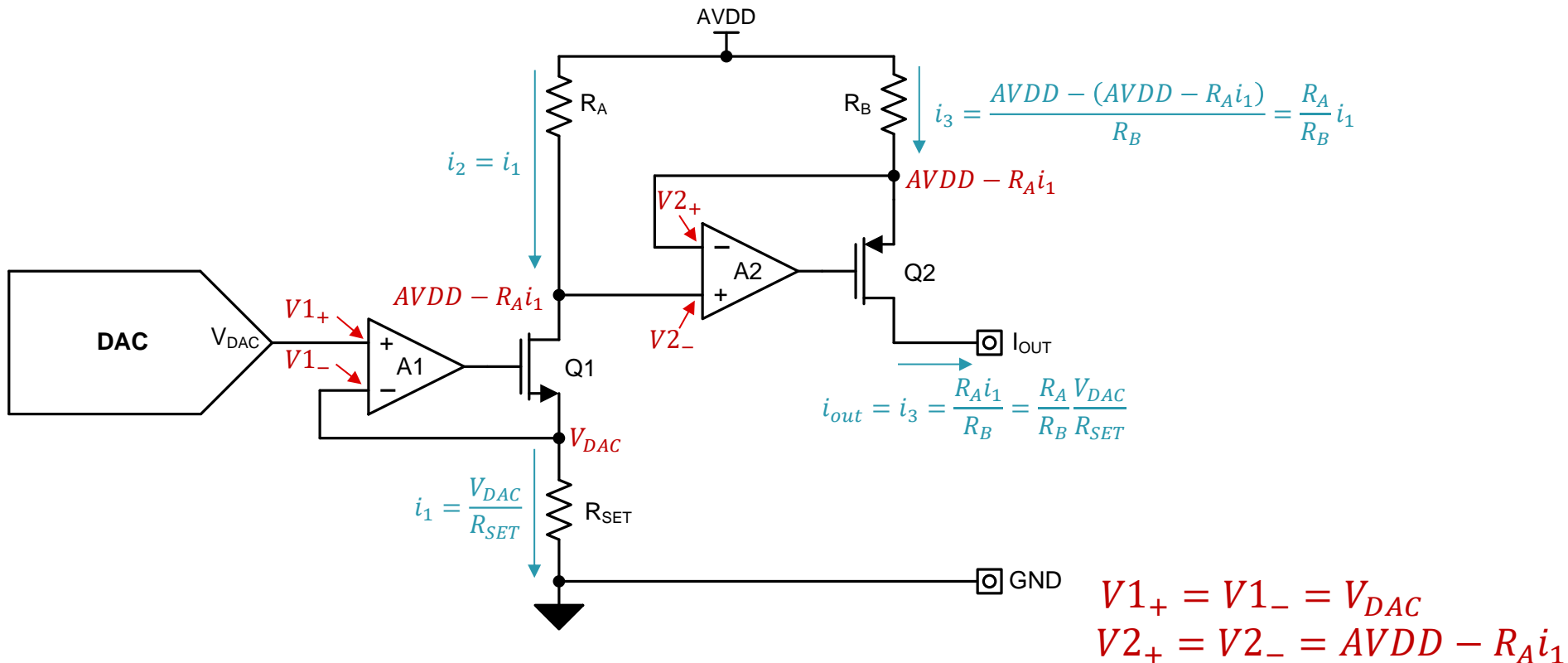


Current Output: Considerations

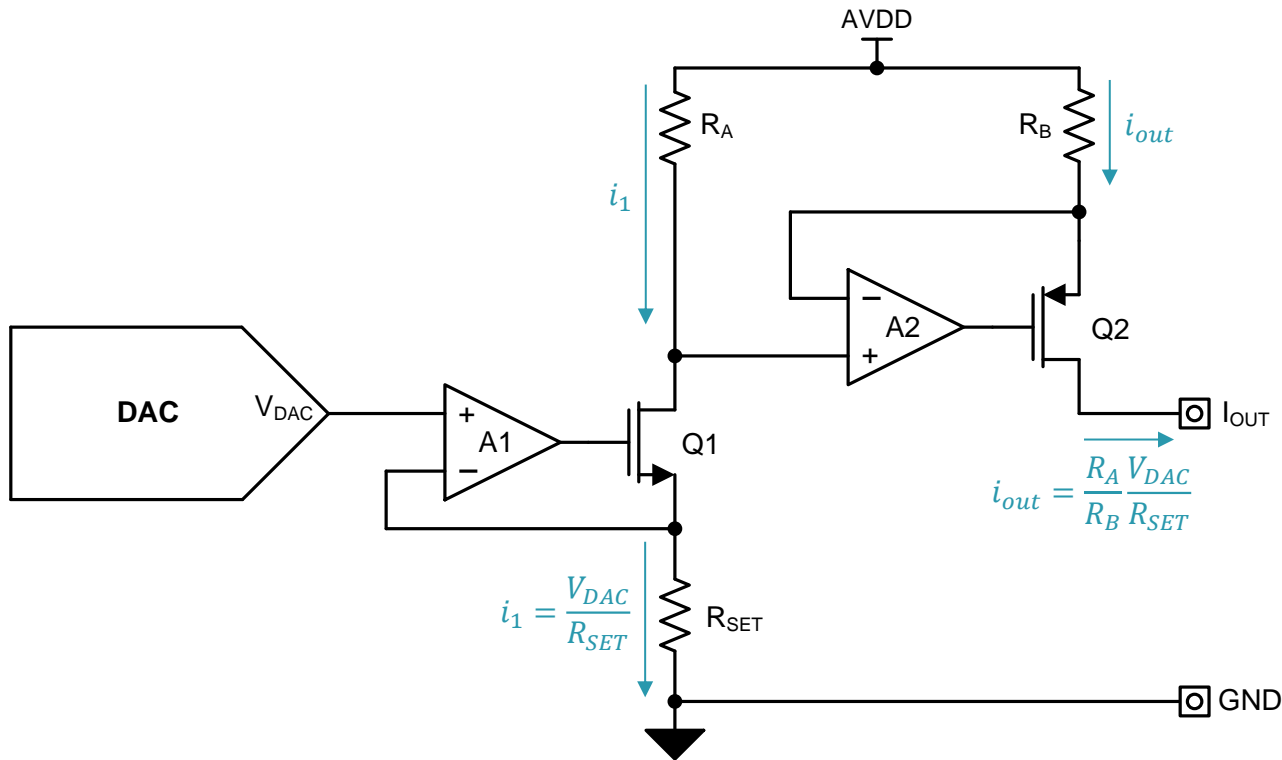

- i_1 current is wasted power
 - All of this current goes straight to ground
- Large i_1 current creates heating / drift of Q1 & R_{SET}
- Ratio of $R_A : R_B$ sets current gain from first stage to output stage
- At full-scale output & low impedance load, Q2 power / heat dissipation rises
 - In layout, keep away from other sensitive components


Current Output: Compliance Voltage

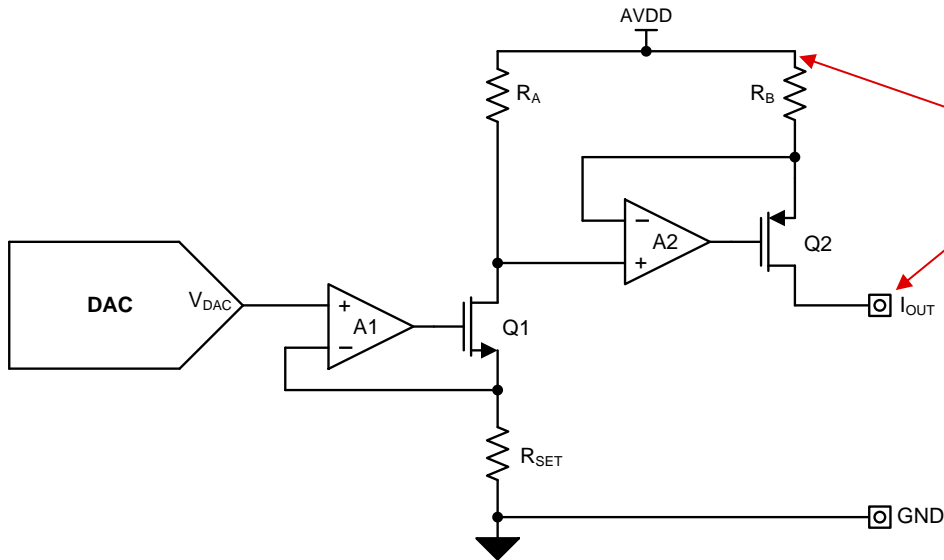

When this potential drops below the transmitter compliance voltage, Q_2 is no longer in saturation

- Compliance voltage is the point at which the voltage potential at the point of load is too high for the voltage to current converter to maintain linear operation
- To accommodate for compliance voltage:
 - Understand the maximum current output
 - Understand the maximum load impedance
 - Ensure that $AVDD > MaxCurrent * MaxLoad + Compliance\ Voltage$

Voltage Output: Theory of Operation

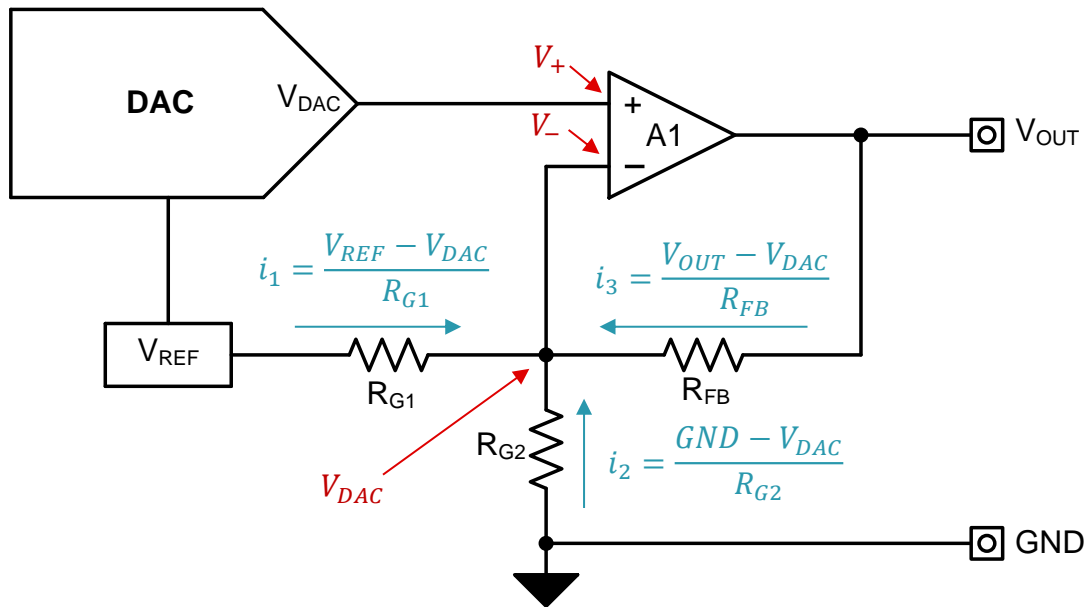


$$\frac{-V_{DAC}}{R_{G2}} + \frac{V_{REF} - V_{DAC}}{R_{G1}} + \frac{V_{OUT} - V_{DAC}}{R_{FB}} = 0$$

$$\frac{-V_{DAC}}{R_{G2}} + \frac{V_{REF}}{R_{G1}} - \frac{V_{DAC}}{R_{G1}} + \frac{V_{OUT}}{R_{FB}} - \frac{V_{DAC}}{R_{FB}} = 0$$

$$\frac{V_{OUT}}{R_{FB}} = \frac{V_{DAC}}{R_{FB}} + \frac{V_{DAC}}{R_{G1}} + \frac{V_{DAC}}{R_{FB}} - \frac{V_{REF}}{R_{G1}}$$

$$V_{OUT} = \left(1 + \frac{R_{FB}}{R_{G1}} + \frac{R_{FB}}{R_{G2}}\right) V_{DAC} - \frac{R_{FB}}{R_{G1}} V_{REF}$$

Voltage Output: Consideration

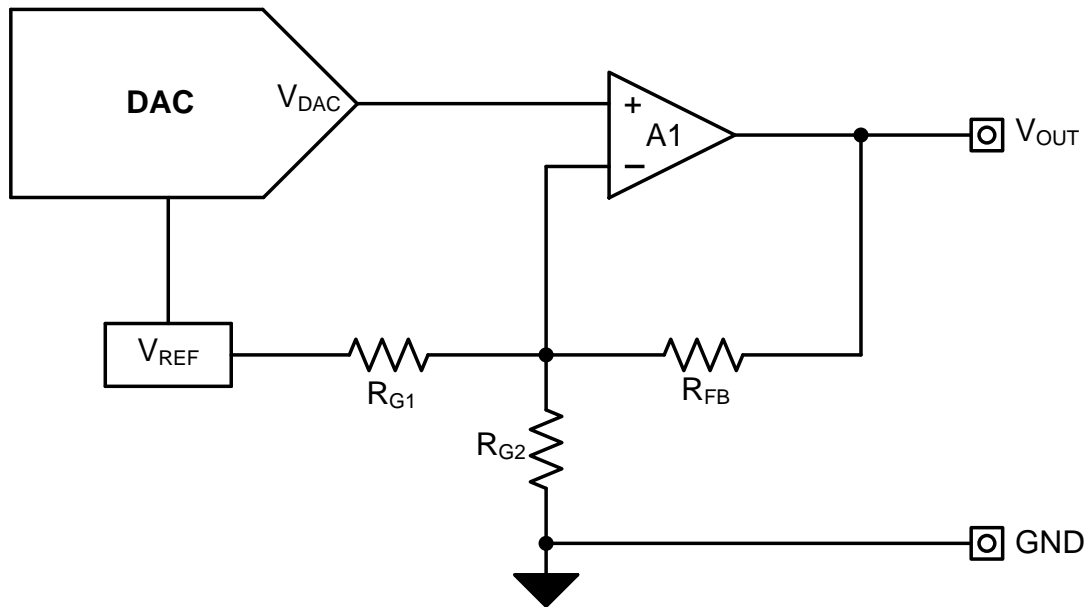

- Select offset gain to set negative full-scale end point

$$V_{NegativeFS} = -\frac{R_{FB}}{R_{G1}}V_{REF}$$

- Modify full-scale range gain


$$V_{FSR} = \left(1 + \frac{R_{FB}}{R_{G1}} + \frac{R_{FB}}{R_{G2}}\right)V_{DAC}$$

- Check full-scale output

$$V_{PositiveFS} = V_{FSR} - V_{NegativeFS}$$

$$V_{OUT} = \left(1 + \frac{R_{FB}}{R_{G1}} + \frac{R_{FB}}{R_{G2}}\right)V_{DAC} - \frac{R_{FB}}{R_{G1}}V_{REF}$$

Design Example: Partially Discrete

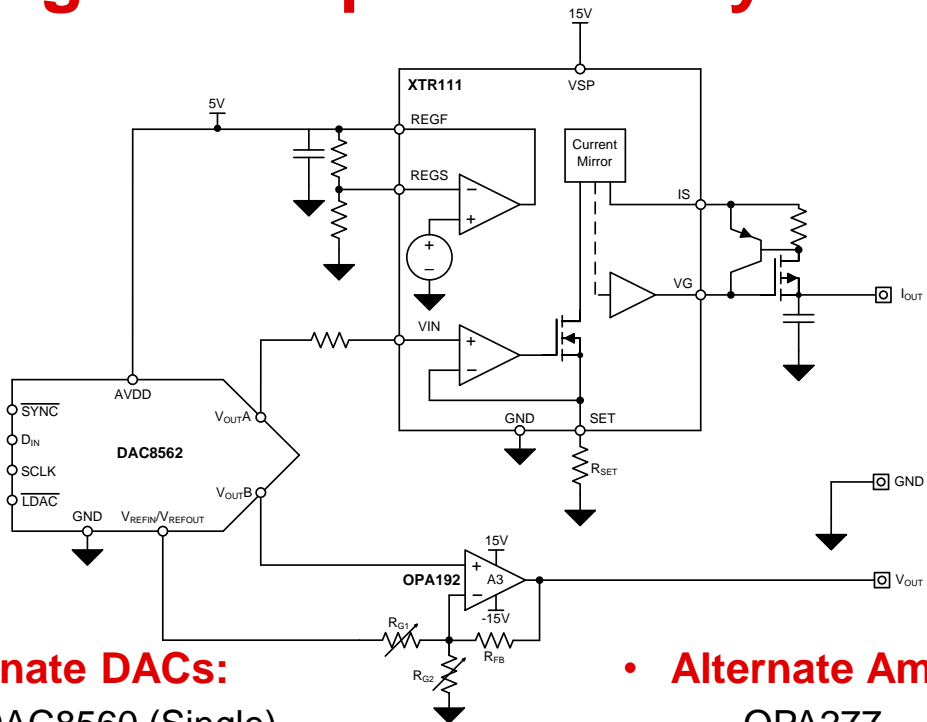

- Alternate XTRs:
 - XTR110 (Internal R_{SET})
 - XTR300 (Source/Sink)

• Alternate DACs:

- DAC8560 (Single)
- DAC8564/8 (Quad/Octal)
- DAC8811/2 (Improved Single/Dual)

• Alternate Amplifiers:

- OPA277
- OPA170/OPA172
- OPA188



TIPD in Test

DAC8760/7760

16-/12-bit DACs with Voltage and 4-20mA Current Outputs

RELEASED

Features


- DAC with Current & Voltage Outputs
- Selectable Ranges
 - Current: 0-20mA; 4-20mA; 0-24mA
 - Voltage: 0-5V; 0-10V; +/-5V; +/-10V (10% over-range)
- TUE: 0.1% FSR max
- Internal Reference (10ppm/°C max)
- Wide Temp Range: -40°C to +125°C
- Fault Detect: Open-Circuit of I-Out, thermal alarm, compliance voltage
- HART Interface
- Reliability: Short-Circuit limit, CRC, Watchdog timer
- Pin compatible to competition: 40-QFN / 24-QSSOP

Applications

- PLC I/O modules
- Sensor Transmitters
- Industrial Automation
- Building Automation

Benefits

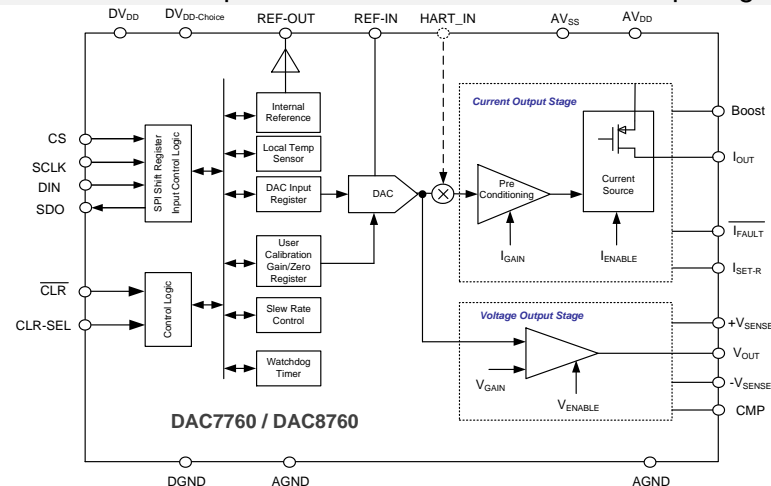- Integrates 3 different components on board to help save board space, cost and reduce design time
- Higher accuracy than competition
- Allows easy upgrade from existing solutions
- Key benefits over competition:
 - Only part with features to improve system reliability
 - Reliable operation in extended industrial temp range



DAC8750/7750

16-/12-bit DACs with 4-20mA Current Outputs

RELEASED

Features


- DAC with Current Outputs
- Selectable Ranges
 - Current: 0-20mA; 4-20mA; 0-24mA
- TUE: 0.1% FSR max
- Internal Reference (10ppm/°C max)
- Wide Temp Range: -40°C to +125°C
- Fault Detect: Open-Circuit of I-Out, thermal alarm, compliance voltage
- HART Interface
- Reliability: Short-Circuit limit, CRC, Watchdog timer
- Pin compatible to competition: 40-QFN / 24-QSSOP

Applications



- PLC I/O modules
- Sensor Transmitters
- Industrial Automation
- Building Automation

Benefits

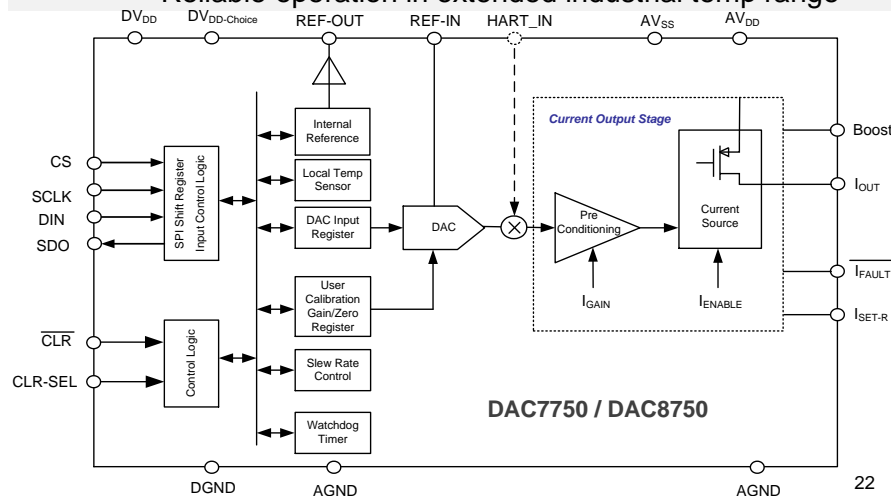- Integrates 3 different components on board to help save board space, cost and reduce design time
- Higher accuracy than competition
- Allows easy upgrade from existing solutions
- Key benefits over competition:
 - Only part with features to improve system reliability
 - Reliable operation in extended industrial temp range




Design Example: Dual Channel Universal Analog Output w/Bipolar Current Outputs

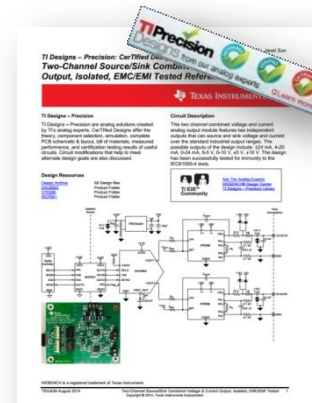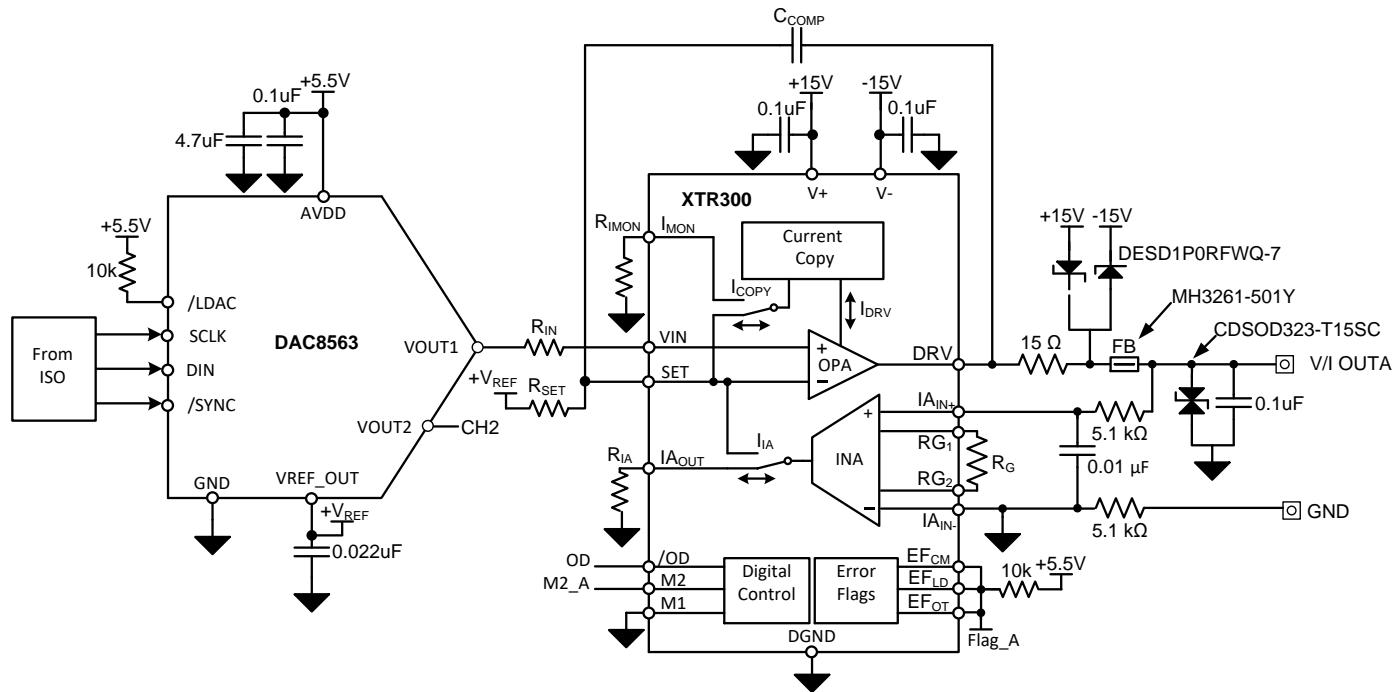


TIPD155

Power Dissipation for PLC AO Modules

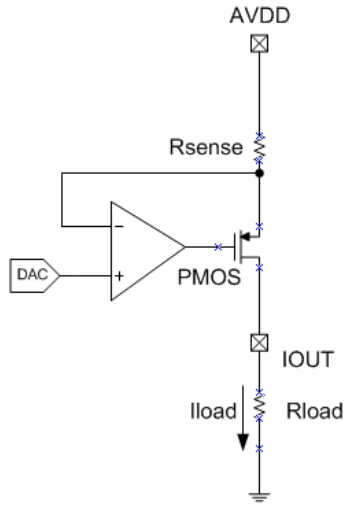Analog Current Output Circuit (No Power Management)




AVDD = 24V
Rload = 1Ω
IOUT = 24mA

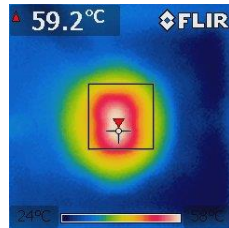


**High Power
dissipation**

	Rload	Chip
Power Dissipation	0.6mW	576mW

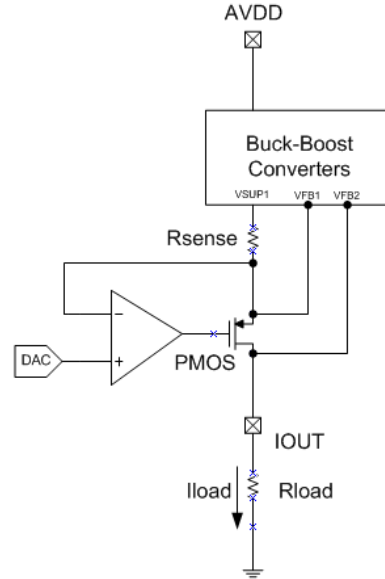Analog Current Output Circuit (Adaptive Power Management)



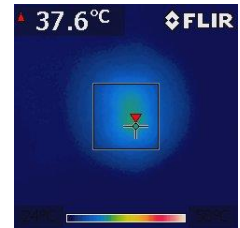AVDD = 24V
Rload = 1Ω
IOUT = 24mA
70% Efficiency




**Low Power
dissipation**

	Rload	Chip
Power Dissipation	0.6mW	185mW

DAC8775 TI Precision Designs

TIPD215

- Less than 1W Quad Channel Analog Output Module with Adaptive power management
- DAC8775 with LM5166
- 13-65V Supply Input <1W total power dissipation

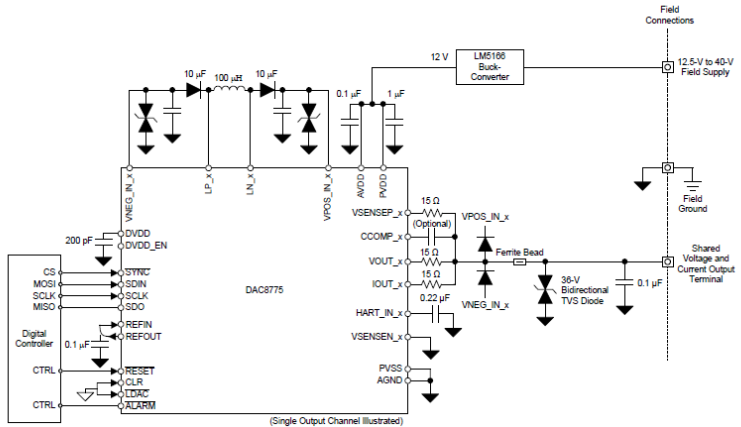


TIPD216

- Quad Channel Industrial Voltage and Current output Driver- EMC/EMI tested
- 4x Channel, Shared V+I Output Terminal
 - IEC61000-4 ESD, EFT, Surge, CI, and RI tested protection circuitry
 - CE / FCC Radiated Emission testing
- DAC8775 Buck-Boost Converter Adaptive Power Management

DC/DC External Components & optional filtering



68x58 mm Solution Size

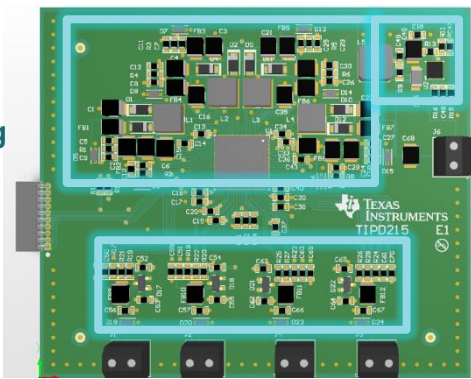

Optional External buck converter

IEC61000-4 Protection Block

Generic Example Circuit

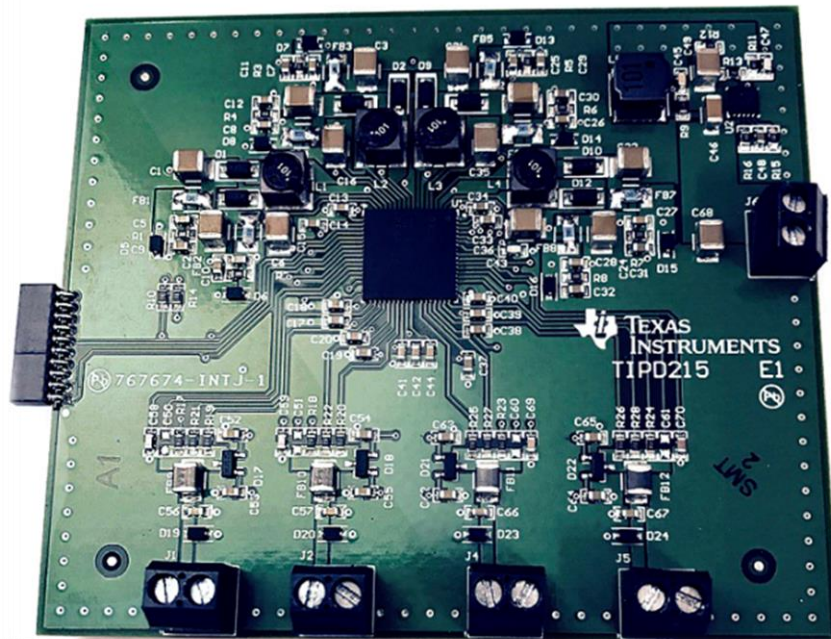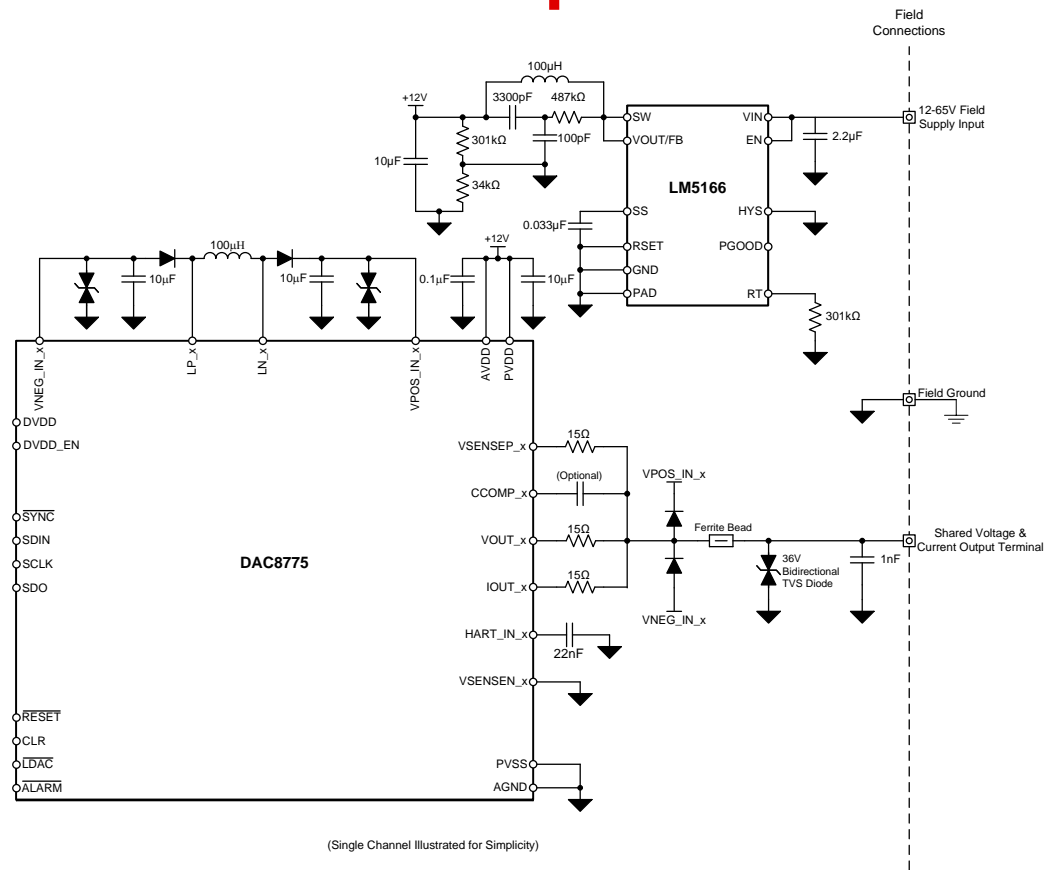

DAC8775

Quad-Channel 16-bit DACs with Voltage/Current Outputs & Adaptive Power

RELEASED

Features


- Integrated DAC and selectable voltage/current ranges
 - I_{out}: 0-20mA; 4-20mA; 3.5-23.5mA; 0-24mA ; ±24mA
 - V_{out}: 0-5V; 0-10V; +/-5V; +/-10V (20% over-range)
 - TUE: 0.1% FSR max; 5V reference: 10 ppm/°C max
- Adaptive Power Management
 - Single supply pin for full chip (12-36V)
 - Single Inductor buck-boost converter generates
 - Current out supply: 4-32V
 - Voltage out supply: +/-15V
 - Auto learn mode
- Integrated LDO for digital supply: 5V
- Enhanced Reliability: Open-Circuit of I-Out, thermal alarm, compliance voltage, Watchdog timer
- Enhanced safety features
- Wide Temp Range: -40°C to +125°C
- Package QFN-72 (10x10 mm)

Applications

- PLC I/O modules
- Sensor Transmitters
- Industrial Automation
- Building Automation

Benefits

- Reduce thermal stress and module size
- Simple power supply scheme
- Overall solution compared to others
 - Saves cost with only one supply pin
 - Lower power dissipation
 - Rated over extended industrial temperature range

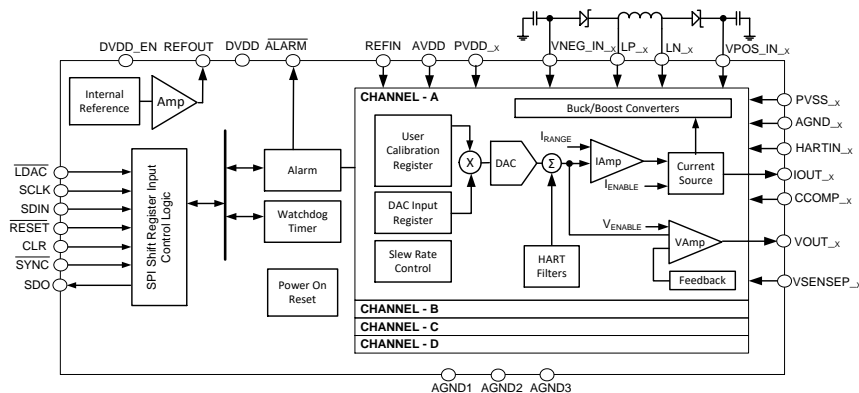

DAC8771

Single-Channel 16-bit DACs with Voltage/Current Outputs & Adaptive Power

RELEASED

Features


- Integrated DAC and selectable voltage/current ranges
 - I_{out}: 0-20mA; 4-20mA; 3.5-23.5mA; 0-24mA ; ±24mA
 - V_{out}: 0-5V; 0-10V; +/-5V; +/-10V (20% over-range)
 - TUE: 0.1% FSR max; 5V reference: 10 ppm/°C max
- Adaptive Power Management
 - Single supply pin for full chip (12-36V)
 - Single Inductor buck-boost converter generates
 - Current out supply: 4-32V
 - Voltage out supply: +/-15V
 - Auto learn mode
- Integrated LDO for digital supply: 5V
- Enhanced Reliability: Open-Circuit of I-Out, thermal alarm, compliance voltage, Watchdog timer
- Enhanced safety features
- Wide Temp Range: -40°C to +125°C
- Package QFN-48 (7x7 mm)

Applications

- PLC I/O modules
- Sensor Transmitters
- Industrial Automation
- Building Automation

Benefits


- Reduce thermal stress and module size
- Simple power supply scheme
- Overall solution compared to others
 - Saves cost with only one supply pin
 - Lower power dissipation
 - Rated over extended industrial temperature range

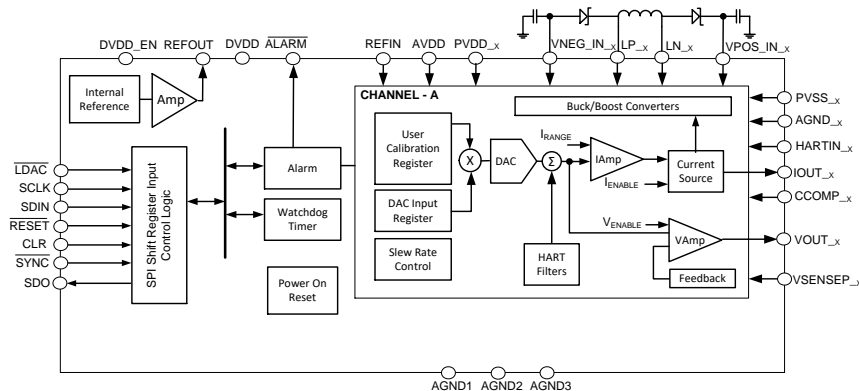

Designing 2-wire Transmitters

Theory of Operation & Design Examples

2-Wire Transmitter: Theory of Operation

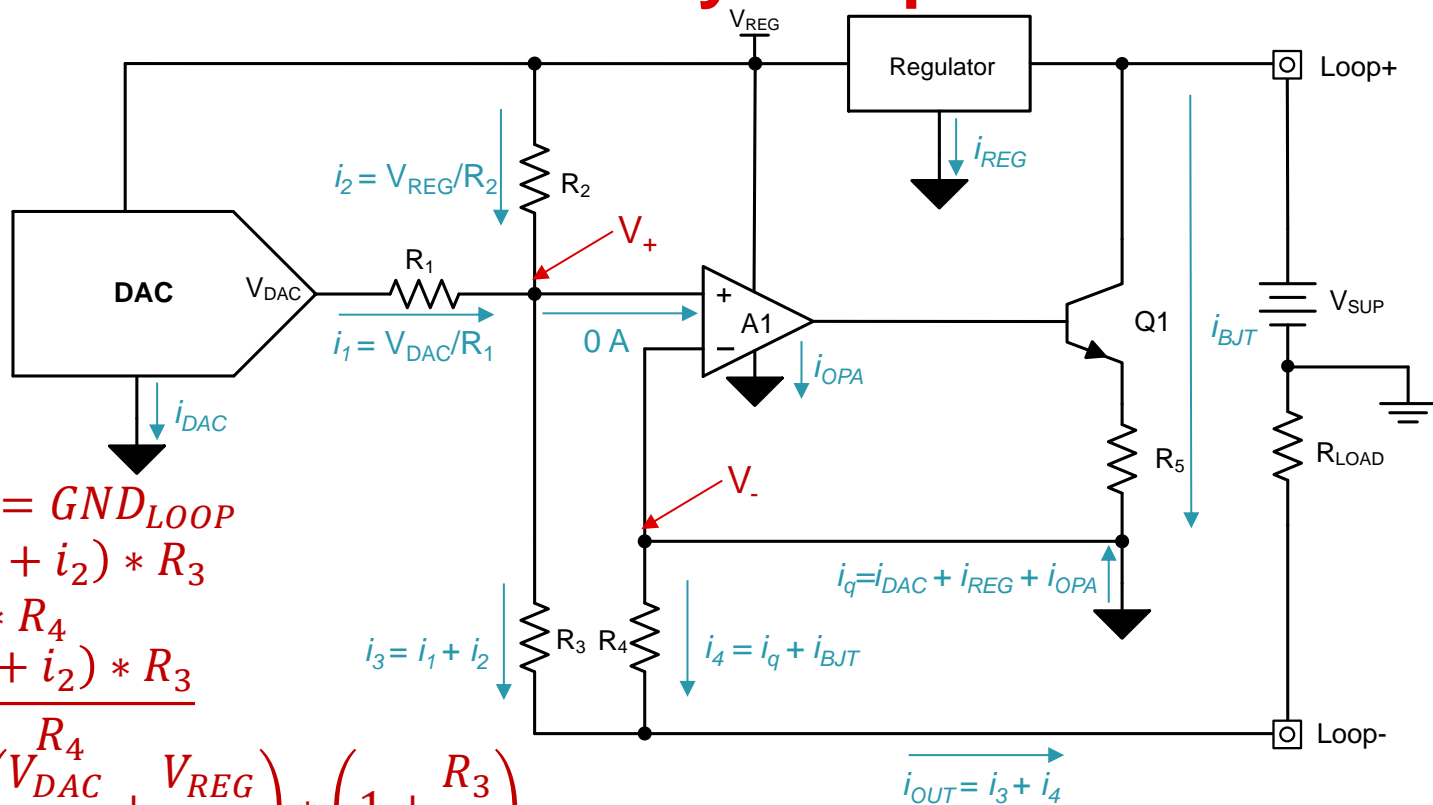

$$V_+ = V_- = GND_{LOOP}$$


$$V_+ = (i_1 + i_2) * R_3$$

$$V_- = i_4 * R_4$$

$$i_4 = \frac{(i_1 + i_2) * R_3}{R_4}$$


$$i_{OUT} = \left(\frac{V_{DAC}}{R_1} + \frac{V_{REG}}{R_2} \right) * \left(1 + \frac{R_3}{R_4} \right)$$

2-Wire Transmitter: Considerations

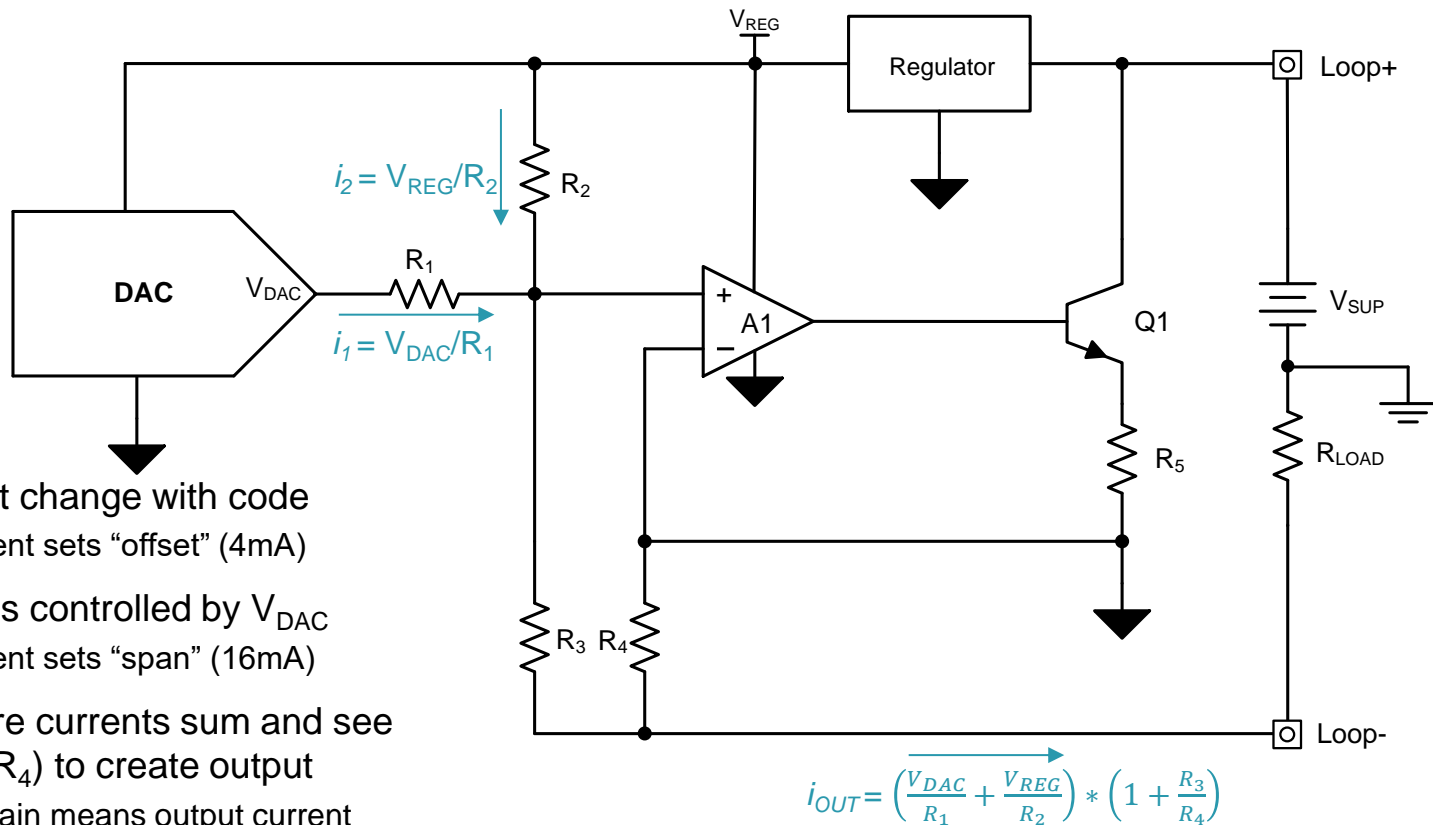



- i_2 does not change with code
 - i_2 current sets “offset” (4mA)
- i_1 current is controlled by V_{DAC}
 - i_1 current sets “span” (16mA)
- i_1 and i_2 are currents sum and see $G=1+(R_3/R_4)$ to create output
 - High gain means output current primarily flows from loop through BJT

2-Wire Transmitter: Compliance Voltage

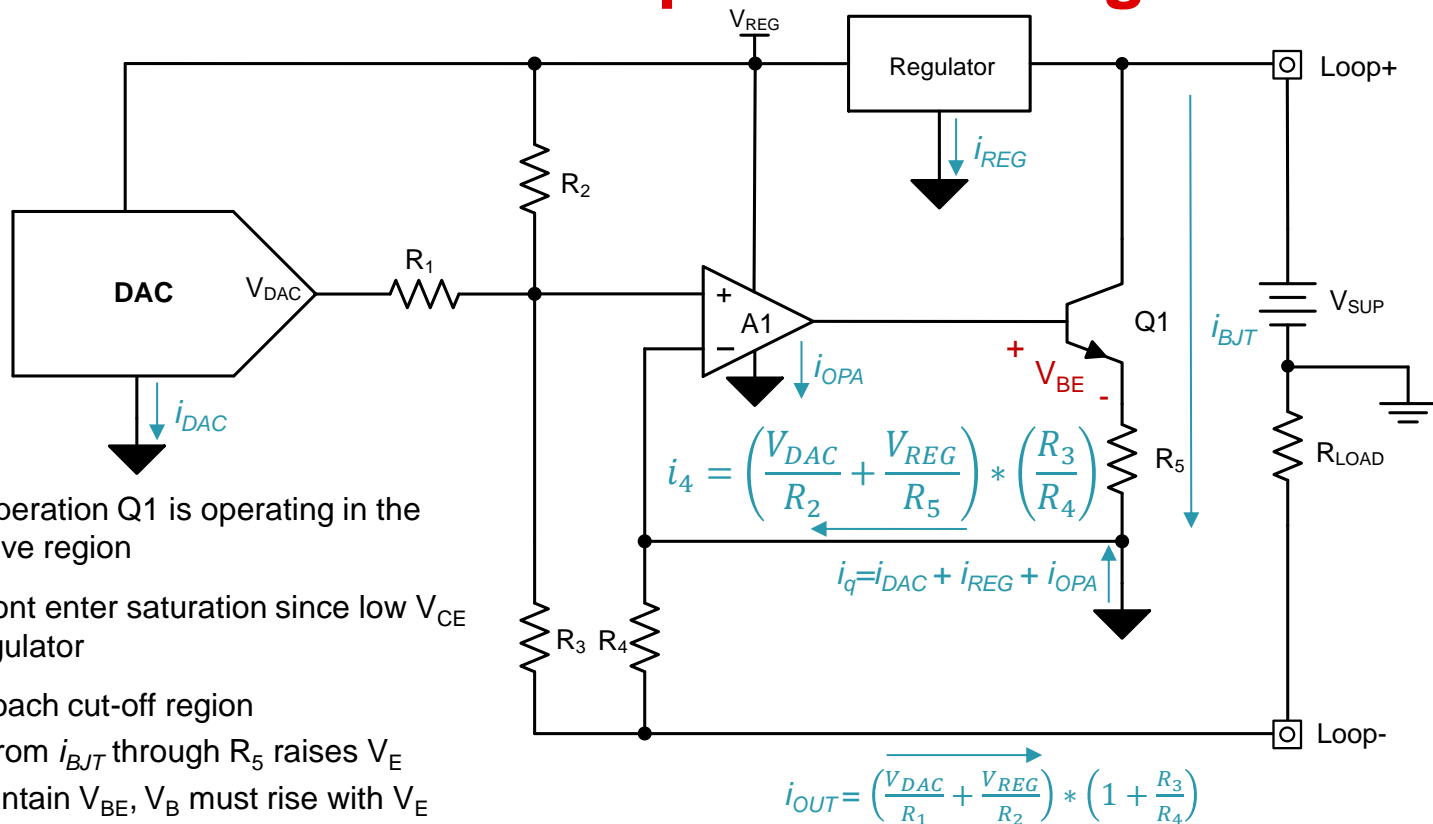

- In normal operation Q1 is operating in the forward-active region
- Probably won't enter saturation since low V_{CE} turns off regulator
- Could approach cut-off region
 - Drop from i_{BJT} through R_5 raises V_E
 - To maintain V_{BE} , V_B must rise with V_E
 - V_B , the op amp output, span is limited

Design Example: Fully Discrete

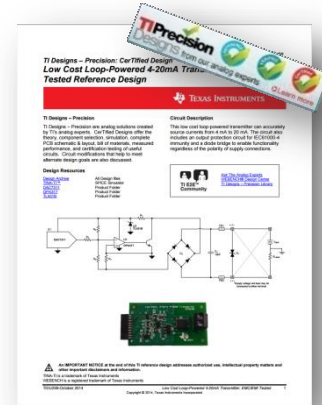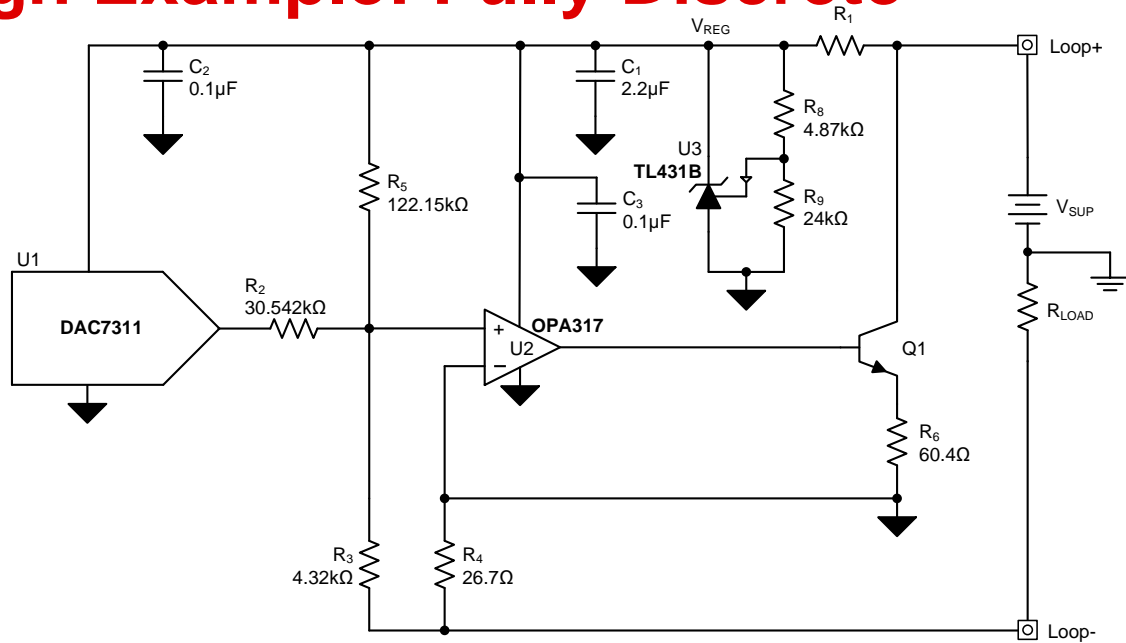

TIPD158



• Alternate DACs:

- DAC5311, DAC6311, DAC7311, DAC8311, DAC8411
- DAC8550/DAC8551 (16-bit, Buffered Output)
- DAC8830 (16-bit, Very High Accuracy)

• Alternate Amplifiers:

- OPA316
- OPA170
- OPA333

Design Example: Partially Discrete

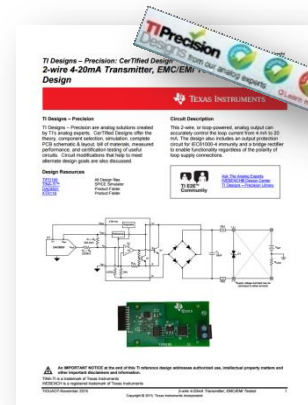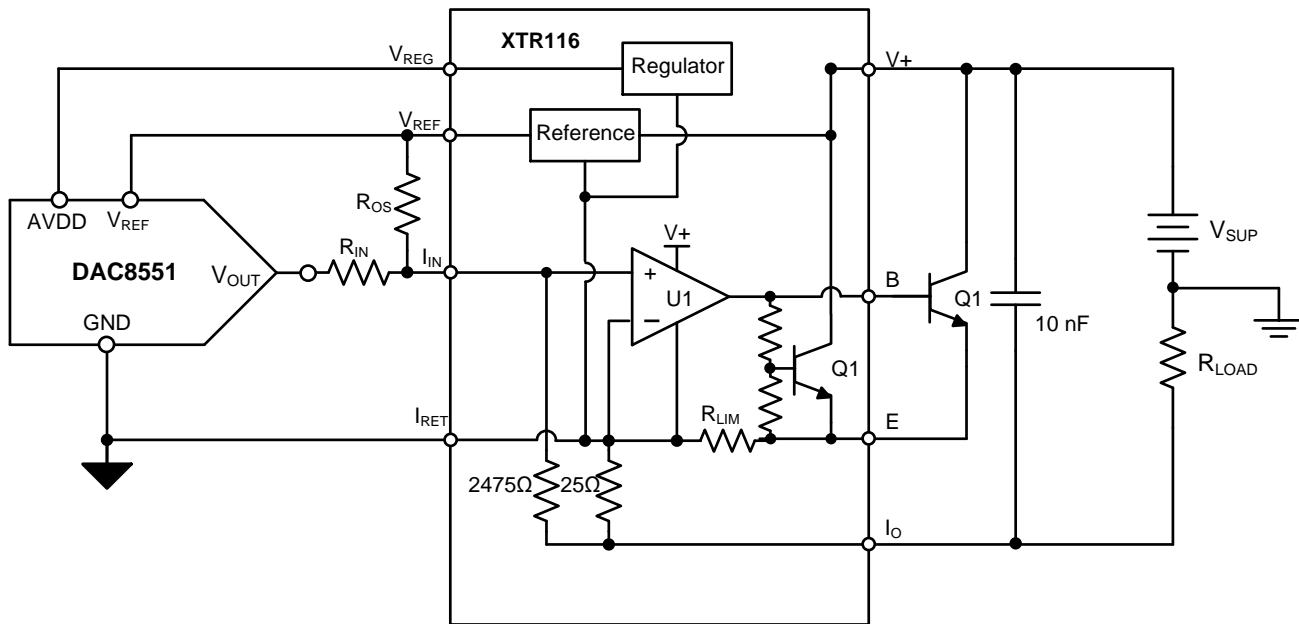

TIPD190

• Alternate DACs:

- DAC5311, DAC6311, DAC7311, DAC8311, DAC8411
- DAC8550/DAC8551 (16-bit, Buffered Output)
- DAC8830 (16-bit, Very High Accuracy)


• Alternate XTRs:

- XTR115
- XTR117

Designing Protection Solutions



*How do parts get damaged? How is this tested?
How do we prevent designs from damage?*

ESD Protection Inside an IC

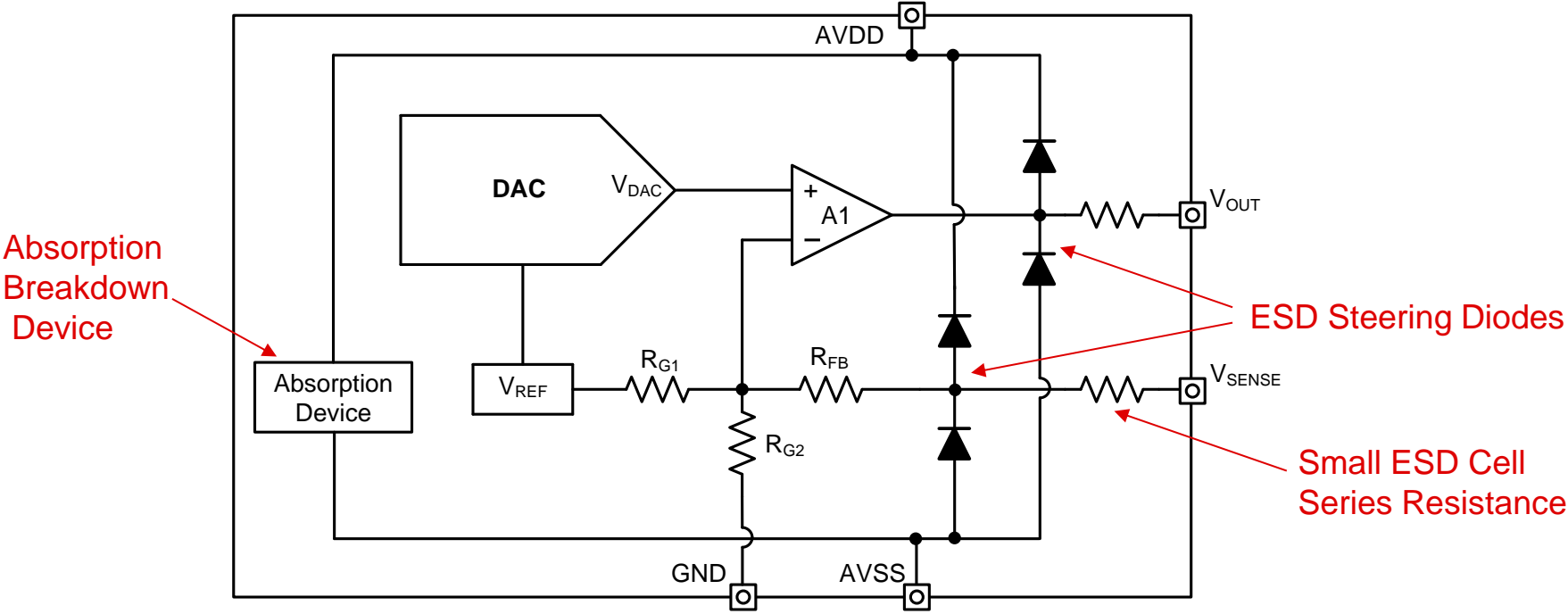



ESD Protection Circuit with ESD Pulse Applied

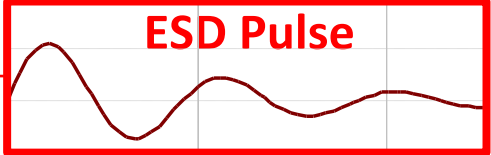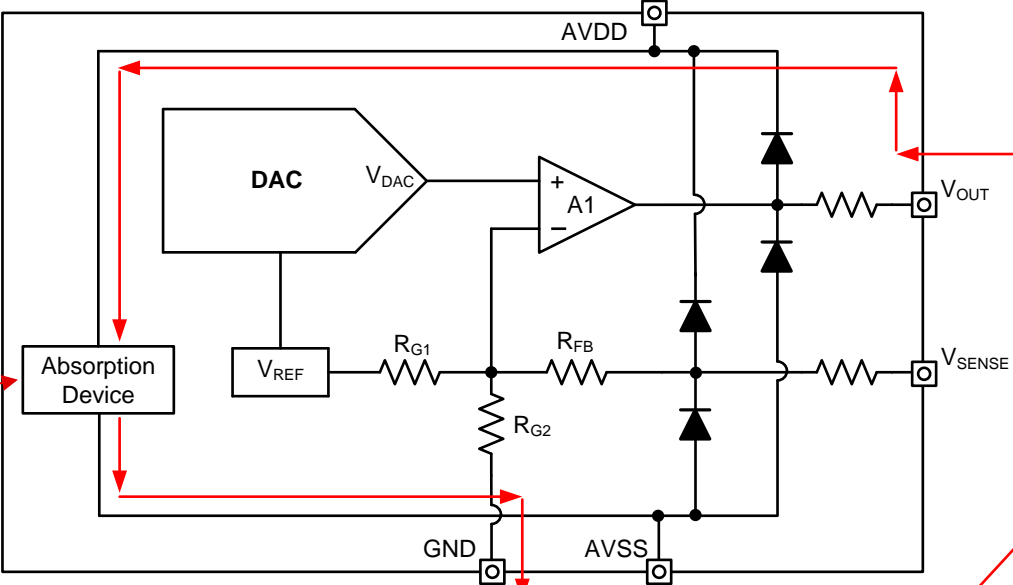ESD diodes direct ESD pulse to absorption device





Types of ESD Simulator Pulses



Human Body Model (HBM)

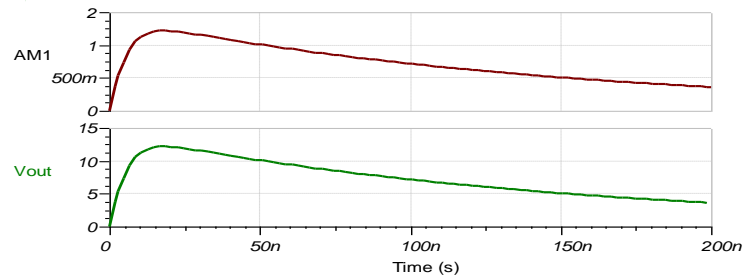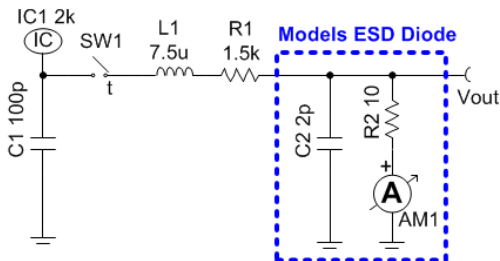

Machine Model (MM)

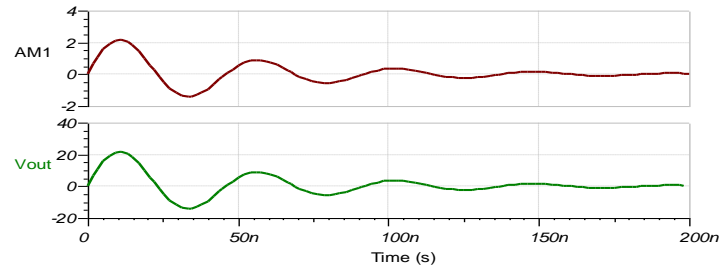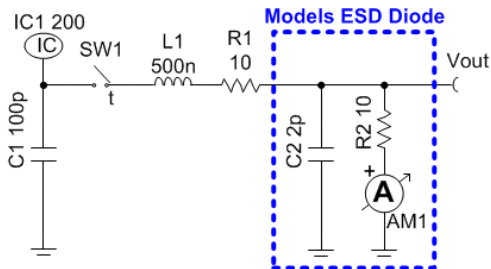

Charged Device Model (CDM)

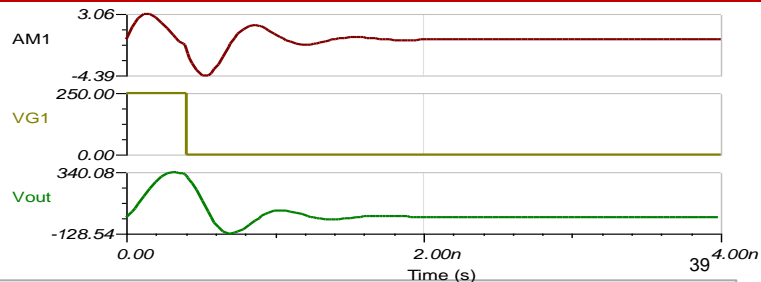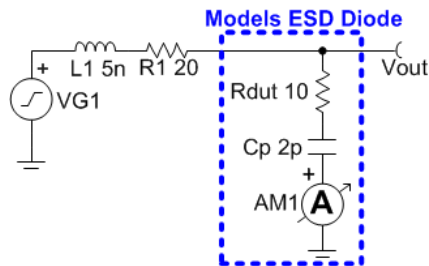

Electrostatic Discharge vs. Electrical Overstress

ESD

- Short duration event (1-100ns)
- High voltage (kV)
- Fast edges
- Low Energy
- Both “in-circuit” and “out-of-circuit”

EOS

- Can be a short or longer duration event
 - Nanoseconds to Milliseconds or more
 - Can be continuous
- High or Lower voltage
 - May be kVs or only a few volts beyond absolute maximum ratings
- High Energy
- “In-circuit” event only

IEC61000-4 Test Suite

- IEC61000-4 contains 35 different immunity test standards
- Most commonly applied immunity tests:
 - Electrostatic Discharges
 - **IEC61000-4-2: Electrostatic Discharge Immunity**
 - HF Conducted Disturbances
 - **IEC61000-4-4: Electrically Fast Transient Immunity**
 - **IEC61000-4-5: Surge Immunity**
 - **IEC61000-4-6: Conducted Immunity Tests**
 - HF Radiated Disturbances
 - **IEC61000-4-3: Radiated Immunity**
 - IEC61000-4-9: Pulse Magnetic Field Tests
 - LF Radiated Disturbances
 - IEC61000-4-8: Power Frequency Magnetic Field Immunity


IEC61000-4 Classifications

- Two Components for each test
 - I. Threat Level
 - II. Class

Classification of results for IEC61000-4 Immunity

Grade	Description
Class A	Normal performance within an error band specified by the manufacturer.
Class B	Temporary loss of function or degradation of performance which ceases after the disturbance is removed. The equipment under test recovers its normal performance without operator interference.
Class C	Temporary loss of function or degradation of performance, correction of performance requires operator intervention.
Class D	Loss of function or degradation of performance which is not recoverable, permanent damage to hardware or software, or loss of data.


Example of Class D Results

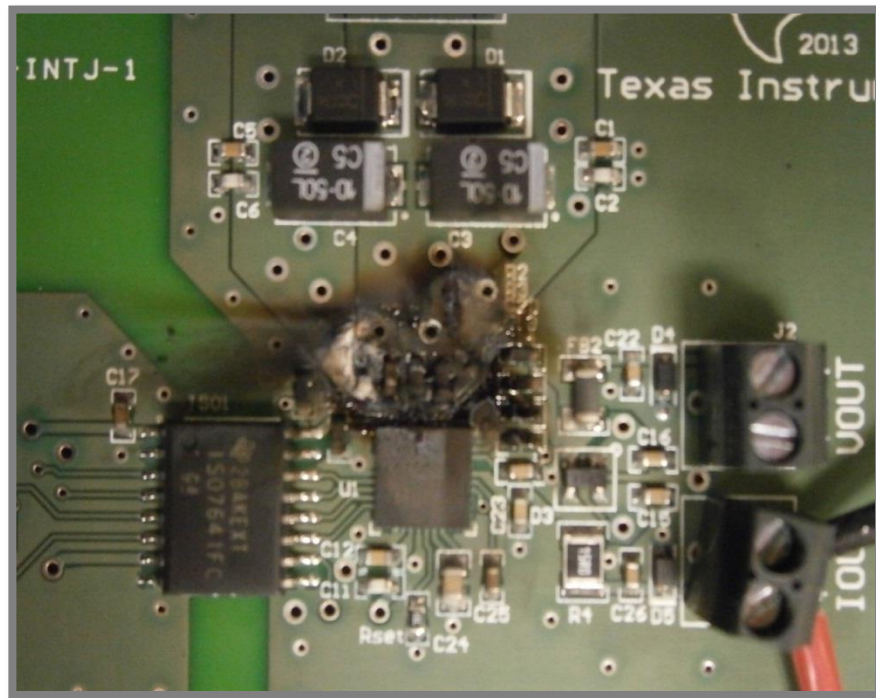

IEC61000-4 Test

- IEC61000-4-2: Electrostatic Discharge Immunity (2kV to 15kV)
 - Simulates the electrostatic discharge of an operator directly onto an electrical component


ESD Test Pulse

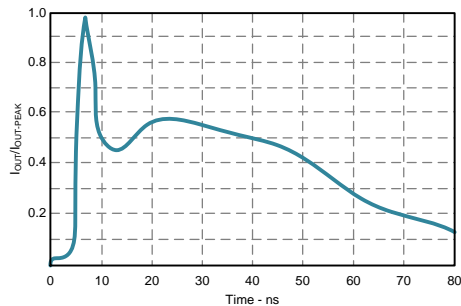

- This is system level immunity
- This ***is not*** JEDEC HBM/CDM/MM device level immunity!!
- Read article for more information:

[Understanding and Comparing the differences in ESD Testing](#)
– T. Kugelstadt & D. Byrd on EDN, Oct 6, 2011

Air Discharge

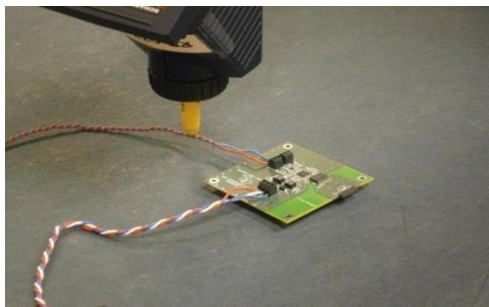

Vertical Coupling




Horizontal Coupling




IEC61000-4 Testing

- IEC61000-4-4: Electrically Fast Transient Immunity (0.5kV to 4kV)
 - Simulates every day switching transients common in industrial applications

EFT Test Pulse

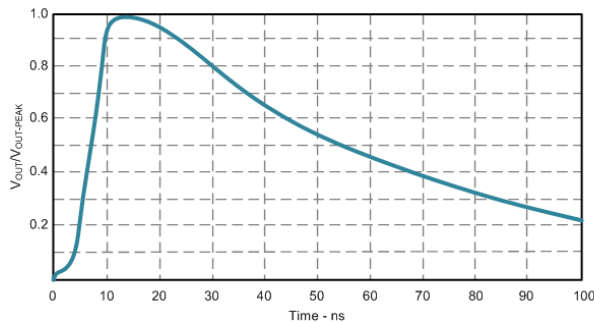

EFT Pulse Train

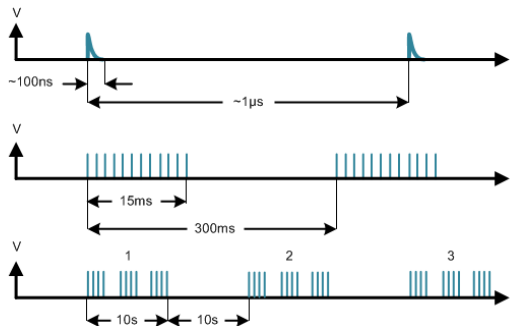


EFT Test Setup




IEC61000-4 Testing

- IEC61000-4-5: Surge Immunity (0.5kV to 4kV)
 - Simulates very severe transients such as lightning strikes
- Output impedance for Surge Immunity tests varies
 - Energy content of test pulse could be very large, protection solution will vary

Surge Test Pulse

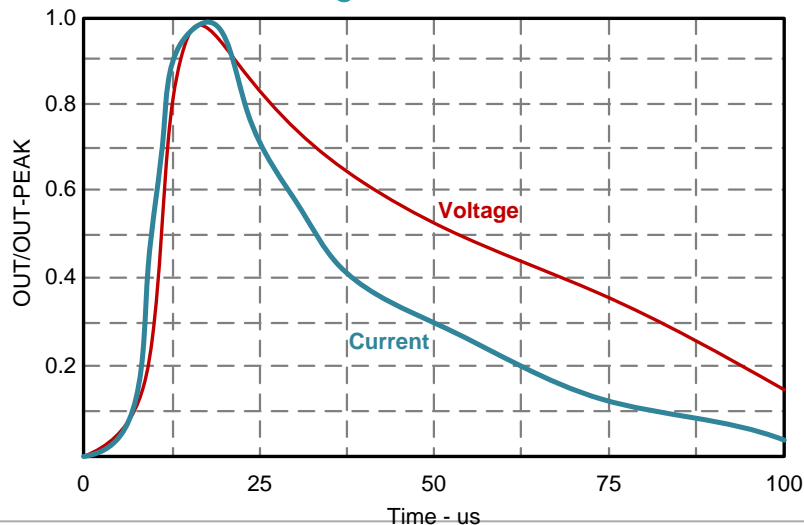

EFT Test Setup

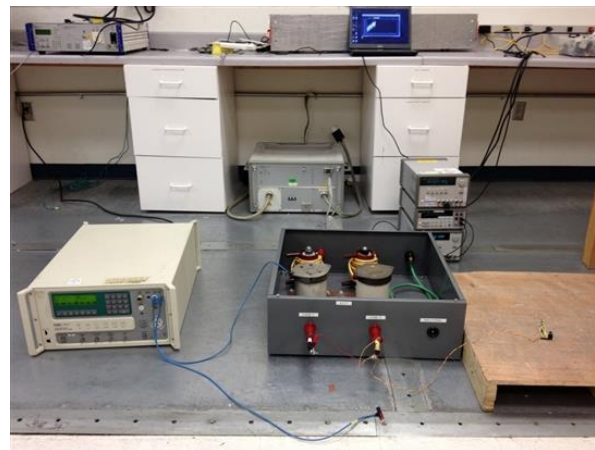


IEC61000-4 Testing

- IEC61000-4-3: Radiated Immunity (1V/m to 30V/m)
 - Simulates exposure to high frequency radiated emissions in the range of 80MHz to 1GHz
- IEC61000-4-6: Conducted Immunity (3V/m to 10V/m)
 - Simulates exposure to radio frequency emissions in the range of 150kHz to 80MHz

RI Horizontal Setup




RI Vertical Setup

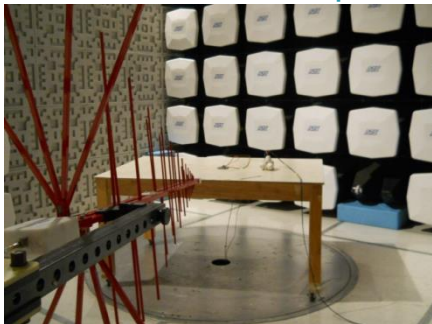


CI Test Setup



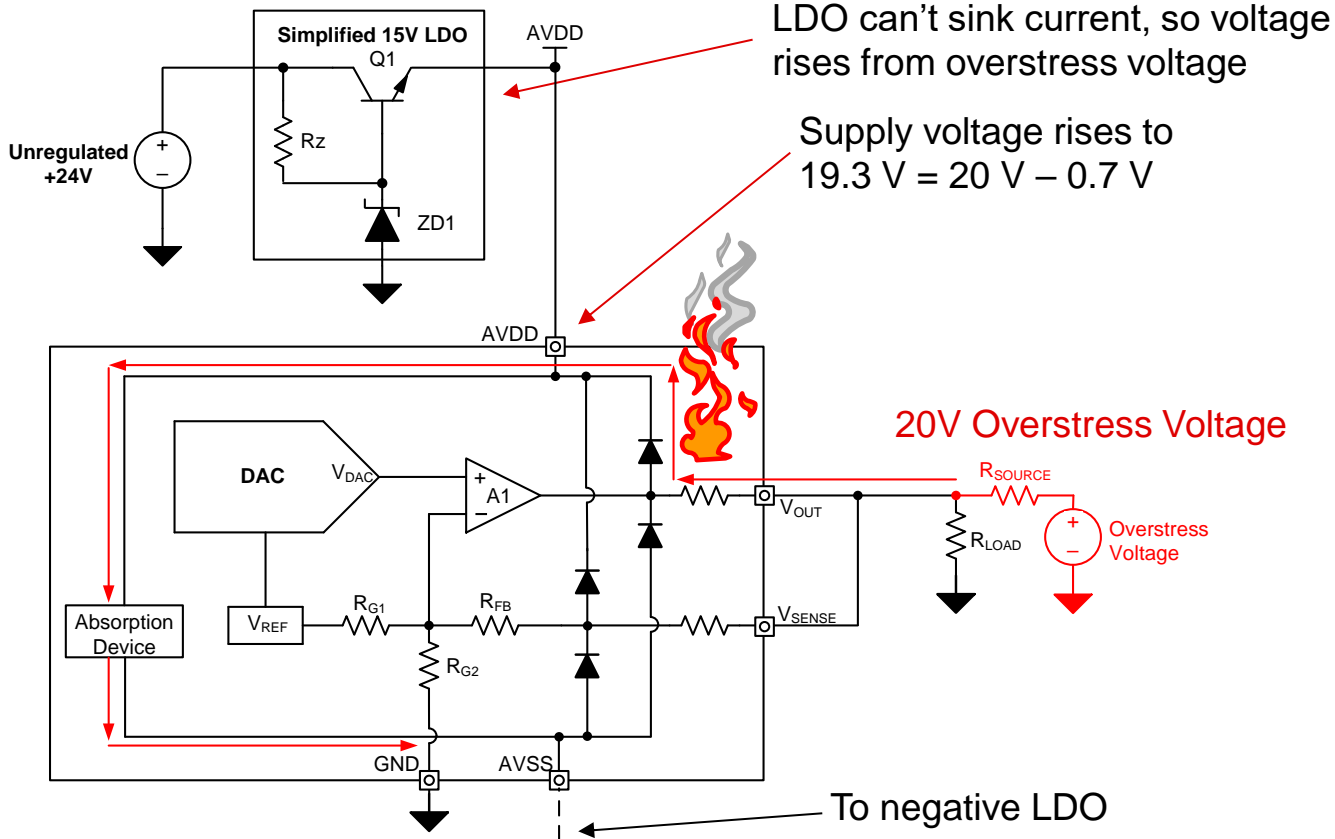
Continuous Electrical Overstress on Output





Fast Electrical Overstress on Output

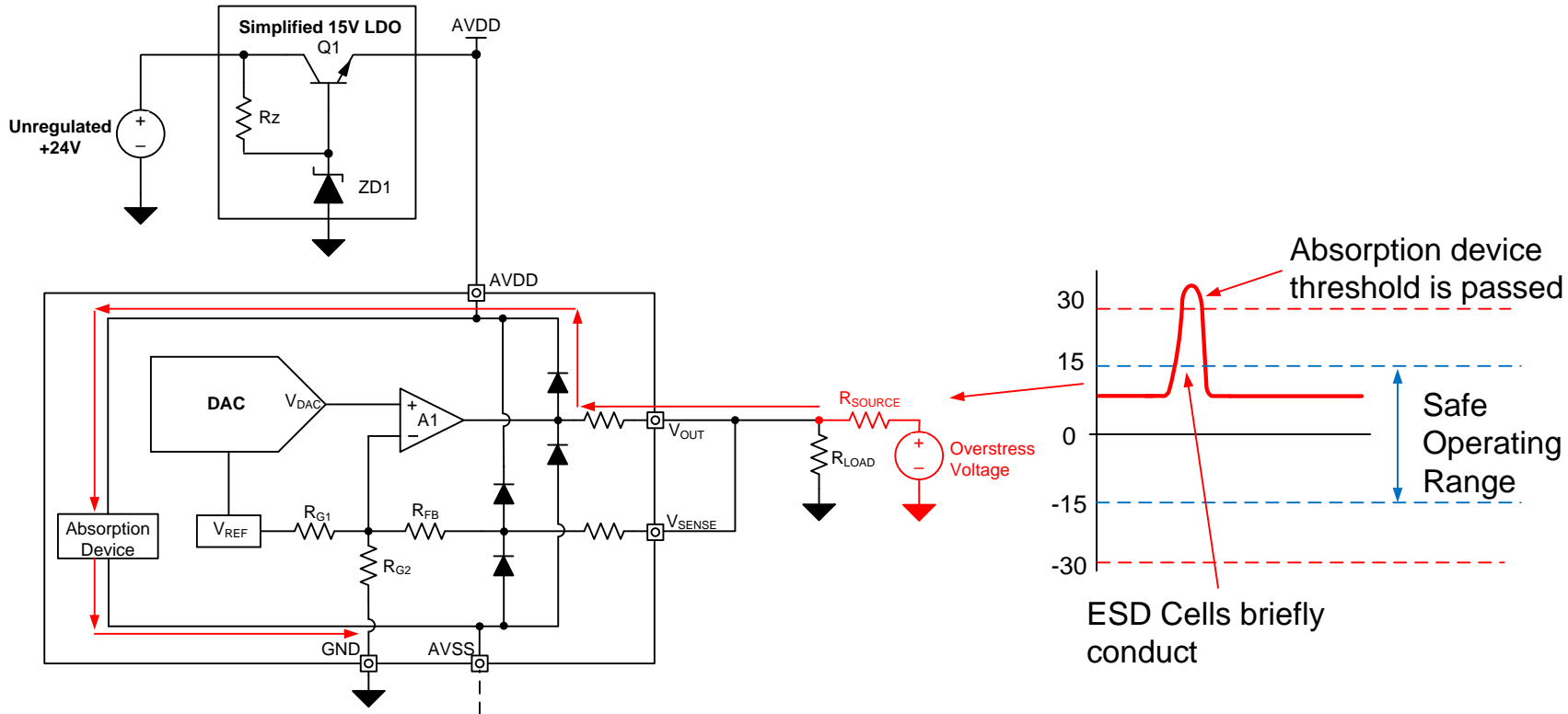

Fast Electrical Overstress on Output

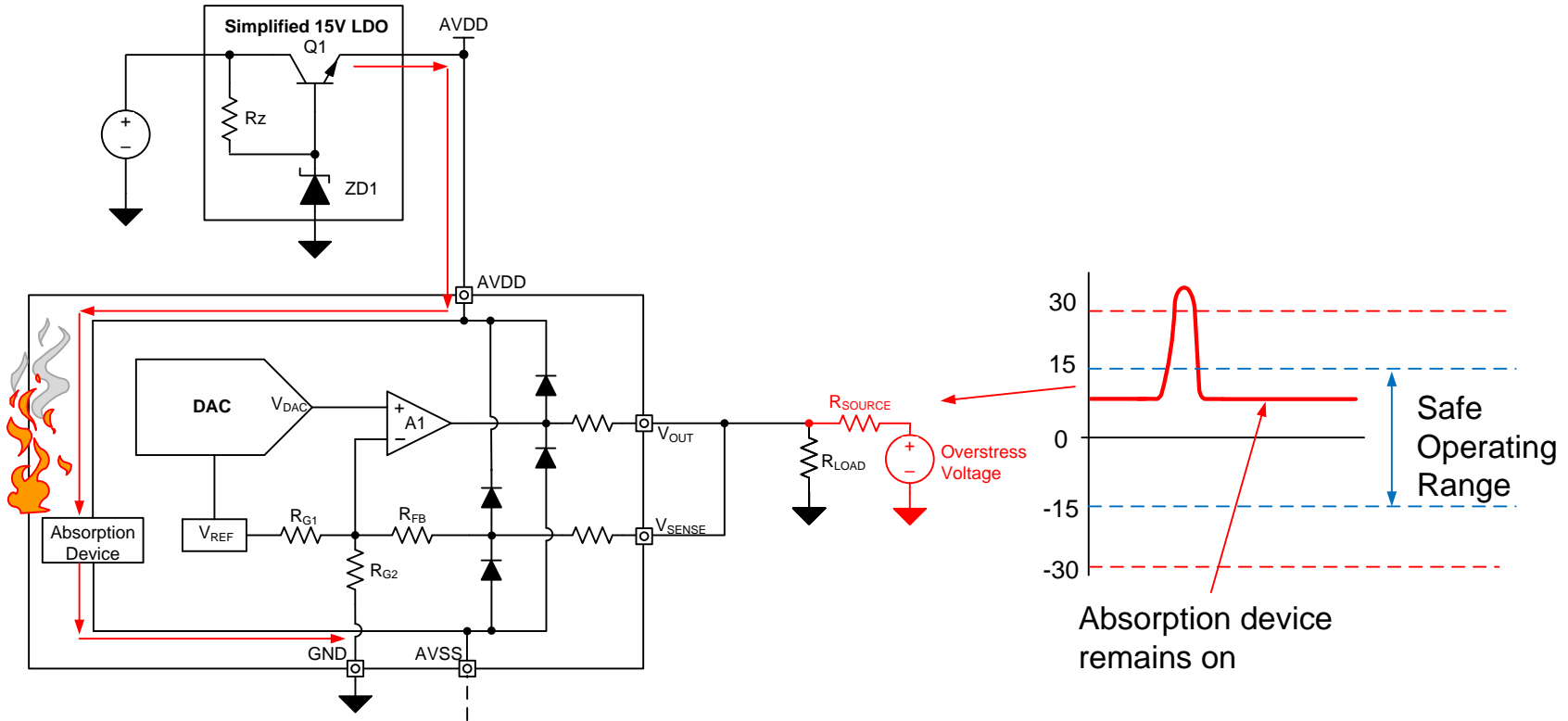

EMC/EMI Tested Analog Output

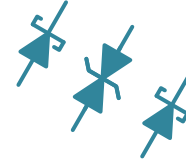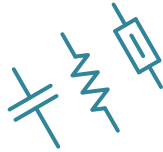


Attenuation

- This method uses passives (resistors, capacitors, ferrite beads) to *attenuate* sudden voltage changes and limit current
- Level of protection depends on ability to anticipate input signal magnitude, frequency and shape
- IR drops skew DC accuracy
- Excessive capacitance limits bandwidth

Diversion

- This method uses voltage clamps (TVS diodes, Schottky diodes)
- These devices *clamp* the input voltage and divert the energy away from the IC
- *Does not limit current*
- Parasitic capacitance, current leakage and response time can complicate design


Simple RC Filter Can Reduce Transients

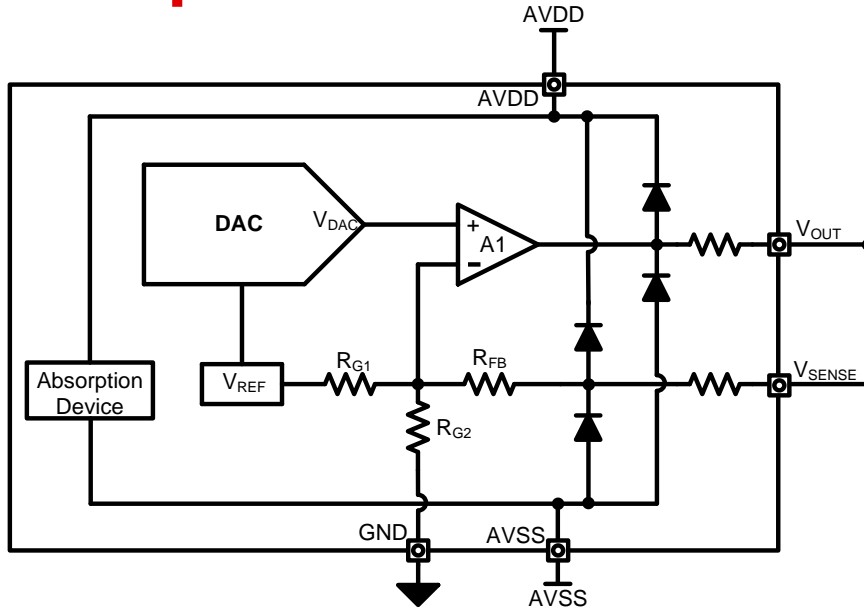

Note: After one time constant, the filter output will be ~63% of maximum

$$f_c = \frac{1}{2\pi C_{Filter} R_{Source}}$$

$$\tau = RC$$

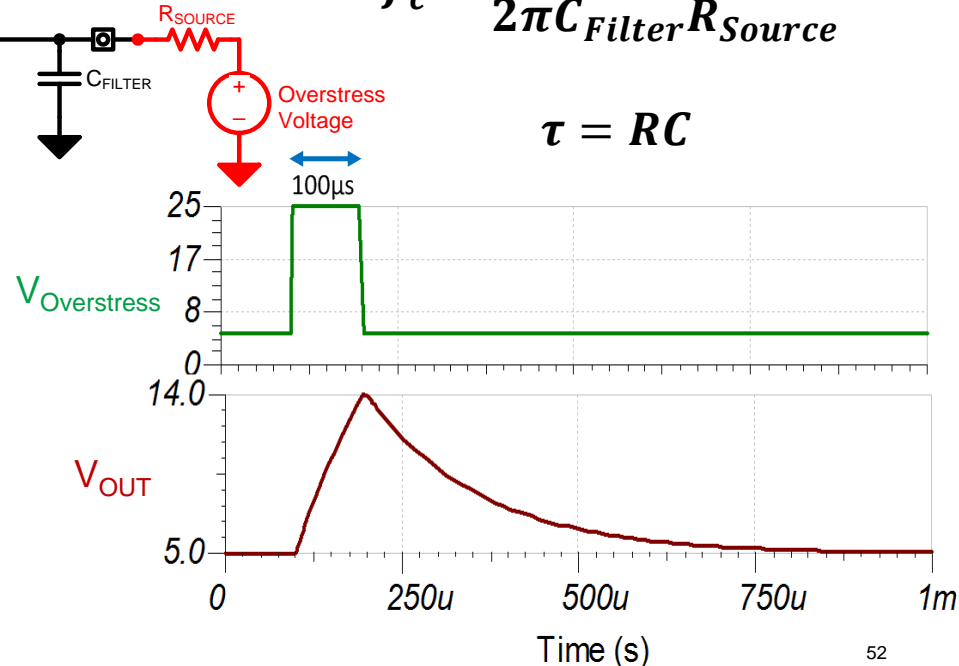

Ferrite Bead/Ferrite Chip

Schematic Symbol



42 m Ω at DC

600 Ω at 600 MHz

3 A rated current


Model




Inductance

Frequency-
variable
resistance


1210 Package (3225 Metric)

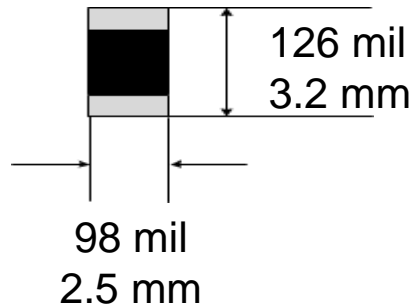


Characteristic

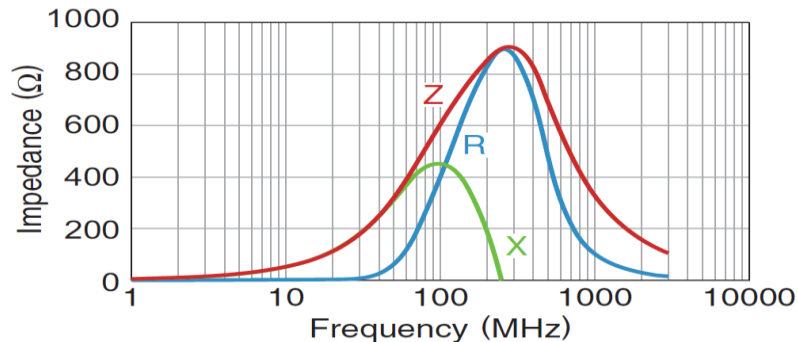

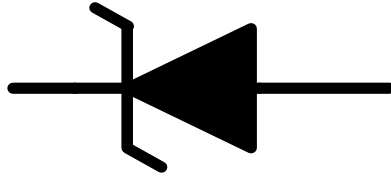Unidirectional Transient Voltage Suppressor (TVS) Diode




Symbol	Parameter
V_{BR}	Breakdown voltage
V_R	Stand-off voltage
V_C	Clamping voltage
V_F	Forward voltage drop
I_{BR}	Breakdown Current @ V_{BR}
I_R	Reverse Leakage @ V_R
I_F	Forward Current @ V_F
I_{PP}	Peak Pulse current @ V_C

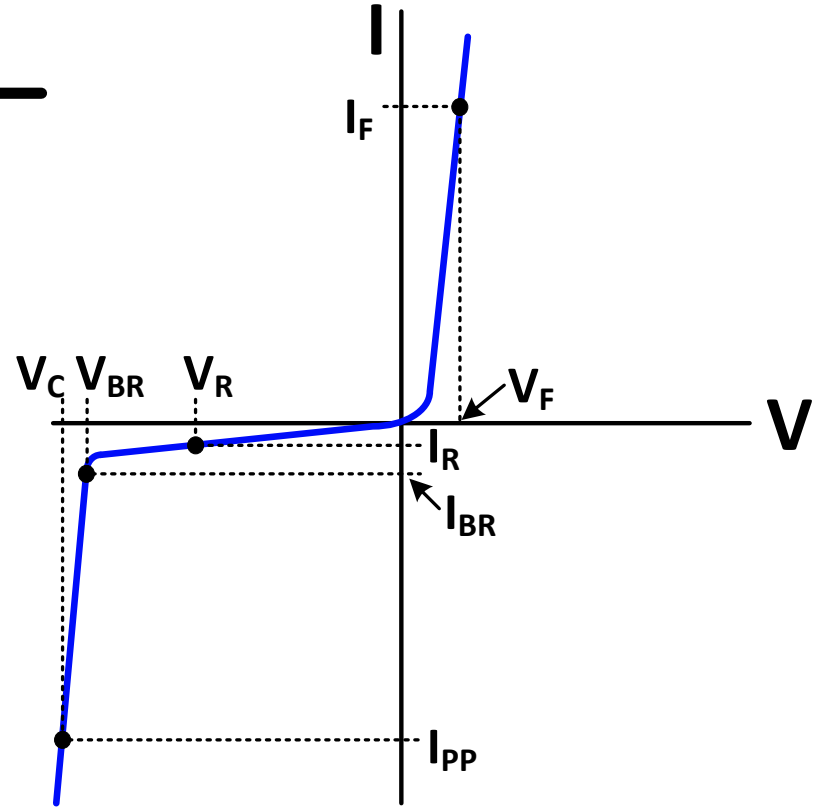


Set V_R = maximum operating supply voltage

Note: leakage current I_R is specified at V_R

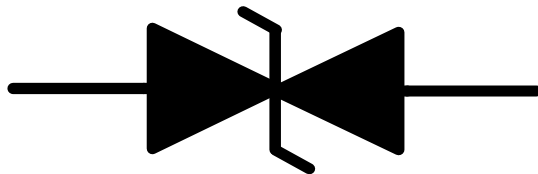Bidirectional Transient Voltage Suppressor (TVS) Diode




Symbol	Parameter
V_{BR}	Breakdown voltage
V_R	Stand-off voltage
V_C	Clamping voltage
V_F	Forward voltage drop
I_{BR}	Breakdown Current @ V_{BR}
I_R	Reverse Leakage @ V_R

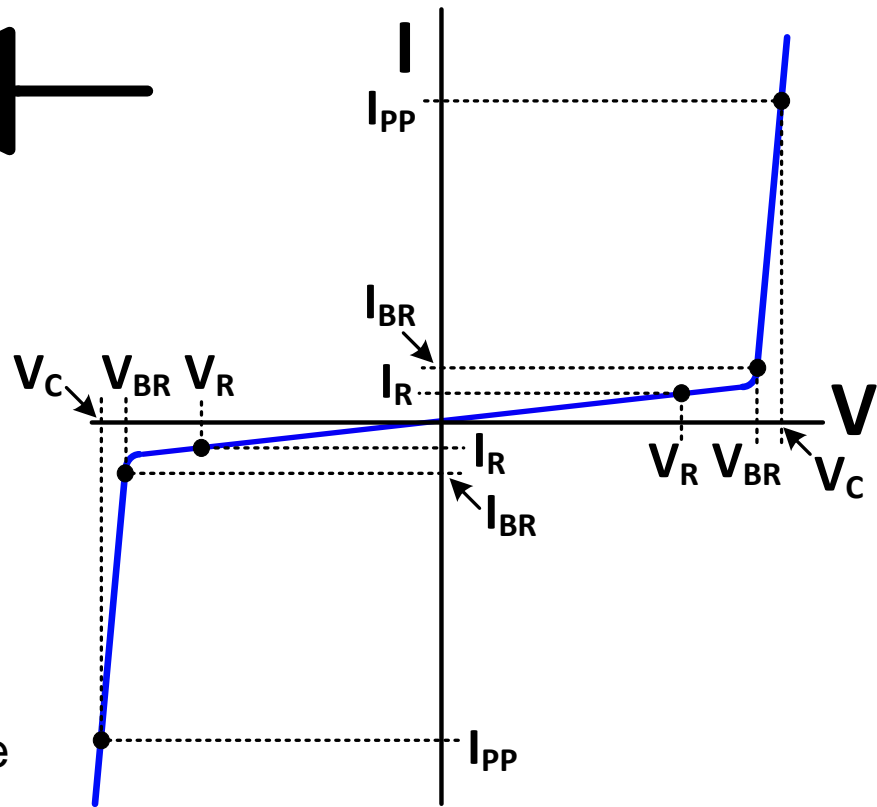


Set V_R = maximum operating supply voltage

Note: leakage current I_R is specified at V_R

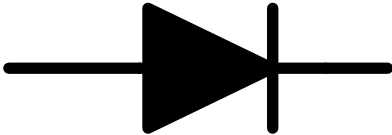
Low Forward Voltage Diodes (may be Schottky)




Symbol	Parameter
V_R	Max reverse voltage
V_F	Forward voltage drop
I_R	Reverse Leakage @ V_R
I_F	Forward Current @ V_F
I_{PP}	Peak Pulse current @ V_C

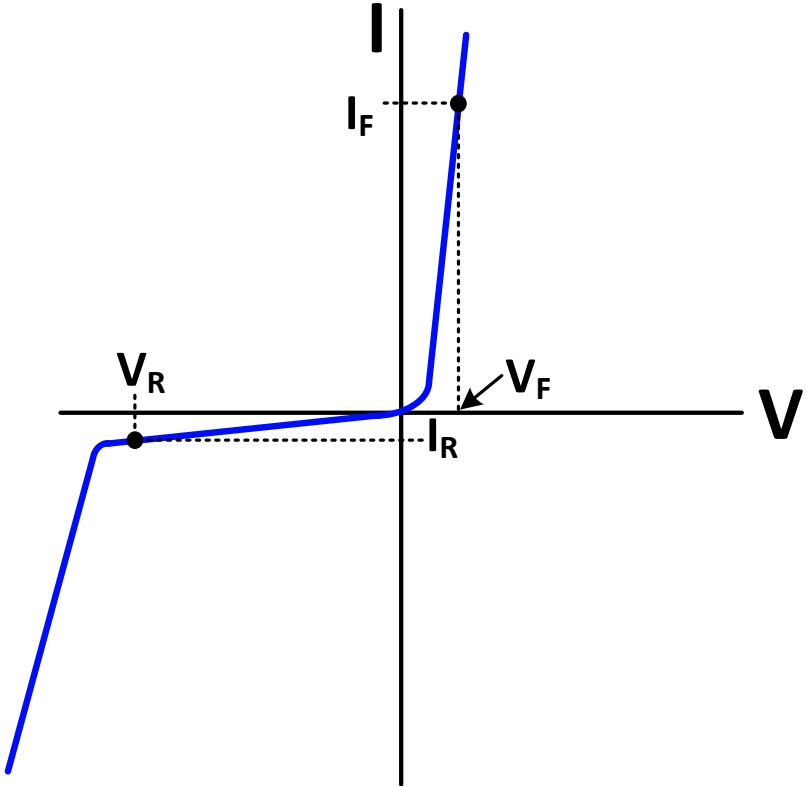


TVS Diodes on Supplies, Pass Element

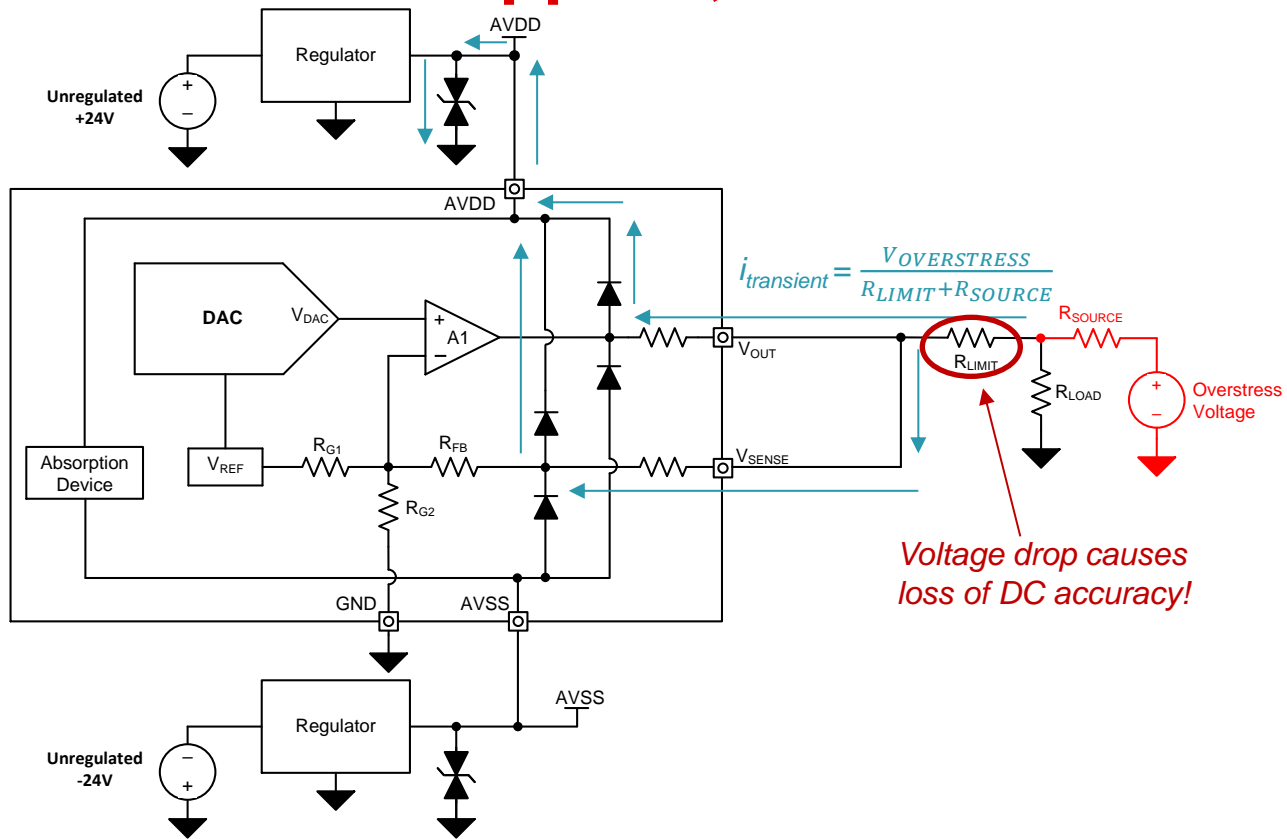

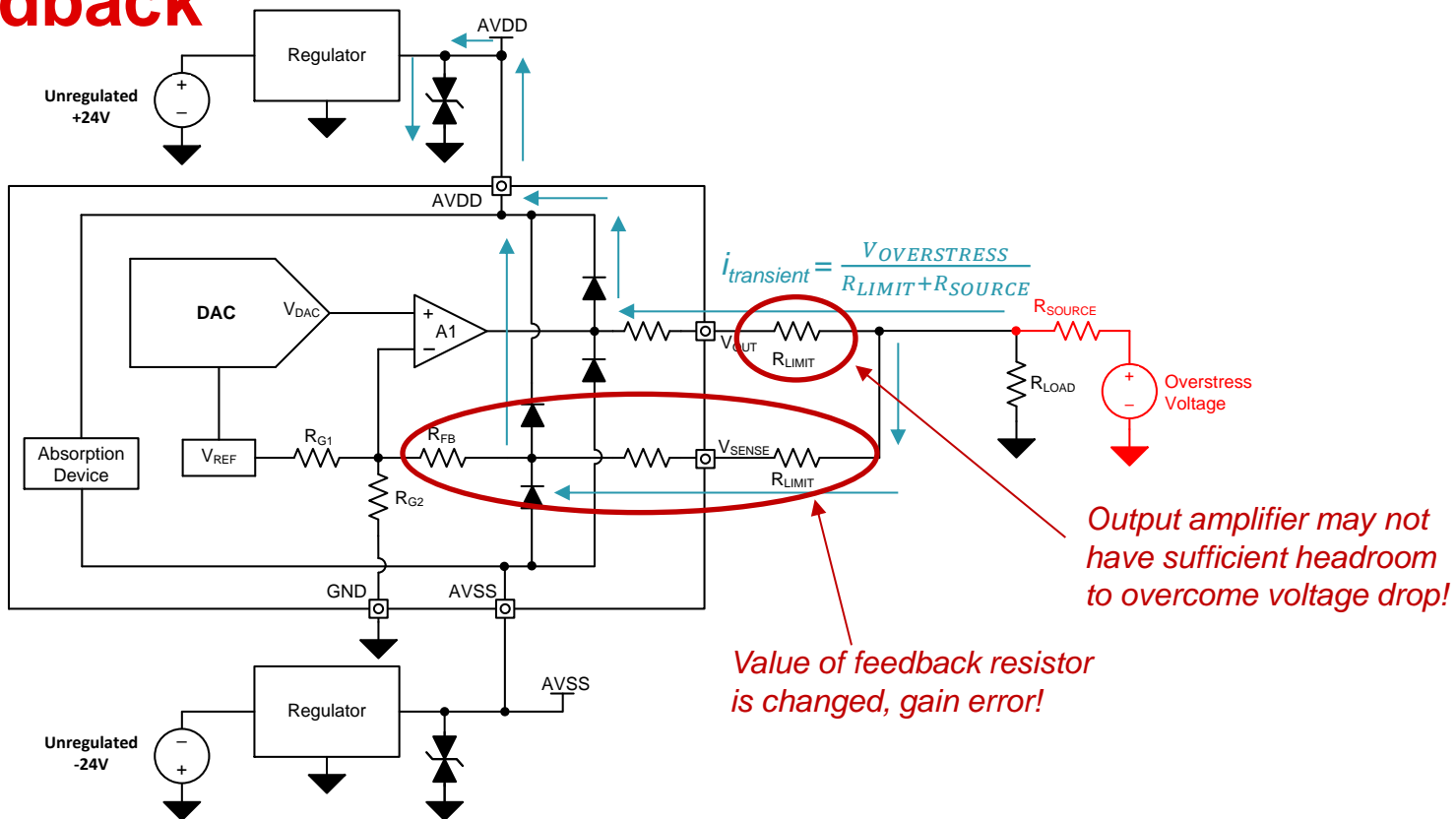
TVS Diodes on Supplies, Pass Elements inside Feedback




TVS Diodes on Output and Supplies

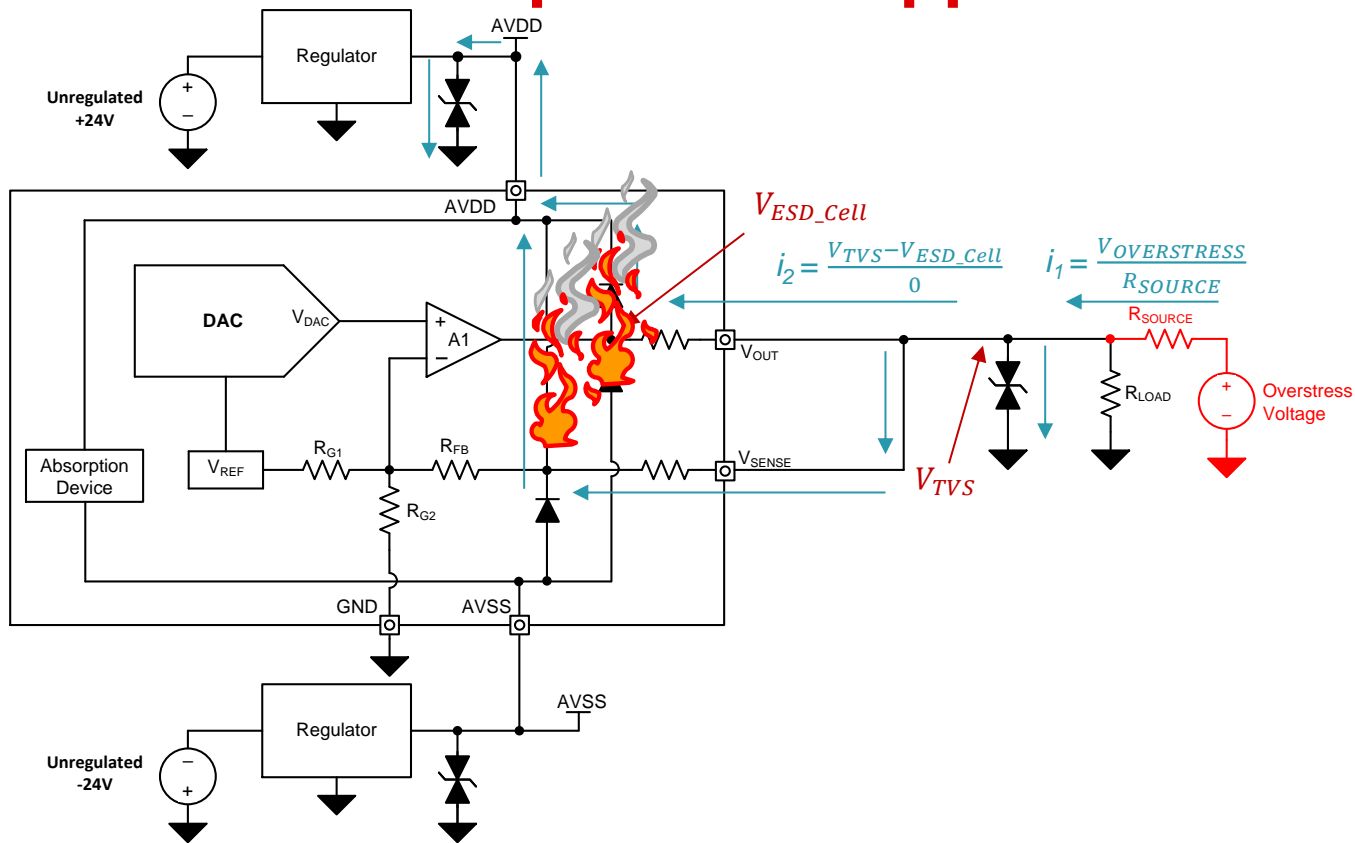


TVS Diodes & Pass Elements

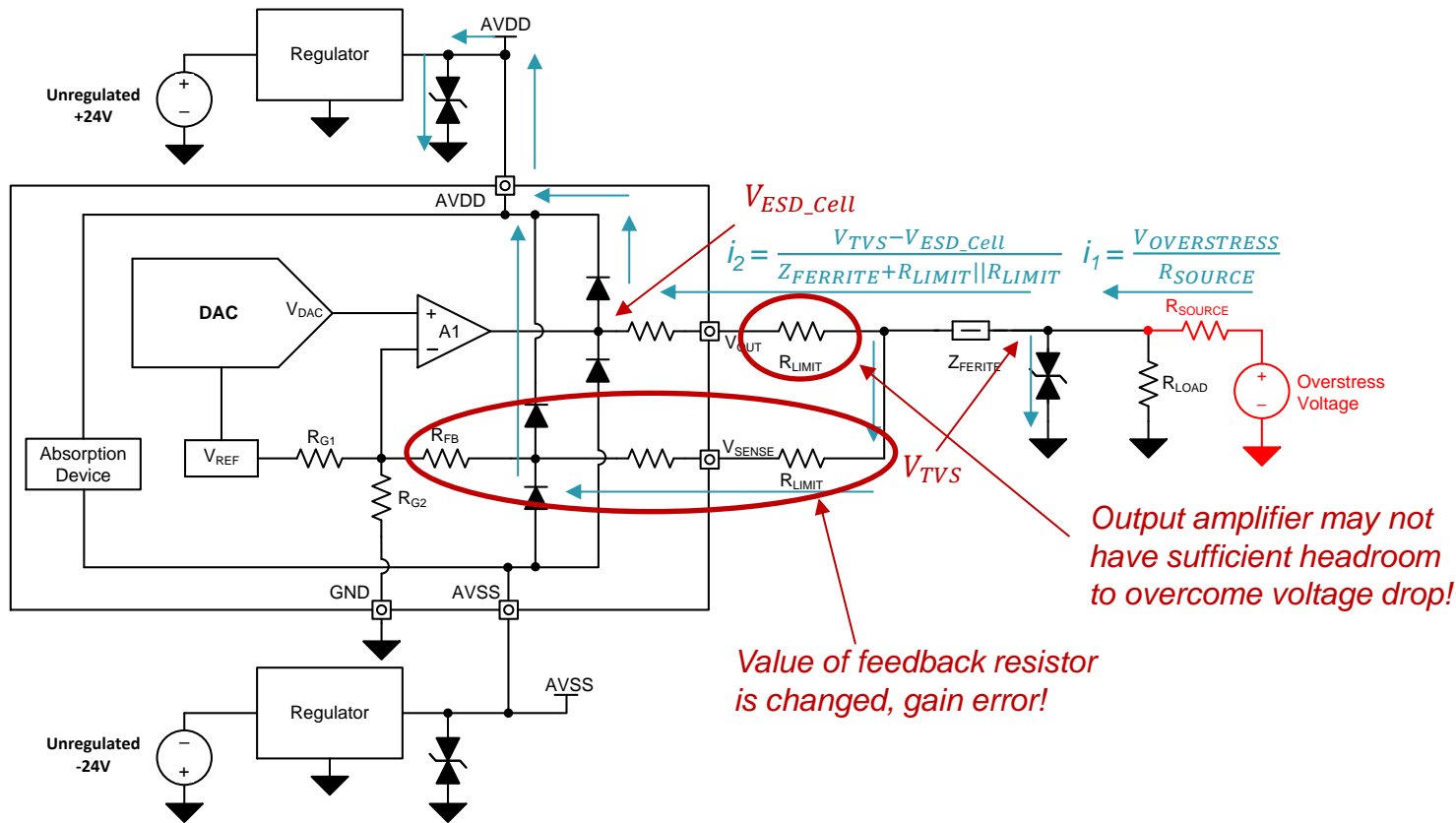

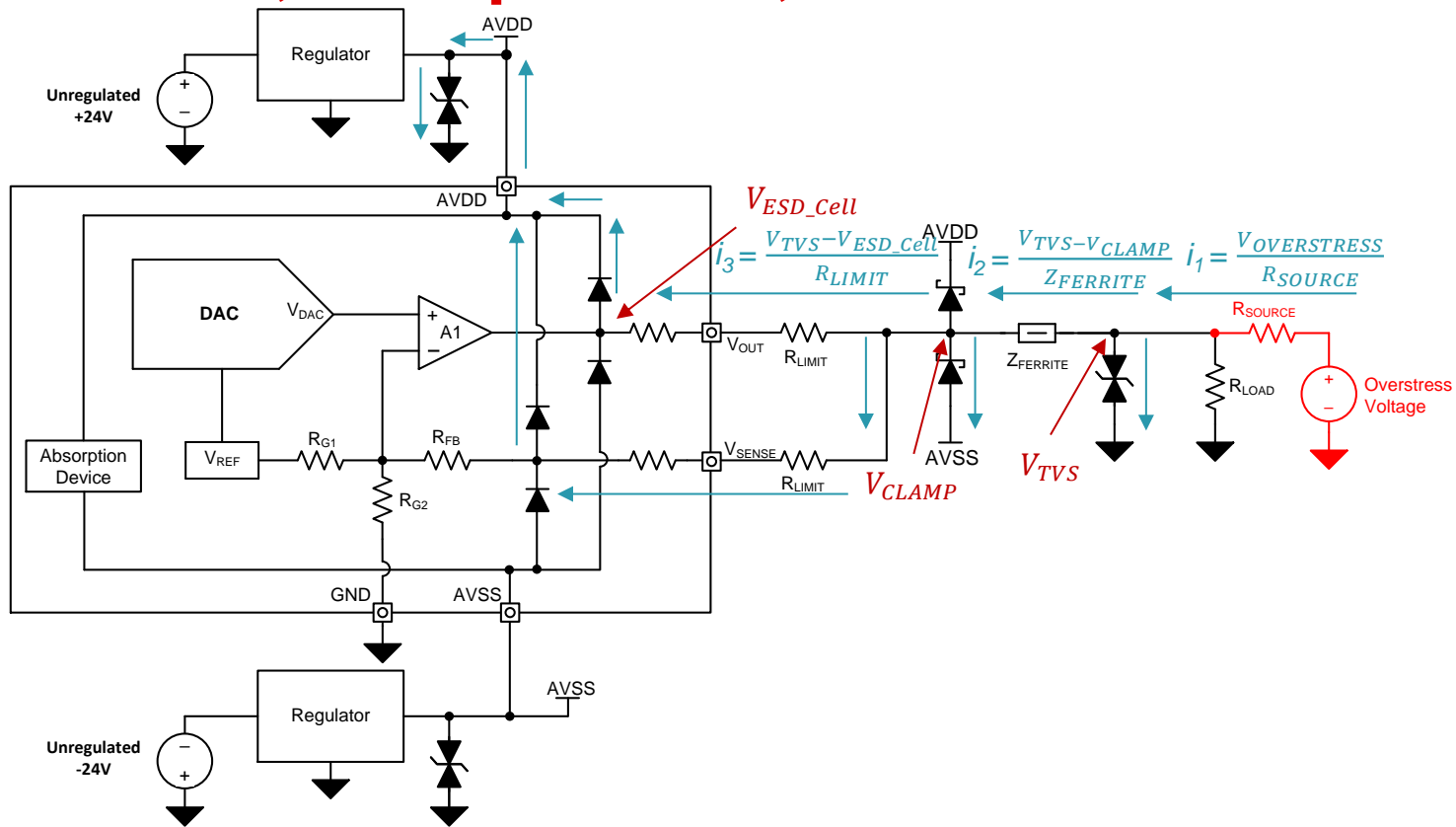TVS Diodes, Clamp-to-Rail, & Pass Elements



Complete Protection Circuit

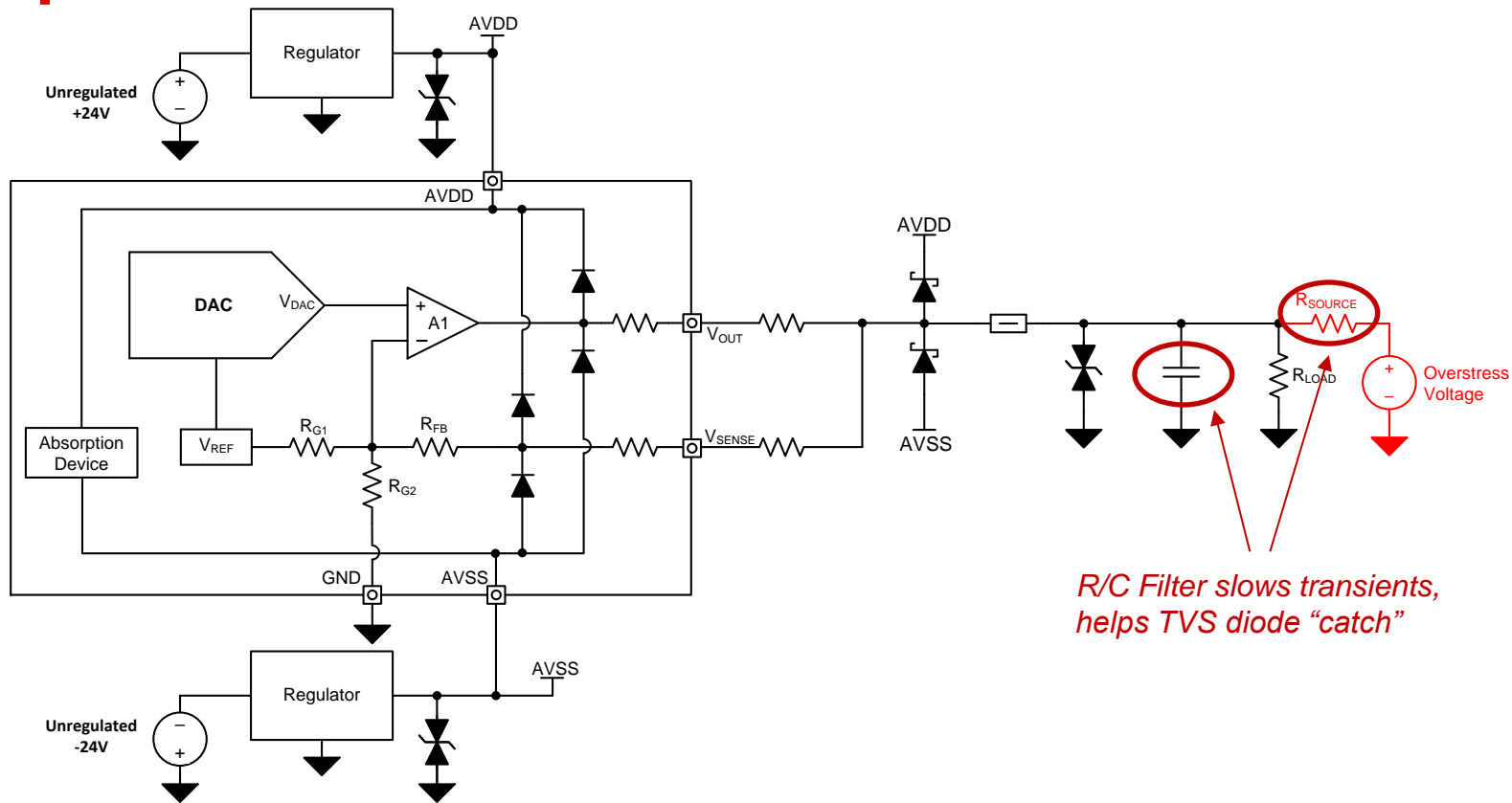

Supporting Collateral

- TI Precision Designs
 - [TIPD101](#): Low-Side Voltage-to-Current Converter
 - [TIPD102](#): High-Side Voltage-to-Current Converter
 - [TIPD119](#): Single Channel Shared Voltage/Current Output Terminal
 - [TIPD125](#): Bipolar +/-10V from a Unipolar DAC
 - [TIPD126](#): Bridge Sensor Conditioner with 2-wire 4-20mA Transmitter, EMC/EMI Tested
 - [TIPD153](#): Single-Channel 3-wire Voltage/Current Output, EMC/EMI Tested
 - [TIPD155](#): Dual Channel Shared Bipolar Voltage/Current Output Terminal
 - [TIPD158](#): Low Cost 2-wire 4-20mA Transmitter, EMC/EMI Tested
 - [TIPD160](#): Analog Linearized 3-Wire PT100 RTD to 2-Wire 4-20mA Current Loop Transmitter Reference Design
 - [TIPD190](#): 2-wire, 4-20mA Transmitter, EMC/EMI Tested Reference Design
 - [TIPD202](#): Analog Linearized 3-Wire PT1000 RTD to 2-Wire 4-20mA Current Loop Transmitter Reference Design
 - [TIPD215](#): Less Than 1-W, Quad-Channel, Analog Output Module w/ Adaptive Power
 - [TIPD216](#): Quad-Channel Industrial Voltage and Current Output Driver, EMC/EMI Tested
- Blog Posts
 - Industrial DACs – Kevin Duke
 - [Part I](#), [Part II](#), [Part III](#), [Part IV](#), [Part V](#), [Part VI](#)
 - [Input Isolation for 3-wire Analog Outputs](#) – Kevin Duke
 - 4-wire 4-20mA Transmitters
 - [Part I](#), [Part II](#), [Part III](#), [Part IV](#)
 - Two-Wire 4-20mA Transmitters: Background & Common Issues – Collin Wells
 - [Part I](#), [Part II](#), [Part III](#), [Part IV](#), [Part V](#), [Part VI](#)
 - Electrical Overstress in a nut shell – Art Kay
 - [Part I](#), [Part II](#), [Part III](#)
 - Get CerTified, not certi-FRIED! Electromagnetic Compatibility Testing Explained – Ian Williams
 - [Part I](#), [Part II](#), [Part III](#), [Part IV](#)



©Copyright 2017 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at TI.com