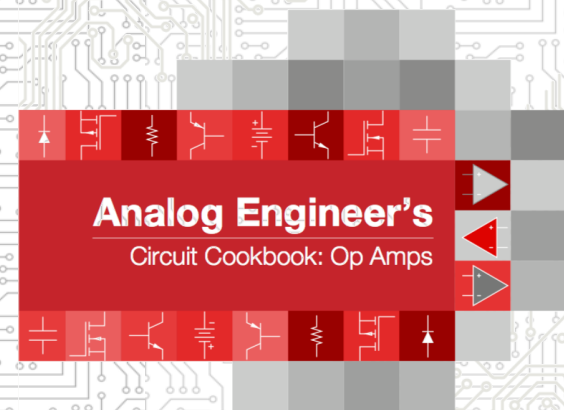


How to Design Single-supply, low-side, unidirectional current sensing circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

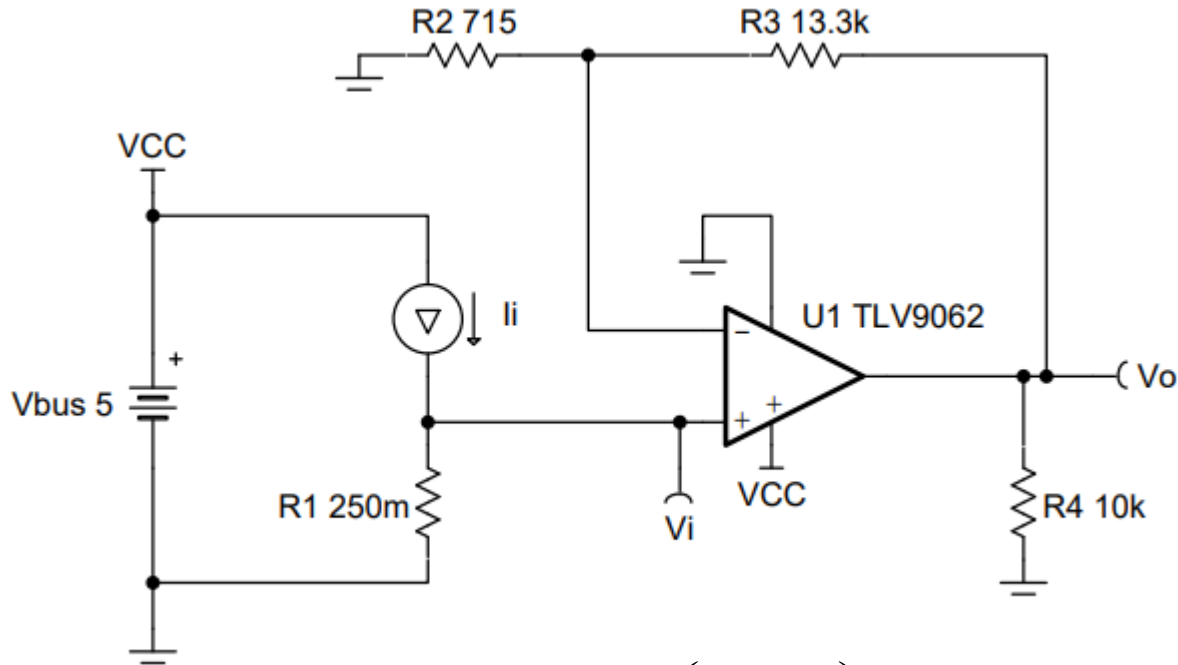

$$V_o = (I_i \times R_1) \times \left(1 + \frac{R_3}{R_2} \right)$$

Design Goals


Input		Output		Full-Scale Range Error	Supply	
I_{iMax}	V_{iMax}	V_{oMin}	V_{oMax}	FSR_{Error}	V_{cc}	V_{ee}
1A	250mV	50mV	4.9V	0.2%	5V	0V

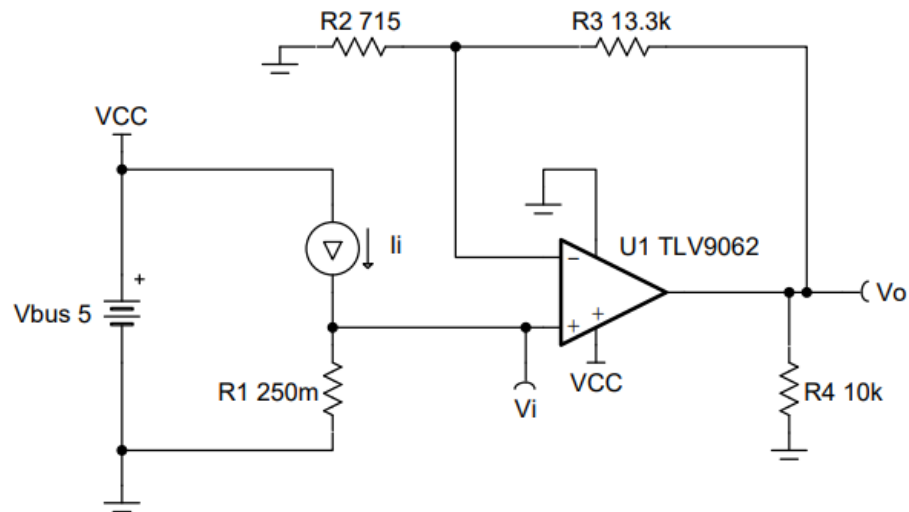

$$V_o = (I_i \times R_1) \times \left(1 + \frac{R_3}{R_2} \right)$$

Design Steps


Input		Output		Full-Scale Range Error	Supply	
I_{iMax}	V_{iMax}	V_{oMin}	V_{oMax}	FSR_{Error}	V_{cc}	V_{ee}
1A	250mV	50mV	4.9V	0.2%	5V	0V

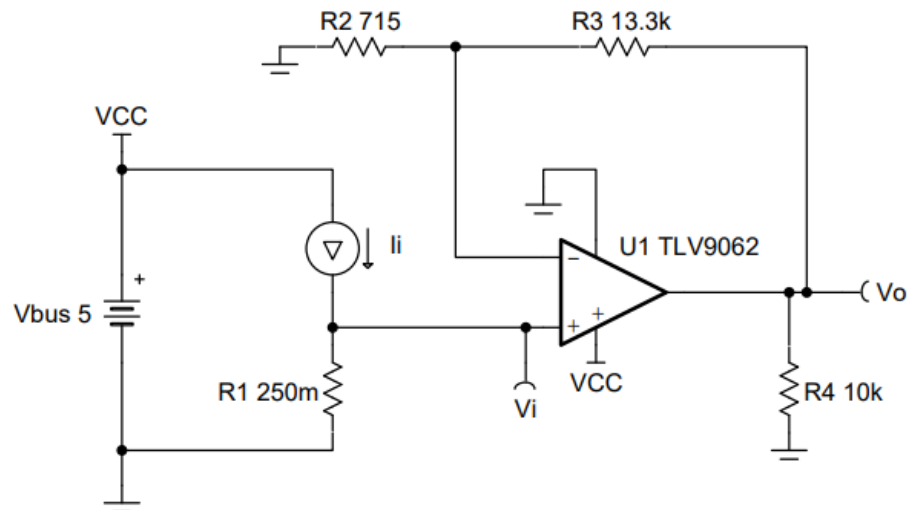

$$R_1 = \frac{V_{iMax}}{I_{iMax}} = \frac{250mV}{1A} = 250m\Omega$$

Design Steps

Input		Output		Full-Scale Range Error	Supply	
I_{iMax}	V_{iMax}	V_{oMin}	V_{oMax}	FSR_{Error}	V_{cc}	V_{ee}
1A	250mV	50mV	4.9V	0.2%	5V	0V

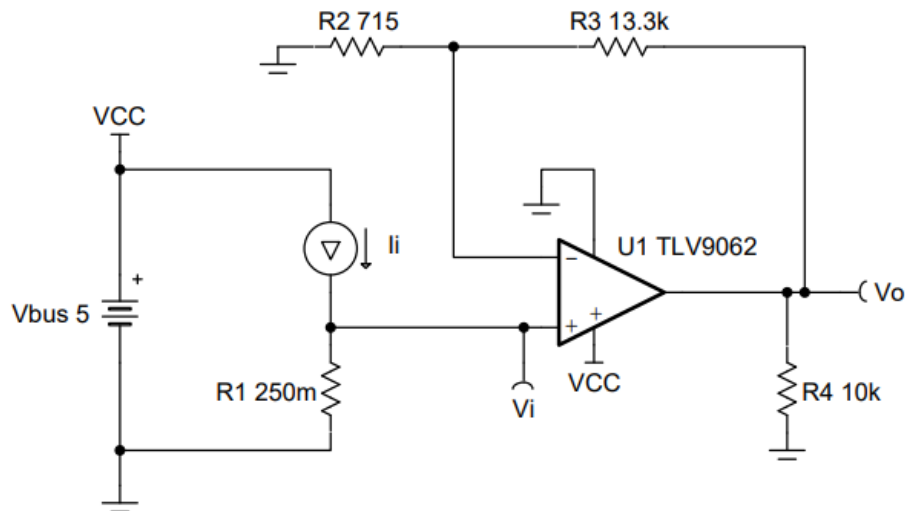

$$\text{Gain} = \frac{V_{oMax}}{V_{iMax}} = \frac{4.9V}{250mV} = 19.6 \frac{V}{V}$$

Design Steps

Input		Output		Full-Scale Range Error	Supply	
I_{iMax}	V_{iMax}	V_{oMin}	V_{oMax}	FSR_{Error}	V_{cc}	V_{ee}
1A	250mV	50mV	4.9V	0.2%	5V	0V

Analog Engineer's Calculator

Select the Calculator

- Data Converters
- Amplifier and Comparators
 - INA Vout vs Vcm
 - Inverting Level Shift
 - Noninverting Level Shift
 - Comparator w Hysteresis
 - Find Amplifier Gain 3 Resistors
 - INA Vcm + Dif Filter
 - Find Amplifier Gain**
- Passive
- Noise
- Stability
- PCB
- Sensor
- Links

Calculator

Type:

R_f :

R_1 :

Target Gain (R_f/R_1):

Best Gain:

Tolerance:


Error(%):

$$R_3 = 13.3k\Omega$$

$$R_2 = 715\Omega$$

Design Steps


Input		Output		Full-Scale Range Error	Supply	
I_{iMax}	V_{iMax}	V_{oMin}	V_{oMax}	FSR_{Error}	V_{cc}	V_{ee}
1A	250mV	50mV	4.9V	0.2%	5V	0V

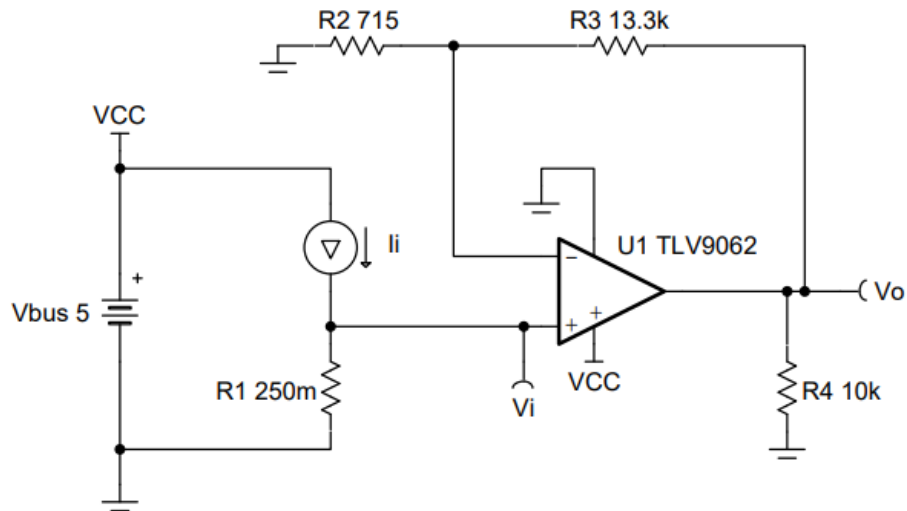

$$I_{iMin} = \frac{V_{oMin}}{R_1 \times \text{Gain}} = \frac{50mV}{250m\Omega \times 19 \frac{V}{V}} = 10.2mA$$

Design Steps

Input		Output		Full-Scale Range Error	Supply	
I_{iMax}	V_{iMax}	V_{oMin}	V_{oMax}	FSR_{Error}	V_{cc}	V_{ee}
1A	250mV	50mV	4.9V	0.2%	5V	0V

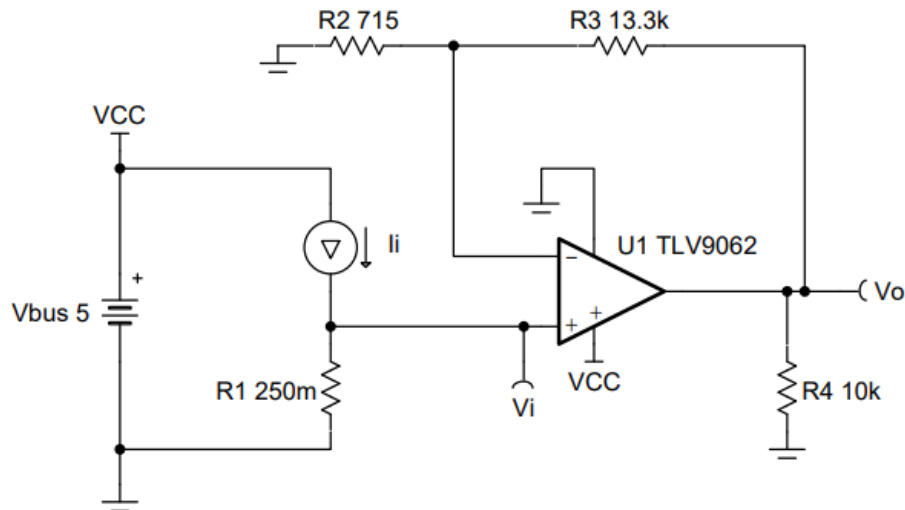



$$FSR_{ERROR} = \left(\frac{V_{OS}}{V_{iMax} - V_{iMin}} \right) \times 100$$

$$FSR_{ERROR} = \left(\frac{300\mu V (typ)}{250mV - 2.55mV} \right) \times 100$$

$$FSR_{ERROR} = 0.12\%$$



DC Results

Input		Output		Full-Scale Range Error	Supply	
I_{iMax}	V_{iMax}	V_{oMin}	V_{oMax}	FSR_{Error}	V_{cc}	V_{ee}
1A	250mV	50mV	4.9V	0.2%	5V	0V

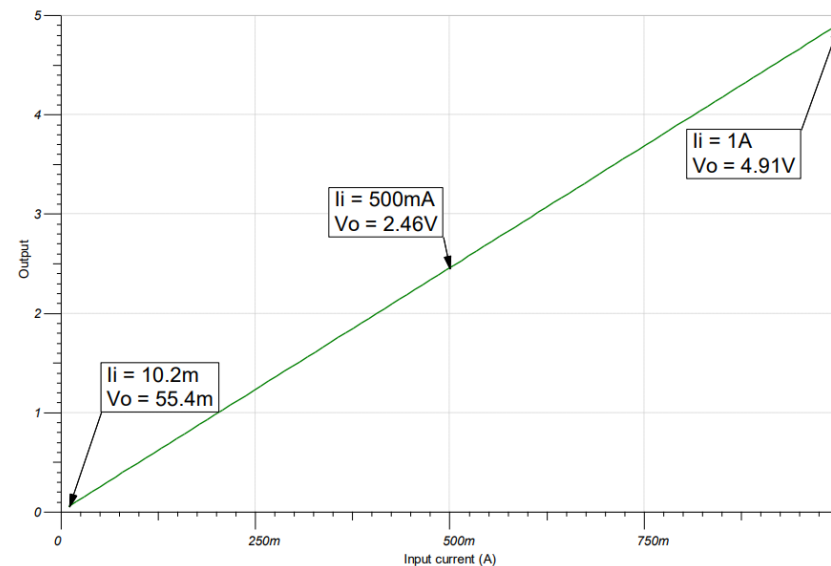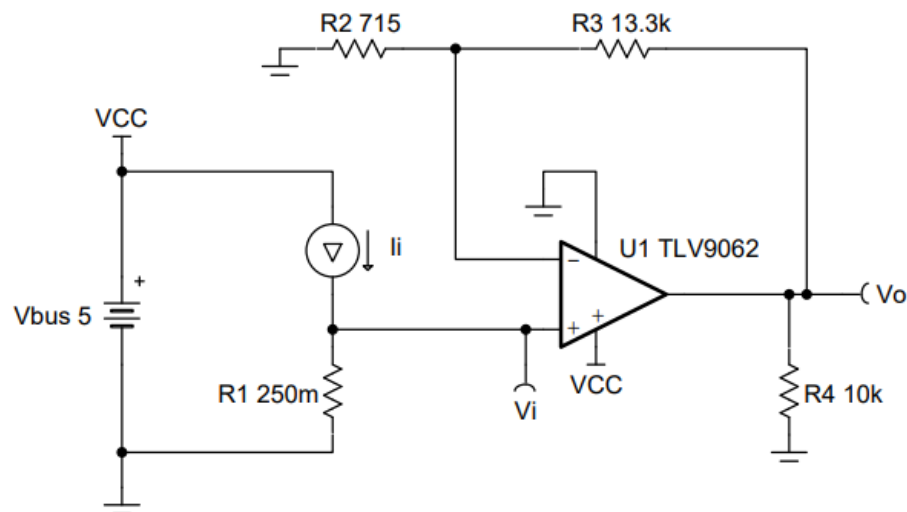

AC Results


Input		Output		Full-Scale Range Error	Supply	
I_{iMax}	V_{iMax}	V_{oMin}	V_{oMax}	FSR_{Error}	V_{cc}	V_{ee}
1A	250mV	50mV	4.9V	0.2%	5V	0V

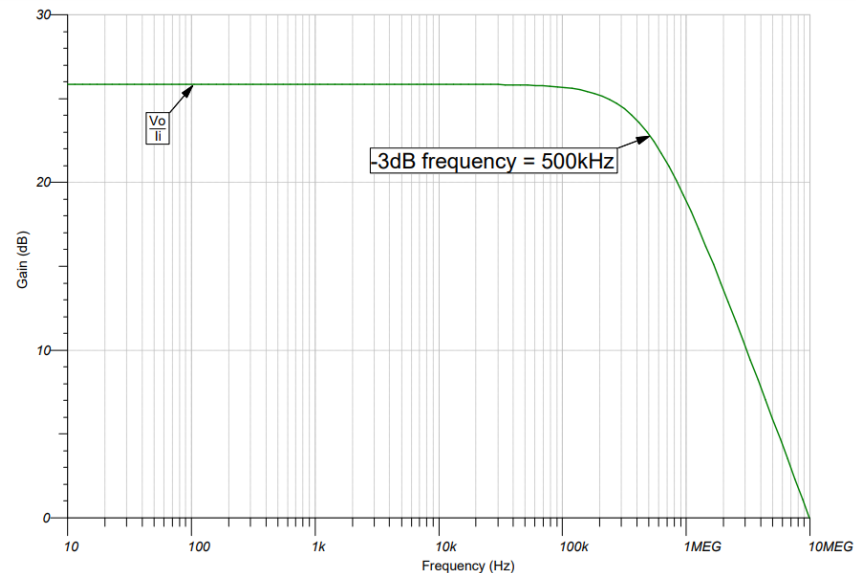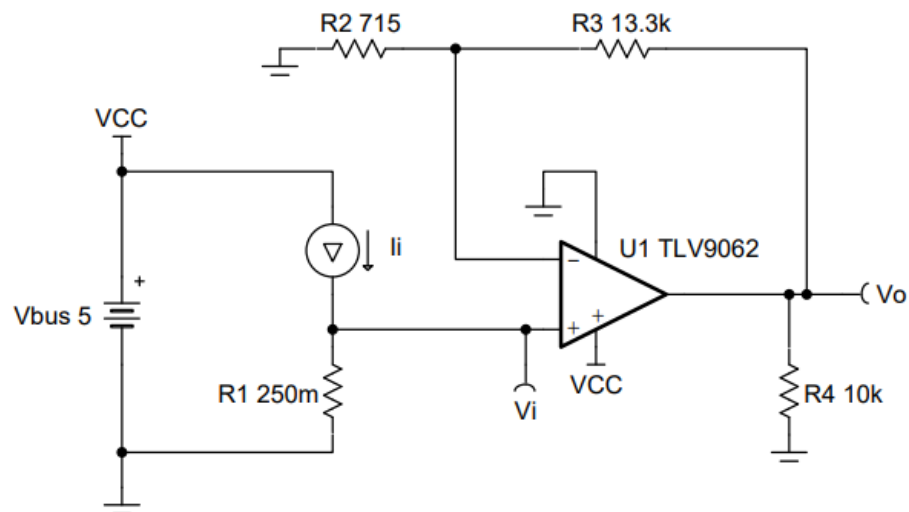

www.ti.com/circuitcookbooks

Design Notes

Input		Output		Full-Scale Range Error	Supply	
I_{iMax}	V_{iMax}	V_{oMin}	V_{oMax}	FSR_{Error}	V_{cc}	V_{ee}
1A	250mV	50mV	4.9V	0.2%	5V	0V

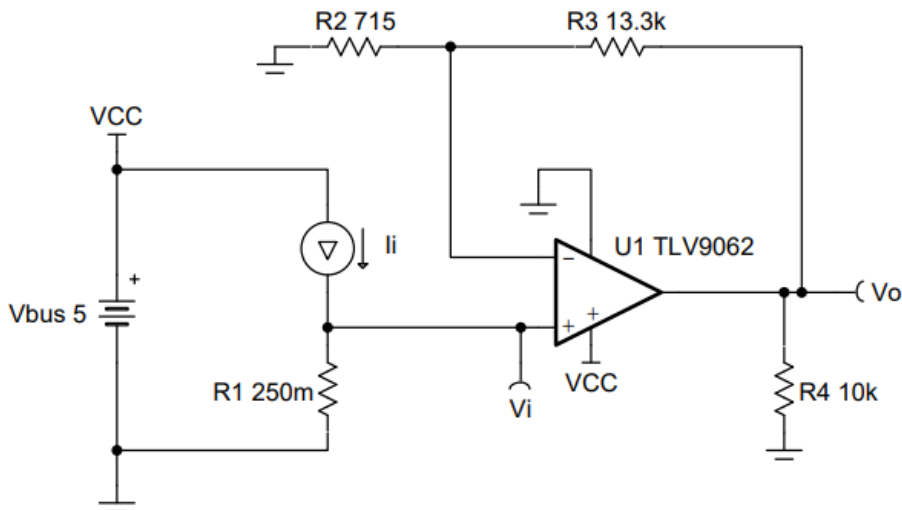

Design Notes:

1. For low-side sensing, use op amps whose V_{cm} includes ground
2. Operate within the linear output voltage swing (See A_{OL} specification) to minimize non-linearity errors.
3. If trying to detect zero load current, a negative charge pump such as LM7705 for the negative supply voltage.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/signalbook

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2019 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)