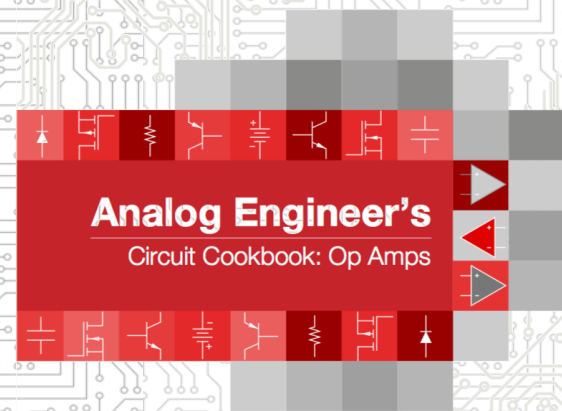


How to Design Temperature sensing with PTC thermistor circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

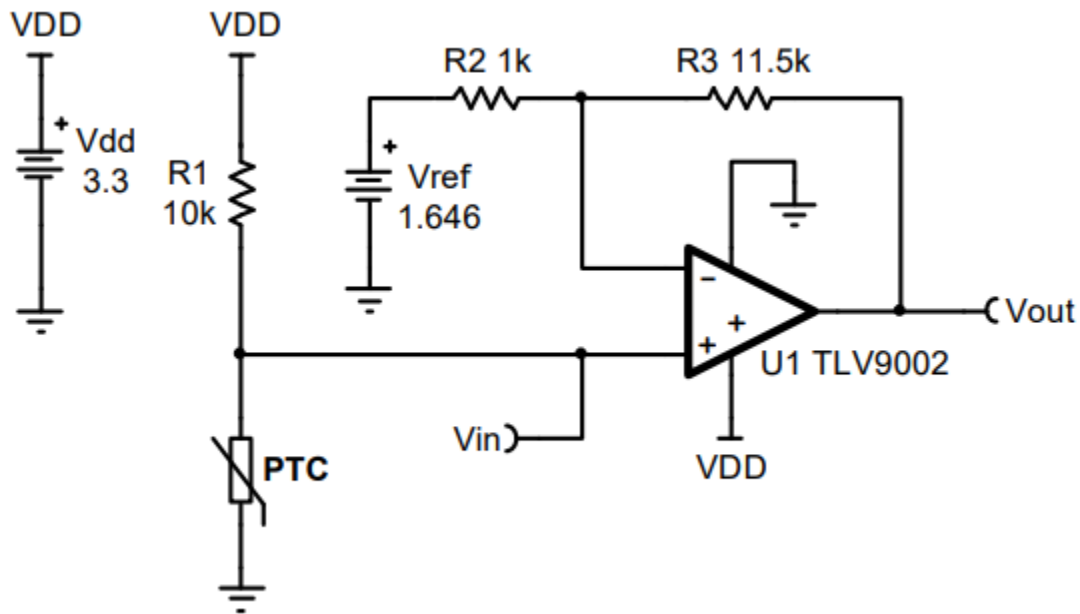

$$V_O = VDD \times \frac{R_{PTC}}{R1 + R_{PTC}} \times \frac{R3 + R2}{R2} - V_{ref} \times \frac{R3}{R2}$$

Design Steps

Temperature		Output		Supply		
T_{Min}	T_{max}	V_{outMin}	V_{outMax}	V_{dd}	V_{ee}	V_{ref}
0 °C	50 °C	50mV	3.25V	3.3V	0V	1.646V

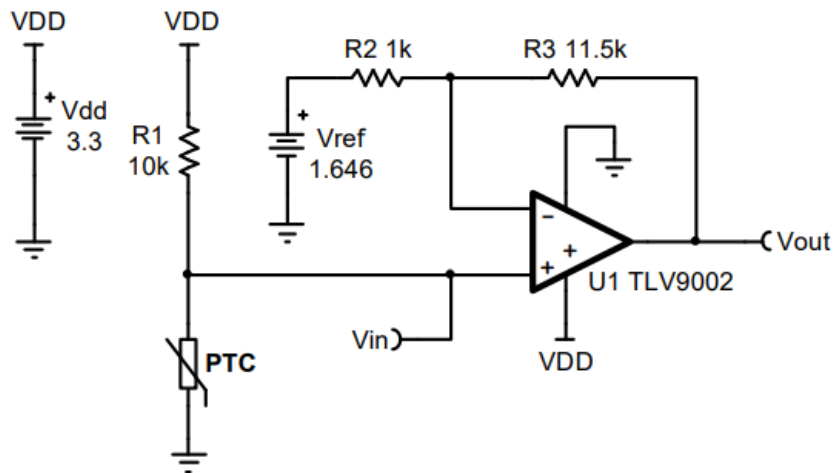

PTC Voltage
Divider, V_{in}


Inverting gain
times V_{ref}

$$V_O = VDD \times \frac{R_{PTC}}{R1 + R_{PTC}} \times \frac{R3 + R2}{R2} + Vref \times \left(-\frac{R3}{R2} \right)$$

Non-inverting
amplifier gain

Design Steps

Temperature		Output		Supply		
T_{Min}	T_{max}	V_{outMin}	V_{outMax}	V_{dd}	V_{ee}	V_{ref}
0 °C	50 °C	50mV	3.25V	3.3V	0V	1.646V

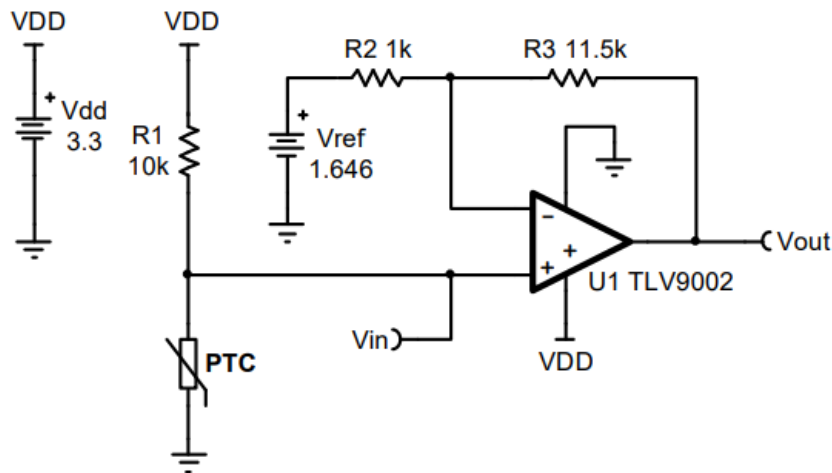

$$R_{PTC_max} = R_{PTC@50^{\circ}C} = 11.611 \text{ k}\Omega$$

$$R_{PTC_min} = R_{PTC@0^{\circ}C} = 8.525 \text{ k}\Omega$$

$$R1 = \sqrt{R_{PTC@50^{\circ}} + R_{PTC@0^{\circ}}}$$


$$R1 = \sqrt{11.611 \text{ k}\Omega + 8.525 \text{ k}\Omega} = 9.95 \text{ k}\Omega$$

$$V_{inMax} = V_{dd} \times \frac{R_{PTC_max}}{R_{PTC_max} + R1} = 1.773 \text{ V}$$

$$V_{inMin} = V_{dd} \times \frac{R_{PTC_min}}{R_{PTC_min} + R1} = 1.519 \text{ V}$$

Design Steps

Temperature		Output		Supply		
T_{Min}	T_{max}	V_{outMin}	V_{outMax}	V_{dd}	V_{ee}	V_{ref}
0 °C	50 °C	50mV	3.25V	3.3V	0V	1.646V

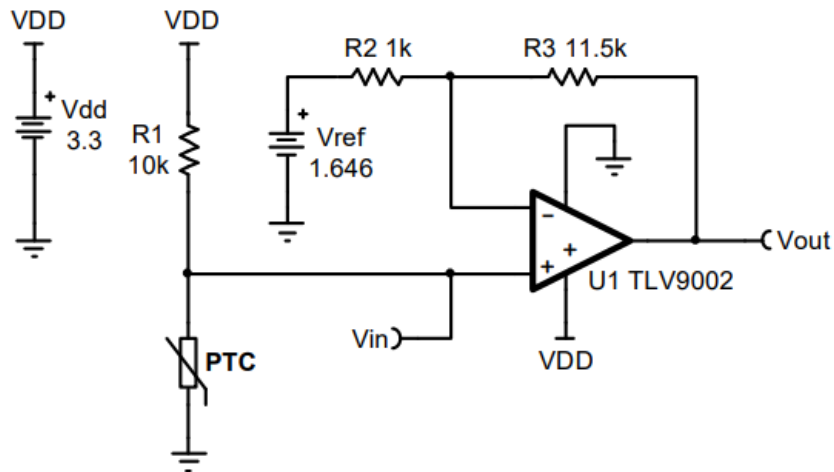

$$Gain_{ideal} = \frac{V_{outMax} - V_{outMin}}{V_{inMax} - V_{inMin}} = 12.598V/V$$

$$Gain = \frac{R2 + R3}{R2}$$


$$R2 = 1\text{ k}\Omega$$

$$R3 = R2 \times (Gain_{ideal} - 1) = 11.598\text{ k}\Omega$$

$$Gain_{actual} = \frac{R2 + R3}{R2} = 12.5\text{ V/V}$$

Design Steps

Temperature		Output		Supply		
T_{Min}	T_{max}	V_{outMin}	V_{outMax}	V_{dd}	V_{ee}	V_{ref}
0 °C	50 °C	50mV	3.25V	3.3V	0V	1.646V

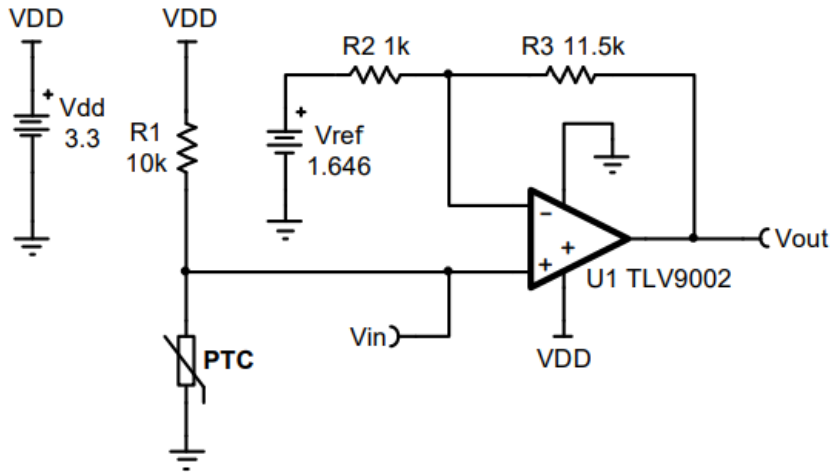

$$V_{o_swing} = (V_{inMax} - V_{inMin}) \times \text{Gain_actual}$$

$$V_{o_swing} = (1.773 \text{ V} - 1.519 \text{ V}) \times 12.5 \frac{\text{V}}{\text{V}} = 3.175 \text{ V}$$

$$V_{oMax} = V_{mid - supply} + \frac{V_{o_swing}}{2}$$



$$V_{oMax} = 1.65 \text{ V} + \frac{3.175 \text{ V}}{2} = 3.238 \text{ V}$$

$$V_{oMax} = V_{inMax} \times \text{Gain_actual} - V_{ref} \times \frac{R3}{R2}$$

$$V_{ref} = \frac{1.773 \text{ V} \times 12.5 \frac{\text{V}}{\text{V}} - 3.238 \text{ V}}{\frac{11.5 \text{ k}\Omega}{1 \text{ k}\Omega}} = 1.646 \text{ V}$$



DC Results

Temperature		Output		Supply		
T_{Min}	T_{max}	V_{outMin}	V_{outMax}	V_{dd}	V_{ee}	V_{ref}
0 °C	50 °C	50mV	3.25V	3.3V	0V	1.646V

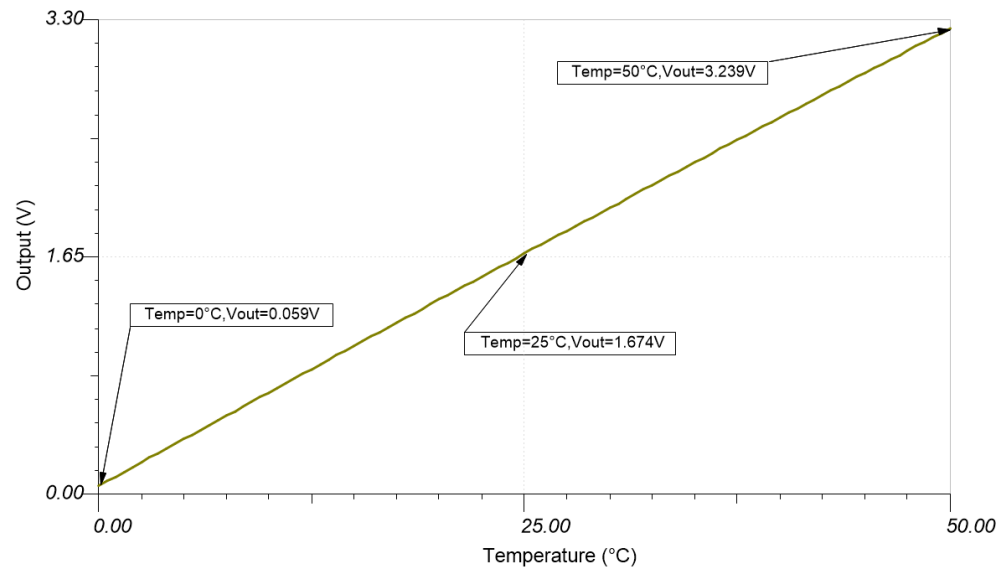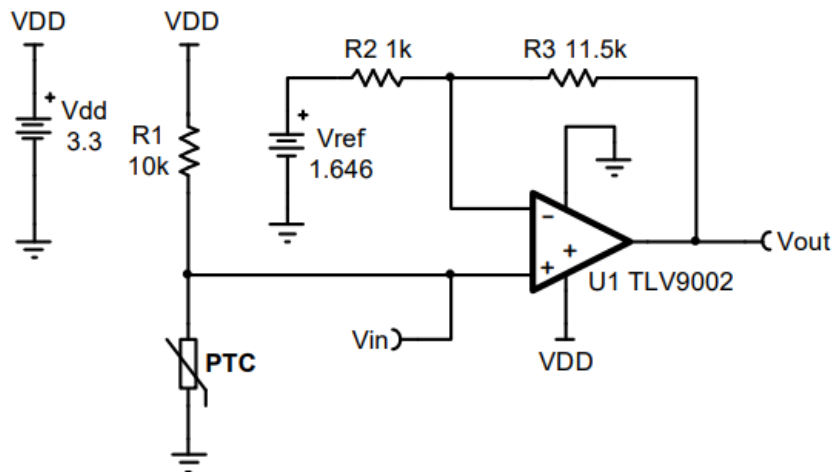


AC Results

Temperature		Output		Supply		
T_{Min}	T_{max}	V_{outMin}	V_{outMax}	V_{dd}	V_{ee}	V_{ref}
0 °C	50 °C	50mV	3.25V	3.3V	0V	1.646V

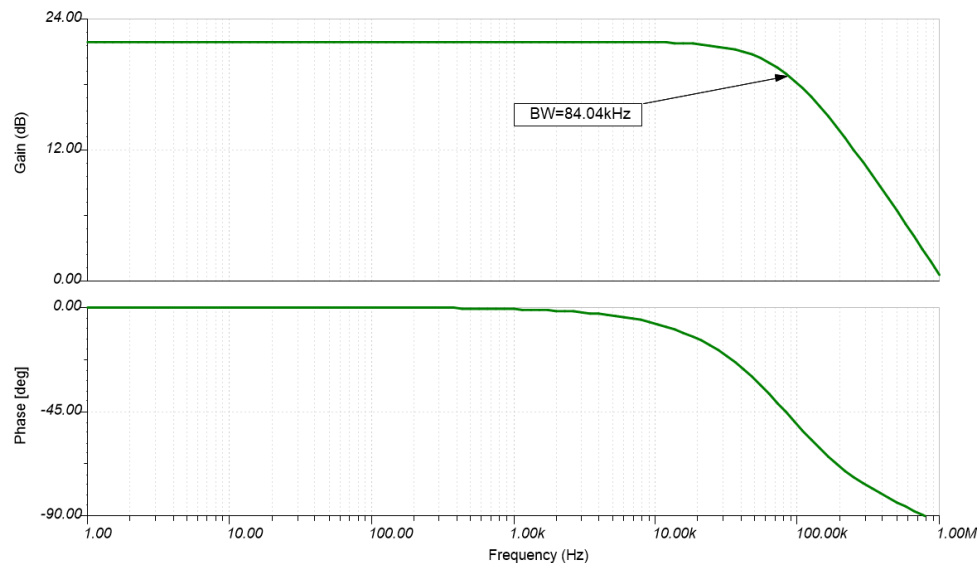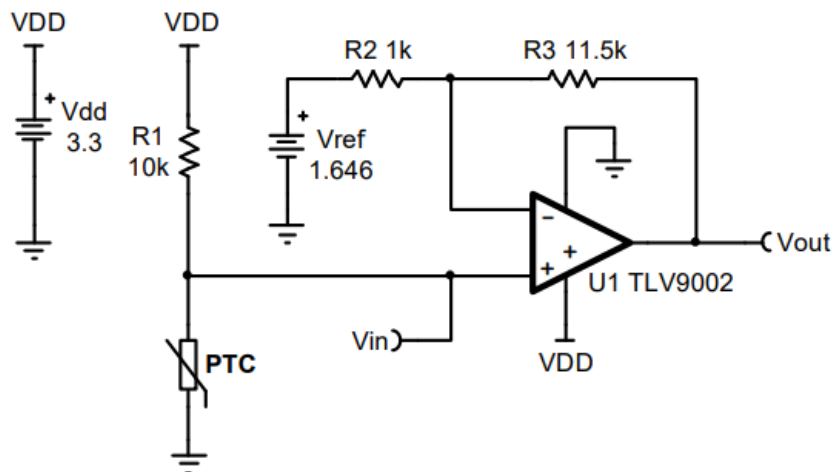

Design Notes

Temperature		Output		Supply		
T_{Min}	T_{max}	V_{outMin}	V_{outMax}	V_{dd}	V_{ee}	V_{ref}
0 °C	50 °C	50mV	3.25V	3.3V	0V	1.646V

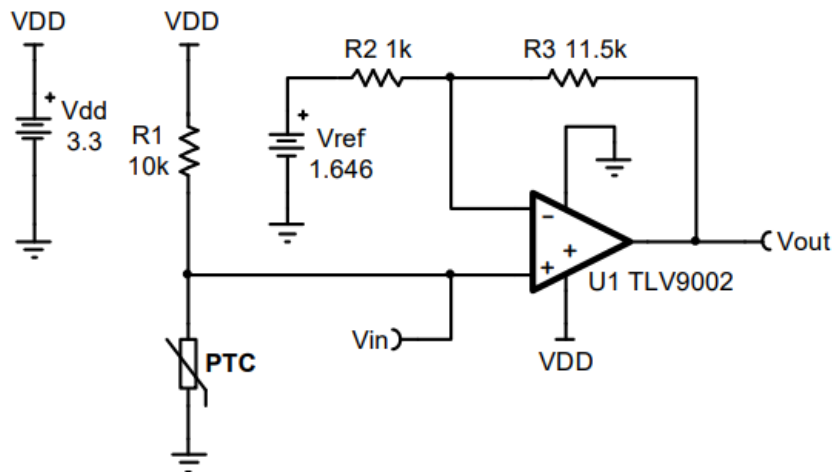

Design Notes:

1. For temperature sensing using a PTC thermistor, the resistor, R1, is chosen based on the temperature range and the PTC's value.
2. Operate within the linear output voltage swing (See A_{OL} specification) to minimize non-linearity errors.
3. The reference voltage, Vref, can be created using a DAC or voltage divider. If a voltage divider is used the equivalent resistance of the voltage divider will influence the gain of the circuit.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/signalbook

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2019 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)