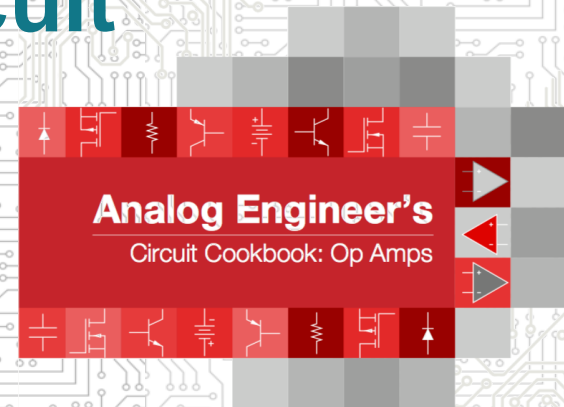


How to Design High-side current-sensing circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

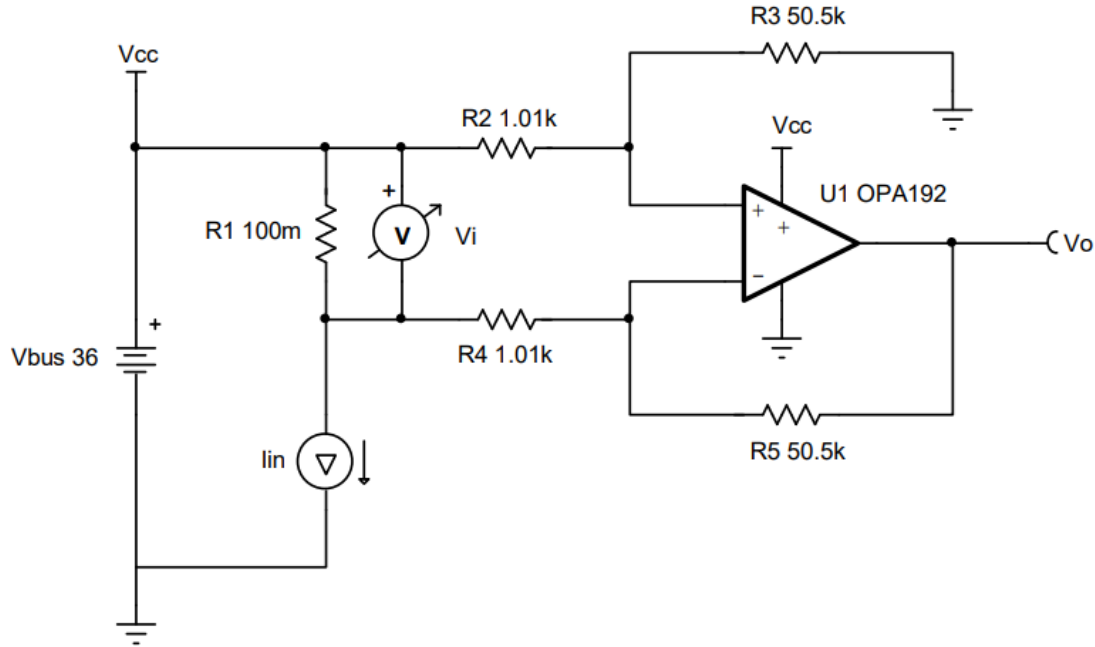

$$V_o = I_{in} \times R1 \times \frac{R5}{R4}$$

Design Goals

Input		Output		Supply	
I_{iMin}	I_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
50mA	1A	250mV	5V	36V	0V

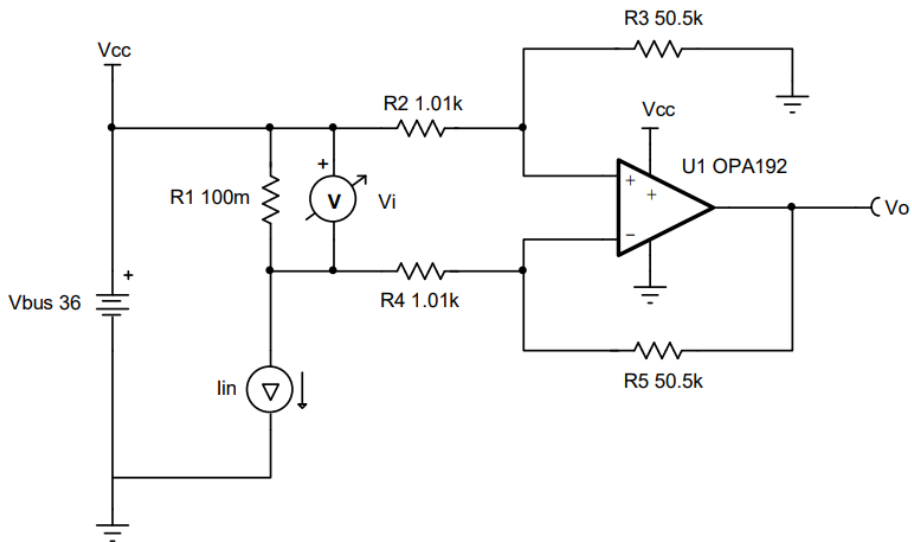


$$V_o = I_{in} \times R_1 \times \frac{R_5}{R_4}$$

Given $R_2 = R_4$ and $R_3 = R_5$

Design Steps


Input		Output		Supply	
I_{iMin}	I_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
50mA	1A	250mV	5V	36V	0V

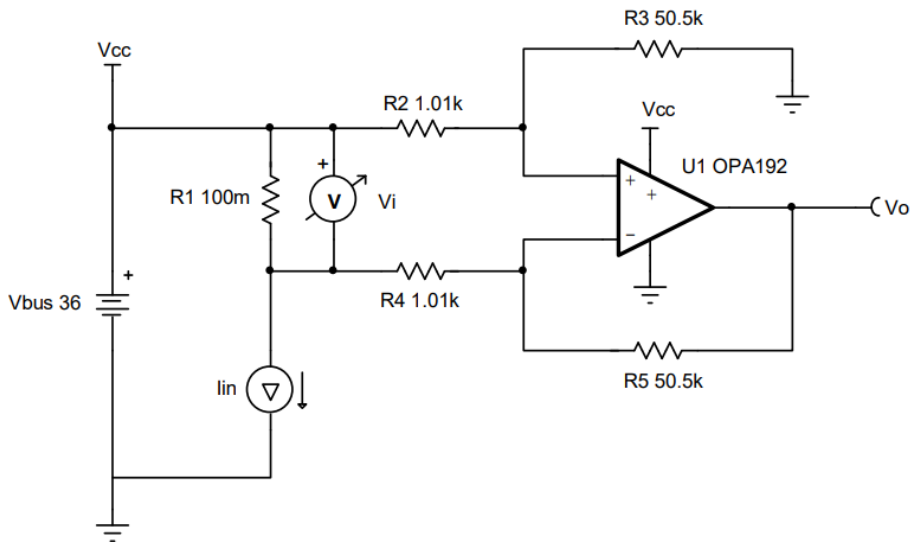

$$R1 = \frac{ViMax}{IiMax} = \frac{100mV}{1A} = 100m\Omega$$

Design Steps

Input		Output		Supply	
I_{iMin}	I_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
50mA	1A	250mV	5V	36V	0V

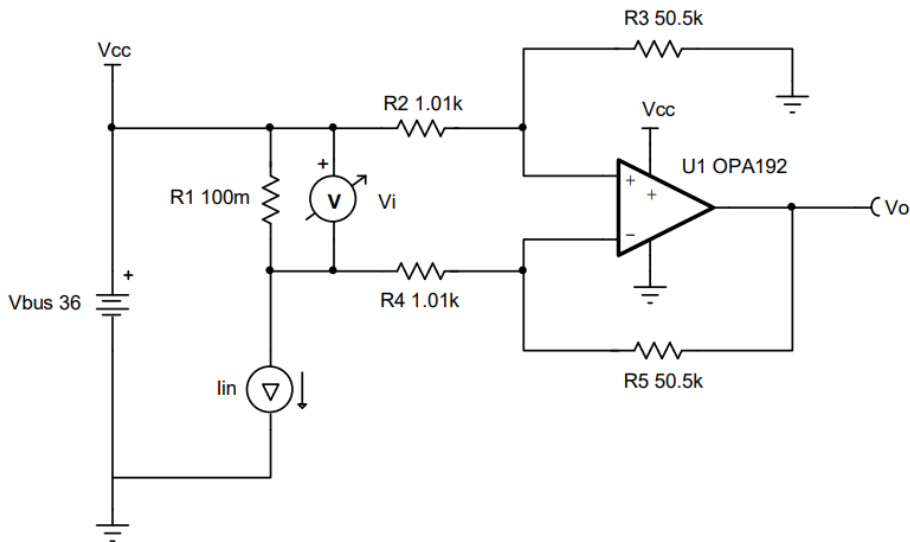

$$Gain = \frac{VoMax - VoMin}{(IiMax - IiMin) \times R1} = 50V/V$$


$$Gain = \frac{R5}{R4}$$

$$R2 = R4 = 1.01 \Omega$$

$$R3 = R5 = R2 \times Gain = 1.01 k\Omega \times 50 \frac{V}{V} = 50.5 k\Omega$$

Design Steps



Input		Output		Supply	
I_{iMin}	I_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
50mA	1A	250mV	5V	36V	0V

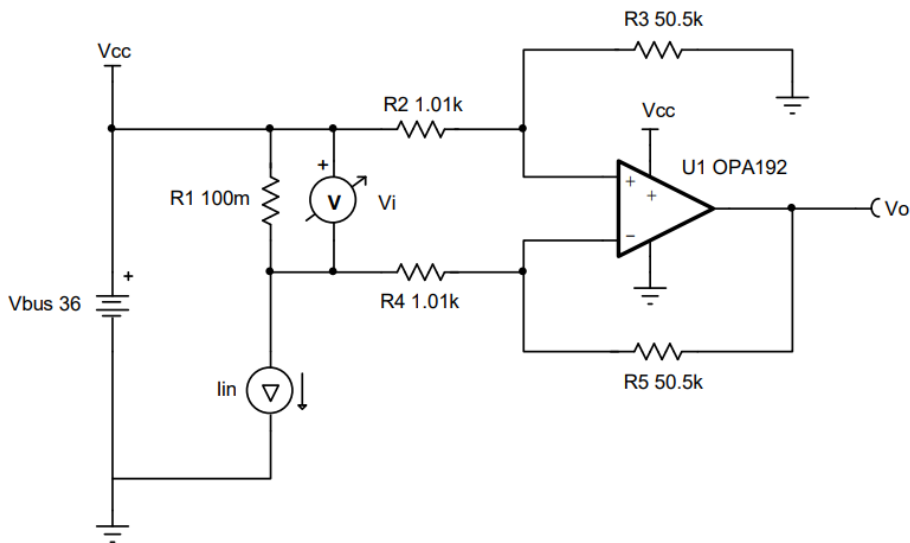

$$V_{cm} = V_{cc} \times \frac{R3}{R2 + R3} = 35.294 V$$



DC Results

Input		Output		Supply	
I_{iMin}	I_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
50mA	1A	250mV	5V	36V	0V

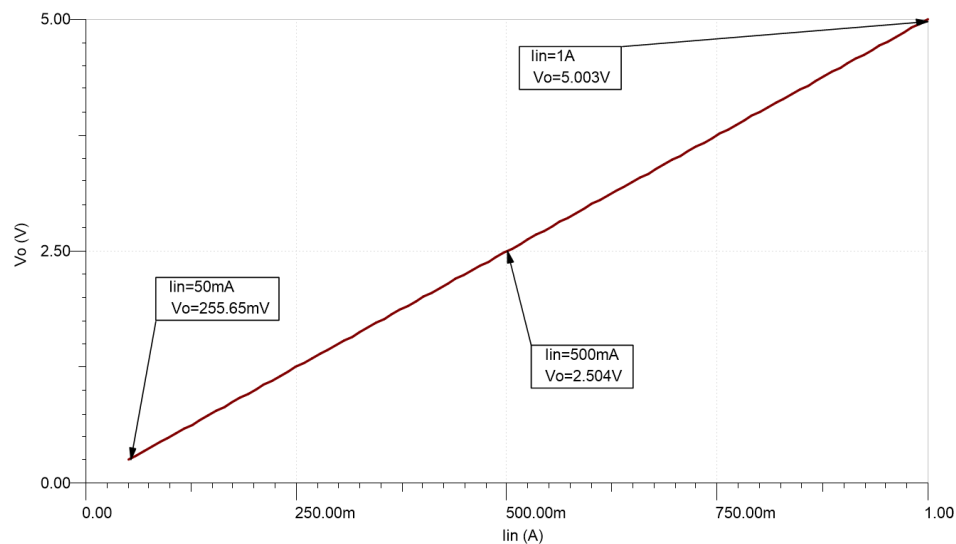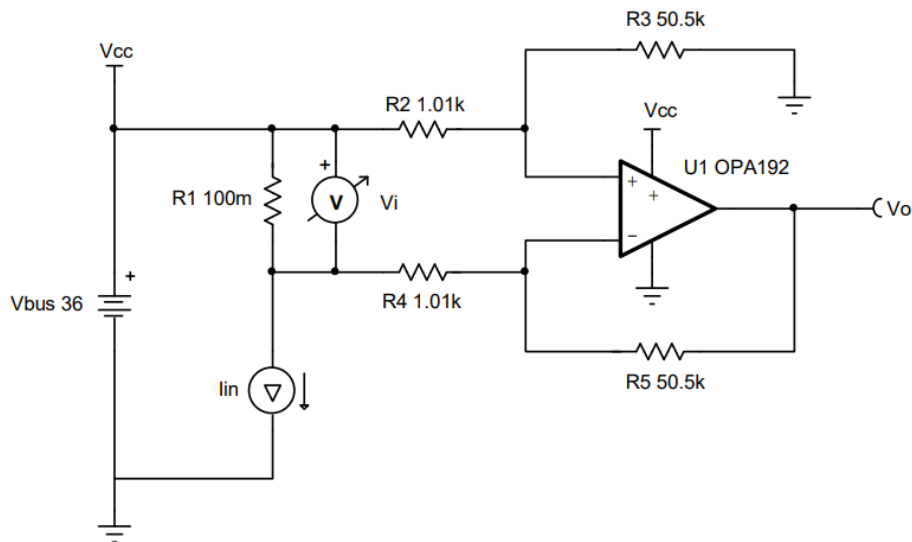


AC Results

Input		Output		Supply	
I_{iMin}	I_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
50mA	1A	250mV	5V	36V	0V

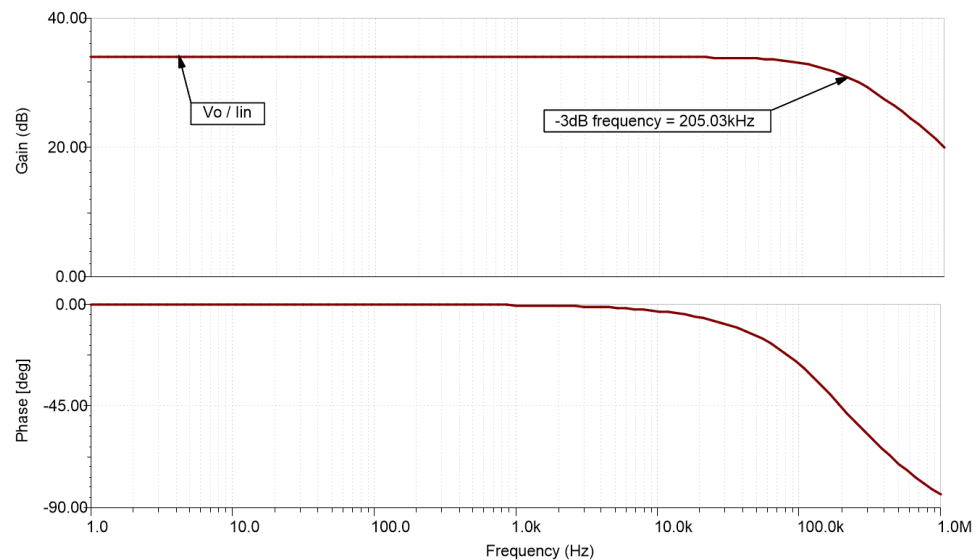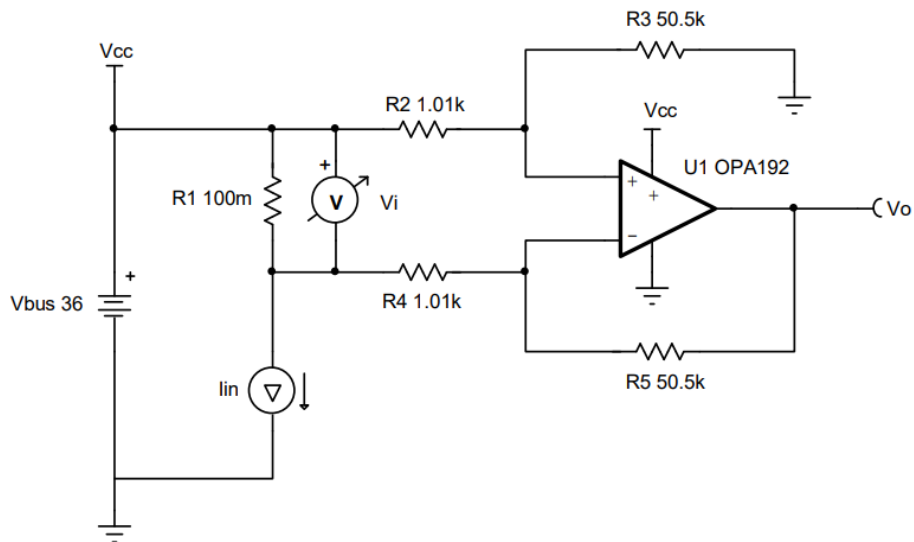

Design Notes

Input		Output		Supply	
I_{iMin}	I_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
50mA	1A	250mV	5V	36V	0V

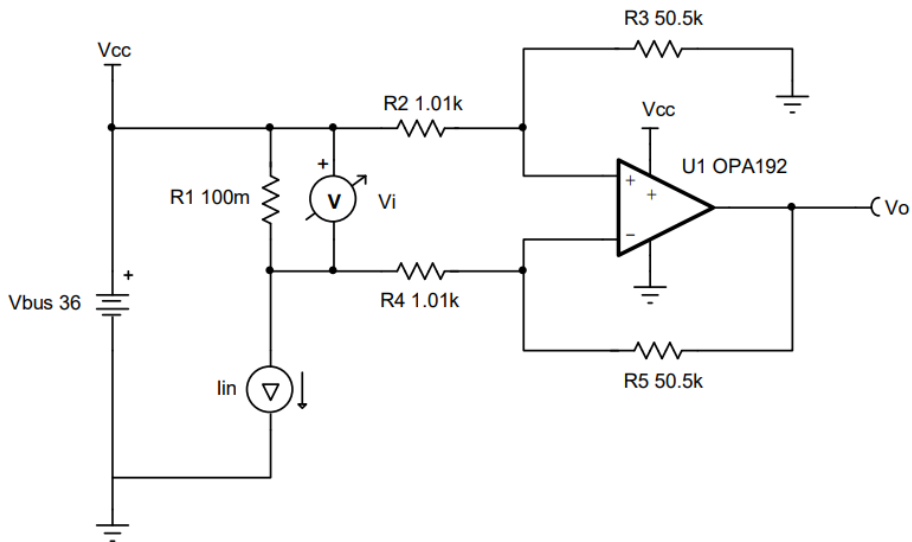

Design Notes:

1. For high-side current sensing, ensure the common-mode voltage is within the linear input operating region of the amplifier.
2. Increasing the shunt resistor increases power dissipation.
3. DC common mode rejection ration (CMRR) performance is dependent on the matching of the gain setting resistors, R2 – R5.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/signalbook

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2019 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)