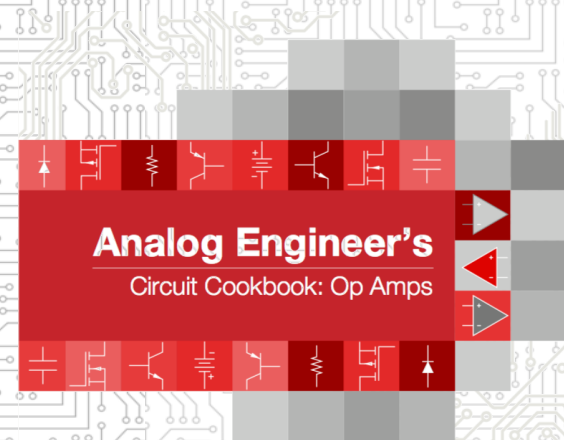


How to Design Full-wave rectifier circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks





Circuit Description

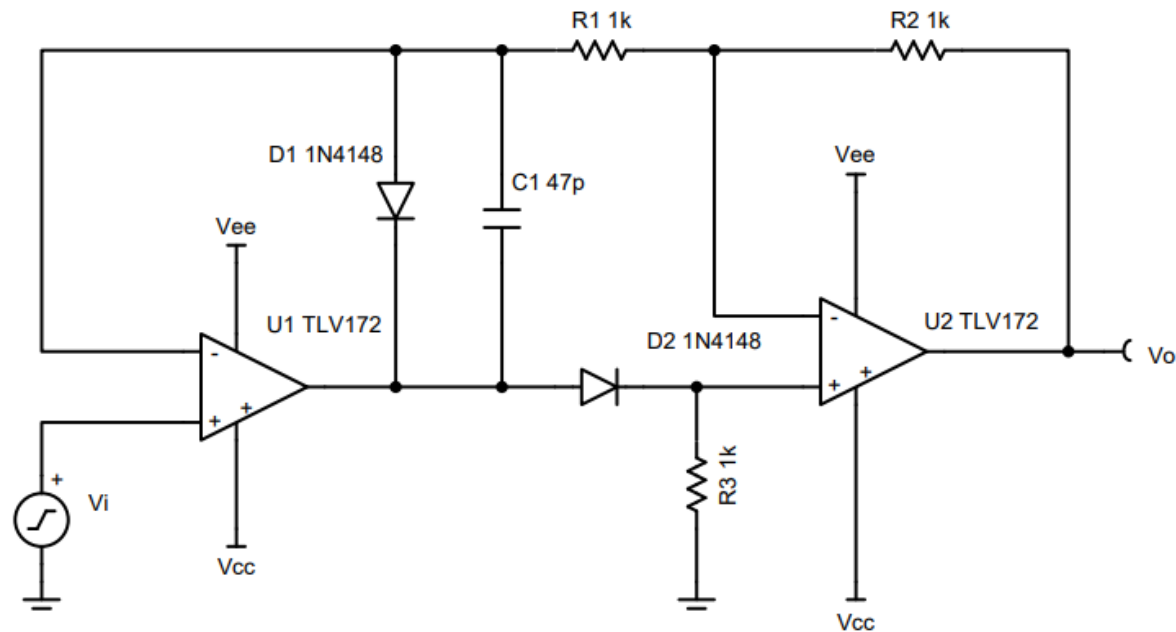

Design Goals


Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
$\pm 25 \text{ mV}$	$\pm 10 \text{ V}$	25 mV	10 V	15 V	-15 V	0 V

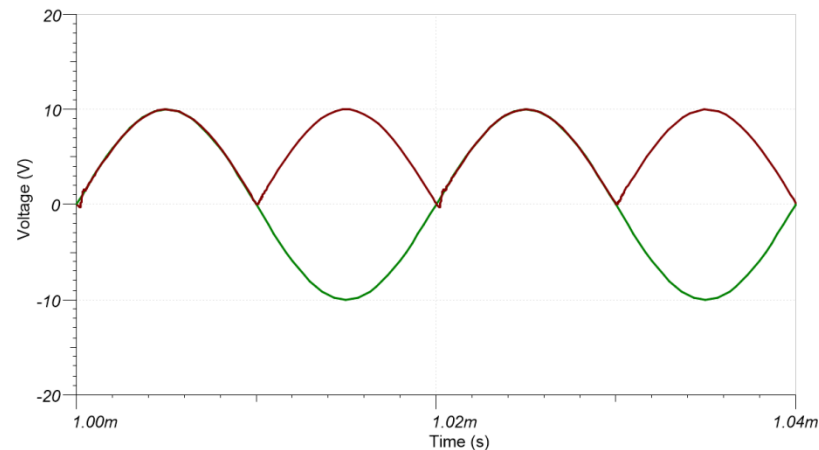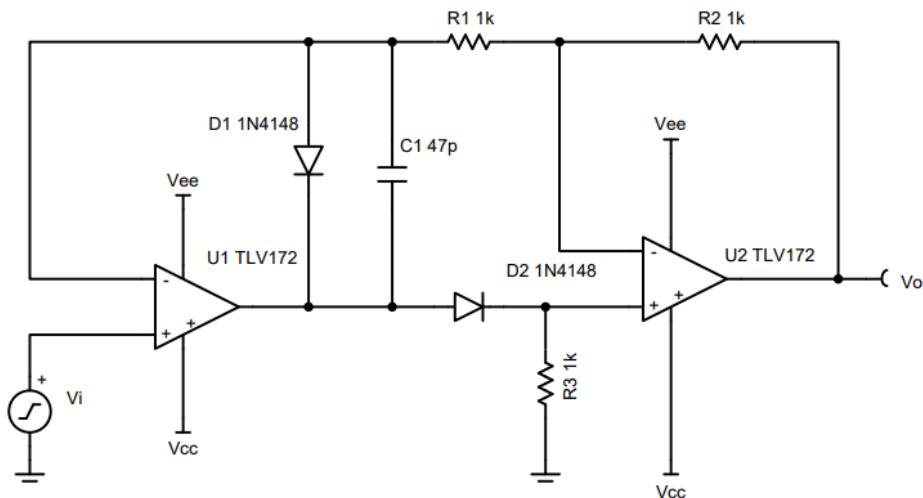

$$V_o = |V_i|$$

Design Steps


Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
$\pm 25 \text{ mV}$	$\pm 10 \text{ V}$	25 mV	10 V	15 V	-15 V	0 V

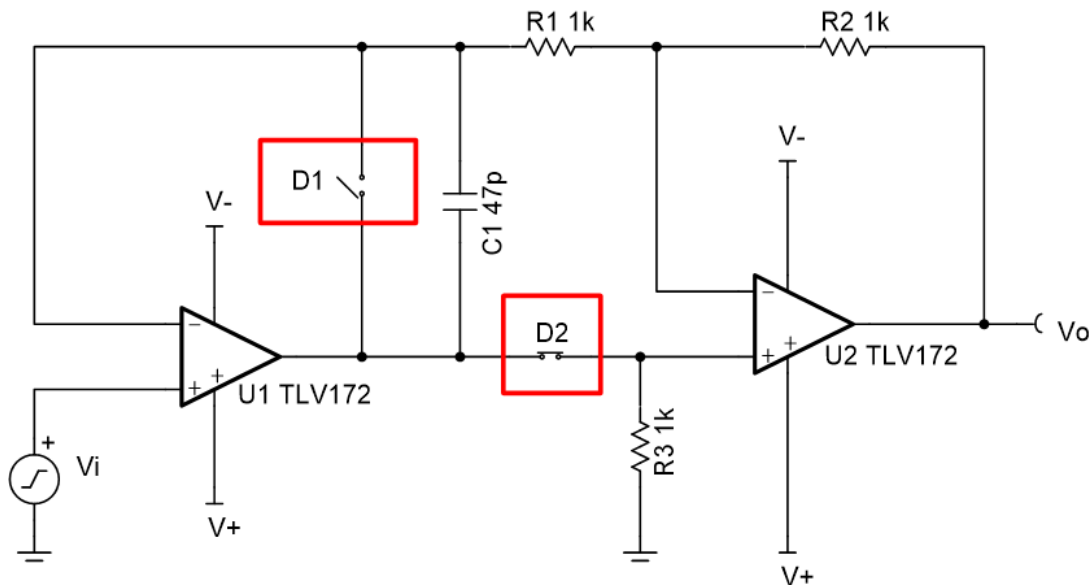

$$V_o = V_i$$

Design Steps

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
$\pm 25 \text{ mV}$	$\pm 10 \text{ V}$	25 mV	10 V	15 V	-15 V	0 V

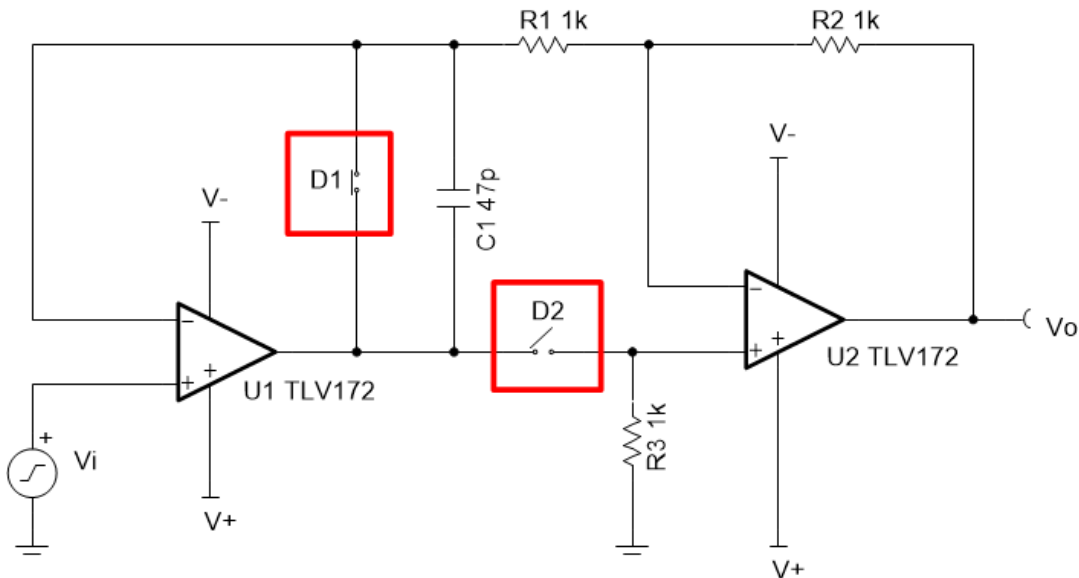



$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

$$R_1 = R_2 = 1 \text{ k}\Omega$$

$$R_3 = 1 \text{ k}\Omega$$



Transient Results

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
$\pm 25 \text{ mV}$	$\pm 10 \text{ V}$	25 mV	10 V	15 V	-15 V	0 V

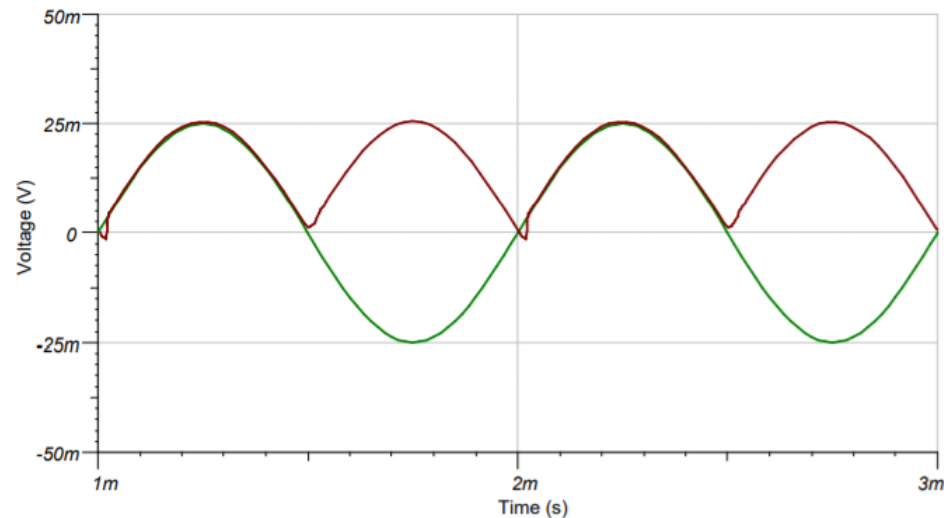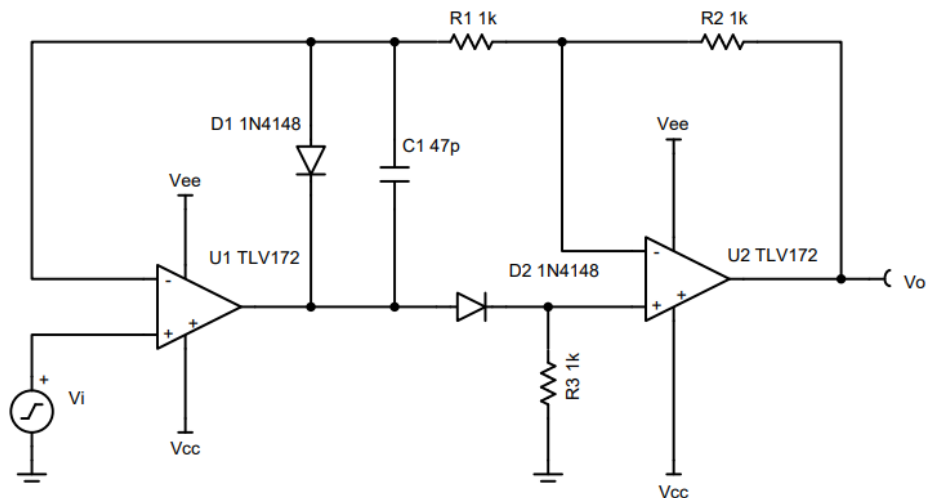


Transient Results

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
$\pm 25 \text{ mV}$	$\pm 10 \text{ V}$	25 mV	10 V	15 V	-15 V	0 V

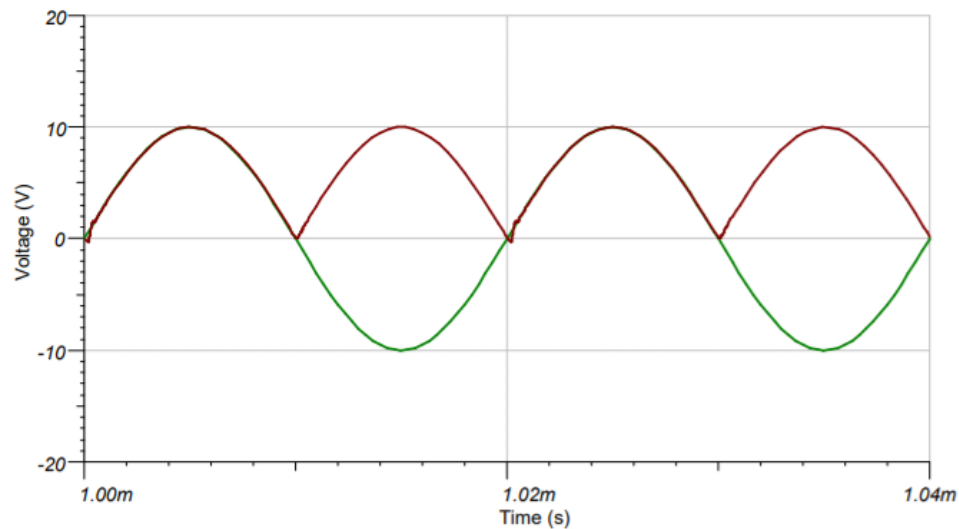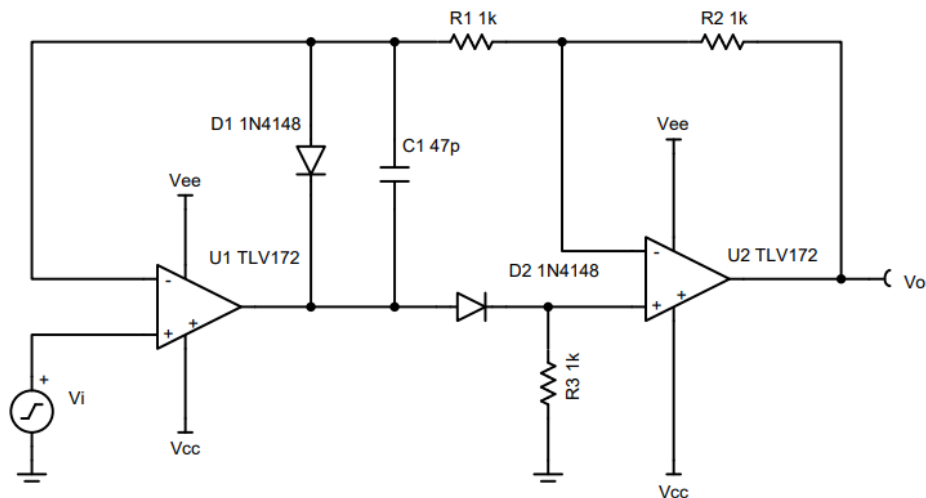

Design Notes

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
$\pm 25 \text{ mV}$	$\pm 10 \text{ V}$	25 mV	10 V	15 V	-15 V	0 V

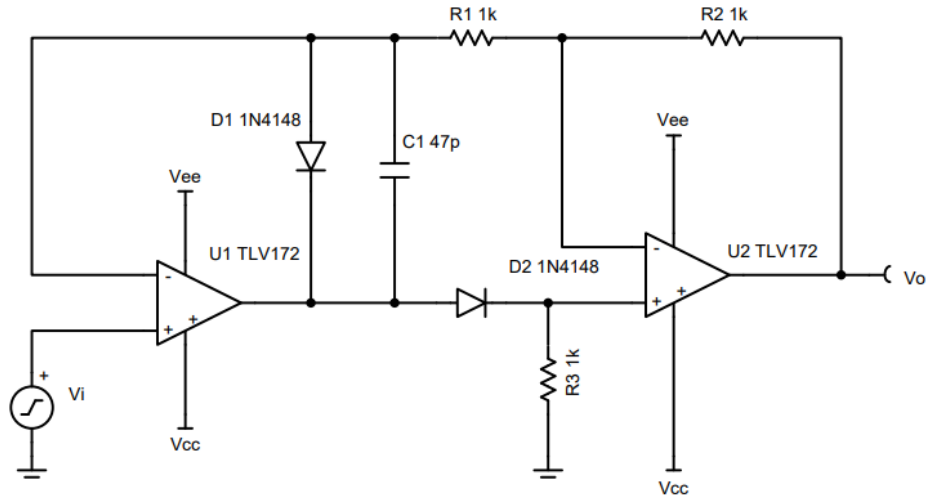

Design Notes:

1. For a full-wave rectifier circuit, be sure to use a fast switching diode for D1 and D2.
2. Select an op amp with sufficient bandwidth and slew rate.
3. Use precision resistors to reduce gain error.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/signalbook

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2019 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)