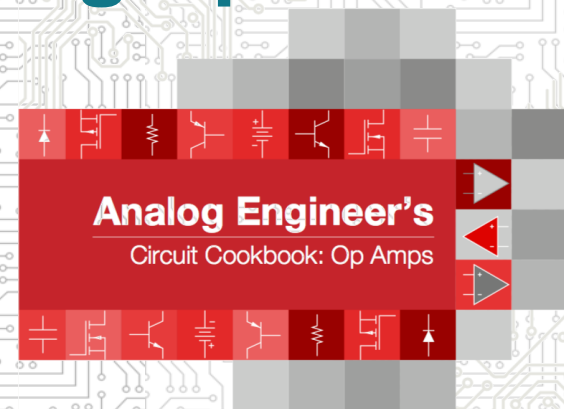


How to Design Single-supply, 2nd order, MFB high-pass filter circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

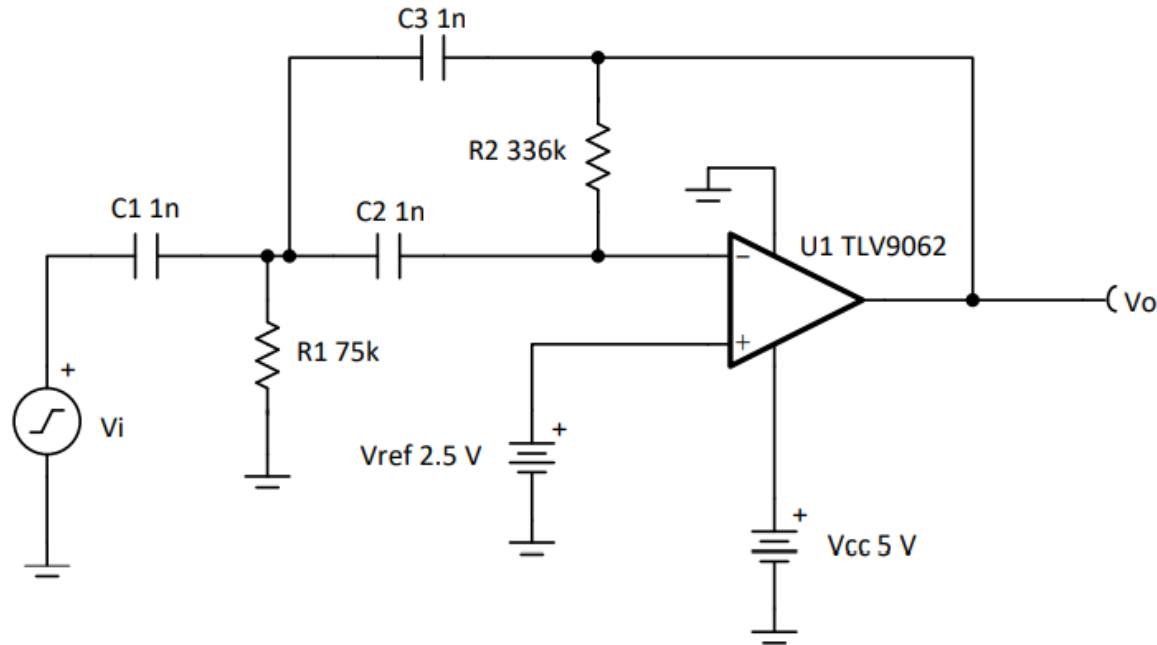

Design Steps

Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45 V	+2.45 V	0.05 V	4.95 V	5 V	0V
Gain		Cutoff Freq. (f_c)	Max Freq. (f_{max})	V_{ref}	
-1 V/V		1 kHz	10 kHz	2.5 V	

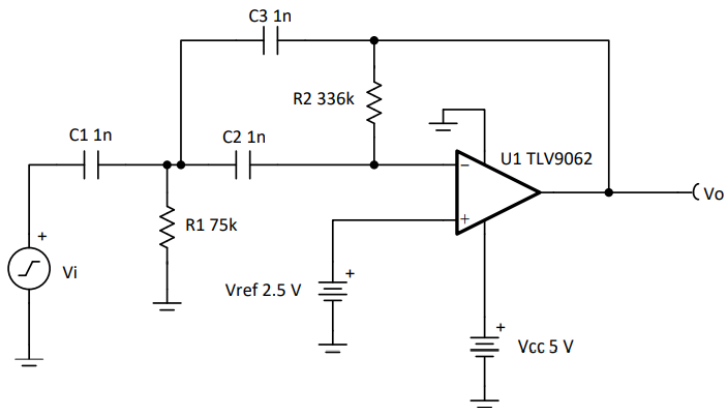


$$H(s) = \frac{-s^2 \frac{C_1}{C_3}}{s^2 + s \frac{C_1 + C_2 + C_3}{R_2 \times C_2 \times C_3} + \frac{1}{R_1 \times R_2 \times C_2 \times C_3}}$$

$$H(s) = \frac{-s^2 \frac{C_1}{C_3}}{s^2 + a_1 \times s + a_0}$$

$$\text{Here, } a_1 = \frac{C_1 + C_2 + C_3}{R_2 \times C_2 \times C_3}, \quad a_0 = \frac{1}{R_1 \times R_2 \times C_2 \times C_3}$$

Design Steps

Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45 V	+2.45 V	0.05 V	4.95 V	5 V	0V
Gain		Cutoff Freq. (f_c)	Max Freq. (f_{max})	V_{ref}	
-1 V/V		1 kHz	10 kHz	2.5 V	

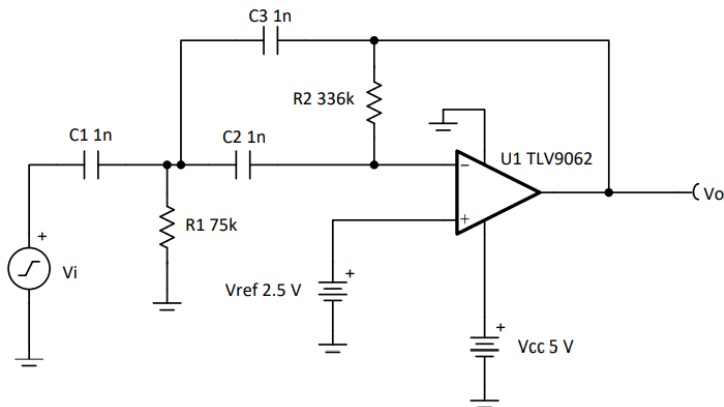

$$\omega_c = 1 \frac{\text{radian}}{\text{second}} \rightarrow a_0 = 1, a_1 = \sqrt{2}, \text{ let } C_{1n} = C_{2n} = C_{3n} = 1 \text{ F}$$


$$\text{Then } R_{1n} \times R_{2n} = 1 \text{ or } R_{2n} = \frac{1}{R_{1n}}, a_1 = \frac{3}{R_{2n}} = \sqrt{2}$$

$$\therefore R_{2n} = 2.1213, R_{1n} = \frac{1}{R_{2n}} = 0.4714$$

a_0 and a_1 are found on TI.com in Table 1 of Active Low-Pass Filter Design (SLOA049).

Design Steps

Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45 V	+2.45 V	0.05 V	4.95 V	5 V	0V
Gain		Cutoff Freq. (f_c)	Max Freq. (f_{max})	V_{ref}	
-1 V/V		1 kHz	10 kHz	2.5 V	

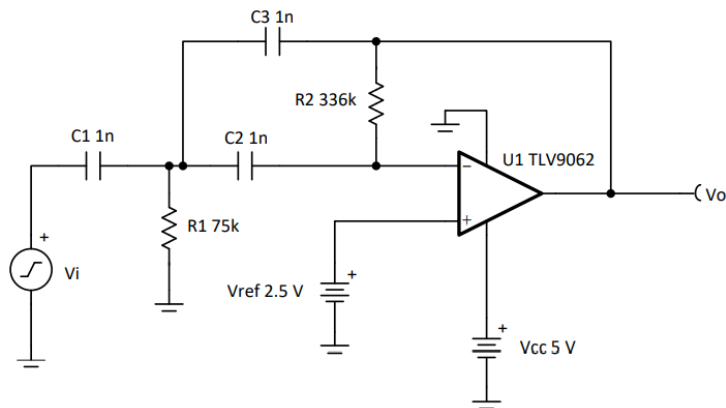

$$R_1 = R_{1n} \times m = (0.4714 \times m), \quad R_2 = R_{2n} \times m = (2.1213 \times m)$$


$$C_1 = \frac{C_{1n}}{m \times \omega_0} = \frac{1}{m \times \omega_0} \text{F}$$

$$C_2 = \frac{C_{2n}}{m \times \omega_0} = \frac{1}{m \times \omega_0} \text{F}$$

$$C_3 = \frac{C_{3n}}{m \times \omega_0} = \frac{1}{m \times \omega_0} \text{F}$$

Design Steps

Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45 V	+2.45 V	0.05 V	4.95 V	5 V	0V
Gain		Cutoff Freq. (f_c)	Max Freq. (f_{max})	V_{ref}	
-1 V/V		1 kHz	10 kHz	2.5 V	

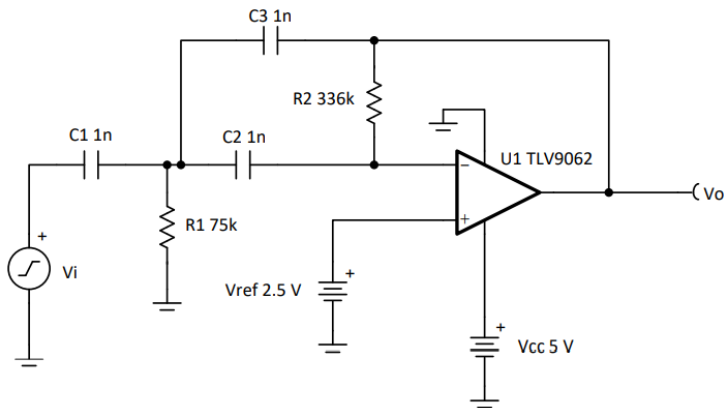

Set C_1 , C_2 , and C_3 to 1nF and calculate m .

Given $\omega_0 = 2 \times \pi \times f_c$, where $f_c = 1\text{kHz}$,

$$C_1 = C_2 = C_3 = \frac{1}{m \times \omega_0} \text{ F} = \frac{1}{m \times 2 \times \pi \times 1\text{kHz}}$$

So, $m = 159155$

Calculate R_1 and R_2 based on m .

$$R_1 = R_{1n} \times m = 0.4714 \times 159155 \approx 75\text{k}\Omega \text{ (Standard Value)}$$

$$R_2 = R_{2n} \times m = 2.1213 \times 159155 \approx 336\text{k}\Omega \text{ (Standard Value)}$$

Design Steps

Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45 V	+2.45 V	0.05 V	4.95 V	5 V	0V
Gain	Cutoff Freq. (f_c)		Max Freq. (f_{max})	V_{ref}	
-1 V/V	1 kHz		10 kHz	2.5 V	

Calculate minimum required GBW and SR for f_{max} . Be sure to use the noise gain for GBW calculations. Do not use the signal gain of $-1V/V$.



$$GBW = 100 \times \text{Noise Gain} \times f_{max} = 100 \times 2 \times 10\text{kHz} = 2\text{MHz}$$

$$SR = 2 \times \pi \times f_{max} \times V_{iMax} = 2 \times \pi \times 10\text{kHz} \times 2.45\text{V} = 0.154 \frac{\text{V}}{\mu\text{s}}$$

The TLV9062 device has GBW of 10MHz and SR of 6.5V/ μ s, so the requirements are met.



AC Results

Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45 V	+2.45 V	0.05 V	4.95 V	5 V	0V
Gain		Cutoff Freq. (f_c)	Max Freq. (f_{max})	V_{ref}	
-1 V/V		1 kHz	10 kHz	2.5 V	

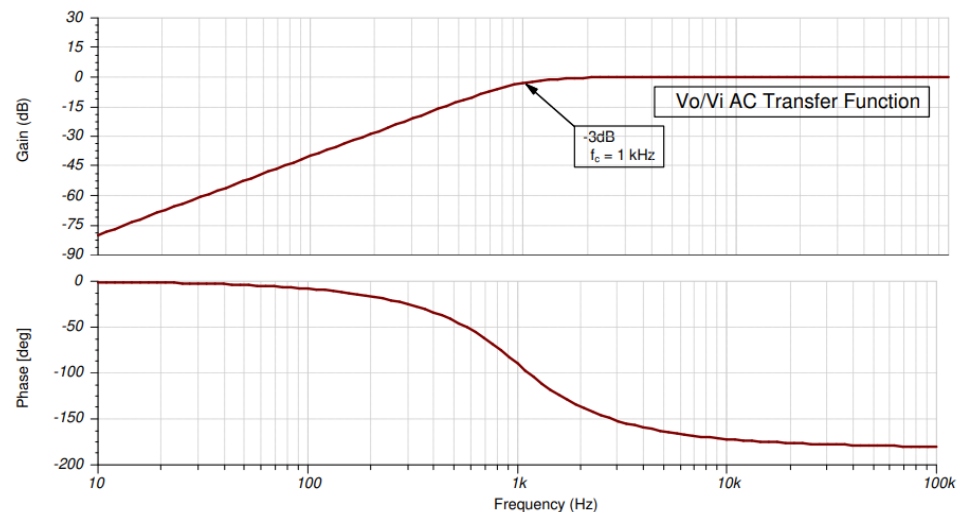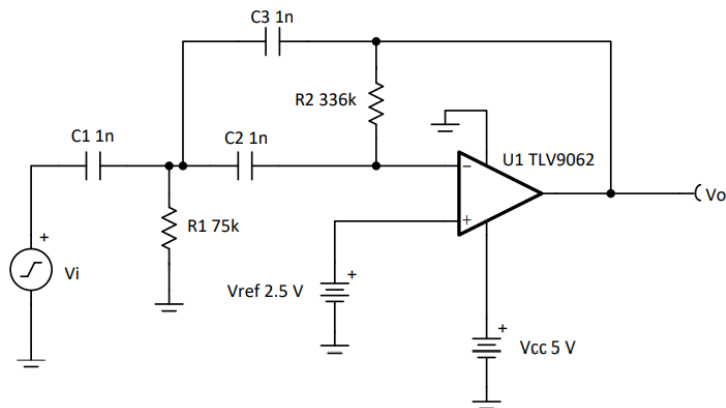

Transient Results



Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45 V	+2.45 V	0.05 V	4.95 V	5 V	0V
Gain		Cutoff Freq. (f_c)	Max Freq. (f_{max})	V_{ref}	
-1 V/V		1 kHz	10 kHz	2.5 V	

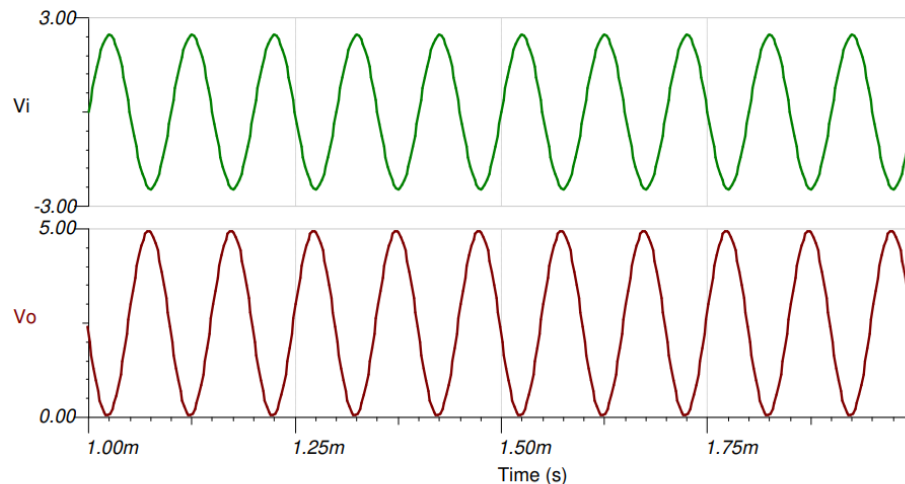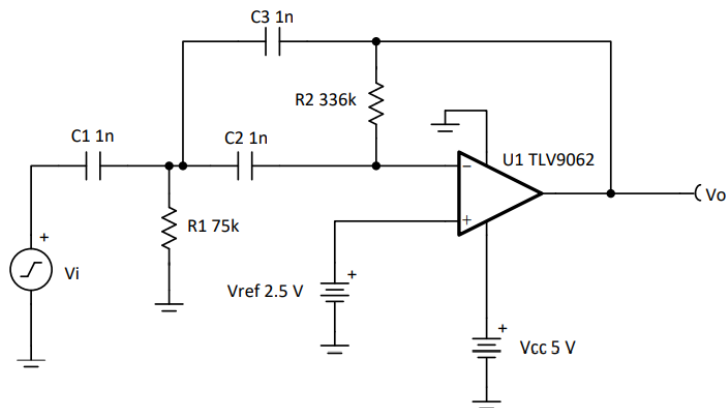

Filter Output in Response to a 5- V_{pp} , 10-kHz Input-Signal (Gain = -1V/V).

Transient Results


Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45 V	+2.45 V	0.05 V	4.95 V	5 V	0V
Gain		Cutoff Freq. (f_c)	Max Freq. (f_{max})	V_{ref}	
-1 V/V		1 kHz	10 kHz	2.5 V	

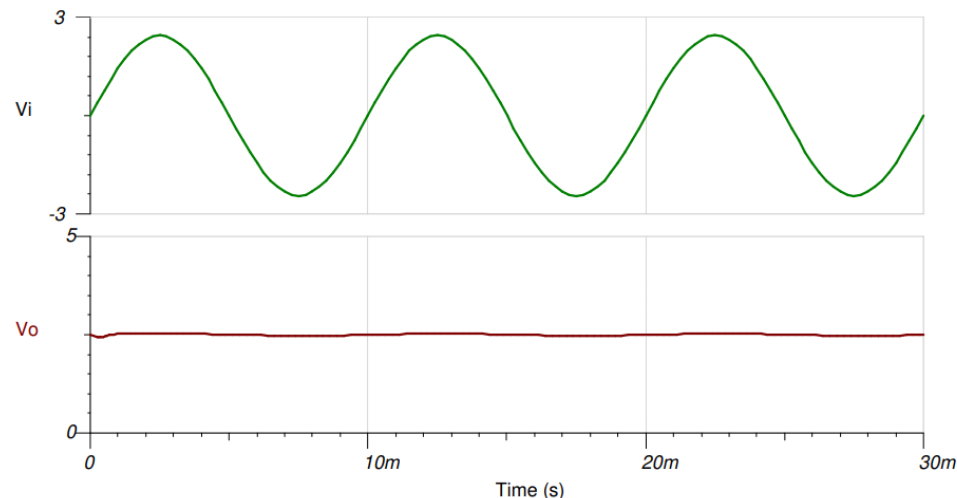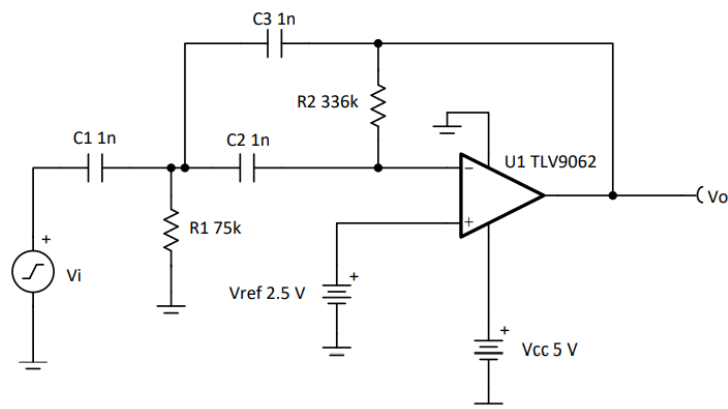

Filter Output in Response to a 5-V_{pp}, 100-Hz Input-Signal (Gain = -0.01V/V)

Design Notes

Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
-2.45 V	+2.45 V	0.05 V	4.95 V	5 V	0V
Gain		Cutoff Freq. (f_c)	Max Freq. (f_{max})	V_{ref}	
-1 V/V		1 kHz	10 kHz	2.5 V	

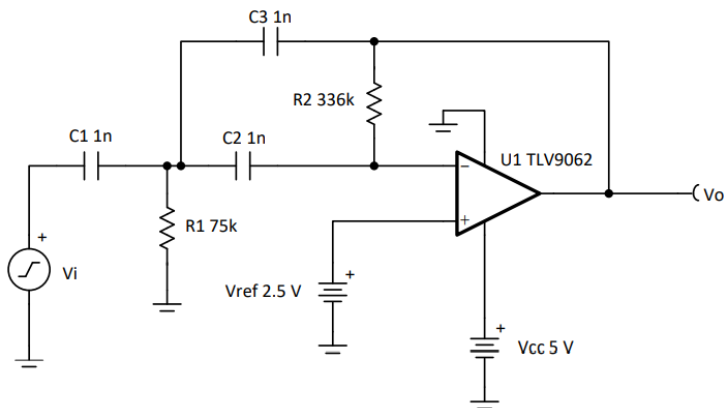

Design Notes:

1. Check common mode range and output swing, and reference to bias the amplifier in single supply designs.
2. Use precision, low-drift passives to minimize errors.
3. Select op amp with sufficient bandwidth and slew rate.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/thesignal

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2021 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)