

# Achieving High-Accuracy Output Below VREF With Space-Grade Multichannel Buck Converters

---



Andrew Fondaw

## ABSTRACT

A typical buck converter application allows regulation of the output voltage as low as the reference voltage of the converter ( $V_{REF}$ ). Occasionally a circuit requires a highly accurate power supply below a reference of the converter. A modified feedback network can be used in conjunction with an external voltage reference to allow a converter to regulate below the reference voltage, but this design degrades the accuracy of the supply by introducing additional error from the external voltage. Using a single voltage reference for multiple channels allows regulation below the reference voltage while maintaining a high level of accuracy. This application note introduces the concept and analysis of this method and provide an example circuit with results using the TPS7H4104EVM.

---

## Table of Contents

<b>1 Introduction</b> .....	<b>2</b>
<b>2 Concept of Operation</b> .....	<b>2</b>
<b>3 Maintaining Output Accuracy</b> .....	<b>4</b>
<b>4 Simulation Results</b> .....	<b>5</b>
4.1 $V_{EXT}$ Output Deviation Effects.....	7
<b>5 Test Results With TPS7H4104EVM</b> .....	<b>8</b>
<b>6 Summary</b> .....	<b>11</b>
<b>7 References</b> .....	<b>11</b>

## Trademarks

All trademarks are the property of their respective owners.

## 1 Introduction


Electronics such as FPGAs and ASICs used in modern spacecraft usually require voltages at or above current point-of-load buck converter reference voltages, typically 0.6V to 1.2V. As advances continue, lower voltage rails with high accuracy are sometimes required for power or bias in one of these systems. While generating a voltage lower than the reference has previously been accomplished; it is often a challenge to meet the accuracy requirements of sensitive rails while doing so, even if the converter meets such requirements in a typical implementation.

Typical methods wherein an external voltage source is used to extend the output range of a converter can be modified in some buck converters to avoid accuracy losses that normally degrade such a configuration. To be compatible with this method, converters must provide more than one independently configurable output channel, and each channel must share the same internal voltage reference.

This application note describes the theory of operation and requirements for a buck converter to produce a high-accuracy output below the reference voltage, how such an implementation prevents degradation of output accuracy, and provide examples of operation in simulation and hardware.

## 2 Concept of Operation

Methods to lower a converter's output voltage below the reference are explored in the application notes [SLVA216](#) and [SLUAA00](#). When these methods are implemented in a feedback divider of the regulator, an external voltage source ( $V_{EXT}$ ) is connected to the feedback node through a resistor ( $R_{EXT}$ ). By varying the voltage of  $V_{EXT}$  and the values of the feedback resistors, the voltage at the output of the regulator can be set. With set feedback resistor values, when  $V_{EXT}$  is raised,  $V_{OUT}$  drops, and when  $V_{EXT}$  is lowered,  $V_{OUT}$  rises.

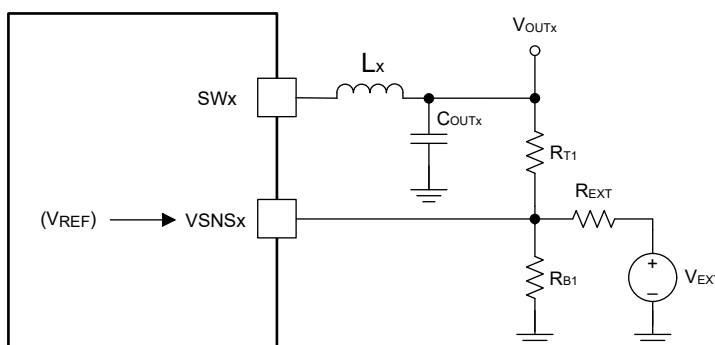

**Figure 2-1. Three Resistor Simplified Schematic**

When  $V_{EXT}$  is greater than  $V_{REF}$ , current from  $V_{EXT}$  flows to GND through  $R_{EXT}$  and  $R_{B1}$ . The additional current from  $V_{EXT}$  through  $R_{B1}$  causes a voltage rise at  $VSNS$ . The control loop of the regulator senses this voltage rise and decreases  $V_{OUT}$  in response, causing current flow through  $R_{B1}$  from  $R_{T1}$  to decrease. As the current through  $R_{B1}$  decreases, the voltage at  $VSNS$  decreases and returns to the reference voltage, but now with  $V_{OUT}$  at a lower level. If enough current is allowed to flow through  $R_{B1}$  such that the current through the top feedback resistor goes to zero,  $V_{OUT}$  is equal to the reference voltage of the regulator. If the current through  $R_{EXT}$  is increased beyond this point, then  $V_{OUT}$  drops below the reference voltage. During this condition, current no longer flows from  $V_{OUT}$  to GND through the feedback divider but rather flows from  $V_{EXT}$  to  $V_{OUT}$  and to GND through  $R_{T1}$  and  $R_{B1}$ .

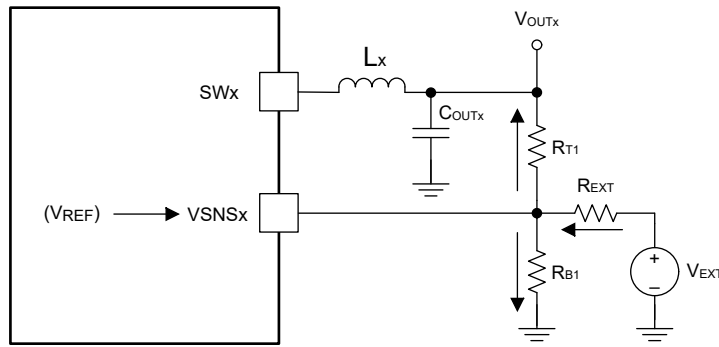


Figure 2-2. Simplified Schematic With Current Flow

In this operating mode  $R_{B1}$  is no longer required, as this mode no longer contributes to the feedback functionally and only serves as a source of error. The bottom resistor can then be removed and replaced with  $R_{EXT}$  which then becomes the new  $R_{B1}$  in the divider.

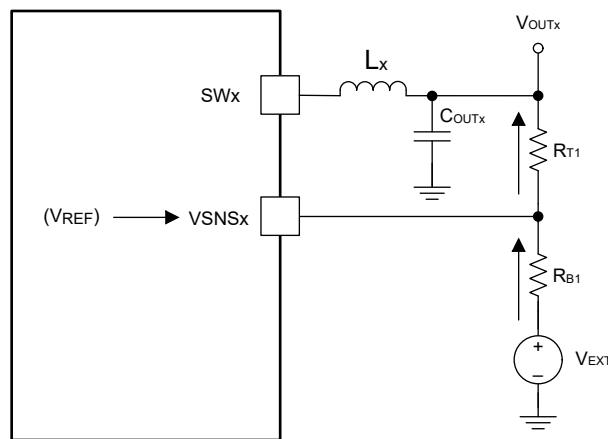


Figure 2-3. Two Resistor Simplified Schematic

In this new configuration, the feedback resistor divider is now formed between  $V_{EXT}$  and  $V_{OUT}$ . When the voltage of  $V_{EXT}$  is greater than  $V_{REF}$ , to maintain  $VSNS$  at the reference voltage,  $V_{OUT}$  must be lower than  $V_{REF}$  to accommodate the voltage drop across  $R_{T1}$ . Stable regulation is still maintained, as when  $V_{OUT}$  drops or rises, the voltage at  $VSNS$  still drops or rises proportionally, as with a standard implementation.  $V_{OUT}$  in this configuration is now determined by the values of  $R_{T1}$ ,  $R_{B1}$ ,  $V_{REF}$ , and  $V_{EXT}$ .


$$V_{OUT} = R_{T1} \times \left( \frac{V_{REF} - V_{EXT}}{R_{B1}} \right) + V_{REF} \quad (1)$$

The configuration shown in Figure 2-3 is already useful, as it allows for  $V_{OUT}$  to be regulated below the reference with only the addition of an external voltage source. However, the problem it introduces can be seen in the equation for  $V_{OUT}$ . Since the output voltage is dependent on both  $V_{REF}$  and  $V_{EXT}$ , errors in both terms must now be considered when calculating output accuracy of the regulator. Since  $V_{EXT}$  is not an accurate voltage source, in this configuration the accuracy of the regulator is permanently degraded by the accuracy of whatever external voltage source is used for  $V_{EXT}$ .

### 3 Maintaining Output Accuracy

Many multichannel regulators use independently generated voltage references to regulate each output. However, the TPS7H410x converters generate only a single internal voltage reference that is shared by all the output channels of the device. This design allows the accuracy degradation of the implementation shown in Section 2 to be bypassed, and device output accuracy to be maintained while regulating below  $V_{REF}$ .

Output accuracy degradation can be avoided by using a second output of the device to generate  $V_{EXT}$ . This configuration only allows  $V_{OUT}$  accuracy to be maintained when a single voltage reference is shared for both channels generating  $V_{OUT}$  and  $V_{EXT}$ . If the two channels do not use the same voltage reference, no accuracy benefit is gained over simply using an external voltage source. The shared voltage reference enables this possibility due to the way that changes in the reference voltage propagate to  $V_{OUT}$ . If  $V_{REF}$  is lowered,  $V_{EXT}$  is also lower, and therefore  $V_{OUT}$  rises. However, since both channels share a common reference,  $V_{REF}$  of  $V_{OUT}$  has also fallen, so  $V_{OUT}$  must fall to compensate, and the additive effects are canceled. The shift in  $V_{REF}$  is not canceled but simply reduced to the same magnitude as a single channel in a standard configuration.

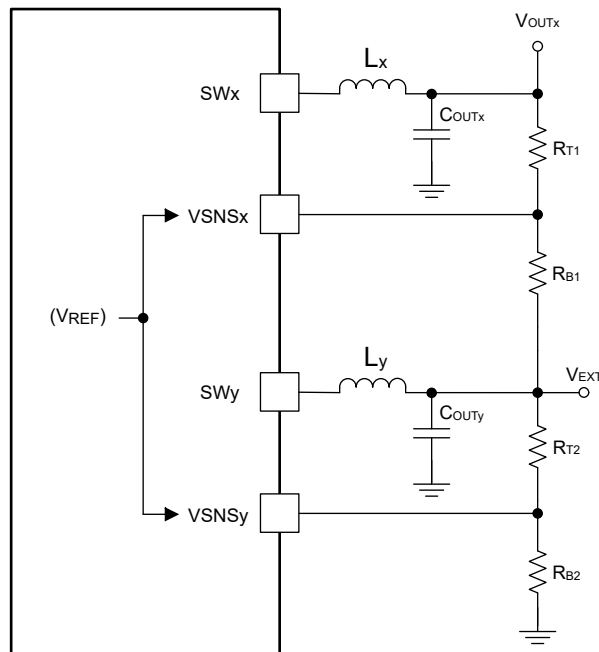

**Figure 3-1. Full System Simplified Schematic**

$$V_{OUT} = V_{REF} \times \left( 1 - \frac{R_{T1} \times R_{T2}}{R_{B1} \times R_{B2}} \right) \quad (2)$$

Equation 2 shows  $V_{OUT}$  when  $V_{EXT}$  is generated by another channel using the same voltage reference. All four resistors from the two feedback dividers are incorporated to make an equation for  $V_{OUT}$  using the full system. Since there is no longer a term from a second voltage reference, all  $V_{REF}$  terms can be grouped and factored into a single term. This gives an equation for  $V_{OUT}$  that is now only dependent on  $V_{REF}$  and a term consisting of feedback divider resistors for both channels. The form is the same as the equation for  $V_{OUT}$  in a standard configuration; the difference lies in the addition of  $R_{T2}$  and  $R_{B2}$  for the second feedback divider. The above simplified schematic shows how the feedback of both channels is connected.  $V_{OUT}$  is the desired output that is below  $V_{REF}$ .

This method does have drawbacks. To achieve the maximum accuracy of the low-voltage output, the channel that is used to generate  $V_{EXT}$  must not be used to power any external loads. While voltage ripple on  $V_{EXT}$  is not a concern, as any ripple must have a frequency at least a decade higher than the device control loop, load-steps from an external load on  $V_{EXT}$  cause perturbations at  $V_{OUT}$ . Therefore, the number of usable channels on the device is effectively reduced by one. Efficiency is reduced due to the need for a channel running that is not providing any power to the load. Sequencing requirements are also introduced, as  $V_{EXT}$

must start up concurrently or before  $V_{OUT}$  to avoid a temporarily higher than desired voltage at  $V_{OUT}$ . Since the TPS7H4104 provides integrated channel sequencing, this is simply resolved by making use of the internal channel sequencing, and selecting a channel for  $V_{EXT}$  that starts up before the channel selected for  $V_{OUT}$ .

### 4 Simulation Results


A simulation was configured and run using the [TPS7H4104-SEP SIMPLIS model](#) provided on ti.com. CH2 was used as  $V_{EXT}$  and CH3 as  $V_{OUT}$ . Channels 1 and 4 are unused in the simulation and are therefore disabled and not shown in [Figure 4-1](#). CH2 was not modified from the original configuration and is set to output 1.2V. CH3 was modified to output a voltage below  $V_{REF}$ , in this case 0.5V was selected. 10.02kΩ was selected for the top resistance of the  $V_{OUT}$  (CH3) feedback divider to match the default values on the TPS7H4104EVM. [Equation 3](#) calculates the bottom resistor value.

$$R_{B1} = R_{T1} \left( \frac{V_{EXT} - V_{REF}}{V_{REF} - V_{OUT}} \right) \tag{3}$$

Using the following inputs results in  $R_{B1} = 61.24k\Omega$ :


- $R_{T1} = 10.02k\Omega$
- $V_{EXT} = 1.207V$
- $V_{REF} = 0.59948V$
- $V_{OUT} = 0.5V$

61.9kΩ was selected for the resistor in the simulation as the closest E96 series value to the calculation result. A switching frequency of approximately 300kHz was also configured for this simulation to avoid violating the minimum on-time specification of the device in the data sheet.  $R_T$ , COMP and RSC for CH3 were also configured using the equations found in the TPS7H4104 data sheet.

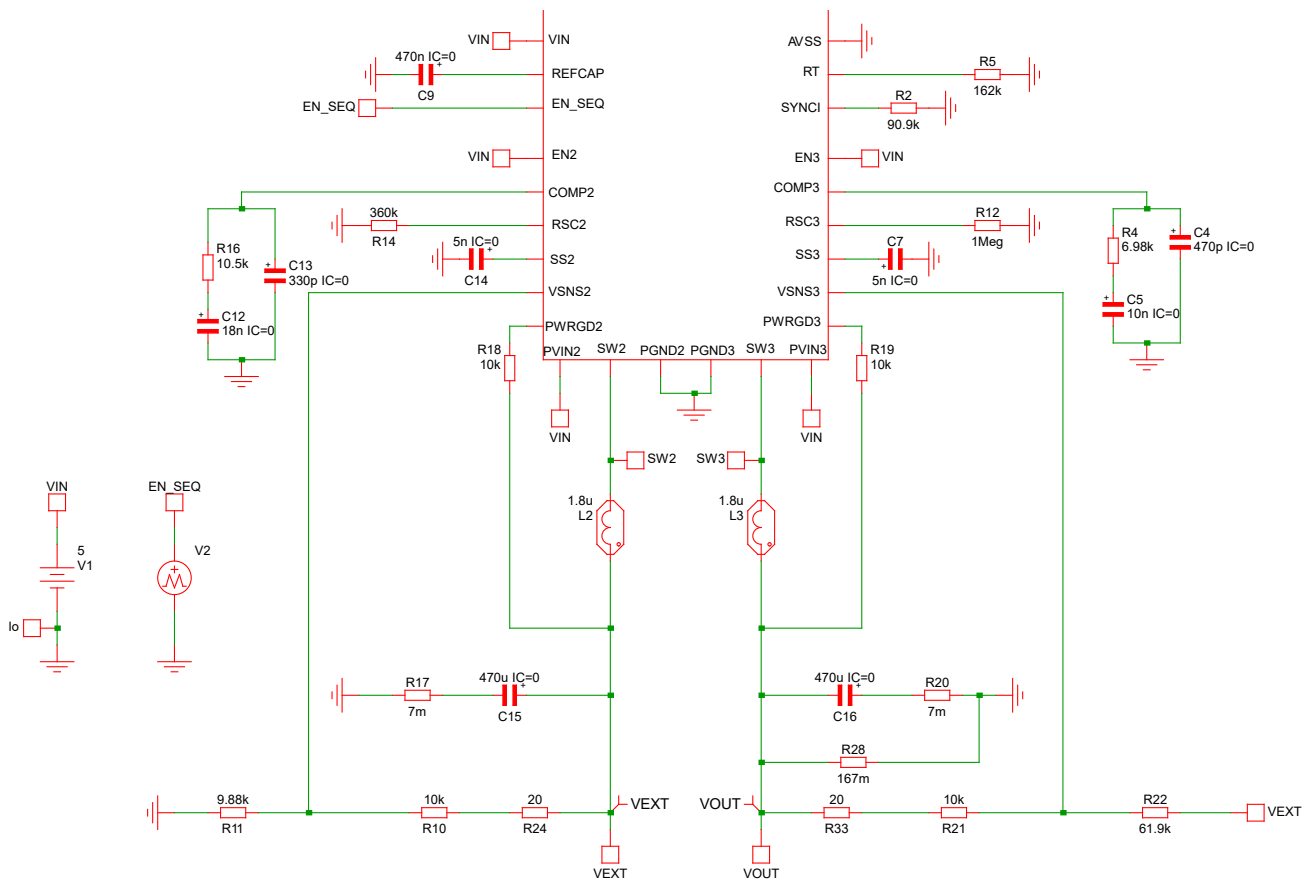

**Figure 4-1. Simulation Schematic**

Startup was simulated with the internal channel sequencing enabled. Since the internal sequencer of the TPS7H4104 brings up channels in numbered order, and CH2 was used for  $V_{REF}$  while CH3 was used for  $V_{OUT}$ , the sequencer enables  $V_{OUT}$  only after  $V_{EXT}$  has finished the soft startup sequence. The plot below shows  $V_{OUT}$  and  $V_{EXT}$  during startup and steady-state operation with a load of 3A applied to  $V_{OUT}$ . As expected,  $V_{OUT}$  regulates to 0.5V, which is 100mV below  $V_{REF}$  as shown in Figure 4-2.

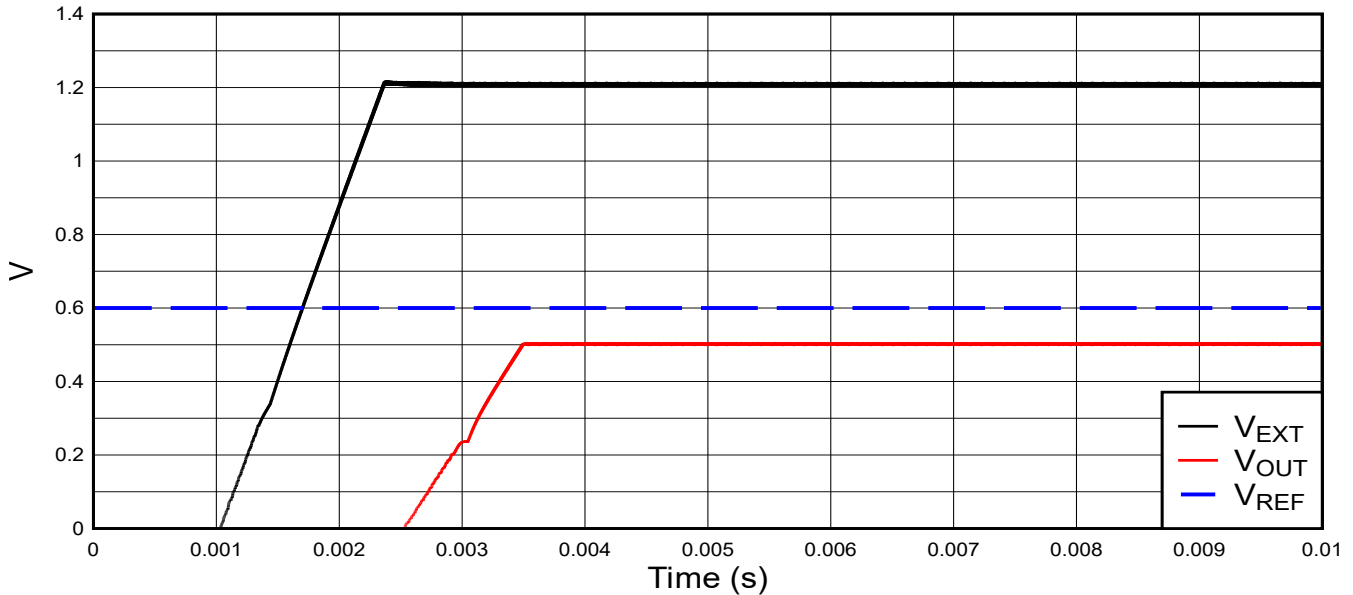

**Figure 4-2. Simulation Startup Results**

Using a simulation allows the ability to vary the internal voltage reference between simulation runs.  $V_{REF}$  was set to the Min, Typ, and Max values shown in the [TPS7H4104 data sheet](#), and the RMS value of  $V_{OUT}$  from 6ms to 10ms of the simulation was recorded. The RMS values for  $V_{OUT}$  along with the corresponding  $V_{REF}$  values are shown in [Table 4-1](#). The percentage shift from the typical value is also calculated for  $V_{REF}$  and for  $V_{OUT}$ .

**Table 4-1.  $V_{REF}$  To  $V_{OUT}$  Error Propagation**

Value	$V_{REF}$ (mV)	$V_{REF}$ Change (%)	$V_{OUT}$ (mV)	$V_{OUT}$ Change (%)
Typ	599.48	-	501.04	-
Min	591.50	-1.33%	494.38	-1.33%
Max	603.50	0.67%	504.40	0.67%

[Table 4-1](#) shows that  $V_{REF}$  changes are propagated to  $V_{OUT}$  without adding extra error. So, a 1% change in  $V_{REF}$  results in a 1% change in  $V_{OUT}$ . This behavior is consistent with the equation for  $V_{OUT}$  that was shown in [Section 3](#), as there is only a single  $V_{REF}$  term to contribute error to  $V_{OUT}$ . This is the same error propagation from  $V_{REF}$  that is seen in a single-channel setup regulating at or above  $V_{REF}$ , so the goal of creating a channel that regulates below  $V_{REF}$  while maintaining the same accuracy has been achieved.

### 4.1 V<sub>EXT</sub> Output Deviation Effects

During operation, it is possible for V<sub>EXT</sub> to deviate from the nominal DC value due to external factors such as line transients, load transients (if V<sub>EXT</sub> is loaded), and single-event transients caused by radiation. The SEE report for the TPS7H4104-SEP, [Single-Event Effects \(SEE\) Radiation Report of the TPS7H4104-SEP](#) shows and discusses the results of testing the TPS7H4104-SEP under a heavy-ion beam. While no SET events 3% or greater in magnitude were observed, a theoretical 3% transient can be induced on V<sub>EXT</sub> in simulation to observe the effects on V<sub>OUT</sub> with different nominal levels of V<sub>EXT</sub>.

In the simulation, a -3% transient was injected directly onto the V<sub>EXT</sub> rail with rise and fall times of 10µs. Three different nominal V<sub>EXT</sub> levels were tested, and transient magnitude was adjusted for each V<sub>EXT</sub> condition to -3% of nominal. Figure 4-3 shows the results for all three V<sub>EXT</sub> levels displayed on a single plot.

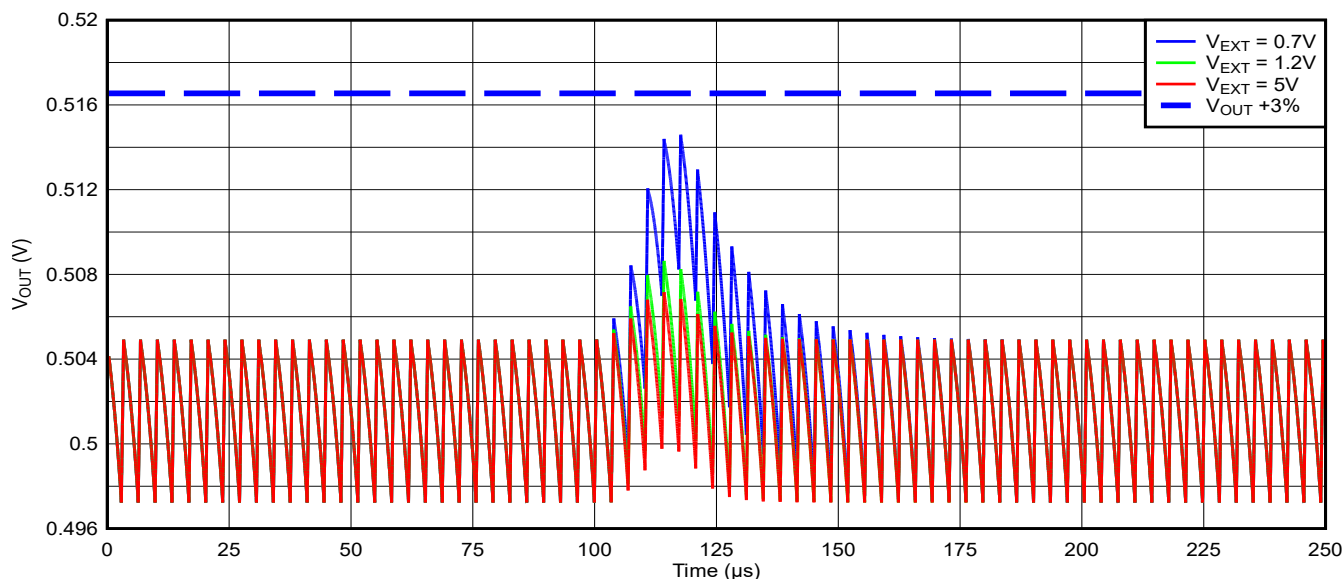


Figure 4-3. Simulation Result of V<sub>EXT</sub> Transient on V<sub>OUT</sub>


The plot above shows that for larger values of V<sub>EXT</sub>, the same percentage deviation from the nominal voltage will produce a smaller disturbance on V<sub>OUT</sub>. The cause of this unintuitive relationship is the voltage drop across R<sub>B1</sub>, and the V<sub>REF</sub> voltage. The current flowing through R<sub>B1</sub> is not determined by the total potential between GND and V<sub>EXT</sub>, but rather between V<sub>EXT</sub> and V<sub>REF</sub>. Since the magnitude of the upset on V<sub>EXT</sub> was determined by the V<sub>EXT</sub> to GND voltage, after V<sub>REF</sub> is subtracted from V<sub>EXT</sub>, smaller values of V<sub>EXT</sub> will end up with larger percentage upsets because V<sub>REF</sub> is a larger portion of the value.

In addition, a modified TPS7H4104EVM with V<sub>EXT</sub> and a low-voltage output channel in a similar configuration as described in section 3 and simulated in section 4 was exposed to a heavy ion beam with an LET of 75MeV. No SET events with a magnitude greater than 2.5% were observed on V<sub>OUT</sub>.

## 5 Test Results With TPS7H4104EVM

To verify this configuration outside of simulation, a TPS7H4104EVM evaluation module was modified to output 0.5V on CH3. Similarly to the previous simulation, the 1.2V output generated by CH2 was used as  $V_{EXT}$  for the CH3 feedback divider. To implement this configuration, four modifications are required to the EVM which are circled in red in [Figure 5-1](#).


- R22 was replaced to set the device switching frequency to approximately 300kHz.
- R17 was depopulated to remove the connection to GND of the feedback divider.
- R33 was populated to be used as  $R_{B1}$
- $V_{EXT}$  was connected to  $R_{B1}$ .

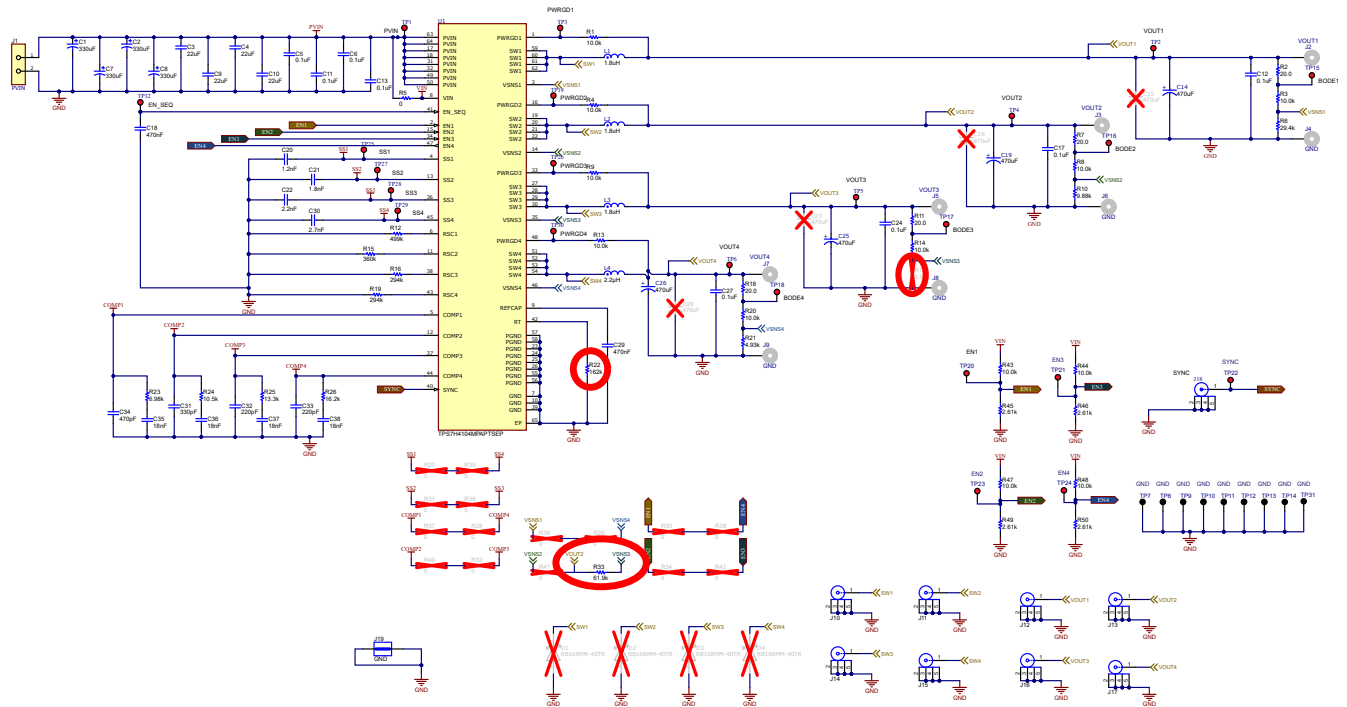

**Figure 5-1. Modified EVM Schematic**




The location of R17 is shown in [Figure 5-2](#).

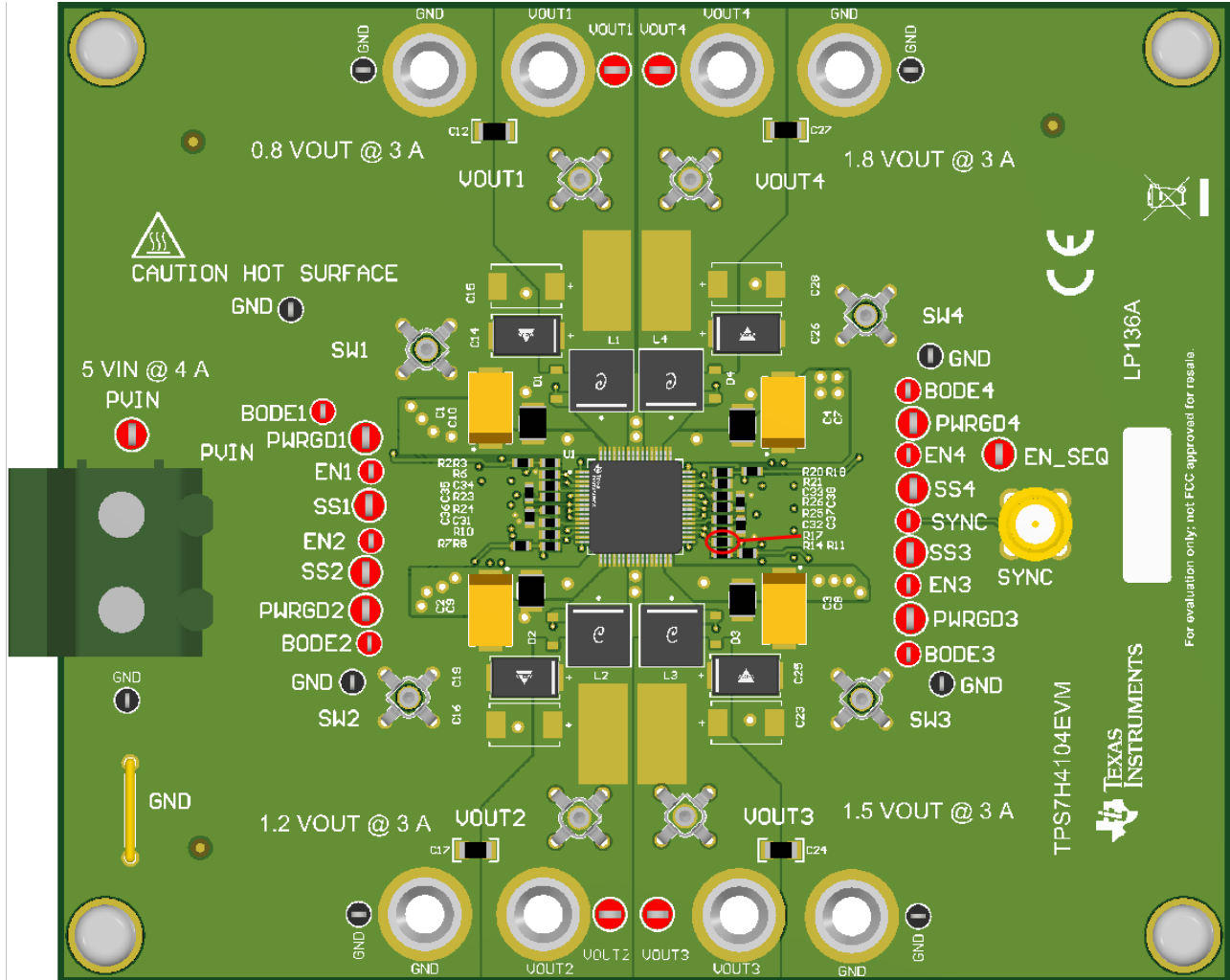


**Figure 5-2. Top-side EVM Board Render**

Modifications to the bottom of the EVM are shown in [Figure 5-3](#). When R33 (RB1) is populated, one pad is connected through a via to VSNS3, while the other pad is connected to a trace that leads to R41. Since R41 is not populated, the left-side pad of R41 can be connected through an external wire to VOUT2 (V<sub>EXT</sub>), this was done by connecting to the bottom side of the VOUT2 test point. The trace connecting R33 to R41 now provides V<sub>EXT</sub> to R<sub>B1</sub>, completing the modified feedback circuit.

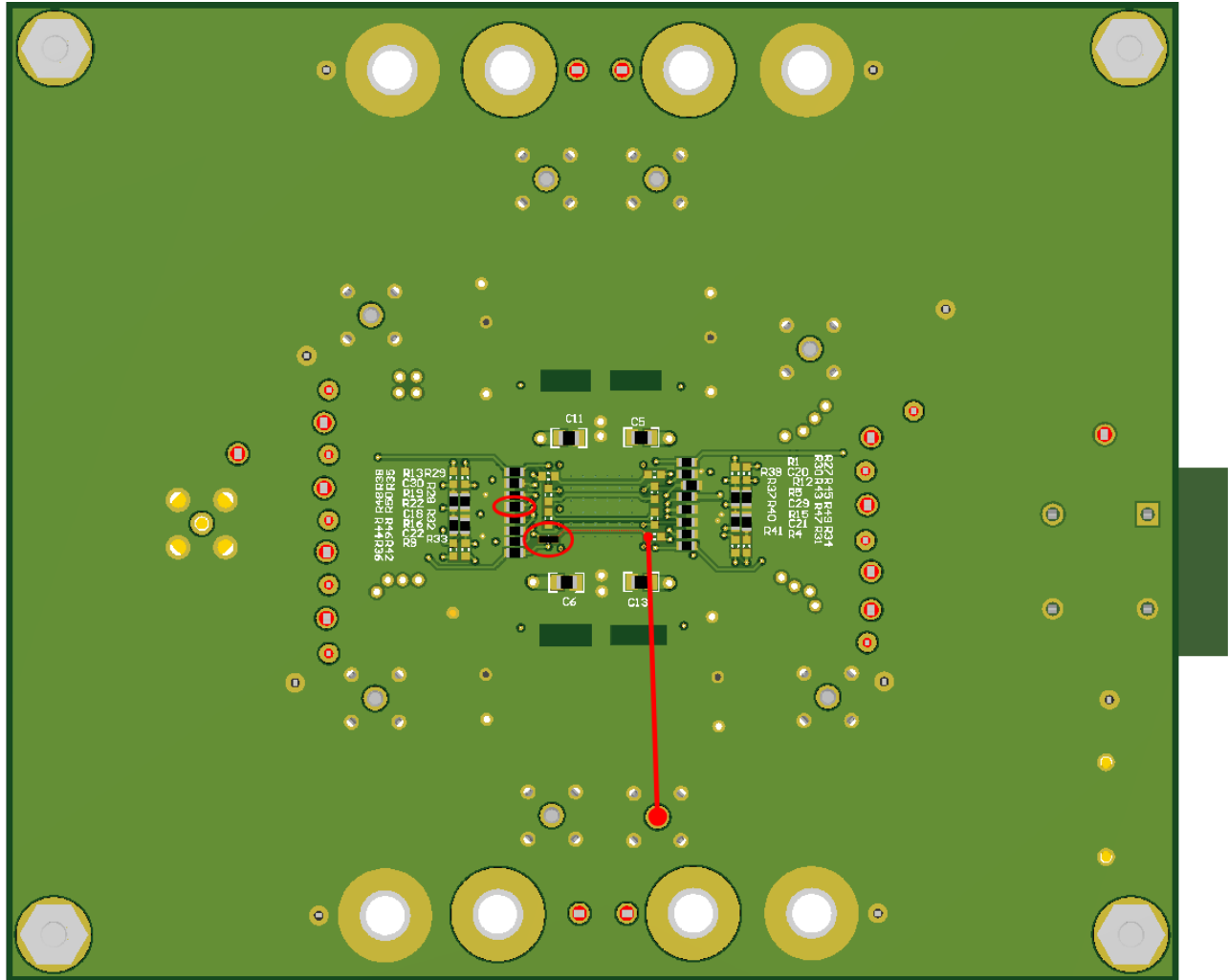

**Figure 5-3. Bottom-Side EVM Board Render**

The modified EVM was powered on with the internal sequencer enabled, and the startup was recorded with a 3A load on  $V_{OUT}$ .

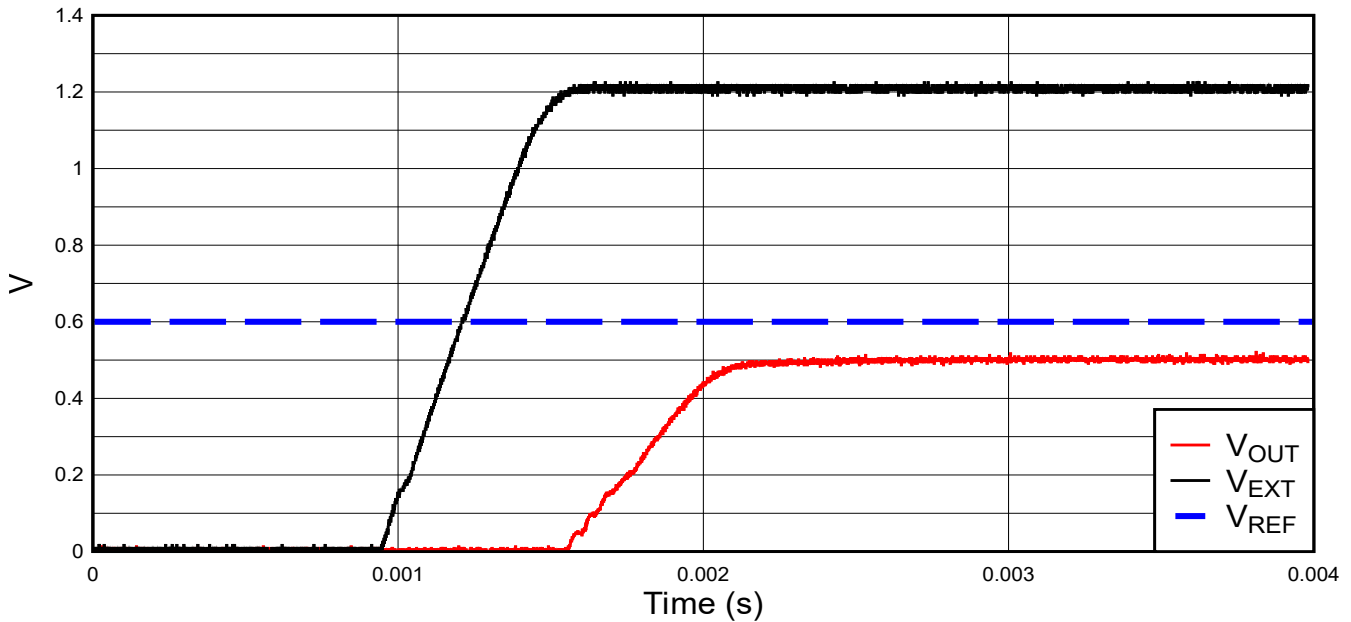

**Figure 5-4. EVM Startup Result**

As expected, the output from the modified EVM matches closely with the simulation results in [Figure 4-2](#), providing a 0.5V output on CH3 using the 1.2V  $V_{EXT}$  generated from CH2.

## 6 Summary

For applications requiring voltage rails at lower voltages than the reference voltage of a buck converter, the demonstrated circuit can be implemented with an external reference to regulate to lower voltages. When maintaining accuracy is also critical for a below-reference rail, multichannel regulators that use a single internal reference, such as the TPS7H4104, can be configured to use one of their outputs to generate the external reference voltage. In doing so, no extra error is introduced from an external reference, and output accuracy is maintained with minimal additional component count. This application note provides details on the theory of operation of such a system, provides simulation results using the TPS7H4104, and details the modification of a TPS7H4104EVM to produce the described high-accuracy sub-reference output.

## 7 References

- Texas Instruments, [Regulating  \$V\_{OUT}\$  Below 1.2 V Using an External Reference](#), application note.
- Texas Instruments, [How to Receive a Lower Output Voltage Than Reference Voltage](#), application note.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2025, Texas Instruments Incorporated

Last updated 10/2025