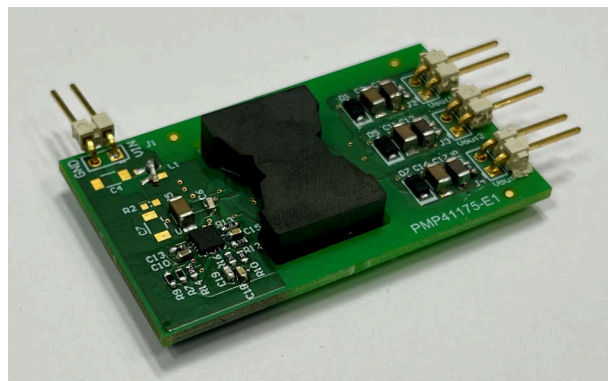


Isolated Bias Supply Reference Design Using PSR Flyback Topology with Planar Transformer



Description

This reference design is a tiny three channel isolated bias supply based on Flyback topology. Providing the voltage supply for isolated gate drivers is a typically use case. The design integrates three 21V, 2W isolated outputs and one 7V non-isolated auxiliary output. The design uses a planar transformer integrated into the printed circuit board (PCB) to reduce the board height and system cost. The LM5158-Q1 converter supports primary-side regulation (PSR) by using an auxiliary winding on the primary side. The maximum efficiency is 88%.




PCB View

Features

- Primary-side regulated flyback for three outputs (21V, 2W) with planar transformer
- Peak efficiency 88% at 6W full load
- Low transformer Parasitic capacitance (<10pF)
- Low height (9mm)
- Compact size in 50mm × 29mm

Applications

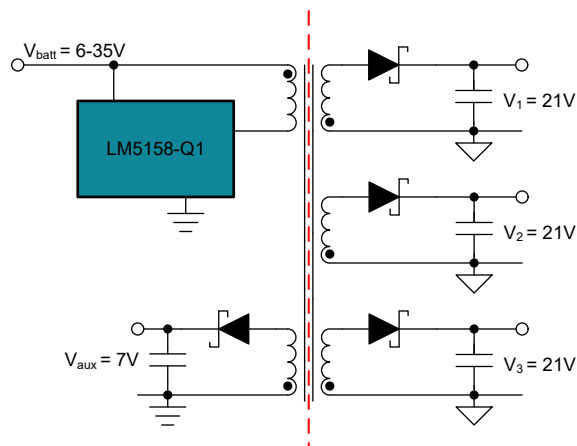- [Onboard Charger](#)
- [Traction inverter](#)
- [DC/DC converter system](#)
- [Automotive HVAC compressor module](#)



Block Diagram

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

| PARAMETER | SPECIFICATIONS |
|---------------------------|-----------------------------|
| Electrical | |
| Input voltage | 6V–35V |
| Output voltage | 3 × 21V |
| Output voltage (Aux) | 7V |
| Output power | 2W for each rail |
| Switching frequency | 400kHz |
| Planar Transformer | |
| Primary inductance | 5uH |
| Leakage inductance | 120nH |
| Parasitic capacitance | 10pF |
| Turn ratio | 2 : 3 : 1 (pri : sec : aux) |
| Magnetic core | PC95PQI20/9Z-12 |
| Creepage and clearance | 4mm |

1.2 Required Equipment

- Power supply, 0–40VDC, 2A
- 3× Active load, 21VDC, 0.1A
- Oscilloscope, 4CH

1.3 Dimensions

The board dimensions are 50mm (length) by 29mm (width) by 9mm (height).

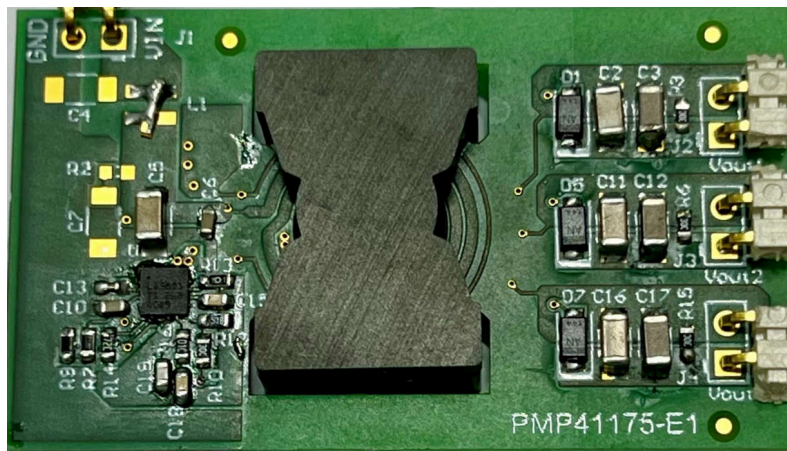


Figure 1-1. Board Top View

2 Testing and Results

2.1 Efficiency Graphs

Figure 2-1 show the efficiency graph.

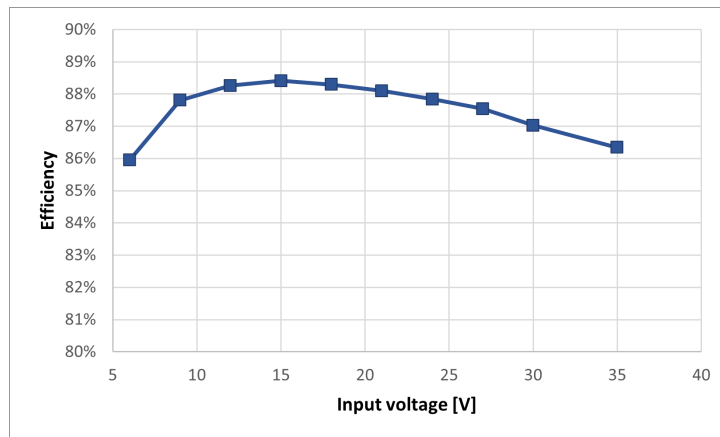


Figure 2-1. Efficiency Graph (3x100mA)

2.2 Load Regulation

Table 2-1. Load Regulation

| Vo1 (V) | Io1 (A) | Vo2 (V) | Io2 (A) | Vo3 (V) | Io3 (A) |
|---------|---------|---------|---------|---------|---------|
| 21.98 | 0 | 21.99 | 0 | 22.01 | 0 |
| 23.33 | 0 | 22.87 | 0 | 19.72 | 0.1 |
| 21.79 | 0 | 19.02 | 0.1 | 22.61 | 0 |
| 19.67 | 0.1 | 22.07 | 0 | 23.39 | 0 |
| 22.88 | 0 | 20.28 | 0.1 | 20.27 | 0.1 |
| 20.61 | 0.1 | 22.73 | 0 | 20.62 | 0.1 |
| 19.14 | 0.1 | 19.16 | 0.1 | 23.45 | 0 |
| 20.81 | 0.1 | 20.82 | 0.1 | 20.83 | 0.1 |

2.3 Thermal Images

Figure 2-2 and Figure 2-3 show thermal images.

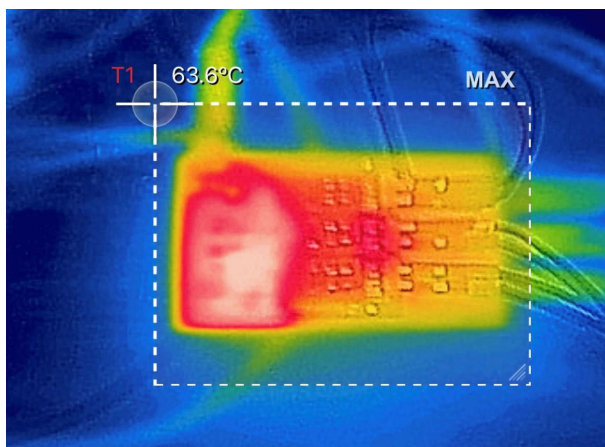


Figure 2-2. Thermal Image, 6V Input, Full Load

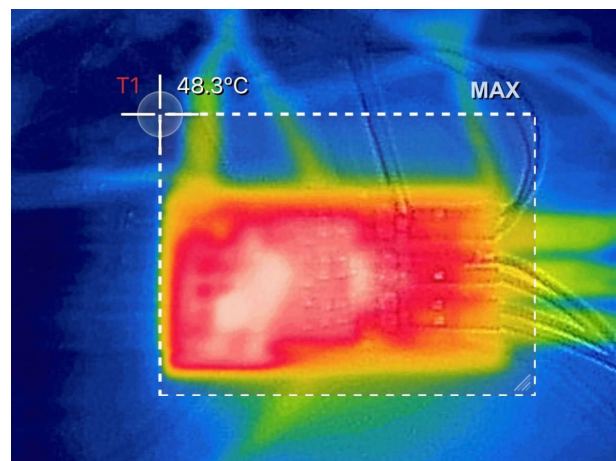


Figure 2-3. Thermal Image, 12V Input, Full Load

3 Waveforms

3.1 Switching

Figure 3-1, Figure 3-2, and Figure 3-3 show the switching behavior.

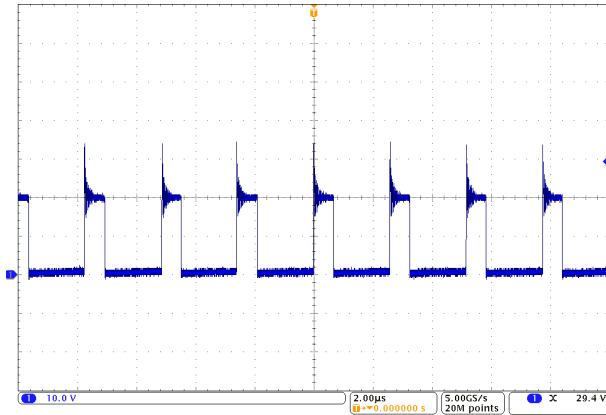


Figure 3-1. Switching, 6V Input, Full Load

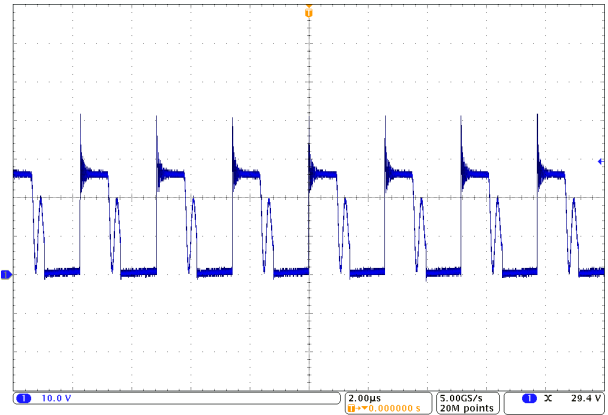


Figure 3-2. Switching, 12V Input, Full Load

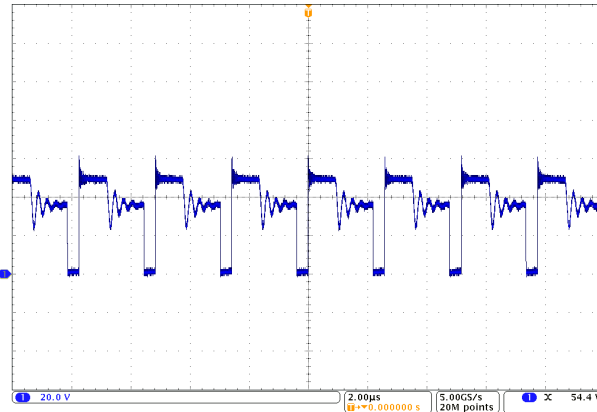


Figure 3-3. Switching, 35V Input, Full Load

3.2 Output Voltage Ripple

Figure 3-4 and Figure 3-5 show the output voltage ripple.

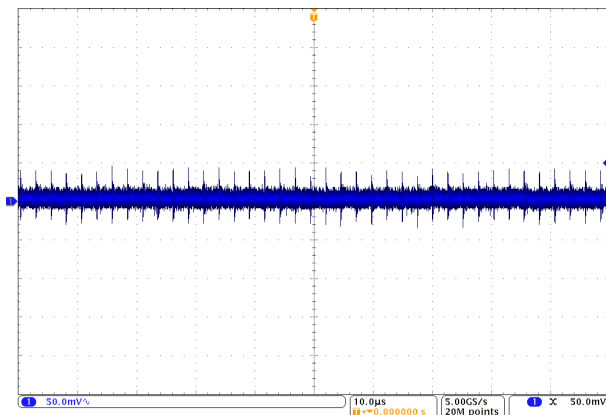


Figure 3-4. VOUT1 Output Voltage Ripple, 12V Input, No Load

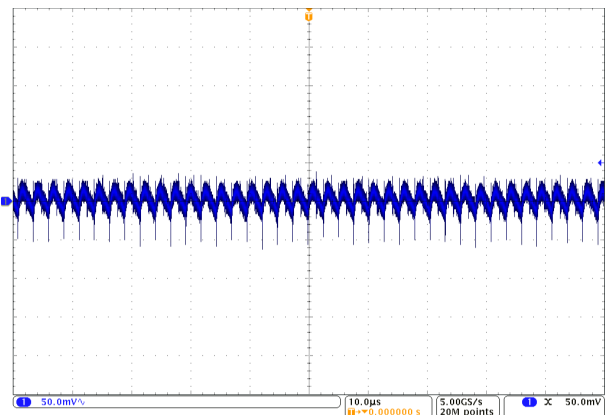


Figure 3-5. VOUT1 Output Voltage Ripple, 12V Input, Full Load

3.3 Load Transients

Figure 3-6, Figure 3-7, and Figure 3-8 show the load transient response.

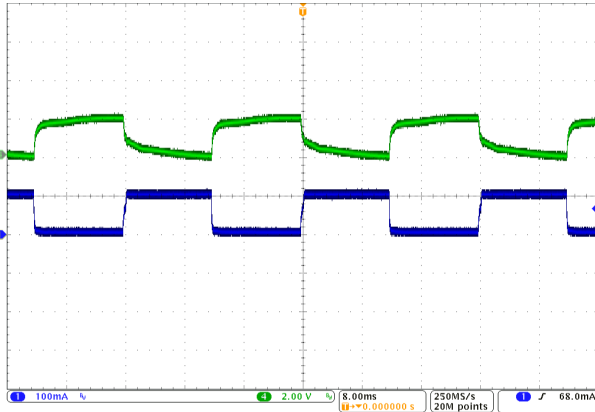


Figure 3-6. V_{out1} Load Transient, 6V Input

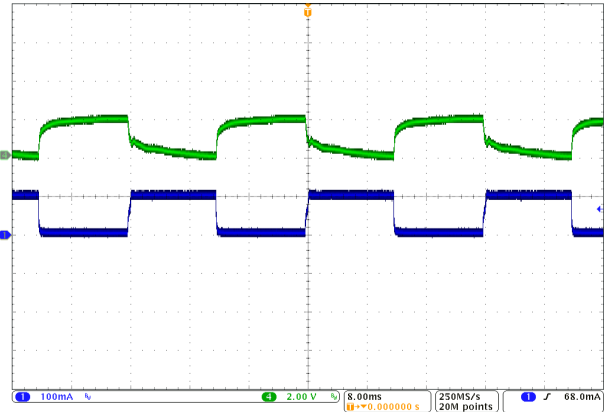


Figure 3-7. V_{out1} Load Transient, 12V Input

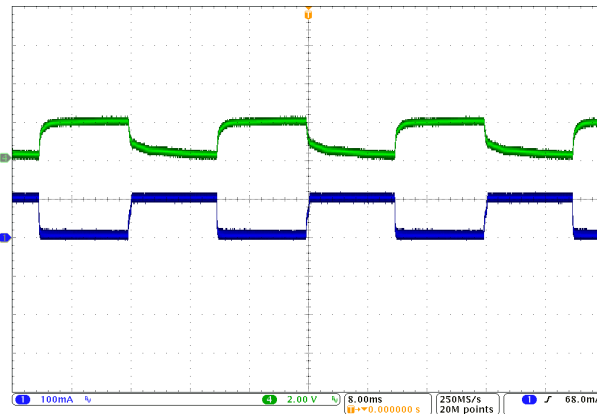


Figure 3-8. V_{out1} Load Transient, 35V Input

3.4 Start-up Sequence

Figure 3-9 and Figure 3-10 show the start-up behavior.

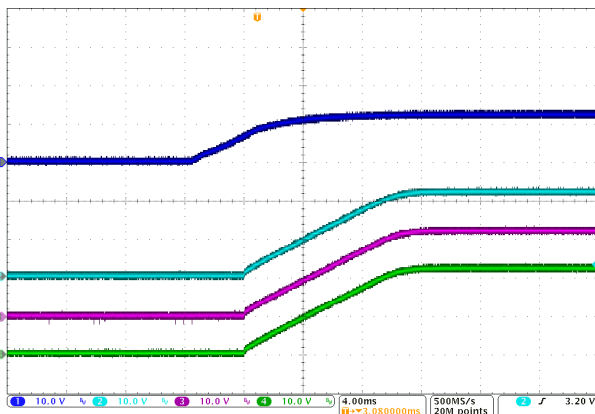


Figure 3-9. Start-Up Waveform, 12V Input, No Load

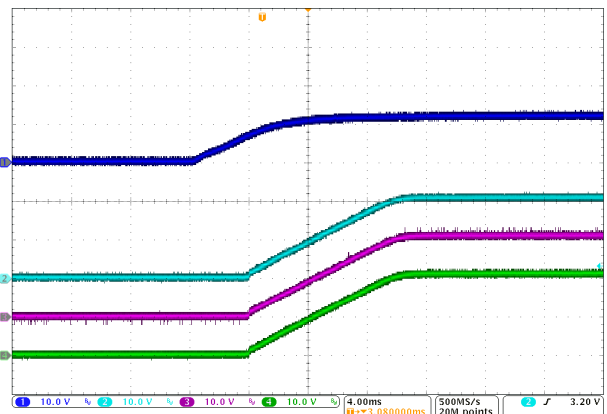


Figure 3-10. Start-Up Waveform, 12V Input, Full Load

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025