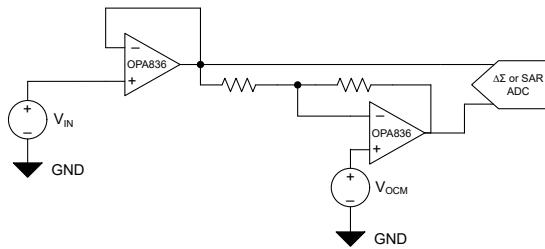



Jason Clark, Rachel Scheller

While more of the industry's newest high-resolution, precision [analog-to-digital converters](#) (ADCs) implement differential inputs to maximize performance, many designers still choose to use single-ended amplifiers because that is what they are comfortable with. But fully differential amplifiers (FDAs) offer many system advantages without sacrificing precision. In this article, the 2025 [THS4536](#) ultra-high precision, low noise 80MHz FDA will be used as an example of how to realize many of the benefits of fully differential amplifiers.


FDAs enable simple single-ended to differential signal conversion with direct current (DC) coupling. In [Figure 1](#) through [Figure 3](#), you can see three different examples of driving a single-ended signal into the differential input of an ADC. However, the FDA offers lower power, lower noise, improved dynamic range and other circuit benefits all while simplifying the overall signal chain.



**Figure 1. ADC Drive using Dual Operational Amplifier (Op Amp)**

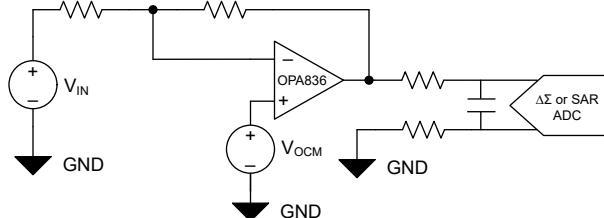

**Figure 2. ADC Drive using Pseudo Differential Input**

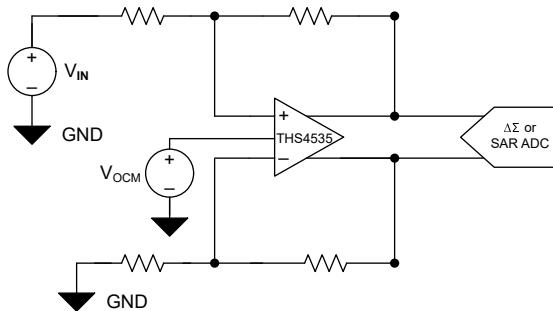


**Figure 3. ADC Drive using Fully Differential Amplifier**

The FDA architecture can help significantly lower total harmonic distortion (THD) by reducing  $HD_2$ . Implementing the FDA method shown in [Figure 3](#), can result in an overall system performance improvement or give you the flexibility to use a lower-power or lower-bandwidth amplifier to meet the same THD.


In addition to lower THD, a single FDA ([Figure 3](#)) will also have  $\frac{1}{\sqrt{2}}$  lower noise for the same power than a pair of single-ended op amps ([Figure 1](#)). For example, an op amp with an input-voltage noise of  $4\text{nV}/\sqrt{\text{Hz}}$  will have a total input-voltage noise of  $4\sqrt{2} \text{nV}/\sqrt{\text{Hz}}$  in the dual op amp circuit configuration. Compare that with a fully differential amplifier, such as THS4536, that has an input-voltage noise also approximately  $4 \text{nV}/\sqrt{\text{Hz}}$ , the total input-voltage noise is equivalent to the FDA due to only one device.

FDA can operate from a single supply voltage and still accept bipolar input signals. [Figure 4](#) shows the [THS4536](#) accepting a  $20\text{Vpp}$  input ( $0\text{V}$  common mode) and outputting  $8\text{Vpp}$  with a  $2.5\text{V}$  common mode. This capability allows you to reduce system complexity by eliminating the negative power supply and any unnecessary signal-attenuation stages. FDAs also include a common-mode output loop to perfectly match the expected ADC input common mode. The  $V_{OCM}$  pin sets the output common mode of the amplifier without the need for any additional compensation.

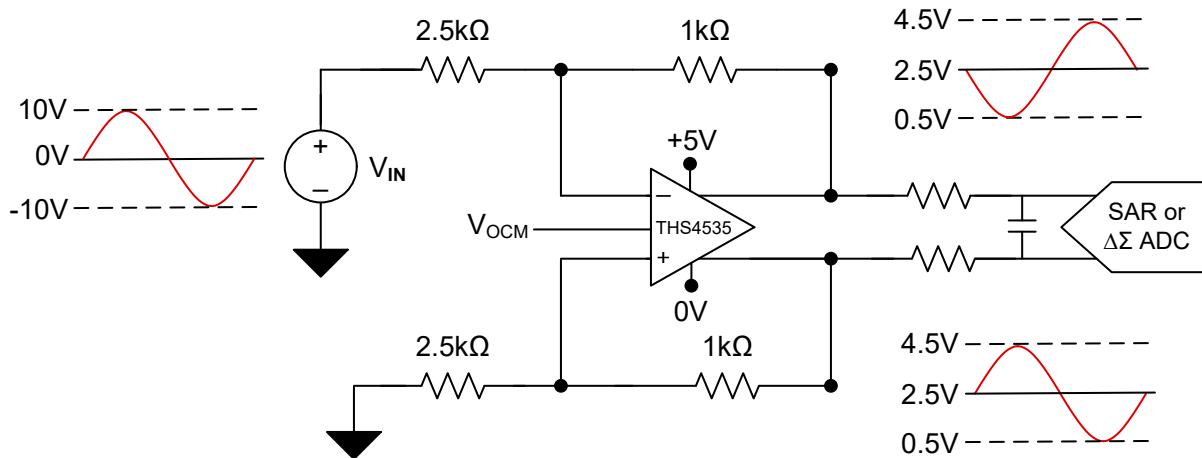


**Figure 4. FDA in Attenuation Configuration**

As shown in [Figure 5](#) and [Figure 6](#), most of TI FDAs are offered in 2 small packages including a [2mm-by-2mm 10-pin QFN \(RUN\)](#), making it the industry's smallest FDA package and suitable for use in even the most space-constrained application.

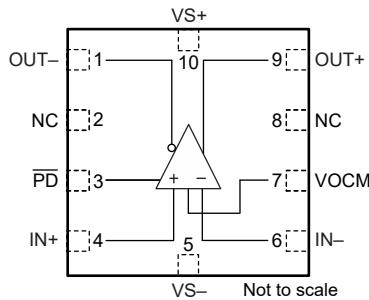


**Figure 5. 2mm-by-2mm 10-Pin QFN**

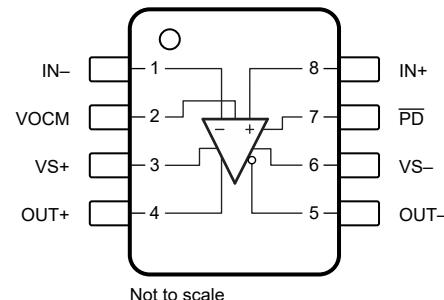

**Figure 6. 5mm-by-3mm 8-Pin VSSOP**

TI's 2025 [THS4536](#) is one of the highest-precision FDAs in the industry, with  $\pm 50\mu\text{V}$  input offset and  $0.8\mu\text{V}/^\circ\text{C}$  offset drift maximum. This enables the improved system performance and minimizes the need for costly and time-consuming system calibrations.

The popular [ADS127L11](#) 24-bit 400KSPS Delta-Sigma ADC offers an example of the impact of FDAs. As [Figure 7](#) shows, the ADC-plus-driver pair achieves a signal-to-noise ratio (SNR) of 102dB and a THD of -115dB with a 1kHz input signal (OSR = 32). This level of performance was achieved while adding less than 24mW of system power, making the THS4536 an essential part of designs that require the minimal power effect while also delivering the best harmonic distortion and precision performance.

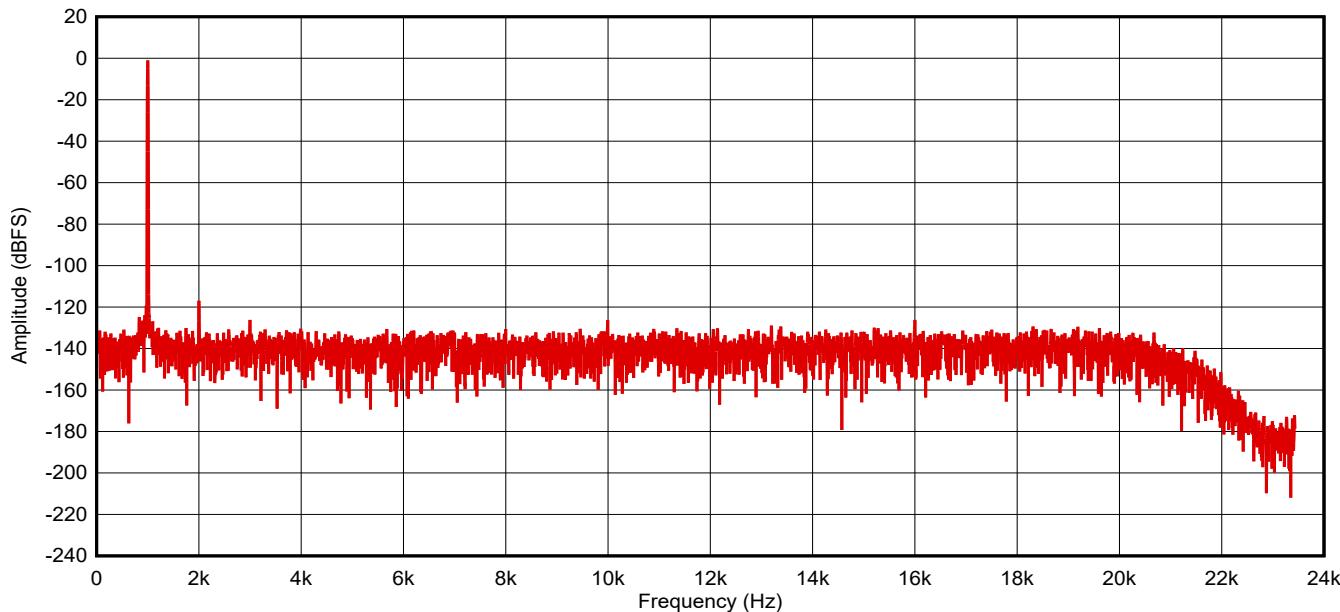

**Figure 7. ADS127L11 with THS4536 Spectrum**

If your ADC has a differential input, a precision FDA, such as the [THS4536](#) could be a good choice to simplify your system design and enable low noise, low power, and low harmonic distortion.

---

## Additional Resources

In addition to this document, see the following references at [www.ti.com](http://www.ti.com).

1. [Texas Instrument's Filter Design Tool](#)
2. [Active Filter Design for Differential ADCs](#)
3. [Operational Amplifiers vs. Fully Differential Amplifiers for Differential ADC Drive](#)
4. [Using the infinite-gain, MFB filter topology in fully differential active filters](#)
5. [Design a front-end to drive a differential ADC](#)
6. [Active Low-Pass Filter Design](#)
7. [AN-1393 Using High Speed Differential Amplifiers to Drive Analog-to-Digital Converters](#)
8. [Single-Ended Input to Differential Output Circuit Using a Fully Differential Amplifier](#)
9. [Using fully differential op amps as attenuators](#)
10. [High Performance Single Ended to Differential Active Interface for High-Speed ADC Developed by Dallas Logic Corp. \(TIDA-00294\)](#)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025