

# Reducing Effects of External RC Filter on Gain Error and Drift in SAR ADC with Integrated AFE



For applications using SAR ADCs with integrated analog front ends (AFE), such as the [ADS8588S](#), an external resistor-capacitor (RC) filter at the input may be necessary to eliminate noise pickup and to protect the input from electrical overstress. However, this filter introduces gain error and gain error drift. The purpose of this TechNote is to show how to calculate the gain error and gain error drift added by the external RC filter. [Figure 1](#) shows the integrated AFE in the [ADS8588S](#) and the external balanced RC filter. It is very important to understand that the external filter requires a resistor on both the positive and negative inputs as shown; matching the input impedances is required for good common mode and noise rejection.

The selection of the external resistor is designed to limit the input current from an overstress event. A typical value for this resistance is 10k ohms, and for maximum protection an external TVS diode is recommended. The capacitor is selected to set the filter cutoff frequency. For this example the cutoff frequency is set to 320Hz for a system monitoring 50 or 60 Hz power signals. The cutoff frequency can be adjusted according to the design requirements.

Adding the external resistor will affect the room temperature gain of the data converter as the resistance is directly in series with the 1M ohm input impedance of the AFE. Assuming the internal input impedance and external resistors are known, this gain error can be mathematically accounted for. However, the [ADS8588S](#) internal impedance has a range of 0.85 Mohm to 1.15 Mohm, which will minimize the effectiveness of this correction. In this example, the corrected gain error would be approximately  $\pm 0.15\%$  from internal impedance variation, whereas the

uncorrected gain error would be about  $1\% \pm 0.15\%$ . Depending on the magnitude of the external resistor used, this gain error will differ but for many applications calibration is used to significantly reduce this error.

The room temperature gain error added to the system by the external resistor is given by the equation below. This gain error equation is based on a voltage divider relationship and is the additional uncorrected error from the external resistor. For this example, the uncorrected gain error due to the external resistor is 0.9901%. For comparison, the [ADS8588S](#) internal maximum gain error is 64 least significant bits which translates to 0.098% [ $100 \times 64 / (2^{16}) = 0.098\%$ ].

$$\text{GainError}(R_{\text{EXT}})_{\text{RoomTemp}} = \frac{1}{1 + \frac{R_{\text{IN}}}{R_{\text{EXT}}}}$$

$$\text{GainError}(R_{\text{EXT}})_{\text{RoomTemp}} = \frac{1}{1 + \frac{1\text{M}\Omega}{10\text{k}\Omega}} = 0.009901 \text{ or } 0.9901\%$$

A simple two point calibration is typically used to correct for gain error in a data converter system. This method will eliminate both the gain error introduced by the external resistor as well as internal device gain error. In this calibration method two test signals are applied and measured at 10% and 90% of the linear range of the input voltage range. These measurements are then used to calculate the slope (m) and offset (b) of the linear transfer function, shown in the equations below.

$$\text{Code} = m \cdot V_{\text{in}} + b$$

$$m = \frac{\text{Code}_{\text{max}} - \text{Code}_{\text{min}}}{V_{\text{max}} - V_{\text{min}}}$$

$$b = \text{Code}_{\text{min}} - m \cdot V_{\text{min}}$$

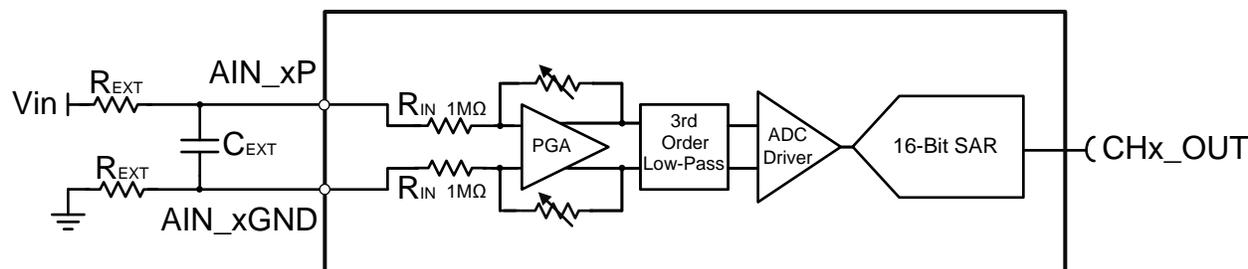


Figure 1. [ADS8588S](#) Integrated Analog Front End with external RC filter

Once the calibration coefficients are determined, they are used to correct for the gain and offset of the data converter and external components, using the equation below. Mathematically, this is done by solving the straight line equation for the input signal. Usually the calibration method is executed during a factory automated test, once the coefficients are calculated, they are stored in memory and used in all subsequent measurements to minimize the error.

$$V_{in\_CALIBRATE} = \frac{\text{Code} - b}{m}$$

Using calibration can reduce gain and offset errors to almost negligible levels. After calibration, most of the residual error is due to noise and drift. Both the internal 1Mohm resistor and the external filter resistor will contribute to the system drift. From the ADS8588S datasheet, the electrical characteristic lists the input impedance maximum drift at  $\pm 25\text{ppm}/^\circ\text{C}$ . For this example a precision low drift external resistor ( $0.1\% \pm 25\text{ppm}/^\circ\text{C}$ ) was used. Using a precision low drift resistor for the filter will achieve best results. To calculate the effect of the external resistor on drift, first find the gain error at high temperature. This is done by calculating the internal and external effective resistance at high temperature as is shown in the equations below. For worst case analysis, the signs of the drift term of the internal and external impedances must be different. If the signs were to be the same, the drift errors from the internal and external impedances would cancel.

$$R_{IN(-25\text{ppm}/^\circ\text{C})} = 1\text{M}\Omega \cdot [-25\text{ppm}/^\circ\text{C} \cdot (125^\circ\text{C} - 25^\circ\text{C}) + 1]$$

$$R_{IN(-25\text{ppm}/^\circ\text{C})} = 0.9975\text{M}\Omega$$

$$R_{EXT(+25\text{ppm}/^\circ\text{C})} = 10\text{k}\Omega \cdot [25\text{ppm}/^\circ\text{C} \cdot (125^\circ\text{C} - 25^\circ\text{C}) + 1]$$

$$R_{EXT(+25\text{ppm}/^\circ\text{C})} = 10.025\text{k}\Omega$$

Next, to calculate gain error drift, calculate the gain error at  $25^\circ\text{C}$ , and at  $125^\circ\text{C}$ .

$$\text{GainError}(R_{EXT})_{\text{RoomTemp}} = \frac{1}{1 + \frac{1\text{M}\Omega}{10\text{k}\Omega}} = 0.009901 \text{ or } 0.9901\%$$

$$\text{GainError}(R_{EXT})_{125^\circ\text{C}} = \frac{1}{1 + \frac{0.9975\text{M}\Omega}{10.025\text{k}\Omega}} = 0.009950 \text{ or } 0.995\%$$

Finally, take the difference of the errors over temperature, divide by the temperature range used and multiply by one million to convert to ppm.

$$\text{GainErrorDrift}(R_{EXT}) = \frac{\Delta\text{GainError}}{\Delta\text{Temperature}} \cdot 10^6$$

$$\text{GainErrorDrift}(R_{EXT}) = \frac{.009950 - .009901}{(125^\circ\text{C} - 25^\circ\text{C})} \cdot 10^6 \text{ ppm}$$

$$\text{GainErrorDrift}(R_{EXT}) = -0.49\text{ppm}/^\circ\text{C}$$

In the ADS8588s datasheet the gain error temperature drift is listed at a maximum  $\pm 14\text{ppm}/^\circ\text{C}$  when using an external reference. This is orders of magnitude larger than the calculated additional drift error introduced by the external resistor ( $-0.49\text{ppm}/^\circ\text{C}$ ), making the introduced error insignificant. The minimal drift error introduced by the external components is possible because both the internal 1Mohm resistance and the external resistance have low drift. This same calculation can be done using different external resistor values. The absolute worst case drift can be kept relatively low if low drift external resistors (e.g.  $\pm 25\text{ppm}/^\circ\text{C}$  or better) are used. For example, the worst case drift introduced by a 1Mohm  $\pm 25\text{ppm}/^\circ\text{C}$  external resistor is about  $\pm 12\text{ppm}/^\circ\text{C}$ .

In summary, an external RC filter is a common way to reduce noise as well as protect the input circuit. This circuit will have some impact on the gain error and drift of the system. This paper demonstrated a method for calculating gain error and drift. For best accuracy, calibration can be used. The drift error can be minimized by using precision low drift external resistors; this drift will generally be significantly lower than the device's drift.

**Table 1. Alternative Device Recommendations**

Device	Optimized Parameters	Performance Trade-Off
<a href="#">ADS8588S</a>	Input Impedance Max Drift $\pm 25\text{ppm}/^\circ\text{C}$	Simultaneous Sampling, 16 Bit, 200-kSPS
<a href="#">ADS8688</a>	Input Impedance Max Drift $\pm 25\text{ppm}/^\circ\text{C}$	MUX, 16 Bit, 500-kSPS
<a href="#">ADS8681</a>	Input Impedance Max Drift $\pm 25\text{ppm}/^\circ\text{C}$	Single Channel, 16 Bit, 1-MSPS

**Table 2. Related Documentation**

<a href="#">TIPLADC 3.2</a>	TI Precision Labs ACD 3.2: Understanding and Calibrating the Offset and Gain for ADC Systems
<a href="#">TIDUC09</a>	High-Accuracy Analog Front End Reference Design Using 16-Bit SAR ADC With $\pm 10\text{-V}$ Measurement Range
<a href="#">TIDU540A</a>	High-Accuracy AC Voltage and Current Measurement AFE for Feeder Terminal Unit Reference Design
<a href="#">TIDU427B</a>	Phase-Compensated, 8-Ch, Multiplexed Data Acquisition System for Power Automation Reference Design

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated