

# Make a –10V to +10V Adjustable Precision Voltage Source


R. Mark Stitt

*High-Performance Analog*

## ABSTRACT

Many situations require a precision voltage source which can be adjusted through zero to both positive and negative output voltages. An example is a bipolar power supply. Have you ever adjusted your unipolar lab supply down to 0V, then swapped the output leads and adjusted it back up to get a negative voltage output? What happened to your circuit when the input from the low impedance source went open circuit? Were you able to actually adjust the output to 0V, or did a small voltage offset limit the range? This precision bipolar voltage source can solve these problems.

Perhaps the most obvious implementation of a bipolar voltage source would be to use a bipolar voltage reference.

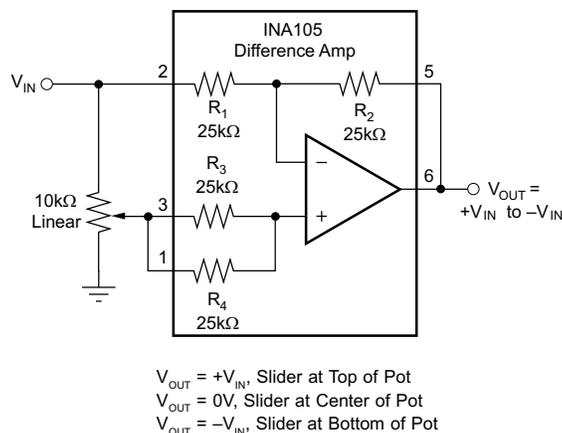


**Figure 1. –1.0V/V to +1.0V/V Linear Gain Control Amplifier**

However, a simpler solution is to use a single voltage reference and a precision unity-gain inverting amplifier. If you use a precision difference amplifier for the unity-gain inverting amplifier, the circuit requires just two chips and a potentiometer.


To understand how the circuit works, first consider the –1.0V/V to +1.0V/V linear gain control amplifier shown in [Figure 1](#). An INA105 difference amplifier is used in a unity-gain inverting amplifier configuration. A potentiometer is connected between the input and ground. The slider of the pot is connected to the noninverting input of the unity-gain inverting amplifier. (The noninverting input of a unity-gain inverting amplifier would normally be connected to ground.) With the slider at the bottom of the pot, the circuit is a normal precision unity-gain inverting amplifier with a gain of –1.0V/V ±0.01% max. With the slider at the top of the pot, the circuit is a normal precision voltage follower with a gain of +1.0V/V ±0.001% max. With the slider in the center, there is equal positive and negative gain for a net gain of 0V/V. The accuracy between –1.0V/V and +1.0V/V will normally be limited by the accuracy of the pot. Precision 10-turn pots are available with 0.01% linearity.

The –1.0V/V to +1.0V/V linear gain control amplifier has many applications. With the addition of a precision +10.0V reference as shown in [Figure 2](#), it becomes a –10V to +10V adjustable precision voltage source.

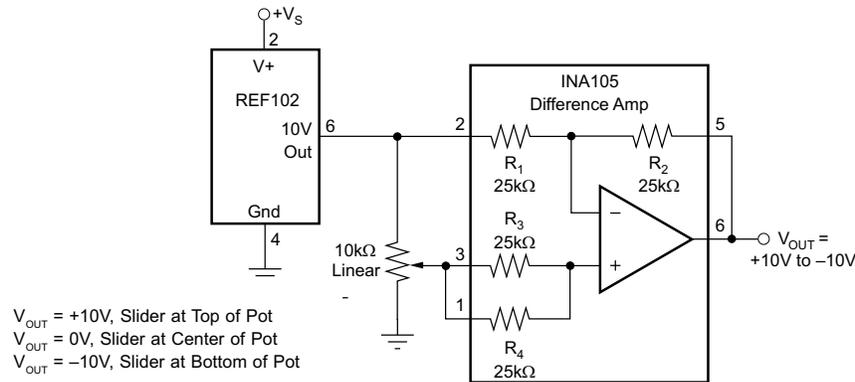

**Figure 2. -10V to +10V Adjustable Precision Voltage Source**

In many instances adjustable voltage sources need the ability to drive high-capacitance loads such as power-supply bypass capacitors. The additional circuitry needed to drive high capacitance is shown in Figure 3. For stability, keep  $C_{LOAD} \times R_3 < 0.5 \times R_2 \times C_2$ . Since access to the op amp inverting input is needed, the unity-gain inverting amplifier is made with an op amp and discrete resistors. For precision,  $R_1$  and  $R_2$  must be accurately matched. Also, load current flows in  $R_3$ . The resulting voltage drop adds to the required swing at the output of the op amp. Keep the voltage drop across  $R_3$  low—less than 1V at full load—to prevent the amplifier output from swinging too close to its power-supply rail.

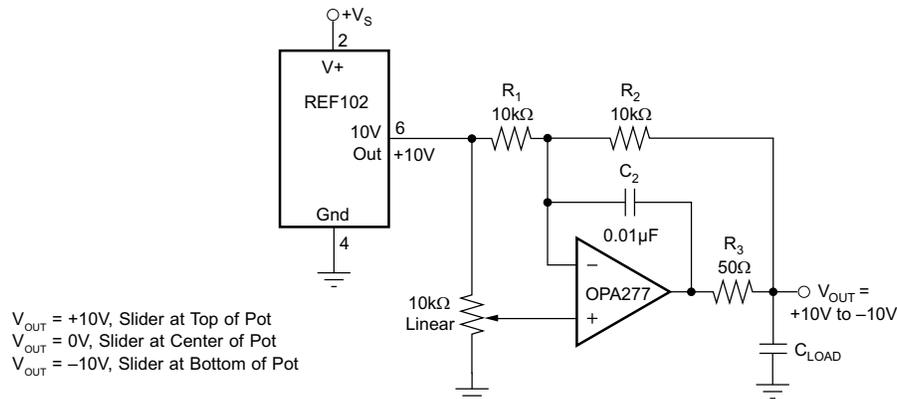

**Figure 3. -10V to +10V Adjustable Precision Voltage Source with High Capacitance-Load Drive Capability**

### Revision History

**Changes from Original (October 2000) to A Revision**

**Page**

- Changed formatting to standard TI application note. .... 1

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)