

# TAS3204 Low Power Operation

Mark Watts

Mixed Signal Audio/Video

## ABSTRACT

For portable or other power-sensitive applications, it may be desirable to decrease the power consumption of the TAS3204 at the expense of decreasing performance and/or increasing external circuitry.

## Power Reduction Techniques

The first technique for reducing power consumption is reducing the clock speed of the digital core. The default clock frequency of the TAS3204 is 135 MHz. Reducing this frequency causes a corresponding linear loss in DSP programming cycles. For example, when operating at 135 MHz (assuming 48-kHz Fs), 2816 cycles are available to the programmer. However, at 67.5 MHz, only 1408 cycles are available. Another drawback of reclocking the digital core is that it can only be done when the part is operated in slave mode and is provided with an external 512Fs clock to drive the analog circuitry. The reason for this can be seen in [Figure 1](#).

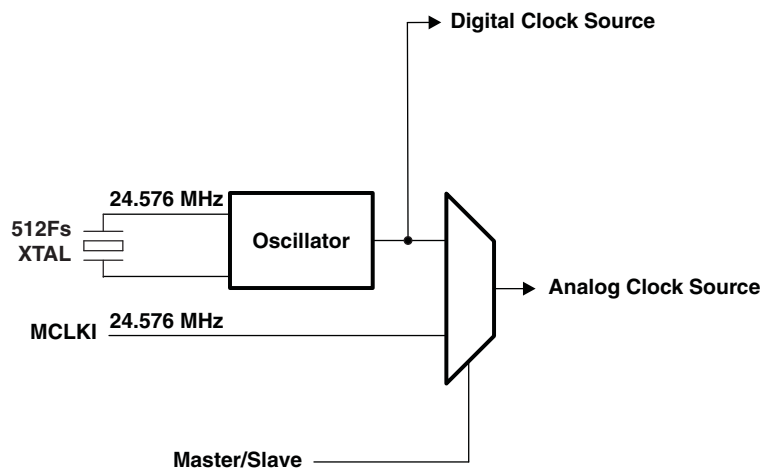


Figure 1. Master/Slave Clock Diagram

The digital core clock is driven by the crystal oscillator regardless of master/slave mode. The analog clock (which must be 24.576 MHz to guarantee analog performance) is driven by the crystal oscillator when the TAS3204 is in master mode, and by an external MCLK when in slave mode. The clock speed of the digital core can be decreased simply by changing crystals.

Using a 12.288-MHz crystal rather than the default 24.576-MHz crystal reduces the operating frequency from 135 MHz to 67.5 MHz. The digital core consumes approximately 130 mA during normal operation at 135 MHz. It consumes approximately 70 mA while operating at 67.5 MHz.

A second technique for reducing power consumption is bypassing the internal 1.8-V linear regulators. This is accomplished by powering down the regulators and providing an external 1.8-V supply. The TAS3204 utilizes linear 1.8-V regulators to derive the digital supply voltages from the single required 3.3-V input power supply. This linear drop results in nearly half of the power consumed by the digital circuitry being dissipated in the 1.8-V regulators. Utilizing a more efficient external 1.8-V switching power supply, such as the Texas Instruments TPS6220x family of step down converters, can significantly reduce this loss. The procedure for using an external supply is to first power down the internal 1.8-V regulators by pulling the VREG\_EN (active low) pin high, then to apply the external 1.8-V source to pins VR\_DIG, VR\_ANA, VR\_PLL. The TAS3204 must either be held in reset during this sequence or be reset after it is complete.

During normal operation using the internal 1.8-V regulators, the digital core of the TAS3204 dissipates approximately 430 mW of power. When powering down the regulators and using an external 1.8-V switching supply, the digital core dissipates approximately 215 mW of power.

The power numbers quoted above reflect only the power consumed by the digital core of the TAS3204. [Table 1](#) summarizes the total power consumption (discrepancy is due to analog power consumption) of the TAS3204, under nominal operation, for the described techniques.

**Table 1. Summary of Power Consumption**

Operating Mode	Total Power Consumption	
	mA	mW
135 MHz, internal regulators on (default operation)	190	627
67.5 MHz, internal regulators on	130	429
135 MHz, bypassing internal regulators	175	405 <sup>(1)</sup>
67.5 MHz, bypassing internal regulators	115	297 <sup>(1)</sup>

<sup>(1)</sup> Due to digital core voltage supply of 1.8 V instead of 3.3 V

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>	Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Low Power Wireless	<a href="http://www.ti.com/lpw">www.ti.com/lpw</a>	Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2007, Texas Instruments Incorporated