

Frequency Dithering with the UCC28180 and TLV3201

Yunsheng Qu

High Performance Isolated Power

ABSTRACT

For some power supplies, even after careful considerations throughout the design cycle, the issue of Electromagnetic Interference (EMI) still remains. Use of Frequency Dithering is an effective and simple way to pass EMC compliance testing. This application note provides a simple circuit to implement frequency dithering for the UCC28180.

Contents

ABSTRACT	1
1 Introduction.....	2
2 Typical PFC converter with UCC28180	2
3 Internal PWM oscillator.....	3
4 Sample Circuit used for Dithering the PWM Oscillator Frequency	4
4.1 frequency dithering variation goal with UCC28180	5
4.2 components calculation of sample circuit.....	5
4.3 Final components selection.....	7
5. Circuit Performance.....	7
6. System performance with dithering circuit.....	10
6.1 PFC ramp up with dithering circuit.....	10
6.2 THD comparison with dithering to without dithering	10
7. Conclusions.....	11
References.....	11

Figures

Figure1.	360W PFC converter with UCC28180	3
Figure2.	Internal oscillator of UCC28180.....	4
Figure3.	Typical Dither Circuit with UCC28180 and TLV32012.....	4
Figure4.	Voltage waveform of C1 of frequency dithering circuit	5
Figure5.	Actual hardware-tested of C1.....	7
Figure6.	PWM signal of the UCC28180 with dithering added	7
Figure7.	PWM signal of the UCC28180 with dithering added (minimum frequency is 58kHz)	8
Figure8.	PWM signal of the UCC28180 with dithering added (central frequency is 65kHz).....	8
Figure9.	PWM signal of the UCC28180 with dithering added (maximum frequency is 72.5kHz).	9
Figure10.	Ramp up with dithering circuit under $V_{in}=110V_{ac}/60Hz$, $380V \times 0.4A$ load	9
Figure11.	Input current with and without dithering circuit	10

1 Introduction

One of the greatest challenges in designing switching power supplies is limiting its Electromagnetic Interference (EMI) with other electronics. In addition to layout techniques to minimize high di/dt current loop areas and snub high dv/dt nodes, extensive filtering, slowing switching edges, and shielding, dithering the pulse width modulator (PWM) frequency has proven to be an effective way to reduce EMI by changing it from narrowband to broadband. To demonstrate how to design such a dithering circuit, this application note shows a simple example of using a TLV3201 comparator to add dither function to a UCC28180 PFC controller. The circuit used to dither the frequency is accomplished by taking advantage of the UCC28180's internal oscillator.

2 Typical PFC converter with UCC28180

Figure 1 is a schematic of a 360W PFC converter with UCC28180 that was designed for a universal input voltage. This application is similar to many PFC converters that use a pulse width modulator (PWM) to control the power converter. UCC28180 is a wide range programmable switching frequency PFC controller by connecting a resistor from FREQ (pin4) to ground, so a dithering circuit can be connected to FREQ (pin4) to dither the switching frequency.

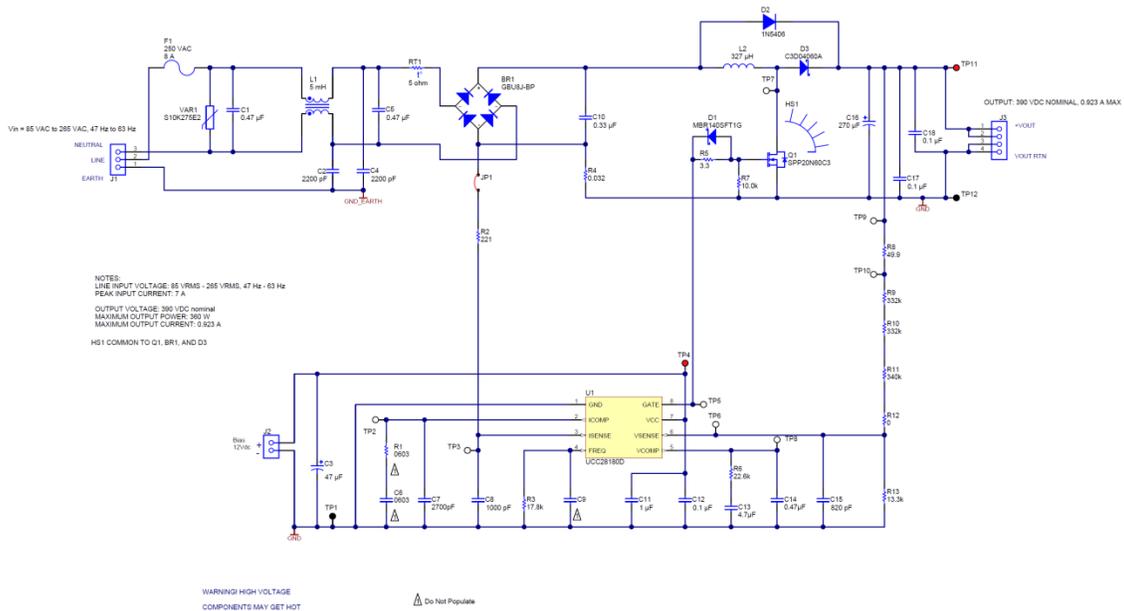


Figure 1. 360W PFC converter with UCC28180

3 Internal PWM oscillator

Figure 2 shows a functional block diagram of the internal circuit that generates the oscillator signal of the UCC28180. The switching frequency is set up by connecting R1 to the FREQ pin. Oscillator gets current signal I1, the final switch frequency is proportional to I1.

The switching frequency is defined as:

$$f = 1.5 \cdot 1417 / RT \quad (1)$$

This is a simplified version of the equation shown in the datasheet.

Where f is in kHz, RT is in kΩ

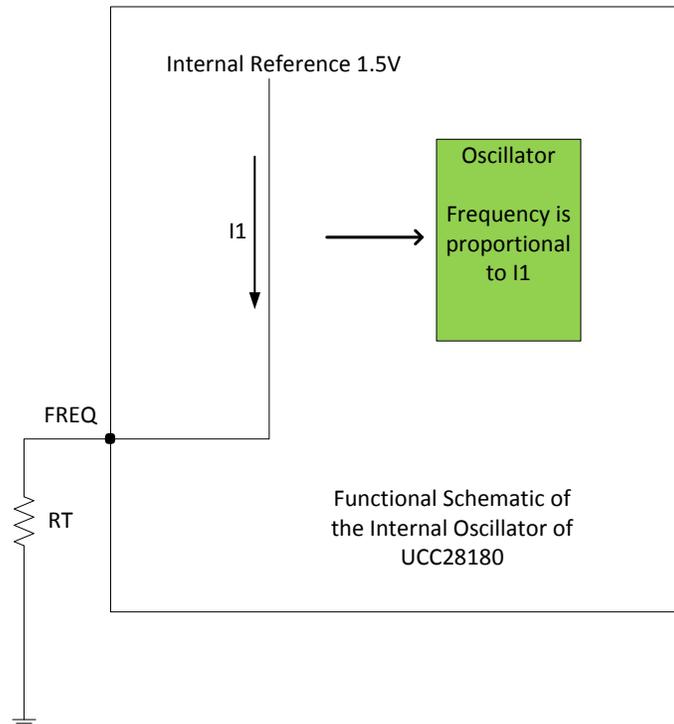


Figure 2. Internal oscillator of UCC28180

4 Sample Circuit used for Dithering the PWM Oscillator Frequency

A typical circuit to apply frequency dithering function is shown in Figure 3 below:

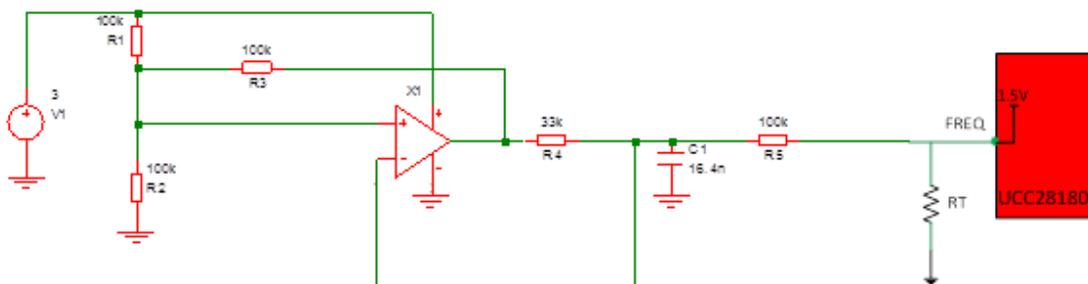


Figure 3. Typical Dither Circuit with UCC28180 and TLV3201

For the UCC28180, the switching frequency is set by the resistor value at the FREQ pin, the FREQ pin itself has an internal 1.5V source and the current out of the FREQ pin determines the switching frequency of the controller, as shown in Figure 2.

4.1 frequency dithering variation goal with UCC28180

In this example, 65 kHz is selected as the central switching frequency of the UCC28180. We will choose an effective dithering magnitude of $\pm 7\text{kHz}$, and dithering rate of 2 kHz. Because central switch frequency is 65 kHz and dithering magnitude is $\pm 7\text{kHz}$, so the maximum switch frequency is 72kHz and the minimum switch frequency is 58kHz.

4.2 components calculation of sample circuit

Based on equation (1):

$$R_T = 1.5 * 1417 / 65 = 32.7(\text{k}\Omega)$$

So the current out of FREQ pin is: $I_1 = 1.5\text{V} / 32.7\text{k}\Omega = 45.87\mu\text{A}$

Dithering current out of FREQ pin is: $\Delta I = \pm(7\text{kHz} / 65\text{kHz}) \times 45.87\mu\text{A} = \pm 4.94\mu\text{A}$

The dithering current comes from the external frequency dithering circuit.

Select $R_5 = 100\text{k}\Omega$, the value of R_5 affects frequency dithering magnitude.

The ripple voltage of C1 is: $4.94\mu\text{A} \times 100\text{k}\Omega = 0.494\text{V}$.

The voltage of C1 is $1.5\text{V} \pm 0.494\text{V}$, the minimum voltage of C1 is 1.006V; the maximum voltage of C1 is 1.994V, as shown in Figure 4.

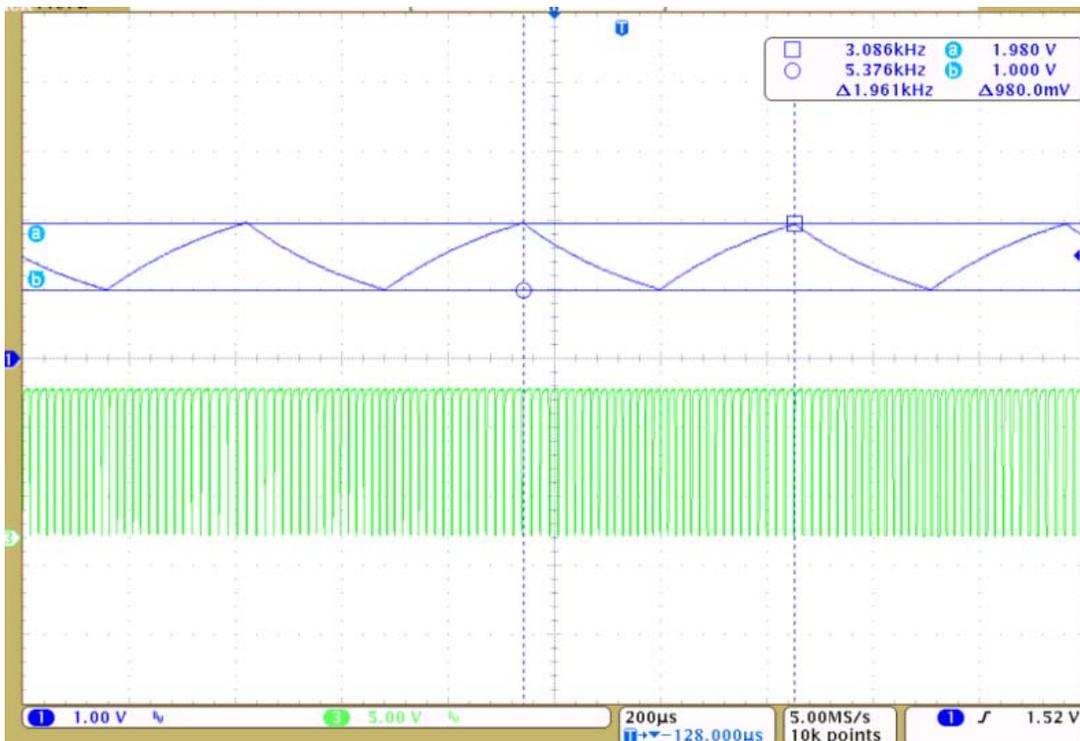


Figure 4. Voltage waveform of C1 of frequency dithering circuit , Ch3 is PWM

A 3V bias voltage is needed for frequency dithering circuit to get symmetrical dithering, because the voltage of FREQ pin is 1.5V. If bias voltage is selected to be 5V, the frequency dithering circuit would not be symmetrical, it is better to select 3V as bias voltage of frequency dithering circuit to get best EMC performance.

R4 limits charge and discharge current for C1, and time factor of R4 and C1 determines dithering rate

- A. Upon initial power-up, the voltage of C1 is 0 V, so the voltage at the non-inverting pin is larger than the inverting pin, the output of the comparator switches high to 3V.**

So the voltage of R2 is VR2:

$$VR2 = 3V \times \left(\frac{R2}{R2 + R1 // R3} \right) = 1.994V \quad (2)$$

The output voltage of comparator charges C1 through R4, increasing voltage at the inverting pin of comparator.

- B. When voltage of C1 is larger than 1.994V, the output voltage of comparator switches low to 0V.**

So the voltage of R2 is VR2:

$$VR2 = 3V \times \left(\frac{R2 // R3}{R1 + R2 // R3} \right) = 1.006V \quad (3)$$

- C. The output voltage of comparator discharges C1 through R4
Once the inverting (-) pin is discharged below the 1.006V threshold, the output voltage of comparator switches high to 3V again, and charges C1 through R4 again, and the process repeats.**

We select $R2=100k\Omega$

Solve R1 and R2 from equation (2) and (3):

R1=100 kΩ, R3=100 kΩ

The actual selection is: R1=100 kΩ, R2=100 kΩ, R3=100 kΩ

From 4.1 and 4.2, the modulating signal will change from 1.006V to 1.994V and back again. With a dithering frequency of 2kHz, the dithering cycle period is $T=500\mu s$. So that the RC time constant of R4 and C1 is equal to the dithering cycle period.

Select $R4=33k\Omega$ because R4 is much smaller than R5

So
$$C1 = \frac{T}{R4} = 15.2nF \quad (4)$$

Therefore we select 2pcs standard 8.2nF cap in parallel to be the charge/discharge cap (C1) to set the modulating frequency.

4.3 Final components selection

Final components selection is:

$R1=100k\Omega$, $R2=100k\Omega$, $R3=100k\Omega$, $R4=33k\Omega$, $R5=100k\Omega$, $C1=8.2nF \times 2$

5. Circuit Performance

Using the components value selection in 4.3 above, the following waveform in Figure 5 was observed at C1:

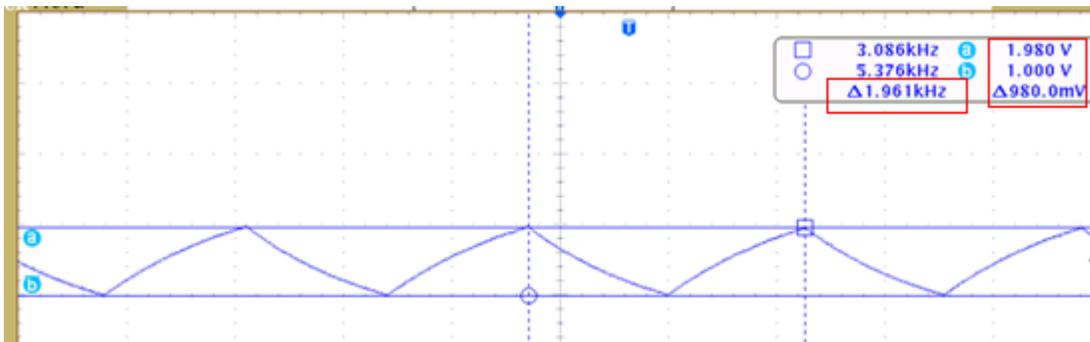


Figure 5. Actual hardware-tested of C1

From Figure 5, we can see 0.98V, 1.961kHz modulation signal, which is very close to our design goals.

PWM signal of UCC28180 with frequency dithering can be observed below in Figure 6:

CH1 = voltage of C1, CH3 = PWM signal of UCC28180

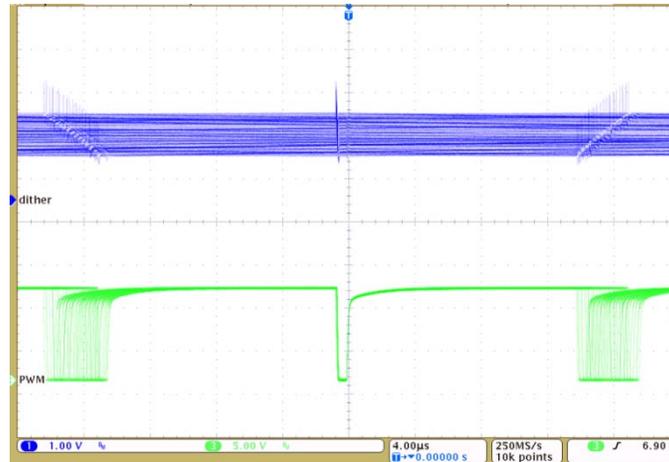


Figure 6. PWM signal of the UCC28180 with dithering added

Figures 7 to 9 show the frequency is varying above and below the 65kHz center frequency.

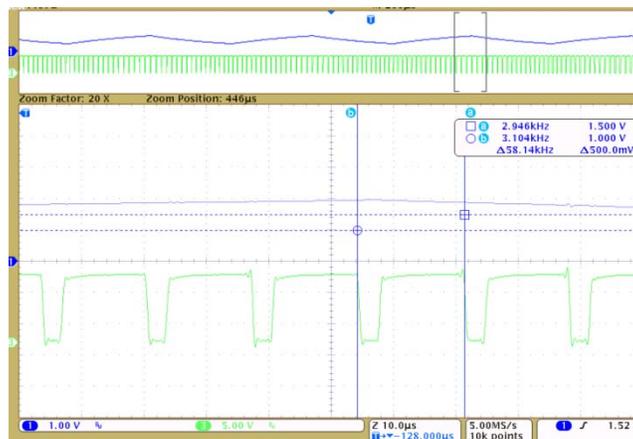


Figure 7. PWM signal of the UCC28180 with dithering added (minimum frequency is 58kHz)

CH3 = PWM signal of UCC28180, CH1 = voltage of C1

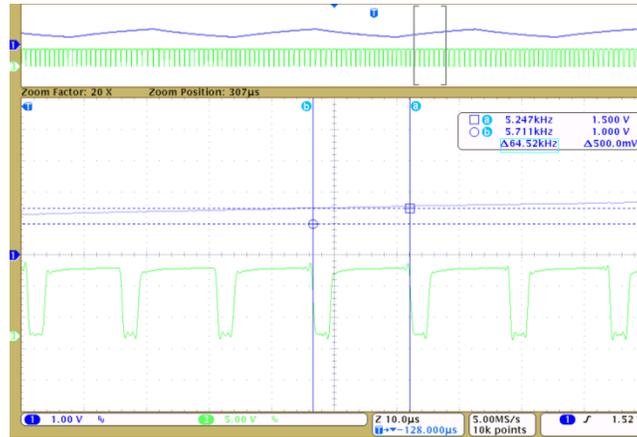


Figure 8. PWM signal of the UCC28180 with dithering added (central frequency is 65kHz)

CH3 = PWM signal of UCC28180, CH1 = voltage of C1

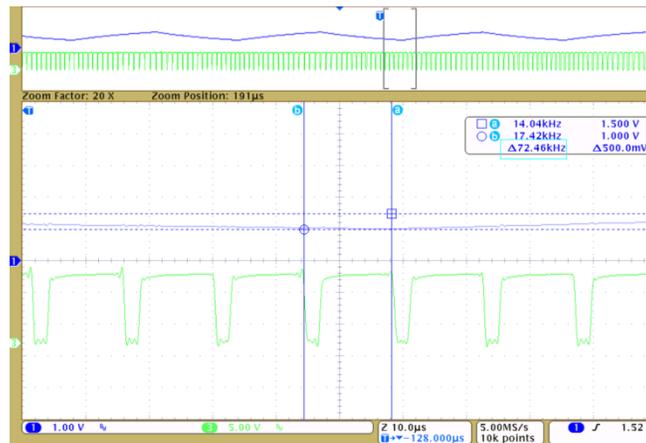


Figure 9. PWM signal of the UCC28180 with dithering added (maximum frequency is 72.5kHz)

CH3 = PWM signal of UCC28180, CH1 = voltage of C1

6. System performance with dithering circuit

6.1 PFC ramp up with dithering circuit

CH1 = voltage of C1, CH2=lin, CH3=PWM signal of UCC28180, CH4=Vout of PFC


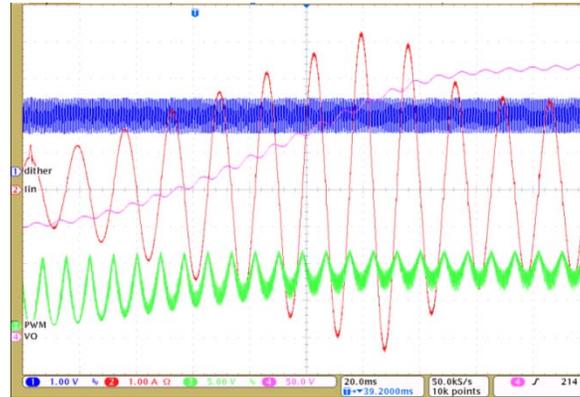


Figure 10. Ramp up with dithering circuit under $V_{in}=110V_{ac}/60Hz$, $380V \times 0.4A$ load

6.2 THD comparison with dithering to without dithering

	Vout	Iout	With dithering THD	without dithering THD
110V/60Hz	380V	0.2A	5.90%	5%
		0.4A	3.90%	3.43%
230V/50Hz	380V	0.2A	19.58%	18.90%
		0.4A	6.04%	5.50%

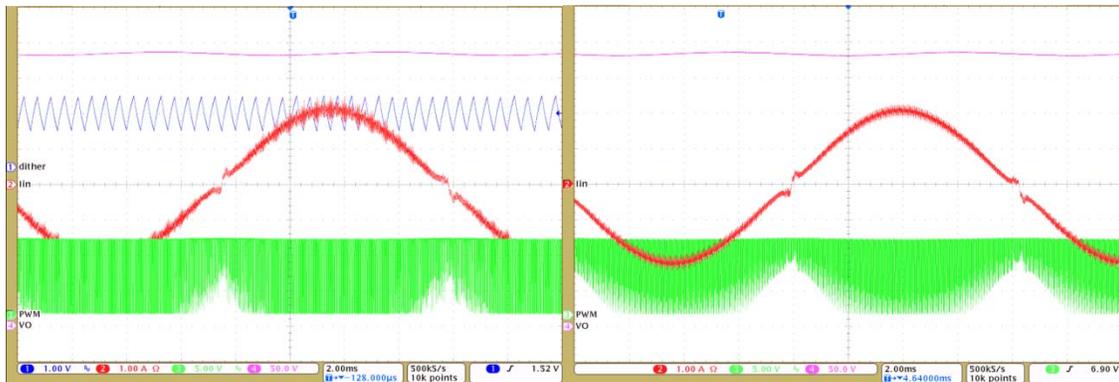

a. $V_{in}=110V_{ac}/60Hz$, $380V \times 0.4A$ load with dithering circuit b. $V_{in}=110V_{ac}/60Hz$, $380V \times 0.4A$ load without dithering circuit

Figure 11. Input current with and without dithering circuit

The system performance is not changed a lot with frequency dithering circuit. Ramp up is not changed with frequency dithering circuit, iTHD is a litter worse, but still good.

7. Conclusions

The frequency dithering technique is used in industry to reduce EMI. This Application Note shows how to design a circuit using the TLV3201 comparator to dither the switching frequency of a UCC28180 PFC controller. It has been seen that with just a few simple components, the current out of the FREQ pin of the controller can be varied to spread the frequency spectrum of converter, which in turn will spread the EMI emissions to lower the narrowband energy amplitude for EMC/I compliance.

References

1. *“PFC Pre-Regulator Frequency Dithering Circuit”, Mike O’loughlin, Texas Instruments’ Literature No. SLUA424A, May 2007*
2. *“Frequency Dithering With the UCC28950 and TLV3201”, John Stevens, Texas Instruments’ Literature No. SLUA646, May 2012*

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com