

Design of a Low Cost, 45W Flasher with Short Circuit Protection Using LM2902 (Quad Op-Amp) and CSD18534

Gitesh Bhagwat

ABSTRACT

This Application note presents the design of a low cost, flasher circuit with short circuit protection. The design incorporates the entire recommended design feature set for two wheeler flashers and includes - low/high voltage operation, half load frequency doubling, and short circuit protection.

A circuit simulation and reference schematic are also provided.

Topic	Page
1 Introduction	2
2 Flasher Specifications	2
3 Design Using LM2902 (Quad Op-Amp) and CSD18534	2
4 Operation	3
5 Test Results	5
6 Conclusion	10
7 References	10

1 Introduction

Automobiles utilize flashers for turn indications. Traditionally such control has been through electromechanical devices. However, the same functionality can be implemented using electronics at a fraction of the cost.

This design proposes such a scheme, which can be used for a load of 45 W.

2 Flasher Specifications

Table 1. Specifications

Sl. No.	SPECIFICATIONS	
1	Operating Voltage	9 V to 16 V
2	Flash Rate	85 c/m \pm 10 c/m at 12.8 V
3	On time Duty Ratio	35% to 60% at 12.8 V
4	Starting Time	<1 sec.
5	Indication of single Bulb Failure	Flashing Frequency Doubles at 21 W (single bulb load)

3 Design Using LM2902 (Quad Op-Amp) and CSD18534

Figure 1 shows the schematic for the flasher design.

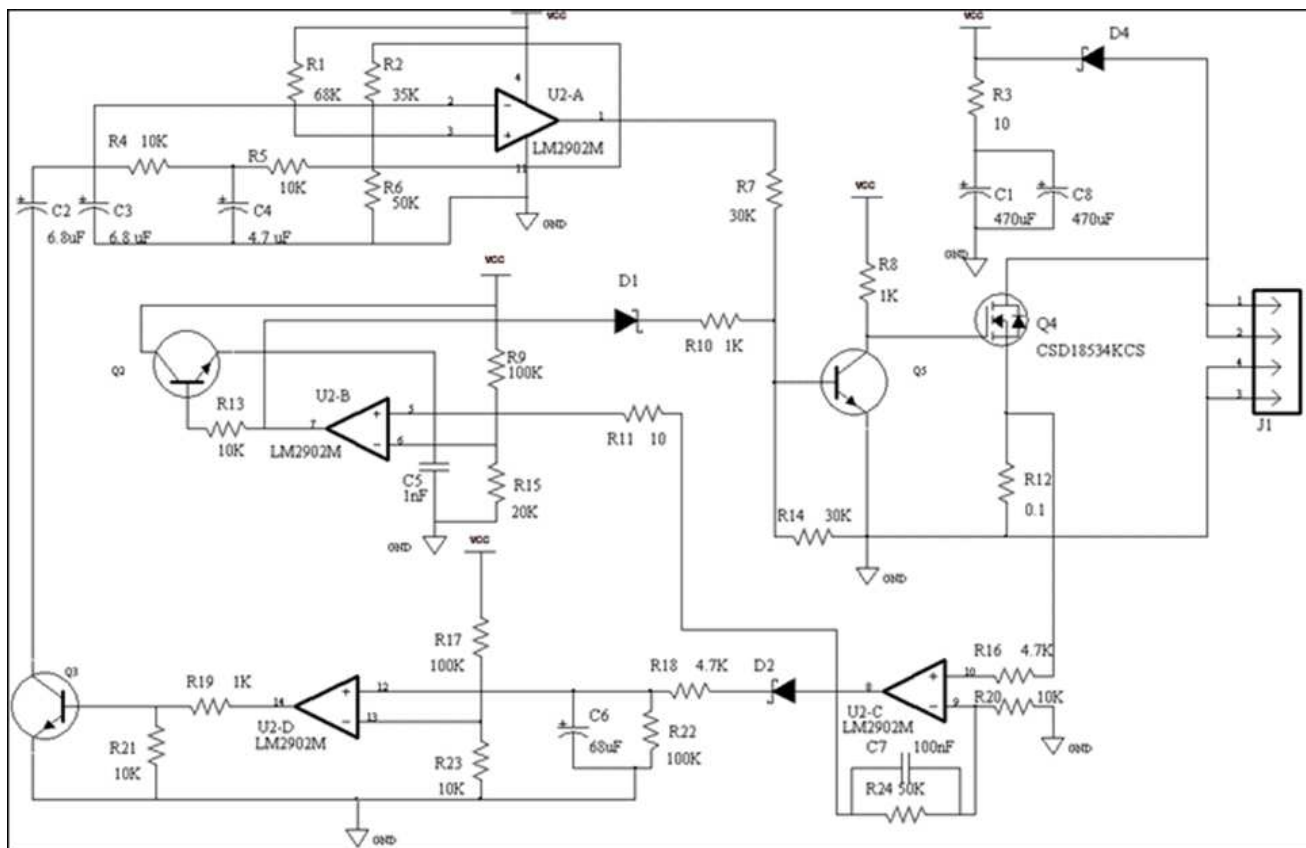


Figure 1. Flasher Schematic

4 Operation

The design of the flasher can be divided into three main segments:

4.1 Oscillator

The Op-amp U2-A acts as an oscillator triggering transistor Q5. This in turn triggers MOSFET Q4. The frequency of oscillation is set to about 85 c/m as required by the specifications.

4.2 Frequency Doubling Circuit

The Op-amps U2-C (Current Sensing Amplifier) and U2-D (Comparator) form a frequency doubling circuit. U2-C senses the load current across resistor R12, and amplifies it by a factor of 6.

U2-D then compares this amplified voltage with a threshold set by resistors R17 and R23.

4.2.1 Full Load Operation

As long as the amplified sensed voltage is higher than the threshold level, output of the comparator is driven high which keeps the transistor Q3 turned on. This transistor, when turned on, brings the capacitor C2 into action by connecting it to ground.

Thus the effective capacitance seen by the U2-A oscillator is approximately a parallel combination of C2 and C3. It is for this combination that the oscillation frequency is set to 85c/m.

4.2.2 Half Load Operation

When the load is halved (failure of one of the bulbs), the sensed and amplified voltage provided by U2-C falls below the threshold set for U2-D. The output of U2-D comparator goes low thereby turning off the transistor Q3. This disconnects capacitor C2.

Now, the U2-A oscillator sees only C3 which is approximately half of the parallel combination of C2 and C3. This results in doubling of the oscillation frequency.


4.3 Short Circuit Protection

The U2-B is another comparator which is used for implementing short circuit protection.

When the output of U2-C exceeds the threshold set by R9 and R15, the output of U2-B goes high. The transistor Q2 latches this high output. The diode D1 provides a unidirectional path for this high output to latch Q6 which in turn latches off MOSFET Q4. This latching action is reversed only by resetting the circuit (disconnecting V_{CC}).

Capacitor C5 connected on the positive terminal of U2-B, introduces a delay in the triggering of U2-B. This is used to avoid false triggering due to high inrush current during cold start. [Figure 2](#) shows the worst case cold start condition with 12.8V battery voltage. The circuit starts up within 1 second and avoids false detection of the initial current spike as a short circuit. The capacitor C5 takes care of the same.

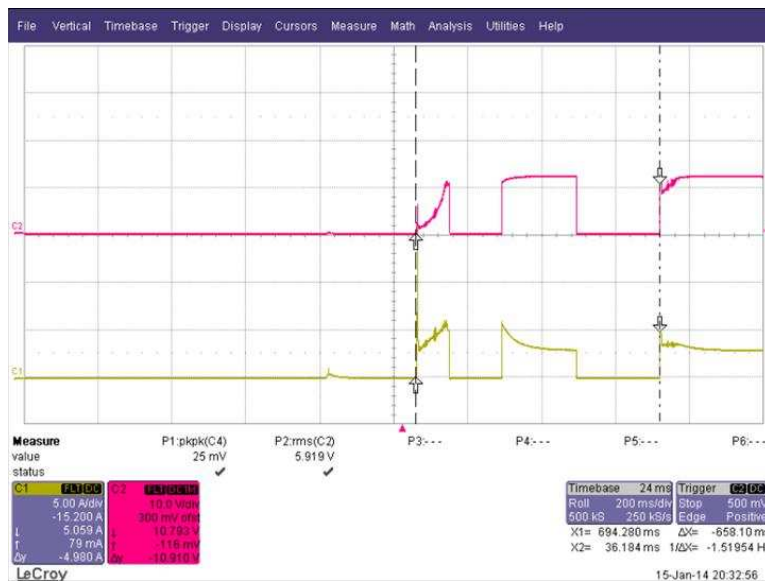The start up time is measured to be 658 ms.



Startup time: 658 ms

Figure 2. Worst Case Cold Start Condition

The design is first simulated in TINA software to fine tune the oscillator, frequency doubler and short circuit protection components. Figure 3. shows a simulation of the same using LM324 as the quad op-amp.

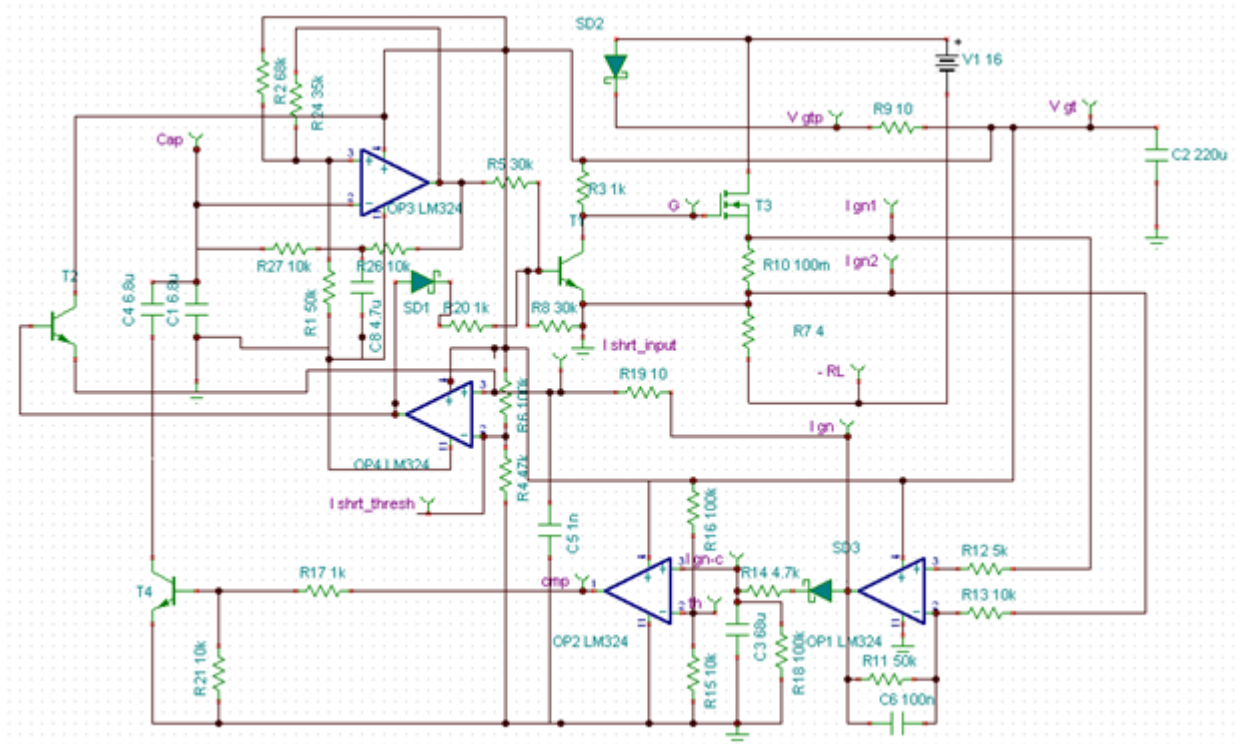


Figure 3. Circuit Simulation in TINA

5 Test Results

Test results for the circuit are divided into two categories: [Operating Voltage](#) and [Short Circuit Test](#).


5.1 Operating Voltage

Operating Voltage	Load
12.8 V	21 W
12.8 V	45 W
9 V	21 W
9 V	45 W
16 V	21 W
16 V	45 W

5.2 Short Circuit Test

Figure 12 shows the waveform of load current in the event of a short circuit.

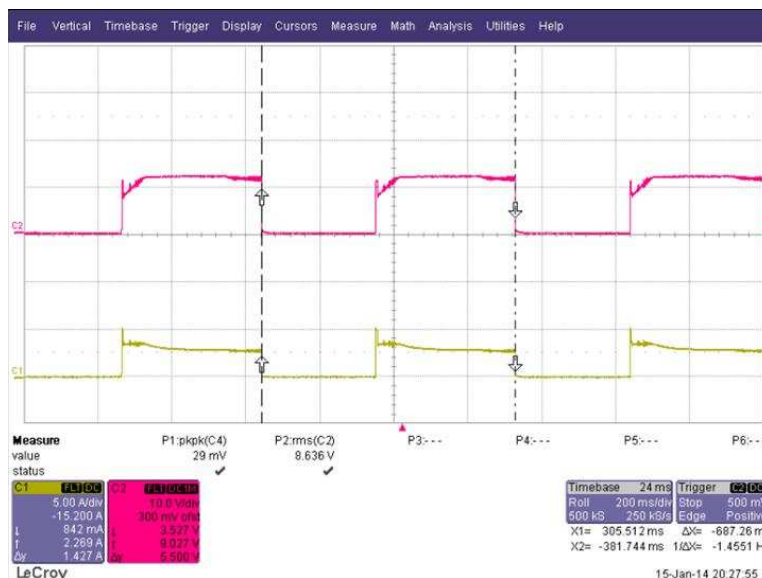Note: In all the measured waveforms that follow, Ch1 (Yellow) is the load current and Ch2 (Pink) is the voltage across the load.



$V_{IN} = 12.8 \text{ V}$

Load = 45 W

Time Period = 687 ms

Frequency = 87 Cycles/min

Figure 4.




$V_{IN} = 12.8 \text{ V}$

Load = 45 W

On Time = 377 ms

Duty Cycle = 55%

Figure 5.

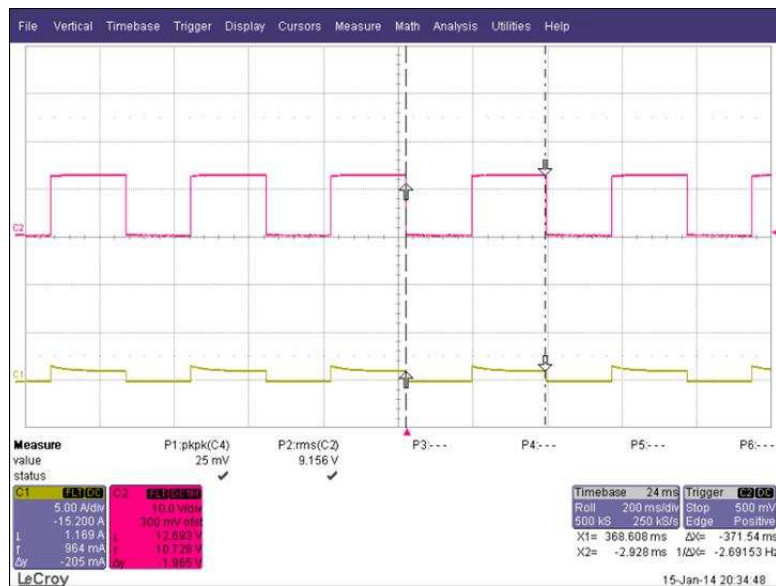


$V_{IN} = 12.8 \text{ V}$

Load = 21 W

Time Period = 371 ms

Frequency = 162 Cycles/min

Figure 6.

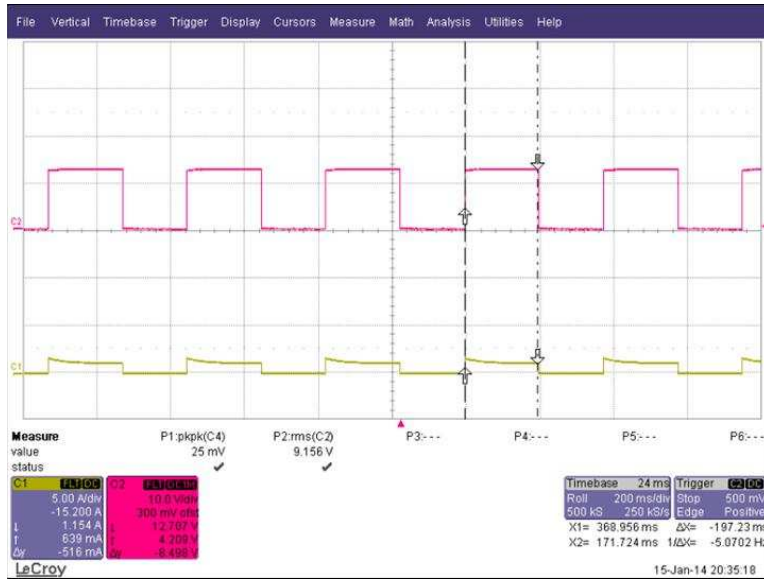

$V_{IN} = 12.8 \text{ V}$

Load = 21 W

On Time = 197 ms

Duty Cycle = 53%


Figure 7.



$V_{IN} = 9 \text{ V}$

Load = 45 W

Figure 8.

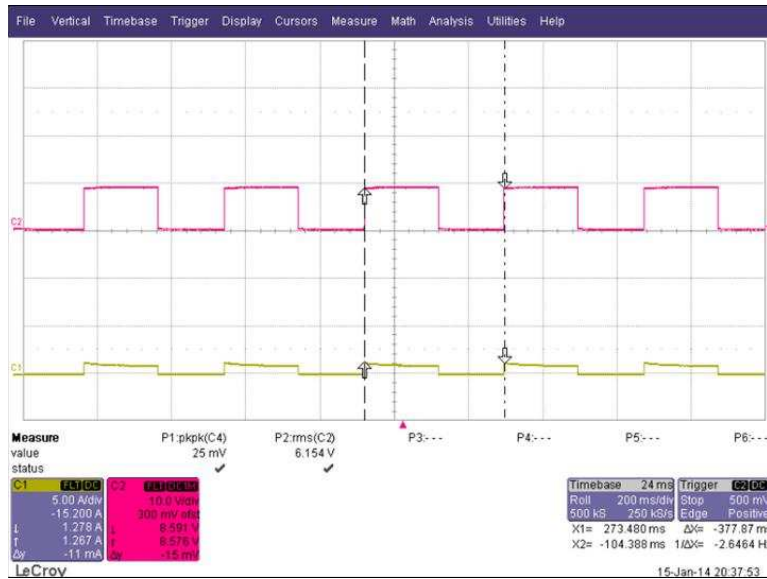

$V_{IN} = 9\text{ V}$

Load = 21 W


Figure 9.



$V_{IN} = 16\text{ V}$

Load = 45 W


Figure 10.

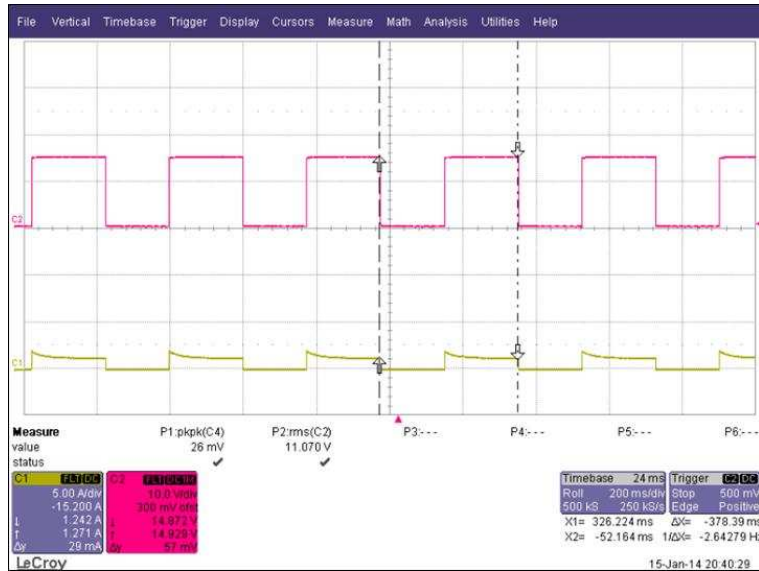

$V_{IN} = 16\text{ V}$

Load = 21 W

Figure 11.

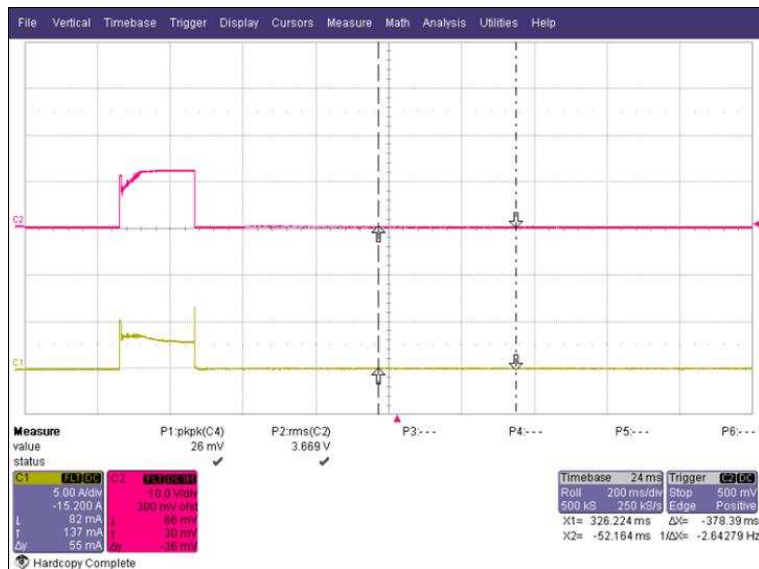

$V_{IN} = 12.8\text{ V}$

Load = 45 W (Before Being Shorted)

Figure 12. Short Circuit Test

6 Conclusion

The design, simulation, and schematic of a low cost flasher have been presented. The design has been tested for all the required specifications which include short circuit protection, and bulb failure detection among others.

7 References

1. LM2902 datasheet: <http://www.ti.com/product/lm2902>
2. CSD18534 datasheet: <http://www.ti.com/product/csd18534kcs>

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com