

# Tips for successful power-up of today's high-performance FPGAs

By Jeff Falin, *Applications, Power Management* (Email: j-falin1@ti.com),  
and Landa Pham, *Marketing, Power Management* (Email: landa@ti.com)

## Introduction

A major issue facing designers of FPGA-based systems is achieving a clean power-up. This article explains FPGA power requirements and the causes of their power-up problems. Then it provides a strategy for powering FPGAs and offers guidance on selecting the appropriate point-of-load dc/dc converter for each power rail.


## The requirements

Most FPGA manufacturers require the core voltage ( $V_{CORE}$ ), and possibly the I/O ( $V_{IO}$ ) or other voltage rails, to ramp up monotonically to a certain voltage with  $\pm 5\%$  steady-state tolerance, at a rate between  $t_{min}/V_{CORE}$  and  $t_{max}/V_{CORE}$  as shown in Figure 1.

The primary reason for the monotonic rise is either an internal power-on-reset (POR) circuit or an external supervisory reset chip that is used to enable certain sensitive analog circuitry, such as a phase-lock loop (PLL) controlled by a voltage-controlled oscillator (VCO). For example, if the voltage were to rise above the POR threshold, then dip below the trip point (outside the POR's hysteresis range) and rise again, the VCO would change frequencies and/or phase, causing the PLL to fall out of phase and lose synchronization.

As shown in Figure 1, further complicating an FPGA power rail's monotonic ramp-up requirement is an inescapable surge current at startup. This surge current,  $I_{CORE_{max}}$ , which consists of capacitance charging current and the FPGA start-up current, can be much greater than the steady-state current,  $I_{CORE_{SS}}$ . Each power rail of an FPGA has a minimum amount of bypass/decoupling capacitance that is used to minimize voltage troughs during load transient steps. This decoupling capacitance is usually on the order of several hundred microfarads. Using  $i_c = C dv/dt$ , we can easily see that, depending on the speed at which the converter is attempting to ramp the rail voltage, the start-up current could be on the order of amperes. In addition, FPGA manufacturers specify minimum in-rush current requirements in the ampere range for some of their devices. These in-rush currents are needed not only to charge the capacitances of the millions of internal components of the FPGA but also to momentarily supply current through a low resistance path to ground created by, for example, stacked complementary transistors that are both on.

Figure 1. Voltage and current start-up profile

 

So, during startup, the power rail's point-of-load dc/dc converter must simultaneously be able to supply a large in-rush current and to maintain a monotonically ramping output voltage with a certain  $dv/dt$ . Therefore, in addition to other components it is powering, the converter's input power supply must be capable of supplying large load currents (load transients) for short periods of time. Since these types of power supplies with low source/output impedance and fast response times are usually expensive, more often a less expensive, lower-current, slower supply is chosen; and decoupling capacitors are added to its output to lower its output impedance. Unfortunately, simply adding more capacitance to such a supply can make its response time even worse and can further complicate the ramp time and surge-current issue.

### The simplest dc/dc converter: The linear regulator

Interestingly, the simplest of dc/dc converters, the linear regulator, can cause the most problems during powering of the core or I/O voltage rails of FPGAs. Based on the setup shown in Figure 2, Figures 3 and 4 illustrate this point. In Figure 2, a typical bench power supply is followed by a linear regulator to power the  $V_{CCO}$  rail of an FPGA that has a specified minimum surge current of 1.5 A (including in-rush current due to charging capacitors).


Figure 3 shows the results of powering the FPGA from Figure 2 with a 3-A current-limited linear regulator and a 5-A current-limited lab supply.

One might assume that simply using a linear regulator with a higher current limit would solve the problem. However, Figure 4 shows that this is not the case when a


9-A current-limited linear regulator, the same 5-A current-limited lab supply, and an FPGA with a specified minimum surge current of 700 mA are used.

Like most linear regulators, these regulators turn on hard at startup and try to provide a regulated voltage within a few hundred microseconds. The regulators quickly reach their current limit and begin to operate like a constant-current source at that current limit. However, the current surge depletes the lab supply's output capacitor quicker than the supply can replenish it. The result is that the input rail falls below the linear regulator's undervoltage lockout (UVLO) circuit. This cycle could repeat indefinitely until the input power rail incrementally increases to a point where the linear regulator does not shut down. Surprisingly, one solution to this particular problem is to


**Figure 2. Linear regulator powering an FPGA**

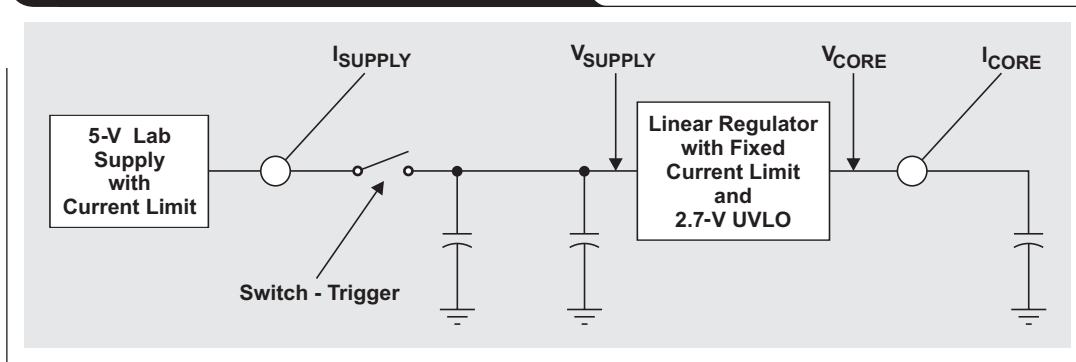

**Figure 3. Start-up profile of a 3-A current-limited linear regulator**

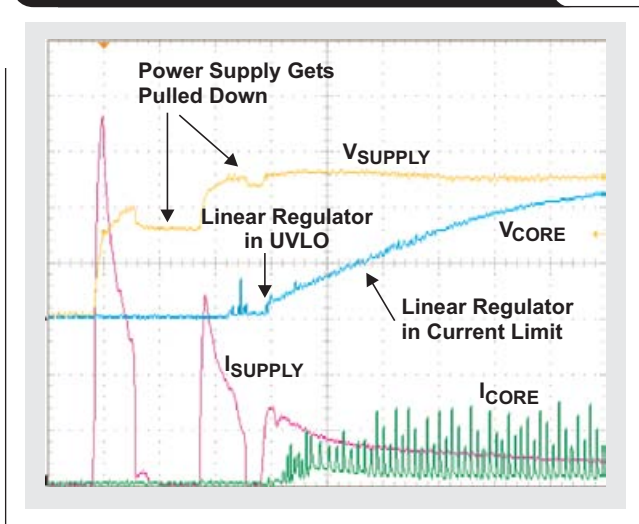

**Figure 4. Start-up profile of a 9-A current-limited linear regulator**

 

use a linear regulator with a lower current limit and possibly to increase the input power supply's decoupling capacitance. However, soft starting is the best solution.

### Soft start to the rescue

System designers seem to have fewer FPGA start-up problems when using switching regulators instead of linear regulators (assuming that the switching regulator feedback loop has been accurately stabilized). Why is this? The primary reason is that almost all switching regulators have built-in soft-start circuitry that minimizes their input and therefore their output surge currents at startup while providing a monotonic voltage ramp. Figure 5 shows the results of powering the same FPGA from Figure 2 with a bench power supply having a  $dv/dt$  of 2 V/ms.

The FPGA in-rush current is significantly reduced when the rail voltage ramps slowly. Most FPGA datasheets specify a minimum and maximum power rail ramp-up time. Therefore, using a point-of-load converter solution that includes ramp-time control is the safest way to power an FPGA.

### Why use sequencing?

Most FPGAs do not require sequencing of their power rails; however, FPGA datasheets may specify the amount of time the rails can tolerate a specific voltage difference. Some datasheets state that powering up one rail before the other will minimize in-rush current at startup. Regardless of an explicit requirement, sequentially ramping up power rails one after another, as shown in Figure 6, is recommended if for no other reason than to minimize the demand on the system power supply.

$V_{CORE}$  is usually powered up before  $V_{IO}$ . Sequential sequencing is the easiest to implement with the output of the first rail, if the voltage is high enough, or with a supervisory circuit to control the enable pin of the second rail, and so on. Most power ICs have active-high enable signals, and many have integrated supervisory (sometimes called "Power Good" or "Power OK") signals.

In some cases it may be preferable to ramp up all rails simultaneously as shown in Figure 7. Simultaneous sequencing is theoretically the most ideal form of sequencing. It ensures short-term and long-term reliability for powering the IC, since all power rails are at the same voltage during startup; however, it typically requires external circuitry. Some power IC manufacturers are providing power ICs with integrated simultaneous start-up circuitry.

Figure 5. Bench supply powering an FPGA

 


Figure 6. Sequential sequencing


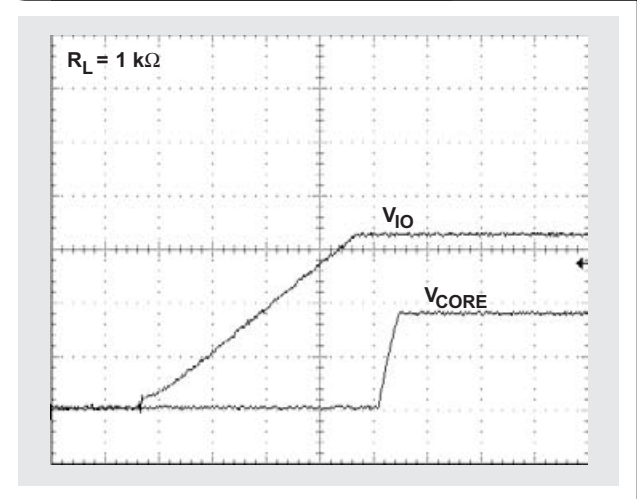


Figure 7. Simultaneous sequencing

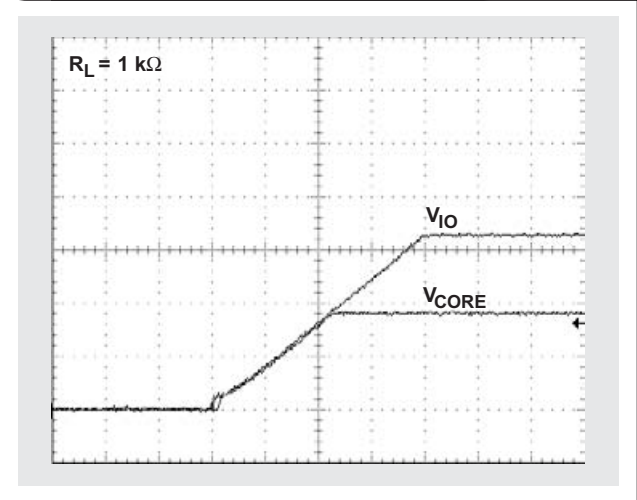

### Most reliable FPGA power-up strategy

Figure 8 shows a robust FPGA power management system that addresses the previously summarized power-up requirements and start-up issues. Incorporating both soft-start and sequential sequencing, this methodology is especially useful when the system power supply capabilities either are unknown or are being taxed by other components in the system.


The supply voltage supervisor (SVS) on the input rail prevents the  $V_{CORE}$  converter from turning on until the input rail is up and its input capacitors are fully charged. This reduces the chances of the in-rush current at startup from pulling down the input rail and tripping the UVLO of the  $V_{CORE}$  converter, as seen in Figure 3. The SVS on the  $V_{CORE}$  rail may be integrated into the converter. Some type of SVS circuitry is most likely needed since the  $V_{CORE}$  voltage is typically too low to drive the enable signal of the  $V_{IO1}$  supply directly. Soft starting one or more of the higher current rails further reduces the chances that start-up problems will occur.

The next design step is determining which point-of-load converter to use for each required rail. This decision depends on a number of factors, including the input supply voltage; the FPGA voltage rail and its tolerance; acceptable output voltage noise/ripple; the steady-state current; expected load transients; system size; and, of course, cost.

### Which dc/dc converter?

The load current and the voltage difference between the input supply and FPGA power rail determine which dc/dc converter to use. Today's IC process node allows for FPGAs, like the Spartan®-3 line from Xilinx®, to operate with core voltages at 1.2 V or less. Depending on the configuration, they may require greater than 1 A of steady-state current. Meanwhile, input power supply rails have stayed at 3.3 or 5 V to power certain I/O peripherals. So, assuming that the system designer wants to use a low-cost linear regulator to derive the  $V_{CORE}$  voltage directly from a 5-V rail, the regulator needs to dissipate  $(5 - 1.2)V \times 1 A = 3.8 W$ . However,


**Figure 8. Robust FPGA power management methodology**

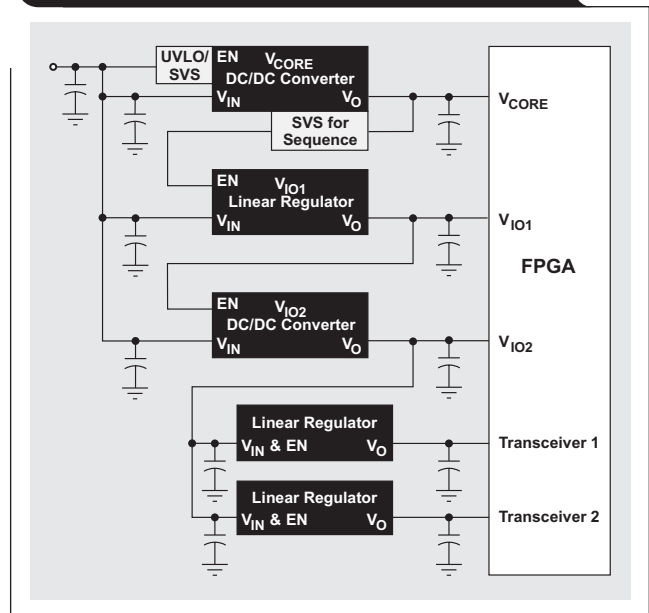

even the largest packaged linear regulator on the market cannot handle more than about 3 W without additional air-flow or external heat-sinking. Therefore, step-down (buck) switching converters, whether with integrated FETs (TPS54610), with external FETs (TPS40003, TPS64203), or in module form (PTH05050), with their higher efficiency and therefore better power dissipation, are the best solution for high-current but low-value  $V_{CORE}$  voltages.

For lower-current  $V_{CORE}$  rails or  $V_{IO}$  above 2.0 V or so, linear regulators should still be considered for their advantages, including simplicity, small size, and low cost. Because very few linear regulators in today's market offer integrated soft start, they suffer from the surge-current problems described earlier. Adding the external circuitry shown in Figure 9 implements soft starting and eliminates these surge-current problems.

**Figure 9. Linear regulator with a PMOS FET for soft start**

 

In Figure 9,  $V_{CORE}$  drives the source of the PMOS FET. Choosing a FET with low on-resistance is critical to ensure that there is little voltage drop across the FET at maximum load current. See Reference 1 for further information.

Due to their low-noise performance, linear regulators are the recommended solution for powering analog rails such as PLL, Xilinx's Virtex-II Pro™ RocketIO™ transceiver, or Stratix™ GX transceiver supplies from Altera®. Since these rails are typically low-current, power dissipation is not an issue.

### Decoupling capacitors


Since FPGAs are digital devices, they have potentially large load-current transient spikes. Most FPGA manufacturers provide guidance to the system designer in selecting the decoupling capacitors for each power rail to minimize load transient effects, such as the power rail being pulled below the -5% tolerance. Figure 10 shows the various sources of steady-state and transient currents on a power rail.

Various "fast-transient-response" point-of-load converters are available. It is generally recommended that a point-of-load converter with a fast transient response be used on fast-switching power rails. Most linear regulators use their output capacitance to set the dominant pole of their feedback loop so that they remain stable with large capacitive loads. However, most switching converters that were optimized for minimal output ripple and/or fast transient response have feedback loops that were compensated to operate within a bounded range of output capacitance and related ESR. So, when stabilizing the feedback loop of the point-of-load switching converter, the system designer must include the decoupling capacitors as part of the converter's output capacitance.

### Conclusion

The secret to successful power-up of FPGAs is to use soft starting and sequencing. The amount of load current and the related power dissipation in the point-of-load converter are the determining factors for choosing a dc/dc converter. Linear regulators are appropriate for higher FPGA core

**Figure 10. Sources of load transient currents**

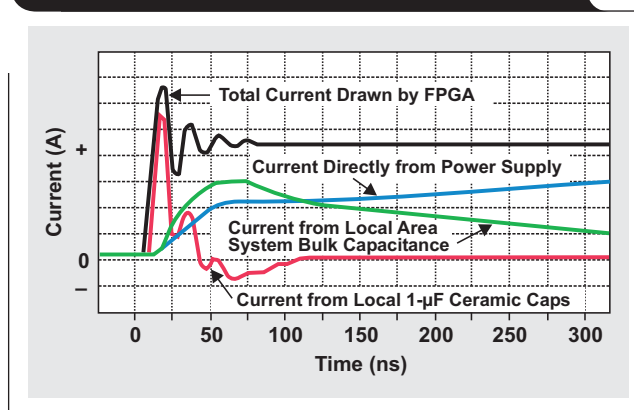

voltages but require additional soft-start circuitry. Lower core voltages require switching regulators due to power dissipation limitations in linear regulators. Switching regulators typically have built-in soft start and do not require additional circuitry.

### Reference

For more information related to this article, you can download an Acrobat Reader file at [www-s.ti.com/sc/techlit/litnumber](http://www-s.ti.com/sc/techlit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. Jeff Falin, "Monotonic, Inrush Current Limited Start-Up for Linear Regulators," Application Report . . . . .	slva156

### Related Web sites

[analog.ti.com](http://analog.ti.com)  
[www.ti.com/xilinxfpga](http://www.ti.com/xilinxfpga)  
[www.ti.com/alterafpga](http://www.ti.com/alterafpga)  
[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)  
 Replace *partnumber* with PTH05050, TPS40003, TPS54610 or TPS64203



## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

## TI Worldwide Technical Support

### Internet

**TI Semiconductor Product Information Center Home Page**  
[support.ti.com](http://support.ti.com)

**TI Semiconductor KnowledgeBase Home Page**  
[support.ti.com/sc/knowledgebase](http://support.ti.com/sc/knowledgebase)

### Product Information Centers

#### Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>		

#### Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	<a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a>		

#### Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>		
Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>		

#### Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>		<a href="mailto:ti-china@ti.com">ti-china@ti.com</a>

### C011905

**Safe Harbor Statement:** This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

**Trademarks:** Stratix is a trademark and Altera is a registered trademark of Altera Corporation. RocketIO and Virtex-II Pro are trademarks and Spartan and Xilinx are registered trademarks of Xilinx, Inc. All other trademarks are the property of their respective owners.

Mailing Address: Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated

SLYT079