

High-Performance Analog Products

Analog Applications Journal

Third Quarter, 2006



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Management	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

Contents

Introduction	4
Data Acquisition	
Using the ADS8361 with the MSP430 USI port	5
The ADS8361 high-performance, 4-port ADC supports dual-port simultaneous conversion and requires very little software overhead to interface to the MSP430 SPI port. This article describes an interface method that offers flexibility to MSP430 applications requiring multichannel, simultaneous data acquisition.	
Power Management	
TPS61059 powers white-light LED as photoflash or movie light	8
Digital camera technology has expanded to other handheld devices like cell phones and PDAs, creating the need for economical and small-footprint photo-light sources. This article presents a simple, low-voltage photoflash or movie-light circuit that uses a white-light LED and the TPS61059 boost converter.	
TPS65552A powers portable photoflash	10
Traditional circuitry for Xenon photoflash tubes has been bulky and prone to early failure due to its high voltage and high current. This article discusses the typical TPS65552A single-chip photoflash charger circuitry that can save space and dynamically respond to power-management control from the camera microcontroller.	
Single-chip bq2403x power-path manager charges battery while powering system	12
Many portable devices must operate without interruption when connected to a battery charger. The unique requirements of the widely adopted lithium-ion battery make the bq2403x charger ideal as a dynamic power-path manager. This article explores some of the power-management capabilities of this single-chip charger.	
Complete battery-pack design for one- or two-cell portable applications	14
Accurately reporting battery capacity is a growing issue in today's portable devices. This article describes the benefits of using the bq2650x and bq27x00 gas-gauge ICs to estimate battery capacity over a broad range of application power levels. Typical one- and two-cell gas-gauge solutions are included along with a solution for battery-pack authentication.	
Interface (Data Transmission)	
Improved CAN network security with TI's SN65HVD1050 transceiver	17
The typical CAN application environment places a heavy demand on network interface devices. This article describes features of the SN65HVD1050 transceiver that allow it to achieve EM immunity, low EM emissions, noise rejection, ESD protection, fault tolerance, and protection during hot plugging or power cycling.	
Index of Articles	20
TI Worldwide Technical Support	23

To view past issues of the
***Analog Applications Journal*, visit the Web site**
www.ti.com/aaaj

Introduction

Analog Applications Journal is a collection of analog application articles designed to give readers a basic understanding of TI products and to provide simple but practical examples for typical applications. Written not only for design engineers but also for engineering managers, technicians, system designers and marketing and sales personnel, the book emphasizes general application concepts over lengthy mathematical analyses.

These applications are not intended as “how-to” instructions for specific circuits but as examples of how devices could be used to solve specific design requirements. Readers will find tutorial information as well as practical engineering solutions on components from the following categories:

- Data Acquisition
- Power Management
- Interface (Data Transmission)

Where applicable, readers will also find software routines and program structures. Finally, *Analog Applications Journal* includes helpful hints and rules of thumb to guide readers in preparing for their design.

Using the ADS8361 with the MSP430 USI port

By Tom Hendrick (Email: t-hendrick@ti.com)

Applications Engineer, Data Acquisition Products

Introduction

The ADS8361 is a dual, 16-bit, 500-kSPS, analog-to-digital converter (ADC) with four fully differential input channels grouped into two pairs for high-speed, simultaneous signal acquisition. Inputs to the sample-and-hold amplifiers are fully differential and are maintained differentially to the input of the ADC. This provides excellent common-mode rejection of 80 dB at 50 kHz, which is important in high-noise environments.

MSP430 devices such as the new MSP430F2013, which contain a universal serial interface (USI), can be used in a very simple and straightforward interface that requires no “glue logic” and very little software overhead. Applications that require precise timing of simultaneous data acquisition channels can use this interface to achieve desired system results.

Hardware

The hardware used to produce the timing diagrams in Figures 2 and 3 includes the eZ430-F2013 Development Tool and the ADS8361EVM.

ADS8361EVM

The ADS8361 is a member of the motor control products family of serial ADCs available from Texas Instruments (TI). The EVM provides a platform to demonstrate the functionality of the ADS8361 ADC with various TI DSPs and microcontrollers while allowing easy access to all analog and digital signals for customized end-user applications. For more information on the EVM, see Reference 1.

eZ430-F2013 Development Tool

The eZ430-F2013 is a complete MSP430 development tool including all the hardware and software necessary to evaluate the MSP430F2013. The hardware is provided in a convenient USB stick form factor. The eZ430-F2013 uses the IAR Embedded Workbench integrated development environment (IDE) to provide full emulation with the option of designing a stand-alone system or detaching the removable target board to integrate into an existing design. For more information, visit www.ti.com/ez430

Hardware interface

A simple three-wire interface is the minimum requirement to connect the eZ430-F2013 and the ADS8361EVM (see Table 1). The hardware connections are shown in Figure 1. The CLOCK, (RD + CONVST), and Serial Data A pins from the ADS8361 are connected respectively to the SCLK, MOSI, and MISO pins of the USI port. The chip select (\overline{CS}) pin is grounded because only one ADC is

Figure 1. Hardware interface block diagram

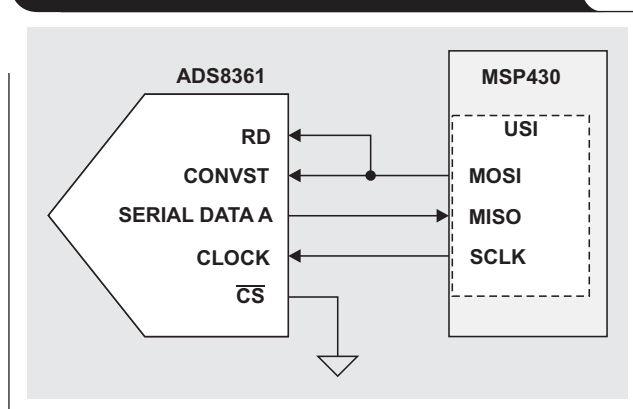


Table 1. Cable requirements

ADS8361EVM	eZ430-F2013
J2.1 — \overline{CS}^*	Optional GPIO
J2.3 — CLOCK	P1.5
J2.13 — Serial Data A	P1.7
J2.7 — (RD + CONVST)**	P1.6

* \overline{CS} can be held to ground by placing a shunt jumper from J2.1 to J2.2.
 ** (RD + CONVST) is created by placing the shunt jumper in location W2 on pins 1 and 2.

placed on the port. If more than one device is on the bus, then chip select should be controlled by any available GPIO on the MSP430 device.

Software interface

All of the software was written and compiled using the Kickstart version of IAR Embedded Workbench for the MSP430. This software is the free version of the IDE and is available for download at www.ti.com/ez430 under “TOOL SUPPORT.” The code used in these examples is available upon request.

USI settings

The USI module provides the basic functionality to support synchronous serial communication schemes. The USI includes built-in hardware functionality to ease the implementation of SPI communication. The USI module also includes interrupts to further reduce the software overhead.

USI control registers 0 and 1 (USICTL0 and USICTL1) set up the basic operation of the serial interface. The port is configured in SPI master mode by setting bits 3, 5, 6, and 7 in USICTL0. The USI counter interrupt is set in

USICTL1 to provide an efficient means of SPI communication with minimal software overhead.

The serial clock polarity, source, and speed are controlled by settings in the USI clock control register (USICKCTL). For the purposes of this article, the polarity of the clock is set to zero (dwells low), and the clock source is the SMCLK with a division factor of one.

Bit clocking and shift register configuration are controlled in the USI port by the bit settings in the USI bit count register (USICNT). The USICNT register has 5 bits that provide up to 32 SCLK cycles per transfer. Setting the USICNT to 0×13 transmits 19 serial clocks from the MSP430 to the ADS8361 on each conversion cycle. Setting the USI16B bit in the USICNT register causes the shift register to act as a 16-bit transmit/receive buffer. Transmitted data is MSB-aligned and commences with the first SCLK cycle.

Starting a conversion

Connecting the MOSI output of the USI port to both the RD and the CONVST inputs on the ADS8361 starts a conversion cycle, and the conversion results are presented on the serial data output pins of the device.

The ADS8361 will begin to output the conversion results (MSB first) on the fourth SCLK cycle. Since the shift register holds the last 16 bits of received data, the entire 16-bit conversion result is captured for further processing. The timing diagram in Figure 2 shows the entire process.

ADS8361 operating modes

The ADS8361 has four operational modes controlled by the M0 and M1 pins. The ADS8361EVM provides jumpers to statically set the operating mode. Using GPIO output on the MSP430 permits the operating mode to be controlled by the microprocessor as well.

For two-channel operation, the EVM should be configured in Mode I or II. Depending on the MSP430 being used, the user has several options on how to receive conversion results. Devices with multiple serial ports can receive data from both the Serial Data A and Serial Data B outputs of the ADS8361. This method involves setting up one port as an SPI master and the other as an SPI slave. The master SPI port would share SCLK with the slave port, and the two serial output pins would be routed to MISO and MOSI.

Two-channel simultaneous sampling

In the case of the eZ430-F2013, there is only a single serial port, which means the ADS8361 must be set in Mode II to receive conversion results from the two simultaneously sampled input channels. This mode presents both conversion results at the Serial Data A output pin (see Figure 3).

Figure 2. Complete single-channel conversion cycle


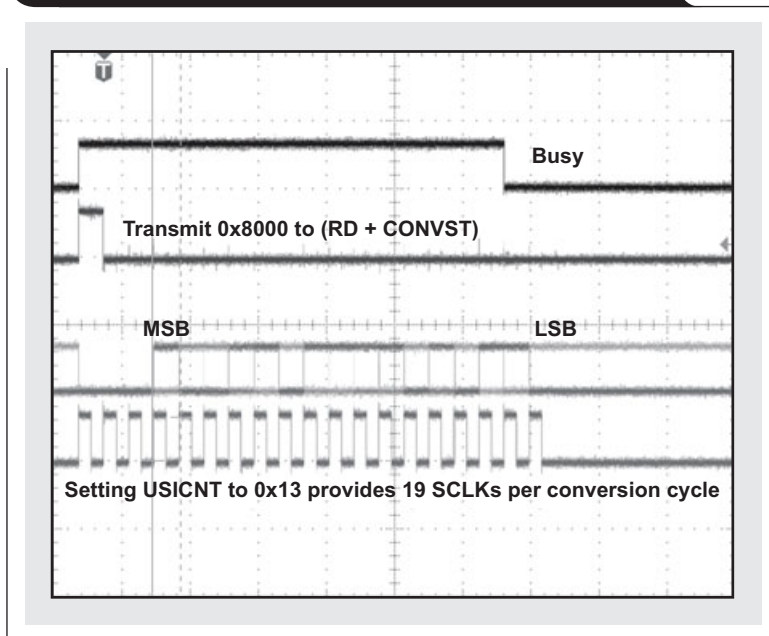


Figure 3. Complete two-channel conversion cycle

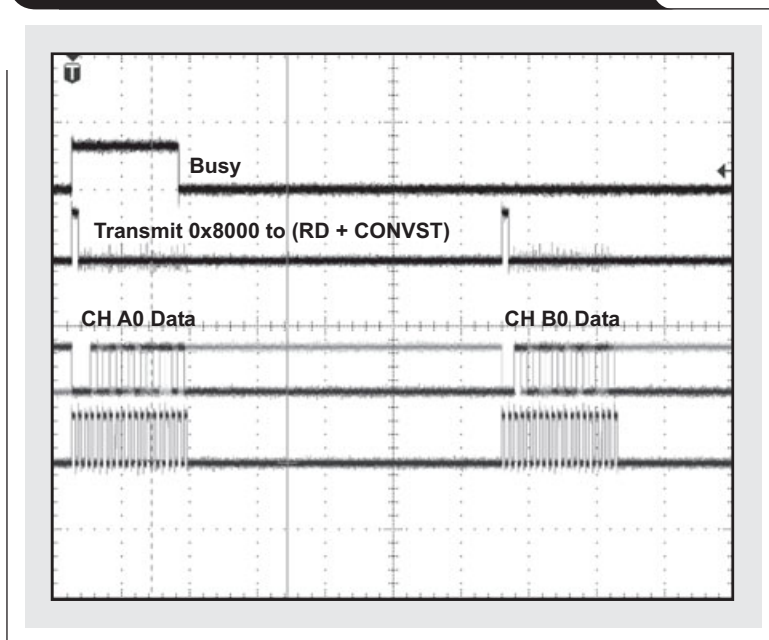

ADS8361 channel ID bits

The serial output stream of the ADS8361 also incorporates two channel ID bits so the controller can use software methods to decipher the received channel information. The first ID bit determines the channel pair, A or B. The second ID bit determines the sampled channel, 0 or 1. In Mode II operation, two of the input channels are converted and a single ID bit is included in the output data stream.

The A/B-channel ID bit is not used in this mode because the pair of inputs sampled depends on the A0 input control pin of the ADS8361. When A0 is low, the channel A0/B0 input pairs are sampled. When A0 is high, the channel A1/B1 input pairs are sampled.

The ADS8361EVM provides a jumper to statically set the input pair via the A0 pin. This too can be controlled if desired with a GPIO on the MSP430, letting the user realize up to four-channel operation—two pairs of simultaneously sampled inputs.

Four-channel sampling

Modes III and IV allow the user to realize four-channel operation of the ADS8361. Mode III provides data from the Serial Data A and B outputs. Receiving data from all four conversions in this mode would require two serial ports configured in a master/slave relationship as described previously.

Mode IV allows a single serial port to receive all four conversion results via the Serial Data A output. In this mode, both the A/B- and 0/1-channel ID bits are passed through to the conversion results. What becomes problematic in this mode when used with the eZ430-F2013 is that the ID bits are essentially lost in the shift register. It is possible to recover these bits via software, but this increases software overhead and adds unnecessary complexity.

When operating in four-channel sequential mode, the ADS8361 can be initialized in such a way that channel integrity can be maintained without the need to decipher the ID bits at all. Using available GPIO, this can be done with a simple software loop at the start of the program that actively manipulates the state of the A0, M0, and M1 inputs. An alternative is to simply ignore the first set of conversion results. The ADS8361 powers up in Mode I by default; if M0 and M1 are fixed to V_{CC} at power up, the

device will enter Mode IV operation with the second conversion cycle. This action presents channel A0 data with the third SPI transfer, followed sequentially by channels B0, A1, and B1.

Conclusion

Using the high-performance ADS8361 with the USI port of MSP430 processors is a relatively simple and straightforward task. Very little software overhead is involved; there is no need to shift or concatenate conversion results as was the case in the simple 8-bit SPI interface of the older UART port found in previous generations of the MSP430. The interface method described in this article brings a new level of flexibility to MSP430 applications that require multichannel, simultaneous data acquisition.

References

For more information related to this article, you can download an Acrobat Reader file at www-s.ti.com/sc/techlit/litnumber and replace “litnumber” with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. “ADS7861/8361 EVM User’s Guide”	slau094
2. “Dual, 500kSPS, 16-Bit, 2 + 2 Channel, Simultaneous Sampling Analog-to-Digital Converter,” ADS8361 Datasheet	sbas230
3. “MSP430x2xx Family User’s Guide”	slau144

Related Web sites

dataconverter.ti.com
www.ti.com/ez430
www.ti.com/msp430
www.ti.com/sc/device/ADS8361
www.ti.com/sc/device/MSP430F2013

TPS61059 powers white-light LED as photoflash or movie light

By Scot Lester (Email: scotlester@ti.com)


Portable Power DC/DC Applications

Manufacturers of smart phones, cell phones, and PDAs are incorporating digital camera technology into their products so they can be used as cameras as well as for their intended use. Each of these devices uses a megapixel CCD camera that generally performs poorly in low-light conditions such as indoors, on cloudy days, or in the morning or evening. To provide a photoflash function for these low-light conditions, manufacturers are starting to turn to new high-power, white-light LEDs. These LEDs output a wide light spectrum and are compact and easy to control. They operate at much lower voltages than Xenon gas-discharge tubes, which require hundreds of volts to flash. Additionally, white-light LEDs can be left on continuously to provide lighting for digital movie photography.

One challenge in using white-light LEDs is powering them with the wide input-voltage range that batteries present. A white-light LED can have a forward voltage ranging from 3.2 to 4.8 V. This falls in the middle of most battery input-voltage ranges, which means the converter needs to be able to step up or step down the input voltage to maintain the forward voltage of the LED.

The Texas Instruments (TI) TPS61058 and TPS61059 are synchronous boost converters for driving high-current LEDs for photoflash and movie-light applications. The TPS61058 can provide up to 500 mA and the TPS61059 up to 800 mA of LED current from a 3.3-V source. The TPS6105x family of boost converters has a special down mode that allows it to step down the input voltage when the input voltage is higher than the forward voltage of the LED. Thus, the TPS61058/9 can both step up and step down the input voltage, allowing these devices to drive a wide range of LEDs from a wide range of input voltages. Figure 1 shows the TPS61059 configured to provide 700 mA of current for an LED photoflash or a constant 200 mA of current for a movie light from an input battery voltage between 2.7 and 5.5 V. Two digital inputs are used to select the LED's mode of operation—off, photoflash, or movie light. The photoflash, movie-light, and soft-start current supplied by the TPS6105x are programmed by an external resistor network that allows the TPS6105x to drive a variety of high-power white-light LEDs.

Figure 1. TPS61059 configured for 700-mA LED photoflash or 200-mA LED movie light

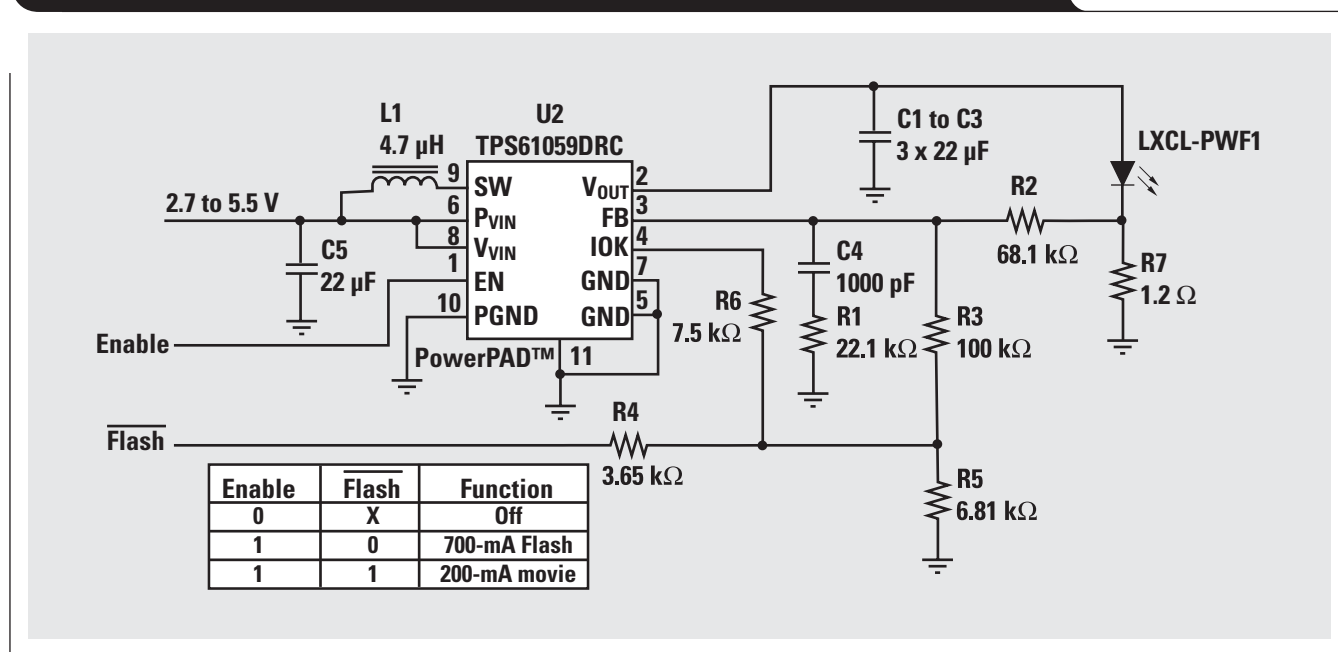

The TPS6105x achieves up to 93% efficiency in movie-light mode and up to 81% efficiency in high-current photoflash mode (see Figure 2). During shutdown, the device completely disconnects the LED from the input source to prevent draining the battery and consumes a low 100 nA of quiescent current.

Additional features are integrated-circuit protection for soft start, thermal shutdown, and open or shorted LEDs, and an integrated anti-ring power switch for low-EMI operation in noise-sensitive applications. All of this is packaged in a 10-pin QFN, which allows for a total solution size of less than 80 mm².

Reference

For more information related to this article, you can download an Acrobat Reader file at www-s.ti.com/sc/techlit/litnumber and replace "litnumber" with the **TI Lit. #** for the materials listed below.


Document Title **TI Lit. #**

1. "Synchronous Boost Converter with Down Mode High Power White LED Driver,"
 TPS61058/9 Datasheetslvs572

Related Web sites

- power.ti.com
- www.ti.com/sc/device/TPS61058
- www.ti.com/sc/device/TPS61059

Figure 2. TPS61059 LED power efficiency versus input voltage

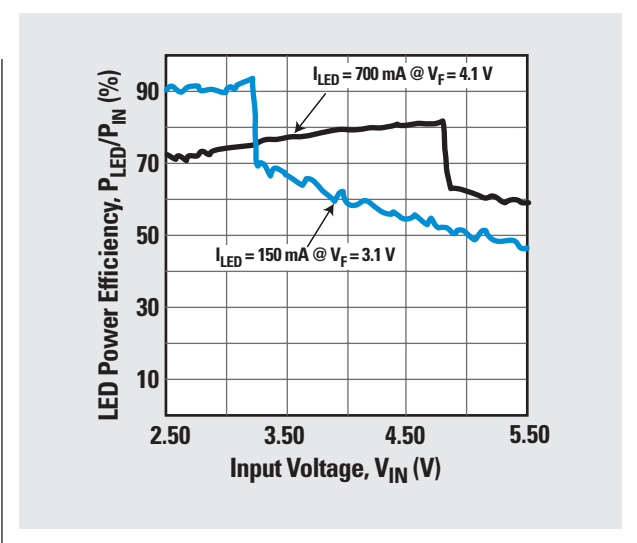

TPS65552A powers portable photoflash

By Scot Lester (Email: scotlester@ti.com)

Portable Power DC/DC Applications

Upper-end equipment for film-based or digital photography requires Xenon flash tubes to photograph in low-light conditions. Xenon flash tubes provide a burst of high-intensity light that is essential for photography of objects at a distance, moving at high speeds, or in low-light conditions. The light spectrum generated by a Xenon gas-discharge tube closely replicates that of the sun, providing very accurate color reproduction.

Xenon flash tubes require a high voltage across their electrodes to flash once a trigger signal is applied. This voltage is typically around 300 V. All of the energy needed to flash the lamp is stored in a bulk capacitor called a photoflash capacitor. Once the lamp is triggered, all of the energy stored in the photoflash capacitor is discharged through the flash tube to produce light. The stored energy in the photoflash capacitor is provided by a specialized boost converter that charges the photoflash capacitor up to 300 V from a much lower battery-input voltage. In the past, this converter was built of bulky discrete components that were difficult to incorporate into the space available in small devices such as cameras.


The Texas Instruments (TI) TPS65552A greatly simplifies and reduces the size of the photoflash charger circuit. Figure 1 shows a photoflash capacitor charger based on

this device. The TPS65552A provides all the necessary charging controls, output feedback, charge completion status, insulated gate bipolar transistor (IGBT) driver, and circuit protections necessary to implement a small, efficient photoflash charger.

The TPS65552A is based on a flyback topology. The output voltage is sensed during the off period of the internal switch, at which time the output voltage is reflected back to the input through the transformer. This eliminates the need for a bulky, high-voltage feedback network on the input and also provides electrical isolation from the input to the output. Once the output voltage reaches its target value, the TPS65552A automatically stops charging and an open-collector output goes low, thus signaling a “ready to flash” condition. This output can drive a status-indicating LED or an input to a microcontroller.

The I_PEAK pin of the TPS65552A controls the peak current that flows through the primary of the flyback transformer, T1, during each switch cycle. To adjust the capacitor charging time, the primary current can be dynamically adjusted from 0.9 to 1.8 A by changing the voltage applied to the I_PEAK pin. This feature allows a microcontroller to dynamically control the current draw of the charger for power management. For example, in a digital still camera,

Figure 1. TPS65552A photoflash capacitor charger

 

a microcontroller can reduce the charger current when a high-current zoom motor is operating, so that both the zoom motor and charger can function at the same time without exceeding the maximum current capability of the camera's battery (see Figure 2). This feature can also be used to extend battery run time. Reducing the peak currents during charging reduces the average current consumption so that a weak battery can still charge the photoflash capacitor.

Historically, the flash has been triggered with a push-button switch or a silicon-controlled rectifier (SCR). However, newer flash modes such as red-eye reduction use multiple bursts of the Xenon lamp. The lamp is triggered for a short flash that does not fully discharge the photoflash capacitor. Then, after a short delay, the lamp is retriggered for the main flash. The push button and SCR cannot reliably start and stop the lamp midflash. The IGBT is capable of handling the currents, which are typically 150 A during a flash. However, like a MOSFET, the IGBT gate requires a large current pulse to quickly turn on; so a high-current driver is required.

The TPS65552A has an integrated high-current buffer to drive the IGBT gate used in the trigger circuit. The IGBT can be driven on and off during flashes to support flash modes such as red-eye reduction or evaluated through the lens (E-TTL).

Reference

For more information related to this article, you can download an Acrobat Reader file at www-s.ti.com/sc/techlit/litnumber and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title **TI Lit. #**

1. "Integrated Photo Flash Charger and IGBT Driver," TPS65552A Datasheetslvs567


Related Web sites

power.ti.com
www.ti.com/sc/device/TPS65552A

Table 1. Typical parts list for circuit in Figure 2

DEVICE	DESIGNATOR	DESCRIPTION	MANUFACTURER
330 FW 120A	C1	Capacitor, aluminum, 120 µF, 330 VDC, ±20%	Rubycon
C3216X7R2J223KT	C2	Capacitor, ceramic, 0.022 µF, 630 V, X7R, 10%	TDK
ES1G	D1	Diode, rectifier, 1 A, 400 V	Diodes Inc.
36FT050	FL1	Flash tube, 400 V max	Xicon
SSM25G45EM	Q1	Transistor, N-channel IGBT, 450 V, 150 A	Silicon Standard
CTX16-17360	T1	Transformer, flyback, 1:10.2	Coiltronics
422-2304	T2	Transformer, trigger	Xicon

Figure 2. Complete photoflash module with power and flash management

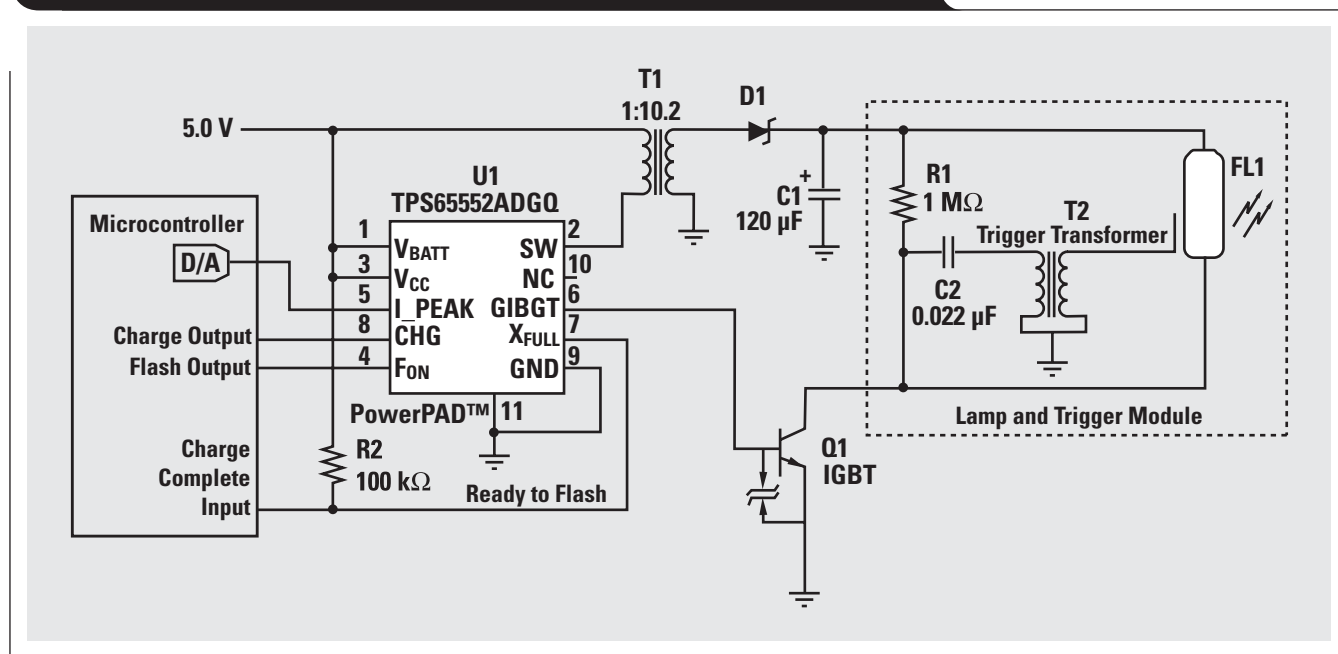

Single-chip bq2403x power-path manager charges battery while powering system

By Jinrong Qian (Email: jqian@ti.com)

Applications Manager, Battery Management Applications

The lithium-ion (Li-ion) battery is widely adopted in portable devices because of its high energy density on both a gravimetric and volumetric basis. Users of applications such as smartphones, PDAs, and MP3 players want to be able to operate the device from an input source without a battery. This requires a power architecture with two separate paths for device system power and battery charging, called “power-path management.”


Dynamic power-path-management (DPPM) battery charger

In the most commonly used battery-charging and system-power configuration, the system load is directly connected to the battery-charger output. This architecture is simple and low-cost but can cause improper charge termination and false safety-timer warnings due to ineffective control of the battery charge current.

The bq2403x family of DPPM battery chargers has a power-sharing capability of simultaneously powering the system and charging the battery. This eliminates the charge-termination and safety-timer issues, minimizes the ac adapter power rating, and improves system reliability. It also allows the system to operate while charging a deeply discharged battery.

Figure 1 is a block diagram of a simplified power-path-management battery charger. When the ac adapter is plugged in, MOSFET Q1 is used to preregulate the system bus voltage, V_{OUT} , which is higher than the maximum battery regulation voltage, V_{BAT} . This establishes a direct path from the adapter input to the system. The MOSFET Q2 is dedicated to charging the battery, so there is no interaction between the battery and the system. When a USB is present and selected, the MOSFET Q3 is fully turned on, the Q3 output provides almost the same voltage as the USB output, and the MOSFET Q2 controls the battery charging.


Figure 1. Simplified power-path-management battery charger

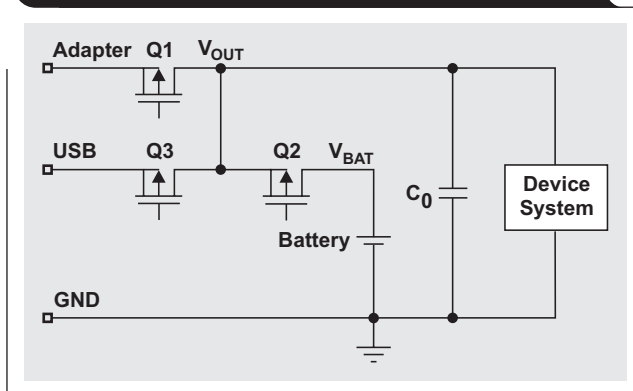

DPPM actively monitors the system bus voltage. If the system bus voltage drops to a preset value due to a limited amount of input current from the adapter or USB, the battery-charging current is reduced until the output voltage stops dropping. The DPPM control tries to reach a steady-state condition where the system gets its needed current and the battery is charged with the remaining current. Because of this, the adapter is designed based on average power from the system, not on maximum peak system power. This allows the designer to use a smaller power rating and a cheaper adapter.

Figure 2 shows a typical DPPM applications circuit. When the total current from the system and battery charger exceeds the current limit of the ac adapter or USB, the capacitors connected to the system bus start to discharge and system bus voltage begins to drop. When the system bus voltage drops to the predetermined threshold set by the DPPM pin, the charge current is reduced to prevent a system crash from overloading the ac adapter. If the system

Figure 2. DPPM battery charger

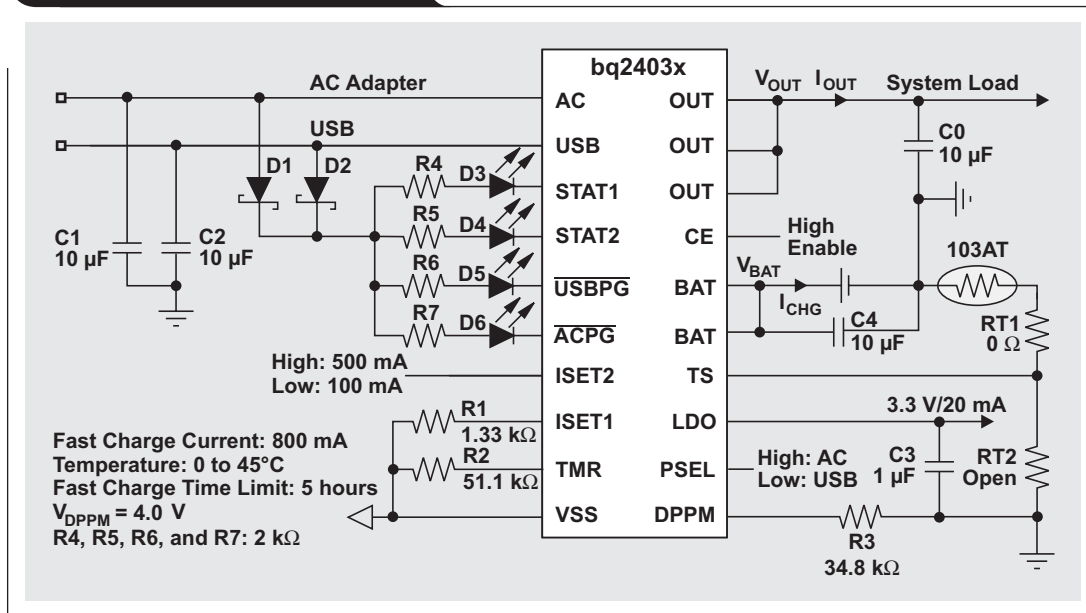

bus voltage cannot be maintained even when the charge current is reduced to 0 A, the battery will temporarily discharge and provide power to the system to avoid a system crash. This is called “battery supplement mode” and is shown in Figure 3 along with the DPPM experimental waveforms.

The DPPM voltage threshold, V_{DPPM} , is set by resistor R3 and is typically below the regulation voltage at the OUT pin to safely keep the system operating. R3 is calculated by

$$R3 = \frac{1.15 \times V_{DPPM}}{100 \mu A}$$

R1 is used to set the fast charge current and is given by


$$R1 = \frac{450 \times 2.5 V}{I_{CHG}}$$

R2 is used to set the safety-timer value. Typically the temperature qualification for allowing a Li-ion battery to be charged is between 0°C and 45°C. RT1 and RT2 are programmed for different temperature ranges.

The battery charger can select either ac or USB power as the main power source through the PSEL pin, and maximum current is also selectable through ISET2 when the USB port is selected.

Three power MOSFETs and a power controller are integrated in a thermally enhanced 3.5×4.5 -mm QFN package. A thermal regulation loop reduces the charge current to prevent the silicon temperature from getting higher than 125°C. Whenever the charge current is reduced either by active thermal regulation or by active DPPM, the safety-timer duration is automatically increased to prevent an unexpected false safety-timer warning. Charge termination is also disabled when either DPPM or the thermal

Figure 3. DPPM experimental waveforms

 

regulation loop is active. This approach prevents false charge termination.

Conclusion

DPPM reduces the battery-charging current while powering the system load when the system bus voltage drops to a predetermined threshold due to limited input current. DPPM also completely eliminates the issues of battery and system interaction such as false charge termination and false safety-timer warnings. The DPPM battery charger is ideal for power systems that simultaneously charge the battery.

Related Web sites

power.ti.com
www.ti.com/sc/device/bq2403x

Complete battery-pack design for one- or two-cell portable applications

By Michael Vega (Email: m-vega3@ti.com)

Portable Power Management Applications

Introduction

Although voltage measurement alone has been used in many portable products to approximate the remaining capacity of the battery, this method may have an error of up to 50%. The relationship between cell voltage and capacity will vary as a function of discharge rate, temperature, and cell aging. For example, a high discharge rate results in a greater voltage drop than a low discharge rate for the same depletion in capacity. Similar characteristics can be noticed when a cell is discharged at varying temperatures.

With the growing demand for products with longer run times, system designers need a more accurate solution. Using a gas-gauge IC to measure the charge that enters or leaves a battery will provide a much better estimate of battery capacity over a broad range of application power levels.

Gas-gauging principle

A gas gauge is an IC that autonomously monitors the capacity of a battery, which it reports to a processor that makes system power-management decisions. A good gas gauge requires at a minimum the means to measure battery voltage, pack temperature, and current; a microprocessor; and a proven gas-gauging algorithm.


The bq2650x and bq27x00 are complete gas gauges that have an analog-to-digital converter (ADC) for voltage and temperature measurements, and another ADC for current and charge sensing. These gas gauges also have an internal microprocessor that runs Texas Instruments (TI) gas-gauging algorithms. These algorithms compensate for self-discharge, aging, temperature, and discharge rate in lithium-ion (Li-ion) cells. The microprocessor frees the host system processor from constantly making these calculations.

The gas gauges have information such as “Remaining State of Capacity,” and the bq27x00 family provides “Run Time to Empty.” The information is available any time the host queries. It is up to the host to notify the end user of the battery information either by means of LEDs or messages displayed on a screen. Using the gas gauges is very easy, as the system processor needs only an I²C or an HDQ communication driver.

Battery-pack circuit description

Figure 1 depicts the application circuit within the battery pack. The battery pack will have at least three to four external terminals available depending on which gas-gauge IC is used.

Figure 1. Typical application circuit

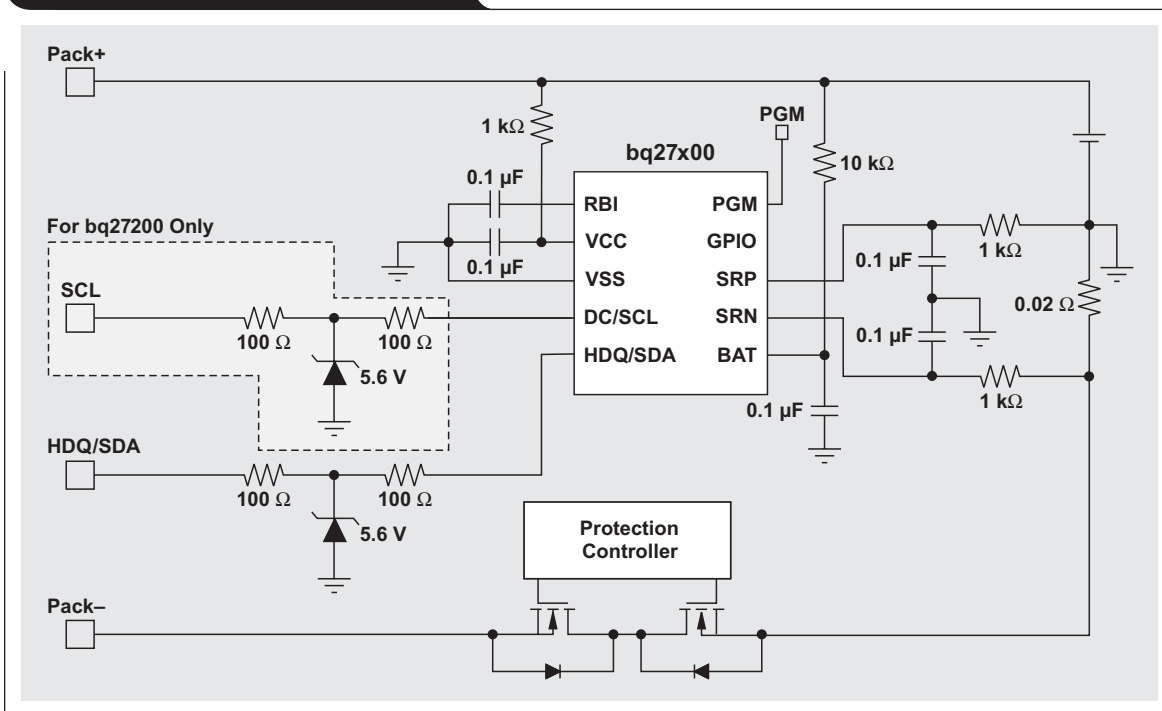

The VCC and BAT pins will tap into the cell voltage for IC power and battery-voltage measurement. A low-value sense resistor is placed at the ground end of the battery cell so that the voltage across the sense resistor can be monitored by the gas gauge's high-impedance SRP and SRN inputs. The current through the sense resistor helps determine the amount of energy that has been charged to or discharged from the battery. When selecting a sense resistor value, the designer must consider that the voltage across it should be no more than 100 mV. A resistor value that is too low may introduce errors at low currents. A board layout must ensure that the connections from SRP and SRN to the sense resistor are as close as possible to the sense resistor's ends; i.e., they are Kelvin connections.

The HDQ/SDA and SCL pins are open-drain devices that each require an external pull-up resistor. The resistor should be on the host or main application side so that the sleep function of the gas gauge is enabled whenever a battery pack is disconnected from the portable device. A recommended pull-up resistor value is 10 k Ω .


Battery-pack authentication

Rechargeable batteries for a portable device must be replaced before the life of the device expires. This has opened up a huge market for counterfeiters to supply cheap replacement batteries that may not have the safety and protection circuits required by the original equipment manufacturer.

Therefore, in addition to gas-gauging functionality, a battery pack may include an authentication feature (see Figure 2). The host challenges the battery pack, which contains an IC (TI's bq26150) that calculates a cyclic redundancy check (CRC). This CRC is based on the challenge and the CRC polynomial secretly defined within the IC. The host also calculates the CRC and compares values to determine if authentication is successful. If not, the host decides whether to try again or disallow powering of the system through the battery.

Once the battery is authenticated, the bq26150 is given a command to ensure that all communication through the data line is relayed between the host and the gas gauge.

Figure 2. Circuit with bq27000 and authentication IC

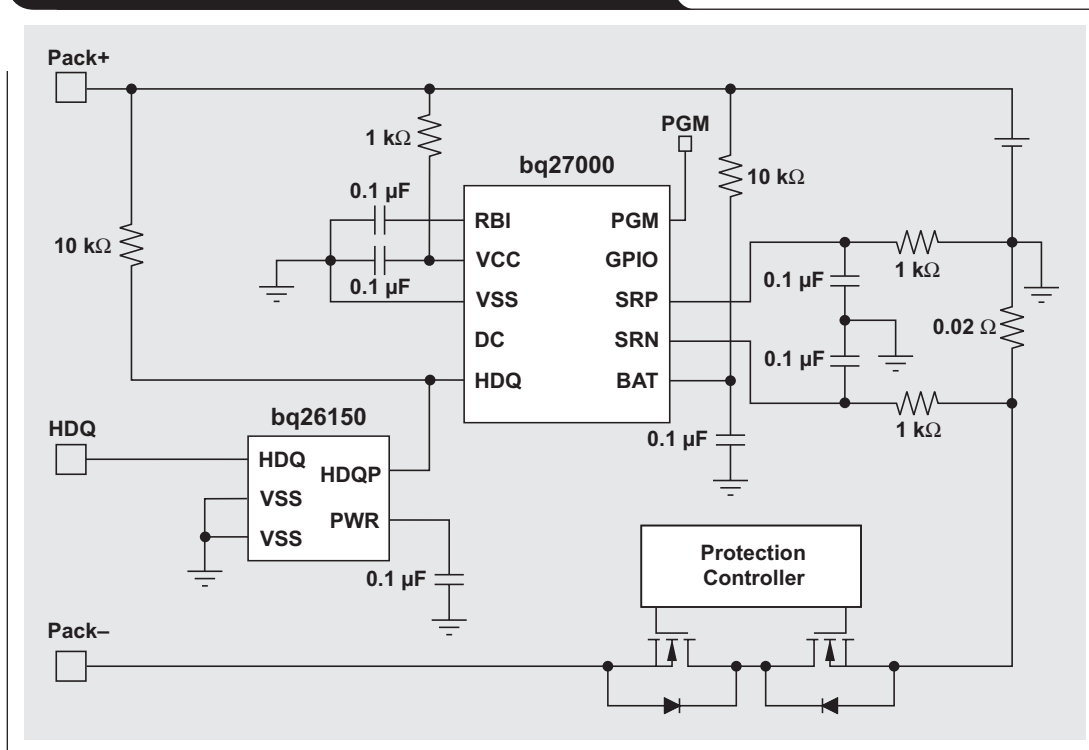

From that point on, the host can follow up on the gas gauge's functionality. The whole authentication process must be repeated upon disconnection from and reconnection to the battery.

Two-cell applications

Figure 3 shows the typical application circuit for supporting two Li-ion cells with the bq26500. An adjustable voltage regulator is added for multicell support. The BAT pin of the gas gauge is connected to the positive side of the bottom cell for a scaled battery-pack voltage measurement.

The host is required to interpret the scaled pack voltage measured by the gas gauge to determine the end-of-discharge threshold and charge termination. Information such as "Remaining State of Capacity" can be used as it is reported by the gas gauge.

Conclusion

The bq2650x and bq27x00 provide battery manufacturers a simple alternative for battery-capacity reporting. The host can obtain a remaining-capacity value just by reading a register from the gas gauge and can then display the result to the end user. By using a gas gauge, the end user can use as much of a battery's charge as possible without being very conservative, because the capacity estimate will be more accurate than that obtained by just measuring cell voltage. The gas gauges can be used in different configurations, permitting authentication features and operation within two-cell applications.


Related Web sites

power.ti.com

www.ti.com/sc/device/partnumber

Replace *partnumber* with bq26150, bq26500, bq27000, bq27200, or TPS71501

Figure 3. Two-cell application with bq26500

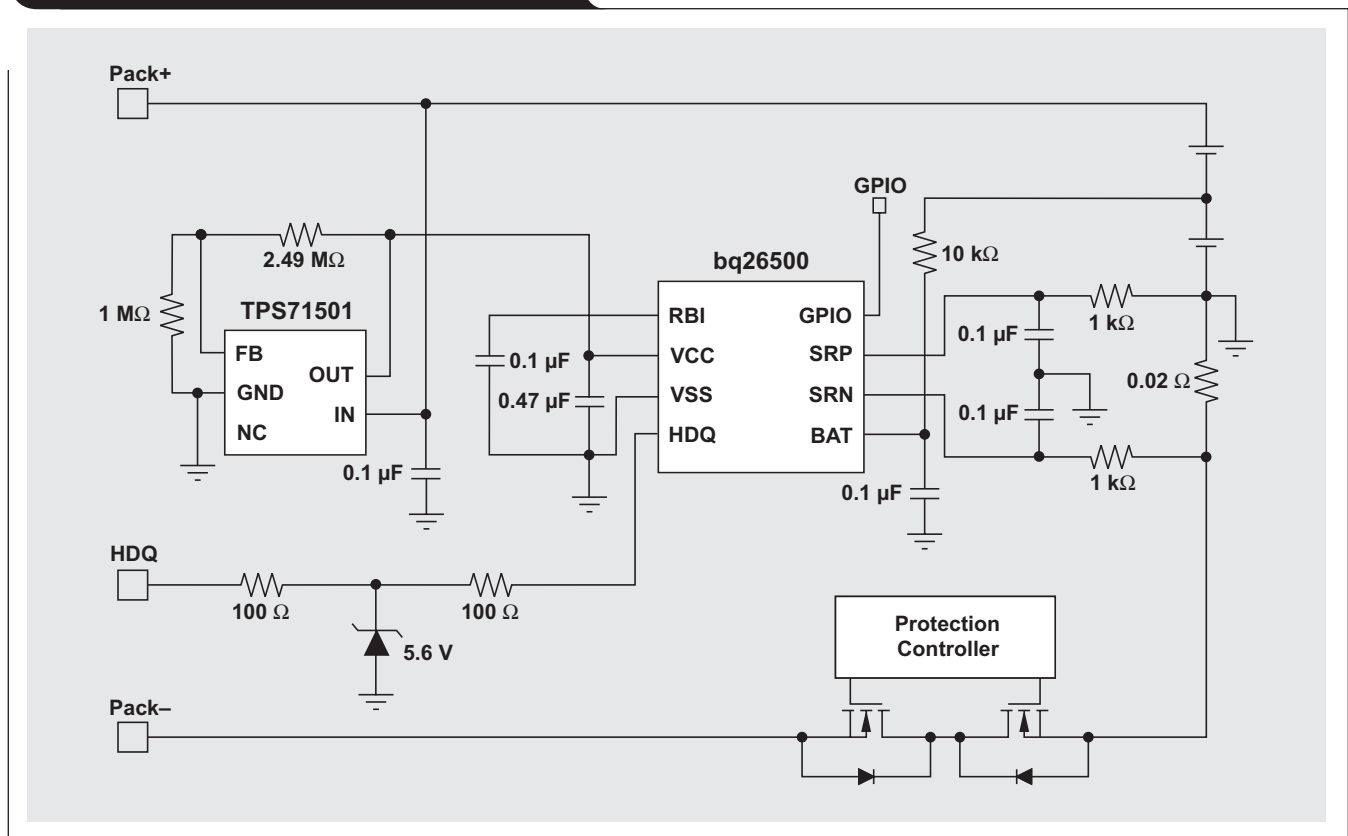

Improved CAN network security with TI's SN65HVD1050 transceiver

By Steve Corrigan (Email: s-corrigan1@ti.com)

New Product Definition

A CAN transceiver must reliably transmit data in extremely harsh operating environments that place an extraordinary electrical burden on the device. Since the transceiver is typically the only interface between expensive node electronics and the CAN bus, many operational security features of the Texas Instruments (TI) SN65HVD1050 take on additional importance in CAN applications. These features include electromagnetic (EM) immunity, low EM emissions, noise rejection, electrostatic discharge (ESD) protection, fault tolerance, and protection during hot plugging or power cycling.

EM immunity

As the EM spectrum becomes more fully utilized, EM fields radiated by a wide range of devices are increasing the probability of interference with other electronic equipment. Due in part to the wireless revolution in electronics, EM interference is increasingly becoming a widespread concern.

Every electronic device has its own unique EM characteristics. The inductance and capacitance of any circuit may develop a common-mode resonance at discrete frequencies that either amplify or attenuate emissions.

The HVD1050 CAN transceiver is designed and tested for EM compatibility without malfunction or degradation of performance in rugged EM environments. "Compatibility" in this definition means both low emissions and high immunity to external EM fields.

Low EM emissions: Balanced signaling and common-mode output

An important requirement of products intended for networking applications is that they behave in a way that does not interfere with the operation of other nearby components or systems. The desired behavior is referred to as "low radiated emissions" and is typically tested according to various quantitative requirements specified at the system or electronic module level.

EM noise is generated by imbalanced high-frequency voltage or current switching. In a CAN transceiver, system-level emission performance must be translated into transceiver characteristics. Specifically, driver output signals are typically mismatched on CANH and CANL, and the resultant EM fields fail to differentially cancel each other as equal and opposite. This output mismatch (displayed in Figures 1 and 2) is referred to in TI datasheets as the peak-to-peak common-mode output voltage, $V_{OC(PP)}$, and may be considered to be a figure of merit for balanced differential signaling.

Measurement of the common-mode output signal is believed to provide all the information necessary to predict performance of system-level emissions. Both time and frequency representations of the output common-mode signal can be analyzed for the purpose of evaluating emissions behavior.

Figure 1. Typical CAN bus $V_{OC(PP)}$ waveform

 


Figure 2. $V_{OC(PP)}$ test setup


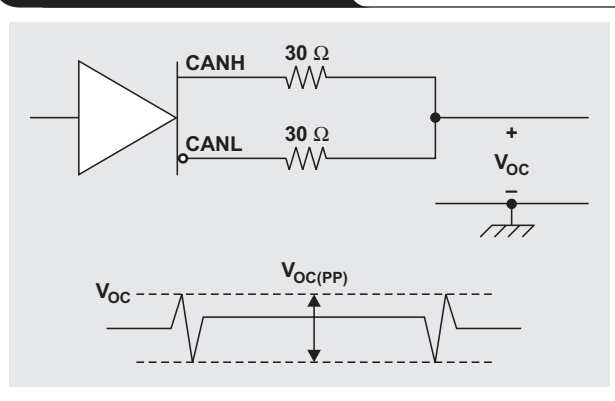


Figure 3. Common-mode noise coupled onto four twisted-pair bus lines

 

High immunity: Common-mode noise rejection

Common-mode noise rejection is an inherent feature of true differential receivers, just as it is with other differential-input circuits such as operational amplifiers. Differential signal pairs are physically close together and are generally exposed to the same noise sources—noise common to each wire. This ensures that exposure to EM fields is nearly equal and common to each line, canceling the differential influence from magnetic field coupling by reversing the polarity in adjacent loops of twist in twisted-pair wiring.

Unwanted noise of various magnitudes easily links the antenna-like bus lines of CAN applications. Pulsing motor controllers, switch-mode power supplies, and fluorescent lighting are typical noise sources that couple onto bus lines (displayed in Figure 3).

A CAN transceiver not specifically designed to reject this coupled noise will respond as if it were data on a bus and send corrupted and meaningless data to a controller.

TI's HVD1050 CAN transceiver is specifically designed and tested for its ability to reject this noise over an extremely wide (–12-V to +12-V) common-mode operating range. The high degree to which the differential receiver rejects coupled noise is evidence of the careful electrical and mechanical design of the receiver components that ensures that input matching is as close to ideal as possible.

Voltage transients and integrated-circuit protection

ESD can occur in any of four ways: A charged body can touch an IC; a charged IC can touch a grounded surface; a charged machine can touch an IC; or an electrostatic field can induce a voltage across a dielectric that is sufficient to

break it down. It becomes readily apparent that a high ESD rating indicates not only a robust transceiver but a robust circuit design as well.

Comparable CAN transceivers on the market provide only 4-kV ESD protection, while the HVD1050 CAN transceiver has an ESD rating of 8 kV when tested in accordance with the Human Body Model (HBM) of JEDEC Standard 22 A114-B. With this ESD rating, the HVD1050 is much better suited to harsh electrical environments than the earlier transceiver versions of other vendors.

To ensure the HVD1050's robustness, it is also tested to ± 200 V in accordance with ISO 7637, test pulses 1, 2, 3a, 3b, 5, 6, and 7.

Fault tolerance

Bus hangs and dominant time-out

CAN bus operators occasionally report that all bus communication comes to a halt when a faulty node places a continuous dominant bit on the bus. This stuck-dominant condition occurs either from a faulty controller or from random slivers of wire, a solder ball, or metal shaving shorts across a transceiver's input (TXD) pin and the adjoining ground (GND) pin.

A dominant-time-out circuit in the HVD1050 prevents the driver from blocking network communication with a hardware or software failure. The time-out circuit is triggered by a falling edge on TXD. If no rising edge occurs before the time-out constant of the circuit expires, the driver is output-disabled, releasing the bus from the stuck-dominant condition. Once the fault is corrected, the circuit is reset by the next rising edge on TXD.

Crushed-cable and short-circuit protection

Bus-cable polarity reversals, accidentally crushed cable, and unintentional shorts of the bus wires to power supplies or ground are common in many CAN applications. To provide protection from these real-world operating events that are common on 24-V industrial buses, the HVD1050 provides short-circuit protection from -27 V up to $+40\text{ V}$. This short-circuit protection extends over any length of time and guarantees that the device will continue normal operation once the fault is removed.

Additional circuit protection is provided with the thermal shutdown circuitry. In the event of a bus short with a runaway current condition, the HVD1050 automatically shuts the device down when thermal conditions exist that could damage internal circuitry.

Hot plugging, power cycling, and glitch-free outputs

Adding additional components to a network most often requires shutting down the entire network to prevent costly system errors. Therefore the ability to plug directly into an operating system becomes a valued asset in many CAN applications.

Plugging an unpowered module directly into a powered system is referred to as “hot plugging” and requires that the transceiver output remain stable during the unpowered to power-up transition without disturbing ongoing network communications.

Many CAN transceivers on the market today have a very low output impedance when unpowered. This causes the device to sink any signal present on the bus and effectively shuts down all data transmission.

For this purpose, the HVD1050's bus pins are biased internally to a high-impedance recessive state. This provides for a power-up into a known recessive condition without disturbing ongoing bus communication. It also maintains the integrity of the bus when power or ground is added to or removed from the circuit.

Together these features of the HVD1050 serve to greatly enhance the operational security of any CAN application.

Related Web sites

interface.ti.com

www.ti.com/sc/device/SN65HVD1050

Index of Articles

Title	Issue	Page	Lit. No.
Data Acquisition			
Aspects of data acquisition system design	August 1999	1	SLYT191
Low-power data acquisition sub-system using the TI TLV1572	August 1999	4	SLYT192
Evaluating operational amplifiers as input amplifiers for A-to-D converters	August 1999	7	SLYT193
Precision voltage references	November 1999	1	SLYT183
Techniques for sampling high-speed graphics with lower-speed A/D converters	November 1999	5	SLYT184
A methodology of interfacing serial A-to-D converters to DSPs	February 2000	1	SLYT175
The operation of the SAR-ADC based on charge redistribution	February 2000	10	SLYT176
The design and performance of a precision voltage reference circuit for 14-bit and 16-bit A-to-D and D-to-A converters	May 2000	1	SLYT168
Introduction to phase-locked loop system modeling	May 2000	5	SLYT169
New DSP development environment includes data converter plug-ins	August 2000	1	SLYT158
Higher data throughput for DSP analog-to-digital converters	August 2000	5	SLYT159
Efficiently interfacing serial data converters to high-speed DSPs	August 2000	10	SLYT160
Smallest DSP-compatible ADC provides simplest DSP interface	November 2000	1	SLYT148
Hardware auto-identification and software auto-configuration for the TLV320AIC10 DSP Codec — a “plug-and-play” algorithm	November 2000	8	SLYT149
Using quad and octal ADCs in SPI mode	November 2000	15	SLYT150
Building a simple data acquisition system using the TMS320C31 DSP	February 2001	1	SLYT136
Using SPI synchronous communication with data converters — interfacing the MSP430F149 and TLV5616	February 2001	7	SLYT137
A/D and D/A conversion of PC graphics and component video signals, Part 1: Hardware	February 2001	11	SLYT138
A/D and D/A conversion of PC graphics and component video signals, Part 2: Software and control	July 2001	5	SLYT129
Intelligent sensor system maximizes battery life: Interfacing the MSP430F123 Flash MCU, ADS7822, and TPS60311	1Q, 2002	5	SLYT123
SHDSL AFE1230 application	2Q, 2002	5	SLYT114
Synchronizing non-FIFO variations of the THS1206	2Q, 2002	12	SLYT115
Adjusting the A/D voltage reference to provide gain	3Q, 2002	5	SLYT109
MSC1210 debugging strategies for high-precision smart sensors	3Q, 2002	7	SLYT110
Using direct data transfer to maximize data acquisition throughput	3Q, 2002	14	SLYT111
Interfacing op amps and analog-to-digital converters	4Q, 2002	5	SLYT104
ADS82x ADC with non-uniform sampling clock	4Q, 2003	5	SLYT089
Calculating noise figure and third-order intercept in ADCs	4Q, 2003	11	SLYT090
Evaluation criteria for ADSL analog front end	4Q, 2003	16	SLYT091
Two-channel, 500-kSPS operation of the ADS8361	1Q, 2004	5	SLYT082
ADS809 analog-to-digital converter with large input pulse signal	1Q, 2004	8	SLYT083
Streamlining the mixed-signal path with the signal-chain-on-chip MSP430F169	3Q, 2004	5	SLYT078
Supply voltage measurement and ADC PSRR improvement in MSC12xx devices	1Q, 2005	5	SLYT073
14-bit, 125-MSPS ADS5500 evaluation	1Q, 2005	13	SLYT074
Clocking high-speed data converters	1Q, 2005	20	SLYT075
Implementation of 12-bit delta-sigma DAC with MSC12xx controller	1Q, 2005	27	SLYT076
Using resistive touch screens for human/machine interface	3Q, 2005	5	SLYT209A
Simple DSP interface for ADS784x/834x ADCs	3Q, 2005	10	SLYT210
Operating multiple oversampling data converters	4Q, 2005	5	SLYT222
Low-power, high-intercept interface to the ADS5424 14-bit, 105-MSPS converter for undersampling applications	4Q, 2005	10	SLYT223
Understanding and comparing datasheets for high-speed ADCs	1Q, 2006	5	SLYT231
Matching the noise performance of the operational amplifier to the ADC	2Q, 2006	5	SLYT237
Using the ADS8361 with the MSP430 USI port	3Q, 2006	5	SLYT244

Title	Issue	Page	Lit. No.
Power Management			
Stability analysis of low-dropout linear regulators with a PMOS pass element	August 1999	10	SLYT194
Extended output voltage adjustment (0 V to 3.5 V) using the TI TPS5210	August 1999	13	SLYT195
Migrating from the TI TL770x to the TI TLC770x	August 1999	14	SLYT196
TI TPS5602 for powering TI's DSP	November 1999	8	SLYT185
Synchronous buck regulator design using the TI TPS5211 high-frequency hysteretic controller	November 1999	10	SLYT186
Understanding the stable range of equivalent series resistance of an LDO regulator	November 1999	14	SLYT187
Power supply solutions for TI DSPs using synchronous buck converters	February 2000	12	SLYT177
Powering Celeron-type microprocessors using TI's TPS5210 and TPS5211 controllers	February 2000	20	SLYT178
Simple design of an ultra-low-ripple DC/DC boost converter with TPS60100 charge pump	May 2000	11	SLYT170
Low-cost, minimum-size solution for powering future-generation Celeron™-type processors with peak currents up to 26 A	May 2000	14	SLYT171
Advantages of using PMOS-type low-dropout linear regulators in battery applications	August 2000	16	SLYT161
Optimal output filter design for microprocessor or DSP power supply	August 2000	22	SLYT162
Understanding the load-transient response of LDOs	November 2000	19	SLYT151
Comparison of different power supplies for portable DSP solutions working from a single-cell battery	November 2000	24	SLYT152
Optimal design for an interleaved synchronous buck converter under high-slew-rate, load-current transient conditions	February 2001	15	SLYT139
–48-V/+48-V hot-swap applications	February 2001	20	SLYT140
Power supply solution for DDR bus termination	July 2001	9	SLYT130
Runtime power control for DSPs using the TPS62000 buck converter	July 2001	15	SLYT131
Power control design key to realizing InfiniBand™ benefits	1Q, 2002	10	SLYT124
Comparing magnetic and piezoelectric transformer approaches in CCFL applications	1Q, 2002	12	SLYT125
Why use a wall adapter for ac input power?	1Q, 2002	18	SLYT126
SWIFT™ Designer power supply design program	2Q, 2002	15	SLYT116
Optimizing the switching frequency of ADSL power supplies	2Q, 2002	23	SLYT117
Powering electronics from the USB port	2Q, 2002	28	SLYT118
Using the UCC3580-1 controller for highly efficient 3.3-V/100-W isolated supply design	4Q, 2002	8	SLYT105
Power conservation options with dynamic voltage scaling in portable DSP designs	4Q, 2002	12	SLYT106
Understanding piezoelectric transformers in CCFL backlight applications	4Q, 2002	18	SLYT107
Load-sharing techniques: Paralleling power modules with overcurrent protection	1Q, 2003	5	SLYT100
Using the TPS61042 white-light LED driver as a boost converter	1Q, 2003	7	SLYT101
Auto-Track™ voltage sequencing simplifies simultaneous power-up and power-down	3Q, 2003	5	SLYT095
Soft-start circuits for LDO linear regulators	3Q, 2003	10	SLYT096
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 1	3Q, 2003	13	SLYT097
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 2	4Q, 2003	21	SLYT092
LED-driver considerations	1Q, 2004	14	SLYT084
Tips for successful power-up of today's high-performance FPGAs	3Q, 2004	11	SLYT079
A better bootstrap/bias supply circuit	1Q, 2005	33	SLYT077
Understanding noise in linear regulators	2Q, 2005	5	SLYT201
Understanding power supply ripple rejection in linear regulators	2Q, 2005	8	SLYT202
Miniature solutions for voltage isolation	3Q, 2005	13	SLYT211
New power modules improve surface-mount manufacturability	3Q, 2005	18	SLYT212
Li-ion switching charger integrates power FETs	4Q, 2005	19	SLYT224
TLC5940 dot correction compensates for variations in LED brightness	4Q, 2005	21	SLYT225
Powering today's multi-rail FPGAs and DSPs, Part 1	1Q, 2006	9	SLYT232
TPS79918 RF LDO supports migration to StrataFlash® Embedded Memory (P30)	1Q, 2006	14	SLYT233
Practical considerations when designing a power supply with the TPS6211x	1Q, 2006	17	SLYT234
TLC5940 PWM dimming provides superior color quality in LED video displays	2Q, 2006	10	SLYT238
Wide-input dc/dc modules offer maximum design flexibility	2Q, 2006	13	SLYT239
Powering today's multi-rail FPGAs and DSPs, Part 2	2Q, 2006	18	SLYT240
TPS61059 powers white-light LED as photoflash or movie light	3Q, 2006	8	SLYT245
TPS65552A powers portable photoflash	3Q, 2006	10	SLYT246
Single-chip bq2403x power-path manager charges battery while powering system	3Q, 2006	12	SLYT247
Complete battery-pack design for one- or two-cell portable applications	3Q, 2006	14	SLYT248

Title	Issue	Page	Lit. No.
Interface (Data Transmission)			
TIA/EIA-568A Category 5 cables in low-voltage differential signaling (LVDS)	August 1999	16	SLYT197
Keep an eye on the LVDS input levels	November 1999	17	SLYT188
Skew definition and jitter analysis	February 2000	29	SLYT179
LVDS receivers solve problems in non-LVDS applications	February 2000	33	SLYT180
LVDS: The ribbon cable connection	May 2000	19	SLYT172
Performance of LVDS with different cables	August 2000	30	SLYT163
A statistical survey of common-mode noise	November 2000	30	SLYT153
The Active Fail-Safe feature of the SN65LVDS32A	November 2000	35	SLYT154
The SN65LVDS33/34 as an ECL-to-LVTTL converter	July 2001	19	SLYT132
Power consumption of LVPECL and LVDS	1Q, 2002	23	SLYT127
Estimating available application power for Power-over-Ethernet applications	1Q, 2004	18	SLYT085
The RS-485 unit load and maximum number of bus connections	1Q, 2004	21	SLYT086
Failsafe in RS-485 data buses	3Q, 2004	16	SLYT080
Maximizing signal integrity with M-LVDS backplanes	2Q, 2005	11	SLYT203
Device spacing on RS-485 buses	2Q, 2006	25	SLYT241
Improved CAN network security with TI's SN65HVD1050 transceiver	3Q, 2006	17	SLYT249
Amplifiers: Audio			
Reducing the output filter of a Class-D amplifier	August 1999	19	SLYT198
Power supply decoupling and audio signal filtering for the Class-D audio power amplifier	August 1999	24	SLYT199
PCB layout for the TPA005D1x and TPA032D0x Class-D APAs	February 2000	39	SLYT182
An audio circuit collection, Part 1	November 2000	39	SLYT155
1.6- to 3.6-volt BTL speaker driver reference design	February 2001	23	SLYT141
Notebook computer upgrade path for audio power amplifiers	February 2001	27	SLYT142
An audio circuit collection, Part 2	February 2001	41	SLYT145
An audio circuit collection, Part 3	July 2001	34	SLYT134
Audio power amplifier measurements	July 2001	40	SLYT135
Audio power amplifier measurements, Part 2	1Q, 2002	26	SLYT128
Amplifiers: Op Amps			
Single-supply op amp design	November 1999	20	SLYT189
Reducing crosstalk of an op amp on a PCB	November 1999	23	SLYT190
Matching operational amplifier bandwidth with applications	February 2000	36	SLYT181
Sensor to ADC — analog interface design	May 2000	22	SLYT173
Using a decompensated op amp for improved performance	May 2000	26	SLYT174
Design of op amp sine wave oscillators	August 2000	33	SLYT164
Fully differential amplifiers	August 2000	38	SLYT165
The PCB is a component of op amp design	August 2000	42	SLYT166
Reducing PCB design costs: From schematic capture to PCB layout	August 2000	48	SLYT167
Thermistor temperature transducer-to-ADC application	November 2000	44	SLYT156
Analysis of fully differential amplifiers	November 2000	48	SLYT157
Fully differential amplifiers applications: Line termination, driving high-speed ADCs, and differential transmission lines	February 2001	32	SLYT143
Pressure transducer-to-ADC application	February 2001	38	SLYT144
Frequency response errors in voltage feedback op amps	February 2001	48	SLYT146
Designing for low distortion with high-speed op amps	July 2001	25	SLYT133
Fully differential amplifier design in high-speed data acquisition systems	2Q, 2002	35	SLYT119
Worst-case design of op amp circuits	2Q, 2002	42	SLYT120
Using high-speed op amps for high-performance RF design, Part 1	2Q, 2002	46	SLYT121
Using high-speed op amps for high-performance RF design, Part 2	3Q, 2002	21	SLYT112
FilterPro™ low-pass design tool	3Q, 2002	24	SLYT113
Active output impedance for ADSL line drivers	4Q, 2002	24	SLYT108
RF and IF amplifiers with op amps	1Q, 2003	9	SLYT102
Analyzing feedback loops containing secondary amplifiers	1Q, 2003	14	SLYT103
Video switcher using high-speed op amps	3Q, 2003	20	SLYT098
Expanding the usability of current-feedback amplifiers	3Q, 2003	23	SLYT099
Op amp attenuators	4Q, 2003	28	SLYT093

Title	Issue	Page	Lit. No.
Amplifiers: Op Amps (Continued)			
Calculating noise figure in op amps	4Q, 2003	.31	SLYT094
Op amp stability and input capacitance	1Q, 2004	.24	SLYT087
Integrated logarithmic amplifiers for industrial applications	1Q, 2004	.28	SLYT088
Active filters using current-feedback amplifiers	3Q, 2004	.21	SLYT081
Auto-zero amplifiers ease the design of high-precision circuits	2Q, 2005	.19	SLYT204
So many amplifiers to choose from: Matching amplifiers to applications	3Q, 2005	.24	SLYT213
Instrumentation amplifiers find your needle in the haystack	4Q, 2005	.25	SLYT226
High-speed notch filters	1Q, 2006	.19	SLYT235
Low-cost current-shunt monitor IC revives moving-coil meter design	2Q, 2006	.27	SLYT242
General Interest			
Synthesis and characterization of nickel manganite from different carboxylate precursors for thermistor sensors	February 2001	.52	SLYT147
Analog design tools	2Q, 2002	.50	SLYT122

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone +1(972) 644-5580
Fax +1(972) 927-6377
Internet/Email support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone
Belgium (English) +32 (0) 27 45 54 32
Finland (English) +358 (0) 9 25173948
France +33 (0) 1 30 70 11 64
Germany +49 (0) 8161 80 33 11
Israel (English) 180 949 0107
Italy 800 79 11 37
Netherlands (English) +31 (0) 546 87 95 45
Russia +7 (4) 95 98 10 701
Spain +34 902 35 40 28
Sweden (English) +46 (0) 8587 555 22
United Kingdom +44 (0) 1604 66 33 99
Fax +(49) (0) 8161 80 2045
Internet support.ti.com/sc/pic/euro.htm

Japan

Fax International +81-3-3344-5317
Domestic 0120-81-0036
Internet/Email International support.ti.com/sc/pic/japan.htm
Domestic www.tij.co.jp/pic

Asia

Phone
International +886-2-23786800
Domestic Toll-Free Number
Australia 1-800-999-084
China 800-820-8682
Hong Kong 800-96-5941
India +91-80-41381665 (Toll)
Indonesia 001-803-8861-1006
Korea 080-551-2804
Malaysia 1-800-80-3973
New Zealand 0800-446-934
Philippines 1-800-765-7404
Singapore 800-886-1028
Taiwan 0800-006800
Thailand 001-800-886-0010
Fax +886-2-2378-6808
Email tiasia@ti.com
ti-china@ti.com
Internet support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

B062706

Auto-Track, FilterPro, PowerPAD, and SWIFT are trademarks of Texas Instruments.
Celeron is a trademark and StrataFlash is a registered trademark of Intel Corporation. All other trademarks are the property of their respective owners.

SLYT243