

Get low-noise, low-ripple, high-PSRR power with the TPS717xx

By Jeff Falin

Senior Applications Engineer

Introduction


While highly efficient switching power supplies are commonly used for long battery life in portable end equipment such as mobile phones and PDAs, the internal circuitry of some of these devices is sensitive to noise and therefore does not operate properly when powered from a switching power supply with output ripple. Audio circuitry, PLLs, RF transceivers, and DACs are just a few examples of such circuits. Linear regulators are ideal for powering these circuits.

Figure 1 shows a simplified block diagram of a linear regulator using a p-channel MOSFET (pFET) as a pass element. A_{OL} is the open-loop gain of the error amplifier, and g_m is the pass-element transconductance. The error amplifier controls the voltage at the gate of the pass element so that the current through the FET keeps the output voltage regulated relative to the internal reference voltage. Assuming that the low-pass filter (LPF) formed by R_{LPF} and C_{LPF} eliminates nearly all internal-reference noise, the output voltage should be ripple- and noise-free for frequencies within the bandwidth of the regulator's control loop. The concept is easy to understand, but achieving a high power-supply rejection ratio (PSRR) over a wide bandwidth with very low quiescent current and in a small package requires innovative circuits. This article highlights the TPS717xx single-output linear regulator, which provides high power-supply rejection (PSR) over a wide bandwidth with very low quiescent current and in a small package. Similar, dual-output versions are available with the TPS718xx and TPS719xx families. This article also provides guidance on component selection and layout techniques for maximizing PSR and minimizing the regulator's self-generated white noise.

What is the PSRR?

The PSRR is a measure of a circuit's PSR expressed as a ratio of output noise to noise at the power-supply input. It provides a measure of how well a circuit rejects ripple at various frequencies injected from its input power supply. In the case of linear regulators, PSRR is a measure of the regulated output-voltage ripple compared to the input-voltage ripple over a wide frequency range and is expressed in decibels (dB). If the pass element in Figure 1 is treated as a variable resistance, R_{DS} , and the error amplifier and bandgap reference are assumed to have been designed to

Figure 1. Simplified block diagram of a linear regulator

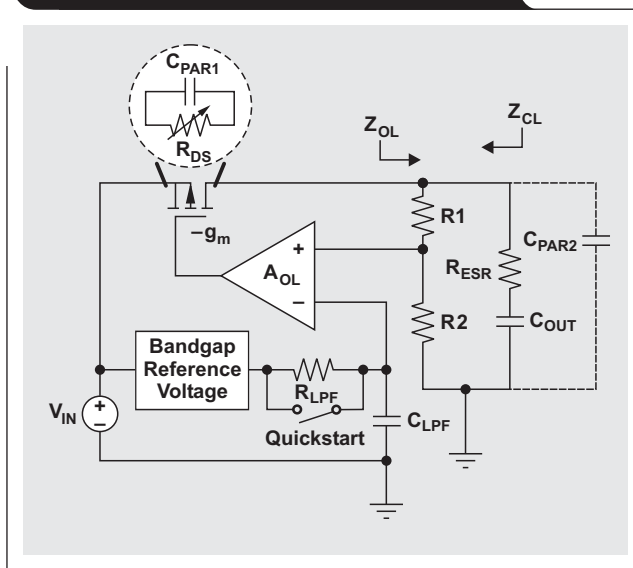

minimize pass-through of the input-voltage ripple, then the PSR is simply a voltage divider, expressed as

$$PSR = \frac{Z_{OL} \parallel Z_{CL}}{Z_{OL} \parallel Z_{CL} + R_{DS}}$$

In this equation, Z_{OL} is the output impedance at the regulator's output, ignoring the effect of the regulator's feedback loop:

$$Z_{OL} = (Z_{COUT} + R_{ESR}) \parallel (R1 + R2) \parallel C_{PAR2},$$

where Z_{COUT} and R_{ESR} are the output capacitor's impedance and equivalent series resistance (ESR), respectively, and C_{PAR2} is the parasitic capacitance of the output components and PCB. Z_{CL} is the impedance looking back into the output of the regulator, including the effect of the regulator's feedback loop:

$$Z_{CL} = \frac{Z_{OL} \parallel R_{DS} \parallel C_{PAR1}}{g_m \times A_{OL} \times f \times \beta},$$

where C_{PAR1} is the passive-element parasitic capacitance, f is the ripple frequency, and β is the feedback factor,

$$\beta = \frac{R2}{R1 + R2}.$$


Figure 2 shows the general shape of a PSRR curve, where $f_{P(dom)}$ is the dominant pole and f_{UG} is the unity-gain bandwidth. If the error amplifier is compensated to have a single-pole response, then the Region 1 PSR for amplifier frequencies below f_{UG} can be approximated by the equation on the left side of the graph. Designing the regulator with a high-gain, wide-bandwidth error amplifier can therefore provide high PSR over a wide range of frequencies. In Region 2, above the control-loop bandwidth, the regulator is no longer effective at providing PSR, so the PSRR reduces to a simple voltage divider as shown on the right side of the curve. As Z_{COUT} decreases relative to R_{DS} , the PSR provided by the passive components on the board increases. If C_{OUT} has high R_{ESR} , the PSR peaks sooner. In Region 3, the IC and board parasitic capacitances (C_{PAR1} and C_{PAR2}) dominate, resulting in a capacitive voltage divider, which typically causes the PSR to decrease again. A larger output capacitor with less ESR will typically improve PSRR in this region, but it can also actually decrease the PSRR at some frequencies. This occurs because increasing the output capacitor may lower $f_{P(dom)}$ and/or f_{UG} , depending on how the regulator is compensated, thereby causing the open-loop gain to roll off sooner.

Maximizing PSR

The TPS717xx family of regulators has incorporated both well-known and patentable circuit techniques to provide high PSR over a wide frequency range. An example of the PSRR is shown in Figure 3.

With the simple model previously explained, it can be shown that the TPS717xx's dominant pole with $C_{OUT} = 1 \mu F$ is at approximately 20 to 30 kHz and the unity-gain frequency is near 400 kHz. Since PSR is a function of the open-loop gain, as the gain varies so will the PSR in Regions 1

Figure 2. PSRR graph

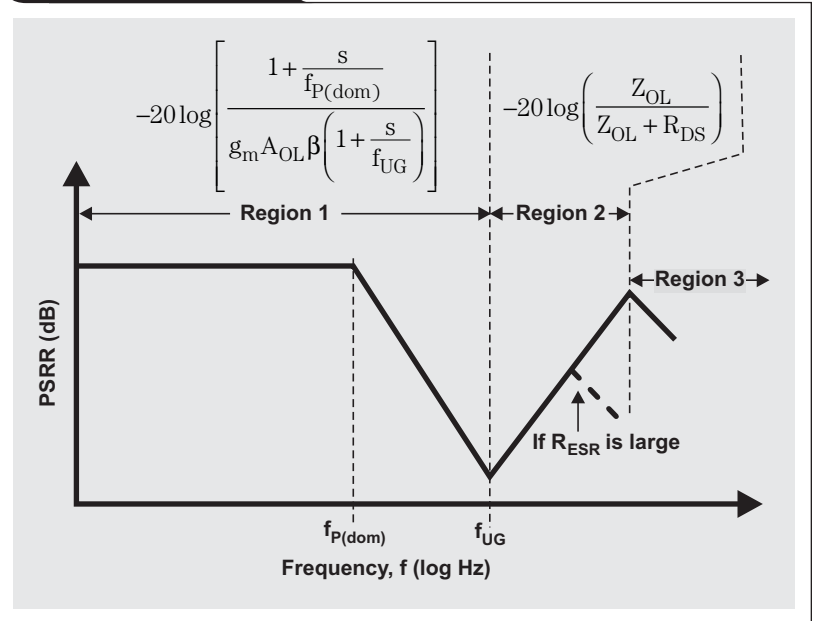


and 2 of Figure 2. Figure 3 shows the TPS717xx's PSRR varying with load current. As load current increases, R_{DS} decreases; therefore Z_{CL} decreases, since a MOSFET's output impedance is inversely proportional to its drain current. In many regulators, where $f_{P(dom)}$ varies with Z_{CL} , increasing the load current also pushes $f_{P(dom)}$ to higher frequencies, which increases the feedback-loop bandwidth. As shown in Figure 3, the net effect of increasing the load current is reduced PSRR.

The differential DC voltage between input and output also affects PSR. As $V_{IN} - V_{OUT}$ is lowered, the pFET (which provides gain) is driven out of the active (saturation) region of operation and into the triode/linear region, which causes the feedback loop to lose gain. Therefore, the PSR of the regulator decreases as V_{IN} approaches V_{OUT} . The lowest PSR, approaching 0 dB, occurs when the device is in dropout ($V_{IN} \approx V_{OUT}$). In this situation, the RC filter formed by the linear regulator's pass-element R_{DS} and output capacitor determines PSR.

Low noise

A linear regulator's self-generated noise is sometimes confused with its PSRR. However, noise is generated by the transistors and resistors in the regulator's internal circuitry as well as by the external feedback resistors. Transistors generate shot noise and flicker noise, both of which are directly proportional to current flow. Flicker noise is indirectly proportional to frequency and so is higher at low frequencies. The resistive element of MOSFETs also generates thermal noise like resistors. Thermal noise is directly proportional to temperature, the resistor's resistance value, and the current flow through the transistors. Transistors and resistors closest to the error-amplifier inputs in the small-signal path cause the

Figure 3. TPS717xx PSRR graph

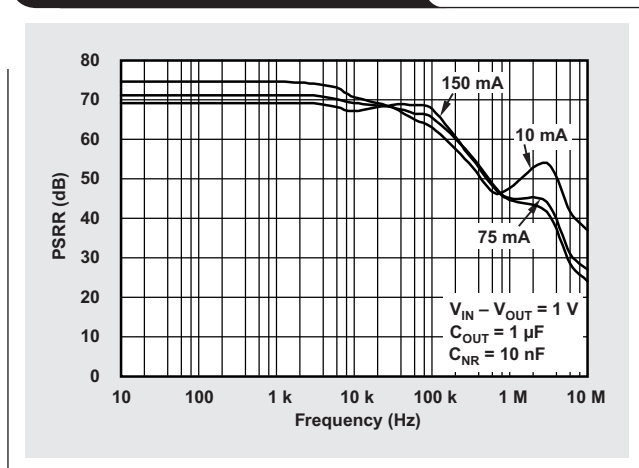

most output noise because their noise is amplified by the regulator's closed-loop gain ($A_{CL} = V_{OUT}/V_{Bandgap} = 1/\beta = 1 + R1/R2$). The noise contribution from components later in the signal path is insignificant when compared to the noise at the error-amplifier inputs. In fact, when modest-sized feedback resistors are used, most of the regulator's noise comes from the amplified bandgap reference. As shown in Figure 1, the simplest way to reduce the bandgap noise is to use a low-pass filter (LPF) consisting of an internal resistor, R_{LPF} , and an external capacitor, C_{LPF} . At startup, this filter would slow down the output-voltage rise without the aid of the "quickstart" transistor. When the quickstart transistor is used, it shorts out the R_{LPF} for a short time at startup so the regulator output can rise quickly. Larger noise capacitors such as C_{LPF} in Figure 1 will reduce the output noise produced by the bandgap until the regulator's other noise sources begin to dominate. Using a noise capacitor that is too large results in the quickstart circuit timer expiring before the $R_{LPF} \times C_{LPF}$ time constant. In this case, the output voltage will rise quickly to a level below regulation and then rise very slowly to its final regulated value.

A regulator's noise output is characterized by two measurements. One is its spectral noise density, a curve that shows noise ($\mu V/\sqrt{Hz}$) versus frequency. The other is the RMS of the spectral noise density integrated over a finite frequency range, also commonly called output-noise voltage (μV_{RMS}). Figure 4 shows the TPS717xx's spectral noise density with different C_{NR} values, where C_{NR} is the same as C_{LPF} in Figure 1.

When noise specifications of different regulators are compared, it is imperative that the two regulators' noise measurements be taken over the same frequency range and at the same output voltage and current values. When output noise values for regulators at two different output voltages are compared, an approximate noise value can be used that is computed by scaling one of the noise measurements by the ratio of the two output voltages. When a

noise-capacitor pin is not available, adding a capacitor across R1 reduces the noise by reducing the closed-loop gain at high frequencies. However, this could potentially slow down start-up time, since the capacitor would have to be charged by the current in the resistor divider; adding such a capacitor could also potentially make the feedback loop unstable.

Component selection and board layout

Proper board layout and capacitor selection are critical to maximizing PSR and minimizing noise. Low-ESR output capacitors maximize PSR at high frequencies but may increase noise. The reason for this is that the low impedance created by the output capacitor and its ESR may improve stability and PSR by removing peaking in the control loop at frequencies near $f_{P(dom)}$, but removing this peaking would also provide higher gain for the internal noise sources. To maximize PSR and minimize noise, it is recommended that V_{IN} and V_{OUT} have separate ground planes that are connected at the regulator's ground pin. The input, output, and noise-reduction capacitors should be very close to the IC, with the ground of the noise-reduction capacitor as close to the regulator's ground pin as possible.

Conclusion

Linear regulators are ideal for providing a low-ripple, low-noise power rail to sensitive analog circuitry. The TPS717xx single-output and TPS718xx/TPS719xx dual-output linear regulators are specifically designed for providing high PSR over a wide frequency range with low noise. These linear regulators also consume very little quiescent current when powered and even less when shut down, helping maximize battery life in portable powered applications that need bursts of regulator power only at irregular intervals.

References

For more information related to this article, you can download an Acrobat Reader file at www-s.ti.com/sc/techlit/litnumber and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title


TI Lit.

1. Vishal Gupta, Gabriel A. Rincón-Mora, and Prasan Raha, "Analysis and Design of Monolithic, High PSR, Linear Regulators for SoC Applications," http://users.ece.gatech.edu/rincon-mora/publicat/journals/socc04_psr.pdf —
2. John C. Teel, "Understanding noise in linear regulators"slyt201
3. John C. Teel, "Understanding power supply ripple rejection in linear regulators"slyt202

Related Web site

power.ti.com

Figure 4. TPS717xx spectral noise density

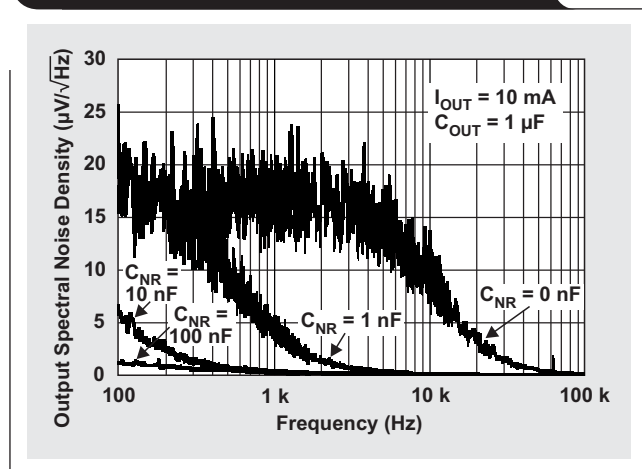

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Management	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone

European Free Call	00800-ASK-TEXAS (00800 275 83927)
--------------------	--------------------------------------

International	+49 (0) 8161 80 2121
---------------	----------------------

Russian Support	+7 (4) 95 98 10 701
-----------------	---------------------

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+(49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm

Japan

Fax

International	+81-3-3344-5317	Domestic	0120-81-0036
---------------	-----------------	----------	--------------

Internet/Email	support.ti.com/sc/pic/japan.htm		
----------------	--	--	--

International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone

International	+886-2-23786800
---------------	-----------------

Domestic	Toll-Free Number
----------	------------------

Australia	1-800-999-084	Malaysia	1-800-80-3973
-----------	---------------	----------	---------------

China	800-820-8682	New Zealand	0800-446-934
-------	--------------	-------------	--------------

Hong Kong	800-96-5941	Philippines	1-800-765-7404
-----------	-------------	-------------	----------------

India	+91-80-41381665 (Toll)	Singapore	800-886-1028
-------	------------------------	-----------	--------------

Indonesia	001-803-8861-1006	Taiwan	0800-006800
-----------	-------------------	--------	-------------

Korea	080-551-2804	Thailand	001-800-886-0010
-------	--------------	----------	------------------

Fax	+886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		
			ti-china@ti.com

C062907

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as TI or its management "believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2007 Texas Instruments Incorporated