

# LM108,LM118,LM741

*Predicting Op Amp Slew Rate Limited Response*




Literature Number: SNOA852

# Predicting Op Amp Slew Rate Limited Response

National Semiconductor  
Linear Brief 19  
August 1972



The following analysis of sine and step voltage responses applies to all single dominant pole op amps such as the LM101A, LM107, LM108A, LM112, LM118 and the LM741. Each of these op amps has an open loop response curve with a shape similar to the one shown in *Figure 1*. The distinguishing feature of this curve is the single low frequency turnover from a flat response to a uniform  $-20$  dB per decade of frequency ( $-6$  dB/octave) drop in gain, at least until the curve passes through the  $0$  dB line. Closing the loop to  $40$  dB ( $\times 100$ ) as shown with a dotted line on *Figure 1* does not change the shape of the curve, but it does move the turnover to a higher frequency. These open loop and closed loop response curves determine the gain applied to small signal inputs. The logical question then arises as to when a signal can no longer be treated as a small signal and the amplifier response begins to deviate from this curve.

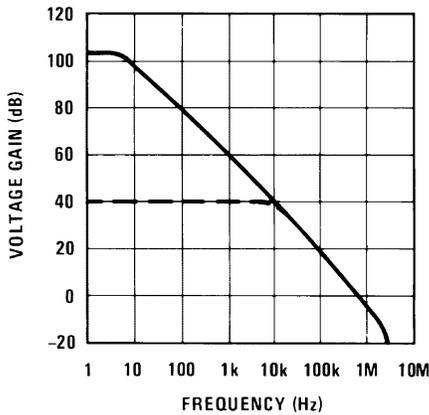

**FIGURE 1. Open and Closed Loop Frequency Response**

The answer lies in the slew rate limit of the op amp. The slew rate limit is the maximum rate of change of the amplifier's output voltage and is due to the fact that the compensation capacitor inside the amplifier only has finite currents<sup>1</sup> available for charging and discharging. A sinusoidal output signal will cease being a small signal when its maximum rate of change equals the slew rate limit  $S_r$  of the amplifier. The maximum rate of change for a sine wave occurs at the zero crossing and may be derived as follows:

$$v_o = V_p \sin 2\pi ft \quad (1)$$

$$\frac{dv_o}{dt} = 2\pi f V_p \cos 2\pi ft \quad (2)$$

$$\left. \frac{dv_o}{dt} \right|_{t=0} = 2\pi f V_p \quad (3)$$

$$S_r = 2\pi f_{\max} V_p \quad (4)$$

where:

$v_o$  = output voltage

$V_p$  = peak output voltage

where:  $v_o$  = output voltage


$V_p$  = peak output voltage

$S_r$  = maximum  $\frac{dv_o}{dt}$

The maximum sine wave frequency an amplifier with a given slew rate will sustain without causing the output to take on a triangular shape is therefore a function of the peak amplitude of the output and is expressed as:

$$f_{\max} = \frac{S_r}{2\pi V_p} \quad (5)$$

*Equation (5)* demonstrates that the borderline between small signal response and slew rate limited response is not just a function of the peak output signal but that by trading off either frequency or peak amplitude one can continue to have a distortion free output. *Figure 2* shows a quick reference graphical presentation of *Equation (5)* with the area above any  $V_{PEAK}$  line representing an undistorted small signal response and the area below a given  $V_{PEAK}$  line representing a distorted sine wave response due to slew rate limiting.

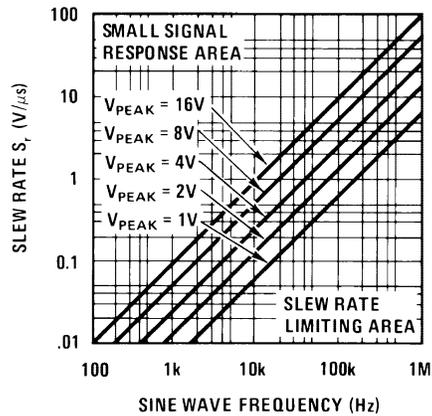


**FIGURE 2. Sine Wave Response**

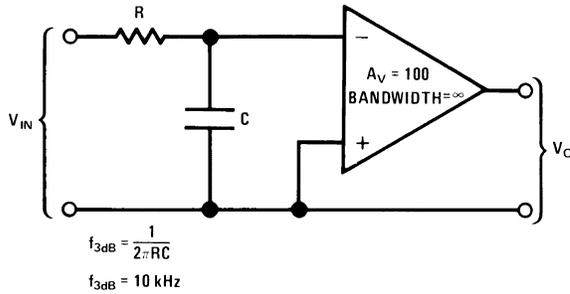As a matter of convenience, amplifier manufacturers often give a "full-power bandwidth" or "large signal response" on their specification sheets.

This frequency can be derived by inserting the amplifier slew rate and peak rated output voltage into *Equation (5)*. The bandwidth from DC to the resulting  $f_{\max}$  is the full-power bandwidth or "large signal response" of the amplifier. For example the full-power bandwidth of the LM741 with a  $0.5V$

$\mu s$   $S_r$  is approximately 6 kHz while the full-power bandwidth of the LM118 with an  $S_r$  of 70 V/ $\mu s$  is approximately 900 kHz.



00872603

**FIGURE 3. Small Signal Op Amp Model**

The step voltage response at the output of an op amp can also be divided into a small signal response and a slew rate limited response. The signal turnover and uniform -20 dB/decade slope shown in the small signal frequency response curve of *Figure 1* are also characteristic of a low pass filter and one can in fact model an op amp as a low pass RC filter followed by a very wideband amplifier. *Figure 3* shows a model of a X100 circuit with a 3 dB down rolloff frequency of 10 kHz. From basic filter theory<sup>2</sup> the 10% to 90% rise time of single pole low pass filter is:

$$t_r = \frac{0.35}{f_{3dB}} \tag{6}$$

which for this example would be 35  $\mu s$ . Again this small signal or low pass filter response ceases when the required rate of change of the output voltage exceeds the slew rate limit  $S_r$  of the amplifier. Mathematically stated:

$$\frac{V_{STEP}}{t_r} \geq S_r \tag{7}$$


This means that as soon as the amplitude of the output step voltage divided by the rise time of the circuit exceeds the  $S_r$  of the amplifier, the amplifier will go into slew rate limiting. The output will then be a ramp function with a slope of  $S_r$  and a rise time equal to:

$$t'_r = \frac{V_{STEP}}{S_r} \tag{8}$$

Substituting *Equation (6)* into *Equation (7)* gives the critical value of  $V_{STEP}$  directly in terms of  $f_{3dB}$ :

$$\frac{V_{STEP} f_{3dB}}{0.35} \geq S_r \tag{9}$$

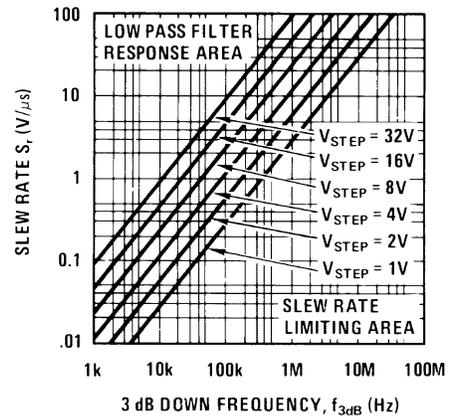which can be graphed as shown in *Figure 4*. Any point in the area above a  $V_{STEP}$  line represents an undistorted low pass filter type response and any point in the area below a given  $V_{STEP}$  line represents a slew rate limited response.



00872604

**FIGURE 4. Step Voltage Response**

The above equations and graphs should allow one to avoid the pitfalls of slew rate limiting and also provide a means of using engineering tradeoffs to extend the response of the single dominant pole type of amplifier.

## References

1. Solomon, J. E.; Davis, W. R.; and Lee, P. L.: "A Self-Compensated Monolithic Operational Amplifier With Low Input Current and High Slew Rate", pp. 14-15, ISSCC Digest Tech. Papers, February 1969.
2. Millman, J. and Hawkias, C. C.: "Electronic Devices and Circuits", pp. 465-466, McGraw-Hill Book Company, New York, 1967.

## Notes

### LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
Americas  
Email: new.feedback@nsc.com

[www.national.com](http://www.national.com)

**National Semiconductor Europe**  
Fax: +49 (0) 180-530 85 86  
Email: europe.support@nsc.com  
Deutsch Tel: +49 (0) 69 9508 6208  
English Tel: +44 (0) 870 24 0 2171  
Français Tel: +33 (0) 1 41 91 8790

**National Semiconductor Asia Pacific Customer Response Group**  
Tel: 65-2544466  
Fax: 65-2504466  
Email: ap.support@nsc.com

**National Semiconductor Japan Ltd.**  
Tel: 81-3-5639-7560  
Fax: 81-3-5639-7507  
Email: nsj.crc@jksmt.nsc.com

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated