

AN-1061 Power Conversion in Line-Powered Equipment

ABSTRACT

This application note describes line-powered equipment and power conversion techniques or methods to solve those typical power needs.

Contents

1	Introduction	2
2	Converting Line Voltage to Safe Low Voltage	4
3	Selecting the DC/DC Conversion Method	5
4	Design for 3-Output Modem Power Supply	7
5	Undervoltage Lockout	8
6	Comparison of Power Supply Solutions	10
7	Simple Switcher Converters	11

List of Figures

1	Typical Power Supply Requirement	2
2	Power Supply Solution Using Isolation Transformer and Low-Voltage DC/DC Converters.....	3
3	AC Line Rectification Methods	4
4	DC/DC Converter Options	5
5	Power Supply Solution Using Linear Regulators	6
6	Power Supply Solution Using Step-Down Switching Regulators	6
7	3-Output Flyback Converter Provides Power for Modem.....	7
8	Schematic for Power Supply of	8
9	Hysteresis Controls Turn-on and Turn-off Thresholds of Undervoltage Circuit.....	9
10	Undervoltage Lockout Circuit with Hysteresis	10

1 Introduction

Most equipment used in the office or home draws its power from the AC line. This line may be between 90 V_{AC} –264 V_{AC} and 47 Hz–63 Hz, depending on which portion of the world the equipment is located. However, the internal circuitry and motors rarely operate at these voltages. It now becomes necessary to provide Power Conversion within the equipment. This conversion means a power supply.

The following examples will describe typical power needs within line powered equipment and methods to solve those power needs. [Figure 1](#) shows an example of a power supply requirement for any given piece of line powered equipment.

The AC input line must be converted by the power supply to provide three DC output voltages which are well regulated over input line and output load. Most circuitry requires low output ripple on its supply voltage. Output ripple is generally specified to be no more than 1% of the output voltage.

The power conversion technique we will address includes a line transformer which provides safety isolation from the line voltage. The line transformer is the only portion of the power supply which needs to meet UL1950, CSA950, or EN60950 (IEC950) standards. All voltages produced by the transformer will be assumed to meet the requirements for SELV (Safe Extra Low Voltage) circuits. These transformers may be purchased as catalog items, or may be specified with custom requirements.

The power supply following the isolation transformer (see [Figure 2](#)) can be easily designed using Texas Instruments Power ICs. Standard data sheets include design procedures and application hints on the use of all parts. Other parts will be supported with design software providing a complete solution.

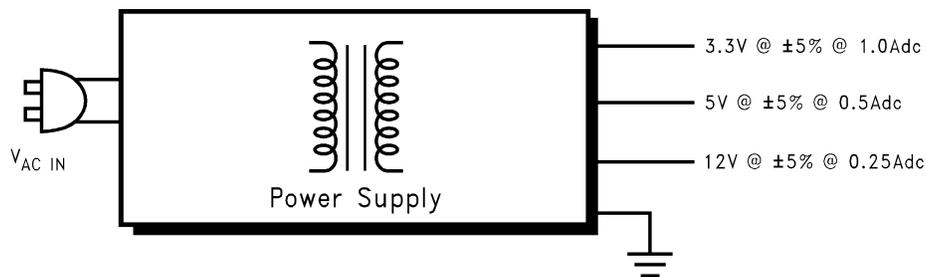


Figure 1. Typical Power Supply Requirement

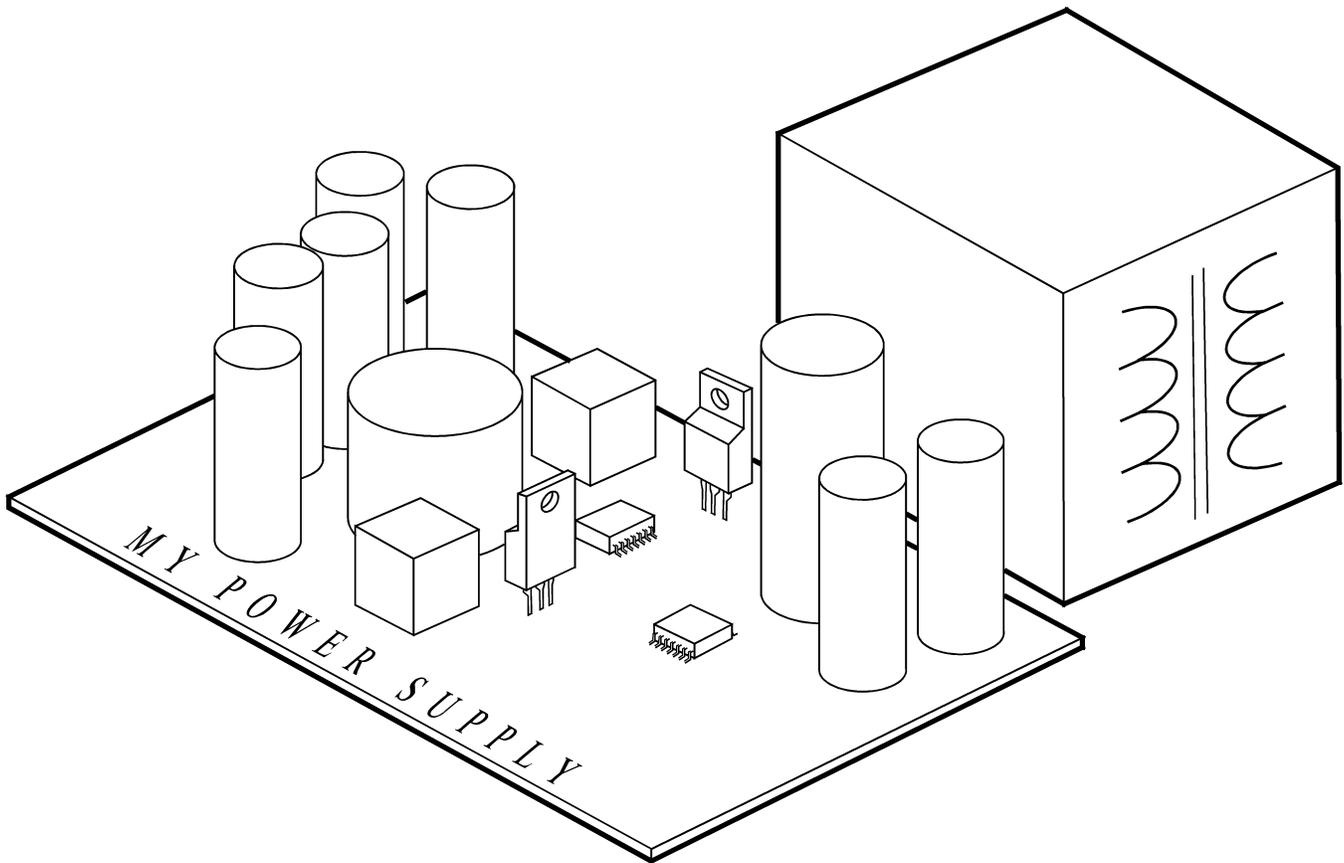


Figure 2. Power Supply Solution Using Isolation Transformer and Low-Voltage DC/DC Converters

2 Converting Line Voltage to Safe Low Voltage

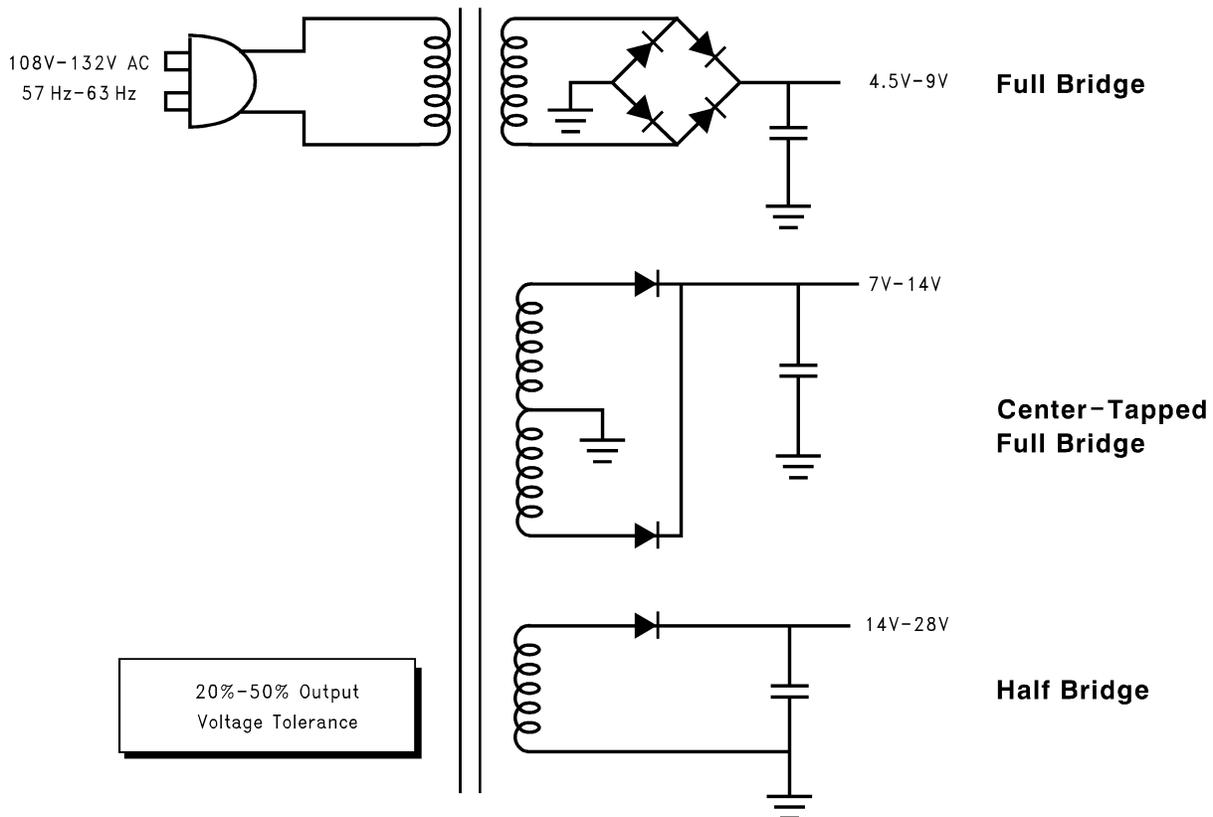


Figure 3. AC Line Rectification Methods

A line frequency transformer will be used to convert the hazardous line voltage to an isolated safe low voltage. One must understand the characteristics of low frequency line transformers to begin to design this type of power supply.

Figure 3 shows three different rectification techniques to develop a basic DC voltage source. The first, Full Bridge, is most efficient in the transformer, but requires a four diode rectification bridge. The second, Center-Tapped Full Bridge, requires more turns of wire in the secondary, but saves two diodes. The output ripple on both Full Bridge designs is the same. The last, Half Bridge, is a low cost method best for low output power. The half bridge creates a DC bias on the winding and as a result should only be used for very low current outputs. A half bridge will also give higher output ripple.

Output regulation is poor in a line transformer. If one assumes an ideal transformer, the regulation of the output will be no better than the input. Typical design requirements for input voltage is nominal $\pm 10\%$ (some require $\pm 12.5\%$). In the case above, nominal is $120 V_{AC}$.

Given a line variation of 10%, the output voltage tolerance is no better than $\pm 10\%$. Adding the resistance of the transformer windings results in output voltage variation with load. The change in output voltage with load is a complex function. The definitive analysis can be found in a paper published by O.H. Shade in the July, 1943 Proceedings of the Institute of Radio Engineers entitled *Analysis of Rectifier Operation*. Although Shade used vacuum tube rectifiers, the analysis still holds true for modern diodes. In general, load regulation can vary from 10% to 40%. In the example above, the load regulation is 25%.

The size of the transformer is a function of a number of items: output power, load regulation, efficiency, maximum allowable temperature rise, and cost (core material is the primary variable).

Since the output voltages are poorly regulated, they can not be used as the output of the power supply. Additional regulation is necessary.

3 Selecting the DC/DC Conversion Method

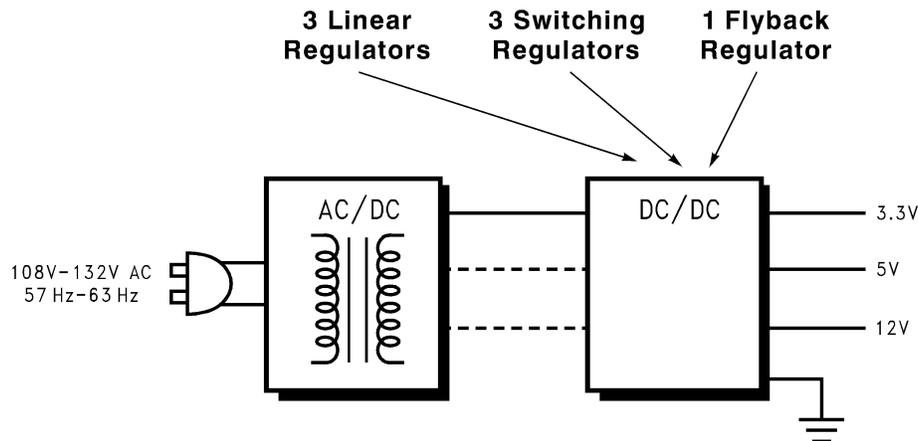


Figure 4. DC/DC Converter Options

As shown in [Figure 4](#), there are generally three ways to provide the tightly regulated DC outputs required in this example.

The first is using three linear regulators from three different transformer outputs. This is the lowest efficiency solution. However, it is also the easiest to design and has the lowest component count. This solution requires an output winding for each supply to obtain acceptable power loss in the linear regulators.

The second is using three switching regulators (buck DC/DC) from a single transformer output. This provides excellent efficiency. However, the design complexity increases slightly and component count may increase. This solution requires only a single poorly regulated output from the transformer.

The third is a single flyback switching regulator. This also provides good efficiency, but is even more complex. The example above has no compelling reason to use a flyback regulator. A more appropriate set of requirements for this type of switching regulator will be presented later.

The solution in [Figure 5](#) shows how one would use linear regulators to obtain the desired regulated output voltages. The bulk capacitors across the rectified transformer windings may be reduced depending on the transformer being used. The linear regulators provide exceptional rejection of the 120 Hz ripple voltage found at the output of the transformer as long as the voltage does not go below the dropout voltage of the linear regulator. The regulator output capacitors are selected using the Application Hints in the datasheet for each part.

Each linear regulator must have a heat sink to prevent over heating. All calculations for power loss in the linear regulators will be performed at 132 V_{AC} input to the transformer and full load on the outputs. This is the worst case condition. The power loss in the linear regulator can be described as:

$$P_{\text{LOSS}} = V_{\text{IN}} \times I_{\text{GND}} + (V_{\text{IN}} - V_{\text{OUT}}) \times I_{\text{L}} \quad (1)$$

Where V_{IN} is the average DC from the transformer, I_{GND} is the ground pin current at full load (see data sheet), and I_{L} is the output current.

The LM3940 is the low dropout regulator chosen for the 3.3V output at 1 A_{DC}. V_{IN} is approximately 5.5 V_{DC}, and the calculated power loss is 2.8W ($I_{\text{GND}} = 110 \text{ mA}$).

The LP2960 is the low dropout regulator chosen for the 5.0V output at 0.5 A_{DC}. V_{IN} is approximately 7.3 V_{DC}, and the calculated power loss is 1.3W ($I_{\text{GND}} = 21 \text{ mA, max}$).

The LM2952 is the low dropout regulator chosen for the 12V output at 0.25 A_{DC}. V_{IN} is approximately 15.9 V_{DC}, and the calculated power loss is 1.3W ($I_{\text{GND}} = 21 \text{ mA, max}$).

The total output power is 8.8W and the total power loss is 5.4W. As a result, the line transformer must provide 14.2W. If lower cost non-LDO were used, there would be an additional 3.8W loss (because of the higher input voltage required, countered by lower supply current). This would result in a 27% increase in transformer size.

If a simple transformer with a single winding was used with LDO regulators, the extra loss would be 14.9W. 12W of this would be the loss in the 3.3V regulator dropping the voltage down from a 14V winding! As a result, three windings are required.

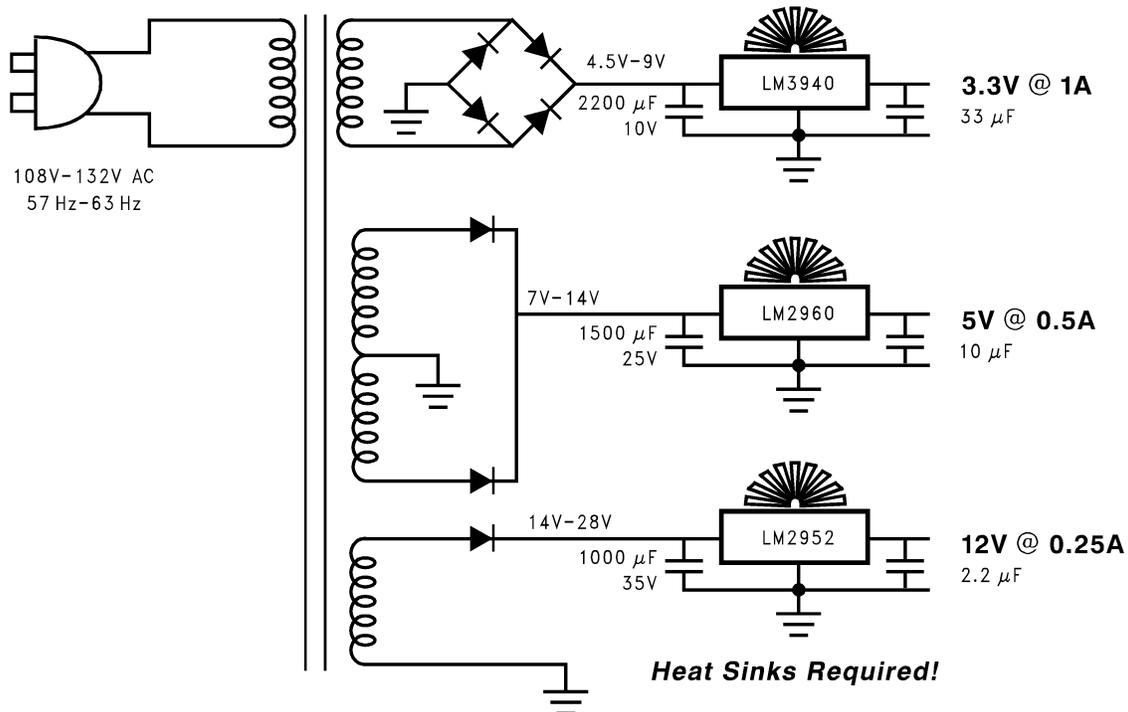


Figure 5. Power Supply Solution Using Linear Regulators

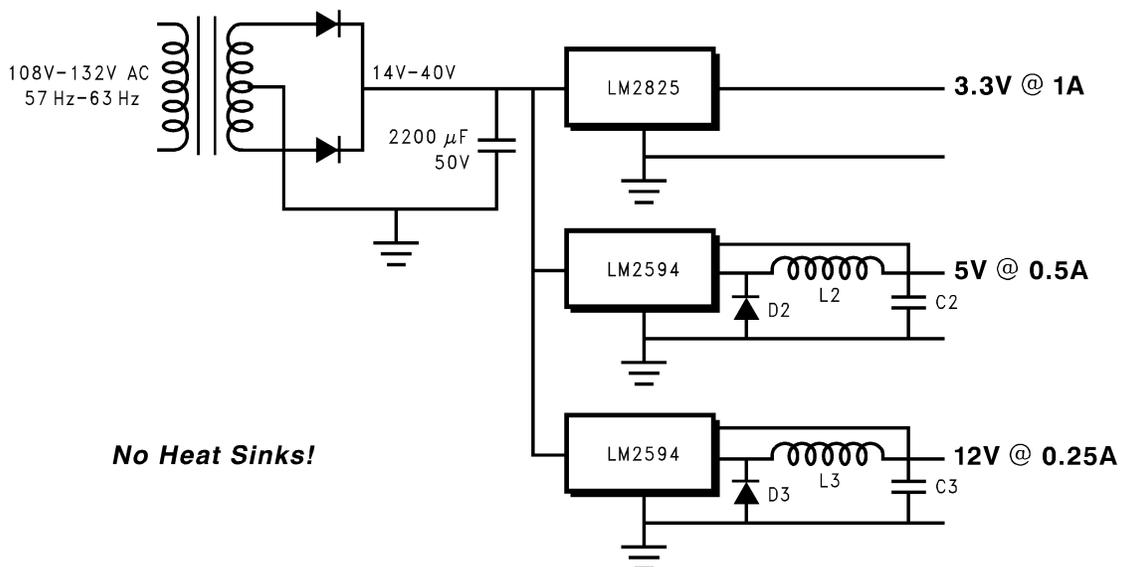


Figure 6. Power Supply Solution Using Step-Down Switching Regulators

Figure 6 shows a solution using three switching regulators. The average voltage supplied by the line transformer is 14V–40V. This voltage represents a relaxation of the line transformer load regulation (from 25% to 40%) and can allow a smaller transformer. Again, the size of the input capacitor may be reduced and 120 Hz ripple rejection is excellent.

None of the switching regulators requires a heat sink given proper heat sinking to the PCB (Printed Circuit Board).

The components are selected by a software design tool, Switchers Made Simple (ver. 4.2.1), which is available for use with SIMPLE SWITCHER DC/DC Converters. Texas Instruments website, www.ti.com is the best place to get a current version.

The overall efficiency of this switching regulator solution is approximately 80%. Therefore, the line transformer only needs to provide 11W. By reducing the required power, line transformer used in this solution can be 22% smaller than that used in the previous linear regulator solution. Also, only one output winding is required, thus simplifying the transformer manufacture.

4 Design for 3-Output Modem Power Supply

The design of [Figure 7](#), for a modem application, required a DC/DC converter that was easy to configure and had low power loss. The modem was external and required that all output voltages be generated from a single output on a plug in wall transformer. To meet these needs, a multi-output flyback switching regulator was used to regulate the voltage developed by the line transformer. Not only does the use of a switching regulator keep the power loss much lower than if a linear regulator were used, the flyback topology is well suited for providing negative voltages while using one of the positive outputs as the feedback point.

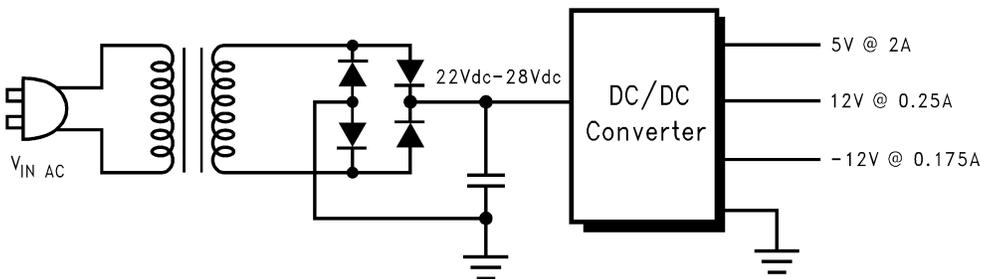


Figure 7. 3-Output Flyback Converter Provides Power for Modem

The easiest way to develop such a DC/DC converter is to generate a SIMPLE SWITCHER converter design with the software tool “Switchers Made Simple.” The customer requirements were entered into the software and the resulting design is shown in [Figure 8](#). This DC/DC converter is approximately 75% efficient.

One important thing to note is that only the +5V output is directly regulated. The 12V and -12V outputs will vary over line and load much more than the 5V winding. For example, if the 5V winding only varies 1% over line and load, the 12V outputs may vary by 5%. This phenomenon is called “cross-regulation”. It is a function of the design of the flyback transformer and the line and load range on all the outputs. For more information on this subject, reference a paper published in the 1995 PCIM Proceedings entitled *Improving Cross Regulation of Multiple Output Flyback Converters* ([SNVA562](#)).

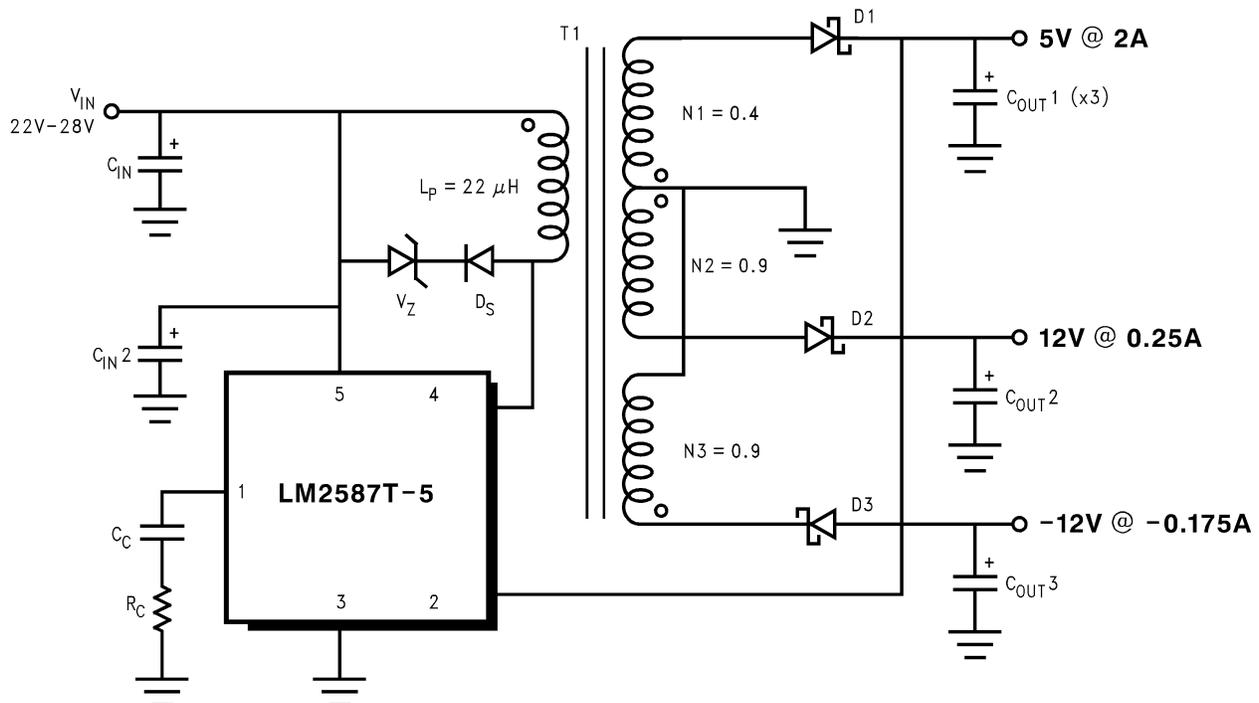


Figure 8. Schematic for Power Supply of Figure 7

U ₁	5.00A	TI	LM2587T-5
T ₁	(Software provides detailed specification ...)		
C _{IN}	270.00 μF ⁽¹⁾	Nichicon	UPL1J271MRH
C _{IN2}	100.00 nF	AVX	SR595C104KAA
C _{OUT1}	2.70 mF (x3)	Nichicon	UPL1V272MRH
C _{OUT2}	330.00 μF	Nichicon	UPL1V331MPH
C _{OUT3}	270.00 μF	Nichicon	UPL1V271MPH
R _C	3.00 kW	Dale	CCF-07302J
C _C	330.00 nF	AVX	TAPA334K035R
D1	Schottky	Motorola	MBR745
D2	Schottky	Motorola	MBR1100
D3	Schottky	Motorola	MBR1100
VZ	20.00V	Motorola	SA20A
D _S	Ultrafast	Motorola	MUR120

⁽¹⁾ May require a larger value if used as the bulk capacitor for the line transformer.

5 Undervoltage Lockout

Although the power supply is designed to operate properly over a given input voltage range, there is no ensured specification that the line voltage available to the customer will always stay within that range. For over-voltage and transient conditions, we can protect our power supply and other internal circuitry by using a zener diode to clamp the input voltage. For brown out conditions we can use an undervoltage lockout circuit in conjunction with the shutdown pins on the Simple Switchers.

The undervoltage lockout must have special features due to the load regulation of the 60 Hz transformer. If we were to set a fixed on/off voltage for the power supply the following sequence of events would occur:

1. The input voltage falls below our minimum operating point (say 105 V_{AC}).
2. The undervoltage circuit trips and turns off the power supply and equipment.

3. The 60 Hz transformer is unloaded and the output voltage jumps up above the on/off trip point.
4. The power supplies try to start and pulls the output of the 60 Hz transformer down again.
5. Steps 2 through 4 repeat constantly causing the power supplies and equipment to oscillate on and off.

The problem is the difference between no-load and loaded output voltage of the 60 Hz transformer. Our undervoltage lockout must be able to turn on the power supplies once the input voltage is within our operating range (about 108 V_{AC}). But, once the supplies turn on, recognize that the output voltage will be pulled down, and not turn off until the input falls below our operating minimum (about 100 V_{AC}).

By using an undervoltage circuit with hysteresis (illustrated in [Figure 9](#)), we can prevent the power supply from oscillating on and off.


V_(turn on) is the no load voltage from the transformer. This is very close to

$$108 \cdot \frac{N_s}{N_p} \cdot \sqrt{2} \tag{2}$$

V_(turn off) is the full load voltage from the transformer at 100 V_{AC}. This value is very sensitive to the load conditions for each design, and should be measured on the bench during design.

ΔV is the difference between these two voltages, and is the value we will use for the undervoltage lockout hysteresis.

The schematic and equations of [Figure 10](#) will provide a hysteretic undervoltage lockout circuit design. Some assumptions have been made to simplify the equations, primarily that R_h >> R₁ and R₂. Also, the current through R₁ and R₂ should be at least 10 times greater than the input current to the comparator. The LM6511 input current is typically less than 50 nA (datasheet maximum over all conditions is 200 nA which occurs at -40°C).

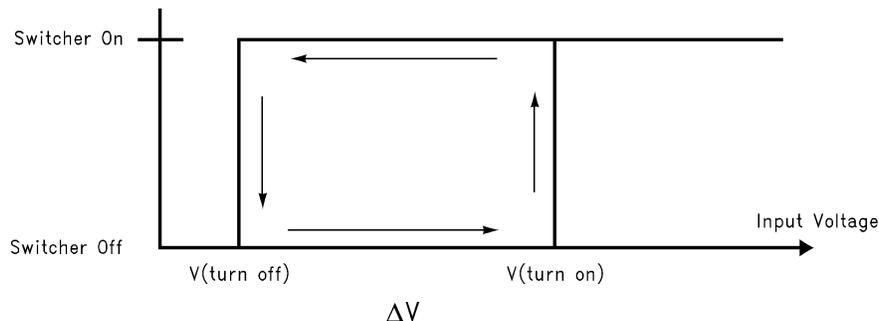

- V_(turn on) = No load voltage from transformer @108 V_{AC}.
- V_(turn off) = Full load voltage from transformer @100 V_{AC}
- ΔV = V_(turn on) - V_(turn off); Hysteresis

Figure 9. Hysteresis Controls Turn-on and Turn-off Thresholds of Undervoltage Circuit

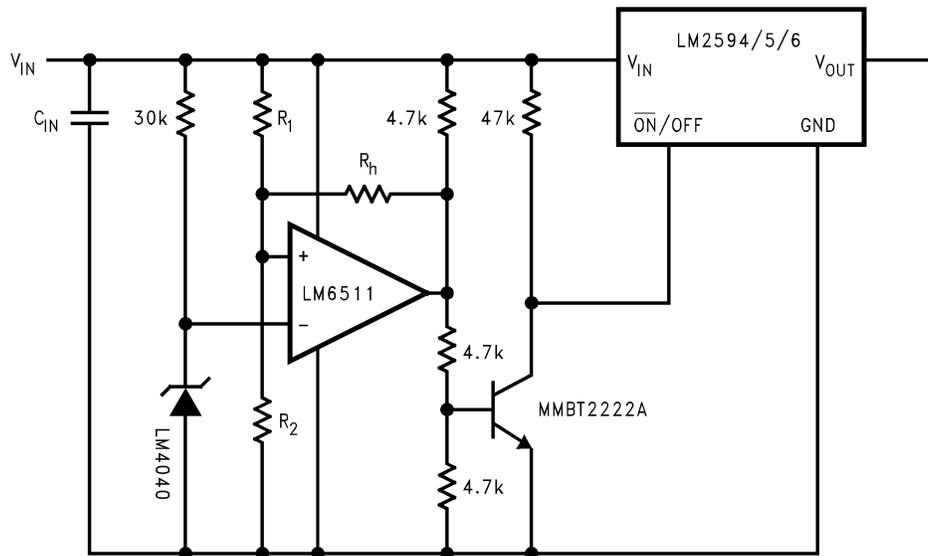


Figure 10. Undervoltage Lockout Circuit with Hysteresis

Once the circuit has been incorporated with the complete power supply and powered circuitry, the values of R_h , R_1 , and R_2 can be optimized.

Make sure to check that the regulator you are using turns on by grounding the on/off pin. Some regulators turn off when grounding this pin. If the logic needs to be inverted, just swap the inputs to the comparator.

6 Comparison of Power Supply Solutions

Table 1. Linear Regulator Solutions vs Switching Regulator Solutions

Linear Regulators	Switching Regulators
No EMI from power supply	Smaller line transformer
	• Lower power
	• One winding
	• Poorer regulation okay
Fewer components in converter	One diode bridge and bulk capacitor required
Typically lower cost	No heat sinks ⁽¹⁾

⁽¹⁾ Small heat sinks may be required at higher ambient temperature or output power levels

As indicated in Table 1, each type of regulator has its own strengths and weaknesses.

The linear regulator provides a fast simple solution. Overall, the linear regulator will be the lowest cost solution. The drawbacks are a complicated line transformer with multiple output windings, low efficiency, and heat sinks to dissipate the power lost in the regulator.

A multi-output line transformer, with output voltages close to the desired levels, can be used with low-dropout linear regulators on each output. This yields a low-component-count power supply.

These LDOs may include:

- LP2980/2 for ≤ 50 mA loads
- LP2950/51/81 for ≤ 100 mA loads
- LP2952/53/54/57 for ≤ 250 mA loads
- LP2960 for ≤ 500 mA loads
- LM3940 for ≤ 1 Amp loads

Switching regulators provide a more efficient solution at the expense of slightly greater complexity. The line transformer can be less expensive than that used for the linear regulator. One benefit of higher efficiency is the ability to omit heat sinks unless the ambient temperature is very high (>50°C at rated current). In some cases the cost of adding a heat sink to a linear regulator is more than a switching regulator.

A single-output line transformer can be used with multiple buck regulators. This yields a high-efficiency power supply with independent control of each output. Or, you could use a single multi-output flyback switching regulator. This yields a relatively simple, high-efficiency supply.

One issue which may arise is EMI from the switching regulators getting back into the AC line. Linear regulators do not generate any EMI. Switching regulators may require a filter stage at the output of the line transformer if the bulk capacitor does not provide sufficient attenuation at the switching frequency.

While new requirements for harmonic content and power factor correction (PFC) are being put in place in Europe, they will not be required on the sub-50W power supplies we are discussing here. Power supplies above 75W input power will require input stages to limit harmonic distortion. All line frequency transformers feeding into an output rectifier and bulk capacitor have distorted input currents. For this reason, none of the solutions here are intended to address these requirements.

7 Simple Switcher Converters

While there are many types of DC/DC voltage converters on the market, there are few that combine the ease-of-use and adaptability of the SIMPLE SWITCHER DC/DC converters. See [Table 2](#) for a selection guide of these converters.

SIMPLE SWITCHER products offer ensured system specifications, such as maximum output voltage tolerance, not just the tolerance of a subsection of the integrated circuit.

In addition, a SIMPLE SWITCHER is easy to configure, with a variety of standard output voltages available. A few external components are required, and they are fully specified in the product documentation. Components which may be unfamiliar to the system designer, such as magnetics, are available as standard part numbers from other vendors.

“Switchers Made Simple” design software is also available from www.ti.com, to customize a SIMPLE SWITCHER converter for a specific application.

Table 2. SIMPLE SWITCHER Power Converters

Buck Converters	Switching Frequency	Output Current	Input Voltage Range	Features
LM2825	150 kHz	1.0A	4.75 V _{DC} –40 V _{DC}	Fully integrated DC/DC Converter IC in a 24-pin DIP requiring no external components with TTL on/off and soft-start
LM2671	260 kHz	0.5A	7 V _{DC} –40 V _{DC}	High efficiency, SO-8, sync to 400 kHz, softstart, TTL on/off
LM2672	260 kHz	1.0A	7 V _{DC} –40 V _{DC}	High efficiency, SO-8, sync to 400 kHz, softstart, TTL on/off
LM2674	260 kHz	0.5A	7 V _{DC} –40 V _{DC}	High efficiency, SO-8, TTL on/off
LM2675	260 kHz	1.0A	7 V _{DC} –40 V _{DC}	High efficiency, SO-8, TTL on/off
LM267X	260 kHz	3.0A, 5.0A	7 V _{DC} –40 V _{DC}	Future products, check for availability
LM2594	150 kHz	0.5A	5 V _{DC} –40 V _{DC}	SO-8, TTL on/off
LM2595	150 kHz	1.0A	5 V _{DC} –40 V _{DC}	TTL on/off
LM2596	150 kHz	3.0A	5 V _{DC} –40 V _{DC}	TTL on/off
LM2597	150 kHz	0.5A	5 V _{DC} –40 V _{DC}	SO-8, Soft-start, μ P reset and error flag, TTL on/off
LM2598	150 kHz	1.0A	5 V _{DC} –40 V _{DC}	Soft-start, μ P reset and error flag, TTL on/off
LM2599	150 kHz	3.0A	5 V _{DC} –40 V _{DC}	Soft-start, μ P reset/error flag, TTL on/off
LM2574	52 kHz	0.5A	7 V _{DC} –40 V _{DC}	TTL on/off
LM2574HV			7 V _{DC} –60 V _{DC}	
LM2575	52 kHz	1.0A	7 V _{DC} –40 V _{DC}	TTL on/off
LM2575HV			7 V _{DC} –60 V _{DC}	
LM2576	52 kHz	3.0A	7 V _{DC} –40 V _{DC}	TTL on/off

Table 2. SIMPLE SWITCHER Power Converters (continued)

Buck Converters	Switching Frequency	Output Current	Input Voltage Range	Features
LM2576HV			$7 V_{DC}$ – $60 V_{DC}$	
Flyback or Boost Converters		Switch Current		
LM2585	100 kHz	3.0A	$4 V_{DC}$ – $40 V_{DC}$	
LM2586	100 kHz	3.0A	$4 V_{DC}$ – $40 V_{DC}$	Synch, on/off, freq. adj to 200 kHz
LM2587	100 kHz	5.0A	$4 V_{DC}$ – $40 V_{DC}$	
LM2588	100 kHz	5.0A	$4 V_{DC}$ – $40 V_{DC}$	Synch, on/off, freq. adj to 200 kHz
LM2577	52 kHz	3.0A	$4 V_{DC}$ – $40 V_{DC}$	

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com