



Literature Number: SNAP001

PLL Fundamentals


Part 1: PLL Building Blocks

Dean Banerjee

Overview

- Oscillators
 - Crystal Oscillators
 - High Frequency Oscillators
 - Voltage Controlled Oscillators (VCO)
 - Silicon Voltage Controlled Oscillators
 - Oscillator Phase Noise
- Other PLL Building Blocks
 - Counters
 - Phase Detector/Charge Pump
 - Loop Filter


Reference Oscillator

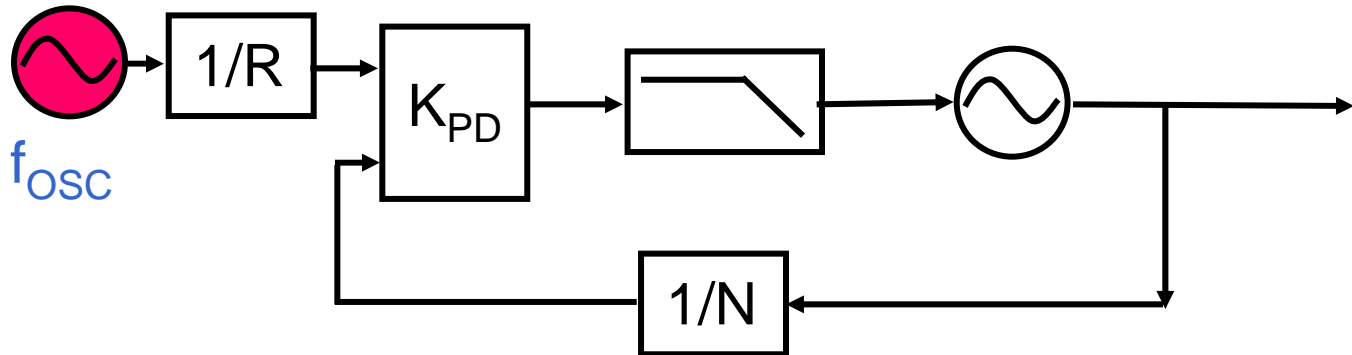

- Typically a fixed frequency of operation = f_{osc}
- Can come in many forms
 - Crystal
 - Crystal Oscillator (XO)
 - Temperature Compensated Crystal Oscillator (TCXO)
 - Oven Controlled Crystal Oscillator (OCXO)
 - Output from another device
 - Recovered clock
 - DDS Signal




The Traditional Oscillator

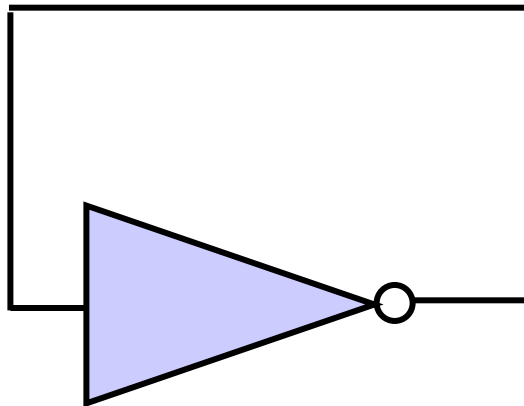

- **Output of Inverter is fed back to the input**
- **Frequency of oscillation is determined by delay of inverter**




The Traditional Oscillator

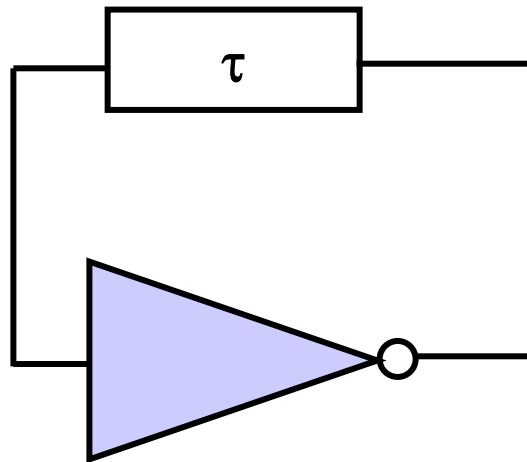


- Delay of τ can be added in feedback path to set the frequency
 - $f = 1/\tau$
- A filter can also be added for a sine wave. Note that it is impossible to filter without delay, so a filter and a delay are related.

Typical Crystal Oscillator

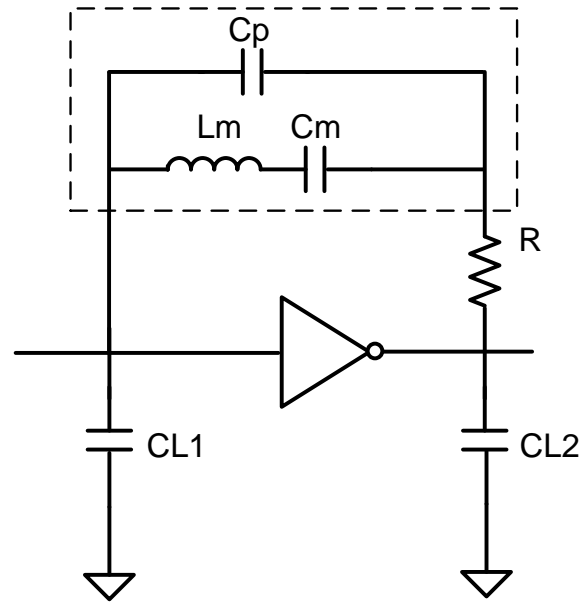

- **Crystal**
 - **L_m (Motional Inductance)**
 - **C_m (Motional Capacitance)**
 - **C_p (Parallel Capacitance)**



VCO (Voltage Controlled Oscillator)

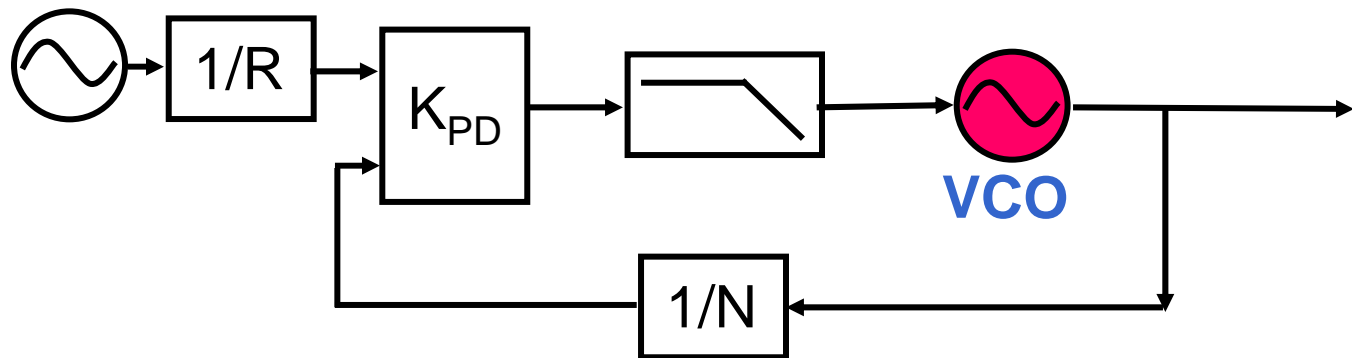

- **The VCO (Voltage Controlled Oscillator)**
 - Converts voltage to frequency
 - Generates frequencies over restricted frequency range
 - Frequency drifts considerably over temperature, voltage and process
 - Typically Much higher frequency than the reference oscillator



VCO Frequency Tuning

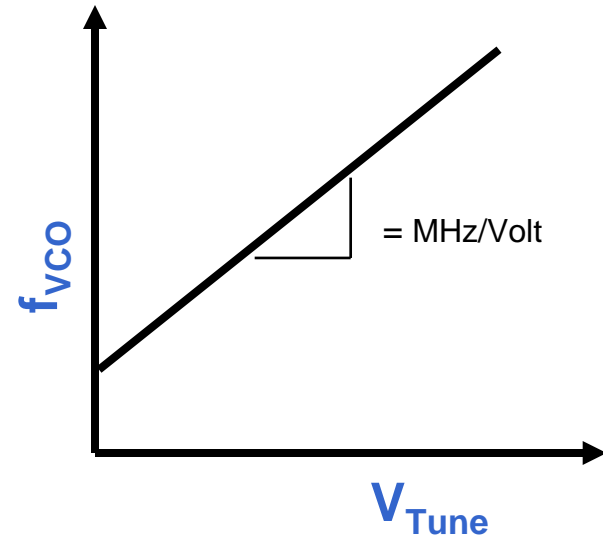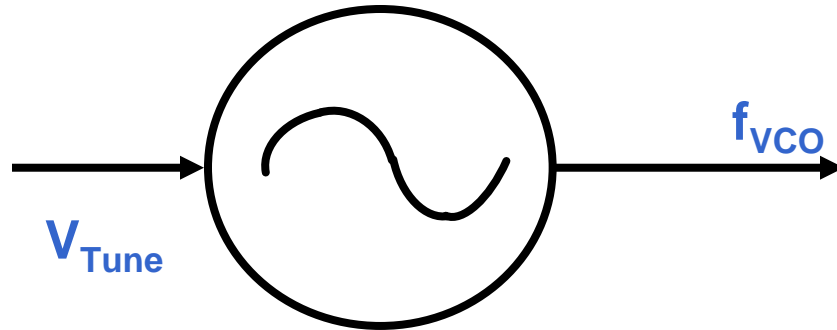


- **VCO Figures of Merit**

- Tuning Range
- Output Power
- Tuning Sensitivity (K_{VCO} in MHz/Volt)
- Tuning Linearity (Want K_{VCO} constant)
- Pushing (Frequency shift over supply voltage)
- Pulling (Frequency shift over load)
- Harmonics (Undesired Multiples of intended frequency)
- Power Consumption
- Size
- Phase Noise

Understanding How VCOs Work

- **Crystals and VCOs are Not the Same**
 - Crystals are typically limited to lower frequencies (<100 MHz)
 - Crystals typically have a frequency range that is too narrow for most applications
- **Hard to Relate VCO Circuits to Crystal Circuits**
 - Higher frequency oscillators like VCOs often contain transistors and MOS devices that deal with currents, not voltages
 - Trying to relate a VCO schematic to this traditional oscillator model takes a lot of imagination.


A Better Way to Think of a VCO

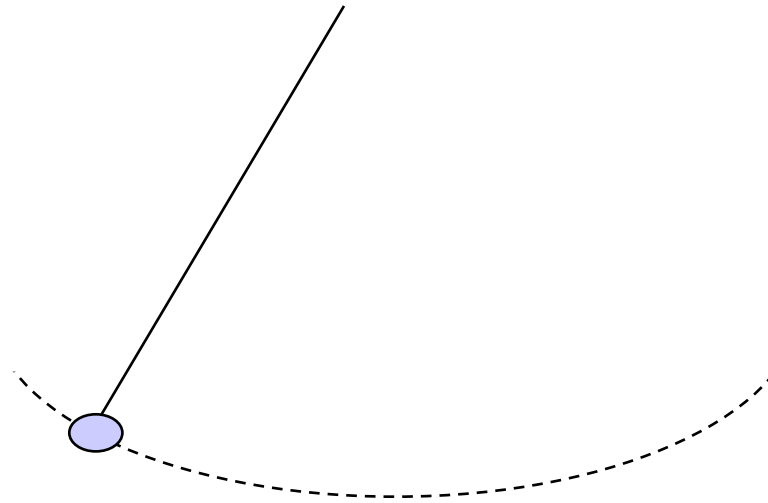

- Neglecting the Impacts of Friction, the pendulum conserves energy. It just converts it between potential and kinetic energy
- In the real world, there is friction, so a small stimulus needs to be applied to keep the circuit going.




The Tank Circuit

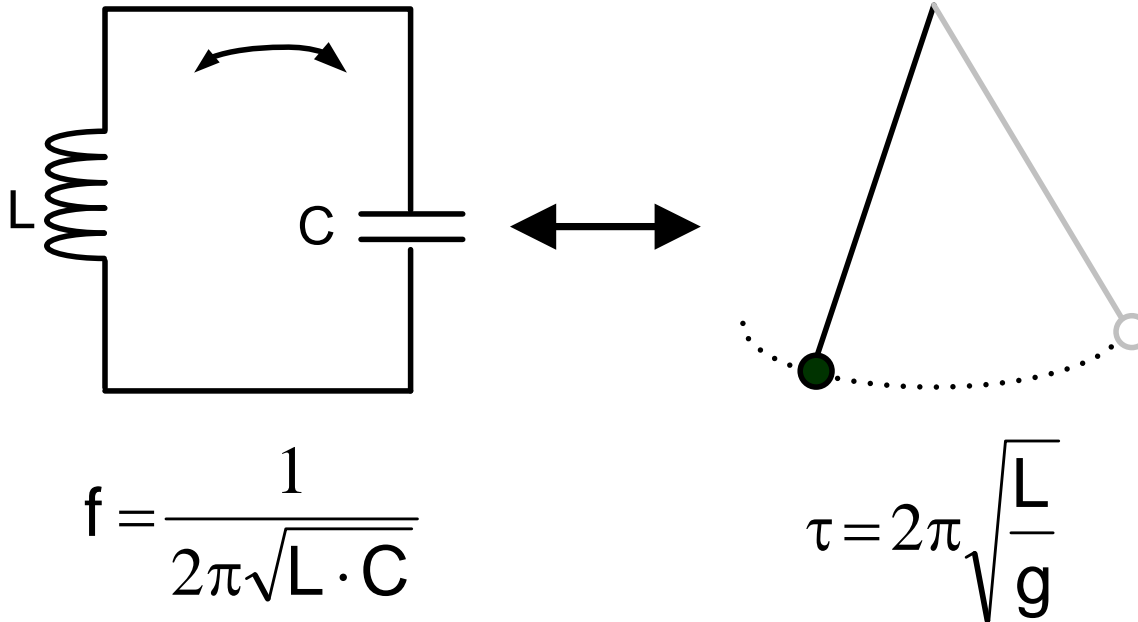

- Tank circuit can be viewed as an electronic spring.
 - When voltage across the capacitor is maximum, current in the inductor is minimum, and vice versa
- Assuming no parasitic resistances, circuit would go on forever, but wouldn't that be nice?


The Real World Inductor

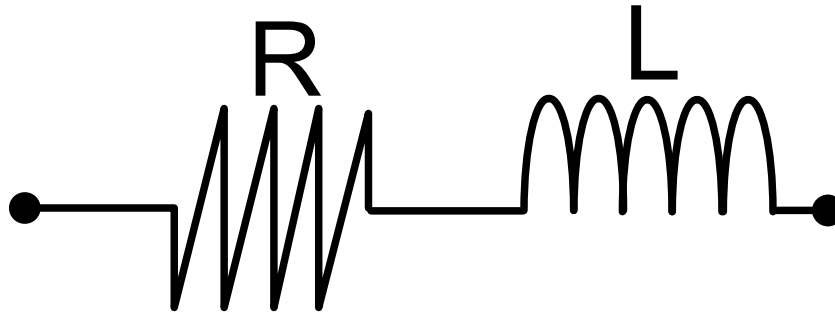

$$Q_L(f) = \frac{X_L}{R_L} = \frac{2\pi \cdot f \cdot L}{R}$$


- **Q is the quality factor, measured at the frequency of interest**
- **Parasitic resistances, such as the one in the inductor cause the circuit to eventually stop oscillating.**
- **Just as with the pendulum, it is necessary to provide some stimulus to keep the circuit going.**

Now Add the Stimulus

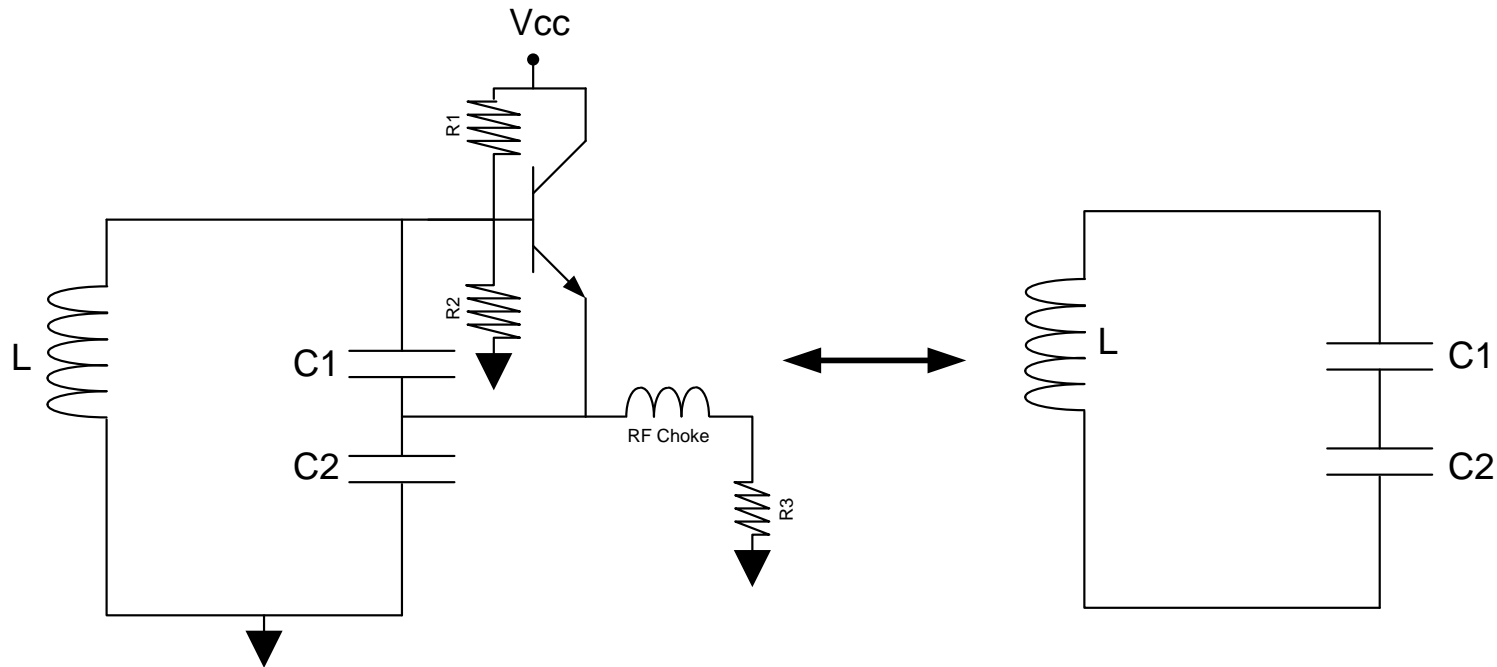


- **Amplified signal from emitter is lightly coupled into the circuit to sustain oscillation**
- **Above Circuit is Colpitts Oscillator**

Typical Clapp (Clapp-Gouriet) Oscillator

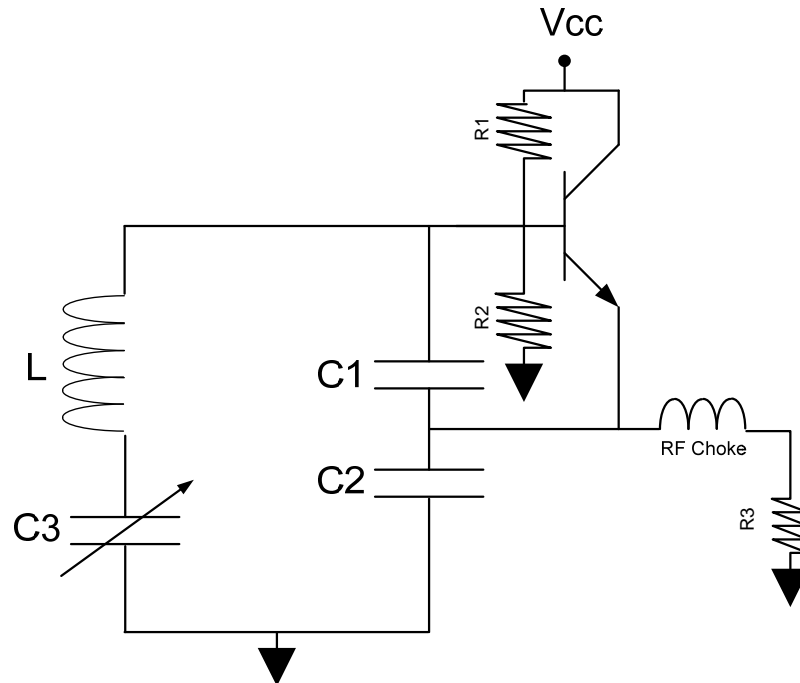

- **Very similar to the Colpitts oscillator, except ..**
 - **Series capacitance C3 (Often adjustable), is typically added**
 - **This is better than Colpitts with a variable capacitor because changing the C3 capacitance does not change the feedback at C1 and C2.**

The Varactor Diode

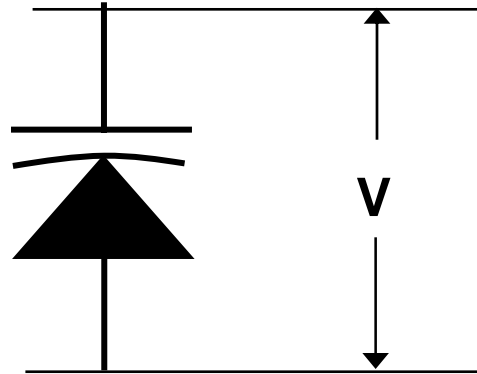


- To implement the variable capacitance for the VCO, a varactor diode is often used. As more voltage is applied to the diode, the capacitance decreases

$$C_{Varactor}(V) = \frac{C_{Varactor}(0\text{volts})}{\sqrt{\phi + V}}$$

- 15-20 pF of capacitance is typical

Complete VCO Circuit

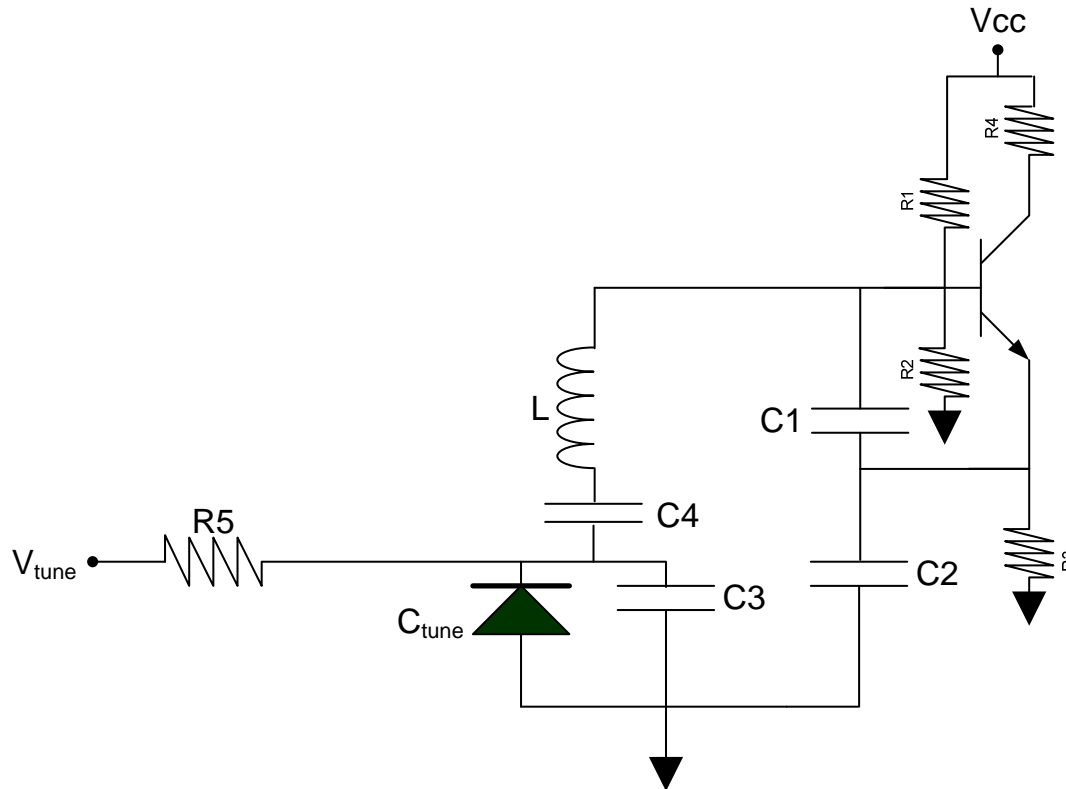


- **Varactor Diode Capacitance Adds to C3**
 - Larger C3 => better Phase Noise, but less tuning range
- **Resistor R5 isolates Tuning voltage from Loop Filter**

Overview

- Oscillators
 - Crystal Oscillators
 - High Frequency Oscillators
 - Voltage Controlled Oscillators (VCO)
 - **Silicon Voltage Controlled Oscillators**
 - Oscillator Phase Noise
- Other PLL Building Blocks
 - Counters
 - Phase Detector/Charge Pump
 - Loop Filter




Integrating VCOs on Silicon

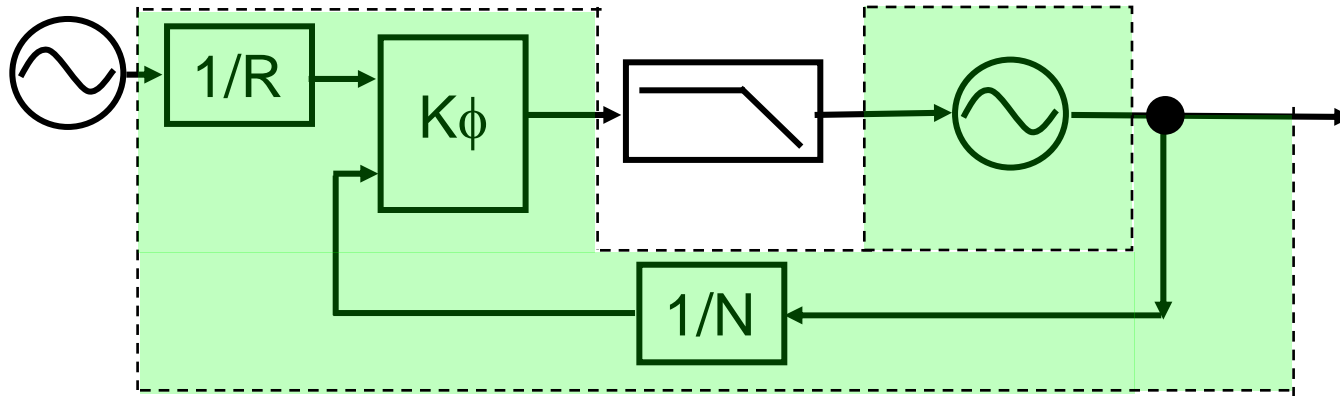

- **Inductance is Typically Formed by Bond Wires**
 - VCO frequencies tend to be higher due to low inductances
 - Can also do small inductors on silicon, but they are small
 - Can allow external inductors to be added for lower frequencies
 - Often easier to generate a higher frequency and divide it down
- **Capacitance is Formed by an Internal Bank of Capacitors**
 - Frequency calibration is typically necessary




Bank of Switched Capacitors

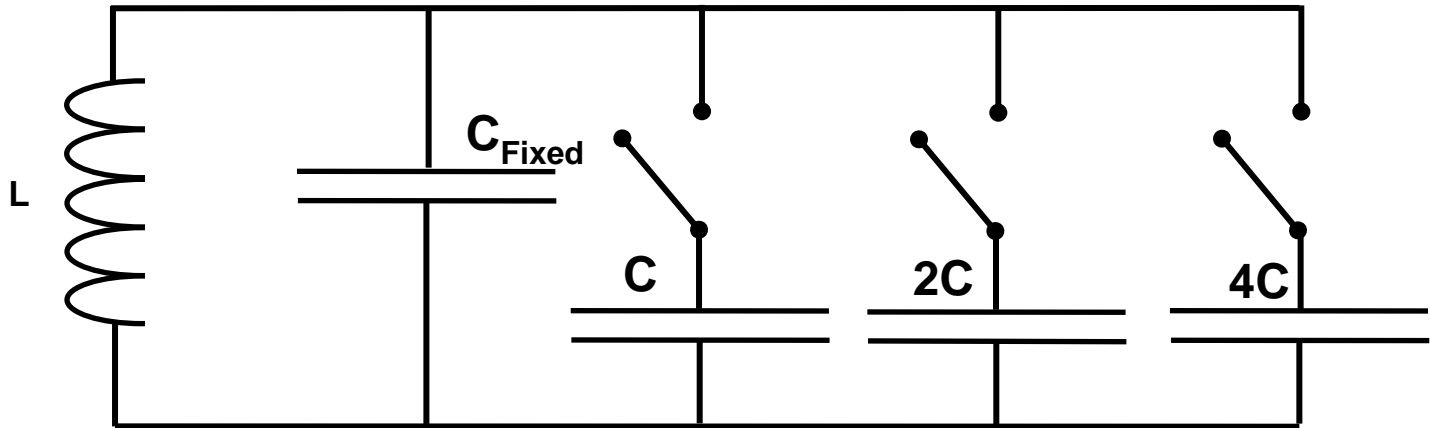

- Capacitors can be switched in and out to create multiple bands
 - The best phase noise and lowest tuning gain is often at the lowest frequency with all the capacitors switched in
- Logic is necessary to switch capacitors in and out to find the correct combination
 - On resistance of the switches is one source of phase noise

Silicon VCO Tuning Range

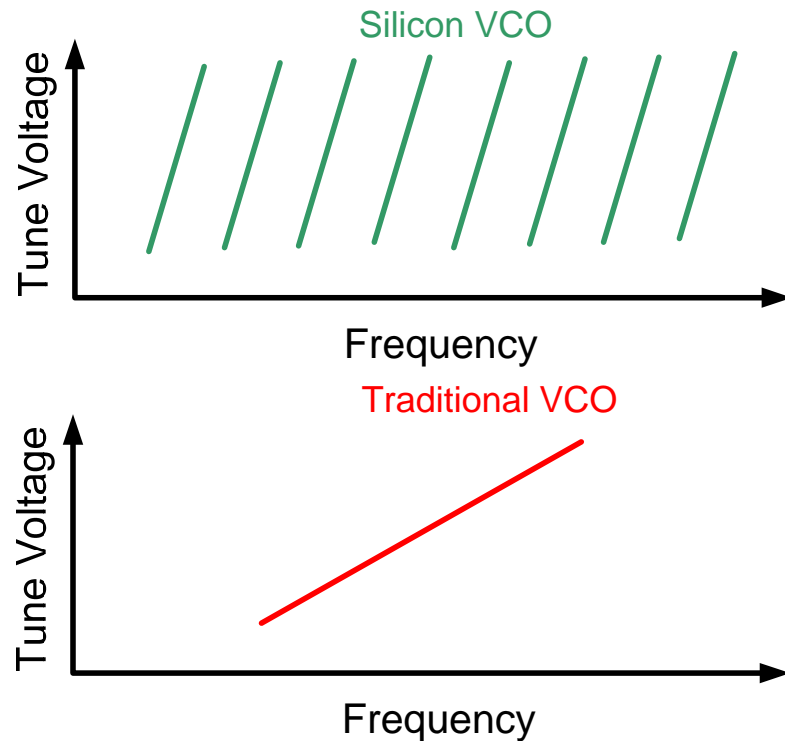- **VCO Range Divided into many bands**
- **These bands cover the whole frequency range and need**
- **Bands need to overlap to account for temperature drift**
- **Correct band is selected when frequency is changed**
- **This technique allows wider tuning range without sacrificing phase noise**





Things to Watch for with Silicon VCOs

- **Temperature Drift**


- If temperature changes without the VCO doing its frequency calibration, tuning voltage drifts towards a rail
- Typically bands overlap to accommodate for this
- National has a proprietary method to deal with this issue

- **Calibration Time**

- Faster for higher OSCin frequencies
- Improves lock time if bandwidth is narrow or if there are large cycle slipping issues
- Hurts lock time if loop filter is fast (i.e. <400 us)

LMX2531 VCO Phase Noise Optimization

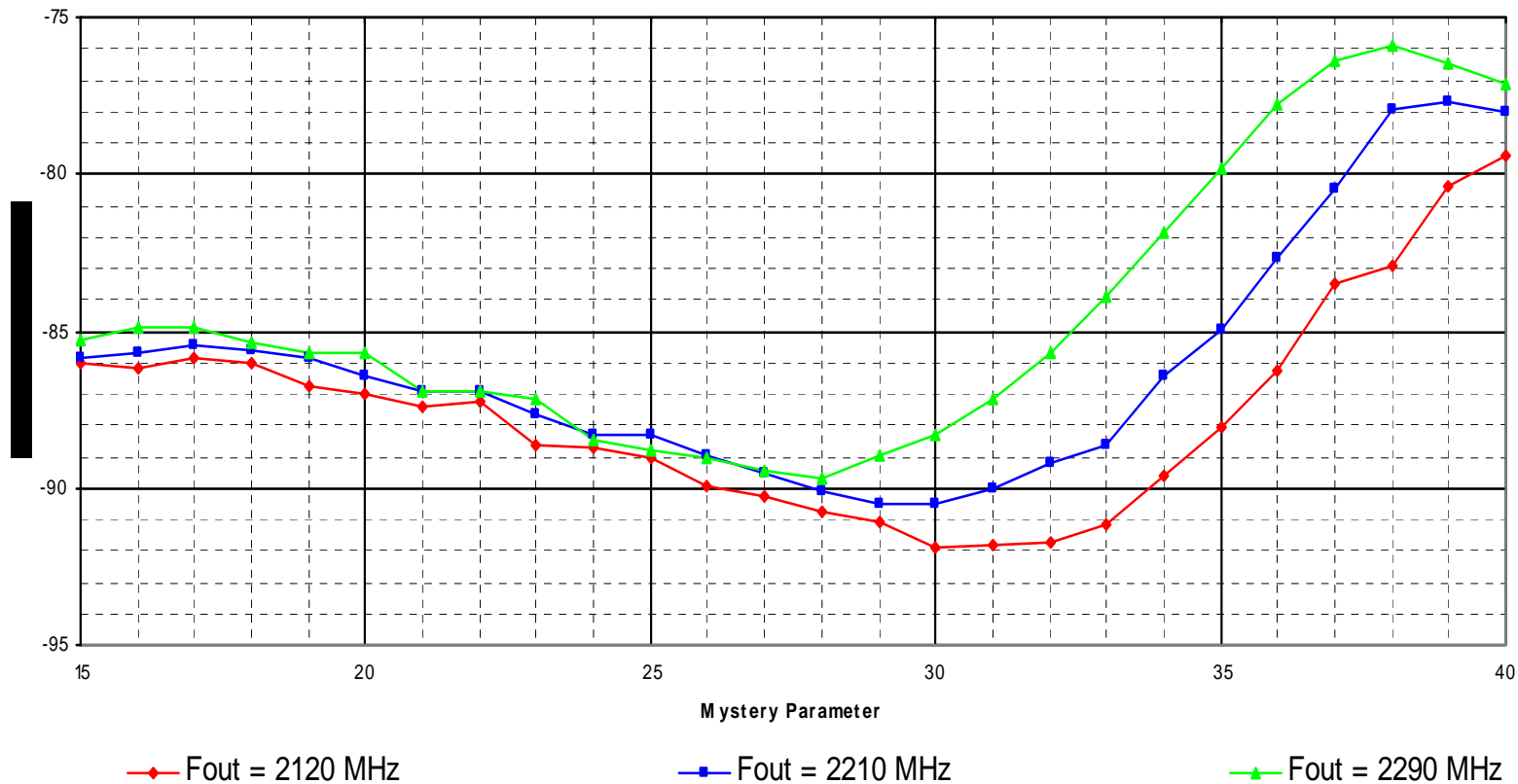Phase Noise vs Mystery Parameter at 10 kHz Offset





Traditional vs. Silicon VCOs

- **Traditional VCO Advantages**

- Potentially better performance (tuning range and/or phase noise) if there is a large tuning voltage supplied
- Can be customized to frequency


- **Silicon VCO Advantages**

- Lower Cost
- Smaller Size
- Higher Reliability
- VCO to PLL mismatch issues eliminated
- Wider tuning range for a given supply voltage
- Extra bells and whistles
 - Programmable Output Power
 - Switchable Dividers

Overview

- Oscillators
 - Crystal Oscillators
 - High Frequency Oscillators
 - Voltage Controlled Oscillators (VCO)
 - Silicon Voltage Controlled Oscillators
 - **Oscillator Phase Noise**
- Other PLL Building Blocks
 - Counters
 - Phase Detector/Charge Pump
 - Loop Filter

Classical Oscillator Phase Noise Model

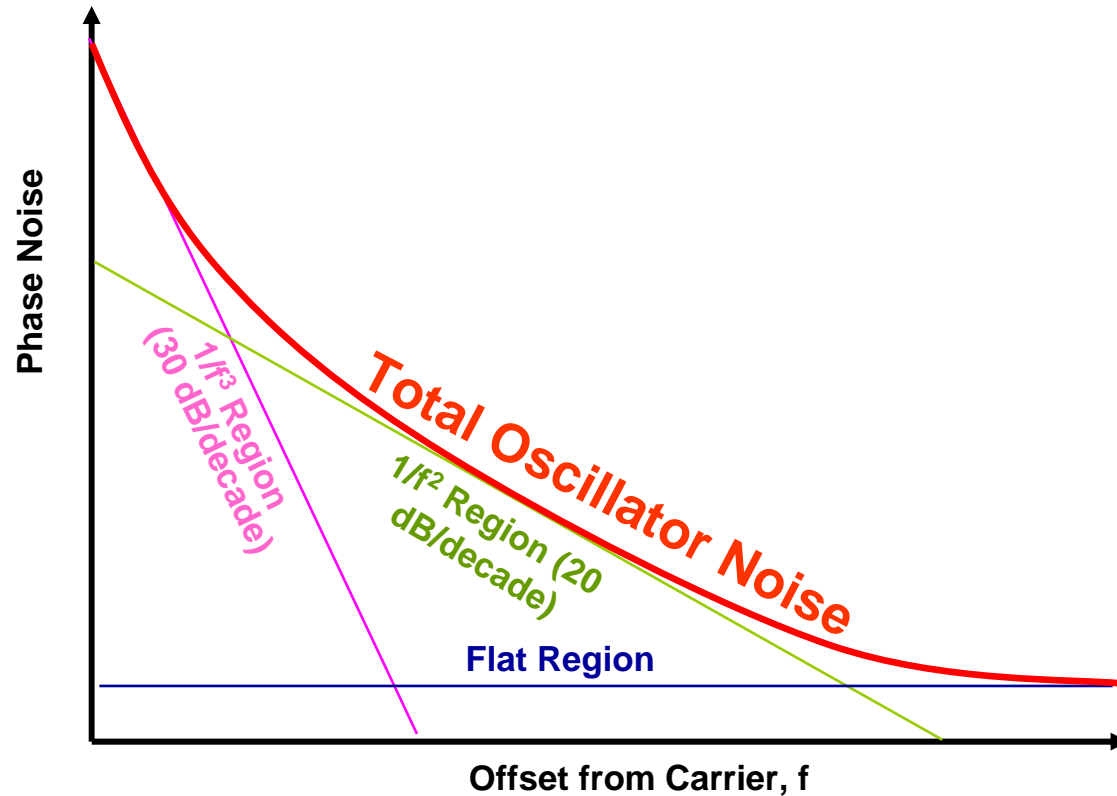



Lesson's Equation

- Lesson's Equation

$$L(f) = 10 \cdot \log \left(N_3 \cdot \left(\frac{f_{\text{default}}}{f} \right)^3 + N_2 \cdot \left(\frac{f_{\text{default}}}{f} \right)^2 + N_0 \right)$$

Diagram illustrating the regions of the equation:

- $1/f^3$ Region points to the $N_3 \cdot \left(\frac{f_{\text{default}}}{f} \right)^3$ term.
- $1/f^2$ Region points to the $N_2 \cdot \left(\frac{f_{\text{default}}}{f} \right)^2$ term.
- Flat Region points to the N_0 term.

- Parameters

- N_3 , N_2 , N_0 are constants to be discussed later
- f_{default} is the a default frequency where these constants are defined, and is constant
- f is the offset frequency



1/f³ Region

- **Noise Coefficient**

$$N3 = \frac{1}{f^3} \text{ Noise Coefficient} = \frac{F \cdot k \cdot T}{P} \cdot \frac{f_{1/f^3} \cdot f_{vco}^2}{8 \cdot Q_L^2 \cdot f_{default}^3}$$

- **Phase noise goes down by 30 dB/decade in this region**
- **Phase Noise is caused by the flicker noise of the transistor**
- **Q_L is the loaded Q of the inductor, and is the most important term and the one with the greatest influence**



1/f² Region

- **N2 Noise Coefficient**

$$N2 = \frac{1}{f^2} \text{ Noise Coefficient} = \frac{F \cdot k \cdot T}{P} \cdot \frac{f_{vco}^2}{8 \cdot Q_L^2 \cdot f_{default}^2} + \frac{2 \cdot k \cdot T \cdot R_{var} \cdot K_{vco}^2}{f_{default}^2}$$

- **Phase Noise goes down by 20 db/decade in this region**
- **R_{var} is the noise resistance of the varactor diode. Note that for a larger VCO gain, K_{vco}, this noise is multiplied.**
 - Putting multiple varactor diodes in parallel helps reduce this noise.
- **Loaded Q_L is also important**



Flat Region

- **Noise Coefficient**

$$N0 = VCO \text{ Noise Floor} = \frac{F \cdot k \cdot T}{P}$$

- **Terms here**


- F is the noise figure
 - T is the temperature in Kelvin
 - k is Boltzmann's constant
 - P is the output power
- **Output buffer dominates here. High output power is good for phase noise because of the thermal noise floor**
 - **Theoretically, the best VCO phase noise is at cold temperature and worse at hot temperature in all three regions**

Overview

- Oscillators
 - Crystal Oscillators
 - High Frequency Oscillators
 - Voltage Controlled Oscillators (VCO)
 - Silicon Voltage Controlled Oscillators
 - Oscillator Phase Noise
- Other PLL Building Blocks
 - **Counters**
 - Phase Detector/Charge Pump
 - Loop Filter




Basic PLL Operation

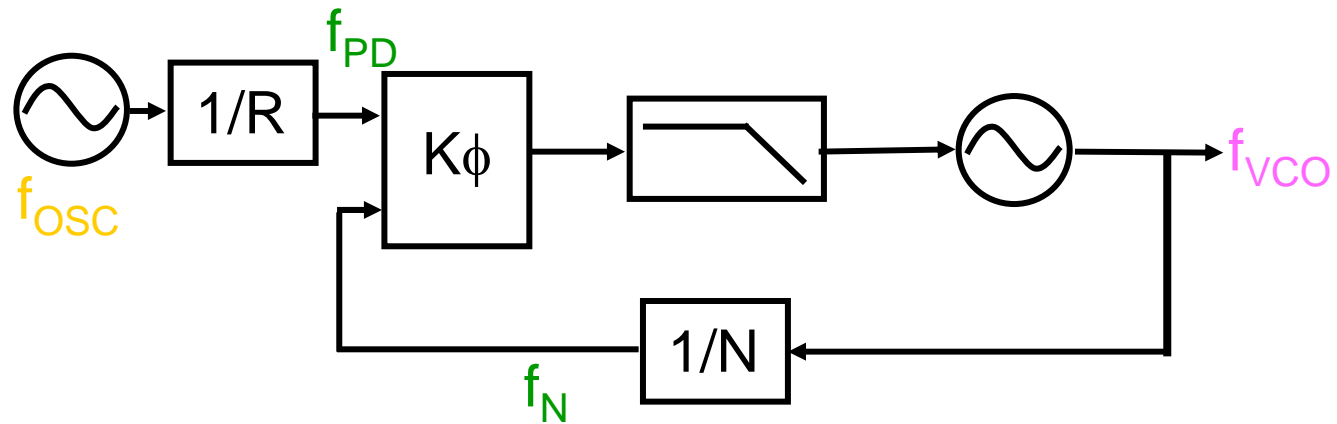

$$f_{osc} / R = f_{PD} = f_N = f_{vco} / N$$


$$f_{vco} = f_{osc} \bullet (N/R)$$

Reference Oscillator and R Counter

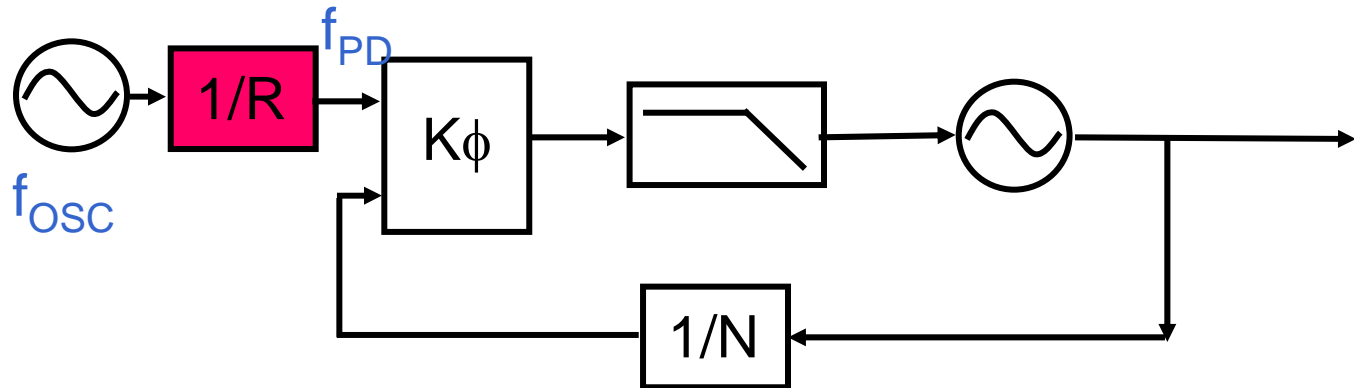

- **Phase Detector Frequency**
 - Fixed frequency of operation = f_{PD}
 - Equal to the channel spacing for an integer PLL
- **R Counter Value**
 - $R = f_{OSC} / f_{PD}$

N Counter

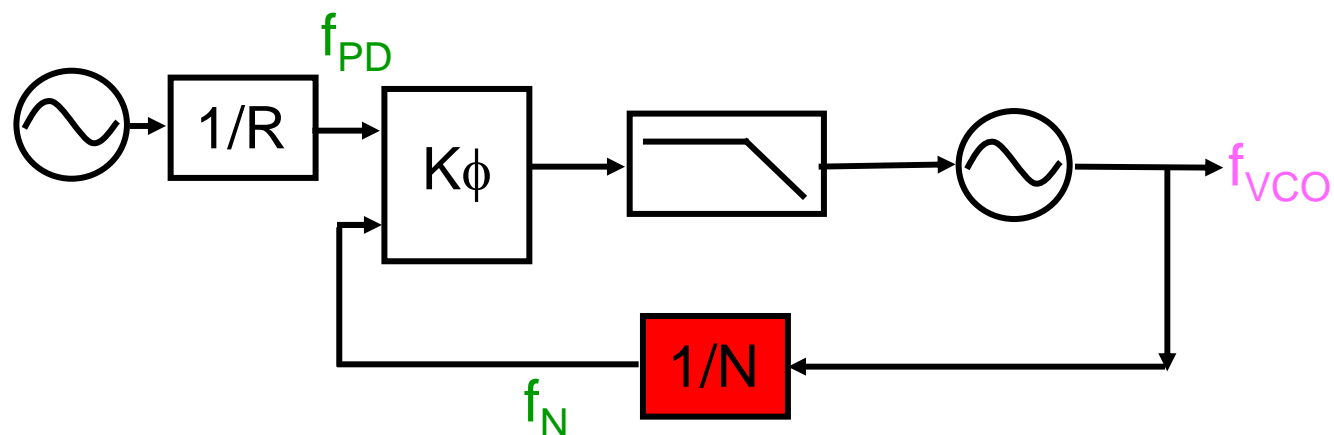


- **N Counter Value**

- $N = f_{VCO}/f_N = f_{VCO}/f_{PD}$


- **Because the input to this counter can be high frequency, prescalers are typically inside this counter**

Dual Modulus Prescalers

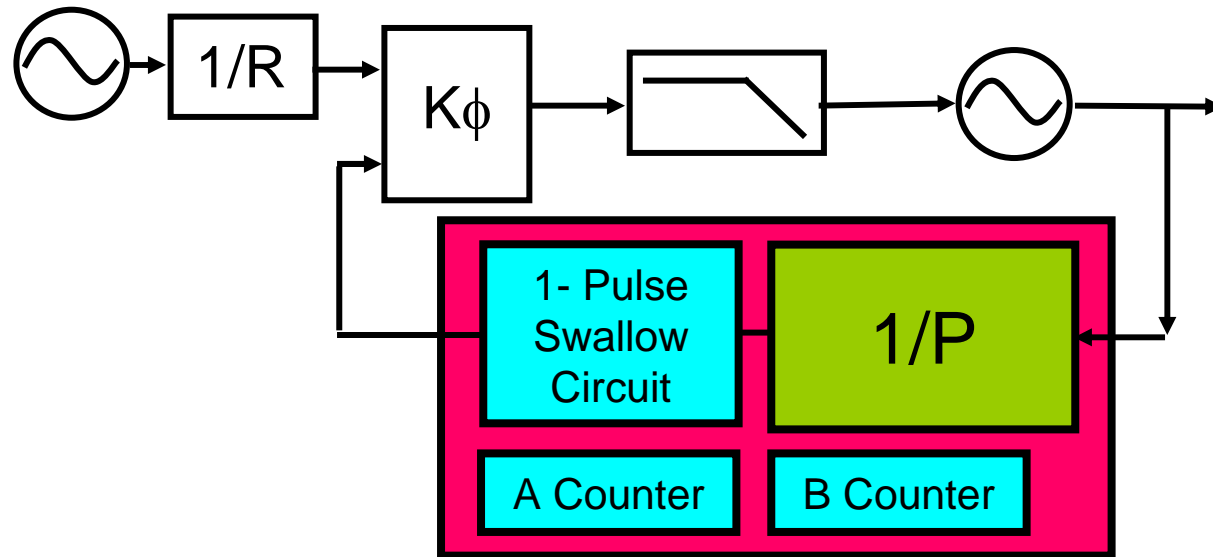


- **VCO Frequency is divided by prescaler**
 - Only the Prescaler has high frequency requirements
- **After the prescaler and the 1-pulse swallow circuit, each cycle decreases the A counter by 1 cycle**
 - This takes a $\bullet(P+1)$ cycles
 - B Counter is also decreased with the A counter

Dual Modulus Prescalers

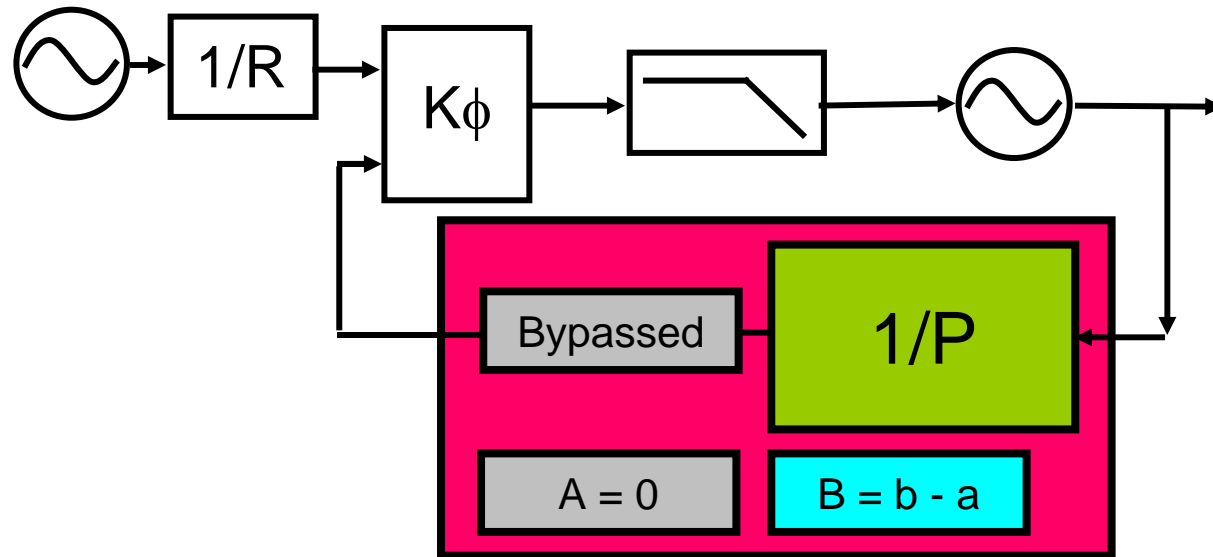

- **After the A counter reaches zero ..**
 - Pulse Swallow circuitry is disabled
 - B counter counts down to zero
 - This takes $(b-a)IP$ cycles
- **Total N Count**
 - $N = a \cdot (P+1) + (b-a) \cdot P = P \cdot B + A$
 - $b \geq a$ is a consequence of this architecture

Quadruple Modulus Prescaler

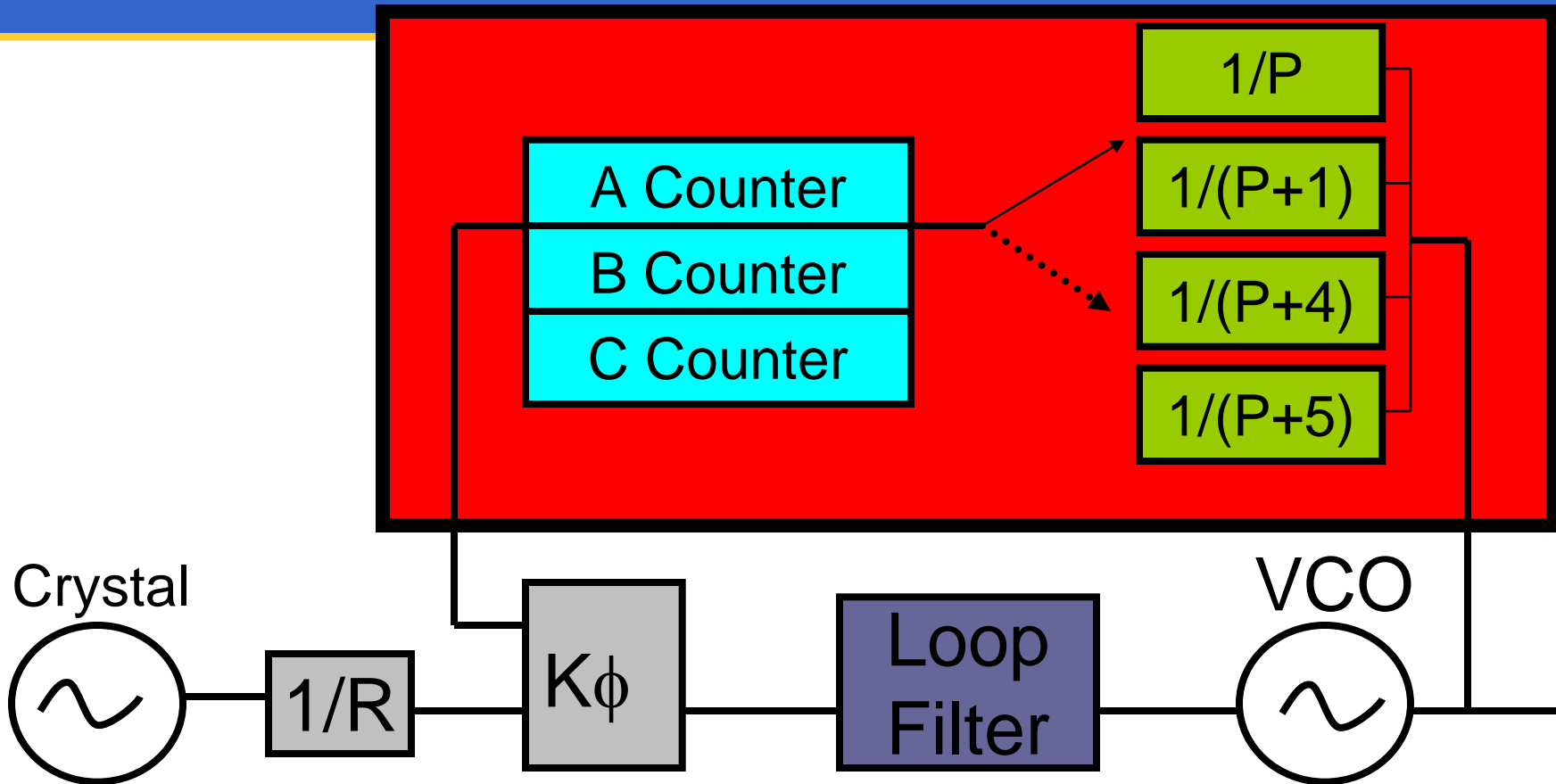


■ Advantage Allows lower divide ratios.

■
$$N = P \cdot C + 4 \cdot B + A$$

Overview


- Oscillators
 - Crystal Oscillators
 - High Frequency Oscillators
 - Voltage Controlled Oscillators (VCO)
 - Silicon Voltage Controlled Oscillators
 - Oscillator Phase Noise
- Other PLL Building Blocks
 - Counters
 - Phase Detector/Charge Pump
 - Loop Filter

Phase Frequency Detector/Charge Pump

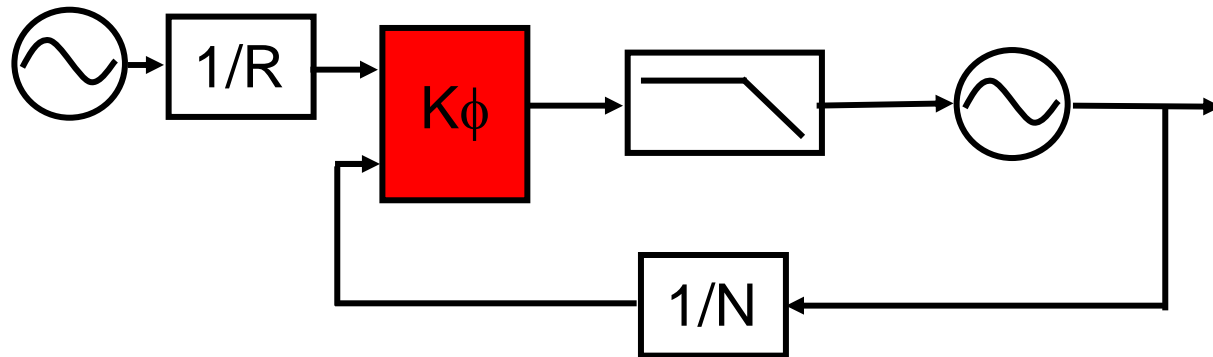


- **Phase Frequency Detector (PFD)**
 - Detects Frequency Error Between N and R Counter
- **Charge Pump**
 - Converts this frequency Error to a Correction Current
- **Usually, the PFD and Charge Pump are Integrated Together**

Phase Frequency Detector/Charge Pump

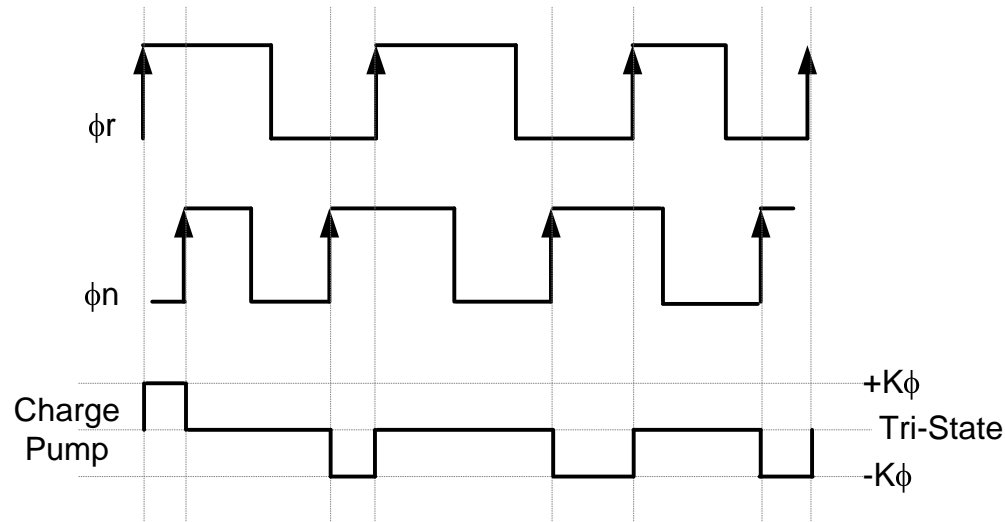


- **Detects differences in input signals**
 - Detects phase error between 2 input signals
 - Detects frequency error between 2 input signals
- **Outputs a voltage to the charge pump**
 - The average value of this voltage is proportional to the phase/frequency error.
 - Along with the rest of the system, ensures the 2 input signals are the same frequency and phase

Phase Frequency Detector/Charge Pump

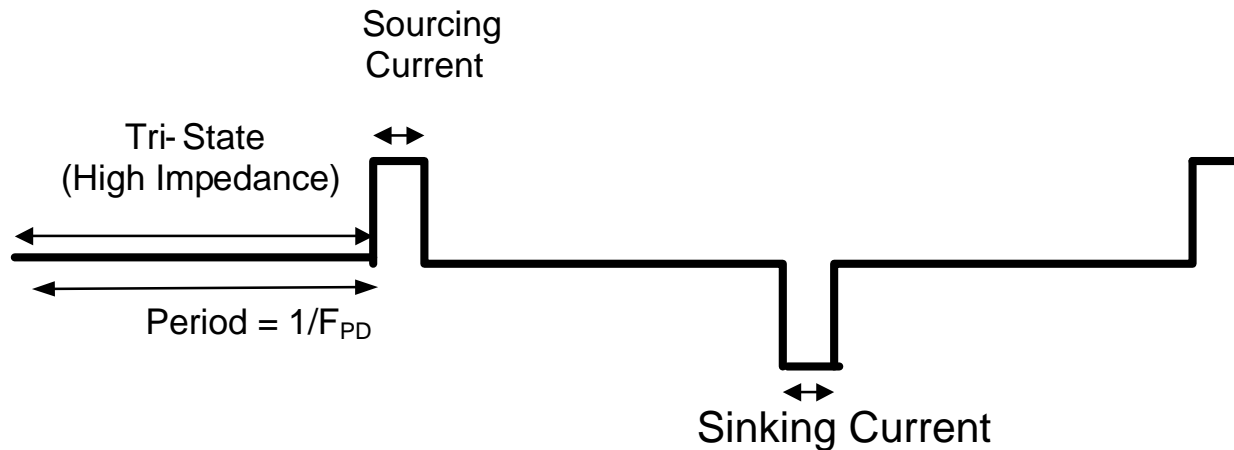


- **Charge Pump/Phase-Frequency Detector**
 - Sources Current if output frequency/phase is too low
 - Sinks Current if output frequency/phase is too high
 - High Impedance (tri-state) if output frequency/phase is correct (within tolerances)
- **Spurs Can Originate from the Charge Pump**
 - Want source and sink currents closely equal
 - Want tri-state to be very low leakage current

Charge Pump Current

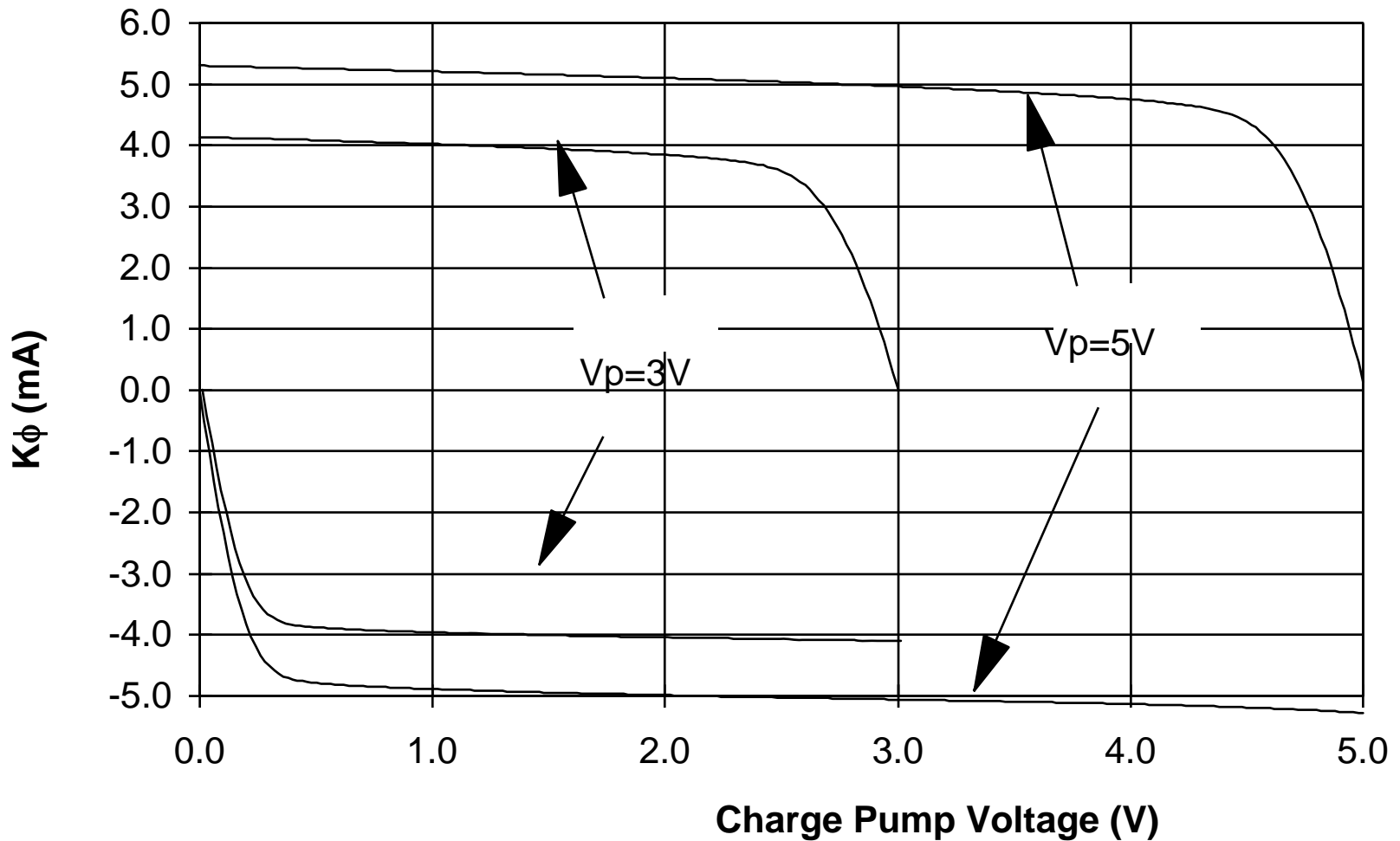

Loop Filter

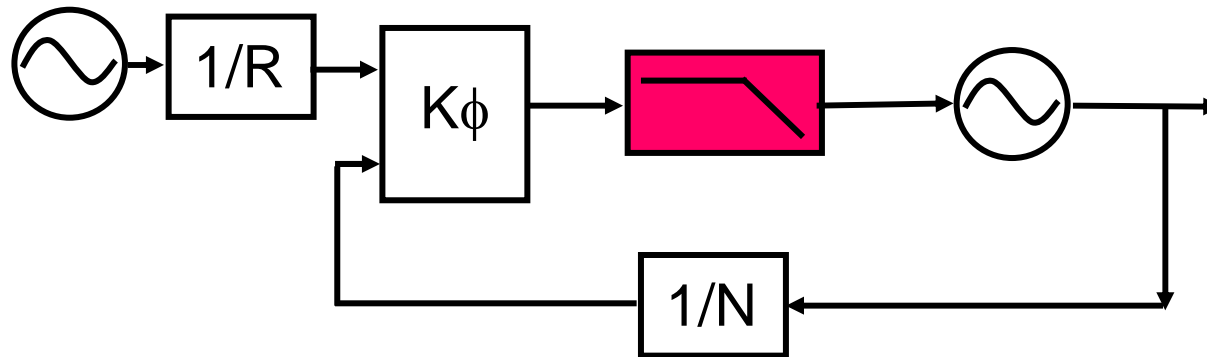

- **The loop filter is a low pass filter**
 - Accumulates correction currents from the Charge pump into a voltage
- **The loop filter has a dramatic effect on performance**
 - Determines the loop bandwidth
 - Impacts switching speed
 - Impacts spurs
 - Can impact phase noise
 - Many Design trade-offs involved
 - National has tools for this

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated