

TI Designs – Precision: Verified Design

Digitally Tunable MDAC-Based State Variable Filter

Reference Design



TI Designs – Precision

TI Designs – Precision are analog solutions created by TI's analog experts. Verified Designs offer the theory, component selection, simulation, complete PCB schematic & layout, bill of materials, and measured performance of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed.

Circuit Description

This MDAC based state variable filter offers highly accurate digital tuning of gain, center/cut off frequency, and quality factor. This circuit provides three separate filter outputs: low pass, band pass, and high pass that can be accessed simultaneously.



Design Resources

[Design Archive](#)
[TINA-TI™](#)
[DAC8812](#)
[OPA277](#)

All Design files
 SPICE Simulator
 Product Folder
 Product Folder



 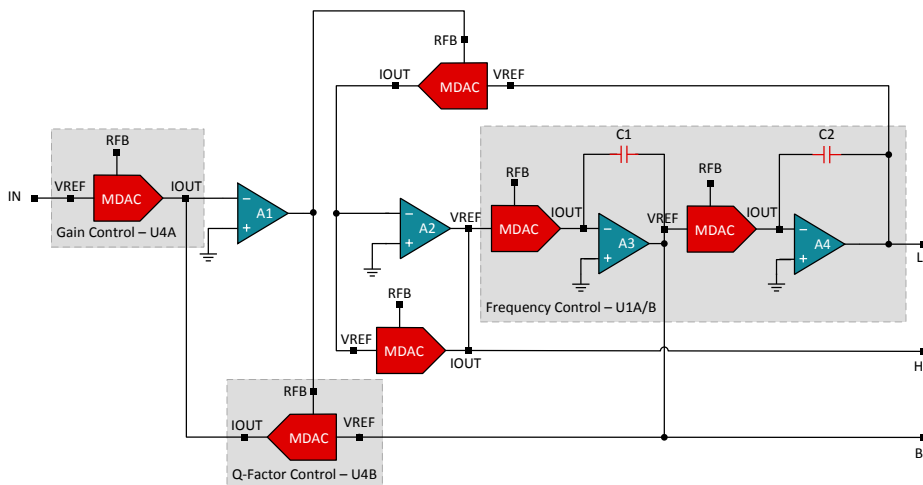[Ask The Analog Experts](#)
[WEBENCH® Design Center](#)
[TI Designs – Precision Library](#)



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

TINA-TI is a trademark of Texas Instruments
 WEBENCH is a registered trademark of Texas Instruments

1 Design Summary

The design requirements are as follows:

- Supply Voltage: 5 V
- AC Input: 1 V_{PP}
- Output: Low pass, Band pass, High pass
- Tunability: Gain, Center/Cut off Frequency, and Quality Factor

The design goals and performance are summarized in Table 1. Figure 1 depicts the measured transfer function of the design.

Table 1. Comparison of Design Goals, Simulation, and Measured Performance

	Goal	Simulated	Measured
Cut Off Frequency Range (3dB)	10 Hz to 30kHz	2.11 Hz to 27.98 kHz	1.99 Hz to 28.76 kHz
	DAC Code Range: 0x0004 to 0xFFFF		
Gain Range	0 dB to 6dB	-54.13 dB to 6.02 dB	-53.31 dB to 6.01 dB
	DAC Code Range: 0x0040 to 0xFFFF		
Quality Factor Range	0 dB to 6dB	0.47 to 2.15	0.46 to 2.14
	DAC Code Range: 0xFFFF to 0x4000		

 


Figure 1: Measured Transfer Function

2 Theory of Operation

An implementation of a state variable filter using discrete resistors is shown in Figure 2

 


Figure 2: State Variable Filter

In Figure 2, amplifier A1 and A2 form summing and inverting stages followed by two op amp integrators, A3 and A4 which act as single pole low pass filters. Amplifiers A3 and A4 are cascaded to form a second-order filter. This configuration provides 3 filter outputs: low pass (LP), band pass (BP) and high pass (HP). The center frequency (in the case of the band pass) or cut off frequency (in the case of the high pass and low pass) is set by the RC circuits on both integrators. For simplicity, this RC combination is typically made equal i.e. $R_3 = R_4$ and $C_1 = C_2$.

In order to analyze this circuit, nodal equations for each node in the circuit must be solved. The resulting transfer function is shown in Equations 1, 2 & 3.

$$\frac{LP}{IN} = \frac{\frac{R_5 \cdot R_8}{C_1 \cdot C_2 \cdot R_1 \cdot R_3 \cdot R_4 \cdot R_6}}{s^2 + \frac{R_5 \cdot R_8}{C_1 \cdot R_2 \cdot R_3 \cdot R_6} \cdot s + \frac{R_8}{C_1 \cdot C_2 \cdot R_3 \cdot R_4 \cdot R_7}} \quad (1)$$

$$\frac{BP}{IN} = \frac{-\frac{R_5 \cdot R_8}{C_1 \cdot R_1 \cdot R_3 \cdot R_6} \cdot s}{s^2 + \frac{R_5 \cdot R_8}{C_1 \cdot R_2 \cdot R_3 \cdot R_6} \cdot s + \frac{R_8}{C_1 \cdot C_2 \cdot R_3 \cdot R_4 \cdot R_7}} \quad (2)$$

$$\frac{HP}{IN} = \frac{\frac{R_5 \cdot R_8}{C_1 \cdot R_1 \cdot R_3 \cdot R_6} \cdot s^2}{s^2 + \frac{R_5 \cdot R_8}{C_1 \cdot R_2 \cdot R_3 \cdot R_6} \cdot s + \frac{R_8}{C_1 \cdot C_2 \cdot R_3 \cdot R_4 \cdot R_7}} \quad (3)$$

$$C_1 = C_2, \quad R_3 = R_4, \quad R_7 = R_8 \quad (4)$$

Equations 1, 2 & 3 are simplified by making the assumptions in Equation 4. Comparing the resulting equations with the standard equation for a band pass filter (Equation 5), yields expressions for gain (A_0), center/cut off frequency (ω), and quality factor (Q) (Equations 6, 7 & 8).

$$\frac{BP}{IN} = \frac{-\frac{A_0 \cdot \omega}{Q} \cdot s}{s^2 + \frac{\omega}{Q} \cdot s + \omega^2} \quad (5)$$

$$A_0 = \frac{-R_2}{R_1} \quad (6)$$

$$\omega = \frac{1}{C_1 \cdot R_3} \quad (7)$$

$$Q = \frac{R_2 \cdot R_6}{R_5 \cdot R_8} \quad (8)$$

3 Component Selection

3.1 DAC Selection

To realize eight discrete resistors a minimum of six MDACs ladders must be used. By using three dual channel MDACs with only six MDAC ladders, resistors R5 and R7 are realized by using the fixed values of two MDAC feedback resistors.

The DAC8812 is a great option for this design. It is a dual channel MDAC with strong linearity and large multiplying bandwidth which makes it ideal for this application.

Generally, MDACs are used in high performance applications that take full advantage of their strong dc specifications. MDACs have a current output and are used in conjunction with an external I-V operational amplifier. However, this design leverages the unique software-controlled output impedance property of MDACs. An important property of MDACs for this application is their reference multiplying bandwidth. The reference multiplying bandwidth changes with the programmed DAC code and the bandwidth is decreased at lower codes when the reference input is highly attenuated as shown in Figure 3. Plots such as these can be found in the datasheet of any MDAC.

 


Figure 3: DAC8812 Reference multiplying bandwidth

 


Figure 4: MDAC equivalent circuit

The resistors in Figure 2 are replaced by MDACs. The circuit equivalents of an MDAC are shown in Figure 4. Resistor R5 and R7 are realized using feedback resistors integrated in the multiplying DACs. The values of these resistors are fixed and cannot be changed by writing to the MDAC. The remaining resistors are realized by the programmable ladder impedance of the MDAC. Table 2 shows the maximum and minimum values for the tunable resistors. Note that resistors R3/R4 and resistors R7/R8 are implemented such that their values are tuned simultaneously (refer to Equation 4). To realize all the resistors in this filter a minimum of six MDACs are required. Therefore three DAC8812, a 16-Bit, dual channel serial input multiplying DAC, are used in this design. The tunable resistor range for the DAC8812 is shown in Table 2. Keep in mind that the resistor ladders in the DAC8812 can vary by ± 20 percent.

Table 2. Measured resistor values tunable range with MDAC DAC8812

Resistors	MDAC	Minimum Value (0xFFFF Code)	Maximum Value (0x0001 Code)
R1	U4 A	5.02 k Ω	33.00 k Ω
R2	U4 B	5.02 k Ω	25.57 k Ω
R3	U2 A	5.00 k Ω	26.91 k Ω
R4	U2 B	5.00 k Ω	22.86 k Ω
R5	U4 B RFB	5.18 k Ω	5.18 k Ω
R6	U1 B RFB	4.96 k Ω	4.96 k Ω
R7	U1 B	4.81 k Ω	22.55 k Ω
R8	U1 A	4.81 k Ω	22.48 k Ω

3.2 Amplifier Selection

This design requires four operational amplifiers. For all of these amplifiers, low input bias current is desired so that the critical parameters of the filter have exclusive tunability via the MDAC based resistors and their matching. The center/cut off frequency range for this design ranges from dc to 30 kHz, therefore high speed/high unity gain bandwidth amplifiers are not required.

The OPA277 was selected for this design because it features a sufficiently low input bias current of 1 nA.

3.3 Passive Component Selection

The high side cut off frequency is determined by the combination of capacitors C1 & C2 and the multiplying bandwidth of the MDAC with the lowest input code. The size of C1 is determined by Equation 7. The desired frequency bandwidth of the filters is 30 kHz. The DAC8812 reference input impedance is 5 k Ω paired with a 1 nF standard value for C1 will result in 32 kHz. In order to comply with Equation 4, both C1 and C2 must be the same value for the equations to be valid.

4 Simulation

The proposed circuit was simulated in TINA-TI™ using SPICE models of both the DAC8822 and OPA277. The choice of using the DAC8822 as a simulation model was based on the core similarity with the DAC8812 and the current lack of availability of a DAC8812 model. The DAC8822 and DAC8812 are very similar devices with the minor functional difference that the DAC8822 has more feedback resistor options. The simulation suite consists of an ac simulation test bench that included center/cut off frequency, gain and quality factor for high pass, low pass and band pass outputs.

Figure 5 shows the realization of the resistors in this circuit using MDAC DAC8822.

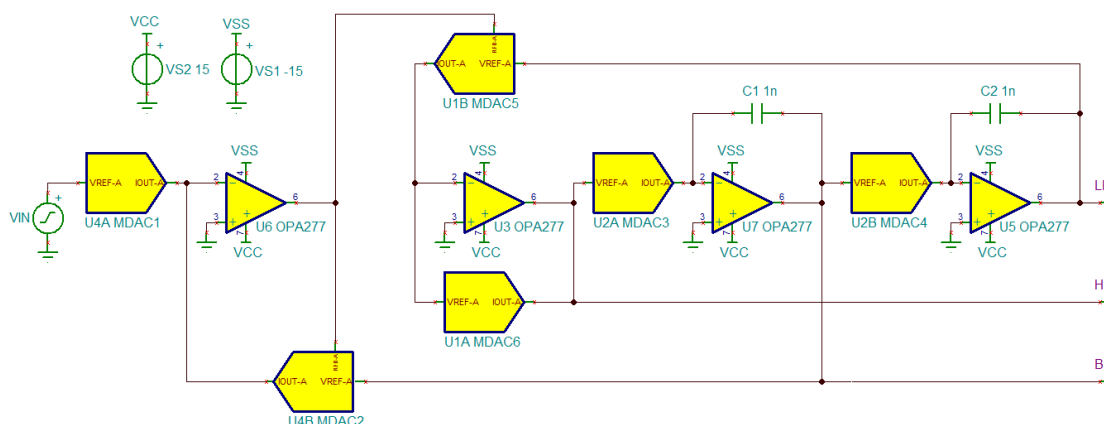


Figure 5: State Variable Filter using DAC8822

4.1 Center/Cut Off Frequency Simulation

The center/cut off frequency simulations were carried out for all the outputs (low pass, band pass and high pass). The MDAC ladders U2A/B can be tuned, thereby changing the frequency from 2.11 Hz (code 0x0004) to 27.98 kHz (code 0xFFFF). See Equation (7). Note that 0x0000 is not used in this design because at this code all the ladder switches are open and the ladder resistance is Hi-Z.

Figure 6 shows center frequency simulations for the high pass output. For frequency simulation data for band pass and low pass filters refer to Appendix B.

 


Figure 6: Cut off frequency simulation – High pass output

4.2 Gain Simulation

The gain simulations were carried out for all the outputs (low pass, band pass and high pass). The MDAC ladder U4A can be tuned, thereby changing the gain from -54.13 dB (code 0x0040) to 6.02 dB (code 0xFFFF). See Equation 6.

Figure 7 shows gain simulations for the low pass output. For gain simulation data for band pass and high pass filters refer to Appendix B.

 


Figure 7: Gain simulation – Low pass output

4.3 Quality Factor Simulation

The quality factor simulations were carried out for all the outputs (low pass, band pass and high pass). The MDAC ladder U4B can be tuned, thereby changing the quality factor from 0.47 (code 0xFFFF) to 2.15 (code 0x4000). See Equation (8).

Figure 8 shows gain simulations for the band pass output.

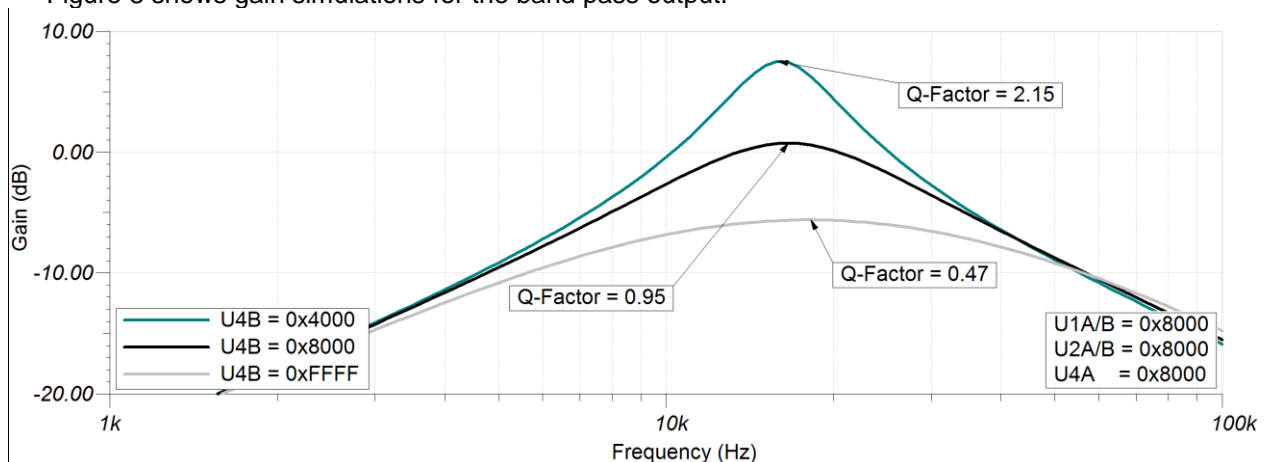


Figure 8: Quality Factor simulation – Band pass output

5 PCB Design

The PCB schematic and bill of materials can be found in the Appendix A.

5.1 PCB Layout

General PCB layout best-practices should be followed for this design. Analog and digital lines must not be traced out parallel to each other in order to reduce the coupling of digital signals onto analog signal paths.

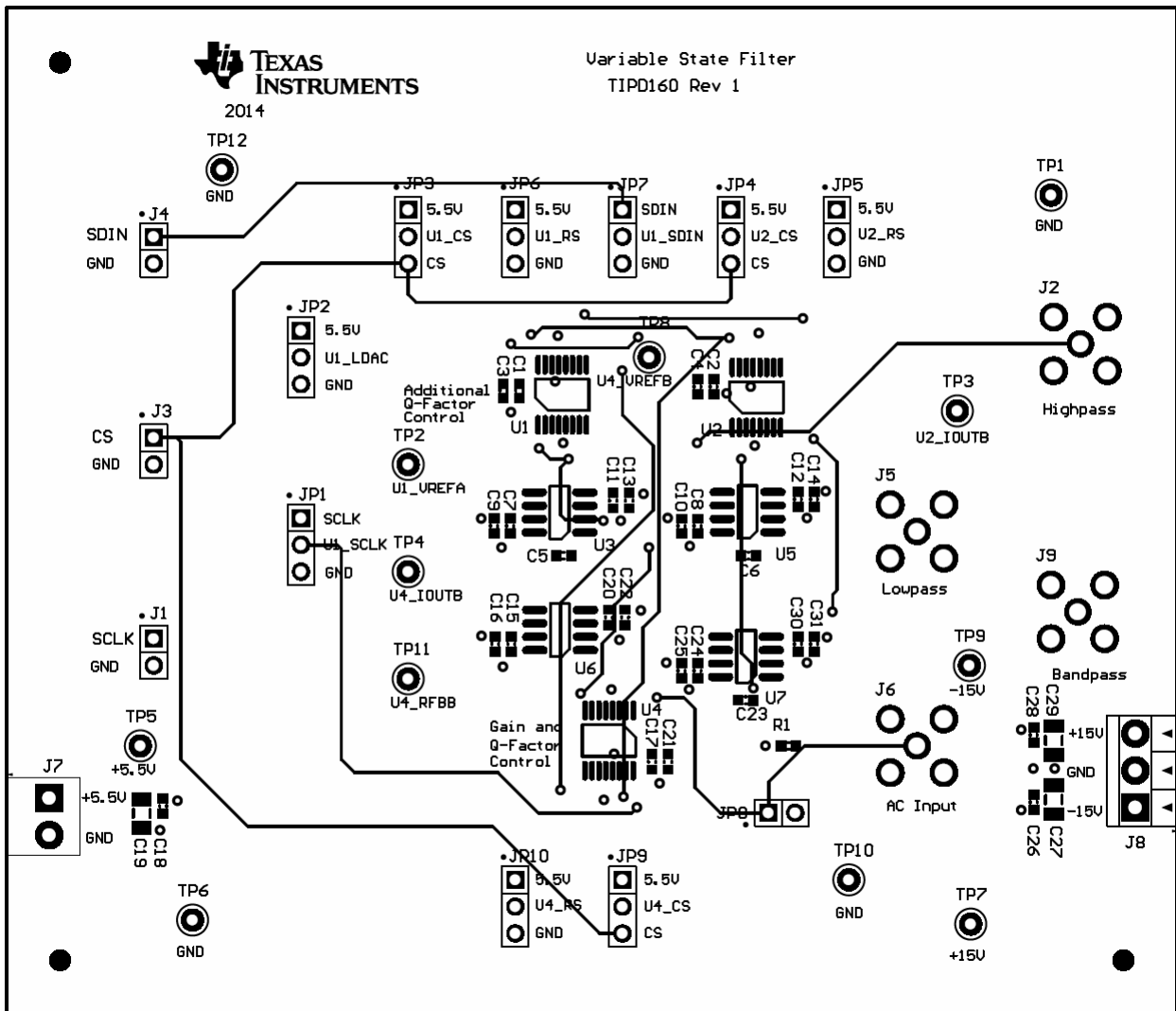


Figure 9: PCB Layout

6 Measurement

The circuit was tested using a bode plot analyzer that provided the input stimulus and measured the output response.

6.1 Center/Cut-off Frequency Measurement

The cut-off frequency setting is directly proportional to the DAC code of U2A/B. Each LSB change will adjust the frequency by approximately 0.5 Hz. For frequency measurement data for band pass and low pass filters refer to Appendix B.

 


Figure 10: Cut-off frequency measurement – High pass output

Table 3. High Pass Frequency Results @ 2 kHz

Code	Simulated Freq.	Measured Freq.	Error
0x0004	2.1100 Hz	1.9900 Hz	-5.69 %
0x8000	14690 Hz	14962 Hz	-1.85 %
0xFFFF	27980 Hz	28757 Hz	-2.78 %

6.2 Gain Measurement

The gain setting is directly proportional to the DAC code of U4A. Each LSB change will adjust the gain by approximately 1 mdB. Measurements at very low codes are susceptible to noise. For gain measurement data for band pass and high pass filters refer to Appendix B.

 


Figure 11: Gain measurement – Low pass output

Table 4. Low Pass Gain Results

Code	Simulated Gain	Measured Gain	Error
0x0040	-54.1276 dB	-53.3100 dB	-0.8176 dB
0x8000	0.0012 dB	0.0007 dB	0.0004 dB
0xFFFF	6.0200 dB	6.0140 dB	0.0060 dB

6.3 Quality Factor Measurement

The quality factor measurement is inversely proportional to the DAC code of U4B. Each LSB change will adjust the quality factor by approximately 52 μ . The quality factor can be controlled independently of gain by using another MDAC to control resistors R5 & R6. For information about how to calculate quality factor, please refer to Appendix B.

 


Figure 12: Quality factor measurement – Band pass output

Table 5. Band Pass Quality Factor Results

Code	Simulated Q-Factor	Measured Q-Factor	Error
0x4000	2.1524	2.1424	-0.46 %
0x8000	0.9461	1.0077	6.52 %
0xFFFF	0.4691	0.4660	-0.65 %

7 Modifications

Depending on the design requirement other multiplying DACs can be used in this design. DAC8812 was selected for its serial interface, high resolution, and superior multiplying bandwidth. Table 6 shows other MDAC options for application that may not require high resolution or that may require a parallel interface. Table 7 shows alternative amplifiers that can be used in this design for larger bandwidth or minimal input bias current.

Table 6. Alternative MDACs

MDAC	Resolution	Channel Count	Interface	Reference multiplying bandwidth
DAC8812	16 bits	2	Serial	10 MHz
DAC8822	16 bits	2	Parallel	10 MHz
DAC8802	14 bits	2	Serial	10 MHz
DAC8805	14 bits	2	Parallel	10 MHz
DAC7822	12 bits	2	Parallel	10 MHz

Table 7. Alternative operational amplifiers

Amplifier	Supply	Bandwidth	Input bias current (Typ.)
OPA277	±18 V	1 MHz	±500 nA
OPA211	±18 V	80 MHz	±50 nA
OPA188	±18 V	2 MHz	±160 pA
OPA170	±18 V	1.2 MHz	±8 pA

8 About the Author

Rahul Prakash is a design and systems engineer in the precision digital to analog converters group at Texas Instruments. Rahul received his B.Tech in Electrical and Electronics Engineering from the Netaji Subhas Institute of Technology, India, and MS in Electrical Engineering from University of Texas at Dallas.

Eugenio Mejia is an applications engineer in the precision digital to analog converters group at Texas Instruments. Eugenio received his Bachelors of Science in Electrical Engineering from Texas A&M University.

9 Acknowledgements & References

1. *Engineer It, What is a multiplying DAC (MDAC)?* ([Video](#))
2. *Build a three phase sine wave generator with the UAF421* ([SBFA013](#))
3. *Design a 60 Hz notch filter with the UAF42* ([SBFA012](#))
4. *TLC7528, Digitally-controlled state-variable filter application information* ([SLAS062E](#))
5. *TIPD137, $\pm 10V$ 4-Quadrant Multiplying DAC* ([TIDU031](#))

Appendix A.

A.1 Electrical Schematic

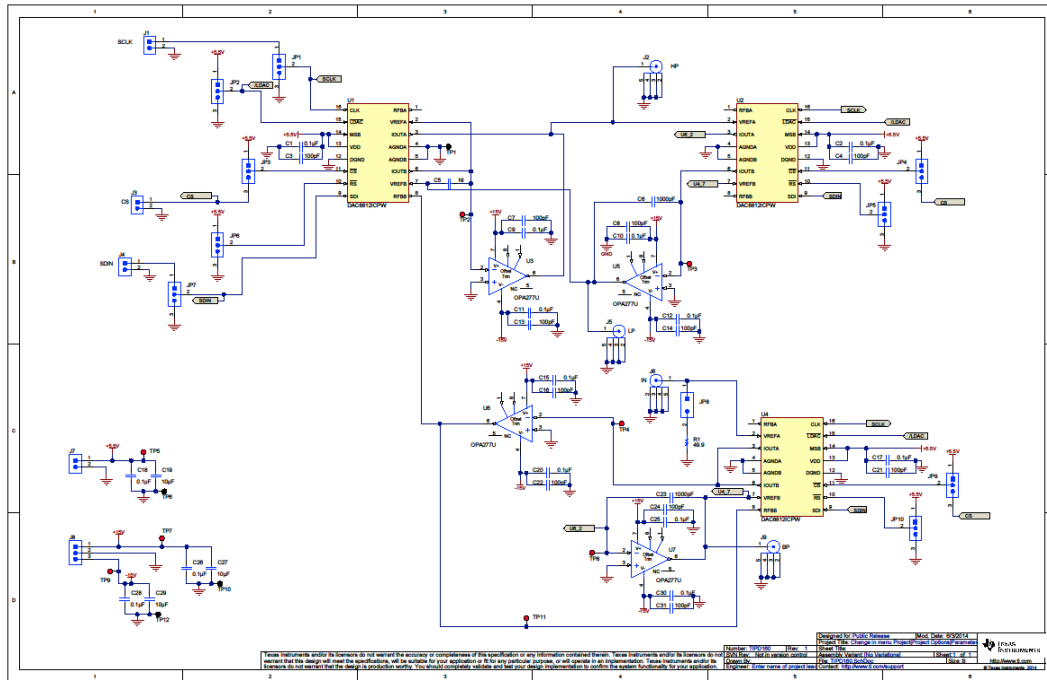


Figure A-1: Electrical Schematic

A.2 Bill of Materials

Item #	Quantity	Value	Designator	Description	Manufacturer	PartNumber
1	14	1uF	C1, C2, C9, C10, C11, C12, C15, C17, C18, C20, C25, C26, C28, C30	CAP, CERM, 0.1uF, 25V, +/-10%, X5R, 0603	MuRata	GRM188R61E104KA01D
2	11	100pF	C3, C4, C7, C8, C13, C14, C16, C21, C22, C24, C31	CAP, CERM, 100pF, 50V, +/-5%, C0G/NP0, 0603	TDK	C1608C0G1H101J
3	1		C5	Not Installed	MuRata	
4	2	1000pF	C6, C23	CAP, CERM, 1000pF, 50V, +/-10%, X7R, 0603	MuRata	GRM188R71H102KA01D
5	3	10uF	C19, C27, C29	CAP, CERM, 10uF, 25V, +/-10%, X5R, 1206	MuRata	GRM31CR61E106KA12L
6	4		J1, J3, J4, JP8	Header, 100mil, 2x1, Gold, TH	Samtec	TSW-102-07-G-S
7	4		J2, J5, J6, J9	Connector, TH, SMA	Emerson Network Power	142-0701-201
8	1		J7	Terminal Block, 6A, 3.5mm Pitch, 2-Pos, TH	On-Shore Technology	ED555/2DS
9	1		J8	Terminal Block, 6A, 3.5mm Pitch, 3-Pos, TH	On-Shore Technology	ED555/3DS
10	9		JP1, JP2, JP3, JP4, JP5, JP6, JP7, JP8, JP10	Header, TH, 100mil, 3x1, Gold plated, 230 mil above insulator	Samtec	TSW-103-07-G-S
11	1	49.9kΩ	RT1	RES, 49.9 ohm, 1%, 0.1W, 0603	Yageo America	RC0803FR-0749R9L
12	4		TP1, TP6, TP10, TP12	Test Point, Miniature, Black, TH	Keystone	5001
13	8		TP2, TP3, TP4, TP5, TP7, TP8, TP9, TP11	Test Point, Miniature, Red, TH	Keystone	5000
14	3		U1, U2, U4	Dual, Serial Input 16-Bit Multiplying Digital-to-Analog Converter, PW0016A	Texas Instruments	DAC8812CPW
15	4		U3, U5, U6, U7	High Precision OPERATIONAL AMPLIFIER, D0008A	Texas Instruments	OPA277U

Figure A-2: Bill of Materials

Appendix B.

B.1 Center/Cut Off Frequency Simulation & Measurements

 


Figure B-1: Cut-off frequency simulation – Low pass output

 


Figure B-2: Cut-off frequency measurement – Low pass output

Table 8. Low Pass Frequency Results

Code	Simulated Freq.	Measured Freq.	Error
0x0004	2.2138 Hz	1.9387 Hz	-12.45 %
0x8000	17.1738 kHz	16.8585 kHz	-1.84 %
0xFFFF	36.81 kHz	35.6480 kHz	-3.16 %

 


Figure B-3: Cut-off frequency simulation – Band pass output

 


Figure B-4: Cut-off frequency measurement – Band pass output

Table 9. Band Pass Frequency Results

Code	Simulated Freq.	Measured Freq.	Error
0x0004	2.2514 Hz	1.9387 Hz	-13.89 %
0x8000	17.7834 kHz	16.7400 kHz	-5.87 %
0xFFFF	35.4852 kHz	35.7890 kHz	0.86 %

B.2 Gain Simulation & Measurements

 


Figure B-5: Gain simulation – High pass output

 


Figure B-6: Gain measurement – High pass output

Table 10. High Pass Gain Results @ 50 kHz

Code	Simulated Gain	Measured Gain	Error
0x0004	-52.8254 dB	-45.7880 dB	-7.04 dB
0x8000	1.2612 dB	1.1631	0.10 dB
0xFFFF	7.3731 dB	7.3293	0.04 dB

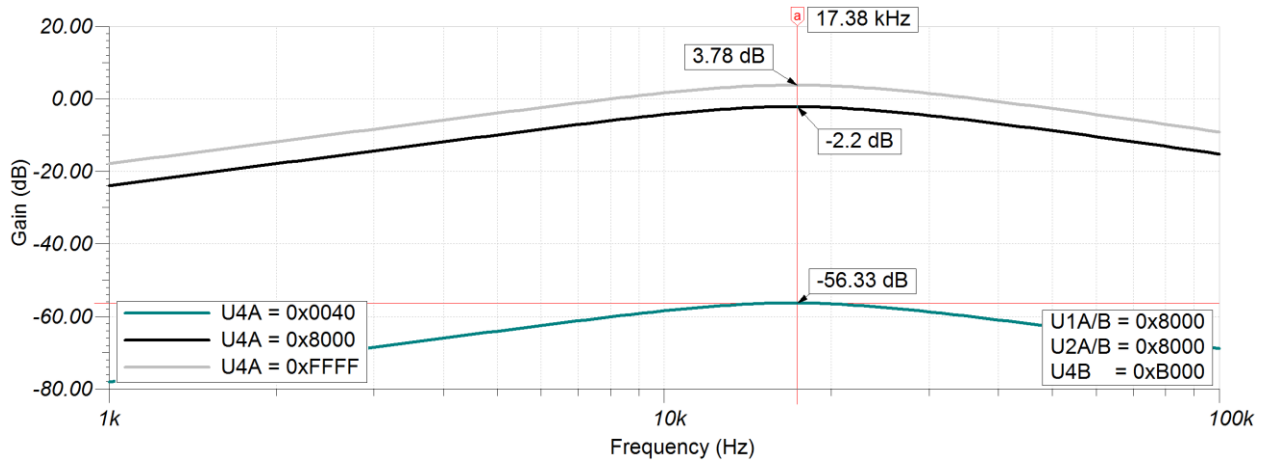


Figure B-7: Gain simulation– Band pass output

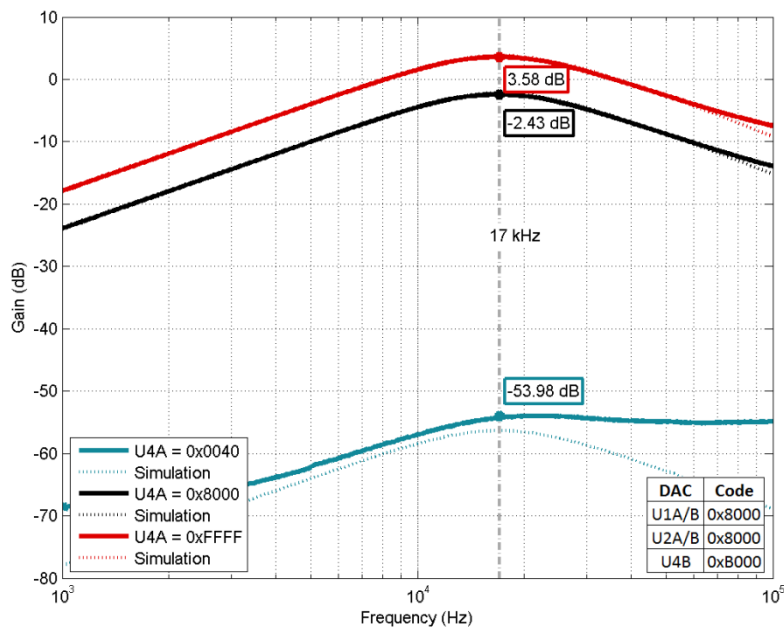


Figure B-8: Gain measurement – Band pass output

Table 11. Band Pass Gain Results

Code	Simulated Gain	Measured Gain	Error
0x0004	3.7835 dB	3.5845 dB	0.20 dB
0x8000	-2.2214 dB	-2.4316 dB	0.21 dB
0xFFFF	-56.3345 dB	-53.9780 dB	-2.36 dB

B.3 Quality Factor Simulation & Measurements

The quality factor is calculated using Equation (9), the center frequency (f_c) and the -3 dB bandwidth (Δf_{3dB}) of the bandpass filter.

$$Q = \frac{f_c}{\Delta f_{-3dB}} \quad (9)$$

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.