

TI Designs: TIDA-00976 高速、ハイサイド電流センスのリファレンス・デザイン




概要

TIDA-00976 TI Designは電流から電圧へ的高速変換回路です。このデザインは、5V~30Vの正の電源レールで高速な電流の測定を行う必要がある、電流センス・アプリケーションに最適化されています。このデザインは同相電圧を30Vから降圧し、2.5Vを中心とする出力電圧を生成して、アナログ/デジタル・コンバータ(ADC)によりサンプリングを行います。出力同相電圧は、さまざまな高精度基準電圧を使用して簡単に変更できます。

リソース

 - [THS4131](#) プロダクト・フォルダ
- [TINA-TI™](#) ツール・フォルダ





特長

- 帯域幅: 15MHz超
- 電流を電圧に変換
- ハイサイドの電圧範囲: 5~30V
- 柔軟な出力同相電圧

アプリケーション

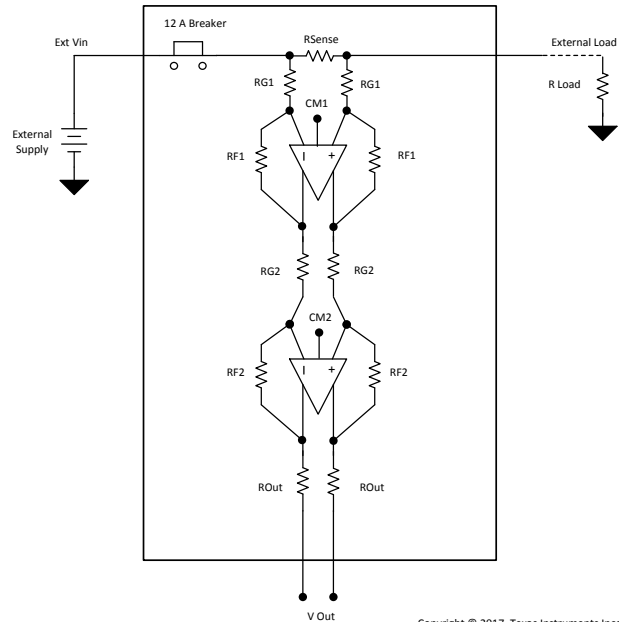 - 電力品質測定器
- 無線周波数(RF)パワー・アンプ(PA)制御およびエンベロープ・トラッキング
- モータ制御
- 力率補正および測定



Copyright © 2017, Texas Instruments Incorporated



使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE(重要な注意事項)をご参照くださいますようお願いいたします。英語版のTI製品についての情報を翻訳したこの資料は、製品の概要を確認する目的で便宜的に提供しているものです。該当する正式な英語版の最新情報は、www.ti.comで閲覧でき、その内容が常に優先されます。TIでは翻訳の正確性および妥当性につきましては一切保証いたしません。実際の設計などの前には、必ず最新版の英語版をご参照くださいますようお願いいたします。

1 System Description

The TIDA-00976 TI Design is a fixed-gain, high-bandwidth, and fully-differential, current-to-voltage conversion circuit designed for high-speed applications. With a supply voltage range of 5 to 30 V, this amplifier provides exceptional flexibility in high-side current-sense applications. With an input voltage of 30 V and typical ADC input voltage ranges of 5 V or less, the TIDA-00976 uses a two-stage configuration to reduce the input voltage range to a safe range for a typical ADC. The TIDA-00976 has been optimized for high-input voltage and large currents. The TIDA-00976 uses two THS4131 high-speed, fully-differential amplifiers (FDAs) to convert an input current to output voltage.

Design options for higher supply voltage and additional filtering are provided to cover additional applications.

1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Supply voltage	5- to 30-V external supply
Current-to-voltage gain	100 to 400 mV _{pp} / Amp
Differential-output common-mode voltage	2.5 V (adjustable)
Target bandwidth	> 15 MHz
Onboard active load	V _{in} = 5 to 30 V; Gain = 500 mV/A
Onboard circuit breaker	12 A

2 System Overview

2.1 Block Diagram

A block diagram of the system is shown in [Figure 1](#). The main portion of the design is two fully-differential amplifiers (FDAs). A circuit breaker and a precision reference are included on the reference design board. There is also a connector for an external load.


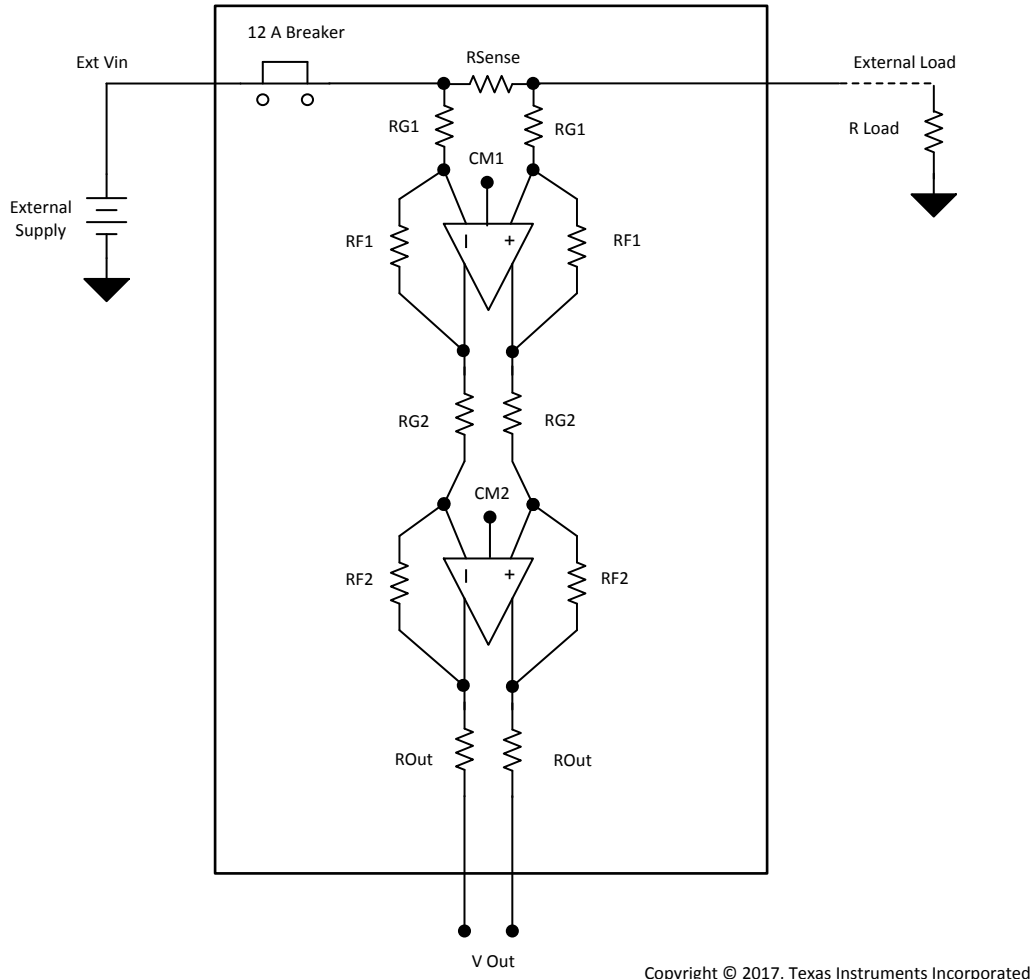


Figure 1. System Block Diagram

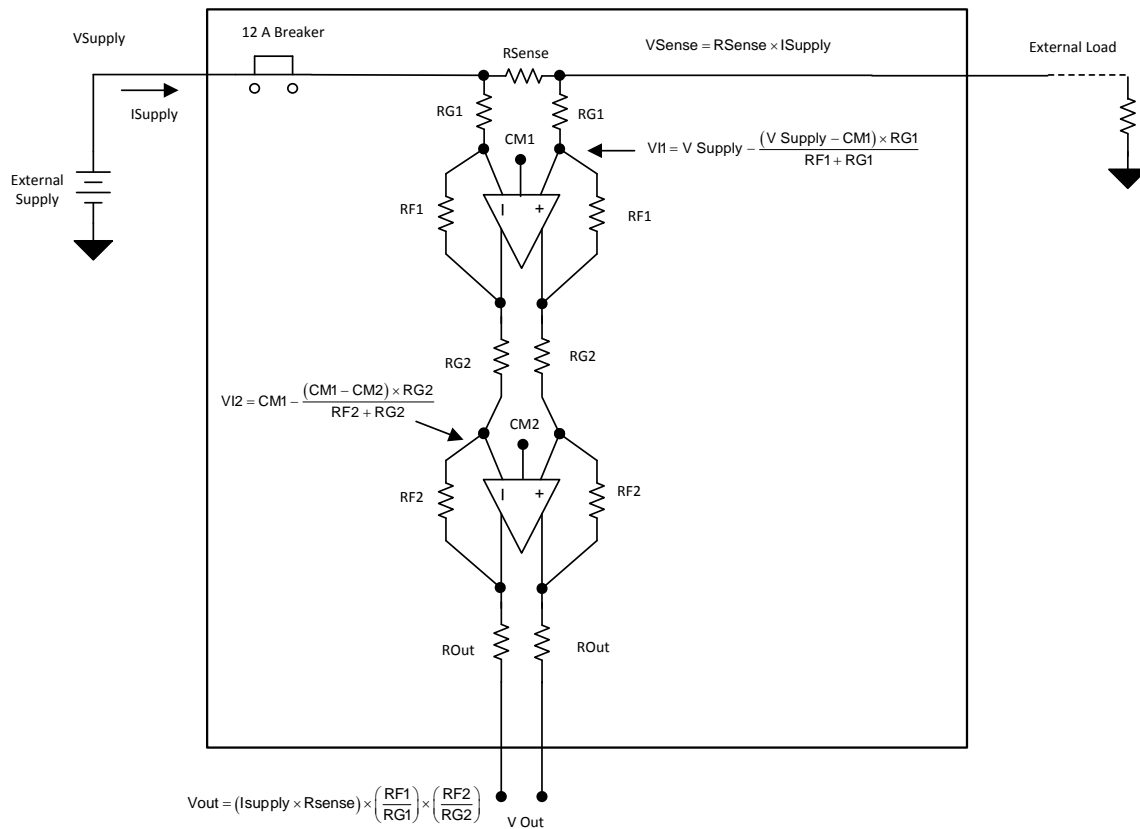2.2 Design Considerations

Voltage calculations at key points in the signal path are annotated in [Figure 2](#).



Copyright © 2017, Texas Instruments Incorporated

Figure 2. Detail of Common-Mode Voltages and Design Equations

2.3 **Highlighted Products**

2.3.1 **THS4131**

This TI Design features the [THS4131](#) FDA. The THS4131 provides an excellent combination of wide supply range, high speed, and low noise, which makes it ideally suited for high-side, current-sense applications. The THS4131 has externally set gain with four resistors.

In addition to a wide supply-voltage range, the THS4131 also has a very wide input common-mode range. The input common-mode voltage can range from $(V_{-} + 1.0 \text{ V})$ to $(V_{+} - 0.5 \text{ V})$. This wide input common-mode range allows flexibility for current sensing from the positive supply rail.

The common-mode rejection ratio (CMRR) provided by the fully-differential signal chain reduces any feed-through from the power supply regulator voltage fluctuations, which increases the power-supply rejection ratio (PSRR) of the current-sense circuit.

2.3.2 **REF5025AID**

The [REF5025](#) is a 2.5-V, low-noise, precision voltage reference. This reference is used to set the output common-mode voltage. The REF50xx series offers several voltage options if required for different ADC common modes.

2.4 **System Design Theory**

The design of TIDA-00976 is a high-side, current-sensing circuit. In a high-side, current-sense system the sense resistor is between the power supply and the circuit. The primary advantage of a high-side, current-sense circuit is that the ground path is undisturbed. Many systems use ground connections to suppress noise and power-supply voltage transients, so the high-side, current-sense option is desirable. The primary drawback of high-side, current-sense circuits is that the supply voltage is now the common-mode voltage of the sense voltage generated on the sense resistor. This reference design uses a THS4131 FDA with an input common mode that can support supply voltages up to 30 V.

An FDA with wide bandwidth is the core of the signal path as shown in [Figure 2](#). In order to support the full supply range of 30 V while also driving a low-voltage ADC, there is a second FDA on the reference design board. If the external VSupply voltage is less than 7 V, the second amplifier may not be necessary. A detail of the common-mode voltages is shown in [Figure 2](#).

In addition to a wide supply-voltage range, the TIDA -00976 also offers a very high frequency response. Without filtering, the core design supports bandwidths up to 15 MHz. This frequency response can be tailored for the specific application with additional components.


2.4.1 Design Options

There are several options built into the TIDA-00976 reference design. These options are shown in [Figure 3](#), which help extend the voltage range and ensure stability of the final circuit.

The first option is the addition of pull-down resistors, which are labeled RB1. These resistors will reduce the amplifier input common-mode pin voltages and allow for an input voltage higher than 30 V to be applied to the external supply port.

To protect the amplifier inputs from voltage transients in a high-noise environment, placeholders for Zener diodes are provided as shown in [Figure 3](#). The reverse-bias rating on the diodes should be rated for at least the maximum supply voltage or 30 V. The addition of the reverse-biased Zener diode might present significant input capacitance that causes frequency-response peaking or instability. As a result, the capacitors CC1 can be used to reduce peaking of the frequency response. A good starting value for this component is 1 pF to 5 pF. A detailed description of stabilizing an amplifier by the addition of an input capacitance can be found in the *Op amp stability and input capacitance* [\[2\]](#).

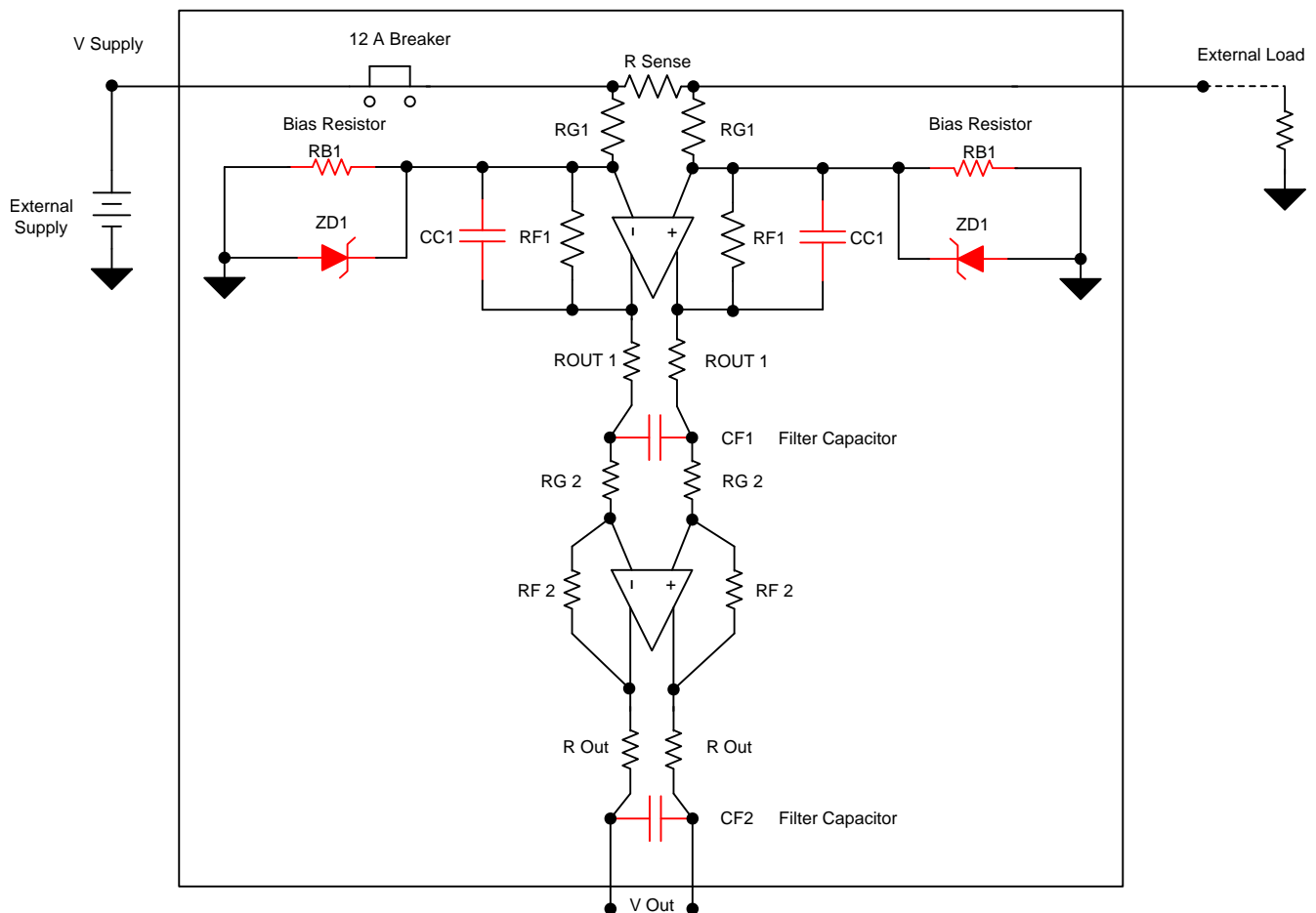In order to reduce sampled noise when using an ADC to measure the system output, the system bandwidth should not be significantly larger than the signal bandwidth. The TIDA-00976 has over 15 MHz of bandwidth. If the sampled signal has lower bandwidth, capacitors CF1 and CF2 can be used to reduce broadband noise.



Copyright © 2017, Texas Instruments Incorporated

Figure 3. Design Options Shown in Red

3 Hardware, Software, Testing Requirements, and Test Results


3.1 Hardware



CAUTION

Caution hot surface. The PCB surface can get very hot while passing high currents. Contact may cause burns. Do not touch

 The performance of the TIDA-00976 was evaluated by simulation in TINA-TI as well as in the lab using an external load. [Fig 4](#) shows the hardware setup diagram for evaluating the reference design for converting a high-side input current to an output voltage.



Copyright © 2017, Texas Instruments Incorporated

図 4. Hardware Setup Diagram

3.1.1 Applying Power and Basic Setup

The TIDA-00976 has a supply voltage range of 5 to 30 V. The following steps detail the TIDA-00976 setup procedure for high-side input current to output voltage testing, as shown in [Figure 4](#).

3.1.1.1 Board Power Supply Setup

The TIDA-00976 reference design supports a supply voltage range of 5 to 30 V.

1. With the supplies disconnected, set the voltage on the DC power supply (capable of sourcing 1-A current) between 5 to 30V. Also, set the current compliance limit to approximately 100 mA on the DC power supply.
2. Keeping the supplies turned OFF, connect the DC power supply to the EXT amp power connection (TP2) and GND (TP1) as shown in [Figure 4](#). Reference the [Figure 7](#) for test-point (TP) and jumper connections. Make sure the shorting block on jumper J8 is connected across pins 1 and 2.
3. Turn on the DC power supply connected to the external amp power connector. The supply current recorded on the power supply should be around 27 mA.

3.1.1.2 Connecting the Digital Multimeter to Measure the Output Voltage

1. Connect the digital multimeter voltage port to OUT+ (J6) and COM port to OUT- (J5), as shown in [Figure 4](#).
2. Set the dial on the multimeter to DC voltage measurement mode. The multimeter measures the voltage difference across the outputs OUT+ and OUT-.

3.1.1.3 Connecting the External High-Current Load and High-Current Testing

1. Connect a high-current, 1- Ω load resistor bank across the connectors J1 (GND) and J2 (LOAD). Ensure that the connector cable is rated for 15 A (14 gauge or larger). The voltage measurement across the 1- Ω load resistor bank is equivalent to the load current being measured.
2. Connect another digital multimeter voltage port across the 1- Ω load resistor bank to measure the voltage across it, as shown in [Figure 4](#).
3. With the supplies turned OFF, connect a high-current bench supply capable of sourcing 15-A current across connectors J4 (external Vin) and J3 (GND). Ensure that the connecting cable is rated for at least 15 A.
4. Turn on the DC power supply connected to the external Vin responsible for providing the input load current. [Figure 5](#) gives the relationship between the input load current and the output voltage measured across the outputs OUT+ and OUT-.


3.1.2 Output Common-Mode Voltage Option


In order to support direct interfacing with an ADC, the TIDA-00976 reference design uses a precision reference (REF5025AID) to set the common-mode voltage of U2. This precision reference allows direct DC coupling with ADCs that require a 2.5-V input common-mode voltage. Options ranging from 2 to 10 V are available in the REF50xx family of precision voltage references.

In the event that another common-mode voltage is desired, move the shorting block on jumper J7 across pins 1 and 2. Connect the Vref+ test point to a bench supply and set the voltage to the desired common-mode voltage. The valid common-mode voltages range from 1 V to (Vs+ - 1 V) for the THS4131.

3.2 Testing and Results


3.2.1 High-Side Current Testing

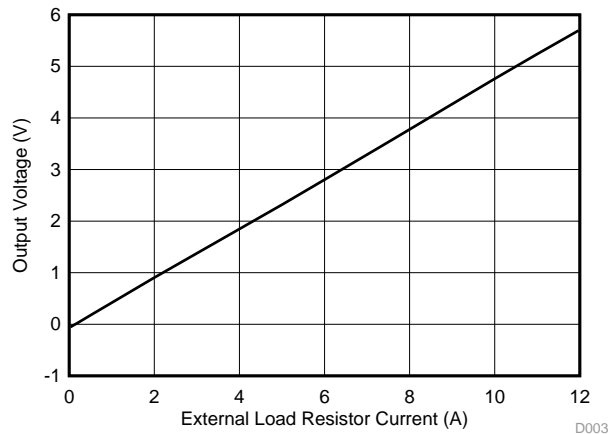
3.1.1 details the setup procedure for high-side current testing.  5 shows the linear relationship between the measured input load current and the output voltage across OUT+ and OUT- or $V_{OUT} = (OUT+) - (OUT-)$.




 5. Output Voltage Versus Load Current

3.2.2 Frequency Response Testing

In order to measure the frequency response without having to source and sink a large current, a differential signal input can be inserted at jumper J9. Replace resistor R1 with a 100-Ω resistor and connect a differential voltage source across J9. The frequency response of the reference design can now be measured with standard 100-Ω differential test equipment.  6 shows the frequency responses of the two-stage current-sense circuit.

 The filtered frequency response in the below graph includes the diode protection circuit at the input (ZD1) along with CC1 of 5pF (see  3). The protection diode used in the circuit is the SMAZ30-13-F with approximately 60 pF of reverse bias capacitance. Also, the CF1 and CF2 are set to 10 pF and 30 pF, respectively. The unfiltered frequency response test is performed by removing all the above mentioned components used for the filtered frequency response.

 

 6. Measured Frequency Response

3.2.3 Common-Mode Voltage Versus Error Current

Due to the high voltages involved, it is important to calculate the power dissipated in the first stage feedback and gain-set resistors. Power dissipation for typical configurations is shown in 表 2. It is important to note that for a given voltage the resistor power will increase as the resistor value decreases. For this reason, there is a trade-off between selecting low resistor values to reduce noise compared with increased power dissipation. When using surface mount resistors, some typical resistor power ratings are shown in 表 3.

表 2. Common-Mode Voltage Versus Error Current

SUPPLY VOLTAGE (V)	ADC INPUT COMMON MODE (V)	CM1 (V)	CM2 (V)	RG1 (Ω)	iRG1 (mA)	pRG1 (mW) / pRF1 (mW)
5	2.5	2.5	2.5	5k	0.17	0.14 / 0.29
7	2.5	3.5	2.5	5k	0.3	0.45 / 0.9
10	2.5	5	2.5	5k	0.33	0.54 / 1.1
15	2.5	7.5	2.5	5k	0.5	1.25 / 2.5
20	2.5	10	2.5	5k	0.67	2.24 / 4.49
30	2.5	15	2.5	5k	1	5 / 10

表 3. Surface Mount Resistor Power Ratings ⁽¹⁾

PACKAGE SIZE	POWER RATING (mW)
0603	125
0402	63
0201	50

⁽¹⁾ Vishay®

3.2.4 Signal Gain Calculation

The current-to-voltage signal gain calculation as well as the common-mode voltage at various nodes in the circuit are shown in 図 2. The individual stage gain is mainly set by the ratio of feedback resistor (RF) and gain-setting resistor (RG). In actual application, the second FDA output interfaces to a low-voltage ADC. As a result, the maximum input voltage swing of the ADC usually sets the maximum signal current that is measured for a given sense resistor and overall gain configuration. 表 4 shows the maximum signal current that can be measured for 3 V_{PP} maximum input at the ADC for the different sense resistor and gain configurations.

表 4. Signal Gain (V/A)

SENSE RESISTOR (Ω)	STAGE 1 GAIN (V/V)	STAGE 2 GAIN (V/V)	OVERALL GAIN (mV/A)	SUPPLY DROOP (mV/A)	MAX. CURRENT (A) at 3 V _{PP}
0.100	2	2	400	100	7.5
0.050	2	5	500	50	6
0.010	2	5	100	10	30
0.010	4	4	160	10	19

3.2.5 Noise and Offset Errors

The primary offset error and noise terms are shown in 表 5 and 表 6, respectively. While the offset voltage and offset currents are the largest terms, they are also systematic and can be calibrated out from the final measurements. It is the noise terms that cannot be calibrated out due to the randomness associated with the noise. For high-side current-sense applications, the input gain-setting resistor (R_G) must be high in order to minimize error currents while applying high-input voltages as discussed in 3.2.3. As a result, the large gain (R_G) and feedback resistors (R_F) have noise that is significantly more than the amplifier noise. An R_G of 5 k Ω has a thermal noise of 9 nV/ $\sqrt{\text{Hz}}$, while the amplifier input-noise voltage is 1.3 nV/ $\sqrt{\text{Hz}}$. A detailed description of calculating noise in a fully-differential amplifier can be found in the *Analysis of fully differential amplifiers*[3].

表 5. Input Referred Offset Error Terms

PARAMETER	V_{os}	I_{os}
Value	0.2 mV	100 nA
Error magnitude with $R_G = 5\text{k}\Omega$, $A_V = 2\text{ V/V}$ BW = 20MHz	0.4 mV	0.33 mV


表 6. Input Referred Noise Error Terms


PARAMETER	V_N	I_N	RG_Noise ⁽¹⁾
Value	1.3 nV/ $\sqrt{\text{Hz}}$	1 pA/ $\sqrt{\text{Hz}}$	5 k Ω
Error magnitude with $R_G = 5\text{k}\Omega$, $A_V = 2\text{ V/V}$ BW = 20MHz	5.8 μV RMS	22 μV RMS	40.5 μV RMS

⁽¹⁾ Thermal Noise = $\sqrt{4kTRG}$

4 Design Files

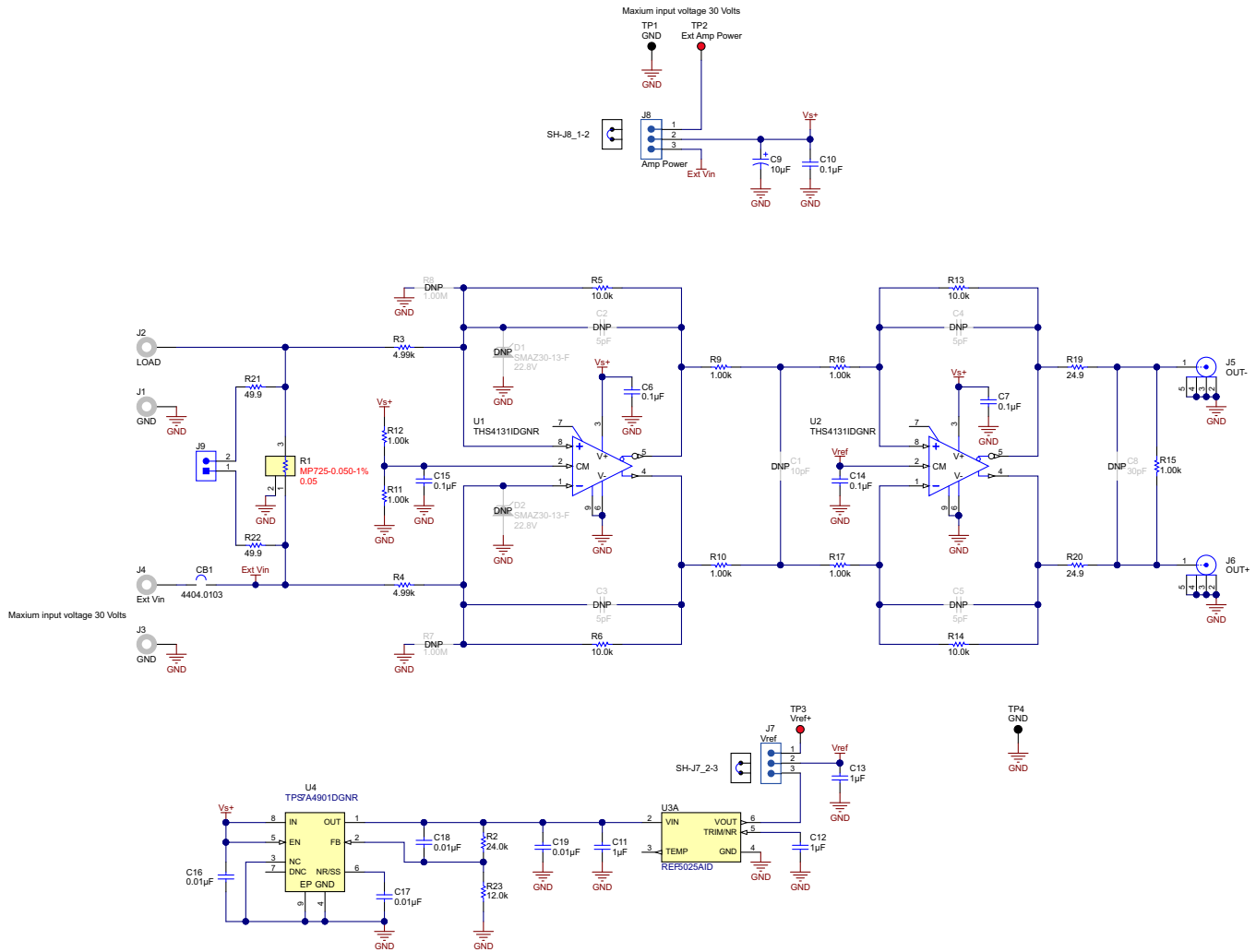4.1 Schematics

To download the schematics, see the design files at [TIDA-00976](#).  7 shows the schematic diagram for the reference design.



Copyright © 2017, Texas Instruments Incorporated

 7. Schematic Diagram

4.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-00976](#).

4.3 PCB Layout Recommendations

4.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-00976](#).

4.4 Altium Project

To download the Altium project files, see the design files at [TIDA-00976](#).

4.5 Layout Guidelines

Figure 8 shows the layout guidelines for this TI Design. The design is built on a four-layer FR-406 dielectric with the layer stackup as shown in Figure 9. The sense resistor for measuring load currents is placed symmetrically between the first THS4131 inputs. Traces carrying the load current to be measured have their widths adjusted for maximum current of 20 A on 2-oz copper thickness.

For layout guidelines related to the THS4131, refer the layout section in the *THS413x High-Speed, Low-Noise, Fully-Differential I/O Amplifiers*[1].

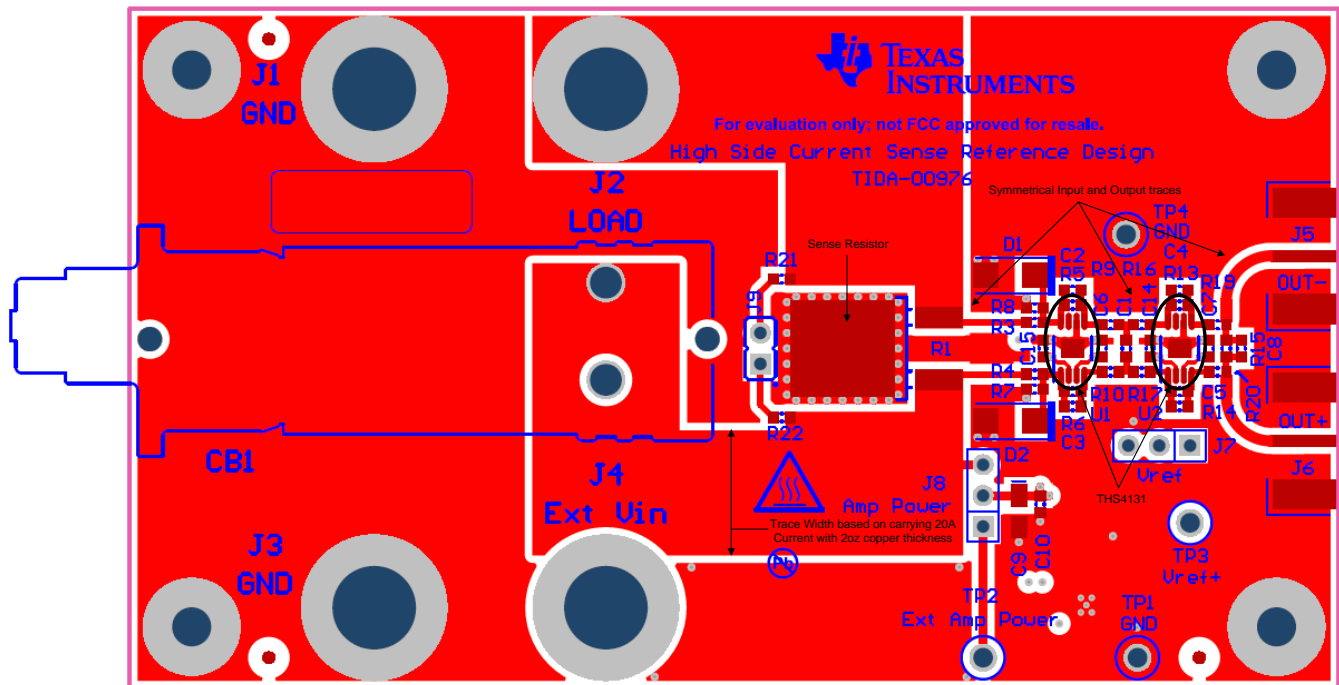


Figure 8. Example Layout (Top Layer)

 


Figure 9. Layer Stackup

4.6 Gerber Files

To download the Gerber files, see the design files at [TIDA-00976](http://www.ti.com/lit/zip/TIDA-00976).

4.7 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-00976](http://www.ti.com/lit/zip/TIDA-00976).

5 Related Documentation

1. Texas Instruments, [THS413x High-Speed, Low-Noise, Fully-Differential I/O Amplifiers](#), THS4130 and THS4131 Datasheet (SLOS318)
2. Texas Instruments, [Op amp stability and input capacitance](#), Technical Brief (SLYT087)
3. Texas Instruments, [Analysis of fully differential amplifiers](#), Technical Brief (SLYT157)
4. Vishay Corporation, [Vishay Resistors](#)

5.1 商標

TINA-TI is a trademark of Texas Instruments, Inc..

Vishay is a registered trademark of Vishay Intertechnology, Inc..

すべての商標および登録商標はそれぞれの所有者に帰属します。

6 About the Author

LOREN SIEBERT is an applications engineer with TI in the High-Speed Amplifier division in Fort Collins, Colorado. He supports applications ranging from 4G and 5G radio base stations to precision, high-accuracy ADC drivers.

TIの設計情報およびリソースに関する重要な注意事項

Texas Instruments Incorporated ("TI")の技術、アプリケーションその他設計に関する助言、サービスまたは情報は、TI製品を組み込んだアプリケーションを開発する設計者に役立つことを目的として提供するものです。これにはリファレンス設計や、評価モジュールに関する資料が含まれますが、これらに限られません。以下、これらを総称して「TIリソース」と呼びます。いかなる方法であっても、TIリソースのいずれかをダウンロード、アクセス、または使用した場合、お客様(個人、または会社を代表している場合にはお客様の会社)は、これらのリソースをここに記載された目的にのみ使用し、この注意事項の条項に従うことに合意したものとします。

TIによるTIリソースの提供は、TI製品に対する該当の発行済み保証事項または免責事項を拡張またはいかなる形でも変更するものではなく、これらのTIリソースを提供することによって、TIにはいかなる追加義務も責任も発生しないものとします。TIは、自社のTIリソースに訂正、拡張、改良、およびその他の変更を加える権利を留保します。

お客様は、自らのアプリケーションの設計において、ご自身が独自に分析、評価、判断を行う責任がお客様にあり、お客様のアプリケーション(および、お客様のアプリケーションに使用されるすべてのTI製品)の安全性、および該当するすべての規制、法、その他適用される要件への遵守を保証するすべての責任をお客様のみが負うことを理解し、合意するものとします。お客様は、自身のアプリケーションに関して、(1) 故障による危険な結果を予測し、(2) 障害とその結果を監視し、および、(3) 損害を引き起こす障害の可能性を減らし、適切な対策を行う目的で、安全策を開発し実装するために必要な、すべての技術を保持していることを表明するものとします。お客様は、TI製品を含むアプリケーションを使用または配布する前に、それらのアプリケーション、およびアプリケーションに使用されているTI製品の機能性を完全にテストすることに合意するものとします。TIは、特定のTIリソース用に発行されたドキュメントで明示的に記載されているもの以外のテストを実行していません。

お客様は、個別のTIリソースにつき、当該TIリソースに記載されているTI製品を含むアプリケーションの開発に関連する目的でのみ、使用、コピー、変更することが許可されています。明示的または黙示的を問わず、禁反言の法理その他どのような理由でも、他のTIの知的所有権に対するその他のライセンスは付与されません。また、TIまたは他のいかなる第三者のテクノロジーまたは知的所有権についても、いかなるライセンスも付与されるものではありません。付与されないものには、TI製品またはサービスが使用される組み合わせ、機械、プロセスに関連する特許権、著作権、回路配置利用権、その他の知的所有権が含まれますが、これらに限られません。第三者の製品やサービスに関する、またはそれらを参照する情報は、そのような製品またはサービスを利用するライセンスを構成するものではなく、それらに対する保証または推奨を意味するものでもありません。TIリソースを使用するため、第三者の特許または他の知的所有権に基づく第三者からのライセンス、あるいはTIの特許または他の知的所有権に基づくTIからのライセンスが必要な場合があります。

TIのリソースは、それに含まれるあらゆる欠陥も含めて、「現状のまま」提供されます。TIは、TIリソースまたはその仕様に関して、明示的か暗黙的にかかわらず、他のいかなる保証または表明も行いません。これには、正確性または完全性、権原、続発性の障害に関する保証、および商品性、特定目的への適合性、第三者の知的所有権の非侵害に対する黙示的保証が含まれますが、これらに限られません。

TIは、いかなる苦情に対しても、お客様への弁済または補償を行う義務はなく、行わないものとします。これには、任意の製品の組み合わせに関連する、またはそれらに基づく侵害の請求も含まれますが、これらに限られず、またその事実についてTIリソースまたは他の場所に記載されているか否かを問わないものとします。いかなる場合も、TIリソースまたはその使用に関連して、またはそれらにより発生した、実際の、直接的、特別、付随的、間接的、懲罰的、偶発的、または、結果的な損害について、そのような損害の可能性についてTIが知らされていたかどうかにかかわらず、TIは責任を負わないものとします。

お客様は、この注意事項の条件および条項に従わなかったために発生した、いかなる損害、コスト、損失、責任からも、TIおよびその代表者を完全に免責するものとします。

この注意事項はTIリソースに適用されます。特定の種類の資料、TI製品、およびサービスの使用および購入については、追加条項が適用されます。これには、半導体製品(<http://www.ti.com/sc/docs/stdterms.htm>)、評価モジュール、およびサンプル(<http://www.ti.com/sc/docs/sampterm.htm>)についてのTIの標準条項が含まれますが、これらに限られません。