

TPA3100D2 Mono Amplifier Configuration

Yang Boon Quek

HPL Audio Power Amplifiers

ABSTRACT

This application report presents two methods of configuring the TPA3100D2 as a mono amplifier.

Contents

1	Single-Channel Configuration	1
2	Paralleled Outputs Configuration	3

List of Figures

1	Single-Channel Configuration	2
2	THD+N Versus Po (Gain = 36 dB, Frequency = 1 kHz, $R_L = 8 \Omega$)	3
3	THD+N Versus Po (Gain = 36 dB, Frequency = 1 kHz, $R_L = 4 \Omega$)	3
4	Paralleled Outputs Configuration	4
5	THD+N Versus Po (Gain = 36 dB, Frequency = 1 kHz, $R_L = 8 \Omega$)	4
6	THD+N Versus Po (Gain = 36 dB, Frequency = 1 kHz, $R_L = 4 \Omega$)	5

List of Tables

1	Recommended Filter Component Values	4
---	---	---

1 Single-Channel Configuration

The TPA3100D2 can be configured as a mono amplifier by using only one channel. Besides using less external components, the single channel can be used to operate above the rated 20-W output power.

1.1 Circuit Implementation

- Power BOTH channels but leave LOUTN and LOU TP floating.
- Remove the VCLAMPL capacitor. Do not tie VCLAMPL to VCLAMPR.
- Remove BSLP and BSLN capacitors and leave LINP and LINN terminals floating.

Single-Channel Configuration

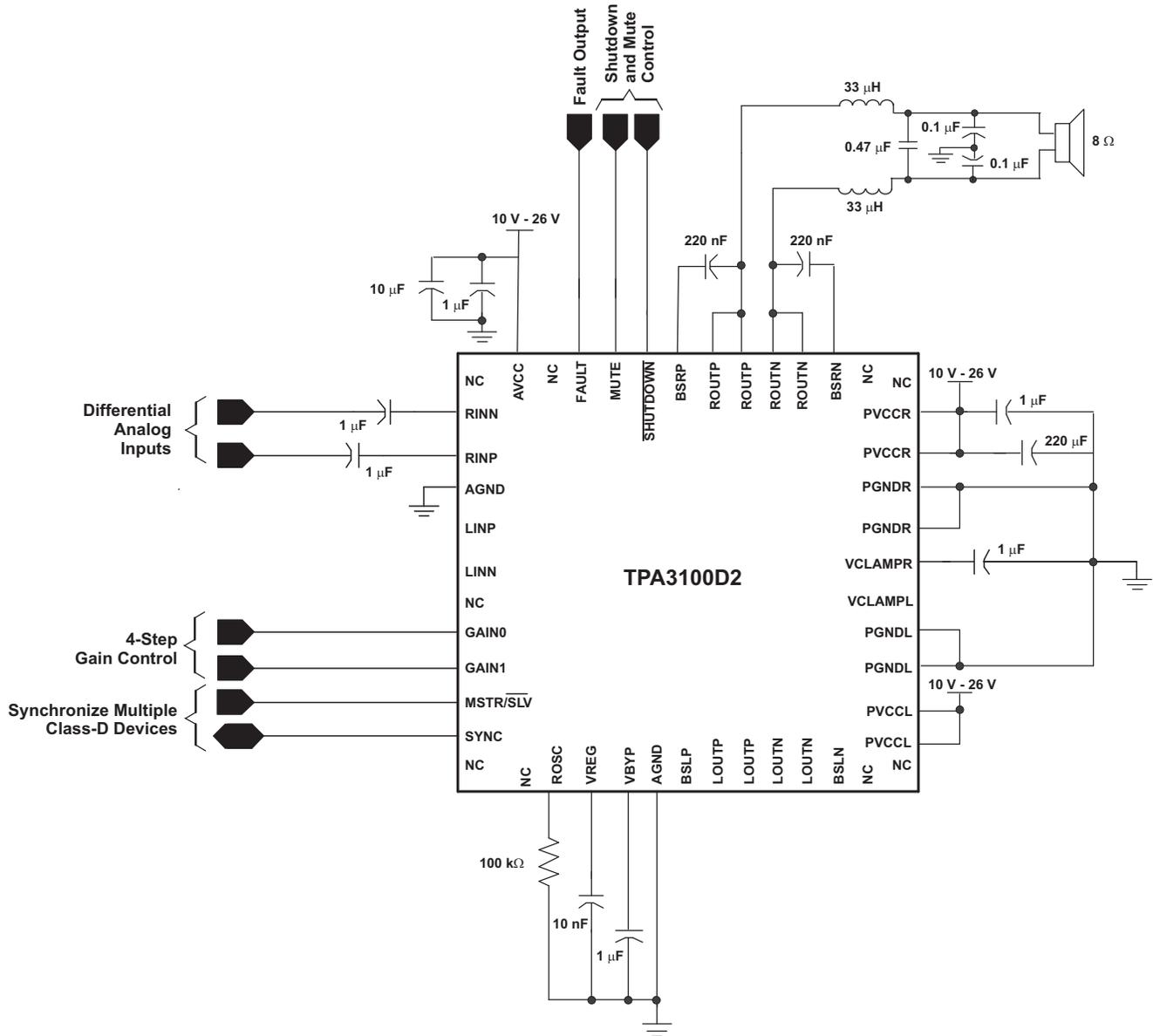


Figure 1. Single-Channel Configuration

1.2 Higher Output Power (Single Channel)

Higher output power is achieved as shown in Figure 2 and Figure 3.

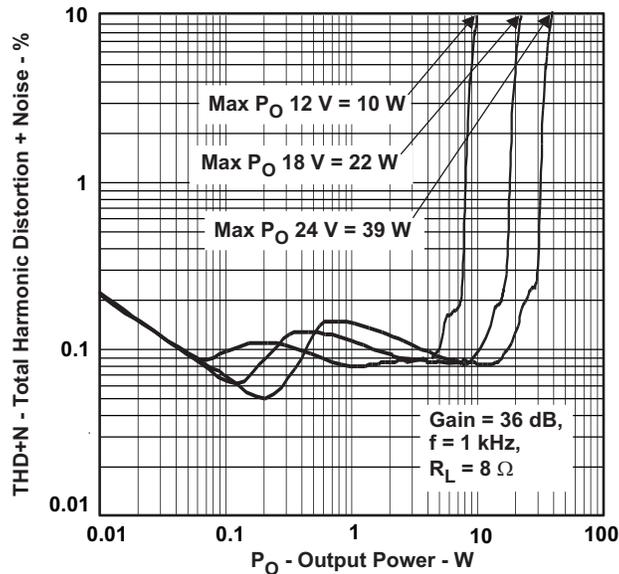


Figure 2. THD+N Versus P_o (Gain = 36 dB, Frequency = 1 kHz, $R_L = 8 \Omega$)

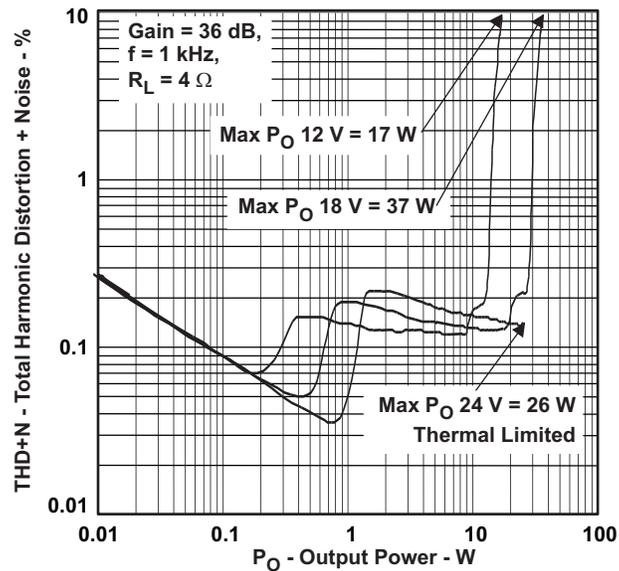


Figure 3. THD+N Versus P_o (Gain = 36 dB, Frequency = 1 kHz, $R_L = 4 \Omega$)

2 Paralleled Outputs Configuration

Another configuration of the TPA3100D2 as a mono amplifier is to parallel the left and right output channels. This can achieve significantly higher output power and better efficiency than the single-channel configuration.

The biggest drawback of the paralleled outputs configuration is the required use of two additional high-current-rated inductors.

2.1 Circuit Implementation

As both audio channels of the TPA3100D2 are designed to be operated independently, tying the outputs together results in a large current draw, and the device short-circuit protection is activated. Thus, a low-pass LC filter is placed between each output and the speaker as shown in Figure 4. Use the recommended L and C values as discussed in the applications report *Class-D LC Filters* (SLOA119).

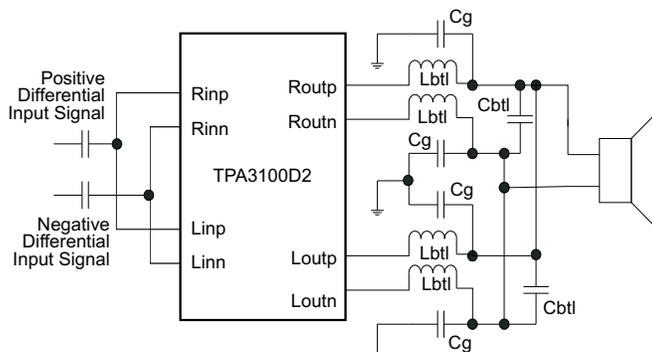


Figure 4. Paralleled Outputs Configuration

Note that the effective load resistance on each channel is equal to two times the speaker impedance.

Table 1. Recommended Filter Component Values

Rspeaker	Lbtl	Cbtl	Cg
4 Ω	33 μH	0.47 μF	0.1 μF
8 Ω	60 μH	0.22 μF	0.022 μF

2.2 Higher Output Power (Paralleled Outputs)

Higher output power can be achieved as shown in Figure 5 and Figure 6.

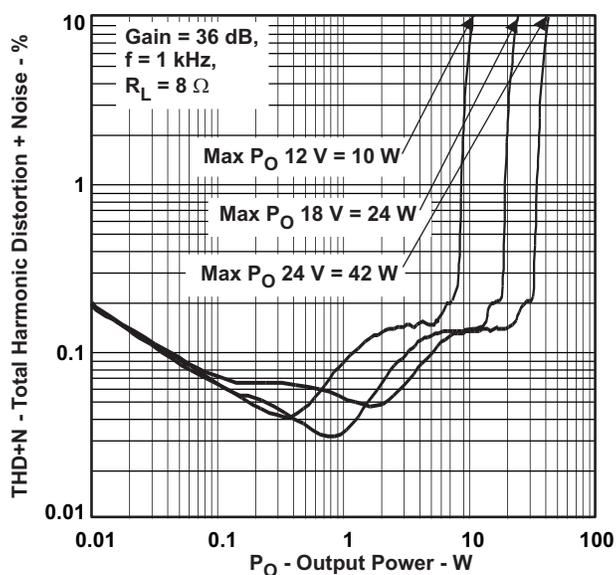


Figure 5. THD+N Versus Po (Gain = 36 dB, Frequency = 1 kHz, $R_L = 8 \Omega$)

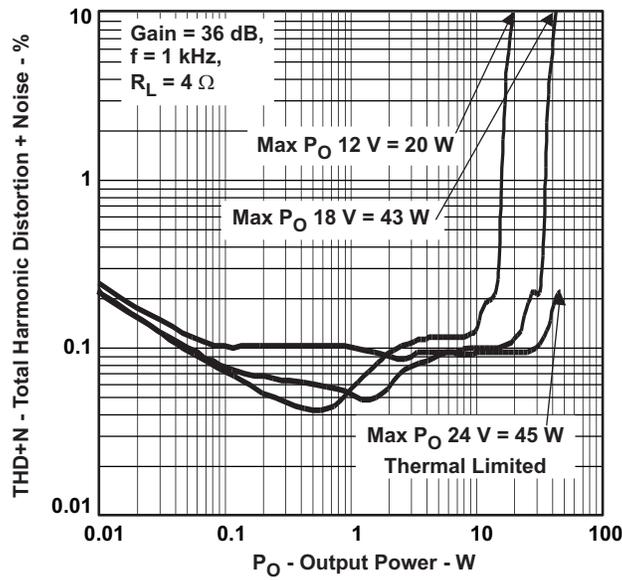


Figure 6. THD+N Versus P_O (Gain = 36 dB, Frequency = 1 kHz, $R_L = 4 \Omega$)

The paralleled output configuration is most effective at $V_{CC}=24$ V and $R_{speaker} = 4 \Omega$. For any other V_{CC} and $R_{speaker}$, the paralleled output configuration provides only marginal increase in output power while increasing the total cost and PCB board space.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
Low Power Wireless	www.ti.com/lpw

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated