

# ***AN-1644 Powering and Dimming High-Brightness LEDs with the LM3405 Constant-Current Buck Regulator***

---

## **ABSTRACT**

This application report describes a few of the many application solutions for the Texas Instruments LM3405 LED driver. The LM3405 device is offered in a 6-pin Thin-SOT (SOT) package and operates at an internal switching frequency of 1.6 MHz, allowing the use of small-value inductors, thereby saving board space.

---

## **Contents**

1	Introduction .....	2
2	Typical Application Circuit .....	2
3	PWM Dimming Using the EN/DIM Pin .....	3
4	Deriving a Self-Biased Boost Voltage When Driving Two or More LEDs in Series .....	5
5	Driving Multiple LED Strings with the LM3405 LED Driver .....	6
6	Driving Parallel LEDs with the LM3405 LED Driver .....	7
7	Conclusion .....	7

## **List of Figures**

1	Typical Application Circuit .....	2
2	PWM Dimming of LEDs by Applying a PWM Signal to the EN/DIM Pin.....	3
3	Average LED Current versus Duty Cycle and Frequency of V_PWM at the EN/DIM Pin.....	3
4	Startup Response of the LM3405 to an EN/DIM Signal with I <sub>F</sub> Set at 1A .....	3
5	Deriving a Self-Biased Boost Voltage from the LED String when Driving Two or More LEDs in Series .....	5
6	Driving Multiple LED Strings.....	6
7	Driving Multiple LEDs in Parallel.....	7

## 1 Introduction

The LM3405 is a 1A, constant-current buck regulator designed to provide a simple, highly-efficient solution for powering LEDs with the highest power density. The low-feedback reference voltage of 205 mV (typical) allows the use of LEDs with large forward voltages. The LM3405 LED driver comes with an integrated 1A high-side power switch, internal current limit, over-voltage protection and thermal shutdown. The LM3405 driver utilizes current mode control with internal compensation offering ease-of-use and predictable, high-performance regulation over a wide range of operating conditions.

## 2 Typical Application Circuit

Figure 1 shows the typical application circuit using the LM3405 regulator driving a single LED. The boost voltage can be derived from  $V_{IN}$  or  $V_{OUT}$ . The BOOST to SW voltage (VBOOST-VSW) should never exceed the operating limit of 5.5V, and must be greater than 2.5V for optimum efficiency.

In Figure 1, the maximum  $V_{IN}$  is 5V and therefore the boost voltage is derived from  $V_{IN}$ . The LM3405 data sheet provides a detailed description of various circuits for boost-voltage generation. The LM3405 driver tightly regulates the FB-pin voltage to 205 mV (typical) and this allows the LED current ( $I_F$ ) to be set by the following equation:

$$I_F = \frac{205 \text{ mV}}{R1} \quad (1)$$

$R1$  (min) is 200 m $\Omega$  such that  $I_F$  (max) is limited to 1A. In case of an over current, the internal current limit will trigger and turn off the internal power switch on a cycle-by-cycle basis. In case of an over voltage (sensed at the FB pin), the internal power switch is turned off. The LM3405 regulator also has a built-in thermal shutdown (with hysteresis) that also turns off the internal power switch if the die temperature exceeds a typical value of 165°C.

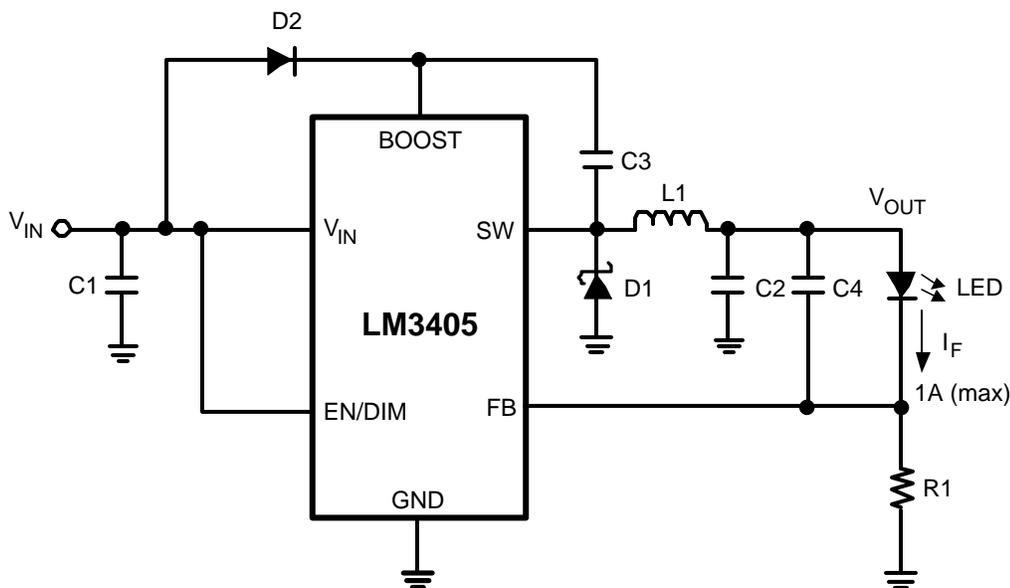


Figure 1. Typical Application Circuit

### 3 PWM Dimming Using the EN/DIM Pin

The LEDs can be dimmed by applying a PWM-logic signal to the EN/DIM pin of the LM3405 driver as shown in Figure 2.

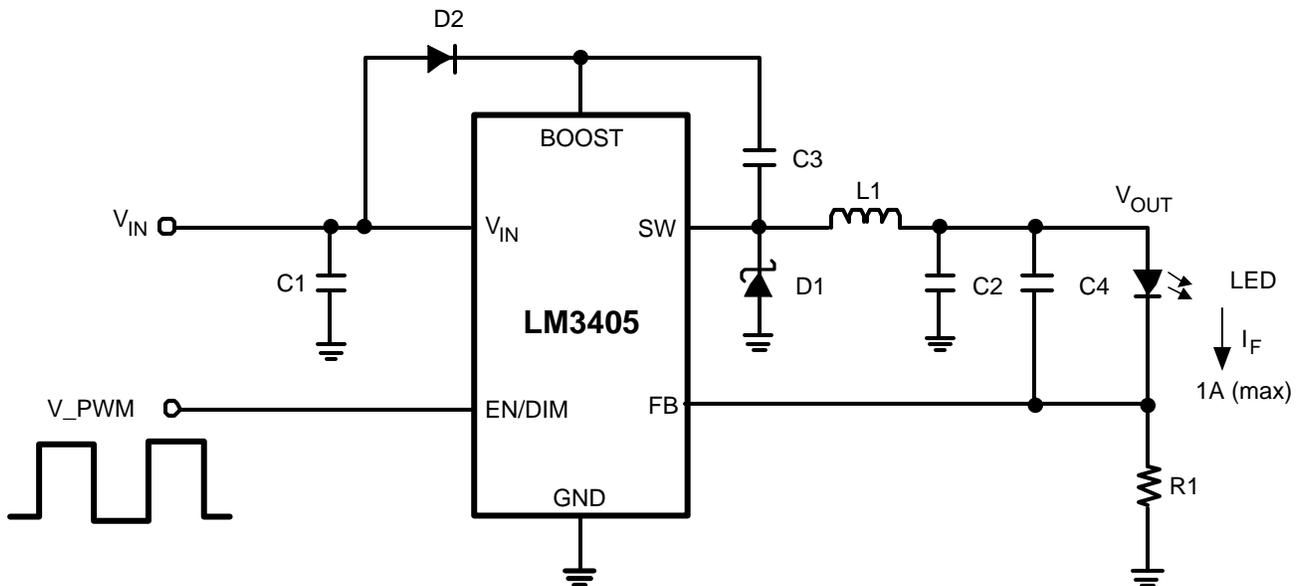


Figure 2. PWM Dimming of LEDs by Applying a PWM Signal to the EN/DIM Pin

A logic high at  $V\_PWM$  enables the IC, and a logic low disables the IC. In this manner, the LED current is turned on and off. In order to eliminate flicker, the lowest PWM-dimming frequency is normally chosen to be above 100 Hz. The upper end of the PWM frequency is determined by the turn-on delay of the LM3405. If the  $V\_PWM$  signal has an ON-time of  $T_{ON}$  and a period of  $T_{PER}$ , the average  $I_F$  is given approximately by Equation 2. Note that the delay in enabling and disabling the IC is not included in Equation 2. Typically the time delay from the instant where  $EN/DIM = 1$  to the instant where  $I_F$  is fully established is approximately 100  $\mu s$  (see Figure 4).

$$I_{F(\text{average})} = \frac{205 \text{ mV}}{R1} \times \left[ \frac{T_{ON}}{T_{PER}} \right] \quad (2)$$

The average LED current is therefore controlled by  $T_{ON}$ ,  $T_{PER}$ , or both and is perceived by the eye as a brightness change. Figure 3 shows the measured average LED current for varying duty cycles and frequencies.

The startup delay of the LM3405 device is shown in Figure 4 for an LED-current setting of 1A. This is the delay from the instant when  $EN/DIM=1$  to the instant when  $I_F$  settles to 900 mA (90% of the set LED current).

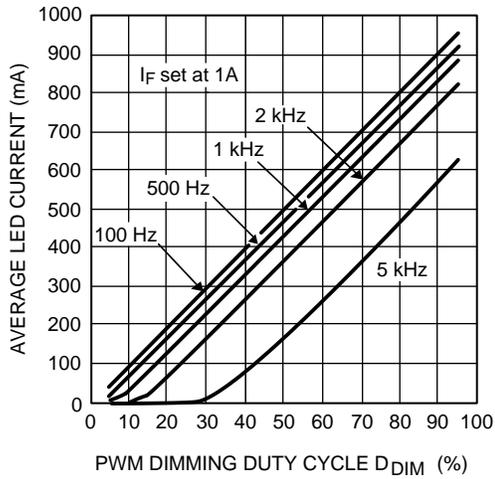


Figure 3. Average LED Current versus Duty Cycle and Frequency of  $V_{PWM}$  at the EN/DIM Pin

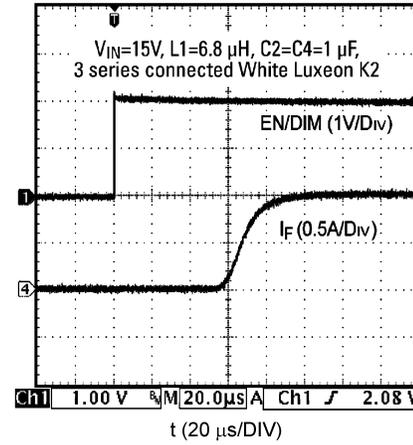


Figure 4. Startup Response of the LM3405 to an EN/DIM Signal with  $I_F$  Set at 1A

#### 4 Deriving a Self-Biased Boost Voltage When Driving Two or More LEDs in Series

In a typical application where two or more LEDs are driven in a single string, the boost voltage is derived from a separate, external low-voltage source so as to meet the (VBOOST-VSW) voltage requirement. This is because when powering two or more LEDs in series,  $V_{IN}$  will be greater than 5V and therefore  $V_{IN}$  cannot be used to provide VBOOST. In this case,  $V_{OUT}$  will also be high and cannot be used to derive VBOOST.

Figure 5 shows another approach for deriving a self-biased boost voltage from the LED string itself without the need for generating a separate low-voltage supply.

The anode of the boost diode D2 is connected to the anode of LED3. The voltage at the anode of LED3 is approximately equal to 205 mV plus the forward voltage  $V_F$  of LED3. This voltage is approximately in the range of 3V to 4V (depending on the  $I_{F3}$  current setting) and meets the BOOST to SW voltage requirement. It must be noted that the current through LED1 and LED2 will be slightly larger than the current in LED3 due to the fact that the average charging current for the boost capacitor C3 will now be provided through LED1 and LED2. Therefore, the LED currents are:

$$I_{F3} = \left[ \frac{205 \text{ mV}}{R1} \right]$$

$$I_{F1} = I_{F2} = I_{F3} + \overline{I_{C3}}$$

where

- $I_{F1}$ ,  $I_{F2}$ , and  $I_{F3}$  are the currents in LED1, LED2, and LED3, respectively
- $\overline{I_{C3}}$  is the average current charging C3 over one switching cycle. (3)

This approach can be used if exact current matching (and hence brightness) is not required between  $I_{F1}$  and  $I_{F3}$  or between  $I_{F2}$  and  $I_{F3}$ .

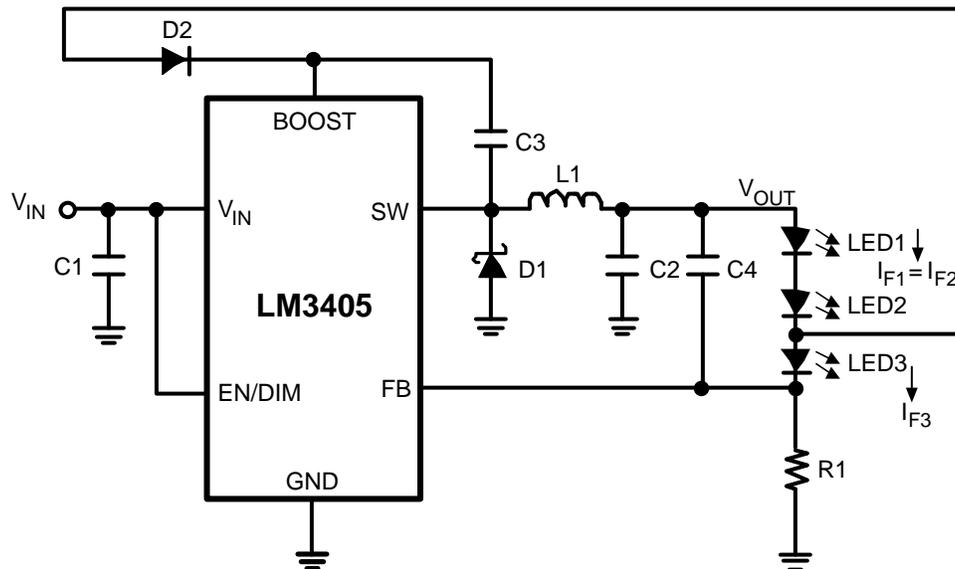


Figure 5. Deriving a Self-Biased Boost Voltage from the LED String when Driving Two or More LEDs in Series

## 5 Driving Multiple LED Strings with the LM3405 LED Driver

The LM3405 LED driver can be used to drive multiple LED strings in parallel as shown in Figure 6. The current in the primary branch (with LED1 and LED2) will be tightly regulated by the feedback loop.

The current in the secondary branch (with LED3) will be regulated based on  $V_{OUT}$ , forward voltage of LED3, and R2. The value of R2 can be adjusted to get the desired brightness for LED3.

$$I_{F1} = I_{F2} = \left[ \frac{205 \text{ mV}}{R1} \right] = I_{\text{PRIMARY}}$$

$$I_{F3} = \frac{205 \text{ mV} + V_{F1} + V_{F2} - V_{F3}}{R2} = I_{\text{SECONDARY}}$$

where

- $V_{F1}$  and  $V_{F2}$  are the respective forward voltages of LED1 and LED2 at the primary current level
- $V_{F3}$  is the forward voltage of LED3 at the secondary current level
- $I_{F1}$  is the current in LED1
- $I_{F2}$  is the current in LED2
- $I_{F3}$  is the current in LED3

(4)

In Figure 6, VBST can be connected to an external DC source of 3V to 5V. VBST can also be derived from the cathode of LED3.

If VBST is derived from the cathode of LED3, this VBST can be written as (assuming  $V_{F1} = V_{F2} = V_{F3} = V_F = 3.8\text{V}$ ):

$$\text{VBST} = 205 \text{ mV} + V_{F1} + V_{F2} - V_{F3} \cong 205 \text{ mV} + V_F \cong 4\text{V}$$

(5)

Note that the average current through LED3 will now be higher since the average current to charge C3 is supplied through LED3 as discussed in the previous section.

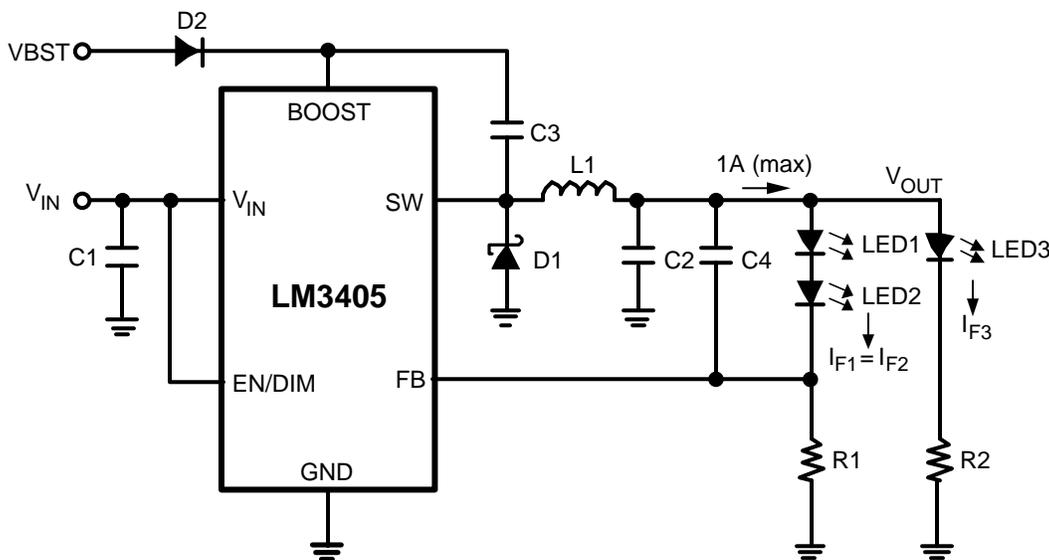


Figure 6. Driving Multiple LED Strings

## 6 Driving Parallel LEDs with the LM3405 LED Driver

Multiple LEDs can be paralleled and connected between  $V_{OUT}$  and FB as shown in Figure 7.

The voltage at the FB pin is regulated to 205 mV by the control loop and therefore the current in R1 is fixed.  $V_{OUT}$  is determined by the LED with the highest forward voltage. This solution has the advantage of having a single resistor set the total currents in the LEDs but has no control of equal current sharing between the LEDs.

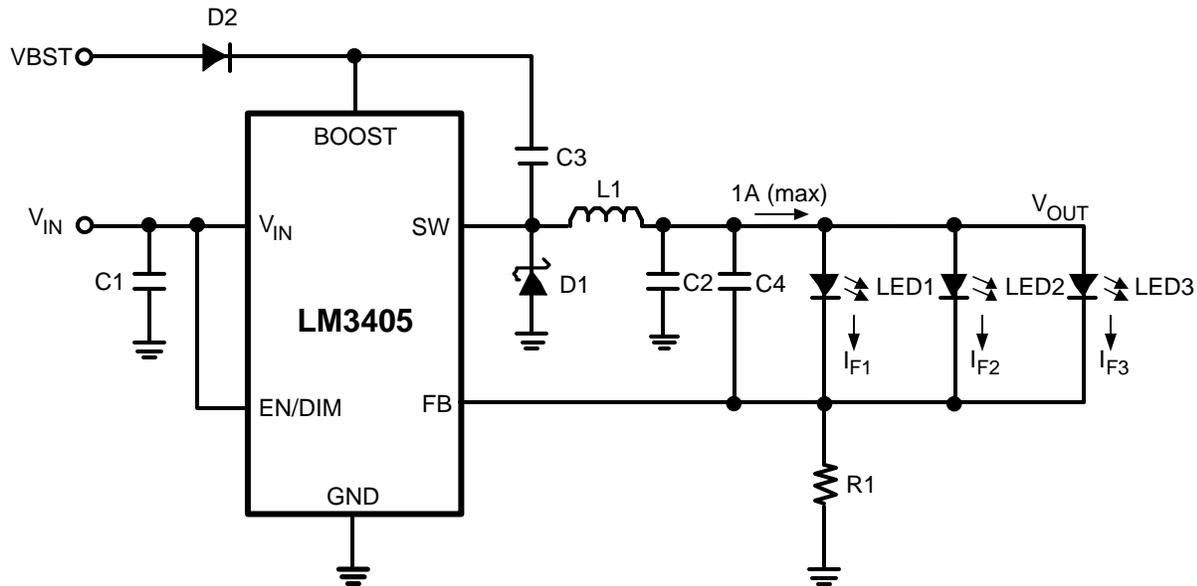


Figure 7. Driving Multiple LEDs in Parallel

## 7 Conclusion

This application report describes a few application solutions using the LM3405 buck regulator. These solutions provide the user with highly-compact, driving and dimming solutions for high-brightness LEDs. For a detailed description of operation and component design guidelines, see LM3405A datasheet ([SNVS508](#)).

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)