

# **AN-1935 LM3445 Off-Line TRIAC Dimmer LED Driver Demo Board**

---

---

---

## **1 Introduction**

The demonstration board included in this shipment converts  $90V_{AC}$  to  $135V_{AC}$  input, and drives seven, or eight series connected LED's at 350 mA average current. The LM3445 switching frequency is set at a nominal 225 kHz. This is a four-layer board using the bottom and top layer for component placement. The demonstration board can be modified to adjust the LED forward current, the number of series connected LEDs and switching frequency.

A bill of materials below describes the parts used on this demonstration board. A schematic and layout have also been included below along with measured performance characteristics. The above restrictions for the input voltage are valid only for the demonstration board as shipped with the schematic below. Please refer to the *LM3445 Triac Dimmable Offline LED Driver* ([SNVS570](#)) data sheet for detailed information regarding the LM3445 device, and the application circuit

## **2 Operating Conditions**

$$V_{IN} = 90V_{AC} \text{ to } 135V_{AC}$$

Seven or eight series connected LEDs

$$I_{LED} = 350 \text{ mA}$$

### 3 Simplified LM3445 Schematic and Efficiency Plot

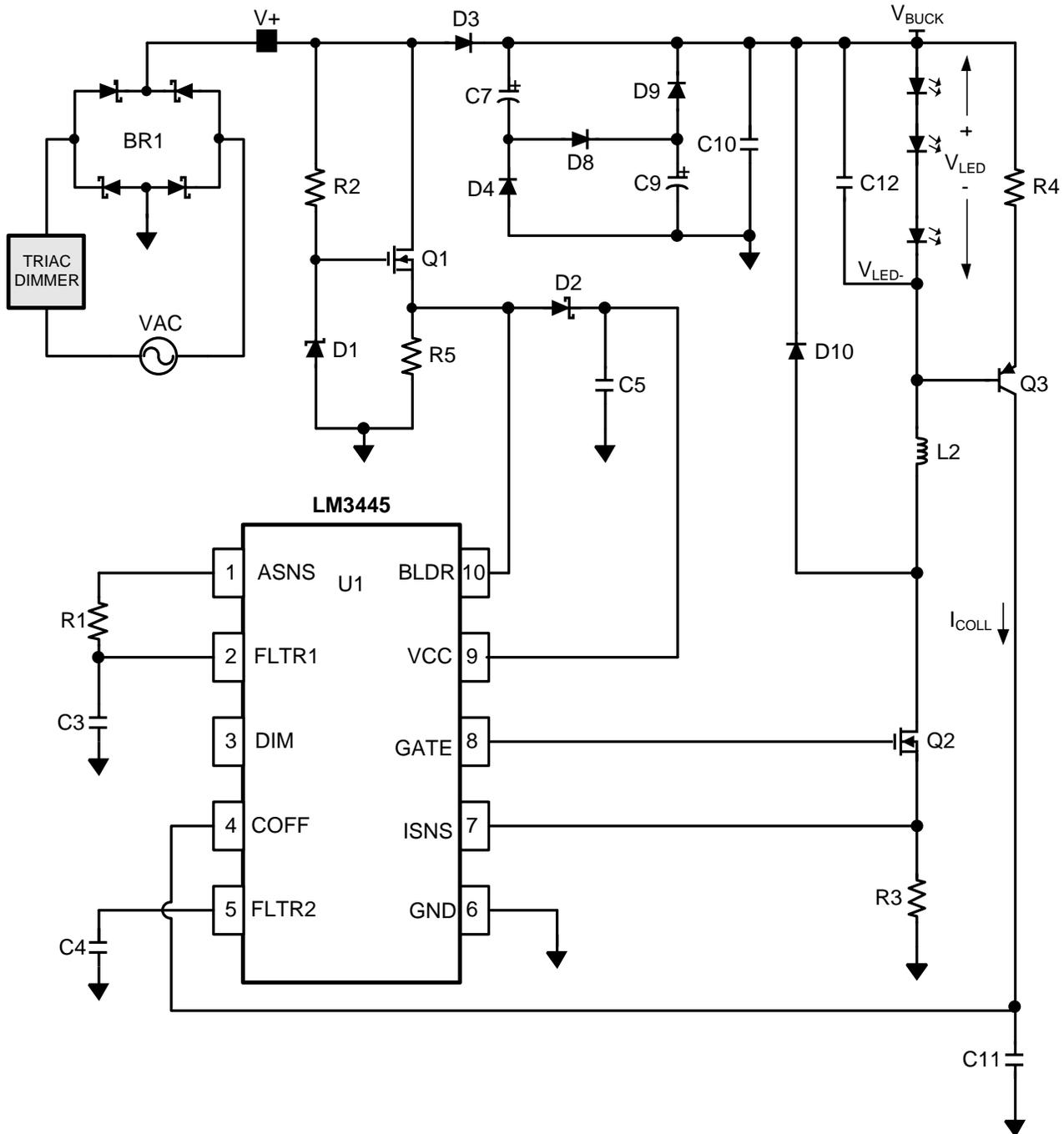
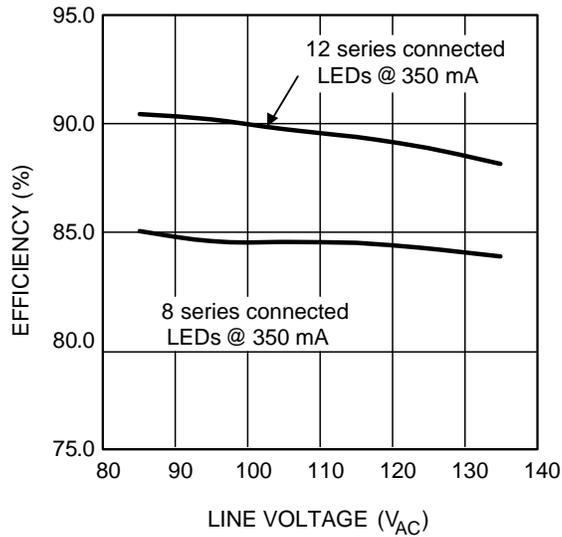


Figure 1. Simplified LM3445 Schematic

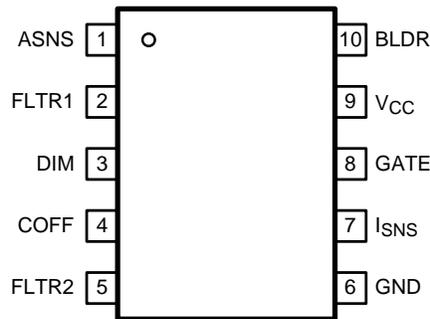


**Figure 2. Efficiency Plot**

**WARNING**

The LM3445 evaluation boards have no isolation or any type of protection from shock. Caution must be taken when handling evaluation board. Avoid touching evaluation board, and removing any cables while evaluation board is operating. Isolating the evaluation board rather than the oscilloscope is highly recommended.


## 4 Pin-Out



**Figure 3. 10-Pin VSSOP**


**Table 1. Pin Description 10 Pin VSSOP**

Pin #	Name	Description
1	ASNS	PWM output of the triac dim decoder circuit. Outputs a 0 to 4V PWM signal with a duty cycle proportional to the triac dimmer on-time.
2	FLTR1	First filter input. The 120Hz PWM signal from ASNS is filtered to a DC signal and compared to a 1 to 3V, 5.85 kHz ramp to generate a higher frequency PWM signal with a duty cycle proportional to the triac dimmer firing angle. Pull above 4.9V (typical) to tri-state DIM.
3	DIM	Input/output dual function dim pin. This pin can be driven with an external PWM signal to dim the LEDs. It may also be used as an output signal and connected to the DIM pin of other LM3445 or LED drivers to dim multiple LED circuits simultaneously.
4	COFF	OFF time setting pin. A user set current and capacitor connected from the output to this pin sets the constant OFF time of the switching controller.
5	FLTR2	Second filter input. A capacitor tied to this pin filters the PWM dimming signal to supply a DC voltage to control the LED current. Could also be used as an analog dimming input.
6	GND	Circuit ground connection.
7	ISNS	LED current sense pin. Connect a resistor from main switching MOSFET source, ISNS to GND to set the maximum LED current.
8	GATE	Power MOSFET driver pin. This output provides the gate drive for the power switching MOSFET of the buck controller.
9	V <sub>CC</sub>	Input voltage pin. This pin provides the power for the internal control circuitry and gate driver.
10	BLDR	Bleeder pin. Provides the input signal to the angle detect circuitry as well as a current path through a switched 230Ω resistor to ensure proper firing of the triac dimmer.

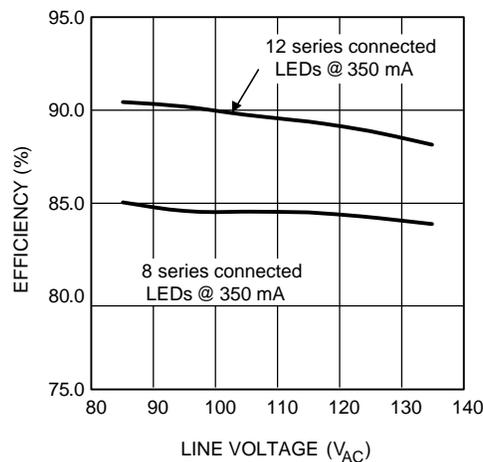

**Figure 4. LM3445 Efficiency vs Input Voltage  
8 and 12 Series connected LEDs @ 350 mA**

5 LM3445 Evaluation Board Schematic

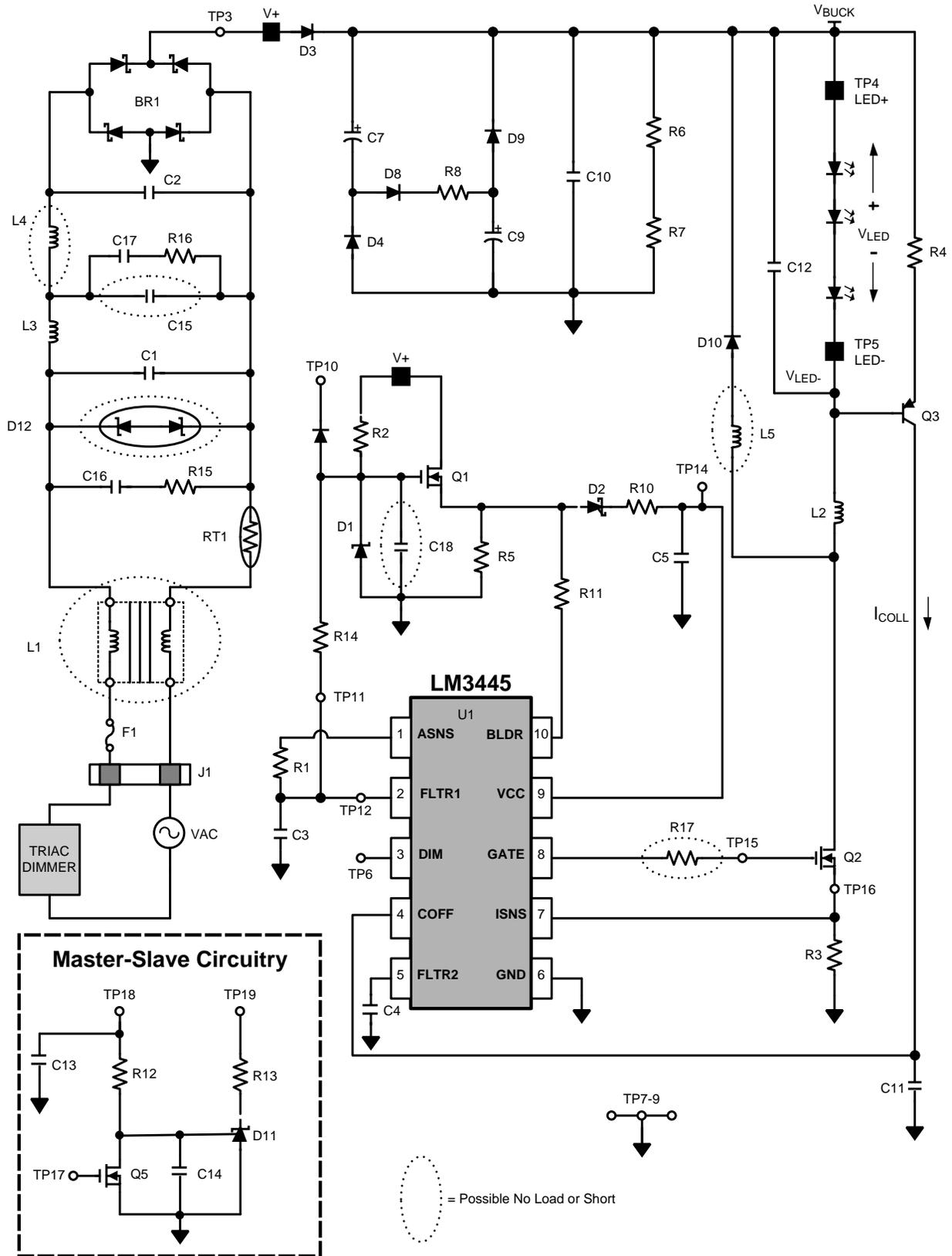

**Table 2. Bill of Materials LM3445 Evaluation Board**

REF DES	Description	MFG	MFG Part Number
U1	IC, CTRLR, DRVR-LED, VSSOP10	TI	LM3445
BR1	Bridge Rectifier, SMT, 400V, 800 mA	Diodes Inc	HD04-T
L1 (no load, short pad)	Common mode filter DIP4NS, 900 mA, 700 $\mu$ H	Panasonic	ELF11M090E
L2	Inductor, SHLD, SMT, 1A, 470 $\mu$ H	Coilcraft	MSS1260-474KLB
L3	Diff mode inductor, 500 mA 1 mH	Coilcraft	MSS1260-105KL-KLB
L4 (no Load, short pad)	Diff mode inductor, 500 mA 1 mH	Coilcraft	MSS1260-105KL-KLB
L5	Bead Inductor, 160 $\Omega$ , 6A	Steward	HI1206T161R-10
C1, C2	Cap, Film, X2Y2, 12.5MM, 250VAC, 20%, 10nF	Panasonic	B32921C3103M(K)
C3	Cap, X7R, 0603, 16V, 10%, 470 nF	MuRata	GRM188R71C474KA88D
C4	Cap, X7R, 0603, 16V, 10%, 100 nF	MuRata	GRM188R71C104KA01D
C5, C6	Cap, X5R, 1210, 25V, 10%, 22 $\mu$ F	MuRata	GRM32ER61E226KE15L
C7, C9	Cap, AL, 200V, 105C, 20%, 33 $\mu$ F	UCC	EKXG201ELL330MK20S
C10	Cap, Film, 250V, 5%, 10 nF	Epcos	B32521C3103J
C12	Cap, X7R, 1206, 50V, 10%, 1.0 $\mu$ F	MuRata	C1206F105K5RACTU
C11	Cap, C0G, 0603, 100V, 5%, 120 pF	MuRata	GRM1885C2A121JA01D
C13	Cap, X7R, 0603, 50V, 10%, 1.0 nF	Kemet	C0603C102K5RACTU
C14	Cap, X7R, 0603, 50V, 10%, 22 nF	Kemet	C0603C223K5RACTU
C15 (no load)	Cap, Film, X2Y2, 12.5MM, 250VAC, 20%, 10nF	Panasonic	B32921C3103M(K)
C16, C17	Cap, X7R, 1206, 250V, 10%, 0.047 $\mu$ F	TDK	C3216X7R2E473K
C18 (no load)	Cap, X7R, 0603, 50V, 10%, 1.0 nF	Kemet	C0603C102K5RACTU
D1	Diode, ZNR, SOT23, 15V, 5%	On Semi	BZX84C15LT1G
D2, D3, D4, D8, D9	Diode, FR, SOD123, 200V, 1A	Rohm	RF071M2S
D10	Diode, FR, SMB, 400V, 1A	On Semi	MURS140T3G
D11	IC, SHNT, ADJ, SOT23, 2.5V, 0.5%	TI	TL431BIDBZR
D12 (No Load)	TVS	Littelfuse	
D13	Diode, SCH, SOD123, 40V, 120 mA	NXP	BAS40H
R1	Resistor, 0603, 1%, 280 k $\Omega$	Panasonic	ERJ-3EKF2803V
R2	Resistor, 1206, 1%, 100 k $\Omega$	Panasonic	ERJ-8ENF1003V
R3	Resistor, 1210, 5%, 1.8 $\Omega$	Panasonic	ERJ-14RQJ1R8U
R4	Resistor, 0603, 1%, 576 k $\Omega$	Panasonic	ERJ-3EKF5763V
R5	Resistor, 1206, 1%, 1.00 k $\Omega$	Panasonic	ERJ-8ENF1001V
R6, R7	Resistor, 0805, 1%, 1.00 M $\Omega$	Rohm	MCR10EZH1004
R8, R10, R17, R18, R19, R21	Resistor, 1206, 0.0 $\Omega$	Yageo	RC1206JR-070RL
R20 (No Load)	Resistor, 1206, 0.0 $\Omega$		
R9	Resistor, 1210, 0.0 $\Omega$	Vishay	CRCW12100000Z0EA
R11	Resistor, 0603, 0.0 $\Omega$	Yageo	RC0603JR-070RL
R12	Resistor, 0603, 1%, 33.2k $\Omega$	Panasonic	ERJ-3EKF3322V
R13	Resistor, 0603, 1%, 2.0k $\Omega$	Panasonic	ERJ-3EKF2001V
R14	Resistor, 0805, 1%, 3.3 M $\Omega$	Rohm	MCR10EZIP335
R15, R16	Resistor, 2210, 820 $\Omega$	Vishay	CRCW2010820RJNEF
RT1	Thermistor, 120V, 1.1A, 50 $\Omega$ @ 25C	CL-140	KC014L-ND
Q1, Q2	XSTR, NFET, DPAK, 300V, 4A	Fairchild	FQD7N30TF
Q3	XSTR, PNP, SOT23, 300V, 500 mA	Fairchild	MMBTA92
Q5	XSTR, NFET, SOT23, 100V, 170 mA	Fairchild	BSS123
J1	Terminal Block 2 pos	Phoenix Contact	1715721
F1	Fuse, 125V, 1,25A	bel	SSQ 1.25



**WARNING**

The LM3445 evaluation boards have no isolation or any type of protection from shock. Caution must be taken when handling evaluation board. Avoid touching evaluation board, and removing any cables while evaluation board is operating. Isolating the evaluation board rather than the oscilloscope is highly recommended.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)