

LM3405A Reference Design for MR16 LED Bulb, 600mA

National Semiconductor
LM3405A
Man Lau
October 2007



1.0 Design Specifications

Inputs	Output #1
VinMin=10.8ACV	Vout1=3.8V
VinMax=13.2ACV	Iout1=0.6A

2.0 Design Description

The LM3405A LED driver has been used for this design. It is a current mode control buck switching regulator designed to provide a simple, high efficiency solution for driving high power LEDs (Typical $V_f = 3.8V$). With a 0.205V reference voltage feedback control to minimize power dissipation, an external resistor sets the current as needed for driving various types of LEDs. The LM3405A uses internal compensation offering ease of use and predictable, high performance regulation over a wide range of operating conditions. Additional features include user accessible EN/DIM pin for enabling and PWM dimming of LEDs, thermal shutdown, cycle-by-cycle current limit and over-current protection.


With the advancement of high brightness LED technology, LEDs are rapidly evolving to become a common light source for general illumination. LEDs are regarded as a longer life, lower energy consumption light source without the toxic material in CFLs. This design is an example of an MR16 form factor LED bulb to replace a halogen light bulb. It is capable of providing 600mA constant current to drive high

brightness LEDs from a 12V AC source. Thanks to the wide operating voltage range of the LM3405A (from 3VDC to 20VDC), a very small input capacitor can maintain continuous operation. Switching frequency is internally set to 1.6MHz, allowing the use of extremely small surface mount inductors and chip capacitors. All these factors help to squeeze the overall dimensions of the PCB to fit the stringent space constraints of the MR16 form factor and this makes LM3405A the best LED driver for this application.

3.0 Features

- VIN range: 12VAC $\pm 10\%$
- 0.6A output current
- Small PCB size
- Can drive a 1W LED
- Single LED application
- Over-current protection
- Thermal shutdown
- Integrated 1.0A NFET

4.0 Schematic

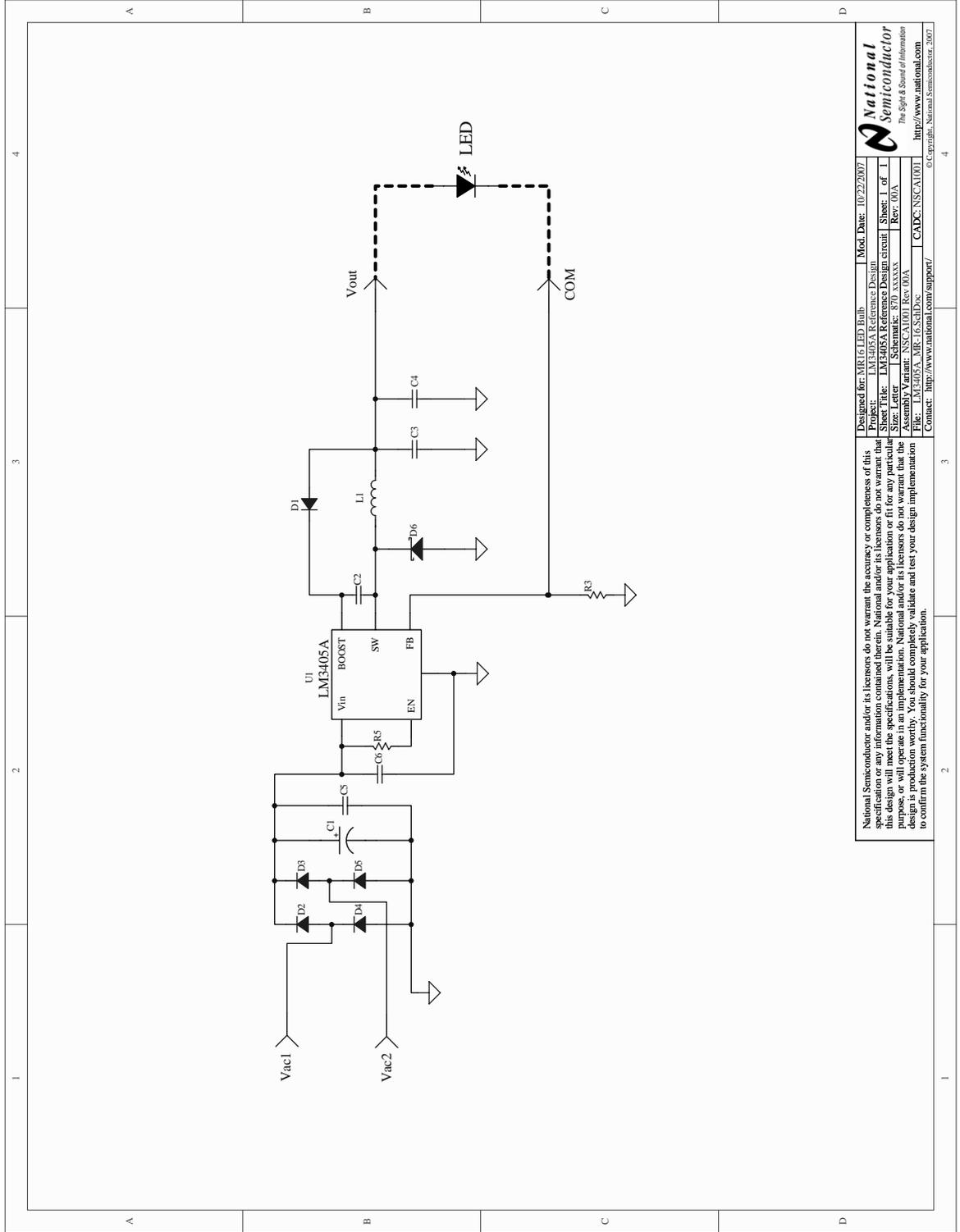

National Semiconductor and/or its licensors do not warrant the accuracy or completeness of this specification or any information contained herein. National and/or its licensors do not warrant that this design will meet the specifications, will be suitable for your application or fit for any particular purpose, or will operate in an implementation. National and/or its licensors do not warrant that the information provided herein is current, complete, or accurate. You should make and test your design implementation to confirm the system functionality for your application.

Designed for:	MR16 LED Bulb	Mod. Date:	10/22/2007
Project Name:	MR16 LED Bulb	Sheet 1 of	1
Sheet Title:	LM3405A Reference Design circuit	Rev:	00A
Size:	Letter	Schematic:	870_A3XXXX
Assembly Variant:	NSCA100 Rev. 00A	CADES:	NSCA100
File:	LM3405A_MR-16_Sch.Doc	Contact:	http://www.national.com/support/



National Semiconductor
The Right Stuff of Information
<http://www.national.com>
© Copyright, National Semiconductor, 2007

schematics

FIGURE 1. Schematic

5.0 Bill of Materials

Item	Part	Manufacturer	Part #	Attribute
1	C1	Lelon or Rabycon	SG or YK, 220uF, 16V	16V, 220uF, 8mm * 7mm
2	C2	Murata	GRM188R71C474KA88	CAP0805, 0.47 uF
3	C3	Murata	GRM188R71C474KA88	CAP0805, 0.47 uF
4	C4	Murata	GRM40X7R103K50	CAP0805, 10nF
5	C5	Murata	GRM219R71C154KA73	CAP0805, 0.15 uF
6	C6	Murata	GRM219R71C154KA73	CAP0805, 0.15 uF
7	D1	Vishay	1N4148W	75V, 200mA, Diode
8	D2	IR	10MQ040N	40V, 1A, Diode
9	D3	IR	10MQ040N	40V, 1A, Diode
10	D4	IR	10MQ040N	40V, 1A, Diode
11	D5	IR	10MQ040N	40V, 1A, Diode
12	D6	IR	10MQ040N	40V, 1A, Diode
13	L1	Sumida	CDH3D13SHPNP-6R8MC	inductor 6.8uH
14	R3	Vishay	CRCW08050R33F	RES0805, 0.33 ohm
15	R5	Vishay	CRCW06031023F	RES0603, 102K ohm
16	U1	National Semiconductor	LM3405A	LM3405A

6.0 Other Operating Values

Operating Values

Description	Parameter	Value	Unit
Modulation Frequency	Frequency	1600	KHz
Total output power	Pout	1	W
Input Voltage	Vin	12	Vac
Output Current (LED current)	Iout	600	mA


7.0 Board Photos



boardphoto2


FIGURE 3. Board photo

8.0 Layouts

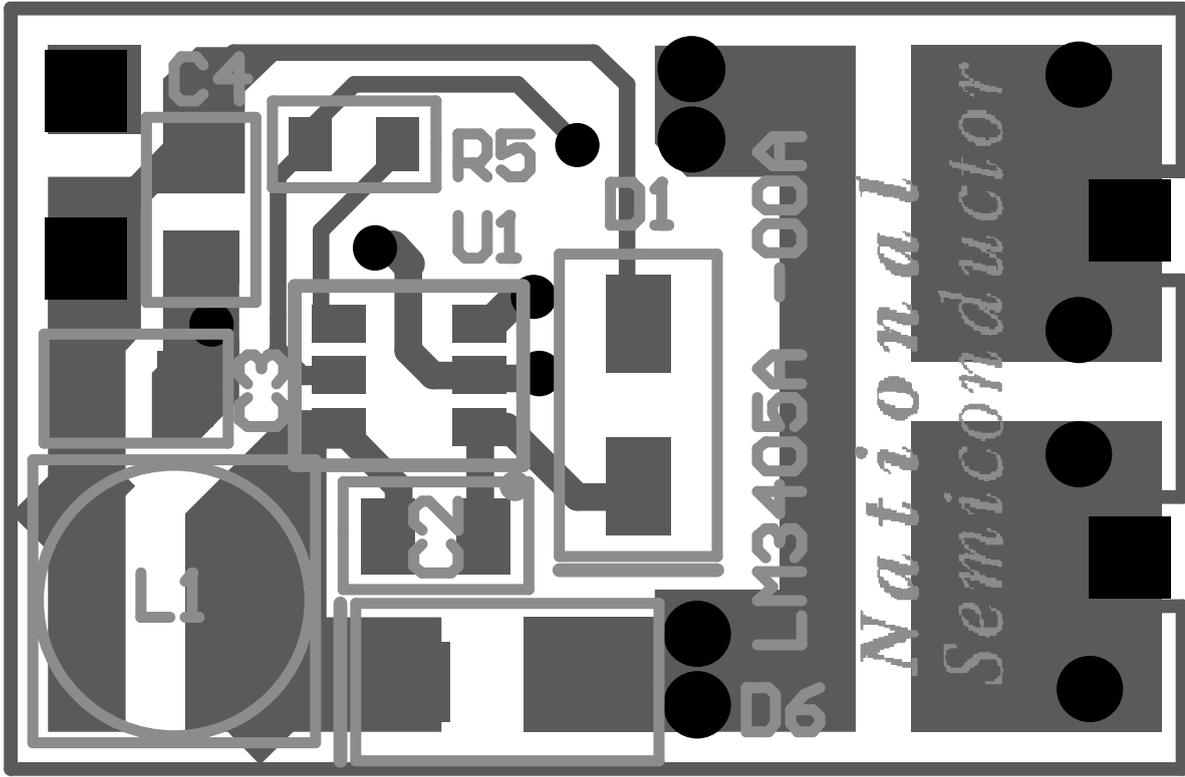

layout6



FIGURE 4. LM3405A - PCB bottom side

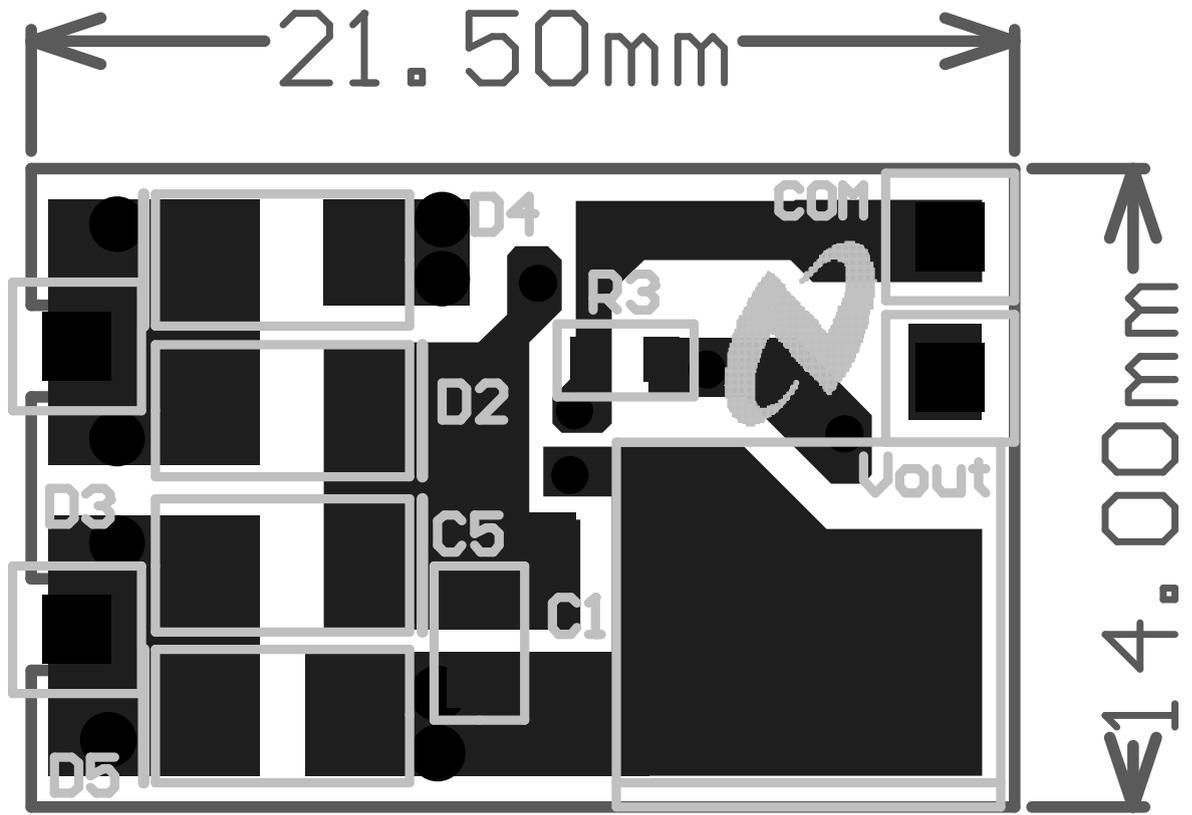

layout7

FIGURE 5. LM3405A - PCB top side

9.0 Waveforms

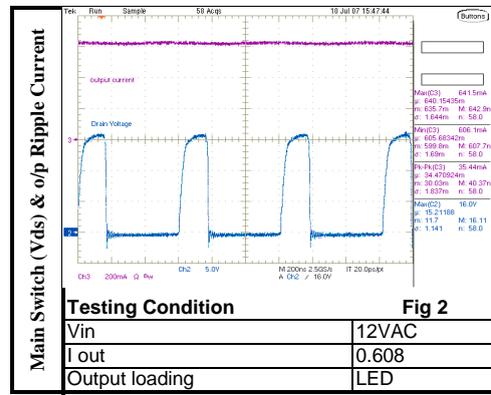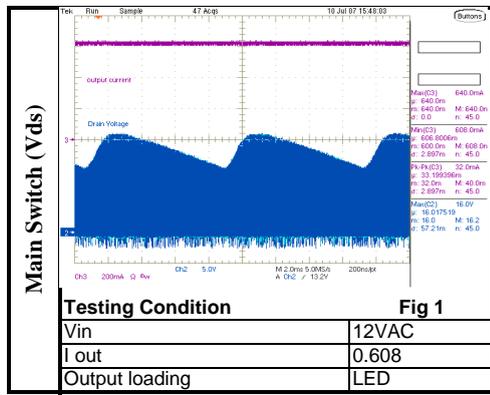

waveform1

FIGURE 6. LM3405A - Waveform

10.0 Appendix

1 Output Voltage & Current

Parameter		Reading	
Vin	Loading	Vo	Io
12.00VAC	LED = 1 pcs	3.34V	0.61A

2 Efficiency

Input voltage	Reading					
	Vin	PF	P in	Vo	Io	Efficiency
12.00VAC	12VAC / 50Hz	0.59	3.60W	3.34V	0.61A	56.41%

Remark : The output loading is LED (Luxeon III LXHL-LM3C green)

image

FIGURE 7. LM3405A - Test data

Notes

LM3405A

Notes

National Semiconductor's design tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Reference designs are created using National's published specifications as well as the published specifications of other device manufacturers. While National does update this information periodically, this information may not be current at the time the reference design is built. National and/or its licensors do not warrant the accuracy or completeness of the specifications or any information contained therein. National and/or its licensors do not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. National and/or its licensors do not warrant that the designs are production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which,
 - are intended for surgical implant into the body, or
 - support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor certifies that the products and packing materials meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.

Leadfree products are RoHS compliant.



National Semiconductor Americas Customer Support Center
 Email: new.feedback@nsc.com
 Tel: 1-800-272-9959

National Semiconductor Europe Customer Support Center
 Fax: +49 (0) 180-530-85-86
 Email: europe.support@nsc.com
 Deutsch Tel: +49 (0) 69 9508 6208
 English Tel: +49 (0) 870 24 0 2171
 Français Tel: +33 (0) 1 41 91 8790

National Semiconductor Asia Pacific Customer Support Center
 Email: ap.support@nsc.com

National Semiconductor Japan Customer Support Center
 Fax: 81-3-5639-7507
 Email: jpn.feedback@nsc.com
 Tel: 81-3-5639-7560

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2012, Texas Instruments Incorporated