

Power Supply Design Seminar

Survey of Resonant Converter
Topologies

Author

Sheng-Yang Yu

Runruo Chen

Ananthakrishnan Viswanathan



Agenda



Introduction

Feature presentation

Live Q&A session

Enter questions into chat at any time



2025 Power Supply Design Seminar



Webinar Series

April 30	Common mistakes in DC/DC converters and how to fix them
May 28	Survey of resonant converter topologies
June 25	Power Factor Correction (PFC) circuit basics
July 30	Power-conversion techniques for complying with automotive emissions requirements
August 27	Switch-mode power converter compensation made easy
September 24	Constructing your power supply – layout considerations



**Last Wednesday of every month
8:00AM & 8:00PM (US Central Time Zone)**

Welcome to the PSDS 2025 webinar series!



The history of Power Supply Design Seminar

- In 1977 Bob Mammano, the “Father of PWM Industry,” started the seminar
- 47+ years
- 26+ seminars
- 100+ technical topics
- 50,000+ customers
- A comprehensive archive of white papers, presentations and videos



Power supply industry legends associated with PSDS:

Bob Mammano, Lloyd Dixon, Bill Andreycak, Robert Kollman, Laszlo Balogh

WWW.TI.COM/PSDS for all prior content


Agenda

- 2- and 3-element resonant topologies fundamentals
- LLC series resonant converter (LLC-SRC) introduction and design example
- Resonant converters for wide input/output voltage range
- Resonant converter variations
- Resonant converter design challenges
- Effects of real life parasitics/parameters
- Resonant converter selection guide – rule of thumb

2- and 3-Element Resonant Topologies Fundamentals



Classical Resonant Topology Structure

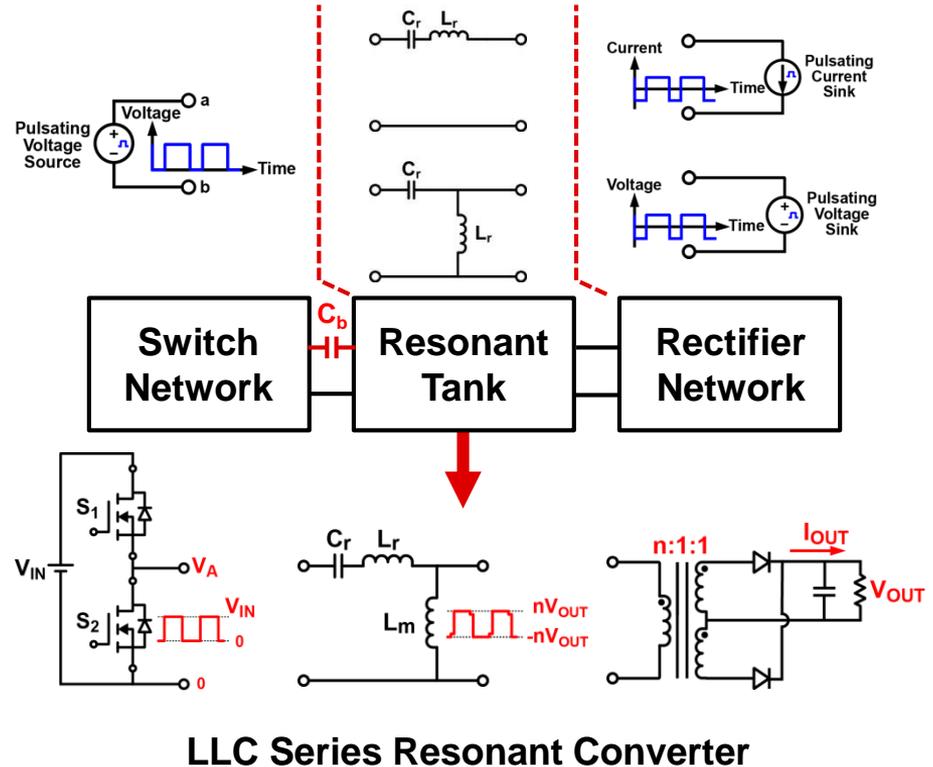- Why?
 - Possible soft-switching over entire load range
- Structure
 - Switch network
 - Resonant tank
 - Rectifier network
- Assumptions
 - Variable frequency control (VFC)
 - Consider only switch network with **pulsating voltage output**




Resonant Topology Analysis

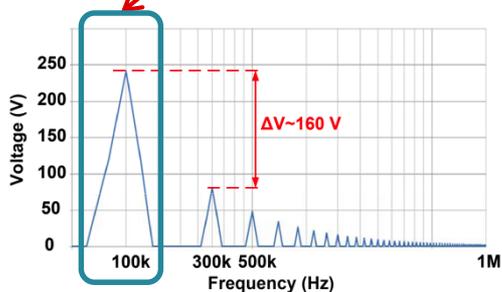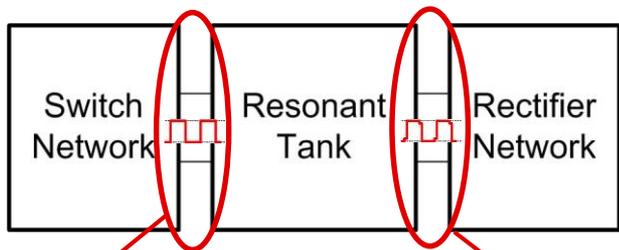
Fundamental harmonic analysis (FHA)
(or so called sinusoidal approximation)




FFT of a Square Wave

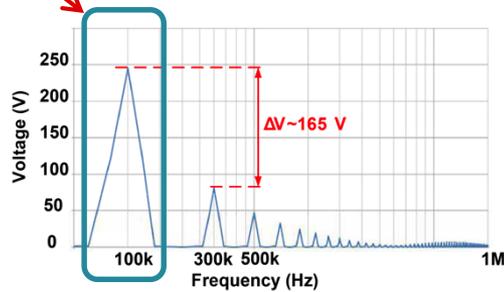





FFT of Resonant Tank Response

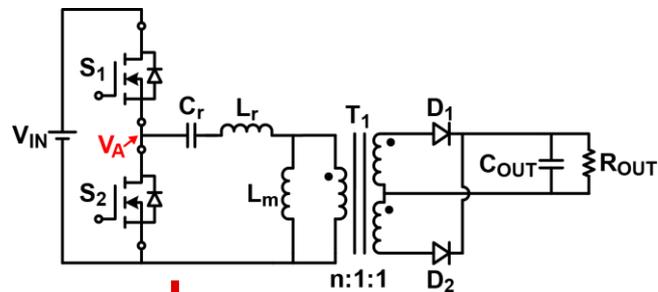

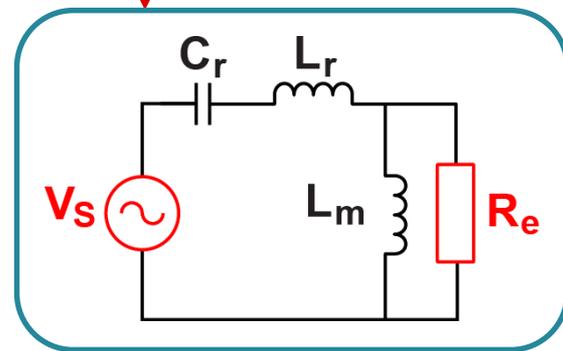
Simple linear circuit with
only 1st order harmonic



Circuit Linearization Example: LLC-SRC

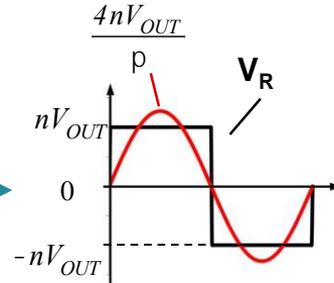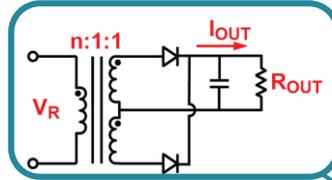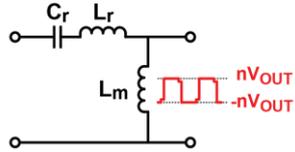
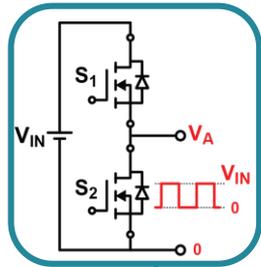


$V_{R(1st)}$: 1st order harmonic of V_R

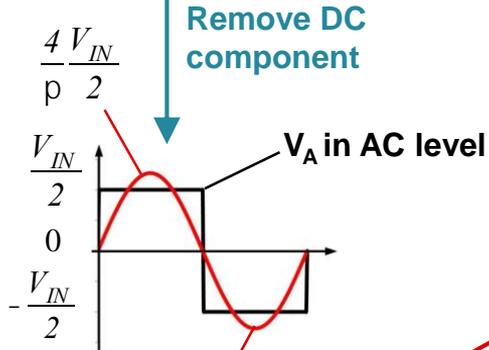

V_s : 1st order harmonic of V_A
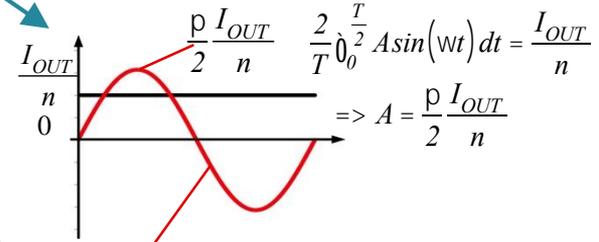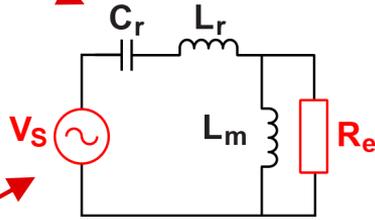
$$V_s(t) = \frac{4(V_{IN}/2)}{p} \sin(\omega_s t)$$





I_R : AC current with half cycle average value to be I_{OUT}/n



$$R_e = \frac{V_{R(1st)}(t)}{I_R(t)} = \frac{8n^2 V_{OUT}}{p^2 I_{OUT}} = \frac{8n^2}{p^2} R_{OUT}$$

Fundamental Resonant Elements



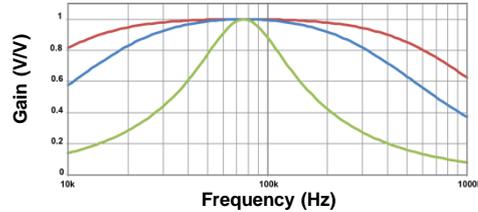
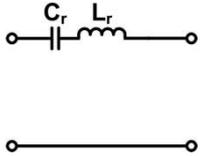
Series Resonance (SR) – Provides “Buck” Function



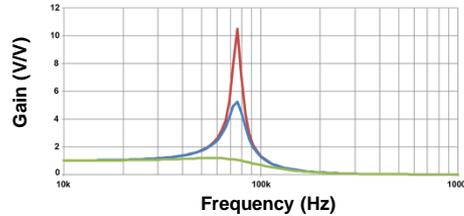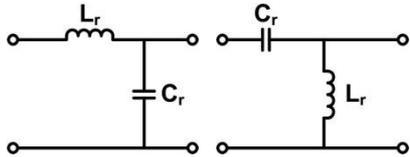Parallel Resonance (PR) – Provides “Boost” Function












Notch Resonance (NR) – Zero Gain at f_r

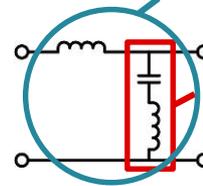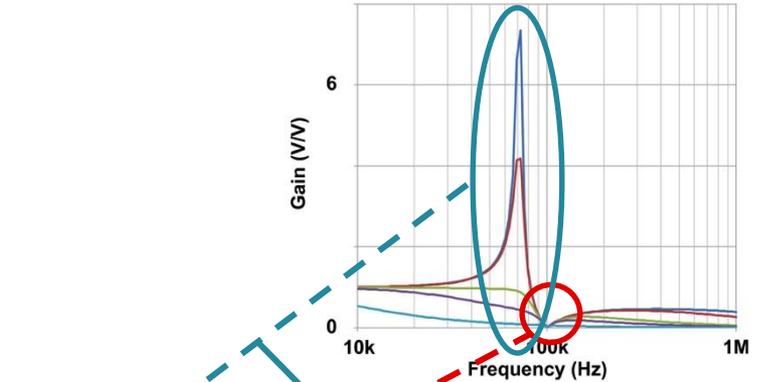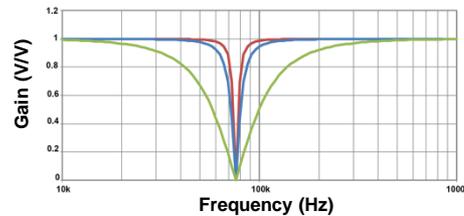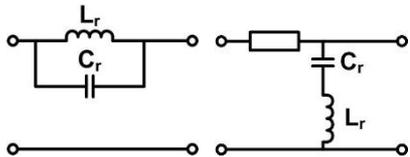


Notch Resonance
Parallel Resonance

2-Element Soft-Switching Resonant Topologies

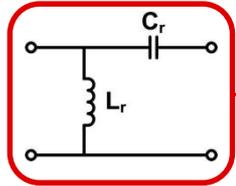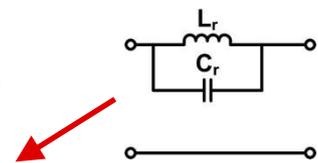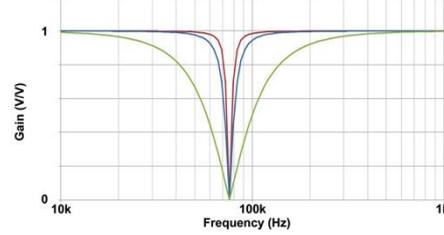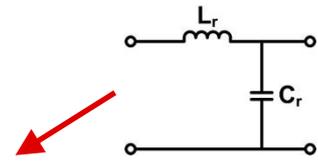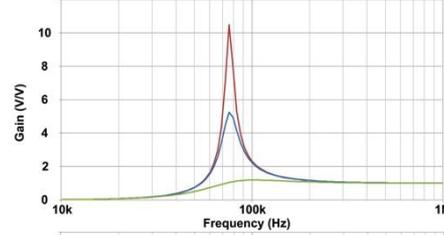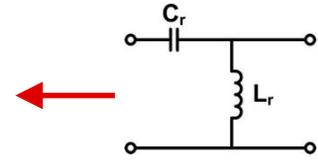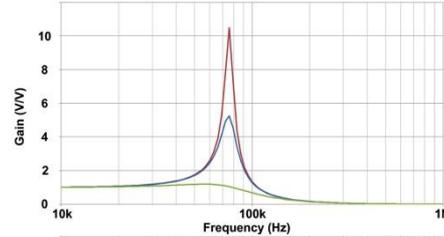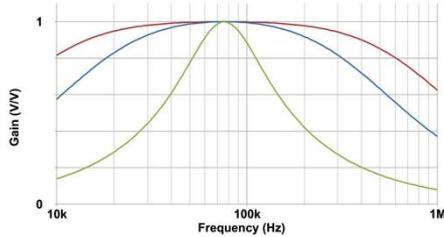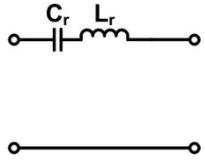
Input/output voltage gain (w/ sinusoidal voltage input)



Inductor voltage clamped - not resonant

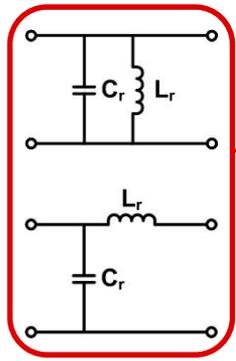


Requires current source

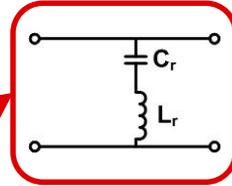

Lack of voltage regulation capability

3-Element Soft-Switching Resonant Topologies

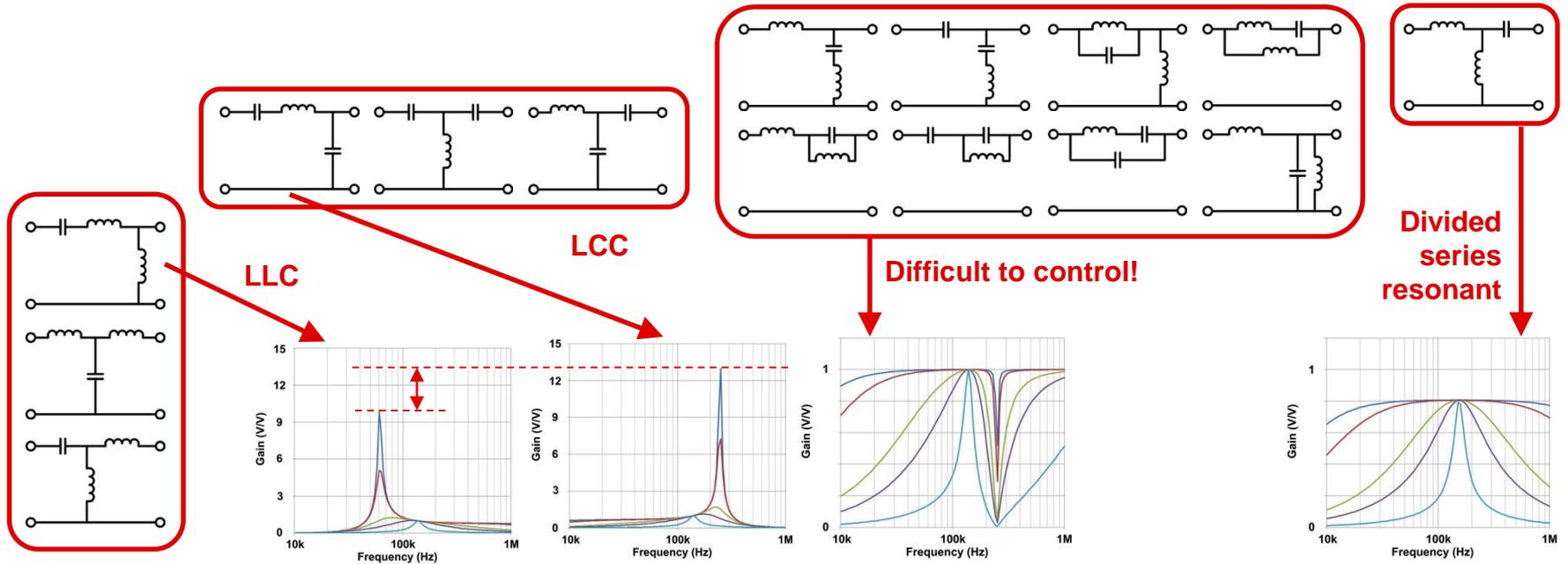- 36 possible resonant tanks, 23 could be used with voltage source
- 15 of the 23 have all resonant elements participate in output voltage/current regulation








How to Achieve Soft-Switching?

Necessary and sufficient soft-switching conditions:

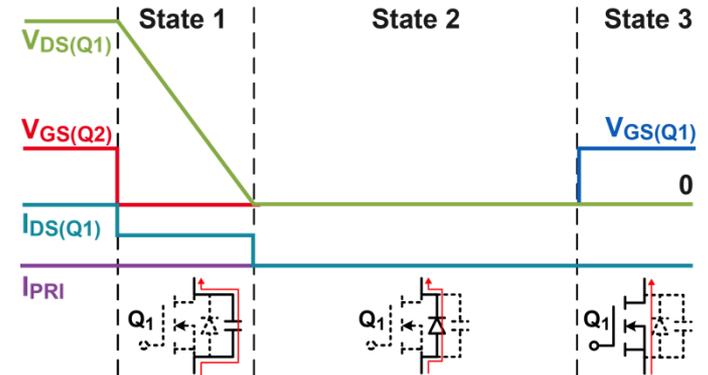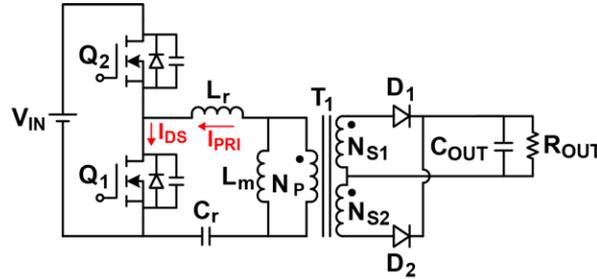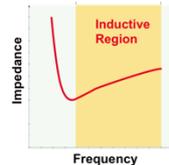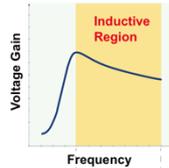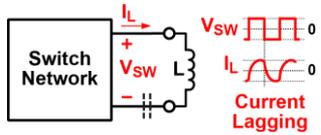1. Inductive input impedance
2. Sufficient energy inside resonant tank for discharging/charging output capacitor of switches in switching network
3. Enough dead-time between switches inside switch network

$$LI_L^2 > C_{TOTAL}V_{SW}^2 = 2C_{OSS}V_{SW}^2$$







LLC Series Resonant Converter (LLC-SRC)

LLC-SRC Key Features

Benefits

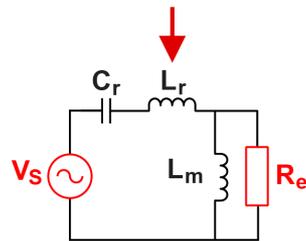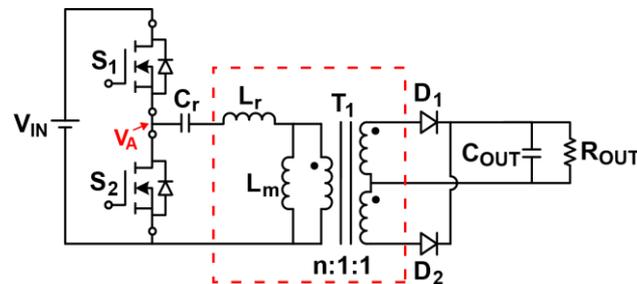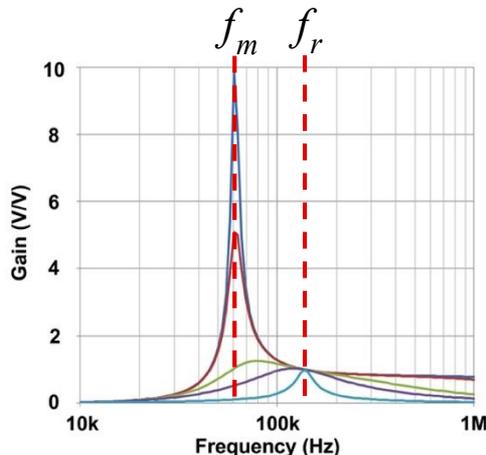
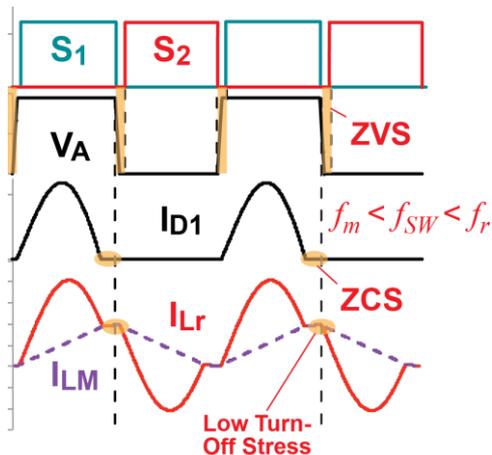
- Easy magnetic integration
- Achieve soft-switching over entire load range
 - Possible for high frequency operation
- Optimized efficiency around f_r






$$\frac{nV_{OUT}}{V_{IN}/2} = \frac{1}{\sqrt{\left(\frac{1}{W^2 L_m C_r}\right)^2 \left(\frac{W^2}{W_m^2} - 1\right)^2 + \left(\frac{1}{W C_r n^2 R_{OUT}}\right)^2 \left(1 - \frac{W^2}{W_r^2}\right)^2}}$$

$$\omega_r = 2\pi f_r = \frac{1}{\sqrt{L_r C_r}} \quad \omega_m = 2\pi f_m = \frac{1}{\sqrt{(L_r + L_m) C_r}}$$

Effect of Resonant Parameter Variations

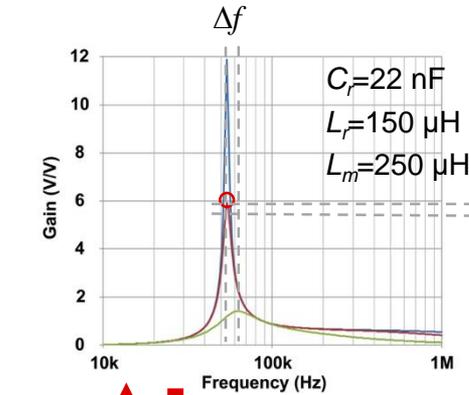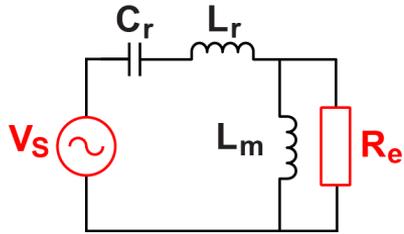

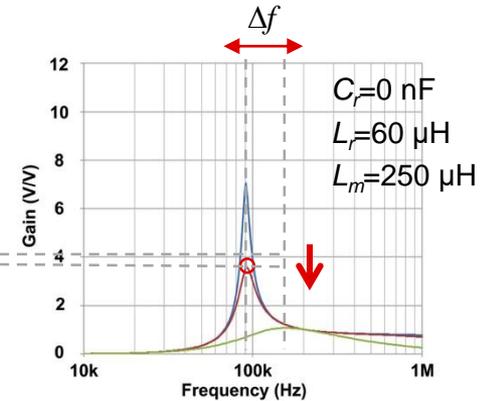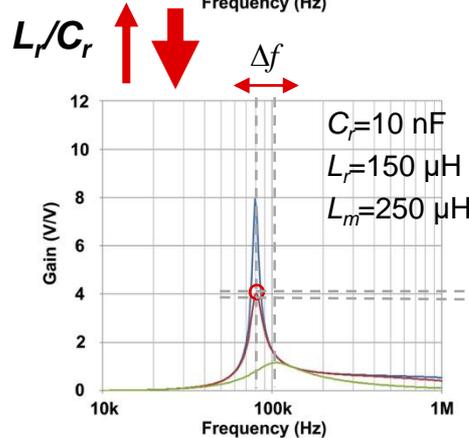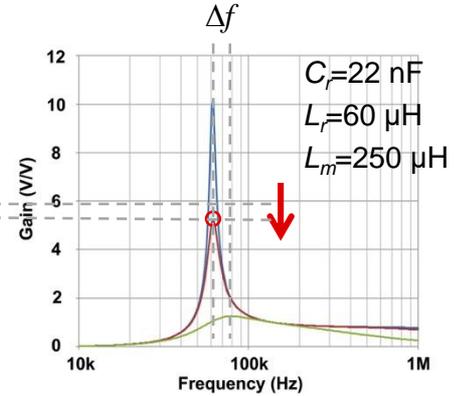- $R_e = 1 \text{ k}\Omega$
- $R_e = 500 \text{ } \Omega$
- $R_e = 100 \text{ } \Omega$



$L_r/C_r \uparrow \downarrow$

$L_m/L_r \uparrow$




LLC-SRC Design Example

Operate right on resonant frequency

- 385 V_{IN} to 48 V_{OUT}, 1 MHz operation
- Peak efficiency: 97.6%
- Weight < 210 g

Power stage

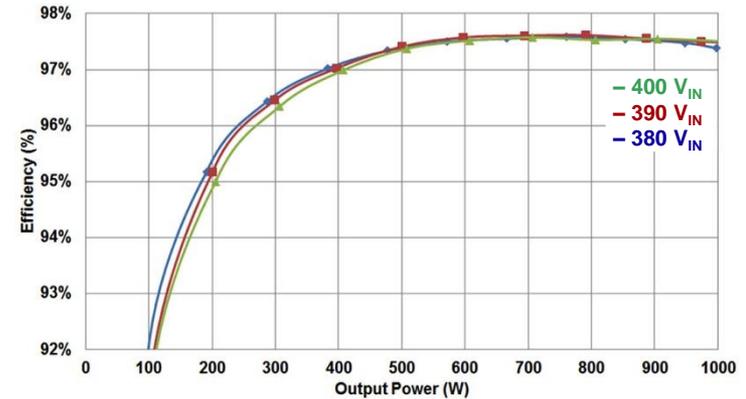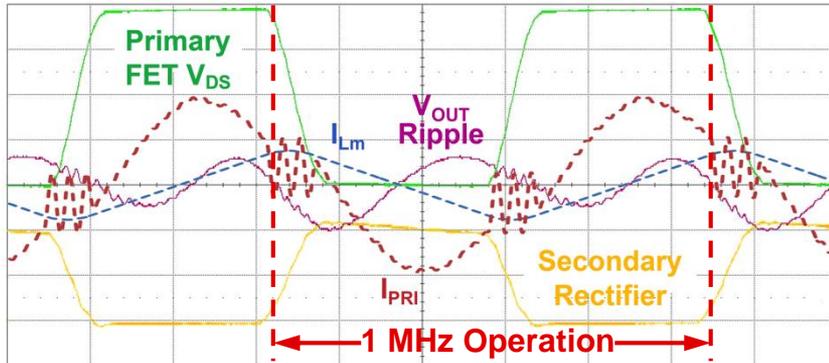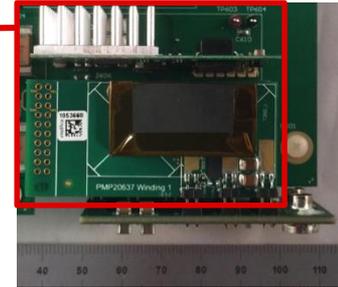55 mm(L) x
45 mm(W) x
40 mm(H)
>165 W/in³




Resonant Converters For Wide Input/Output Voltage Range

The Need for Wide Input/Output Voltage Range


- AC/DC applications without need for PFC
- Battery charger
- Lighting



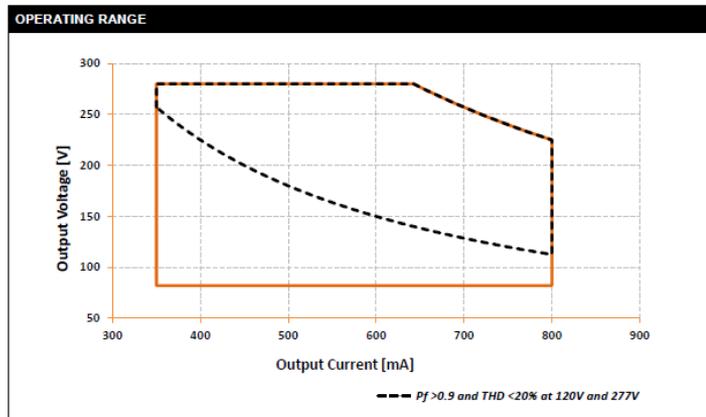Deep dimming:
down to 0.1%
load dimming
(dim to dark)




LED PSU spec

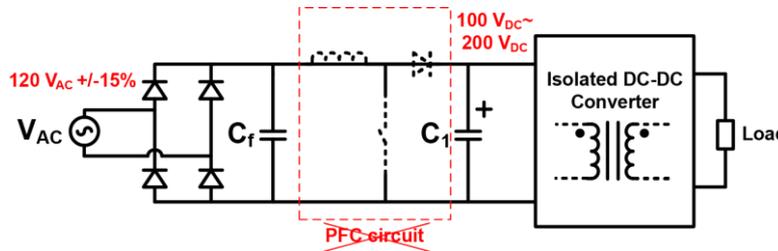

EN61000-3-2 harmonic requirements

Harmonic Order N	75 W < P < 600 W Maximum Permissible Harmonic Current (mA/W)
3	3.4
5	1.9
7	1.0
9	0.5
11	0.35
13	0.269
15 < n < 39	3.85/n

80PLUS

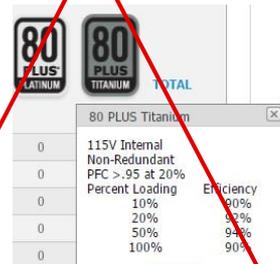


Candidates' Comparison – LLC vs LCC


Voltage gain

- LCC can achieve zero gain at high frequency

	LLC	LCC
f_{r1}	$\frac{1}{2p\sqrt{(L_r + L_m)C_r}}$	$1 / (2p\sqrt{L_r \frac{C_r C_p}{C_r + C_p}})$
f_{r2}	$\frac{1}{2p\sqrt{L_r C_r}}$	$\frac{1}{2p\sqrt{L_r C_r}}$

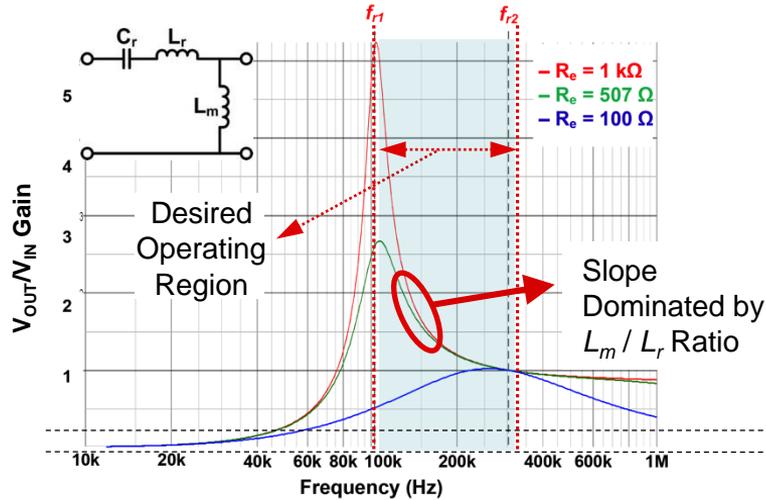

LLC Voltage Gain

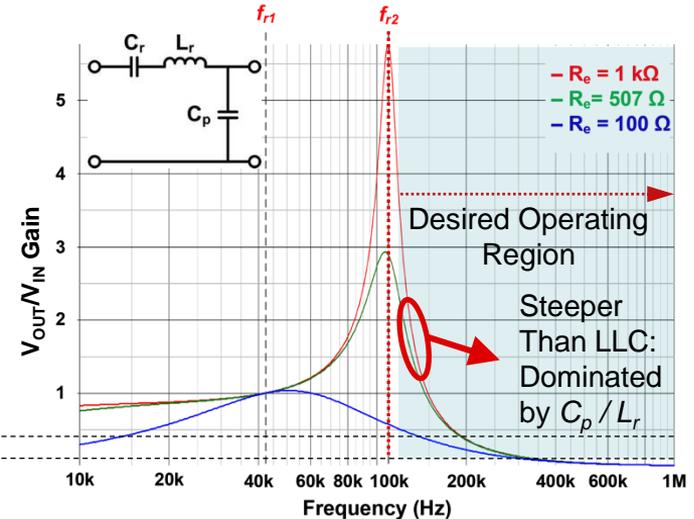



LCC Voltage Gain

Resonant Converter Designs for Lighting

- LLC resonant tank parameters: $L_r=40\ \mu\text{H}$, $L_m=300\ \mu\text{H}$, $C_r=7\ \text{nF}$
- LCC resonant tank parameters: $L_r=300\ \mu\text{H}$, $C_r=0.047\ \mu\text{F}$, $C_p=8.2\ \text{nF}$

Target spec:

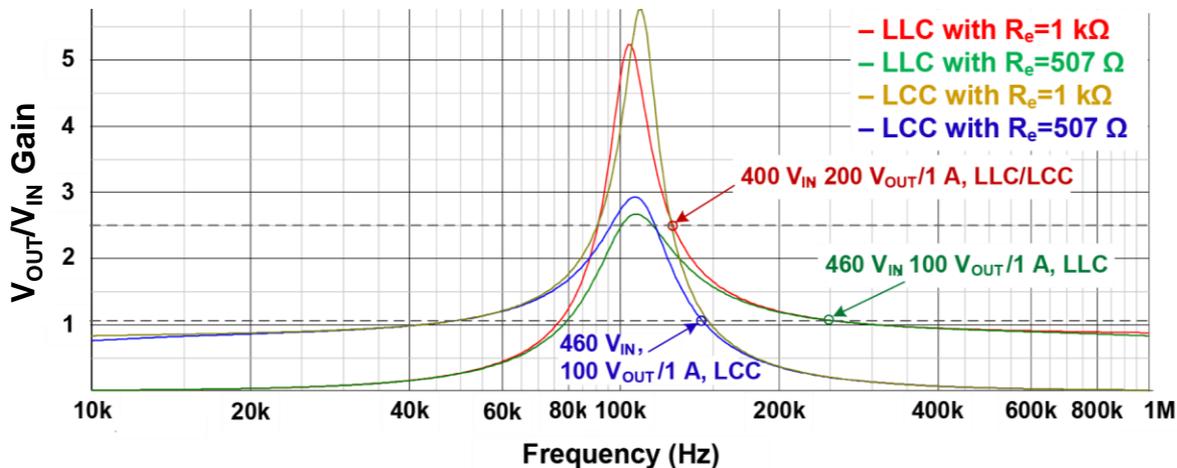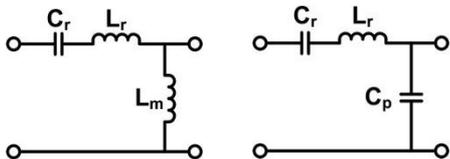
- V_{IN} range: 400-460 V
- V_{OUT} range: 100-200 V
- I_{OUT} : 1 A, $P_{\text{OUT}} = 200\ \text{W}$



Simulation Results (LLC & LCC for Lighting)


V_{IN} (V)	V_{OUT} (V)	I_{OUT} (A)	LLC I_{PRI} (A_{RMS})	LCC I_{PRI} (A_{RMS})	LLC f_{SW} (kHz)	LCC f_{SW} (kHz)	LLC $I_{C(OUT)}$ (A_{RMS})	LCC $I_{C(OUT)}$ (A_{RMS})
400	200	1	1.73	2.69	131	122	1.37	1.97
460	200	1	1.69	2.76	138	125	1.32	1.98
400	100	1	0.775	1.65	196	130	0.904	1.66
460	100	1	0.709	1.7	245	135	0.722	1.67

$$\Delta F_{LLC} > \Delta F_{LCC}$$

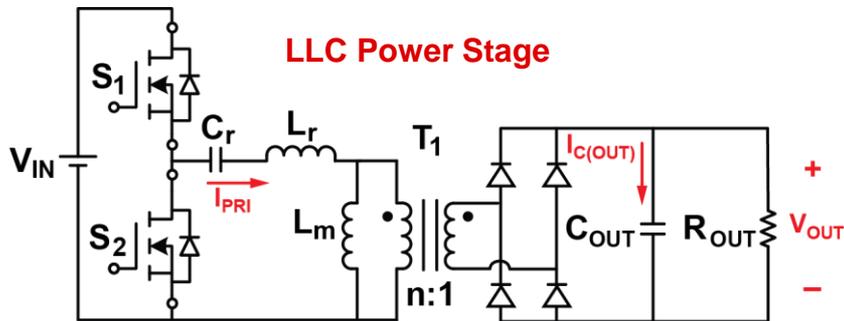

LLC has lower RMS current than LCC

- Implies better efficiency on LLC


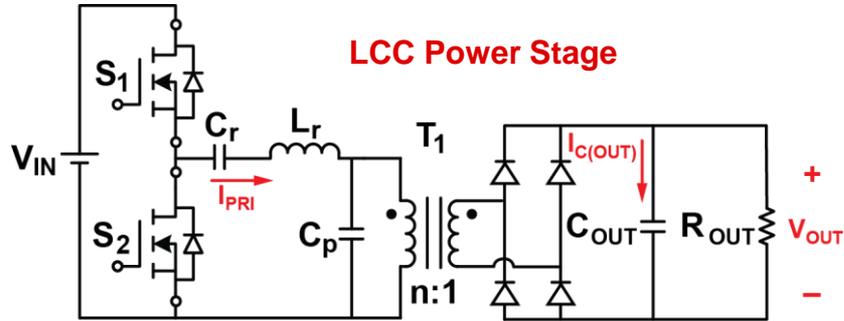


LCC has narrower frequency variation

- May not need bursting at light load


Resonant Converter Variations

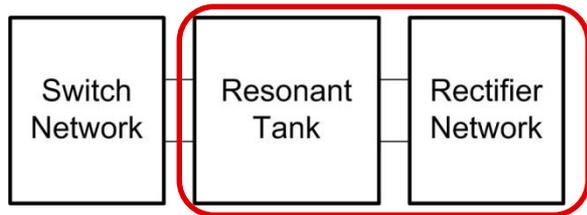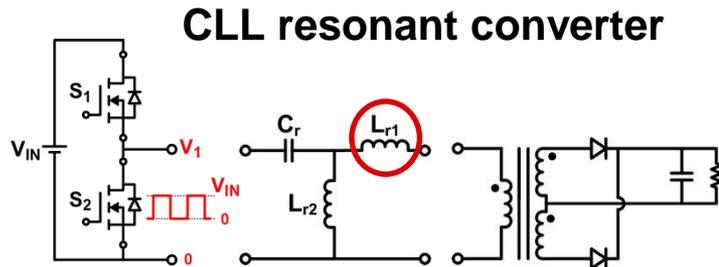Integrate Resonant Tank and Rectifier Network




Combine resonant and rectifier stage


$$L_{r1} = n^2 L_{OUT}$$

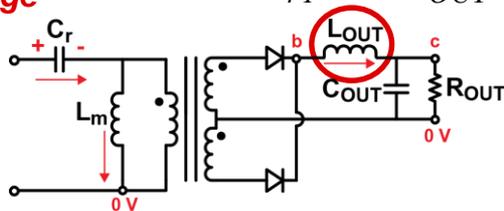

$f_{sw} < f_{r1}$

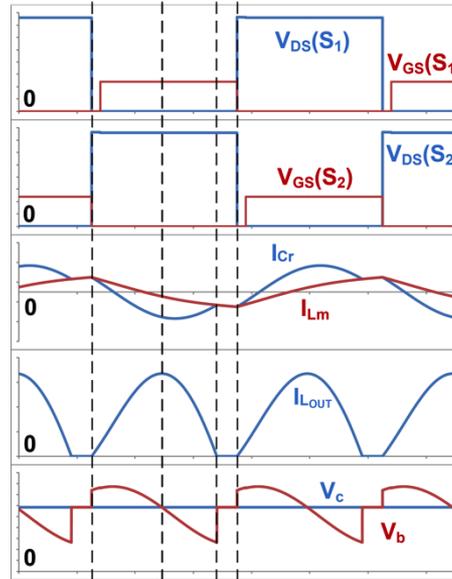

$f_{sw} > f_{r1}$

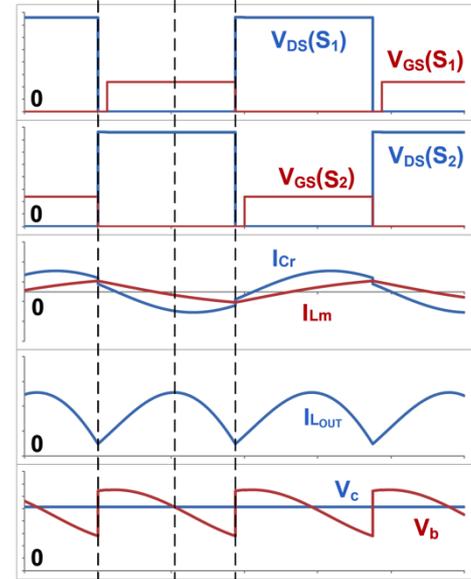


Possible size reduction and efficiency improvement!



$$f_{r1} = \frac{1}{2\pi\sqrt{C_r(L_{r1} // L_{r2})}}$$

$$f_{r2} = \frac{1}{2\pi\sqrt{C_r L_{r2}}}$$

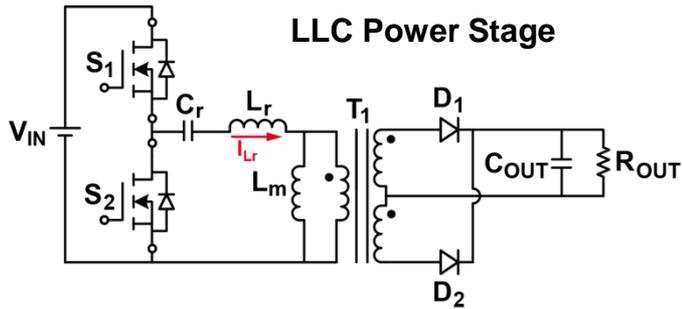LLC & CLL Resonant Inductor Loss Comparison




LLC I_{Lr} is equivalent to CLL I_{Cr} !

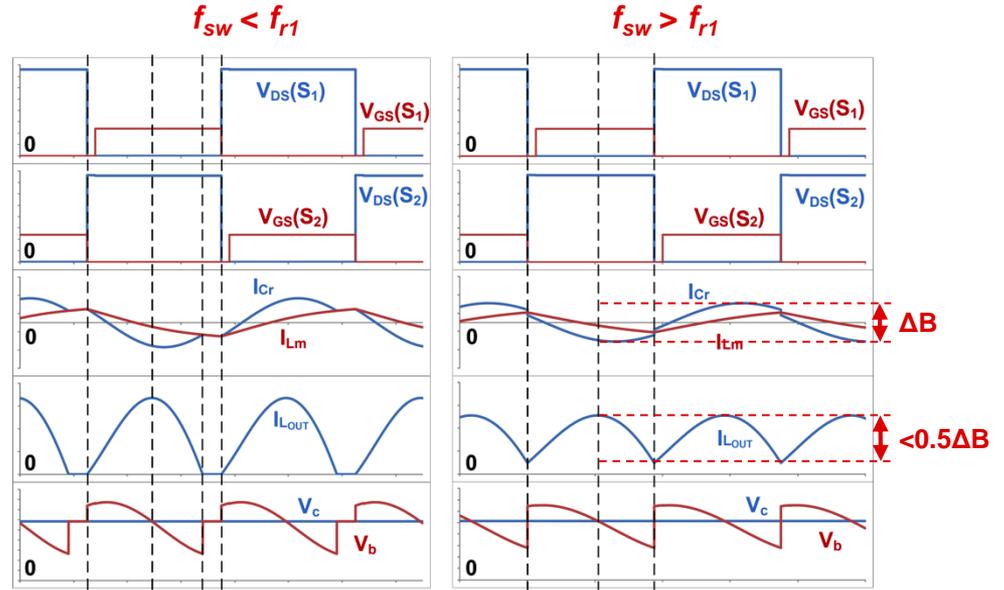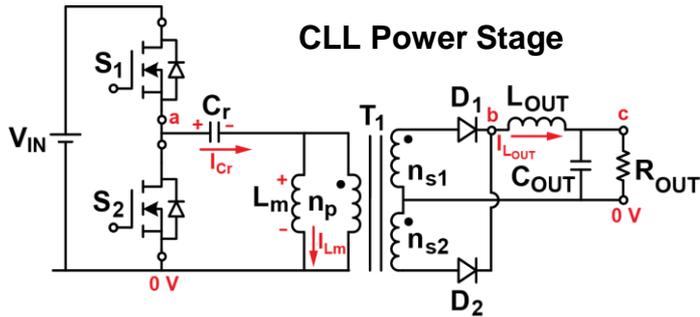


LLC L_r to CLL $L_{OUT} \Rightarrow$ less than half ΔB , frequency doubled

$$P_{CORE} = kDB^a f^b$$

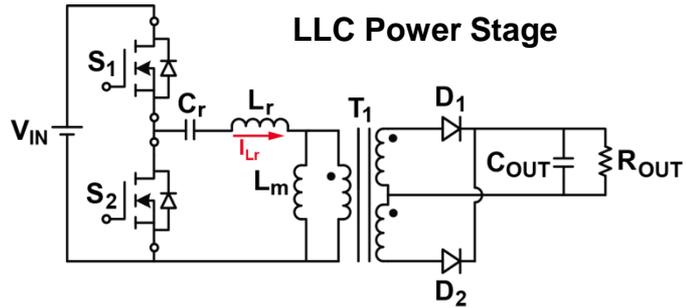
LLC & CLL Resonant Inductor Loss Comparison



FEA simulation setting and results:

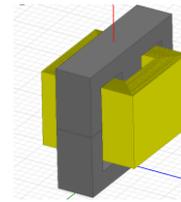

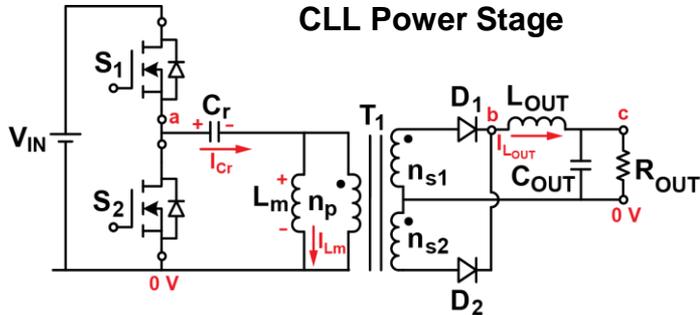
Core: EE19 (3C95)
Copper sheet —
Width: 10 mm
Thickness: 0.05 mm




	LLC	CLL
Inductance	73 μ H	1.2 μ H
Turns	24	3
Parallel winding	1	8
R_{DC}	31.5 m Ω	0.48 m Ω

	$f_{sw}=f_{r1}$	$f_{sw}>f_{r1}$	$f_{sw}<f_{r1}$
LLC L_r loss (winding/core)	0.87 W (0.4 W/0.47 W)	1.11 W (0.38 W/0.73 W)	0.69 W (0.35 W/0.34 W)
CLL L_r loss (winding/core)	0.43 W (0.12 W/0.31 W)	0.23 W (0.07 W/0.15 W)	0.53 W (0.14 W/0.39 W)


LLC & CLL Prototypes and Comparison

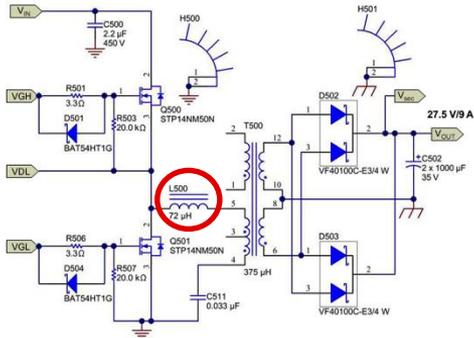

LLC-SRC


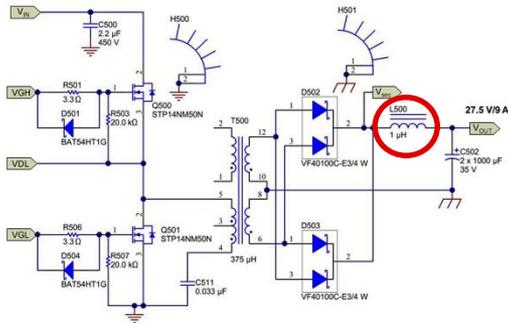


CLL

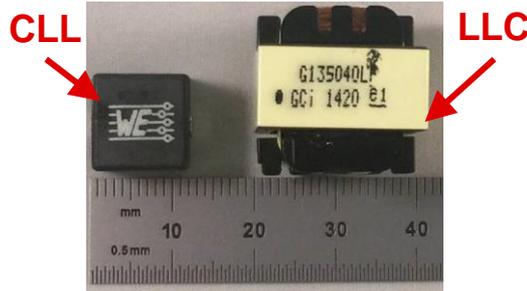

Resonant Inductors



Smaller size and 1% better efficiency!

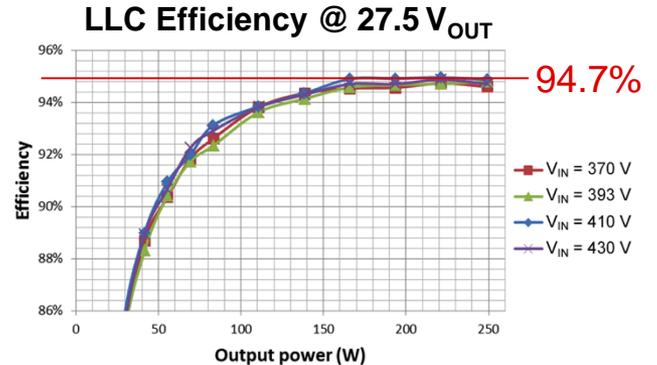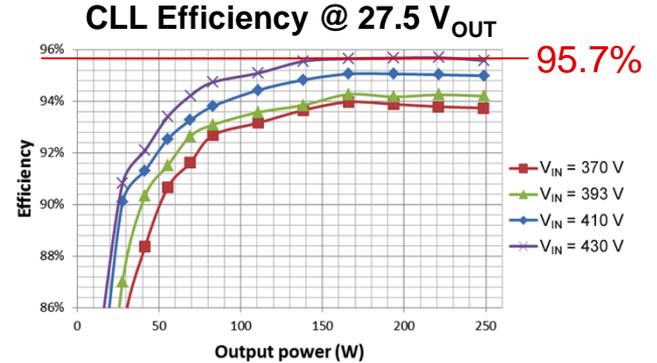

Resonant Converter Design Challenges

States of Operation

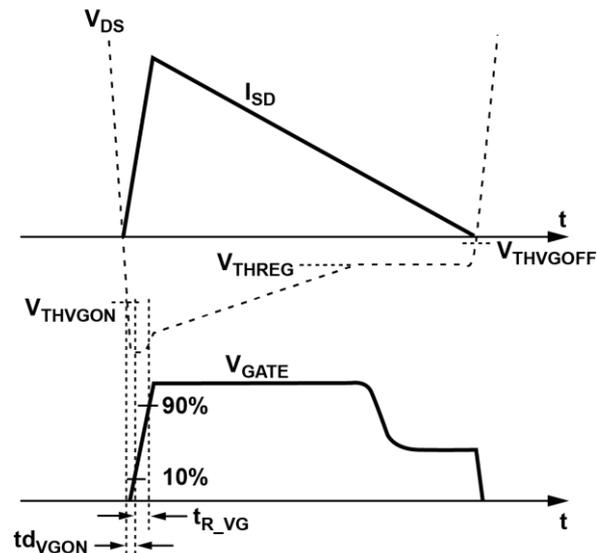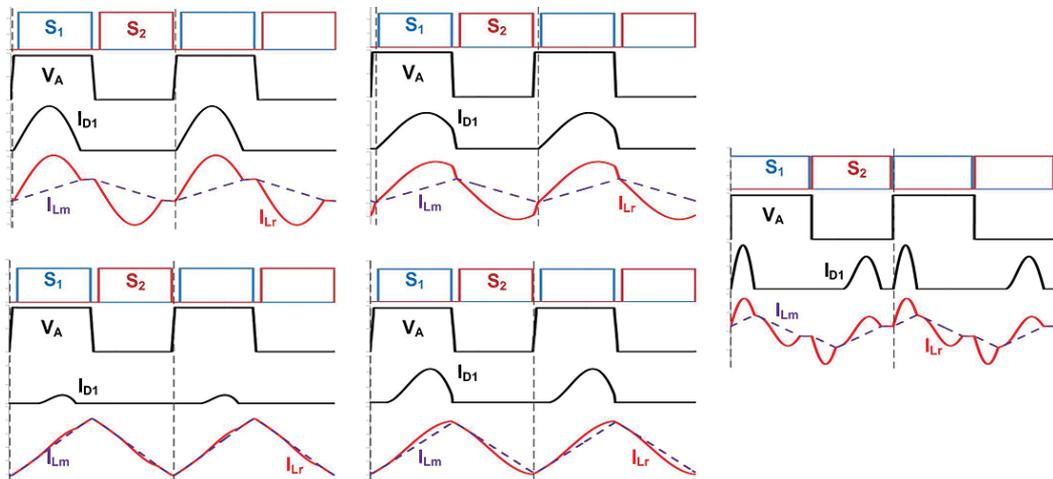- Lots of states – not just DCM and CCM in PWM converter
 - LLC-SRC: more than 5 possible states
 - Output rectifier does not always conduct current when corresponding primary switch turns off →
Can't just turn SR on when primary switch off!



V_{DS} Sensing for SR Control



Resonant Converter Transient Response

- **Variable frequency control (VFC)**

- Analogous to voltage mode control
 - Slow transient response
 - Higher order plant transfer function
 - Poor input voltage rejection

- **Hybrid hysteresis control (HHC)**

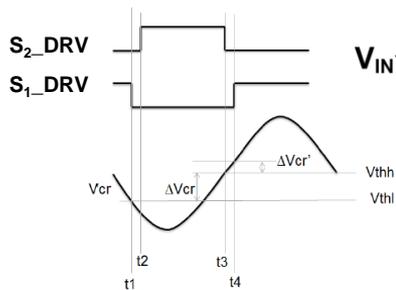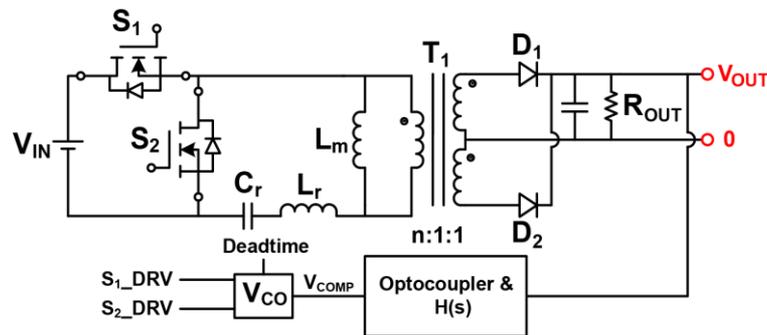
- Analogous to current mode control
 - Fast transient response
 - ~1st order plant gain
 - Inherent line rejection



$$V_{thh} = DC + V_{COMP} * 0.5$$

$$V_{thl} = DC - V_{COMP} * 0.5$$

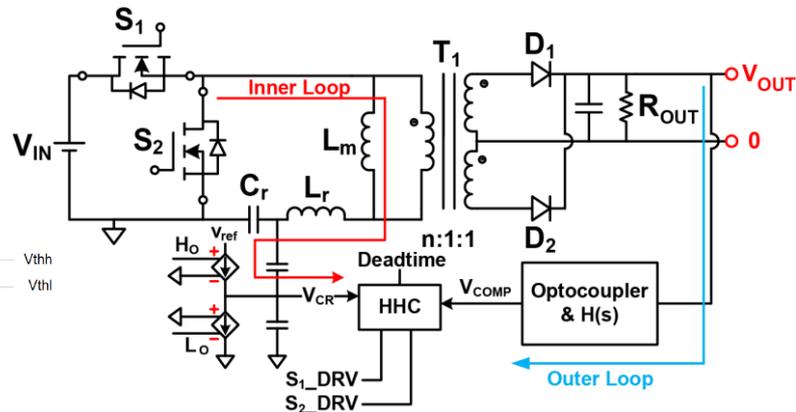
Where DC is common mode voltage reference








Transient Response Comparison: VFC vs HHC

No load to full load transient

- VFC: >20% V_{OUT} deviation

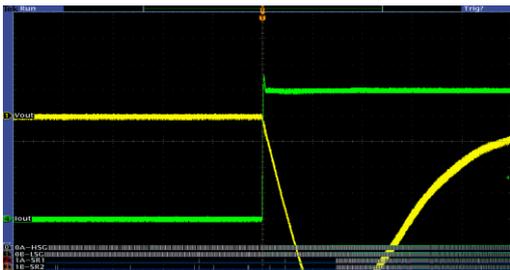

- HHC: 1.25% V_{OUT} deviation

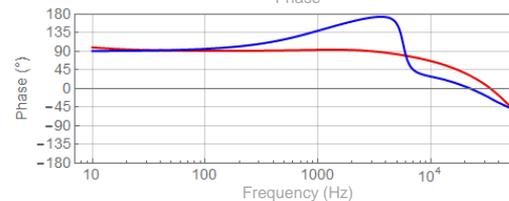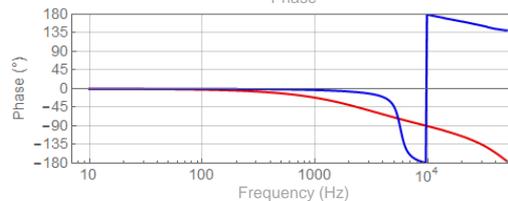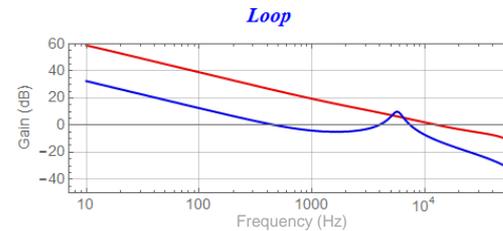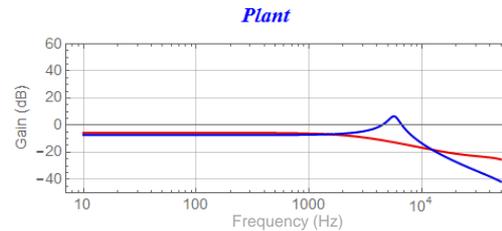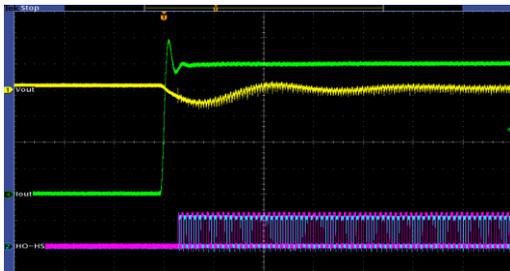


- **VFC**

- **HHC (with 25% C_{OUT} reduction)**


Effects Of Real Life Parasitics/Parameters

Non-Ideal Transformer





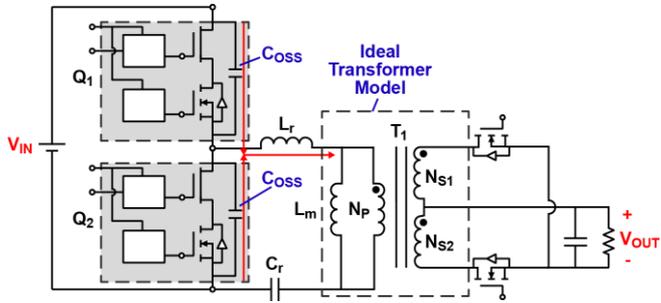
- Magnetizing inductance
- Transformer winding capacitance



Ideal Transformer




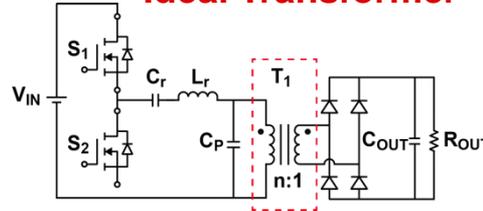


Real Transformer

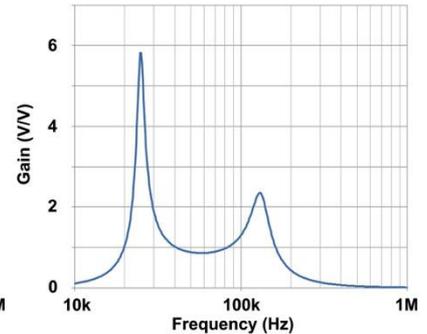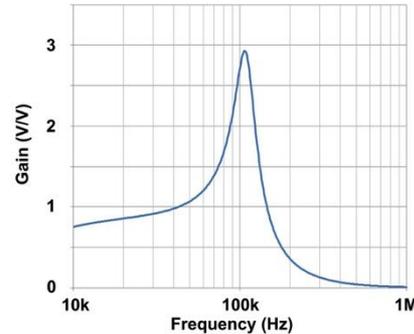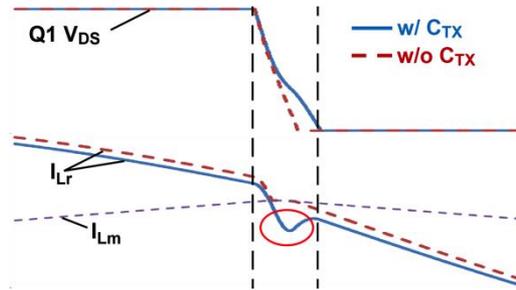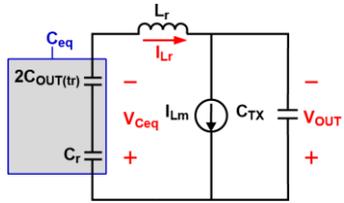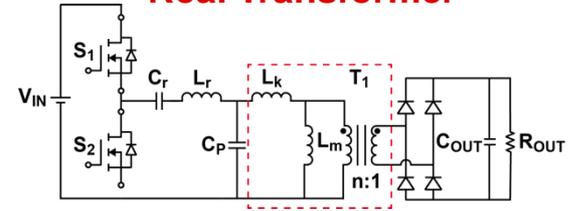

Component Parasitics

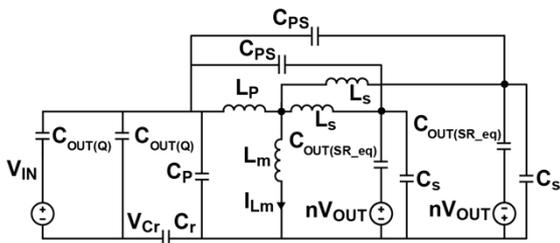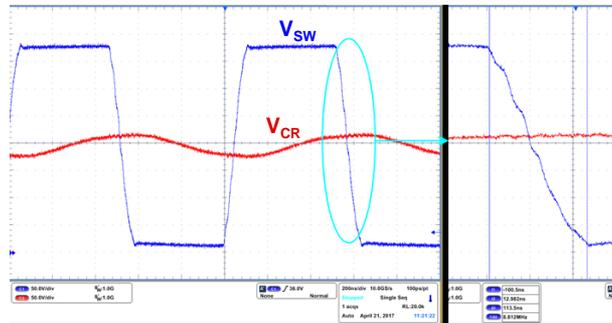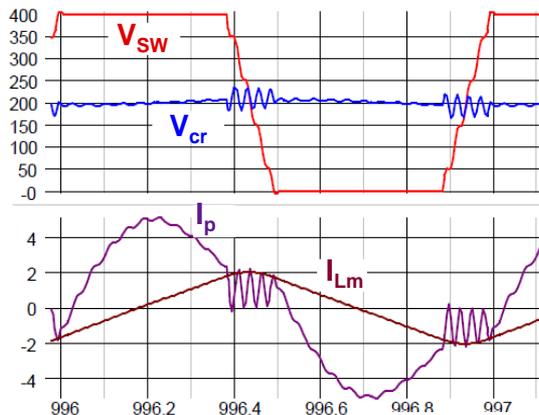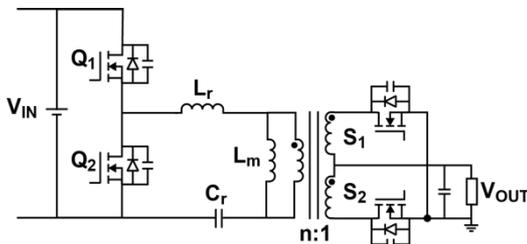- More parasitics – 1 MHz LLC as an example
 - C_{OSS} (primary FET and SR FET), winding capacitances






Deadtime Transient Model

$$C_{eq} = 2C_{ps} + \frac{1}{\frac{1}{2C_{O_SR_eq} + C_s} + \frac{1}{2C_{O_Q} + C_p}}$$

Both winding capacitance and MOSFET C_{OSS} dominate the ringing

Non-Ideal Switches

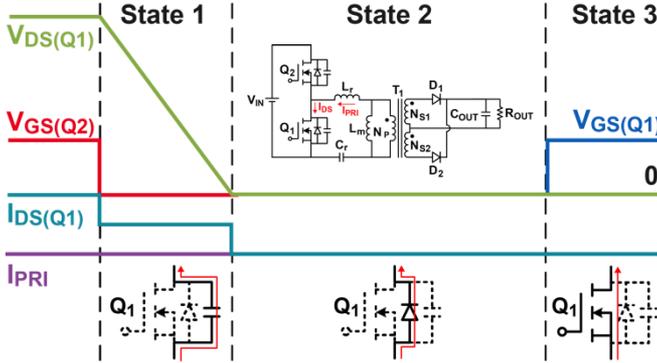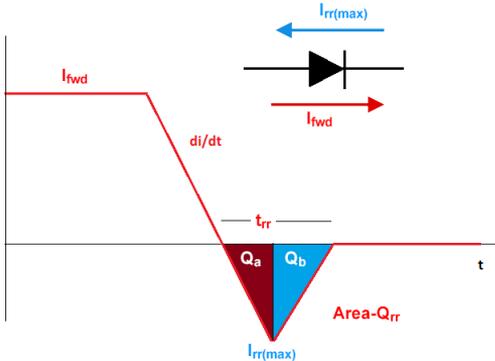
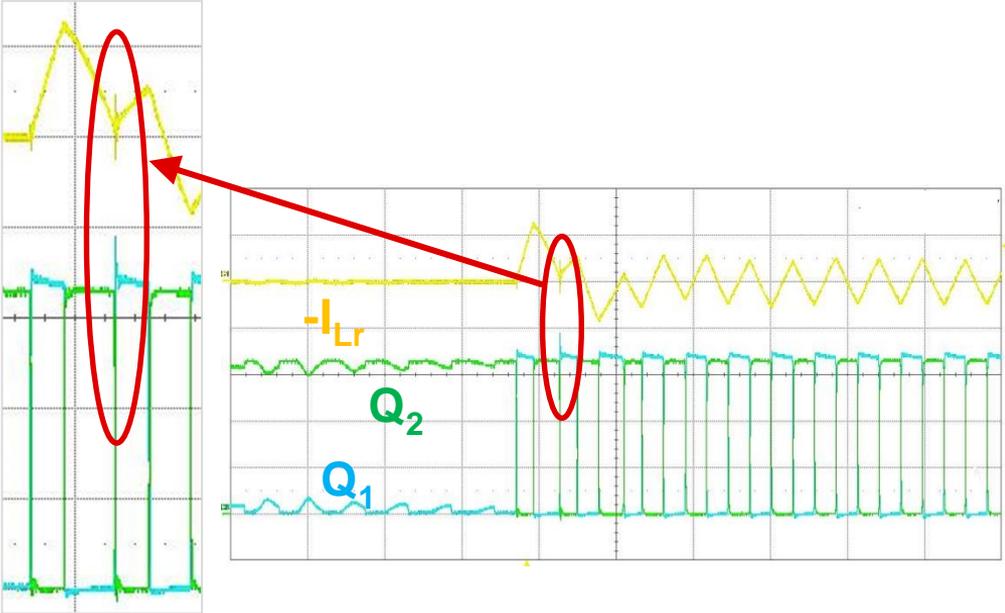
MOSFET body diode reverse recovery charge



Wide Bandgap Devices for Resonant Converter

- Benefits of wide bandgap devices (SiC & GaN)
 - Zero or minimum Q_{rr}
 - No body diode reverse recovery concern
 - Linear output capacitance
 - Minimize the duration of dead-time
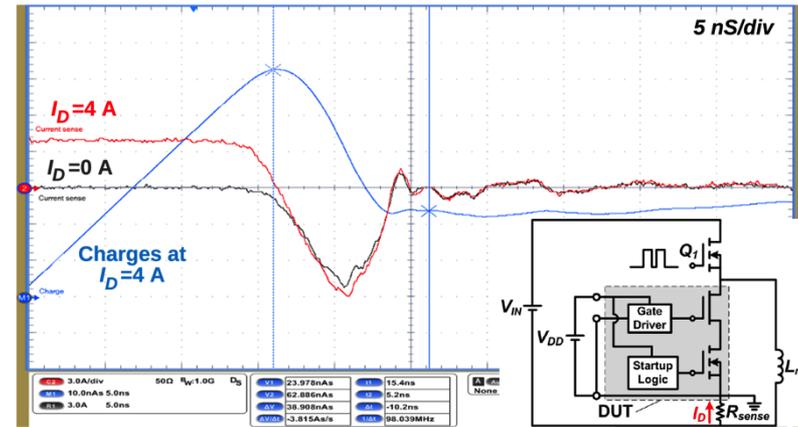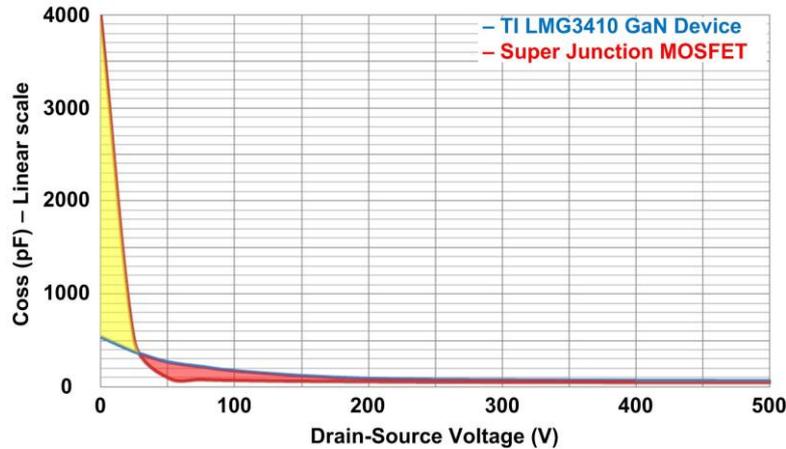
$$t_{DT} = \frac{20 \cdot V_{DS} C_{oss} (V_{DS}) V_{DS}}{I}$$








Dual-Pulse Test Results of TI LMG3410 GaN Device

Resonant Converter Selection Guide

Rule of Thumb on Resonant Converter Selection

- More resonant elements → less efficient
- More capacitors → higher gain & narrower frequency variation
- Avoid notch resonance

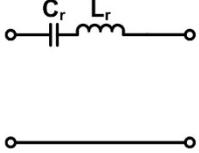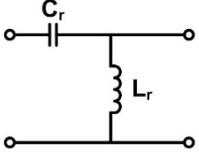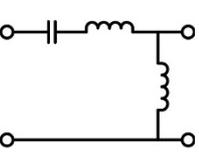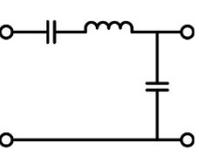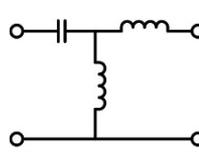	LC Series	LC Parallel	LLC	LCC	CLL
					
Frequency variation	Wide	Wide	Moderate	Narrow	Moderate
Component voltage/current stresses	Lowest	High	Low	Highest	High
ZVS(input)/ ZCS(output)	ZVS	ZVS	ZVS & ZCS	ZVS	ZVS & ZCS

Primary
Switches

Secondary
Rectifiers

Summary

- Fundamentals of resonant converter: structure and analysis method
- Soft-switching conditions of resonant converters
- Design examples and comparison of three resonant converters:
 - LLC, LCC, CLL
- Common issues and design challenges

References

- B. Yang, "Topology Investigation for Front End DC–DC Power Conversion for Distributed Power System," Ph.D dissertation, VPI&SU, Sept. 2003.
- Daocheng Huang et al, "Classification and Selection Methodology for Multi-Element Resonant Converters," 2011 IEEE APEC.
- R. Yu, G. K. Y. Ho, B. M. H. Pong, B. W. K. Ling and J. Lam, "Computer-Aided Design and Optimization of High-Efficiency LLC Series Resonant Converter," in *IEEE Transactions on Power Electronics*, vol. 27, no. 7, pp. 3243-3256, July 2012.
- High Efficiency and High Power Density 1 kW Resonant Converter Reference Design with TI HV GaN FET: <http://www.ti.com/tool/PMP20637>
- 400 VDC Input to 28 V/9 A Output Compact, High Efficiency CLL Resonant Converter Reference Design: <http://www.ti.com/tool/PMP9750>



© Copyright 2025 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2025, Texas Instruments Incorporated