

Get Smarter about 'Zero' Standby Power in Your Next Appliance Design



Yuan Tao

Some appliances, especially those plugged into AC power, continue to draw electricity even after you have ostensibly shut them down. In fact, 5-15 percent of the energy consumed by a home is from appliance standby power. Energy-saving technology helps keep standby power at a zero power level while always connected to Wi-Fi®, which will be a top trend in next-generation appliances.

International Electrotechnical Commission (IEC) 62301:2011 specifies methods of measuring electrical power consumption in standby and relevant low-power modes (off mode and network mode). These methods apply to electrical products with a voltage range that lies wholly or partly between 100V_{AC} and 250V_{AC} for single-phase products and 130V_{AC} and 480V_{AC} for other products. Clause 4.5 of IEC 62301:2011 classifies measurements of less than 5mW as zero power, which is now the basis for a zero-power marketing campaign as a target for no-load standby power dissipation in electronic devices and appliances. Products meeting this IEC requirement can earn a zero power label.

Most home appliances need a bias power supply and dual power rails for the entire system of 3.3V for the system controller and 12V for the power module. [Figure 1 shows the 15W Dual Isolated Output Bias Power Supply with 4mW Zero Standby Power Consumption Reference Design](#), which provides dual isolated outputs of 3.3V and 12V while also achieving very low power consumption in standby mode: 3mW at a 115V_{AC} input and 4.4mW at a 230V_{AC} input. This reference design is a good fit for isolated offline systems that require minimal standby power, high efficiency and fault protection.

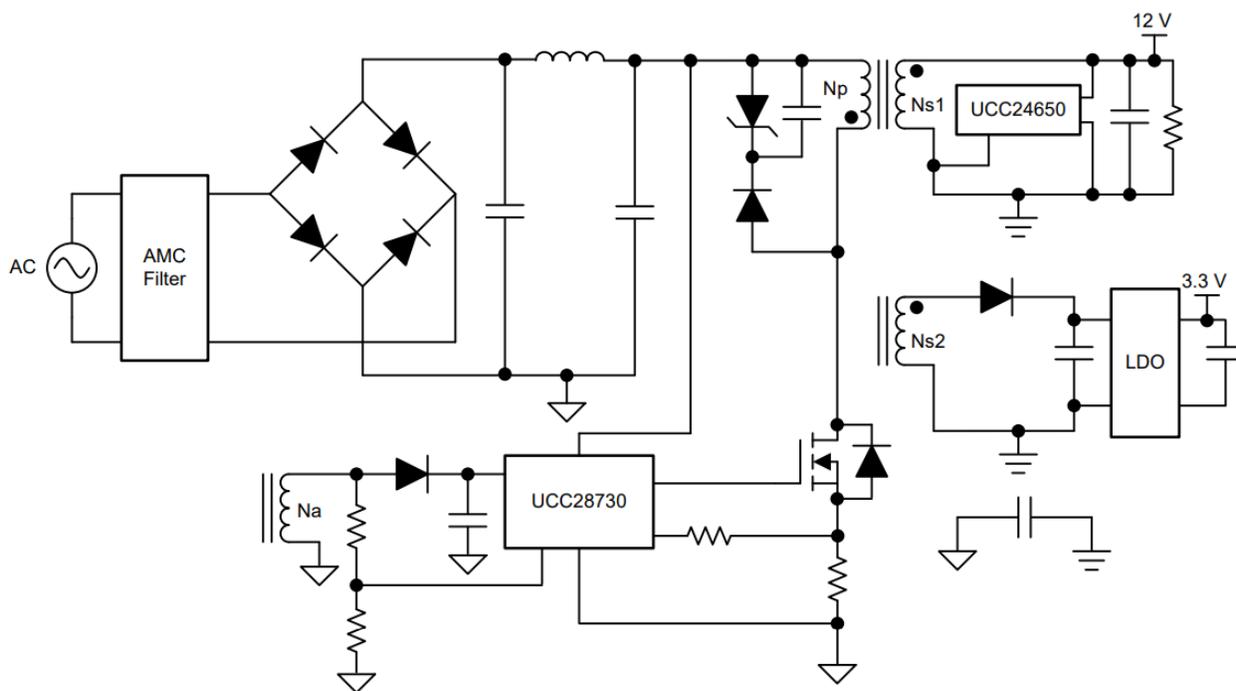


Figure 1. Block Diagram of the 15W Dual Isolated Output Bias Power Supply Reference Design

The traditional method of achieving zero power is to use a mechanical switch or relay to cut the main power path. But this method does also cut off the power to Wi-Fi or any touch keys or proximity sensors that are typically expected to wake up the system when needed. The reference design in [Figure 1](#) shows the basic power supply topology to achieve zero standby power. It keeps whatever minimal functionality and components such as the microcontroller (MCU), touch key controller, any sensors, Wi-Fi, light-emitting diode (LED) driver or any other parts required alive even during standby and allows for multiple wake-up options that way. Accordingly one could divide the system into two portions: ‘active during standby’ and ‘active during ON’.

Depending on the system configuration there are two options to design the power tree. For one of the options [Figure 2](#) shows the block diagram of a single power supply system with an extra standby path.

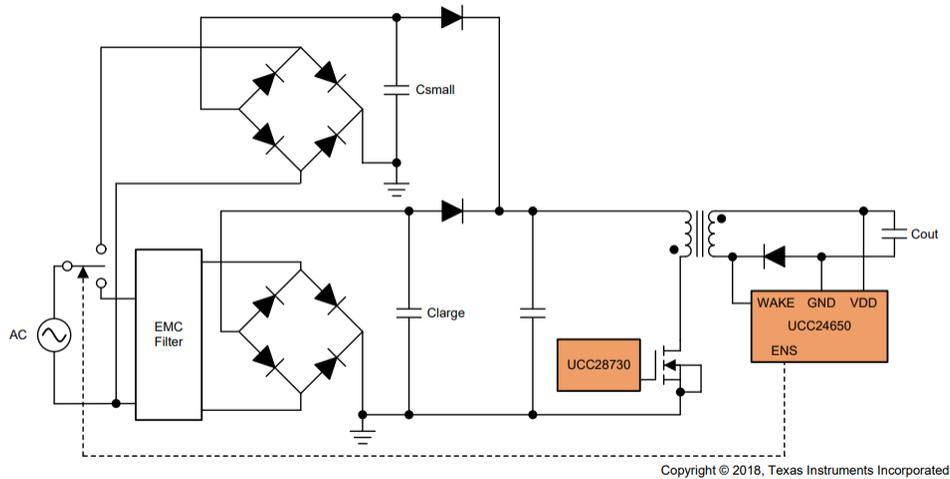


Figure 2. Block Diagram of a Single Power Supply System with Extra Standby Path

During normal operation, the system in [Figure 2](#) operates with electromagnetic interference (EMI) filter circuit and a large capacitor (C_{large}) that has a larger leakage current. In standby mode, UCC28730 flyback controller work under very low switching frequency (32Hz), the ENS pin of the UCC24650 voltage monitor switches the relay to an extra standby path, which operate with a small capacitor (C_{small}) that has much less leakage current and no EMI filter.

For major appliances with higher power capabilities [Figure 3](#) demonstrates the second option where the power tree is separated into a high power path that includes power factor correction (PFC), DC/DC converter and a DC/AC inverter and the auxiliary power supply.

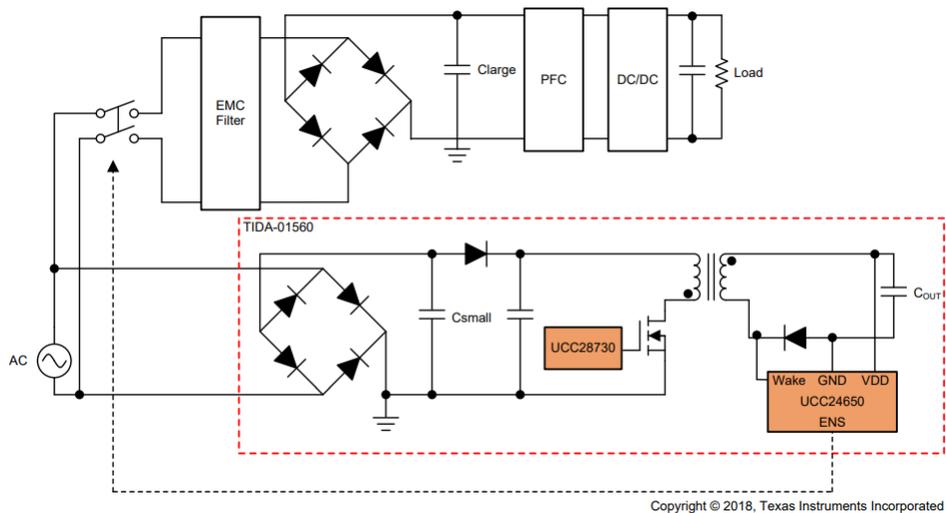


Figure 3. Block Diagram of Power Converter System with Bias Power Supply

During 'ON' mode a UCC28730 flyback controller serves as the auxiliary power supply for main power stage. During standby mode, the ENS pin of the UCC24650 shuts off the relay and disconnects the main power stage. Only the flyback converter is connected to the power line.

Wi-Fi is a key technology for the Internet of Things (IoT), and one of key features of smart appliances is remote control via a wireless connection or the cloud. Thanks to latest advancements in technology it is possible to achieve zero power standby even for systems with Wi-Fi in 'always connected' mode.

In order to verify and test this a [SimpleLink™ Wi-Fi CC3220SF wireless MCU LaunchPad™ development kit](#) is powered by the 15W dual isolated output bias power supply with 4mW zero standby power consumption reference design and configured in "always connected" low-power mode while connected to an access point. In this mode, the device can enter deep sleep mode, in which voltage levels are lowered, fast clocks are off and memories are in retention mode. To keep the connection with the access point between two sockets, a special beacon maintains contact during every long sleep interval. [Figure 4](#) shows a system that uses the reference design to power Wi-Fi. The system uses the 3.3V output and the 12V output has no load. The [IMETER-BOOST](#) evaluation module (EVM) monitors the current of the 3.3V power supply, an AC source provides V_{ACIN} and a digital power meter monitors the power consumption of the whole system. [Figure 5](#) shows the AC input power consumption.

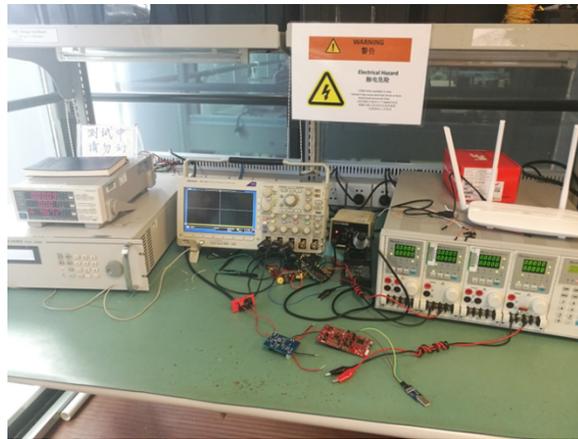


Figure 4. The System Powering Wi-Fi and Meeting Zero Standby Power

When the input voltage is $110V_{AC}$, the standby power is 3.86mW; when the input voltage is $230V_{AC}$, the standby power is 4.217mW. This system's standby power is thus below 5mW and can earn a zero power label.





Figure 5. Standby Power Test Results under 110VAC_{IN} And 230VAC_{IN}

Energy standards such as the Department of Energy Clean Energy Standard Tier 2 and Level VI Energy Efficiency are becoming more strict. These standards drive the need higher efficiency and lower standby power in appliance applications. The 15W power supply reference design demonstrates how the UCC28730 can provide ultra-low standby power without sacrificing startup time. It leaves enough margin from the 5mW power budget to enable 'zero power standby' with several wake-up options including Wi-Fi while lowering power usage over the universal input.

Additional Resources

- Learn more about TI products for your next-generation [appliance](#) designs.
- Read these blog posts:
 - [“Cut the power and complexity of your appliance designs.”](#)
 - [“How to build a cost-competitive and robust auxiliary power supply.”](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated