
Test Report: PMP21404

High-Efficiency Boost Converter Power Supply Reference Design for Automotive DC/AC Inverter

🔱 Texas Instruments

Description

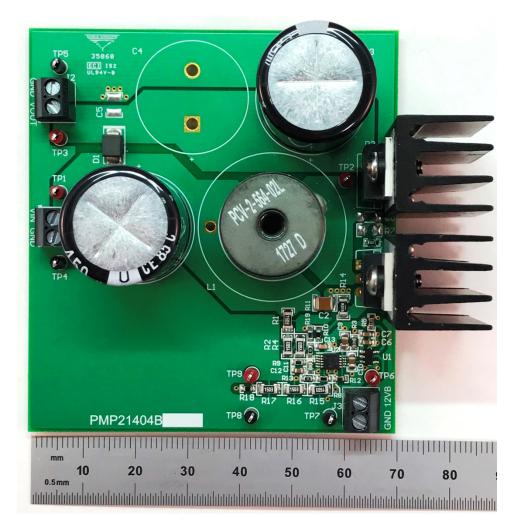This single-phase boost converter operates over an input voltage range of 120 V- 350 V and provides a nonisolated output of 221 V/0.87 A. Input voltages above 221 V are passed through to the output. With an efficiency of greater than 97%, component losses are reduced which result in lowers operating temperatures and minimal heat sink requirements.



<u>____</u>

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.



1 Test Prerequisites

1.1 Voltage and Current Requirements

PARAMETER	SPECIFICATIONS	
Input voltage range	120 V – 350 V	
Output voltage	221 V, for Vin < 221 V	
	Vin, for Vin > 221 V	
Output current	0.87 A	
Switching frequency	125 kHz	
External bias voltage	12 V	

Table 1. Voltage and Current Requirements

1.2 Required Equipment


- Power supply capable of 400 V and 3 A
- 12 V / 0.1 A bias power supply
- 250 Ohm/200 W resistive or 400 V/1 A active load
- Digital Multimeters
- 500 MHz oscilloscope and probes
- Stability measurement device (Venable or Bode)



2 Testing and Results

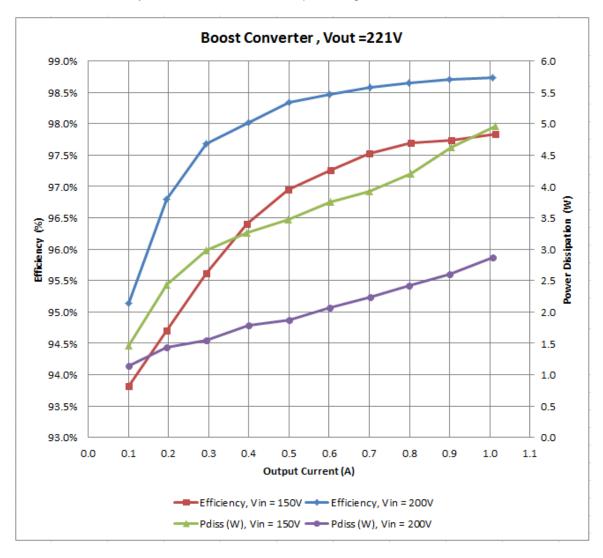2.1 Efficiency and Regulation Graphs


The boost converter efficiency is shown below with the input voltage set to 150 V and 200 V.





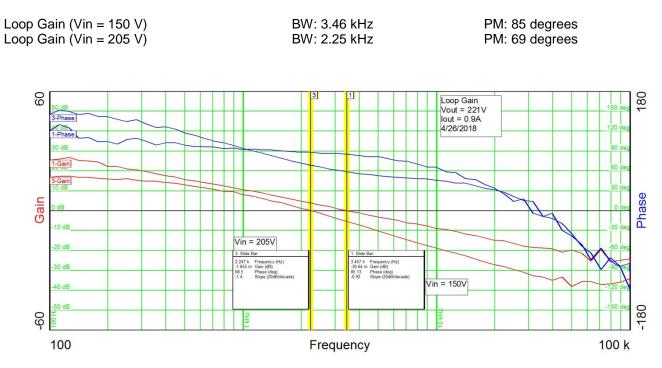
2.2 SEPIC Loop Gain

The plot below shows the boost converters loop gain with the input voltage set to 150 V and 205 V while loaded at 0.9 A.



The plot below shows the boost converters loop gain with the input voltage set to 150 V and 205 V while loaded at 0.18 A.


Loop Gain (Vin = 150 V)	BW: 392 Hz	PM: 91 degrees
Loop Gain (Vin = 205 V)	BW: 416 Hz	PM: 102 degrees

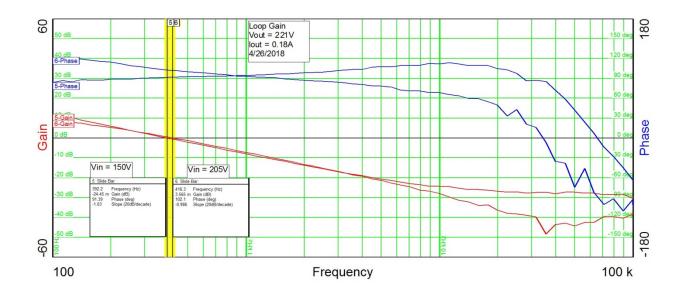



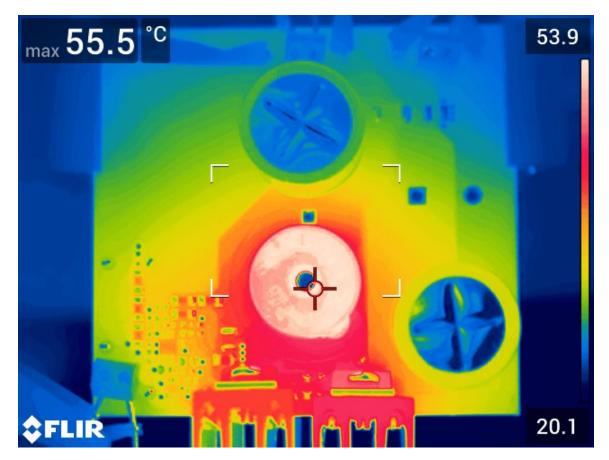2.3 Thermal Image

A thermal image is shown below with the boost converter operating at 150 V input and 221 V/0.9 A output (room temp, no airflow).







3 Waveforms

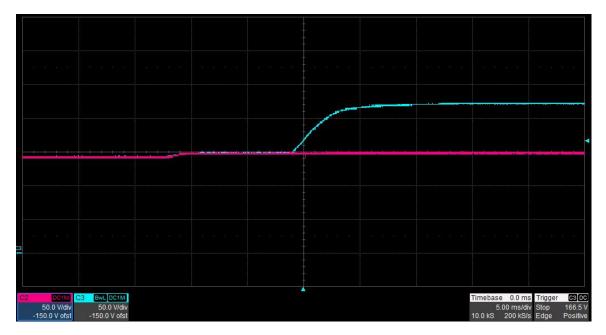3.1 Startup

The photo below shows the startup of the 221 V output voltage (Blue) after the input voltage (RED) crosses the UVLO threshold of 142 V. lout = 0 A. (50 V/DIV, 5 mS/DIV)



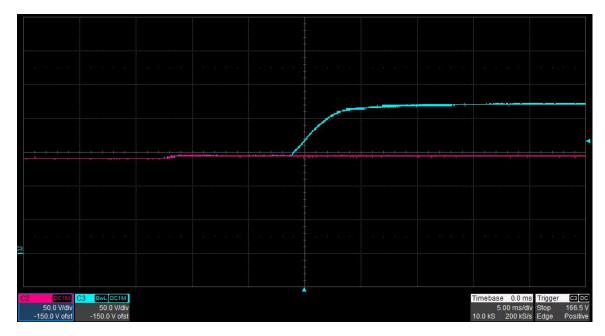
The photo below shows the startup of the 221 V output voltage (Blue) after the input voltage (RED) crosses the UVLO threshold of 142 V. lout = 0.9 A. (50 V/DIV, 5 mS/DIV)






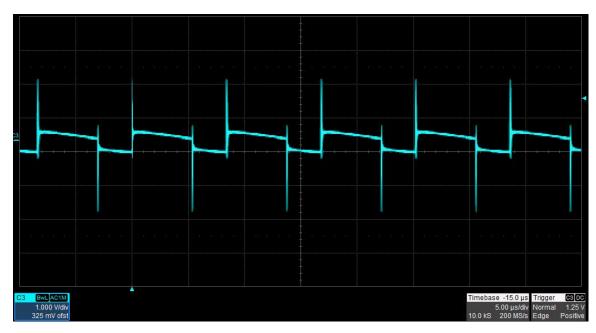3.2 Output Ripple Voltage

The output ripple voltage (AC coupled) is shown in the figure below. BWL = 20 MHz, Vin = 142 V, Vout = 221 V, Iout = 0.9 A (1 V/DIV, 5 uS/DIV)



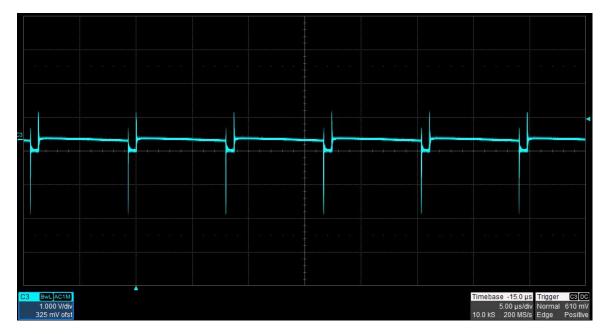
The output ripple voltage (AC coupled) is shown in the figure below. BWL = 20 MHz, Vin = 205 V, Vout = 221 V, Iout = 0.9 A (1 V/DIV, 5 uS/DIV)





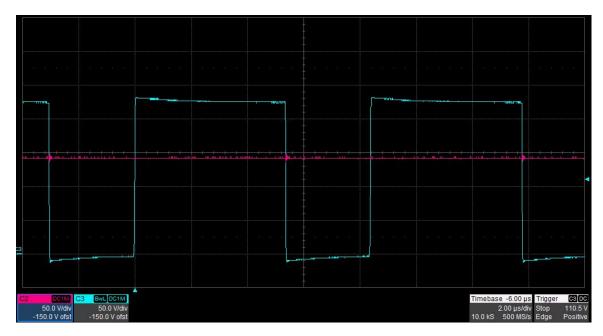3.3 Switch Node Waveforms

The photo below shows the FET switching voltage at TP2 and the input voltage. Vin = 142 V, Vout = 221 V, Iout = 0.9 A. (50 V/DIV, 2 uS/DIV)




The photo below shows the FET switching voltage at TP2 and the input voltage. Vin = 142 V, Vout = 221 V, Iout = 0.019 A. (50 V/DIV, 2 uS/DIV)






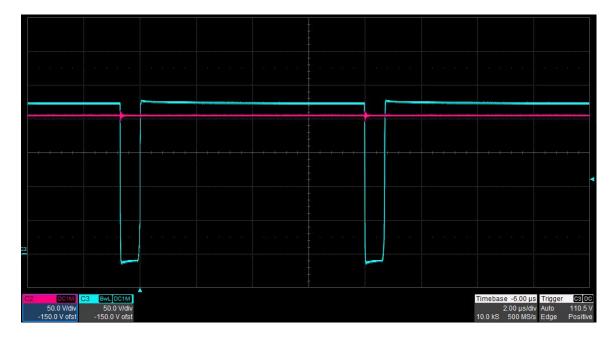The photo below shows the FET switching voltage at TP2 and the input voltage. Vin = 205 V, Vout = 221 V, Iout = 0.9 A. (50 V/DIV, 2 uS/DIV)



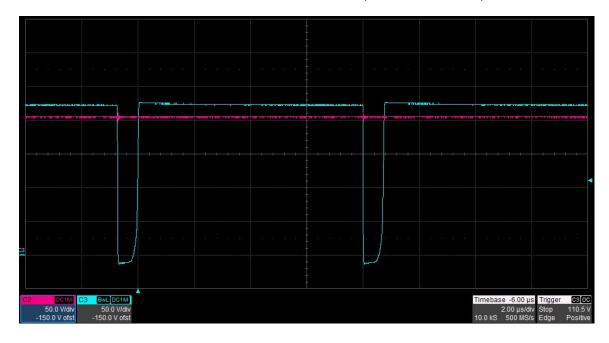
The photo below shows the FET switching voltage at TP2 and the input voltage. Vin = 205 V, Vout = 221 V, lout = 0.18 A. (50 V/DIV, 2 uS/DIV)






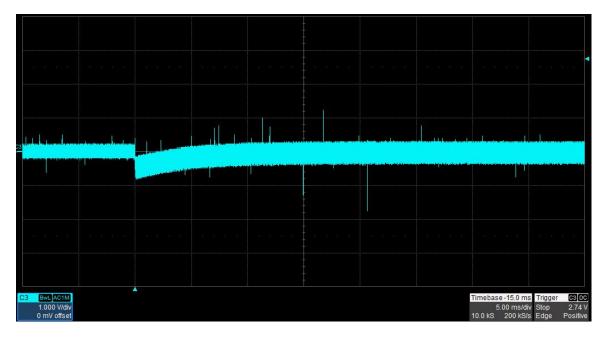3.4 Load Transient

The photo below shows the 221 V output voltage (ac coupled) when the load current is stepped from 0.45 A to 0.9 A. Vin = 150 V. (1 V/DIV, 5 mS/DIV)



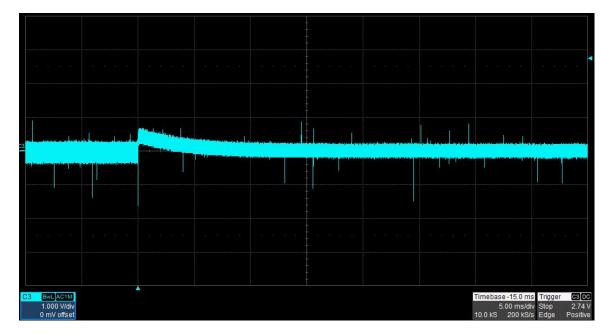The photo below shows the 221 V output voltage (ac coupled) when the load current is stepped from 0.9 A to 0.45 A. Vin = 150 V. (1 V/DIV, 5 mS/DIV)



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (https://www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated