

Test Data For PMP10737 08/17/2015

TEXAS INSTRUMENTS



Contents

1.	Design Specifications	. 3
2.	Circuit Description and PCB details	.3
3.	PMP10737 Board Photos and Schematic	.4
4.	Thermal Data	.6
5.	Waveforms	.7



1. Design Specifications


Vin Minimum	7VDC
Vin Maximum	35 VDC(OVP at 25V)
Vout1	12V
lout 1	1A
Vout2	12V
lout 2	5A
Protection	Input Overvoltage and Reverse Polarity

2. Circuit Description and PCB details

PMP10737 is a reference design that provides protection from reverse voltage (Smart Diode) and overvoltage using discrete components.


Input voltage range is between 7V to 35V with OVP at 25V.

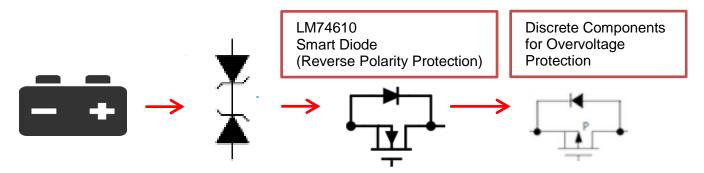LM74610 is used for Battery reverse protection which utilizes a charge pump to drive an N-channel FET to provide a resistive path for the bypass current to flow.



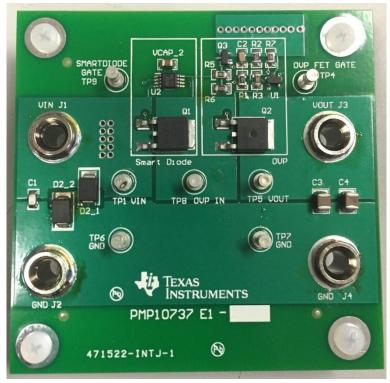
The Board dimension of PMP10737 PCB is 2735mil * 2700mil. Two layer PCB was used for the design.





3. PMP10737 Board Photos and Schematic


Board Photo (Top)

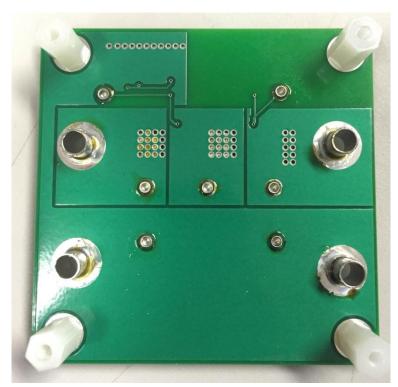

Board Photo (Bottom)




Test Report PMP10737

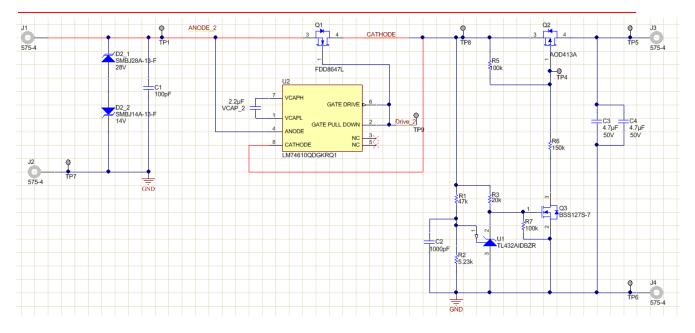


NOTE: TVS diodes are placed in both directions to protect the circuitry from high voltage transients.



4. Thermal Data

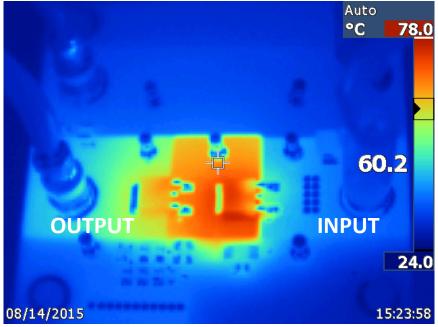

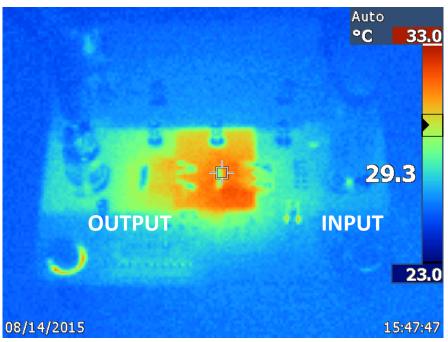
IR thermal image taken at steady state with 12Vin and 5A load current.



IR thermal image taken at steady state with 12Vin and 1A load current.




5. Waveforms

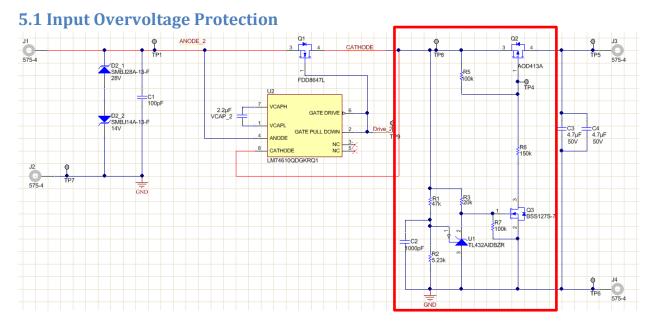


Discrete components are used for overvoltage protection. When the shunt regulator (U1) senses a voltage higher than 2.5V at R2, its output will go low which stops driving the N-channel FET (Q3). Q3 then acts as an open which ties the gate and source of the P-channel FET (Q2) together. The gate will not be driven which then prevents an output voltage. A timing capacitor (C2) is placed in parallel with R2 to prevent the circuit from outputting OV when there are quick high voltage surges.

Test Report PMP10737



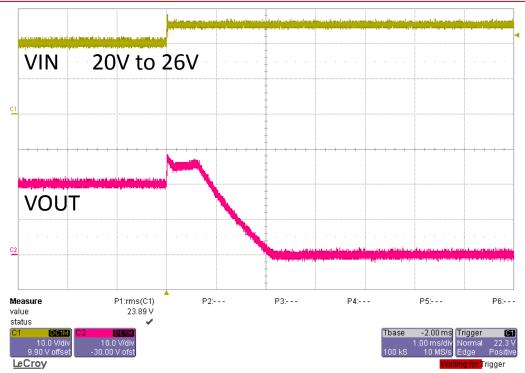


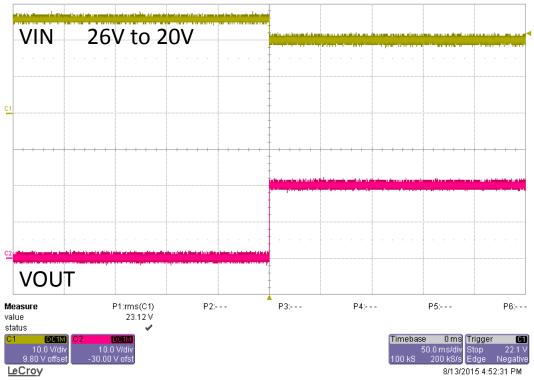Transition to overvoltage condition. Protection at 25V.




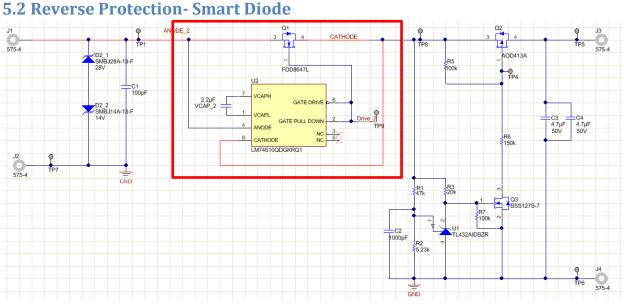Transition from overvoltage to normal condition






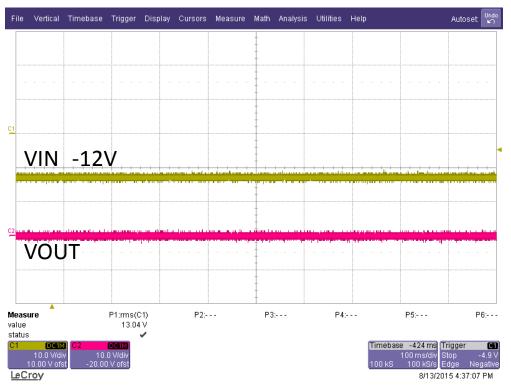
The LM74610 Smart Diode is placed before the overvoltage protection for reverse battery protection. For more information on the LM74610 functional and electrical characteristics, see the LM74610 Smart Diode Controller data sheet (<u>LM74610</u>).



Continuous Reverse Voltage at Input

 



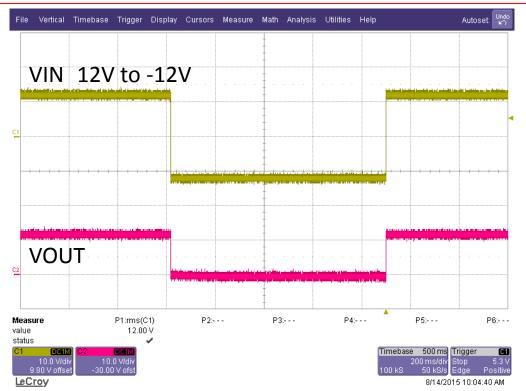

Transition to Reverse Voltage at Input

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (https://www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated