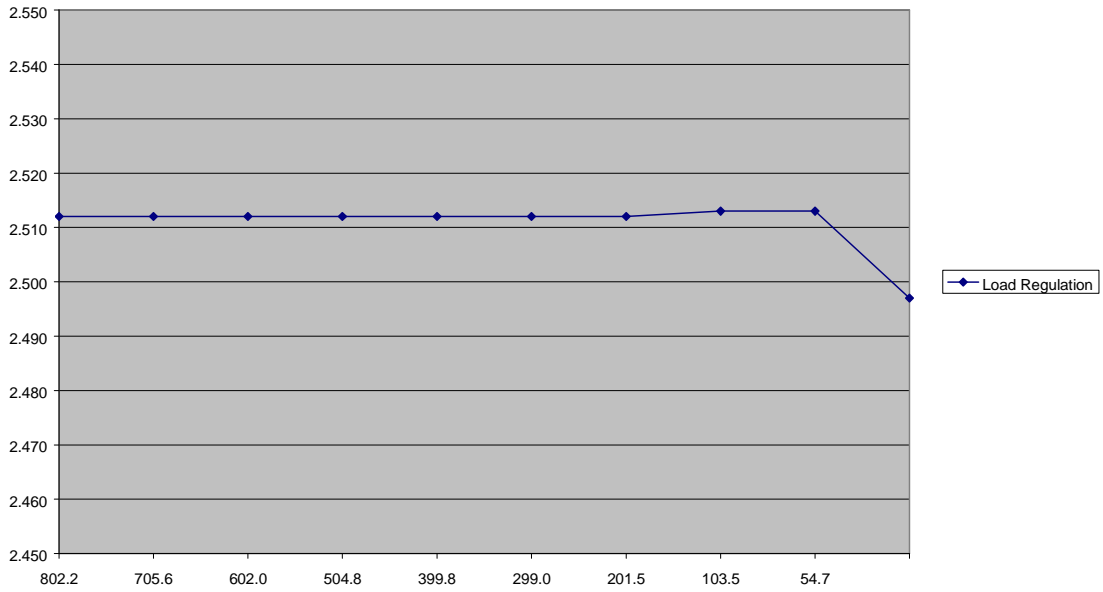



## 1 Load Regulation

The load regulation of the output is shown in the graphs below, for the two different nominal input voltages.

### Load Regulation for Vin=12V




### Load Regulation for Vin=5V

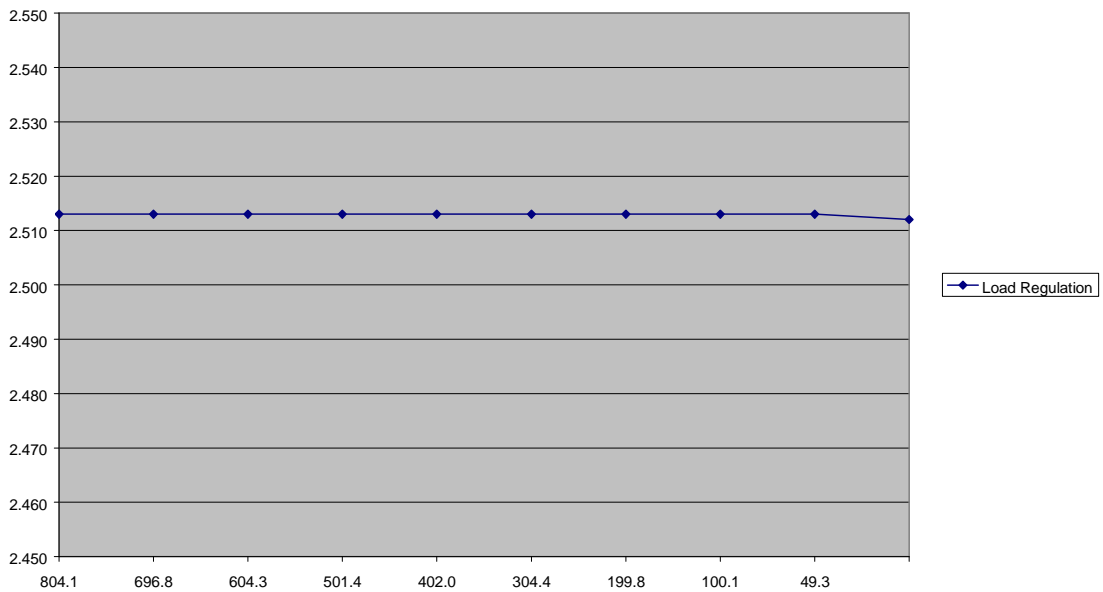
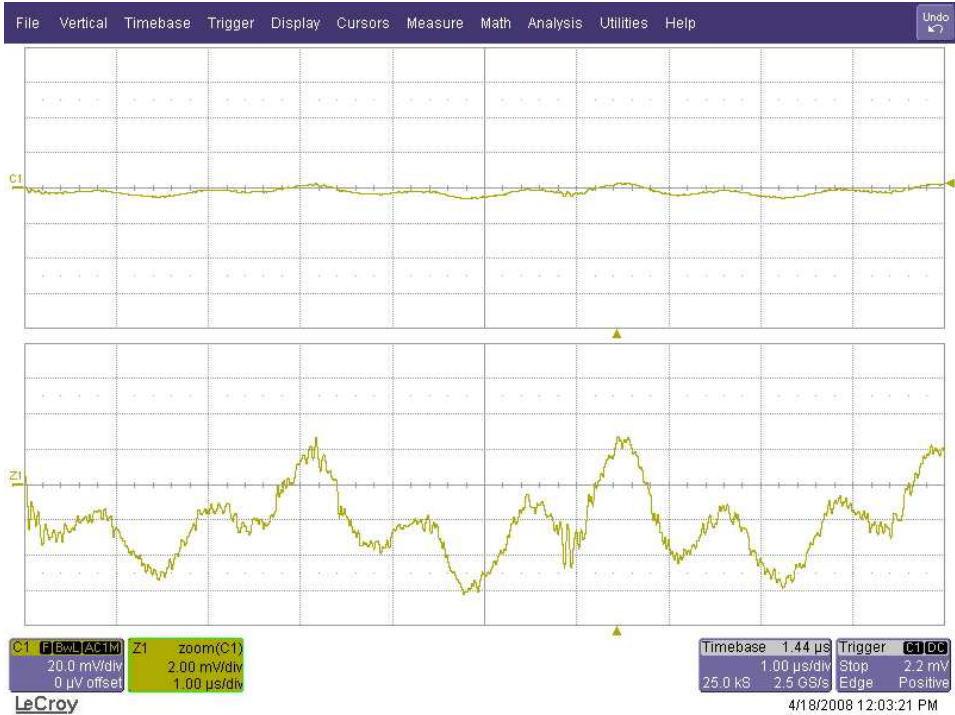
## 2 Output Ripple Voltage

The output ripple voltages are shown in the figures below, for the two different nominal input voltages.



12V Input, 0.8A Output



5V Input, 0.8A Output

## 3 Switch Node Waveform

The figures below show the voltage on diode D1, for the two different nominal input voltages. The converter is switching at 300kHz.



12V Input, 0.8A Output




5V Input, 0.8A Output
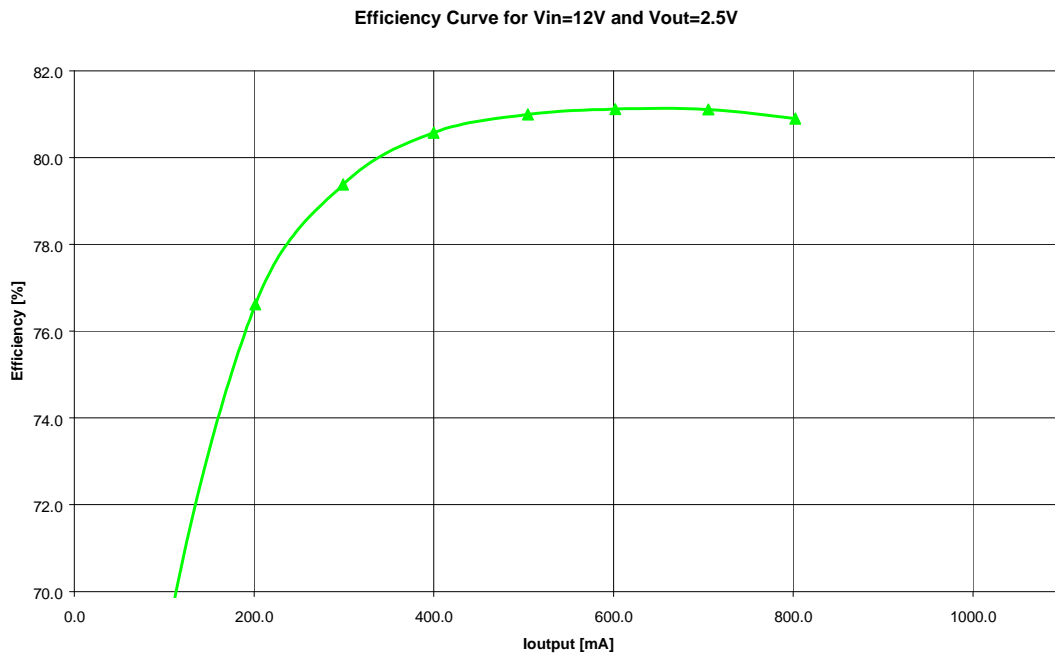
## 4 Efficiency

The efficiency diagrams are shown in the figures below for the two different nominal input voltages.


**NOTE:** *the measured values are related to the assembly situation on the board, where diode D1 is MBR340TR (3A) due to the unavailability of the selected diode MBR540TE (5A) during laboratory tests . Therefore, an efficiency improvement of some percentage point is expected with the selected diode, especially at 5V input, for reduced conduction losses.*



The following table shows the measured values for **12V input**:

Vin[V]	Iin[mA]	Vout[V]	Iout[mA]	Pin[W]	Pout[W]	$\eta$ /%
<b>12.08</b>	206.2	<b>2.512</b>	802.2	2.491	2.015	<b>80.9</b>
<b>12.08</b>	180.9	<b>2.512</b>	705.6	2.185	1.772	<b>81.1</b>
<b>12.09</b>	154.2	<b>2.512</b>	602.0	1.864	1.512	<b>81.1</b>
<b>12.09</b>	129.5	<b>2.512</b>	504.8	1.566	1.268	<b>81.0</b>
<b>12.09</b>	103.1	<b>2.512</b>	399.8	1.246	1.004	<b>80.6</b>
<b>12.10</b>	78.2	<b>2.512</b>	299.0	0.946	0.751	<b>79.4</b>
<b>12.10</b>	54.6	<b>2.512</b>	201.5	0.661	0.506	<b>76.6</b>
<b>12.10</b>	31.2	<b>2.513</b>	103.5	0.378	0.260	<b>68.9</b>
<b>12.11</b>	19.3	<b>2.513</b>	54.7	0.234	0.137	<b>58.8</b>
<b>12.11</b>	3.6	<b>2.497</b>	0.0	0.044	0.000	<b>0.0</b>

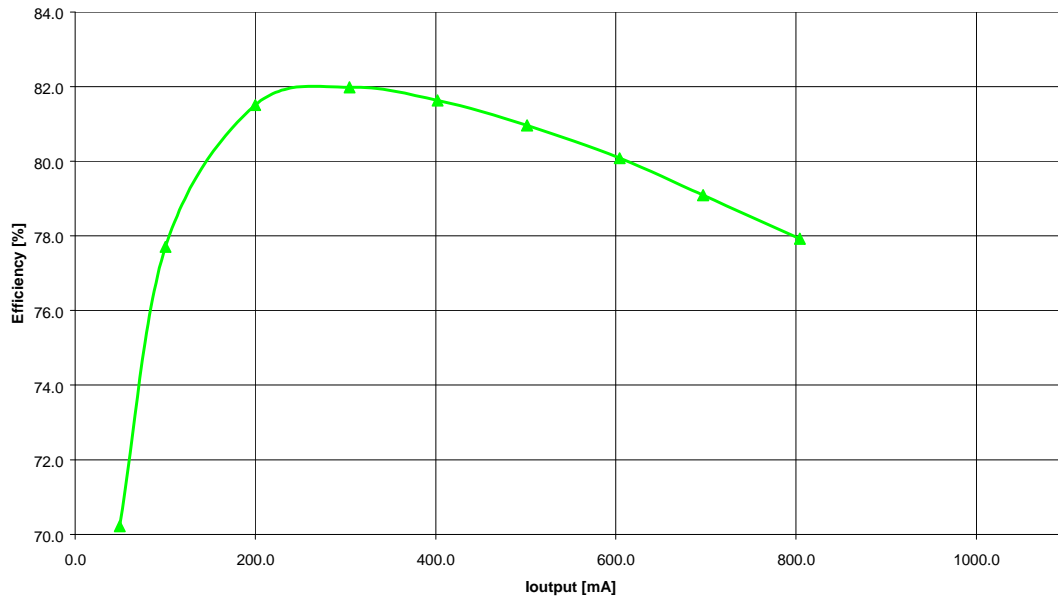Efficiency Curve for Vin=5V and Vout=2.5V




The following table shows the measured values for **5V Input**:


Vin[V]	Iin[mA]	Vout[V]	Iout[mA]	Pin[W]	Pout[W]	$\eta$ %
<b>5.01</b>	517.3	<b>2.513</b>	804.1	2.593	2.021	<b>77.9</b>
<b>5.02</b>	441.3	<b>2.513</b>	696.8	2.214	1.751	<b>79.1</b>
<b>5.02</b>	377.6	<b>2.513</b>	604.3	1.896	1.519	<b>80.1</b>
<b>5.03</b>	309.3	<b>2.513</b>	501.4	1.556	1.260	<b>81.0</b>
<b>5.04</b>	245.5	<b>2.513</b>	402.0	1.238	1.010	<b>81.6</b>
<b>5.05</b>	184.8	<b>2.513</b>	304.4	0.933	0.765	<b>82.0</b>
<b>5.06</b>	121.8	<b>2.513</b>	199.8	0.616	0.502	<b>81.5</b>
<b>5.07</b>	63.9	<b>2.513</b>	100.1	0.324	0.252	<b>77.7</b>
<b>5.07</b>	34.8	<b>2.513</b>	49.3	0.176	0.124	<b>70.2</b>
<b>5.07</b>	6.4	<b>2.512</b>	0.0	0.032	0.000	<b>0.0</b>
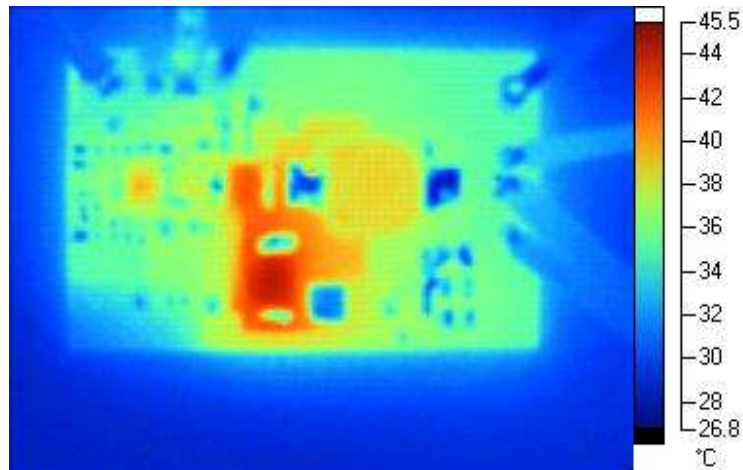
## 5 Thermal Analysis

The figures below show the IR thermal images of the prototype board, for the two different nominal input voltages.





**12V Input, 0.8A Output**

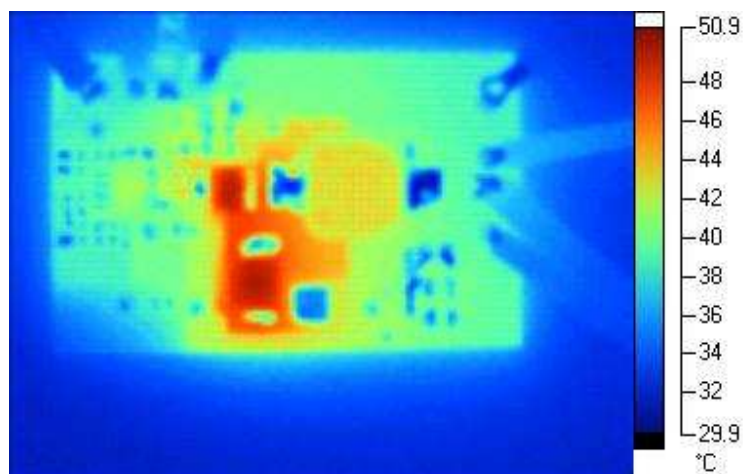


**5V Input, 0.8A Output**

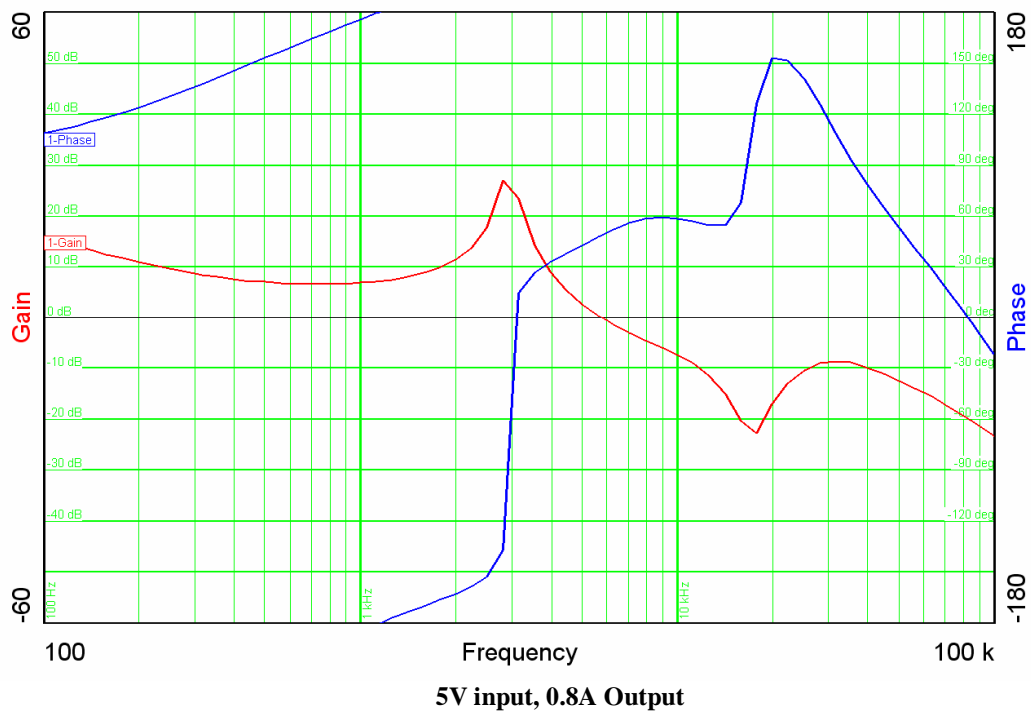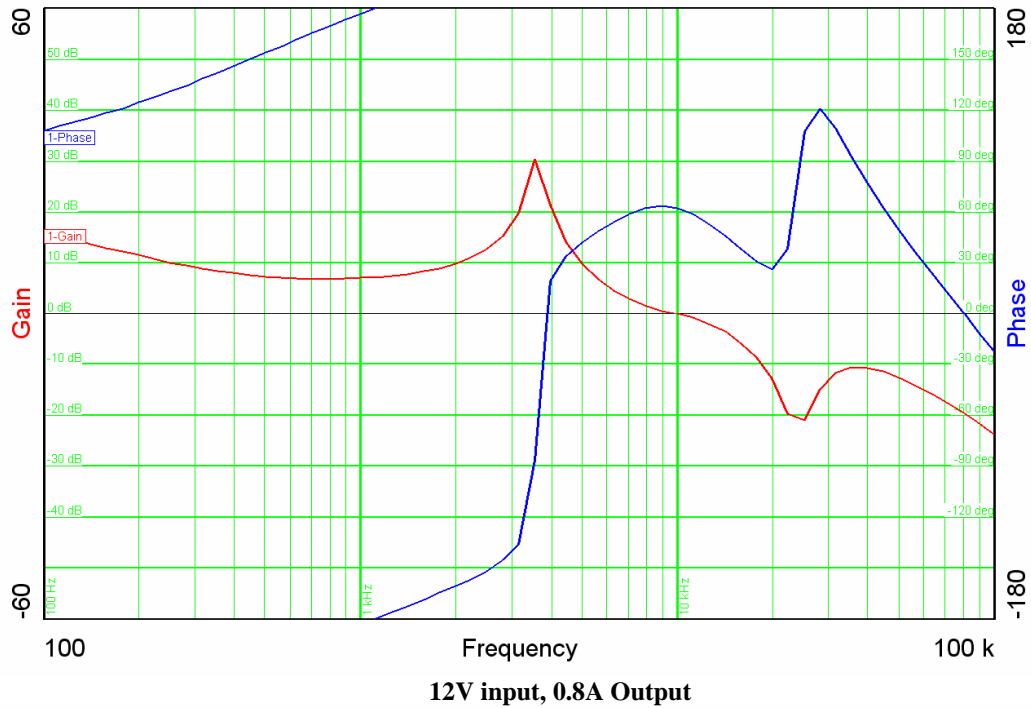
## 6 Control Loop Frequency Response

The figures below show the open loop response at full load 0.8A and after entering in the discontinuous mode, for the two different nominal input voltages.



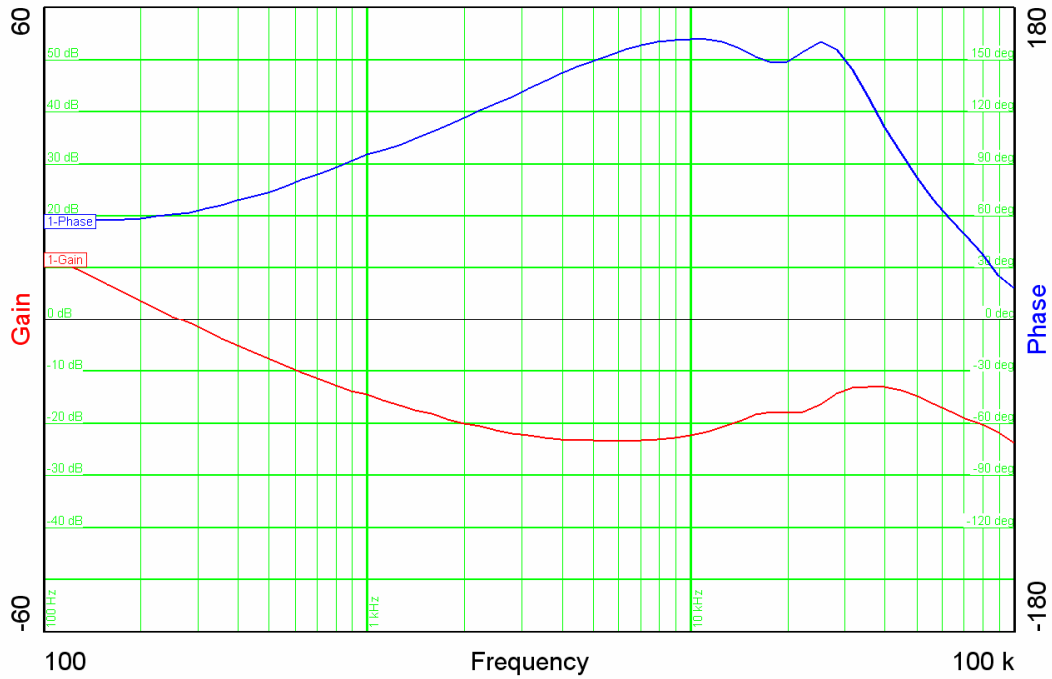

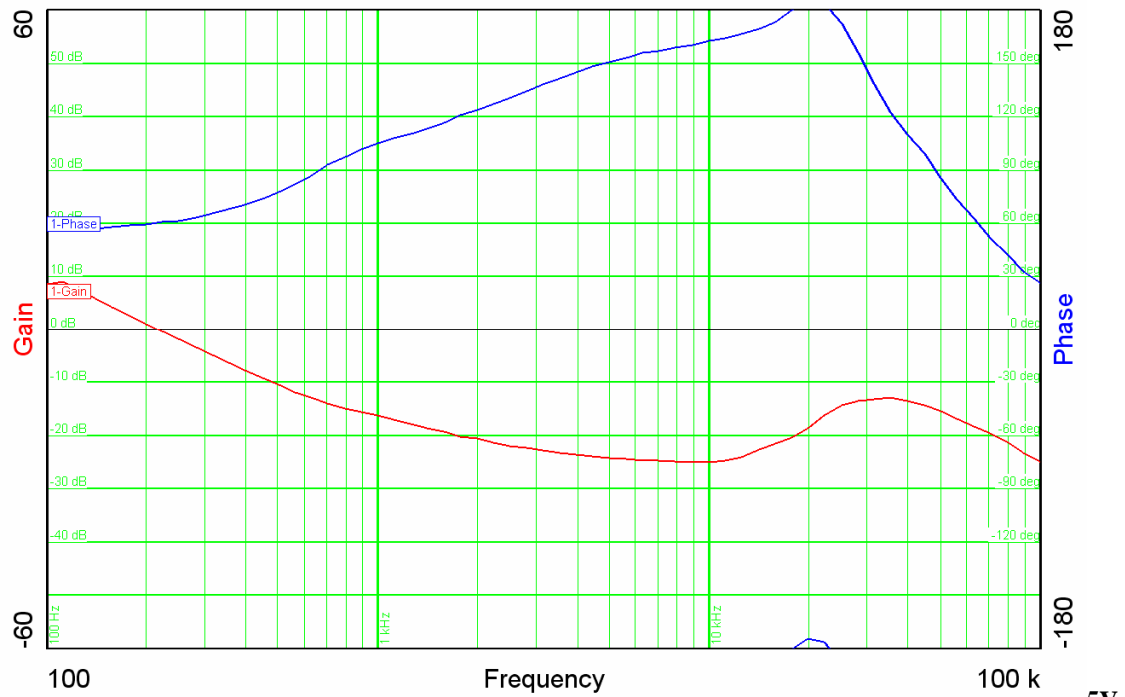**12V input, discontinuous output (discontinuous mode starts for output current less than 90mA)**




**5V input, discontinuous output (discontinuous mode starts for output current less than 50mA)**



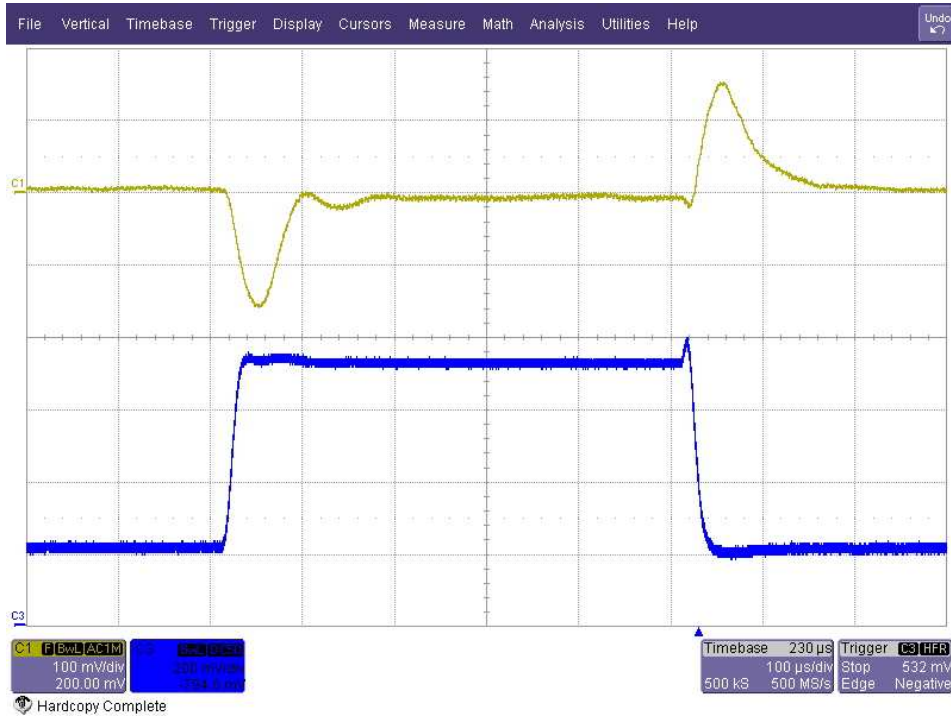
## 7 Load Transients

The figures below show the response to load transients, for the two different nominal input voltages. The current is stepping from 0.2 A to 0.7 A. Channel 1: Vout (AC coupled), channel 2: Iout (0.2A/div)



12V Input

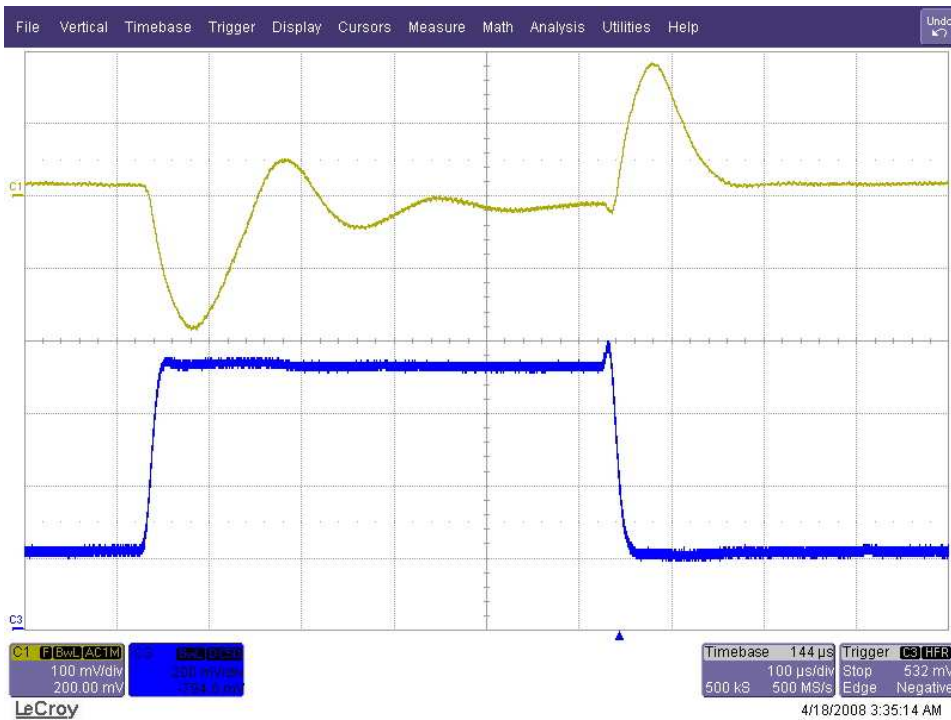

5V Input

## 8 Startup

The startup waveforms are shown in the figures below, for the two different nominal input voltages.



12V Input, 0.8A Output



5V Input, 0.8A Output

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated