

Introduction

The converter board has been developed for a Spoerle (Arrow) embedded DC/DC platform. Therefore the mechanical and electrical specification are intended to satisfy or improve the request. Signals for Power Good and Enable are available to enable sequencing, voltage scaling, diagnosis.


It operates from DC 24V +/- 15% with three Buck topology to three different outputs:

- 12V@1A, Buck controlled by TPS40200 (current limitation 2A)
- 5V@5A, Synch-Buck controlled by TPS40140 together with the 3.3V output (requested is 2A, actual current limitation 5.7A);
- 3.3V@5A, Synch-Buck controlled by TPS40140 together with the 5V output (requested is 2A, actual current limitation 5.7A)


For the 12V output (TPS40200) the switching frequency is 280kHz, for the other two outputs (TPS40140) the switching frequency is 350kHz.

Full MatchCad sheet of the three converters are also provided with complete calculation of power stage and control.

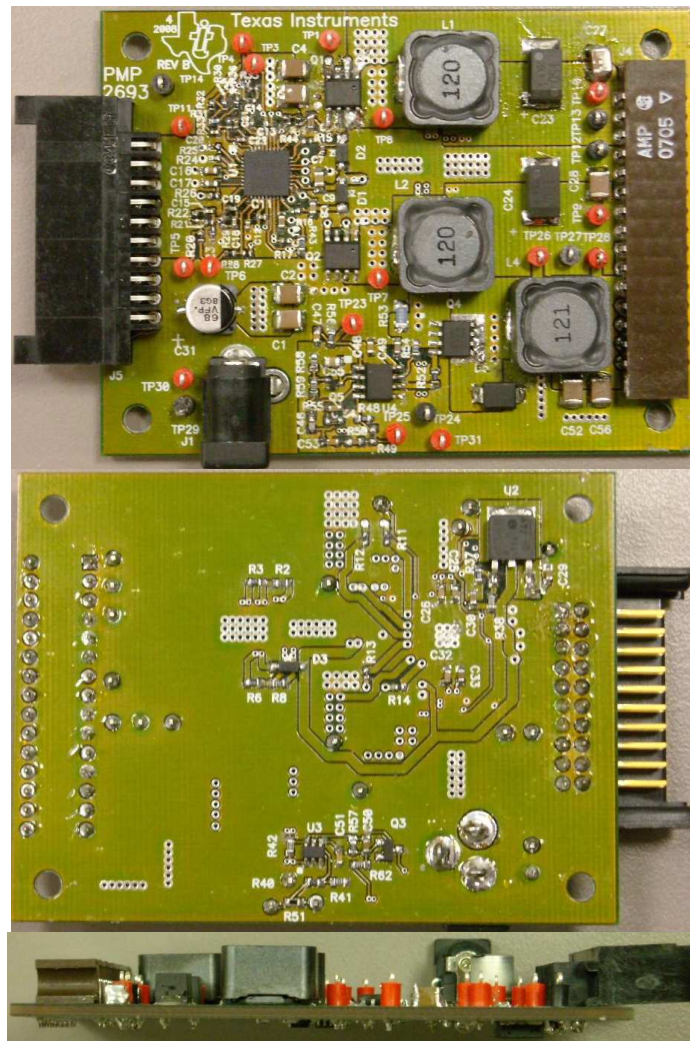
In the following the pictures (Top, Bottom, Side) of the realized board.




1 Main Waveforms

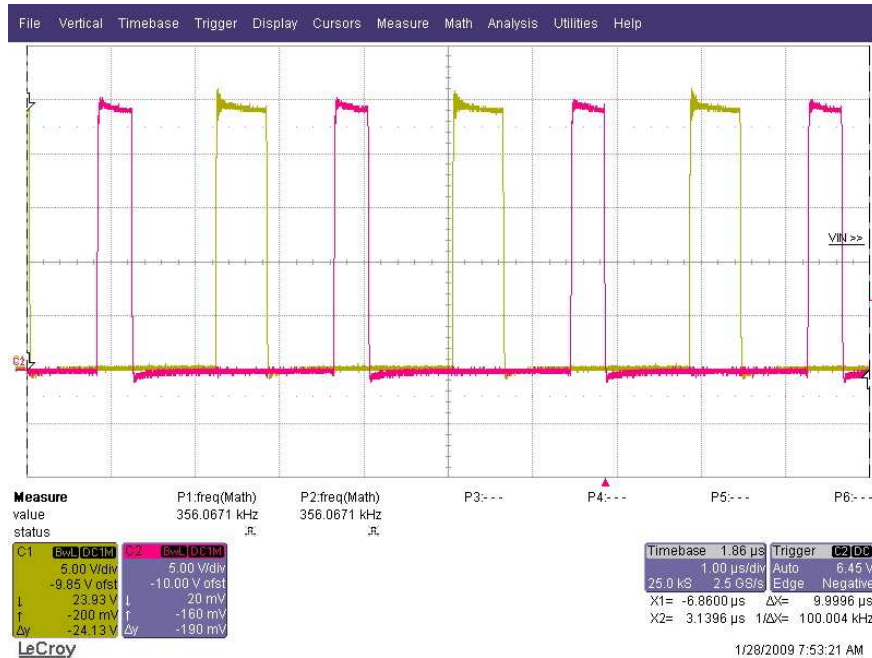

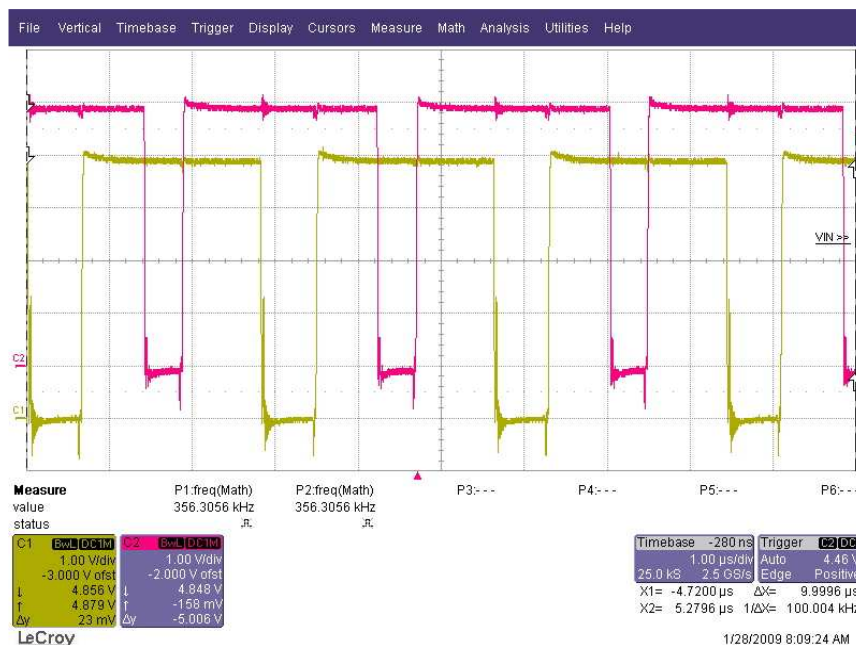
Switch Nodes of Synch-Buck (TPS40140): Vds Q1:B, TP8 (C2), Vds Q2:B, TP7 (C1)



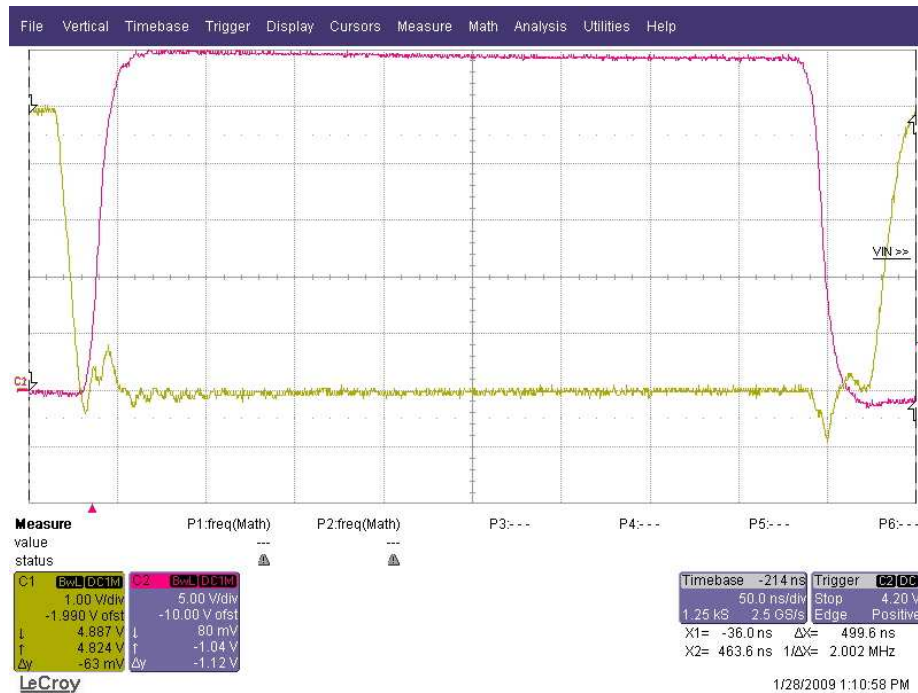
Low Side Mosfet Gates of Synch-Buck (TPS40140): Vgs Q1:B, (C2), Vgs Q2:B, (C1)



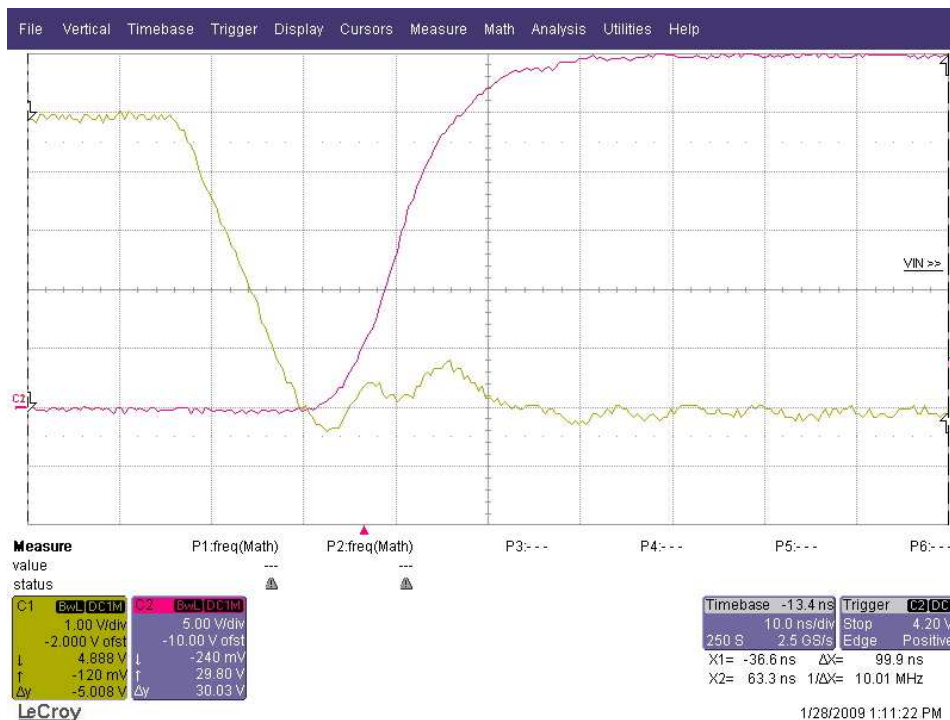
Gates of Synch-Buck for 5V output (TPS40140): VgGND Q2:A, (C2), VgGND Q2:B, (C1)



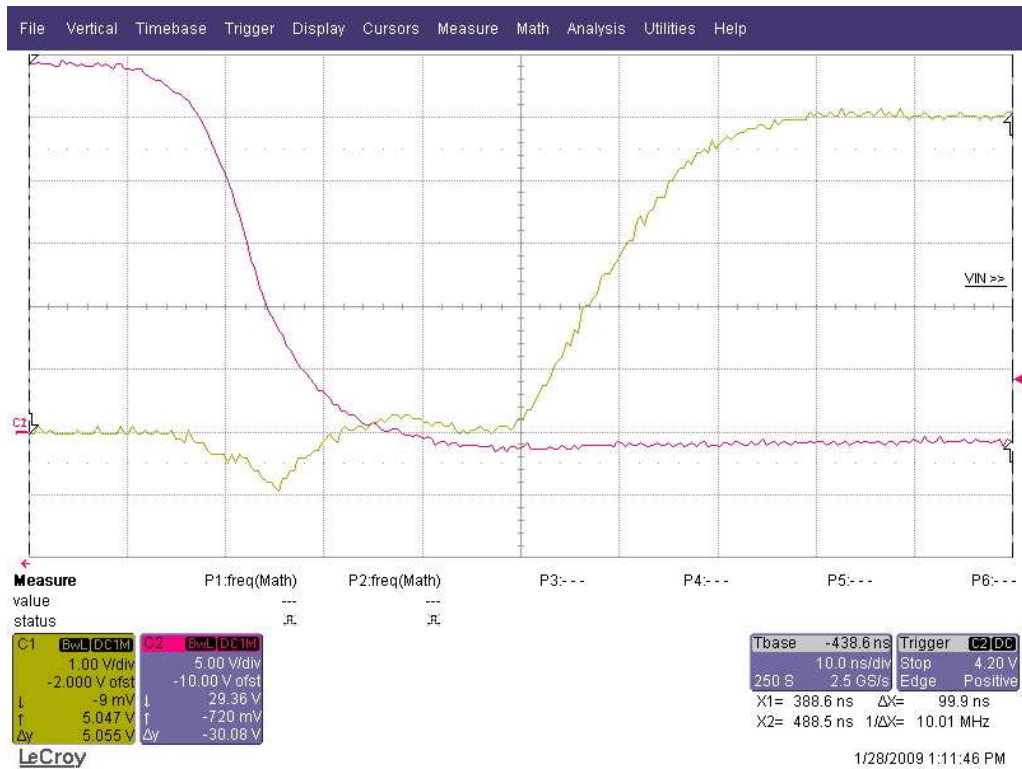
Gates of Synch-Buck for 5V output (TPS40140): VgGND Q2:A, (C2), VgGND Q2:B, (C1)



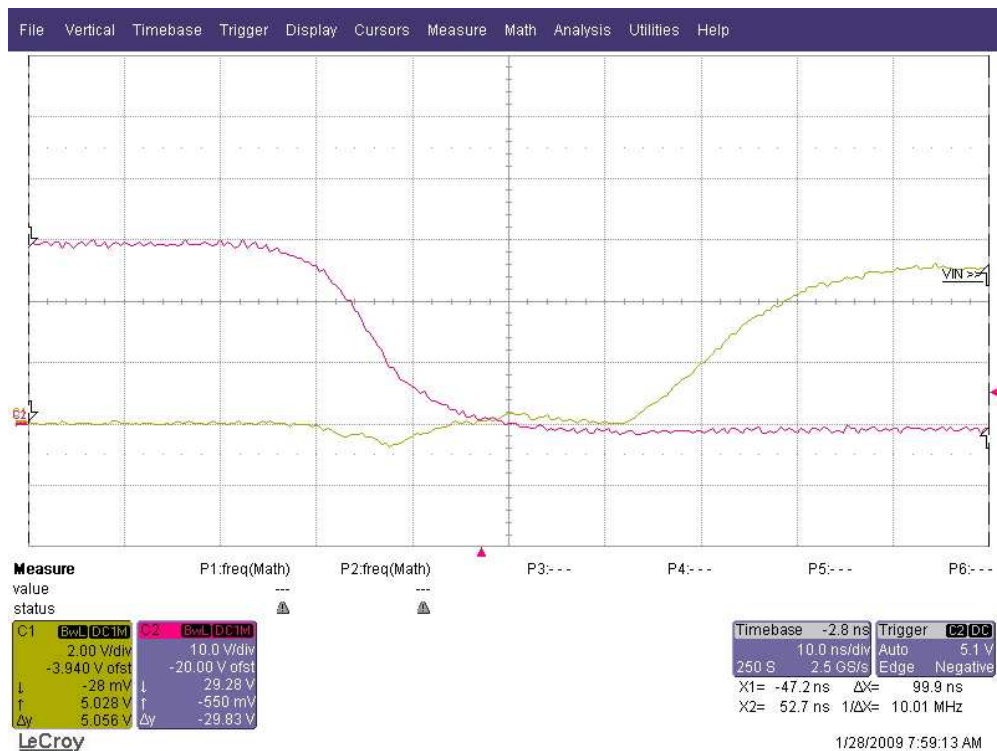Gates of Synch-Buck for 5V output (TPS40140): VgGND Q2:A, (C2), VgGND Q2:B, (C1)



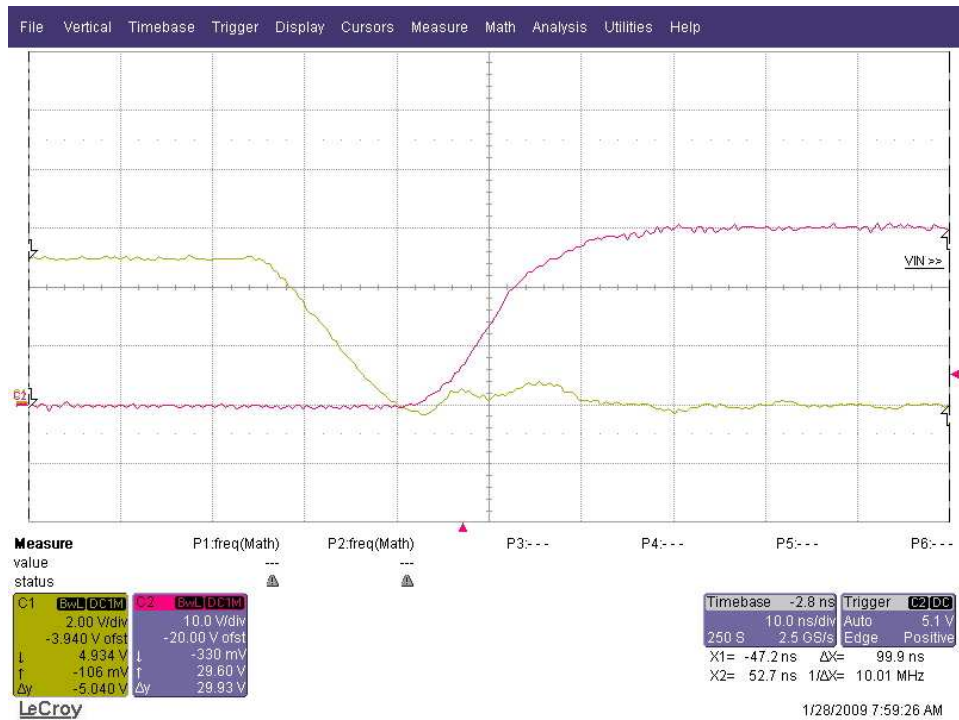Gates of Synch-Buck for 3.3V output (TPS40140): VgGND Q1:A, (C2), VgGND Q1B, (C1)




Gates of Synch-Buck for 3.3V output (TPS40140): VgGND Q1:A, (C2), VgGND Q1B, (C1)



Switch Node and High Side Mosfet Gate of the 12V output Buck (TPS40200): VdGND Q4, TP26

2 Efficiency and Load Regulation

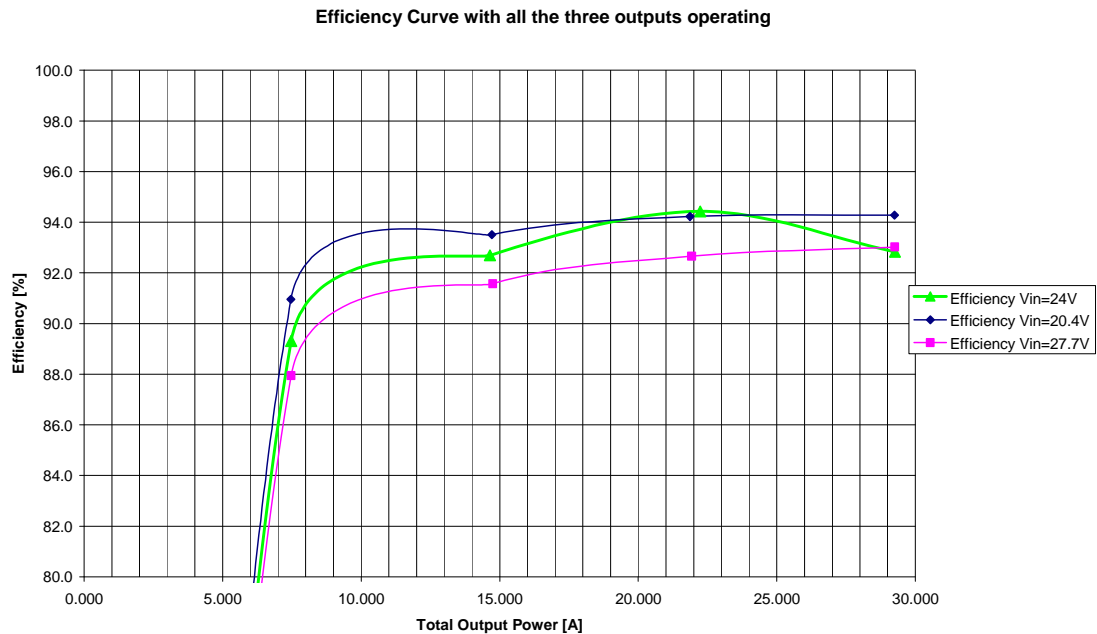
The efficiency diagrams are shown in the figure below for 6.5V, 9V, 12V input voltage, as a function of the output current.



The following table shows the measured values:

Vin[V]	Iin[mA]	Vout1[V]	Iout1[mA]	Vout2[V]	Iout2[mA]	Vout3[V]	Iout3[mA]	Pin[W]	Pout[W]	η %
24.26	0.027	12.23	0.000	5.04	0.000	3.35	0.000	0.655	0.000	0.0
24.18	0.346	12.23	0.256	5.03	0.511	3.35	0.529	8.366	7.472	89.3
24.09	0.656	12.23	0.504	5.03	1.004	3.34	1.027	15.803	14.648	92.7
24.08	0.978	12.23	0.775	5.02	1.513	3.34	1.546	23.550	22.237	94.4
24.01	1.313	12.22	1.006	5.02	2.016	3.34	2.054	31.525	29.266	92.8
20.08	0.028	12.23	0.000	5.04	0.000	3.35	0.000	0.562	0.000	0.0
20.68	0.397	12.24	0.256	5.04	0.516	3.33	0.520	8.210	7.468	91.0
20.60	0.764	12.24	0.504	5.03	1.017	3.34	1.028	15.738	14.717	93.5
20.55	1.129	12.24	0.755	5.02	1.495	3.34	1.530	23.201	21.861	94.2
20.44	1.518	12.23	1.006	5.01	2.013	3.35	2.051	31.028	29.253	94.3
27.79	0.028	12.23	0.000	5.04	0.000	3.35	0.000	0.770	0.000	0.0
27.68	0.307	12.23	0.256	5.03	0.511	3.35	0.529	8.498	7.473	87.9
27.67	0.582	12.23	0.504	5.03	1.021	3.34	1.032	16.104	14.746	91.6
27.65	0.856	12.23	0.755	5.02	1.504	3.34	1.541	23.668	21.931	92.7
27.59	1.140	12.23	1.006	5.02	2.012	3.34	2.052	31.453	29.257	93.0

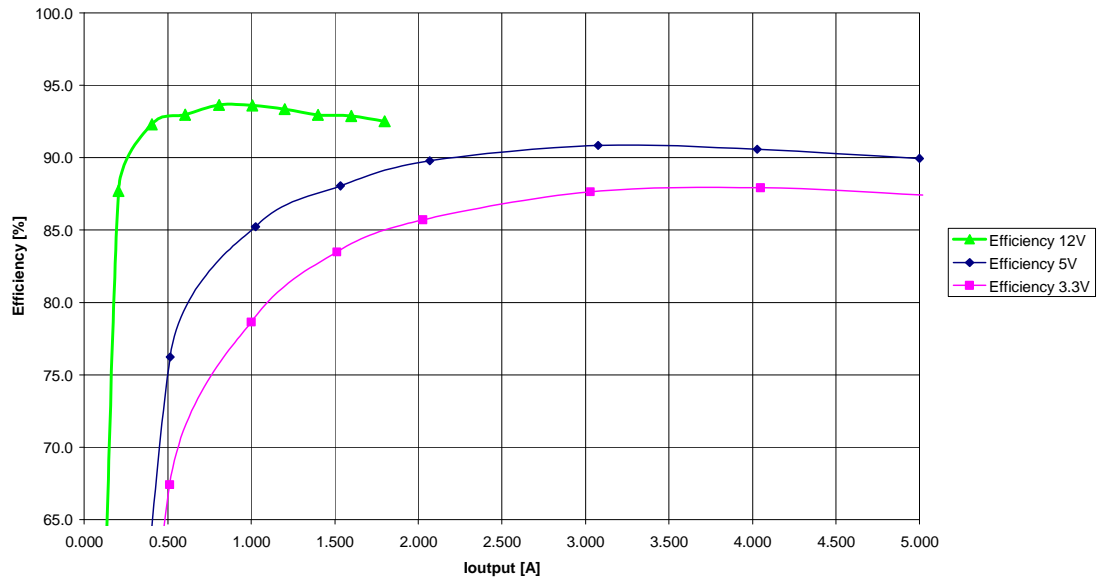Efficiency Curve for each Vout = 12 V, 5V, 3.3V (with the other two outputs with EN to GND)




The following table shows the measured values, of each output power measured with the other two outputs shut-off by the Enable pin connected to Ground. The efficiency is effected however by the performance of the linear regulator, when the 5V output is shut-off, because in this condition the regulator provides the supply to the TPS40140.


Vin[V]	Iin[mA]	Vout1[V]	Iout1[mA]	Pin[W]	Pout2[W]	η %
24.44	0.013	12.23	0.000	0.318	0.000	0.0
24.41	0.117	12.22	0.205	2.856	2.505	87.7
24.37	0.220	12.22	0.405	5.361	4.949	92.3
24.35	0.326	12.22	0.604	7.938	7.381	93.0
24.32	0.433	12.22	0.807	10.531	9.862	93.6
24.32	0.540	12.22	1.006	13.133	12.293	93.6
24.24	0.648	12.22	1.200	15.708	14.664	93.4
24.26	0.758	12.22	1.399	18.389	17.096	93.0
24.22	0.868	12.22	1.598	21.023	19.528	92.9
24.21	0.981	12.22	1.798	23.750	21.972	92.5
24.43	0.029	5.04	0.000	0.708	0.000	0.0
24.40	0.139	5.03	0.514	3.392	2.585	76.2
24.39	0.248	5.03	1.025	6.049	5.156	85.2
24.36	0.359	5.02	1.534	8.745	7.701	88.1
24.34	0.475	5.02	2.068	11.562	10.381	89.8
24.26	0.699	5.01	3.075	16.958	15.406	90.8
24.20	0.917	4.99	4.028	22.191	20.100	90.6
24.13	1.147	4.98	4.999	27.677	24.895	89.9
24.44	0.032	3.35	0.000	0.770	0.000	0.0
24.42	0.104	3.35	0.511	2.540	1.712	67.4
24.41	0.174	3.34	1.000	4.247	3.340	78.6

24.39	0.248	3.34	1.512	6.049	5.050	83.5
24.38	0.324	3.34	2.027	7.899	6.770	85.7
24.33	0.473	3.33	3.029	11.508	10.087	87.6
24.29	0.631	3.33	4.047	15.327	13.477	87.9
24.25	0.786	3.32	5.019	19.061	16.663	87.4

3 Control Loop Frequency Response

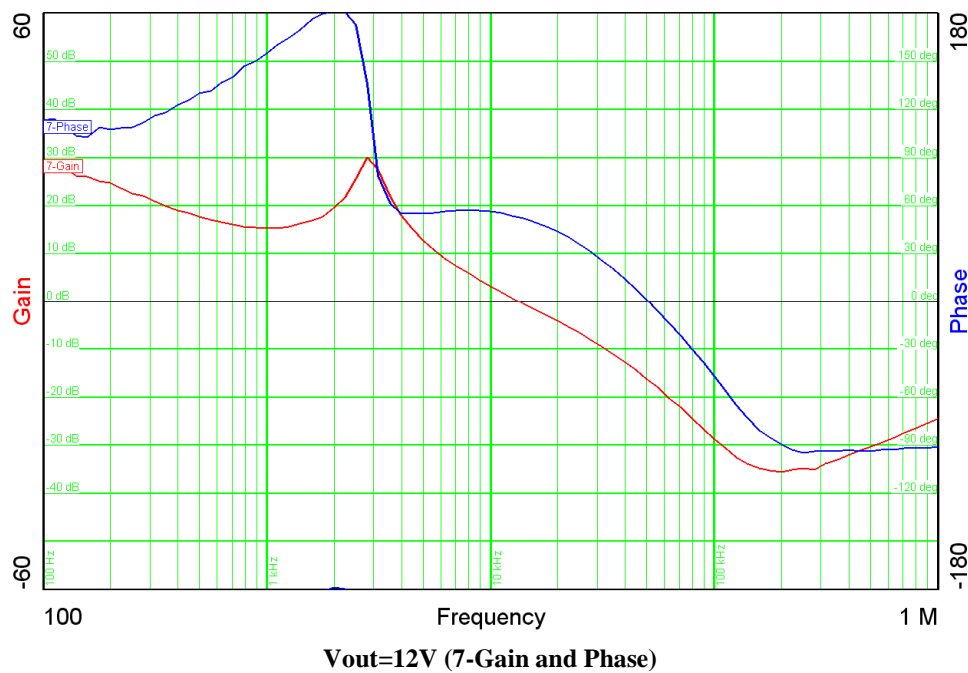The figures below show the open loop response for $V_{out}=12V$, $V_{out}=5V$, and $V_{out}=3.3V$ at full output load and $V_{in}=24V$.




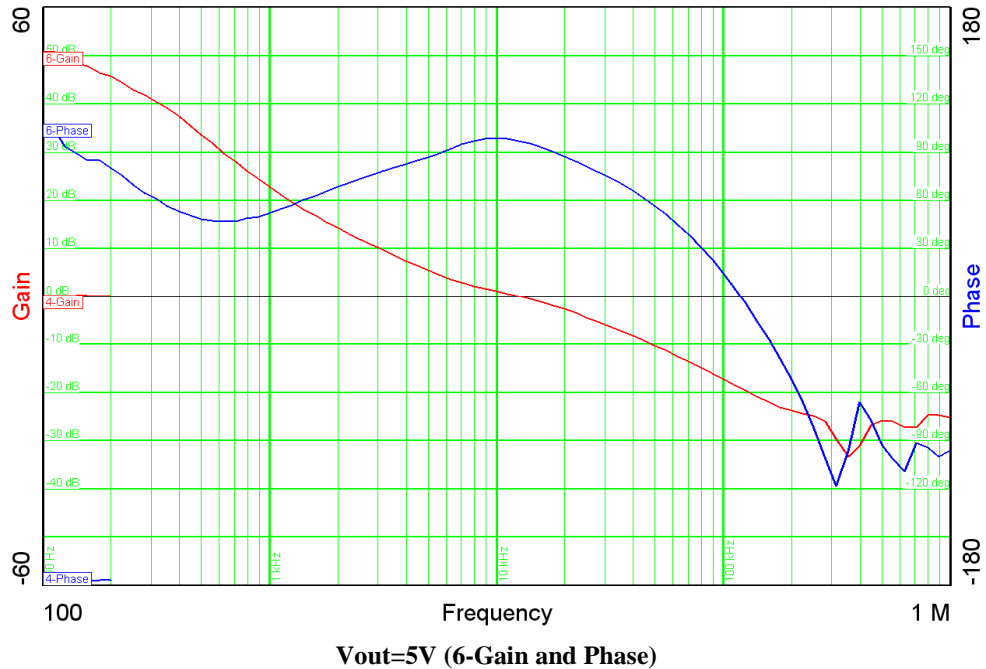


4 Load Transients

The figure below show the response to load transients applied to each output.

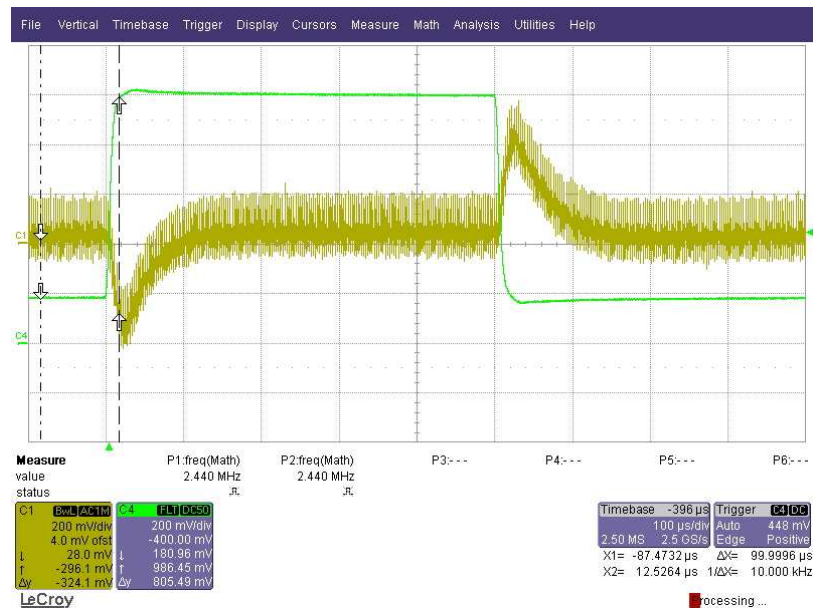
The current on the Output is stepping from minimum continuous mode load to full load (1A for $V_{out}=12V$ and 2A for $V_{out}=5V$ and $V_{out}=3.3V$) and viceversa, with $V_{in}=24V$.



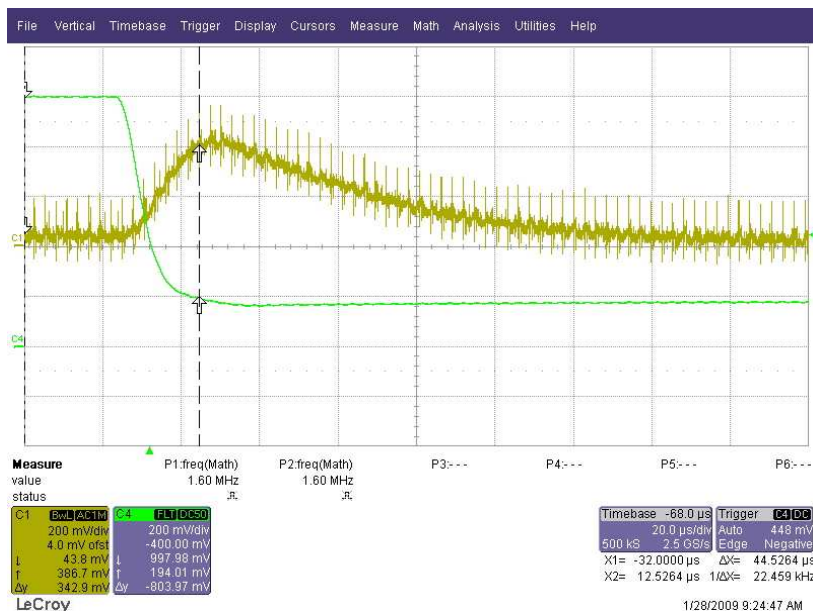
Vout=12V (C2), Iout (C4, 200mA/V current probe)



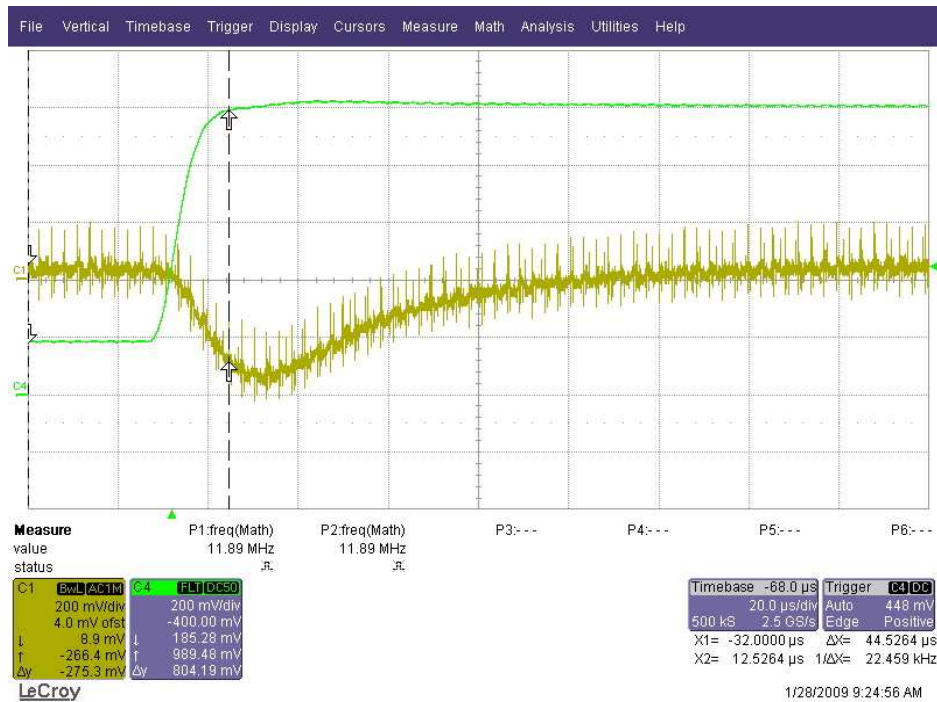
Vout=12V (C2), Iout (C4, 200mA/V current probe)



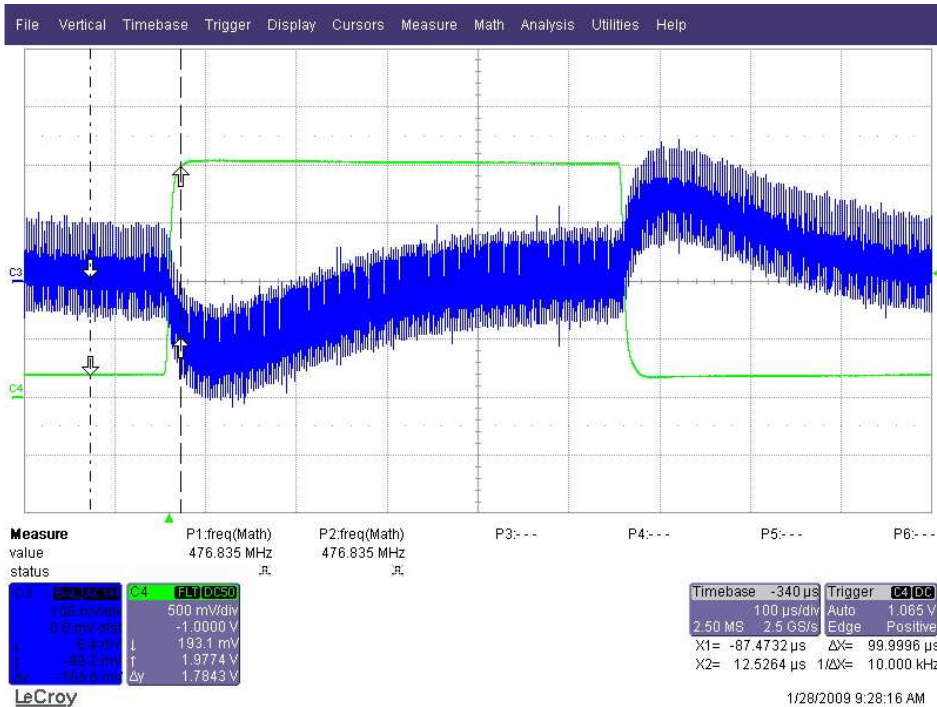
Vout=12V (C2), Iout (C4, 200mA/V current probe)



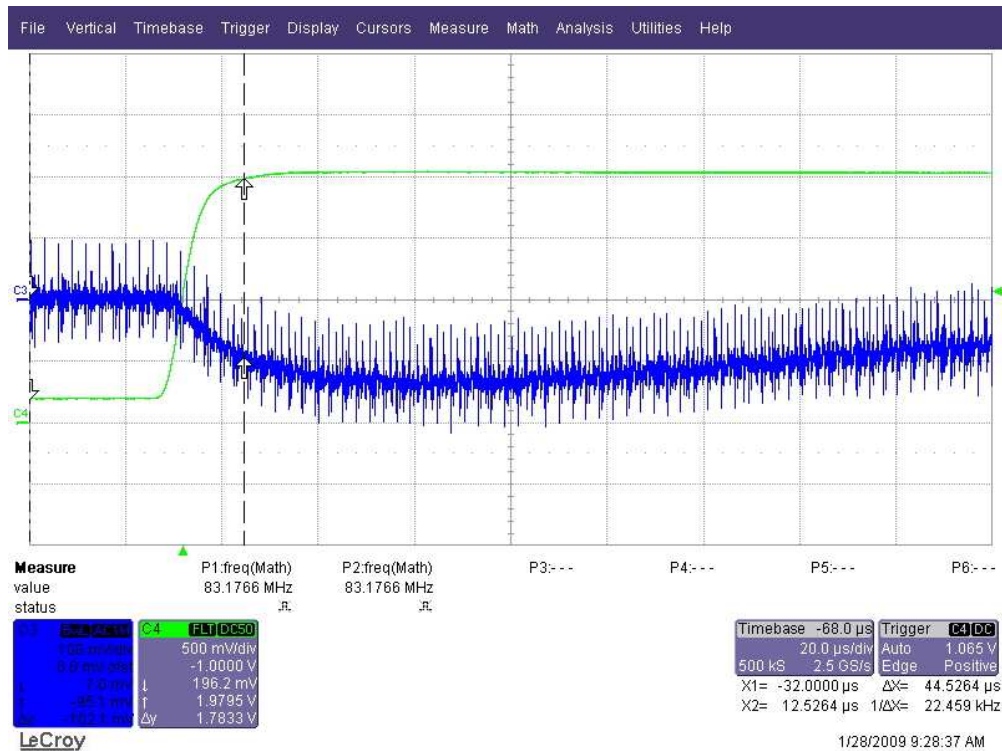
Vout=5V (C2), Iout (C4, 500mA/V current probe)



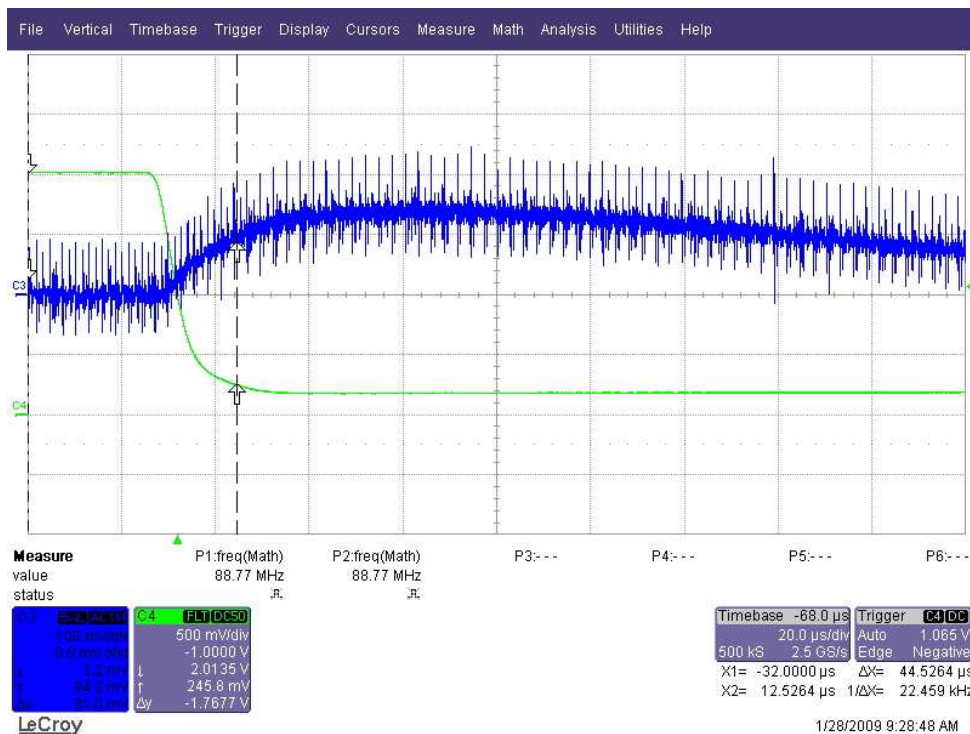
Vout=5V (C2), Iout (C4, 500mA/V current probe)



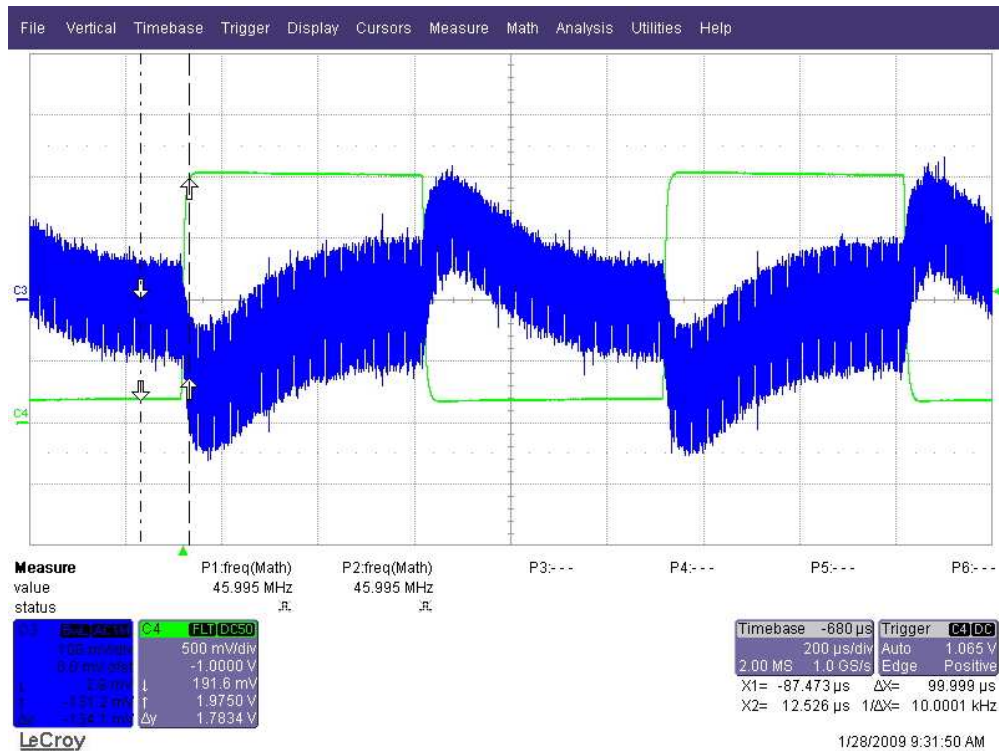
Vout=5V (C2), Iout (C4, 500mA/V current probe)



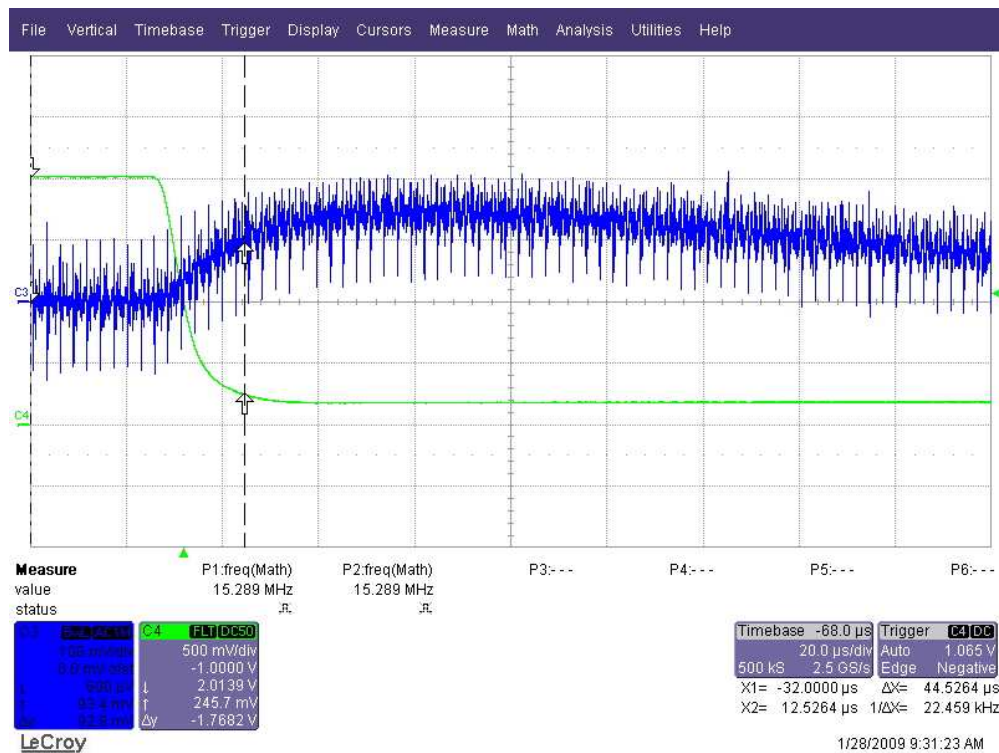Vout=3.3V (C2), Iout (C4, 500mA/V current probe)



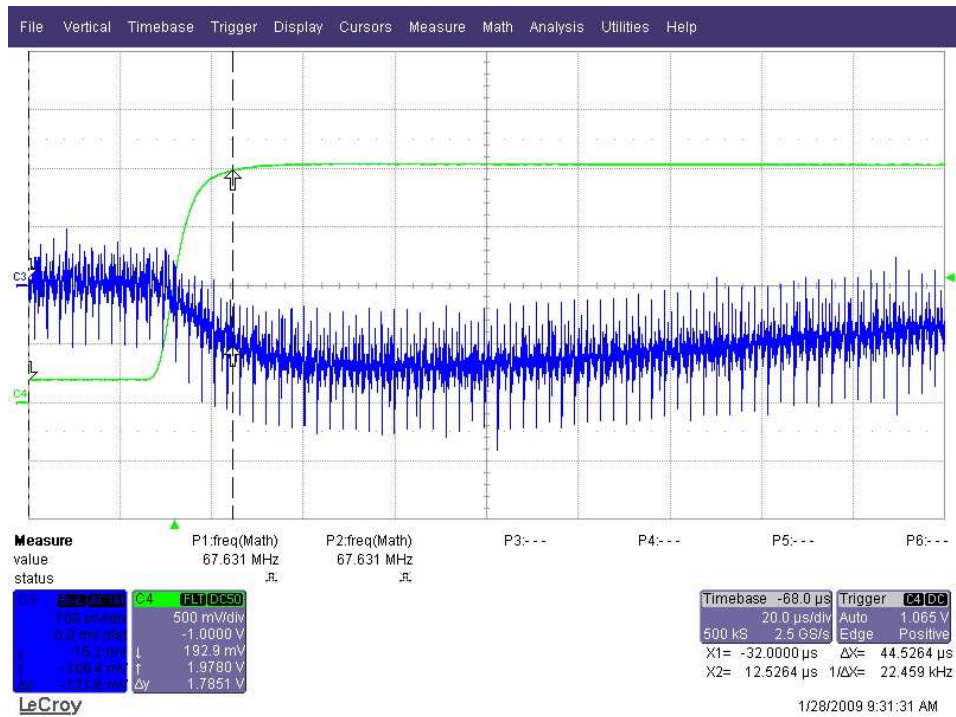
Vout=3.3V (C2), Iout (C4, 500mA/V current probe)




Vout=3.3V (C2), Iout (C4, 500mA/V current probe)

5 Output and Input Ripple Voltage

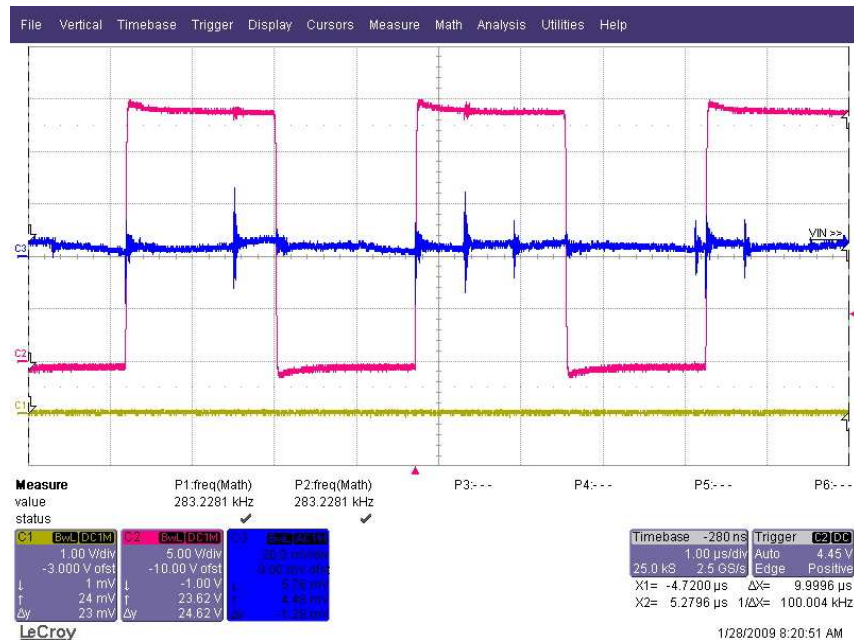
The output ripple voltage for the different output is shown in the figures below:



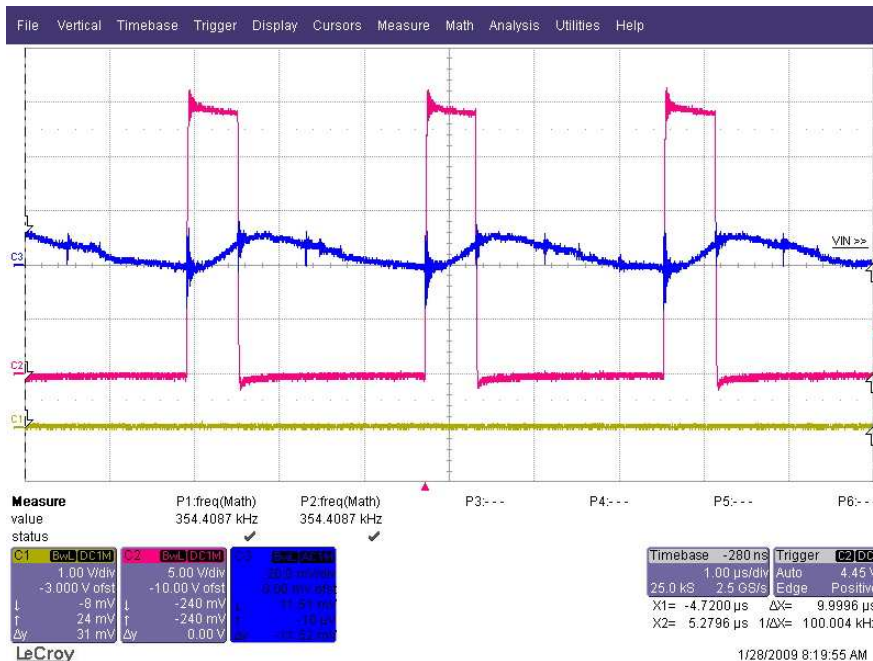Output ripple at the V=12V output (C3), Switch node TP26 (C2), at Iout=1A




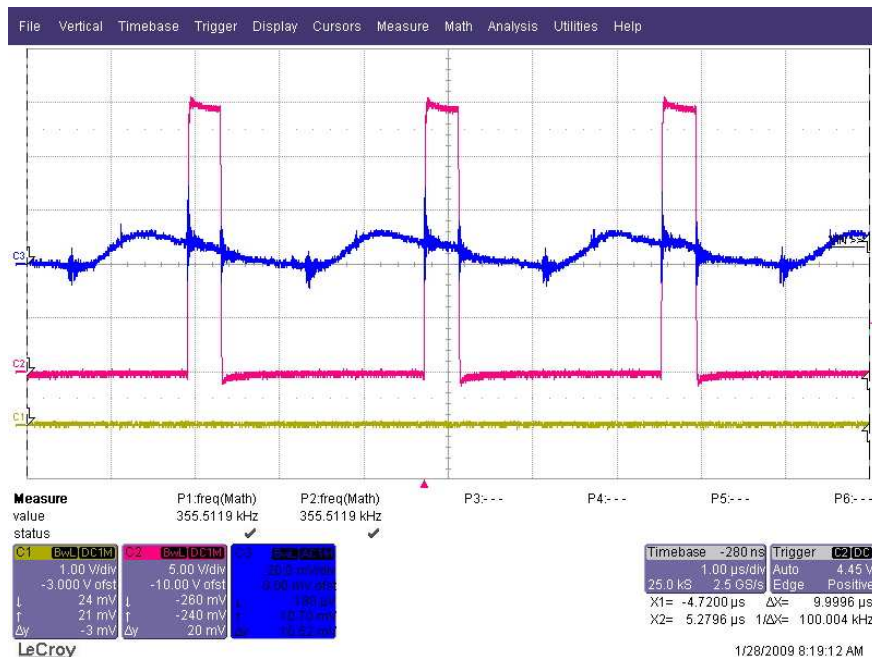Output ripple at the V=5V output (C3), Switch node TP7 (C2), at Iout=2A



Output ripple at the V=3.3V output (C3), Switch node TP8 (C2), at Iout=2A

6 Start-up Waveforms

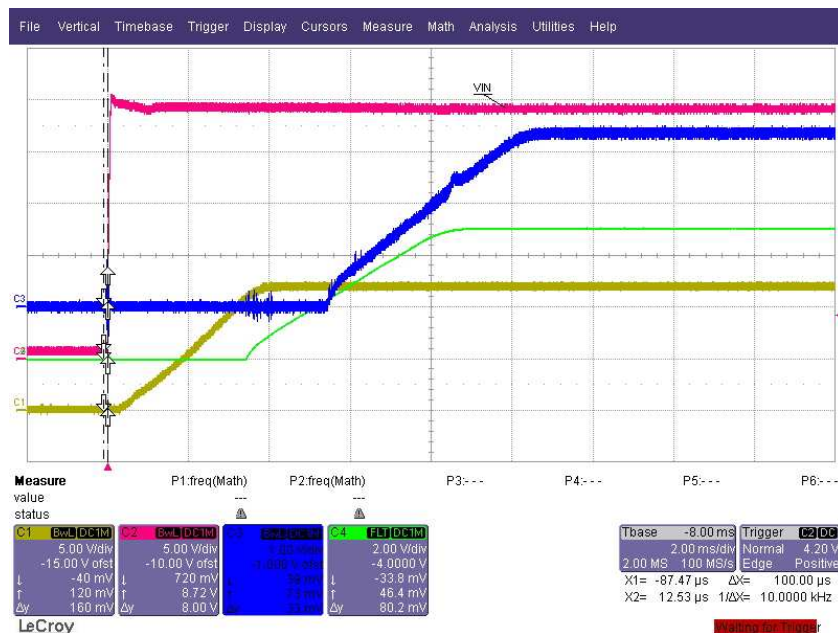


Input Voltage start Start-up Waveforms: Input voltage (C2), Output Voltage 12V (C1) @1A
Output Voltage 5V (C4) @2A, output Voltage 3.3V (C3) @2A

7 Thermal Images


The thermal images of board are taken for the Top Side and Bottom side of the board at the temperature of $T=25^{\circ}\text{C}$ ambient, at output load $V_{\text{out}}=12\text{V}@1\text{A}$ $V_{\text{out}}=5\text{V}@2\text{A}$ $V_{\text{out}}=3.3\text{V}@2\text{A}$.

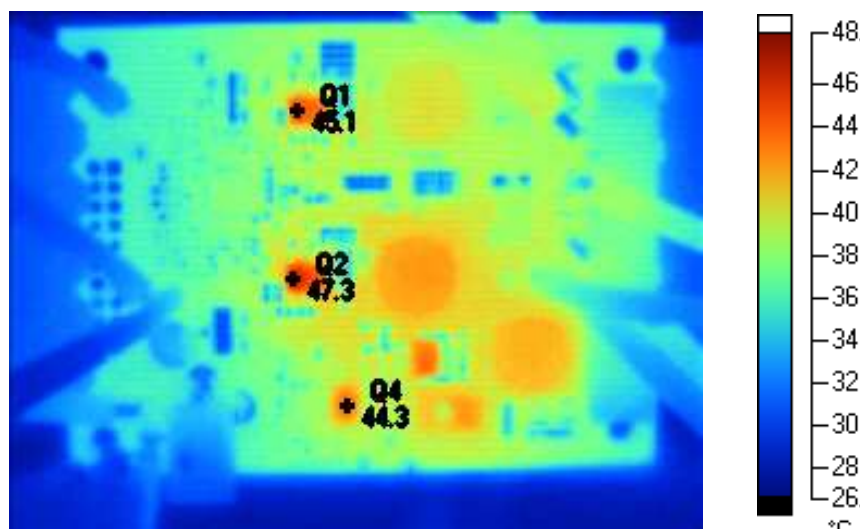In every picture the hottest spot is indicated, together with the temperature of the most significant components.



Top Side

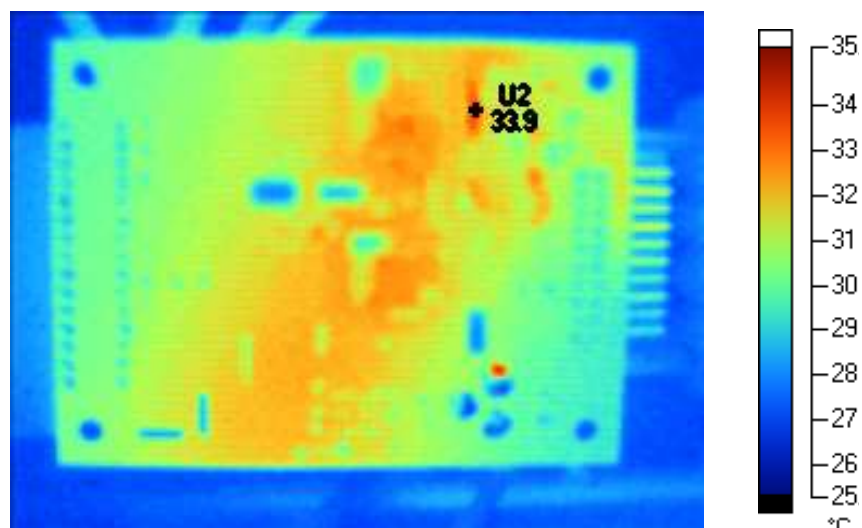Output Load $V_{\text{out}}=12\text{V}@1\text{A}$, $V_{\text{out}}=5\text{V}@2\text{A}$, $V_{\text{out}}=3.3\text{V}@2\text{A}$, Output Power 30W



Bottom Side

Output Load $V_{\text{out}}=12\text{V}@1\text{A}$, $V_{\text{out}}=5\text{V}@2\text{A}$, $V_{\text{out}}=3.3\text{V}@2\text{A}$, Output Power=30W

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated