

# Designing USB for short-to-battery tolerance in automotive environments



**Jeff Skarzynski**  
*Systems Engineer*  
*Integrated Protection Devices*  
*Texas Instruments*

# Explore solutions for protecting a $V_{BUS}$ line against vehicle battery shorts.

As vehicle manufacturers continue to make automotive infotainment systems an extension of the mobile media consumption experience, universal serial bus (USB) becomes more ubiquitous in the infotainment architecture. While USB was originally a purely consumer interface, it has since been co-opted into environments with much more stringent protection requirements. Among these is the need to protect against shorts to a car battery. This paper explores the challenges with protecting the  $V_{BUS}$  line for USB and presents three different solutions to the problem.

## $V_{BUS}$ to car battery – a hot plug-like event

First and foremost, a protection device must be used in series with the  $V_{BUS}$  connection to provide protection against overvoltage. Since the standard  $V_{BUS}$  on USB outputs 5V DC, a DC voltage of 12-18V poses a problem to an unprotected circuit. Using a protection solution such as the TPD3S714-Q1 will provide the overvoltage and DC-blocking protection that will solve an overvoltage problem. The sudden shorts to car battery, however, introduce transients to the  $V_{BUS}$  line. Since the protection device essentially acts as an open path once it responds and turns off, the short-to-car battery should emulate an ideal resistor, inductor and capacitor (RLC) circuit response (Figure 1).

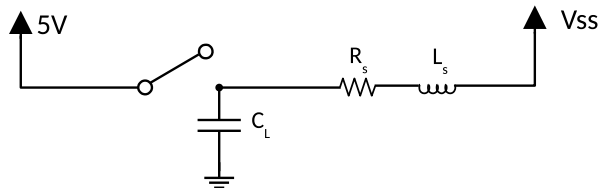


Figure 1: Ideal model of short-to-battery transient

The cabling used to do shorts is represented by  $R_s$  and  $L_s$ ;  $V_{SS}$  represents the car battery, and the output capacitance of the 5V  $V_{BUS}$  is represented by  $C_L$ . Since both the cabling resistance and the capacitor resistance in ceramic capacitors

are very small, one would expect nearly an ideal underdamped response of double the applied step voltage (Figure 2).

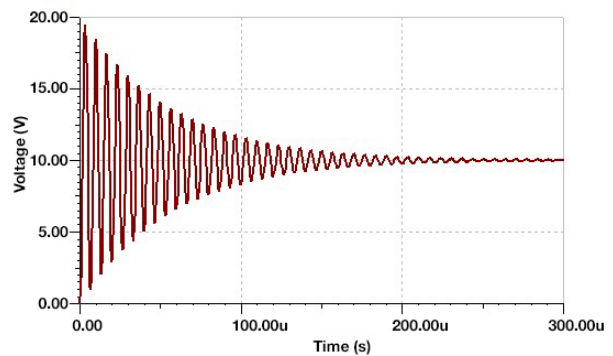


Figure 2: Example RLC series step response to 10V

In our initial testing, we noticed that voltage was not actually double the expected ringing – in some cases this was causing early failures of our protection device. When testing the capacitor by itself, we found the ringing was actually three times greater than the applied DC voltage.

Figure 3 shows a 1  $\mu$ F X7R 50 V-rated ceramic that rings above the maximum rated voltage when an 18 V short is applied. After some thought and experimentation we found the root cause: ceramic capacitor derating versus applied voltage.

Our 50-V capacitor would derate to nearly 10 percent of the original capacitance during ringing.

Since our short-to-battery testing simulates a short through a cable, the cable inductance (which stays constant) forces a sinusoidal current even as the capacitance of the ceramic drops rapidly. This causes the strange peaking shown in **Figure 3** and was the reason for our early failures. By more careful design on the output of  $V_{BUS}$ , these problems can be prevented. Three options are presented as solutions, each with their own advantages and disadvantages.

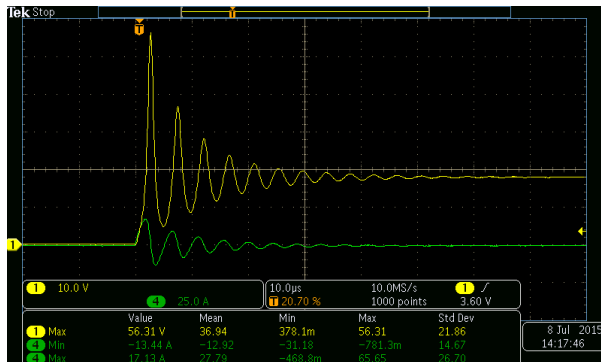


Figure 3: 1  $\mu$ F 50V X7R ceramic shorted to 18V through a 1-m cable

## Short-to-battery hot plug solutions

### Choosing capacitors by derating curves

Although examining capacitor derating curves may make sense, this is something that designers often overlook during component selection. Although a ceramic capacitor is rated for a DC voltage of 50 V, it does not mean it will be anywhere near the rated capacitance on the label at 50 V. The capacitors we ended up settling on for our short-to-battery testing were 100 V, 1  $\mu$ F, X7R ceramics. The derating curve put these at approximately 80 percent of the original capacitance at our peak overshoot voltage of 36 V. By keeping the capacitance closer to constant over the working voltage we reduced ringing and overshoot significantly.

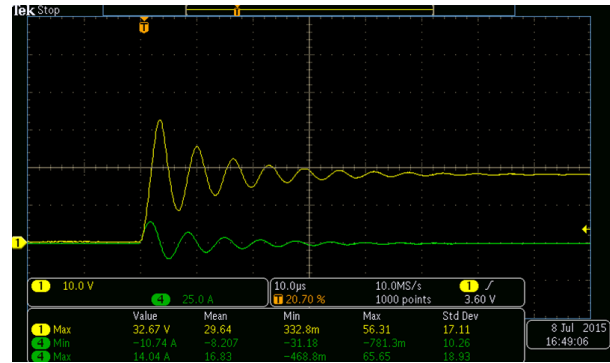


Figure 4: 1  $\mu$ F 100V X7R ceramic shorted to 18V through a 1-m cable

**Figure 4** demonstrates the difference capacitor selection can have for the exact same short as applied in **Figure 3**.

Advantages:

- fewer system components
- smaller footprint

Disadvantages:

- capacitor cost increase
- smaller output capacitance

### Employing an R-C snubber circuit

Although perhaps the trickiest to design, the R-C snubber circuit can prevent overshoot ringing altogether by choosing the right component values. In addition to the output capacitance, another capacitor with a resistor in series can be added to push the response of the hot plug closer to critically damped. First, the maximum cable length and cable gauge should be analyzed to give an approximate cable inductance of the system. Our testing uses a 1-m, 18 American wire gauge (AWG) cable which results in approximately 1.5  $\mu$ H of effective inductance. Coupled with the existing output capacitance of 1  $\mu$ F, we first need to choose a snubber capacitance that will dominate during transient events. A good rule of thumb is to use 10 times the load capacitance. Since capacitance of the  $V_{BUS}$  FET while off is negligible compared to the 1  $\mu$ F, a 10  $\mu$ F capacitor should be used.

Since the goal is to try to dampen the overshoot without causing too many issues, we want to design for a critically damped per the series RLC equation

$$(1) \zeta = \frac{R}{2} \sqrt{\frac{C}{L}} = 1$$

Plugging in our snubber capacitance of 10  $\mu\text{F}$  and cable inductance of 1.5  $\mu\text{H}$  gives us a required  $R \approx 775 \text{ m}\Omega$ . With these, it is always wise to run a quick simulation to make sure our assumptions are correct. See **Figures 5 and 6** for simulation results showing the difference that adding a snubber can have on a system.

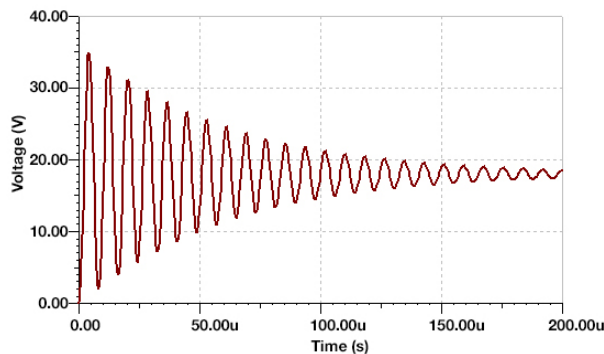


Figure 5: Undamped RLC simulation

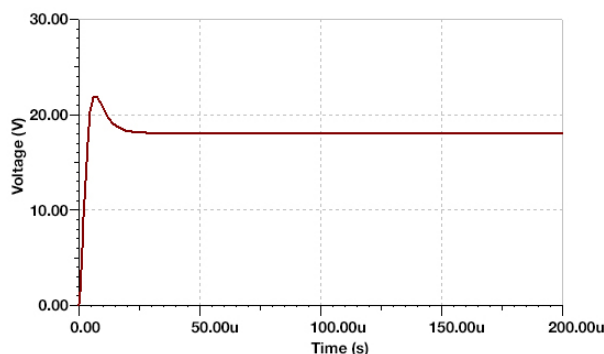


Figure 6: Damped RLC simulation

Advantages:

- can provide best protection against overshoot

Disadvantages:

- more complicated to design
- most components required

### Adding an external TVS diode

The third and final method for solving the ringing issue is perhaps the simplest: adding a small transient voltage suppressors (TVS) to aid in clamping the ringing. By choosing a TVS rated slightly above the working voltage (for example, a 20-V TVS for an 18 V maximum short-to-battery system), the clamp will react during the initial ringing but should not conduct under DC steady-state conditions. In our experience, a small 0603-sized TVS should provide enough clamping to dampen the ringing and prevent any capacitance related overshoot.

Advantages:

- simplest to design

Disadvantages:

- additional components and board space
- TVS may be more expensive than capacitor or snubber solutions

### Summary

Designing for short-to-battery faults in a USB system can be challenging, but using some of the techniques presented can help prevent any missteps while designing for the  $V_{\text{BUS}}$  transients. Any of the three options presented will do the job adequately, but each has their own advantages and disadvantages. Proper capacitor selection to handle derating may be more costly per capacitor, but it is the smallest solution size. Using an R-C snubber will provide the best defense against overshoot, but requires the most calculation and design. A TVS may be the easiest to design, but could be the most expensive solution.

### References

1. More information on TI's [ESD protection solutions](#).
2. Download the [TPD3S714-Q1](#) data sheet.

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

The platform bar is a trademark of Texas Instruments.

All other trademarks are the property of their respective owners.

© 2016 Texas Instruments Incorporated  
Printed in the U.S.A.

**SLLY019**

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)