

LM26400Y

Powering Multi-Rail Systems Using the LM26400Y Regulator



Literature Number: SNVA529

Today's electronic systems typically have multiple DC voltage rails that are powered by point-of-load regulators. The input rail to these regulators can be an AC adapter, an intermediate bus, a battery, or a USB power rail. Often it is desirable to find a power solution that can handle a relatively wide input range, is reasonably integrated, and simple to use. National Semiconductor's LM26400Y dual buck switching regulator addresses such applications. It has an operating input voltage range of 3V to 20V and a guaranteed maximum duty cycle of 90% so it is able to handle a large range of step-down conversions. The LM26400Y device has integrated power FETs and internal-loop compensation. The two packages offered, TSSOP and LLP, have an exposed pad that allows unimpeded heat flow from the die to the PCB surface.

Many Features Enable Flexibility

Figure 1 is a simplified block diagram of the LM26400Y regulator. The device features separate soft-start, enable pins, and internal bootstrap diodes. Sequencing of the regulator can be controlled by toggling the enable pins at different times or slewing the soft-start pins at different rates. The integrated bootstrap diodes can simplify designs when a bootstrap bias is not readily available in the system. The two channels switch at the same 500 kHz frequency but are 180° out of phase, reducing the AC current in the input capacitors.

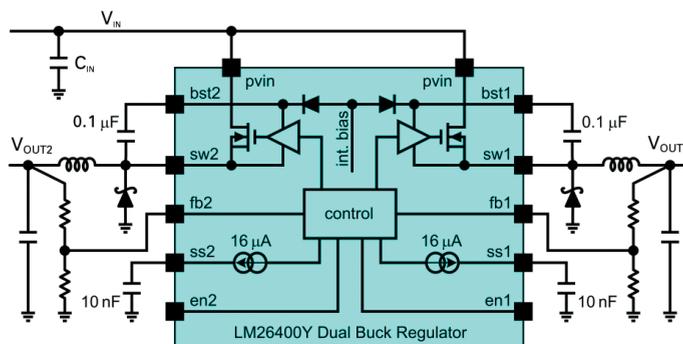


Figure 1. Simplified View of the LM26400Y Regulator

FPGA Power-Up

In this article, the LM26400Y is powering a popular FPGA off of an input voltage range of 4.75V to 13.2V. The example uses an FPGA-based subsystem that has six functions in the chip that need power as listed below:

Supply	Function	Voltage
VCCINT	Core	1.2V
VCCAUX	Auxiliary	2.5V
VCCO_0-3	4 I/O Banks 0-3	1.2/1.5/1.8/2.5/3.3V

To interface effectively with different output buffer standards, the four I/O banks can work at five different voltage levels.

To design a power supply solution for the FPGA, more must be known about the application. The power required by the six functions in the chip can vary dramatically depending on the utilization ratio. The power estimation tool provided by the FPGA vendor translates the usage scenario into terms a power designer can readily utilize:

	VCCINT	VCCAUX	VCCO_0	VCCO_1/2/3
Voltage	1.2V	2.5V	2.5V	3.3V
Current	1.75A	0.62A	1.41A	1.27A

VCCAUX and VCCO_0 are the same voltage level and could share a voltage regulator. However, in this case, VCCO_0 needs to power up separately to satisfy peripheral device sequencing, and thus a total of four voltage rails are employed.

All four rails may ramp up independently of each other as long as they reach their nominal voltage levels within 0.2 ms to 50 ms in a monotonic fashion. The only potential concern to meet that requirement is VCCINT. According to the datasheet, if VCCINT comes up earlier than VCCAUX, there can be a surplus current (366 mA typical) on the VCCINT rail which appears somewhere after VCCINT hits 0.5V.

The board hosting the FPGA is to be plugged into two kinds of systems, one supplying an input of 12V +/-10%, the other an input of 5V +/-5%. The FPGA voltage regulators need to handle an input range from 4.75V to 13.2V. A linear solution is not an option due to the unacceptable power losses which are worst at the 12V input.

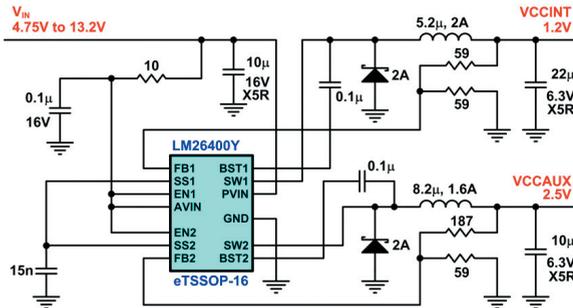


Figure 2. FPGA Power - VCCINT and VCCAUX

Based on the estimates above, plus some safety margin (because those numbers are just estimates), two switchers are required of up to 2A each for VCCINT and VCCO_0, one switcher of approximately 1A for VCCAUX and one switcher of approximately 1.5A for VCCO_1, VCCO_2, and VCCO_3 combined. One LM26400Y regulator can be used to generate VCCINT and VCCAUX and another to generate the I/Os. The schematic for the VCCINT (1.2V) and VCCAUX (2.5V) supply is shown in Figure 2.

The startup behavior is shown in Figure 3. Although the two channels share a 15 nF soft-start capacitor, VCCAUX will rise twice as fast as VCCINT due to the greater voltage-divider ratio. This allows the power

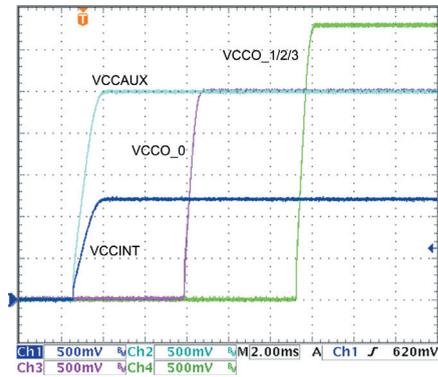


Figure 3. FPGA Solution - Startup

designer to avoid the surplus current of a few hundred milliamps mentioned above.

Regarding the other two FPGA rails, the VCCO_0 (2.5V) circuit uses the same design as VCCAUX as does the VCCO_1/2/3 (3.3V) circuit except for the upper feedback resistor. The enable pins of the VCCO circuits are not tied to the input voltage due to the potential sequencing requirement of peripheral devices. Two separate ON signals are generated by the system to turn on the VCCO circuits independently. They also have separate soft-start capacitors which are 15 nF each.

This design has been bench verified with the typical efficiency of the VCCO_1/2/3 regulator shown in Figure 4.

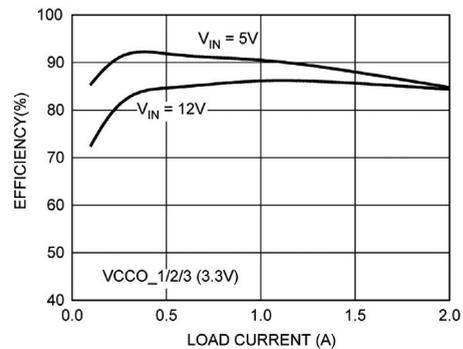


Figure 4. FPGA Solution - Efficiency

To read more about Powering Multi-Rail Systems Using the LM26400Y Regulator, including a POS systems barcode scanner example, visit www.national.com/ae5

National Semiconductor
2900 Semiconductor Drive
Santa Clara, CA 95051
1 800 272 9959

Mailing Address:
PO Box 58090
Santa Clara, CA 95052

National Semiconductor
The Sight & Sound of Information

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated