

Choosing the Right Linear Regulator for Your Application



Literature Number: SNVA570

Technology Edge

Choosing the Right Linear Regulator for Your Application

By Martin Moss, Product Marketing Manager

Linear regulators are often used as a band-aid by design engineers and are often chosen in later stages of the product development. The design engineer is concentrating more on how to make the complex BB or RF ASIC work, rather than the power/performance of the linear regulator that he or she may select.


Linear regulators are often selected by the key specifications in the traditional bullet list than by the very critical core and performance characteristics that usually lay inside the cover of the datasheet. Specifications are very often misleading — what is advertised on the front sheet represents the key parameters, but has no value when not combined with other connecting parameters.

For instance, ground current is one of these parameters. This situation has developed because the competitive nature of the linear regulator market dictates that manufacturers of devices recognize the need to get the time restricted engineer to spend more than a passing glance at the device. Also, there is no true standardization in the way information is presented. Different scales, temperatures, and loads only cause confusion for the design engineer trying to compare parts.

Linear regulators — what are they?

The modern linear regulator provides many ingenious architectural fixes for challenging requirements. Essentially, a linear regulator is an operational amplifier and a pass transistor. The operational amplifier uses two points of reference — the internal band gap reference and a resistor divider chain on the output. During regulation, the voltage value of the resistors divider network provides feedback to the operational amplifier where it is compared with the band-gap reference.

Depending on the result, the pass transistor will turn on more or less current. This is a closed-loop system based around two main poles, these being the internal pole of the Error Amplifier/pass transistor and the external pole of the output current demand and ESR of the output capacitor. Manipulation of these two dominant poles affects the performance of the device and is a main contributor to the stability of the loop.

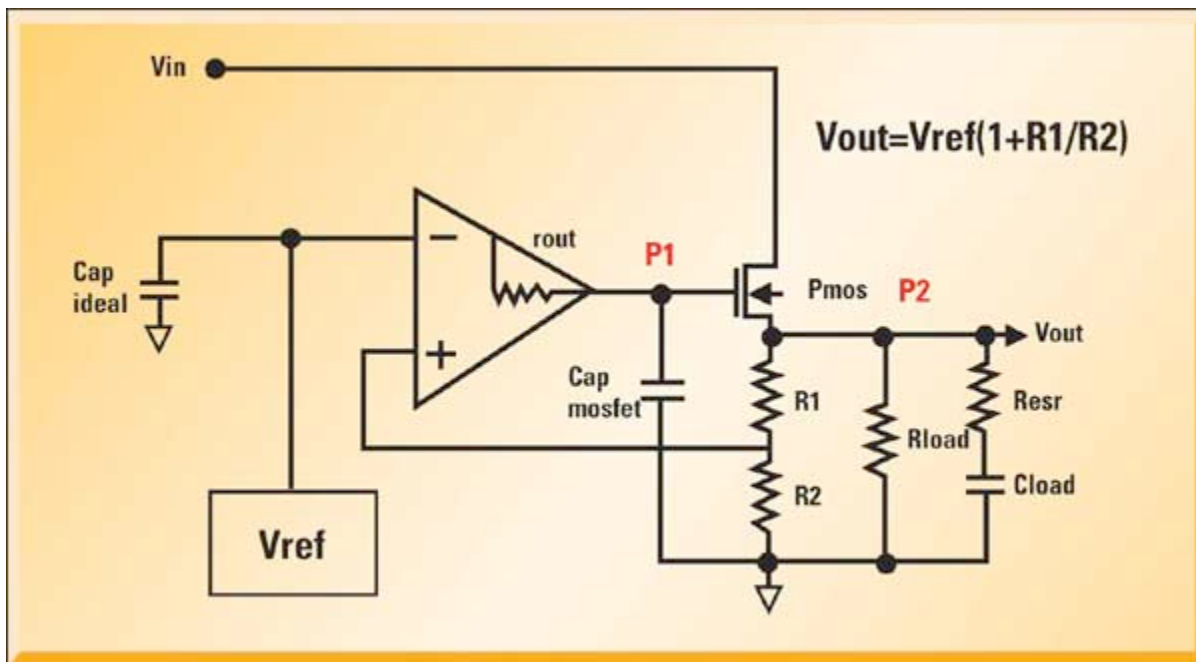

Understanding linear regulator classification

Increased efficiency is a constant demand from the design engineer. This translates into a reduction of the I_q and forward

drop voltage. As manufacturers improve these figures of merit of the linear regulator, it has undesired side effects on other characteristics. General-purpose linear regulators are designed such that they can offer the best all-around performance possible. Characteristics which often oppose each other are weighted evenly. Package selection is primarily decided on cost and wide market acceptance.

Digital linear regulators

Digital linear regulators are designed to support the main digital cores of a system. Modern DSPs and microcontrollers have to work with rapid efficiency and often high current requirements.

Emerging markets that require wireless standards require large amounts of filtering. This puts tremendous strain on the digital processing cores in terms of software loading which translates into demanding and lightning-quick responses from the power management devices. These functions drive the main characteristics that are important for digital loads. Line and load regulation/ transients are primary functions. These parameters, though they are not often easy to find in the datasheets, are stated in two ways: percent deviation of V/I or actual V/I values. These should be referenced to a load current or change in input voltage.

Battery-operated and low-power

Systems have long periods of non-operation. Digital linear regulators are designed to go to sleep during these periods, but start up rapidly when needed. During the sleep mode all of the main operations of the linear regulator — including the band gap — are switched off. It is critical that fast turn-on times do not cause excessive overshoot. Overshoot and the ability of the linear regulator to cope with overshoot are linked to I_q . With decreasing I_q , it is a challenge to maintain or improve this.

What is needed is the ability to drive internal capacitance nodes rapidly and have available current to do it. As we further reduce the available current to drive this, the linear regulator's ability to react is reduced.

Assuming that you do design a fast enough circuit and there is overshoot, one way to overcome this is by using a capacitor to dampen it. Consequently this makes the capacitance load higher and creates the demand for higher I_q .

Analog/RF linear regulators

Analog linear regulators are mainly driven around the air interface requirements. The air interface is the Achilles's heel of portable communications, as the signal is highly susceptible to noise and attenuation. So when considering an analog linear regulator, it is important that the device itself does not add further noise to the wanted signal and that it suppresses noise from other generating sources. Analog regulators need good noise figures which are measured in V_{rms} and suppression, which is PSRR (power supply rejection ratio), measured in dBs.

Noise reduction

The band-gap reference and the pass transistor are the main sources of noise. Adding an external bypass capacitor can reduce this noise, but this adds costs and increases form factor. It is possible within silicon to add internal capacitors to help, this as the noise at the transistor level is actually a combination of two factors: thermal noise and flicker noise. Electrons colliding against each other and also electrons being trapped in the SiO_2 level are the cause. PSRR is the ability of the device to suppress the unwanted noise generated by another regulating component or noise generator. This is particularly important in the analog environment, as analog IC devices are more susceptible to noise than digital.

The noise itself has a direct correlation to ground current as it is a factor of the drive to the transistors. The lower the drive current in the Mosfets, the worse the flicker and thermal noise. Lower drive translates once again into lower I_q .

So when selecting linear regulators, it is important to review the product details to evaluate the overall performance needed to your unique application.

To learn more about power, visit AnalogU.national.com

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated