

48V to 24V GaN Buck Converter Industrial Power Supply Reference Design



Description

This reference design is designed for high efficiency and small form factor. The design showcases the LMG708B0 Gallium Nitride (GaN) synchronous buck converter and operates over an input voltage range of 44V to 52V to deliver a 24V at 9.5A output.

The design uses a printed circuit board with less than 34.6cm², which can be used to drive a 200W humanoid robot hand demo from a 48V battery.

Resources


PMP31431	Design Folder
LMG708B0	Product Folder
TLV3401	Product Folder

Features


- Peak efficiency of 97.7%
- Adjustable current limit
- Forced pulse width modulation (PWM) or diode emulation
- Current monitoring
- Integrated GaN field effect transistor (FET)

Applications


- [Humanoid robot motor drive](#)

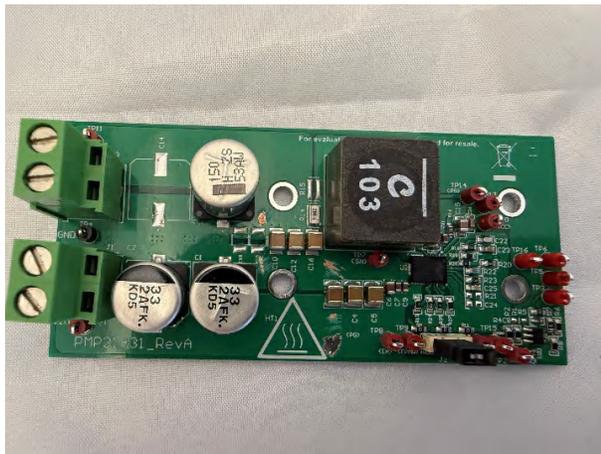

Top View of Board

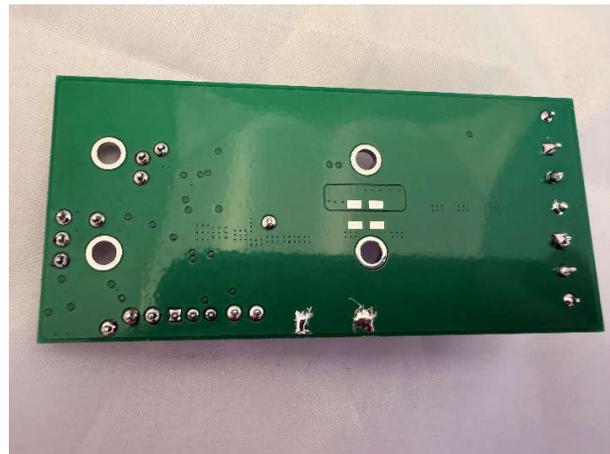

Bottom View of Board

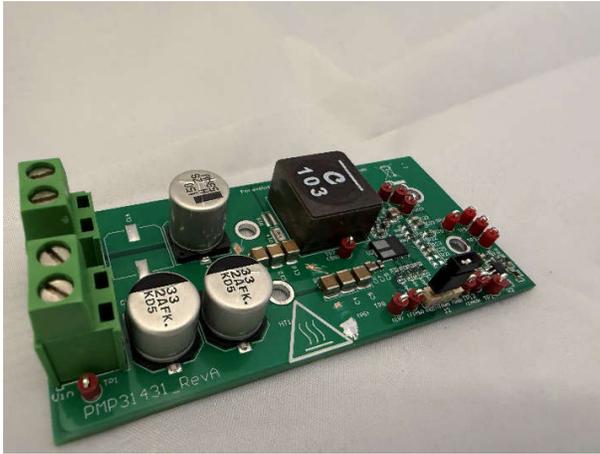

Angled View 1 of Board



Angled View 2 of Board

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Parameter	Specifications
Input Voltage Range	44V to 52V
Output Voltage	24V
Maximum Output Current	9.5A
Topology	Buck

1.2 Dimensions

The outline of the board is 86.5mm × 40mm with four copper layers. The copper thickness is 70µm on each layer.

2 Testing and Results

2.1 Efficiency Graphs

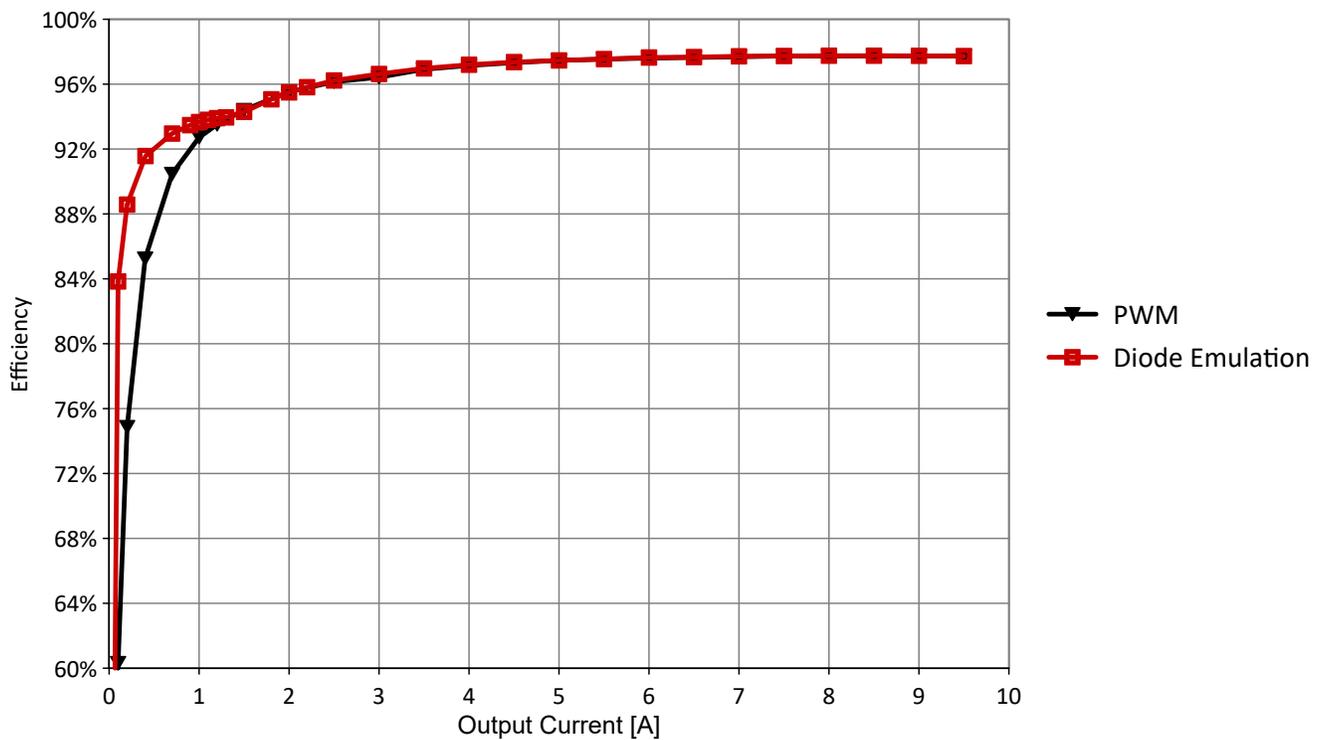


Figure 2-1. Efficiency versus Output Current

2.2 Loss Graph

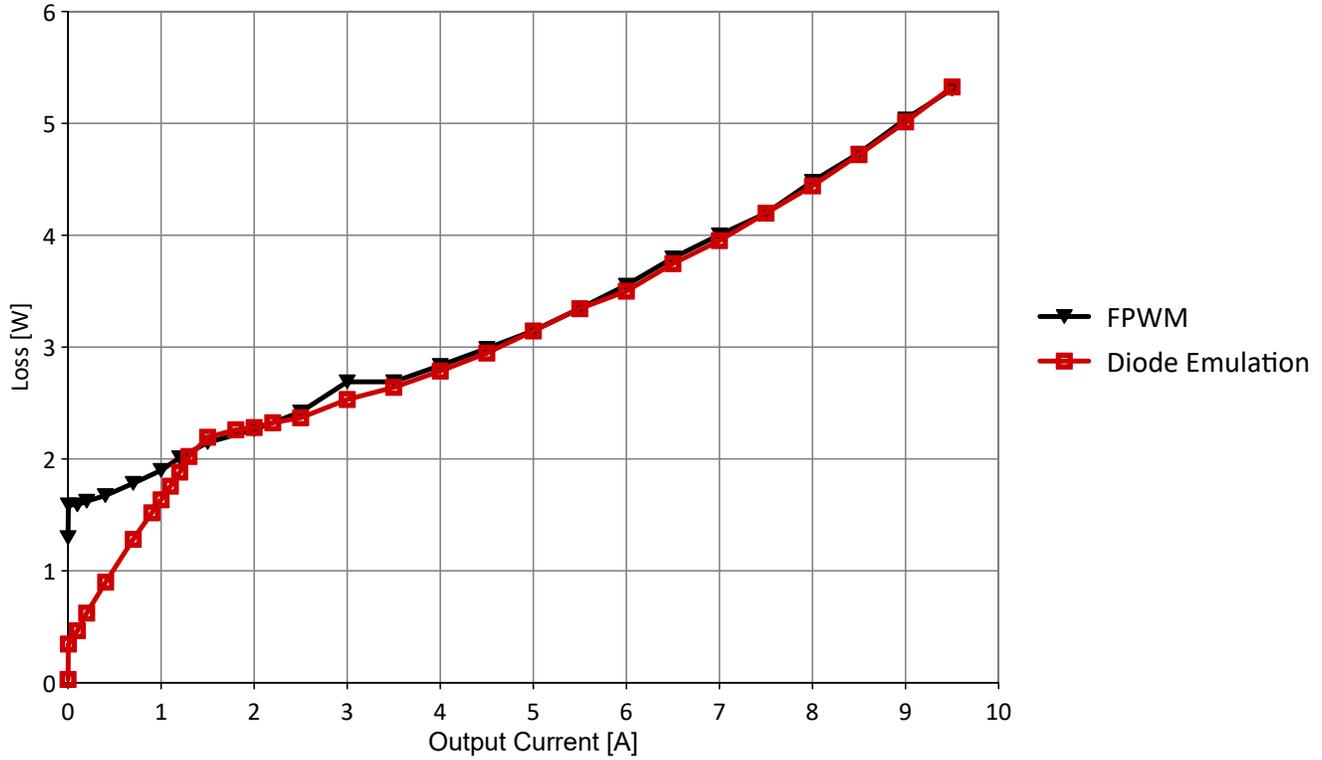


Figure 2-2. Loss versus Output Current

2.3 Load Regulation

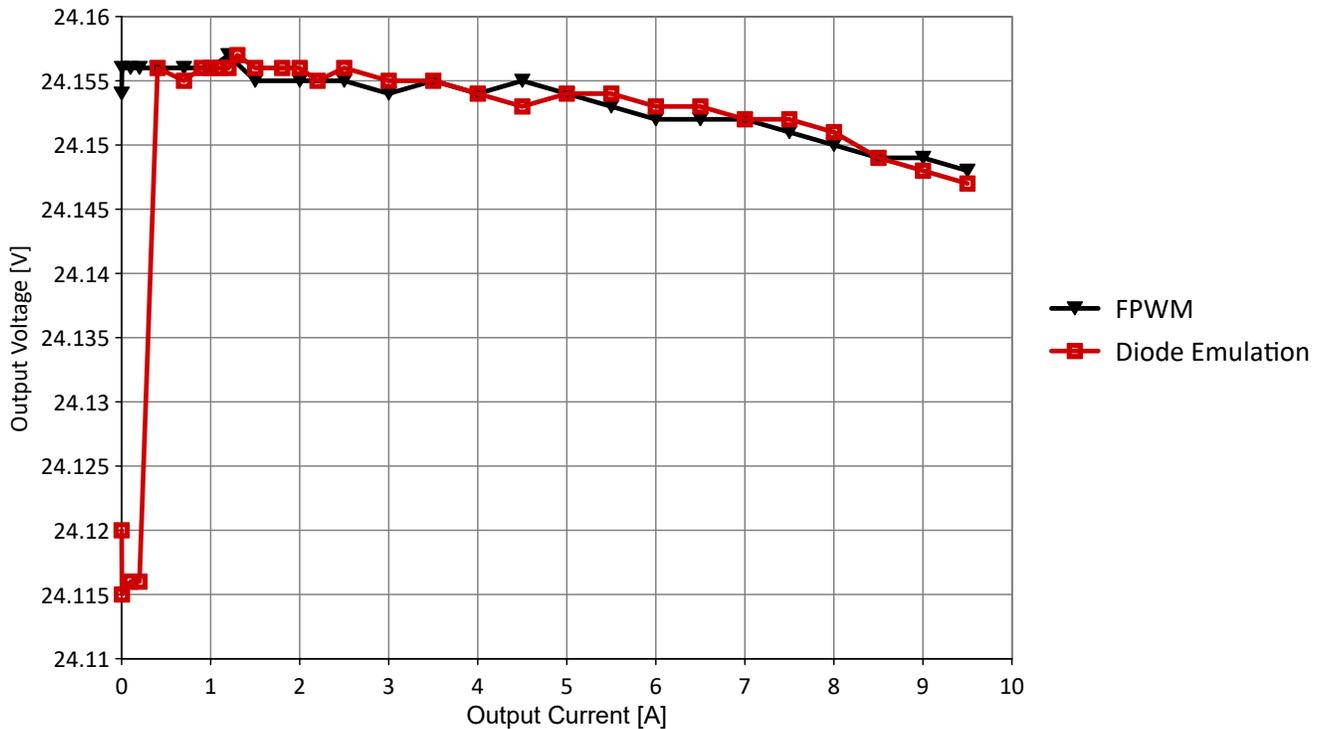


Figure 2-3. Output Voltage versus Output Current

2.4 Thermal Images

The thermal image in [Figure 2-4](#) was done after 10 minutes with 48V input voltage and 9.5A output current.

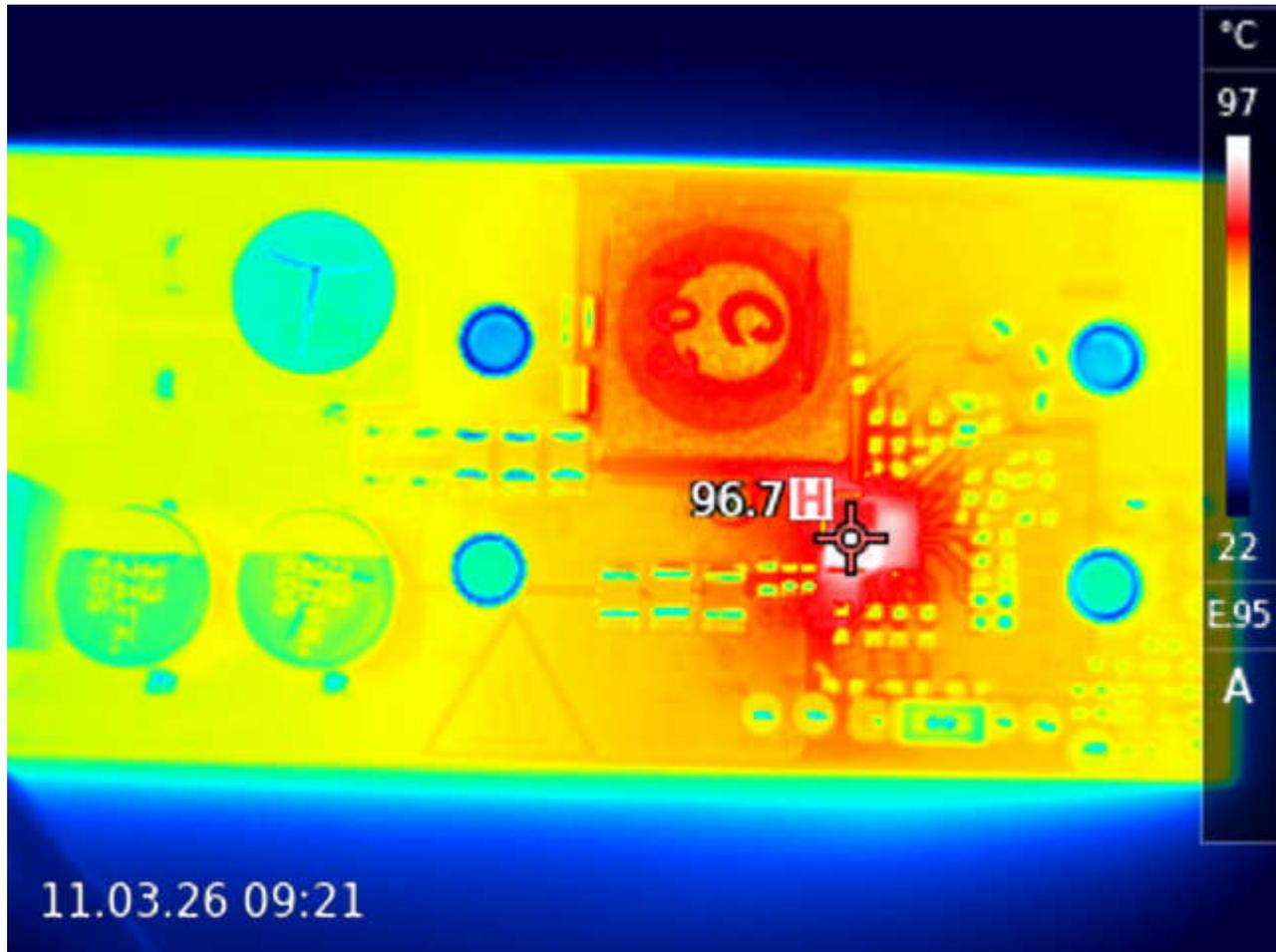


Figure 2-4. Thermal Image at 48V_{IN} and 9.5A_{OUT}

2.5 Bode Plots

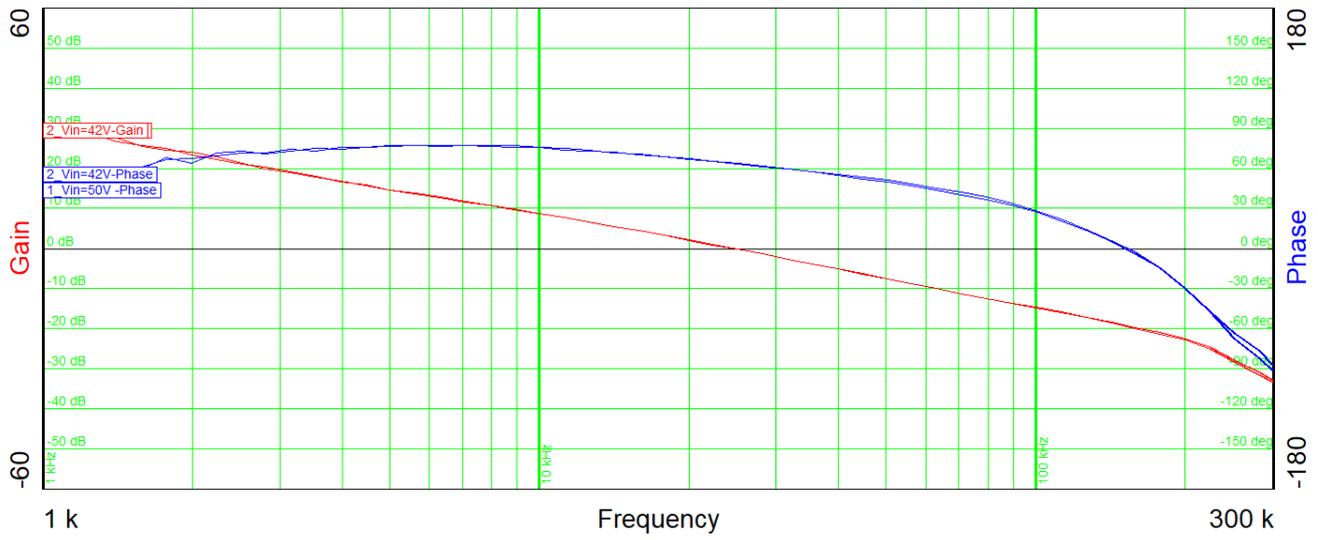


Figure 2-5. Bode Plot with $9.5A_{OUT}$

	$42V_{IN}$	$50V_{IN}$
Bandwidth (kHz)	24.5	24.4
Phase margin	64°	63.5°
Slope (20dB/decade)	-1.18	-1.17
Gain margin (dB)	-19.3	-19.5
Slope (20dB/decade)	-1.38	-1.44
Frequency (kHz)	152	151

3 Waveforms

All waveform images were captured with 48V input voltage.

3.1 Switching

3.1.1 9.5A Output Current

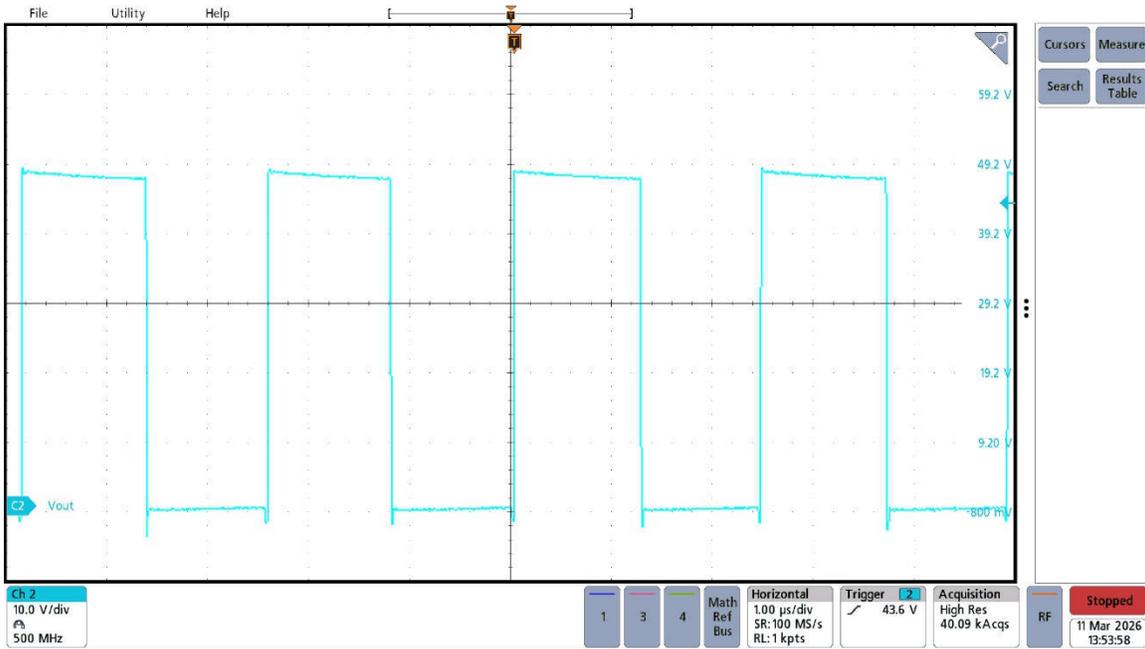


Figure 3-1. Switching With 1µs/div

Figure 3-2 displays the same measurement as in Figure 3-1 with a different time base.

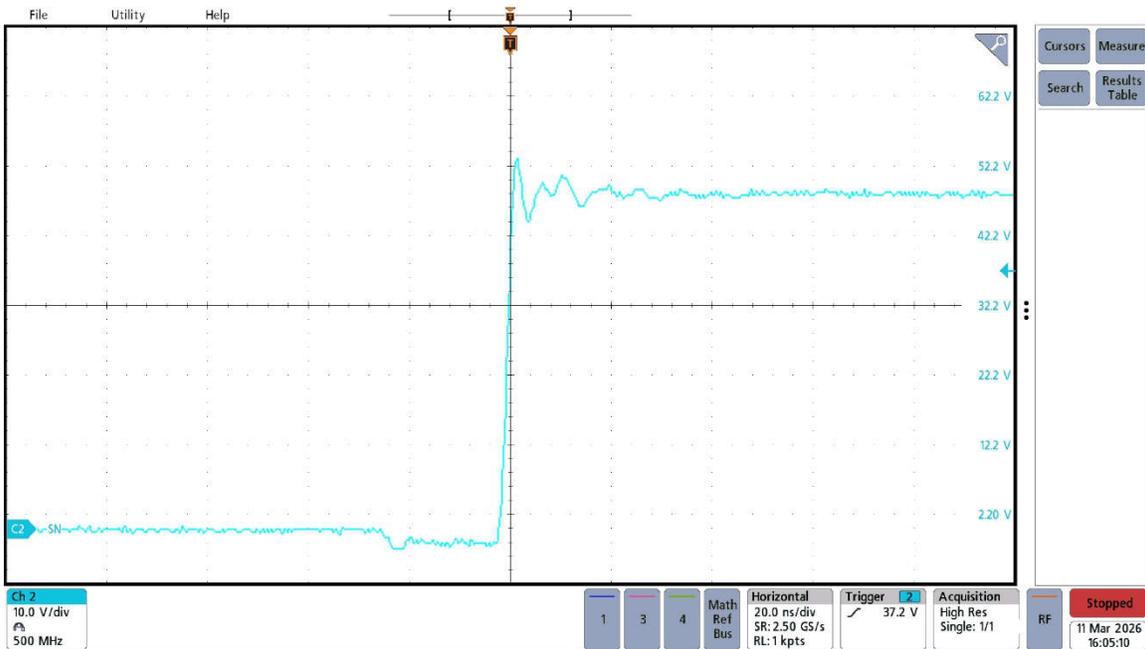


Figure 3-2. Switching with 20ns/div

3.1.2 No Load

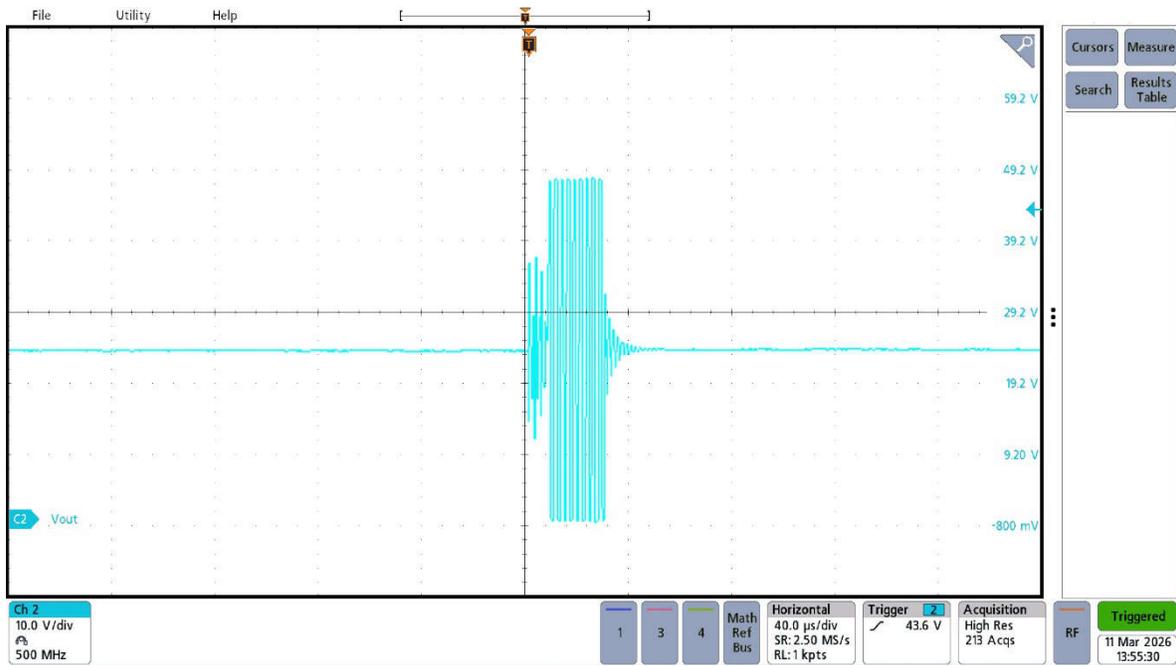


Figure 3-3. Switching without Load and 40µs/div

3.2 Output Voltage Ripple

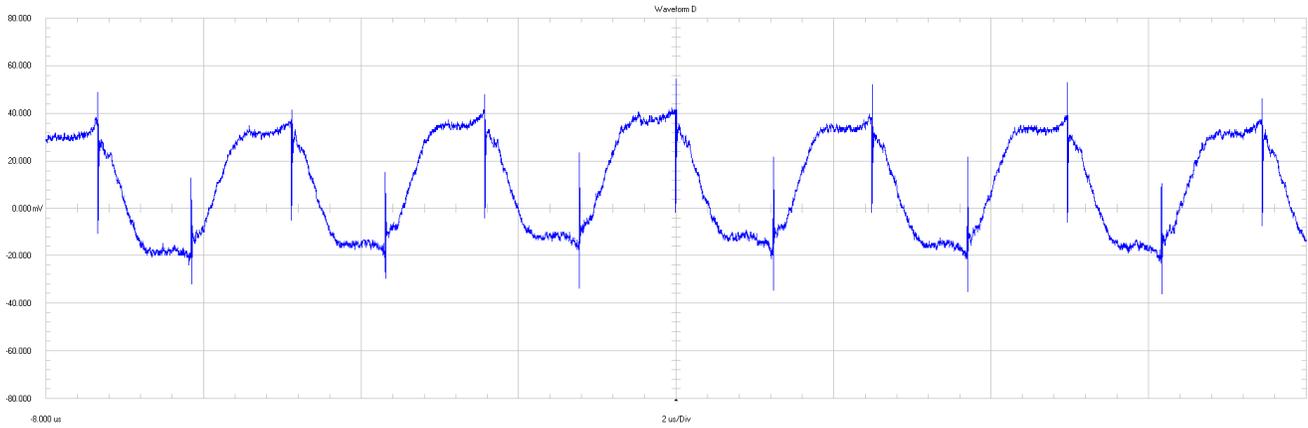


Figure 3-4. Output Voltage Ripple with 9.5A Output Current (20mV/div; 20MHz Bandwidth)

3.3 Input Voltage Ripple

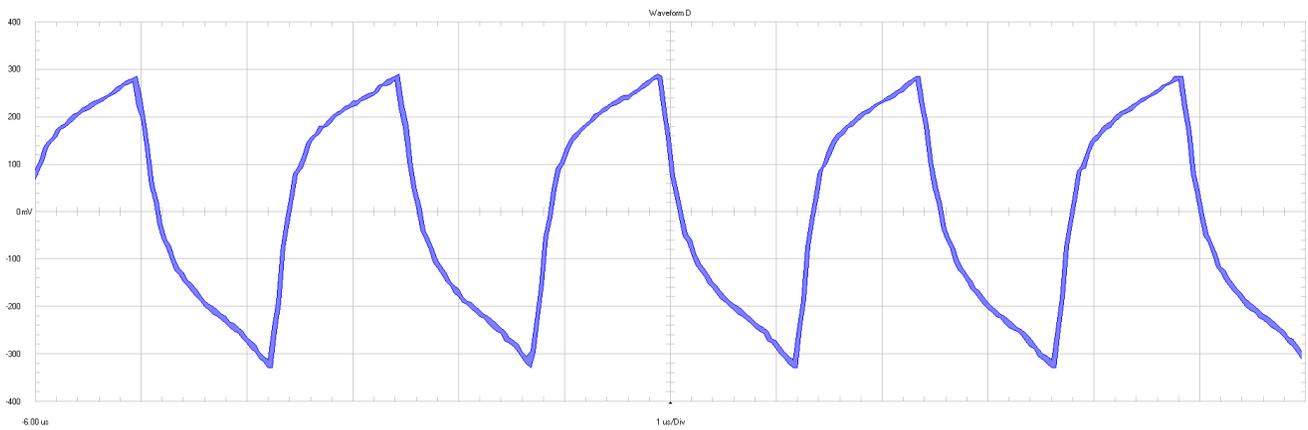


Figure 3-5. Input Voltage Ripple with 9.5A Output Current (100mV/div; 20MHz Bandwidth)

3.4 Load Transients

3.4.1 4.5A to 9A Output Current

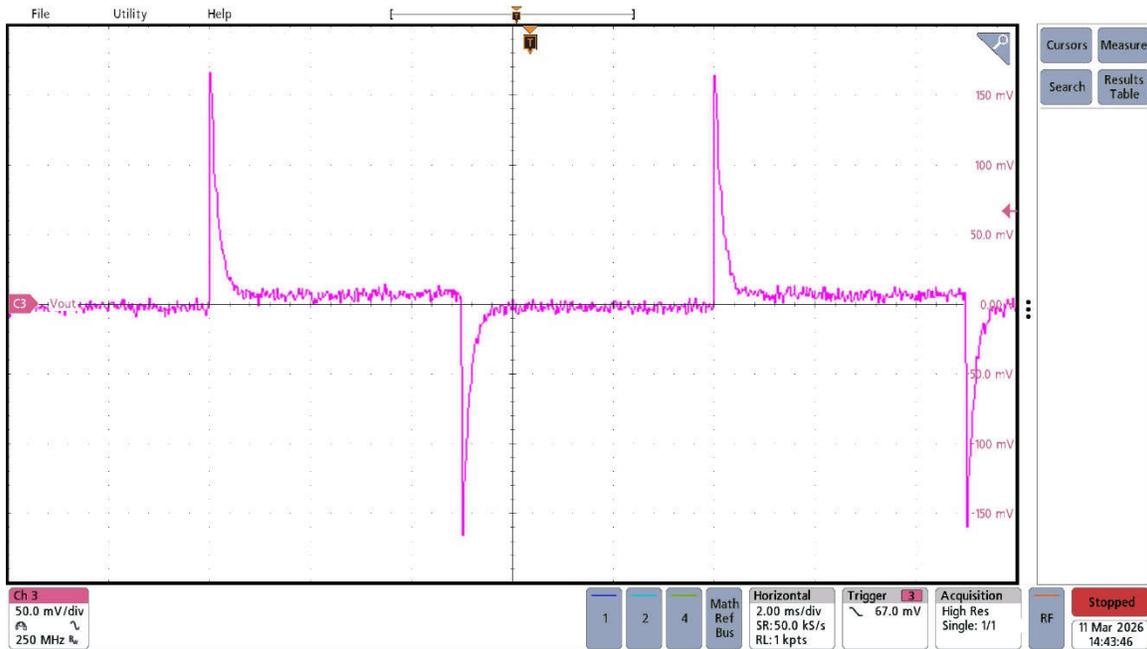


Figure 3-6. Load Transient 4.5A to 9A 50mV/div and 2ms/div

3.4.2 0A to 9A Output Current

3.4.2.1 FPWM Mode

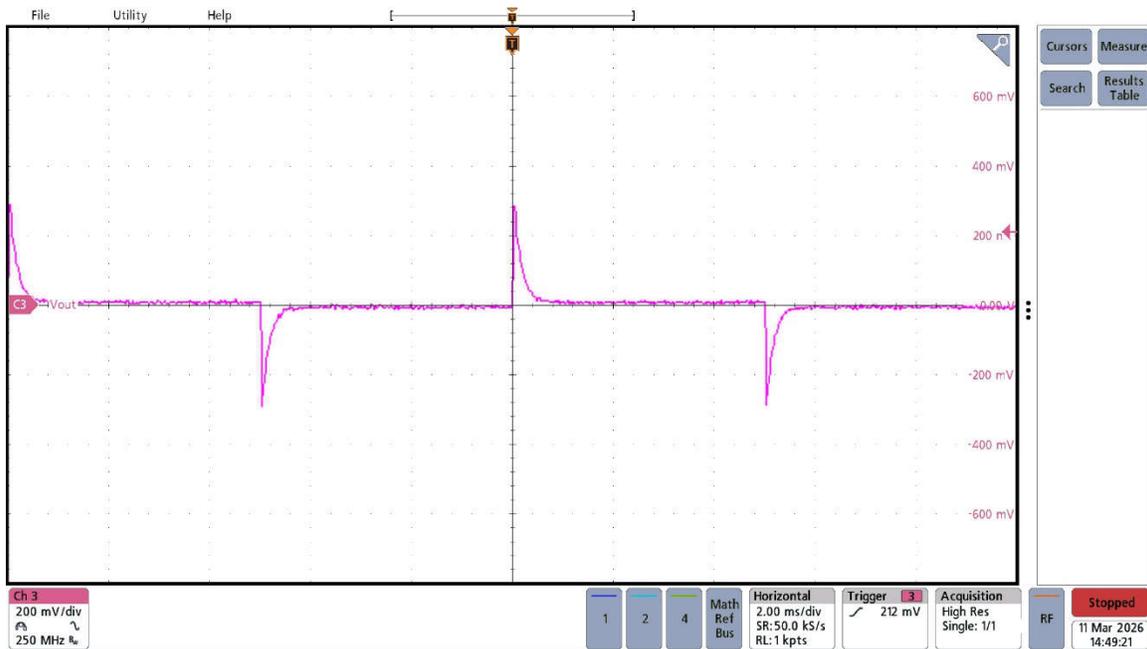


Figure 3-7. Load Transient 0A to 9.5A FPWM Mode (200mV/div, 2ms/div)

3.4.2.2 Diode Emulation Mode

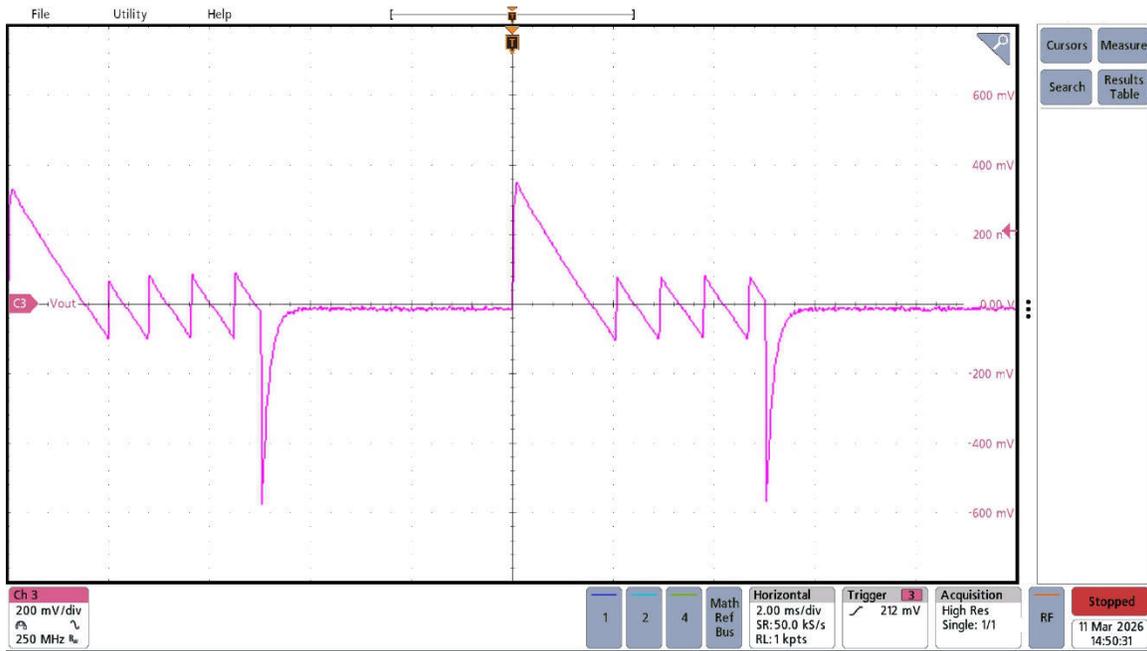


Figure 3-8. Load Transient 0A to 9.5A Diode Emulation Mode (200mV/div, 2ms/div)

3.5 Start-up Sequence

3.5.1 Start-up into 9.5A Output Current

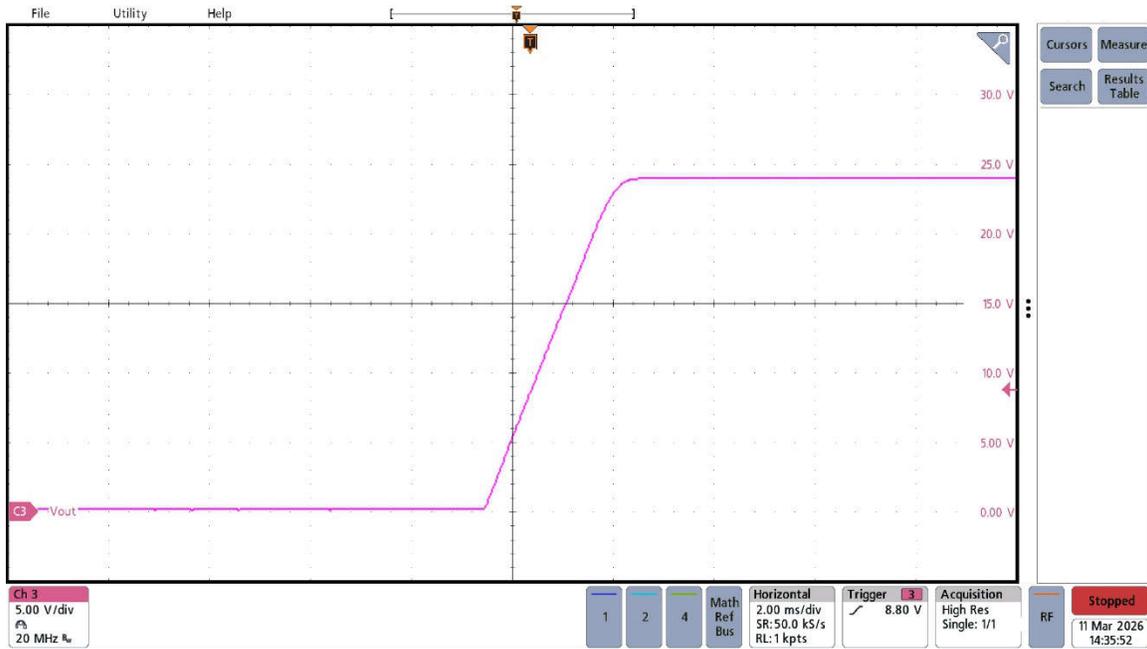


Figure 3-9. Start-up into 9.5A Output Current

3.5.2 Start-up without Load

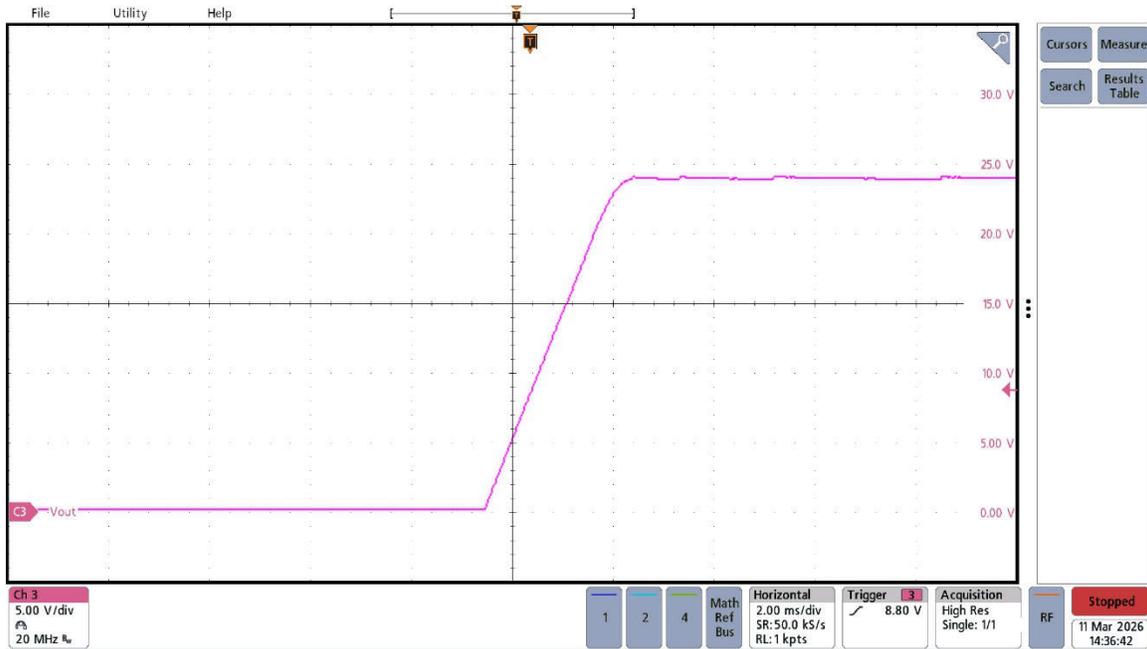


Figure 3-10. Start-up without Load

3.6 Shutdown Sequence

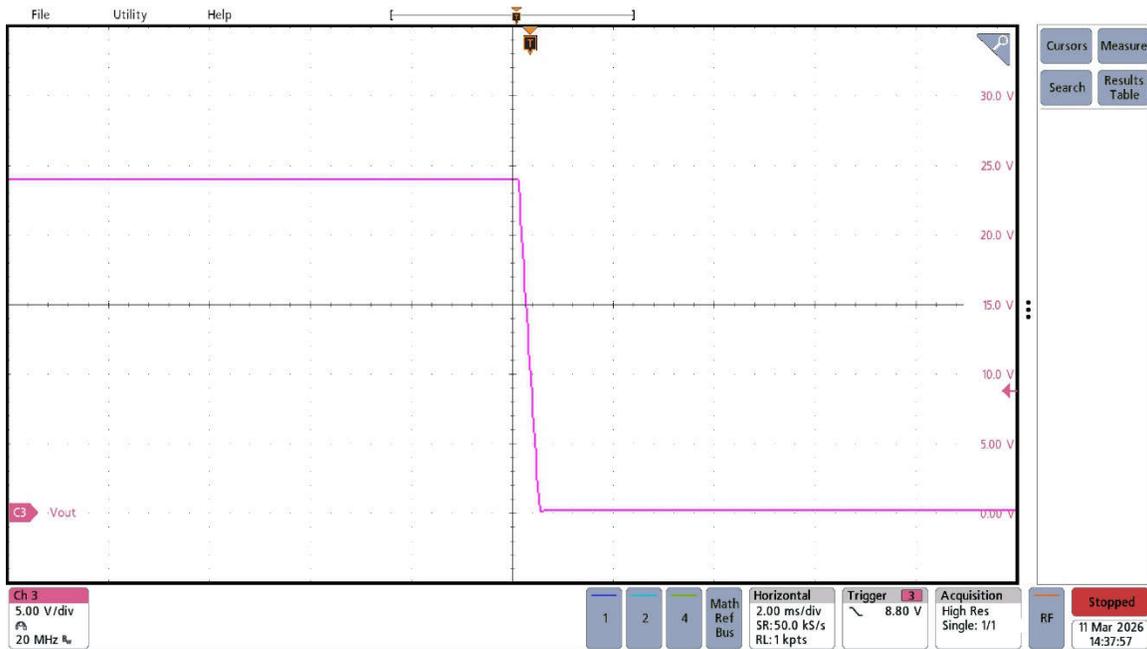


Figure 3-11. Shutdown from 9.5A Output Current

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025