

## **IBIS models for LVDS buffers in ADS528x and AFE5805**

Texas Instruments  
Dec 9, 2007

## How to use the models:

1. **Choose the LVDS drive current setting.** The various current settings are 3.5 mA (default), 0.5 mA, 1.5 mA, 2.5 mA, 4.5 mA, 5.5 mA, 6.5 mA, 7.5 mA. The selected setting can be chosen in HSPICE through the keyword MODEL. For example, the 3.5 mA drive is chosen as MODEL = "lvds\_obuf\_3.5". Although models have been provided for all these current settings, it is recommended that current settings lower than 1.5 mA not be used.
2. **Choose the LVDS internal termination setting.** The various internal termination settings are "None" (default), 260 Ohm, 150 Ohm, 94 Ohm, 125 Ohm, 80 Ohm, 66 Ohm and 55 Ohm. Once chosen, the appropriate termination should be added as a resistor of the corresponding value between the positive and negative outputs of the IBIS model for the LVDS buffer.
3. **Choose the package.** These IBIS models can be used for the any of the following devices – ADS5281IPFP (80-pin TQFP), ADS528xIRGC (64-pin QFN) or AFE5805ZCF (135-ball BGA). The values of R\_pkg, L\_pkg and C\_pkg for all these three package options are indicated in the IBIS model files.
4. **Choose the IBIS file for use in simulation.** There are three ibis files – lvds\_100.ibs, lvds\_75.ibs and lvds\_50.ibs. These correspond to the three values of loading (100, 75 and 50 Ohm) for which the models have been developed. To determine which one is to be used in a simulation, compute the effective resistive loading on the LVDS buffer. For example, if an internal termination setting of 260 Ohm is used, and the termination at the receiver is 100 Ohm, then the effective resistive loading is 260 Ohm in parallel with 100 Ohm, which is 72.2 Ohm. Choose the file that corresponds to the loading closest to the computed value ( 72.2 Ohm). So for this case, choose the file lvds\_75.ibs. If the internal termination was set to "None" and a 100 Ohm termination was used at the receiver, then the model of choice would have been in lvds\_100.ibs.

The syntax for instantiating the buffers in HSPICE, with the output terminals as LOUTP, LOUTM and input terminals as HI, LO is as follows:

```
BoutputP puP pdP  LOUTP  HI  FILE = "lvds_75.ibs"  MODEL = "lvds_obuf_3.5" TYP=typ POWER=ON
BUFFER = OUTPUT RAMP_RWF = 1 RAMP_FWF = 1 INTERPOL=2
BoutputM puM pdM  LOUTM  LO  FILE = "lvds_75.ibs"  MODEL = "lvds_obuf_3.5" TYP=typ POWER=ON
BUFFER = OUTPUT RAMP_RWF = 1 RAMP_FWF = 1 INTERPOL=2
```

In the above statements, puP, pdP and puM, pdM are the internal pull-up and pull-down nodes of the P and M respectively.

To further include an internal termination of 260 Ohm, add the following line:  
RTERM LOUTP LOUTM 260

**Note:** HI and LO are complementary inputs to the buffer and have logic levels of 0V (for low) and 1.8V (for high). In HSPICE, they could be defined as follows:


```
VLO LO 0 PULSE(0 1.8 1e-10 1e-10 1e-10 9e-09 20e-09)
VHI HI 0 PULSE(1.8 0 1e-10 1e-10 1e-10 9e-09 20e-09)
```

## Method of modelling the LVDS buffer through IBIS

Since the LVDS buffer has differential inputs and outputs, some additional considerations are involved while modeling it through IBIS.


### LVDS buffer architecture

The structure of the LVDS buffer is shown in Figure 1. HI and LO refer to the differential input to the buffer. Voltage levels of 0 Volts and 1.8 Volts correspond to logic levels of '0' and '1' at HI and LO. LOUTP and LOUTM are the differential output of the buffer. The buffer consists of two current sources (one NMOS and one PMOS) and a set of four switches to change the direction of the current flowing into the external load.

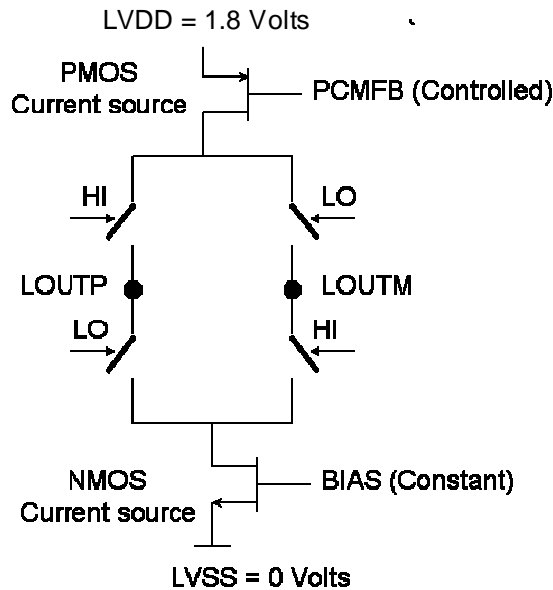

**Figure 1.** LVDS buffer architecture

While the NMOS current source is a constant current source (its value set by one of the four current mode settings), the PMOS current source is controlled through a feedback loop as shown in Figure 2.

 


**Figure 2.** Controlling the PMOS current source

The PMOS current source is controlled so as to maintain the output common mode voltage of the buffer equal to a reference voltage of 1.2 Volts.


### Pulldown and Pullup V-I tables

Since the LVDS buffer does not have a tristate, the power and ground clamp data are merged into the pullup and pulldown tables. The switches are controlled using HI and LO and the voltage at LOUTP is swept from  $-VDD$  to  $2*VDD$ . The setup for the pulldown data is as shown in Figure 3. A load resistor connects LOUTM to the common mode voltage of  $VBG=1.2$  Volts. In Figure 3, this resistor is shown to be 50 Ohm, which corresponds to a differential loading of 100 Ohm between LOUTP and LOUTM. The models generated with this loading therefore comprise the file lvds\_100.ibs. Similarly, models in files lvds\_50.ibs and lvds\_75.ibs are generated with resistors (as in Figure 3) of 25 Ohm and 37.5 Ohm respectively.

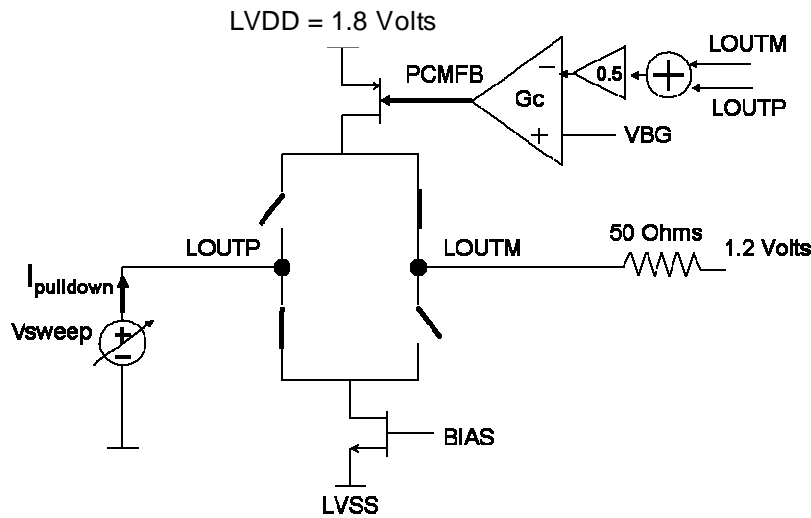

**Figure 3.** Voltage sweep for Pulldown table


The pullup data is generated by the method shown in Figure 4. Here again, the resistor on LOUTM is 50 Ohm, indicating that this is for the models in file lvds\_100.ibs.

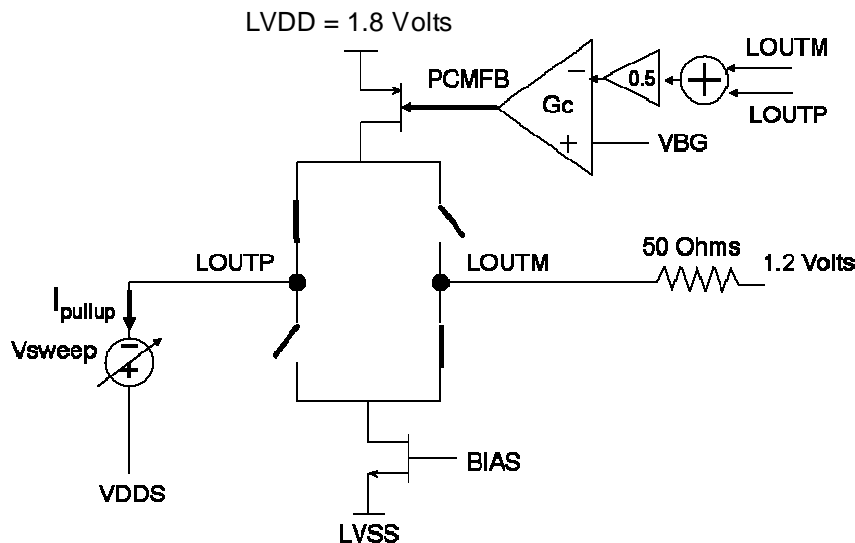

**Figure 4.** Voltage sweep for Pullup table

## Generating the V-t table


The V-t tables are generated using the setup shown in Figure 5.

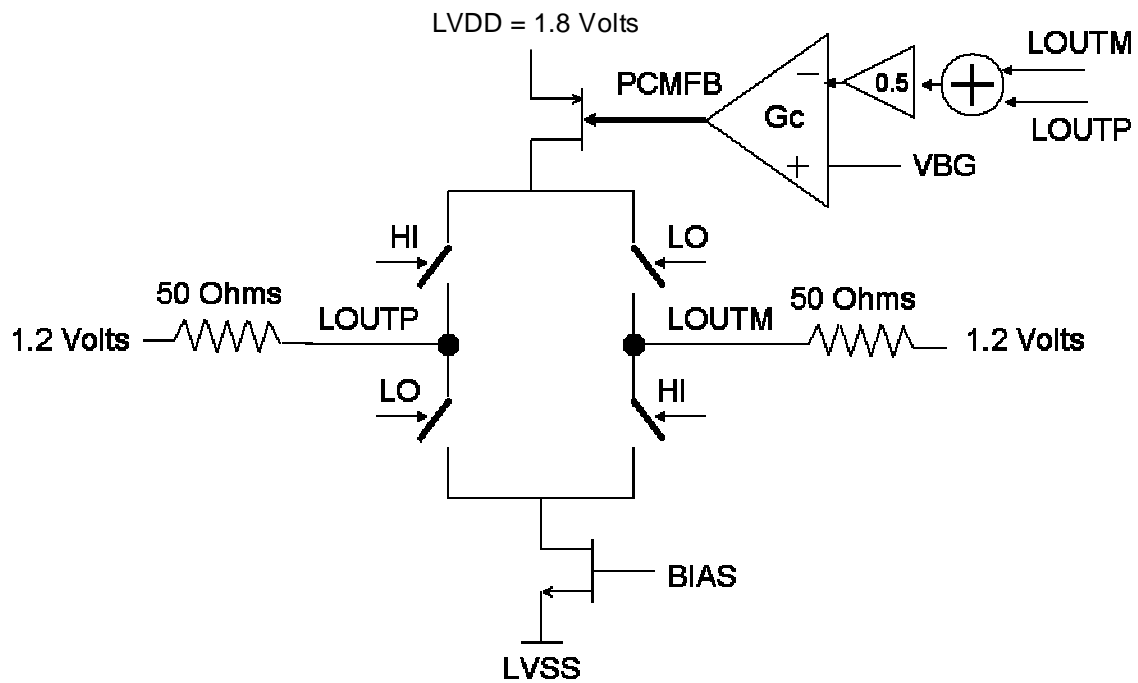


**Figure 5.** Generation of V-t table

### Comparison of IBIS model with the actual circuit

The IBIS models were generated and compared with the actual circuit through SPICE simulations. Figure 6 shows the simulation environment for the actual LVDS buffer, while Figure 7 shows the identical environment used for the IBIS model.

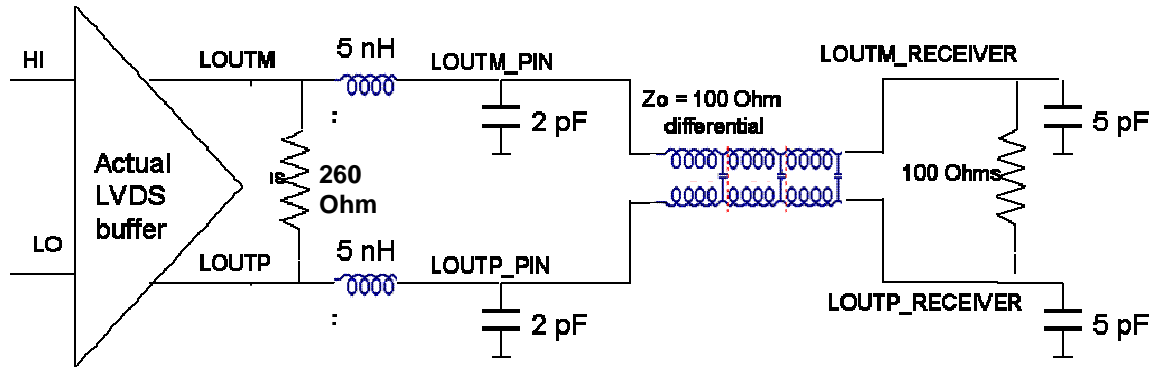


**Figure 6.** Simulation environment for the actual circuit of the LVDS buffer

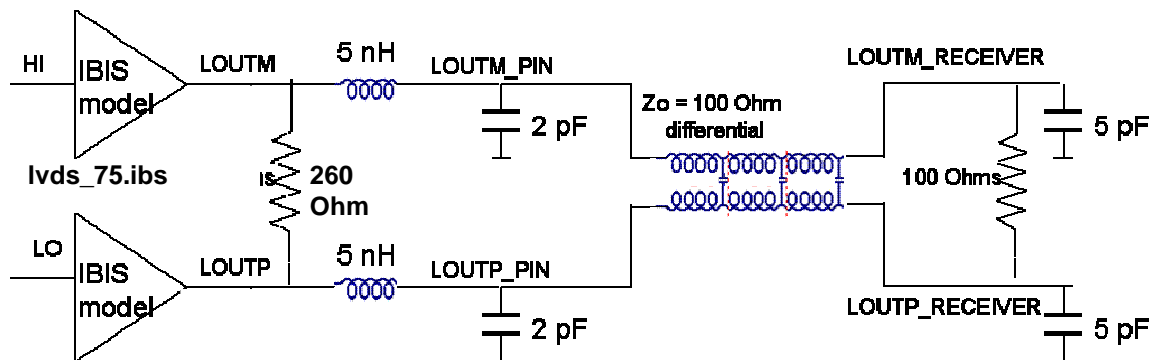

**Figure 7.** Simulation environment for the IBIS model of the LVDS buffer

Figure 8 shows a comparison of the SPICE simulation results obtained from the IBIS model with those from the actual circuit. These waveforms correspond to the difference between the voltages on nodes LOUTP\_RECEIVER and LOUTM\_RECEIVER. The delay of the transmission line was set to 100 ps.

 

**Figure 8.** Comparison of simulation results

Green Waveform– LOUTP\_RECEIVER-LOUTM\_RECEIVER (Actual circuit)

Pink Waveform– LOUTP\_RECEIVER-LOUTM\_RECEIVER (IBIS model)

As can be observed, there is a close match between the actual circuit and its IBIS model.

## MODEL SUMMARY

### Modeling conditions:

Condition	typ/ min/ max
LVDD	1.8 V/ 1.65 V/ 1.95 V
VBG (Common mode reference)	1.2 V/ 1.1 V/ 1.3 V
Junction temperature (Tj)	25/ 125/ -40 (degree C)
Process setting	nominal/ weak/ strong

### Package Characteristics:

ADS5281IPFP – 80-pin, TQFP package

Characteristics	typ/ min/ max
R_pkg:	0.5 / NA / NA
L_pkg	5 nH/ NA/ NA
C_pkg	2 pF/ NA / NA

ADS5281IRGC, ADS5282IRGC – 64-pin, QFN package

Characteristics	typ/ min/ max
R_pkg:	0.5 / NA / NA
L_pkg	2 nH/ NA/ NA
C_pkg	0.3 pF/ NA / NA

AFE5805ZCF – 135-ball, BGA package

Characteristics	typ/ min/ max
R_pkg:	0.3 / NA / NA
L_pkg	5 nH/ NA/ NA
C_pkg	1 pF/ NA / NA

### Quality Verification:

The created IBIS models are verified as follows:

1. Visual check of each characteristics using the s2iplt tool
2. Syntax check by IBISCHK4
3. Behavior of IBIS models and actual circuit compared using SPICE



## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>	Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Low Power Wireless	<a href="http://www.ti.com/lpw">www.ti.com/lpw</a>	Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2007, Texas Instruments Incorporated