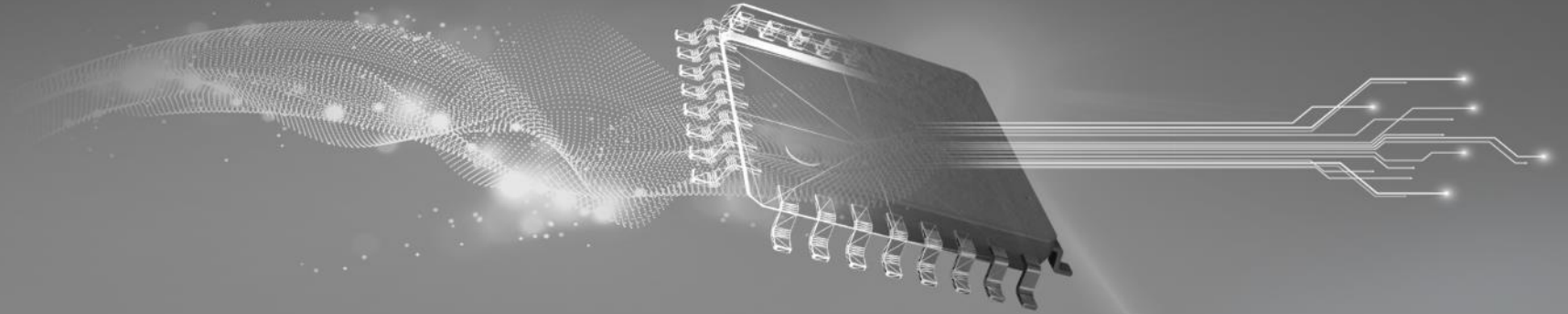


TI TECH DAYS




Precisely measuring current in 48-V vehicles

Dan Harmon

Current and Position Sensing


Agenda

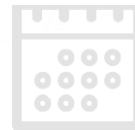

- TI Current Sensing Solutions
- 48V Current Sensing Alternatives
- Automotive 48V Applications
- Key 48V Current Sense Devices




Use the Webex Chat

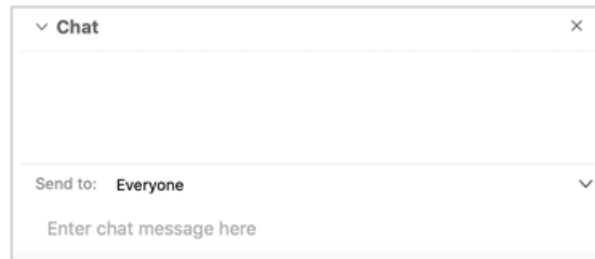

TI Current Sensing Solutions


Shunt-based Solutions

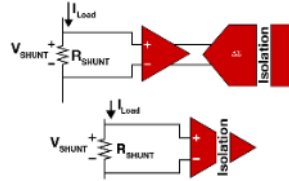


Isolated Options

Directly measures the current through a relatively small ohmic valued (shunt) resistor.

Non-Isolated Options


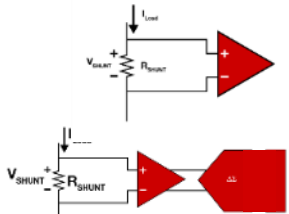


Magnetic Solutions

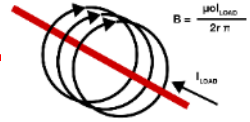

Non-invasive & Isolated

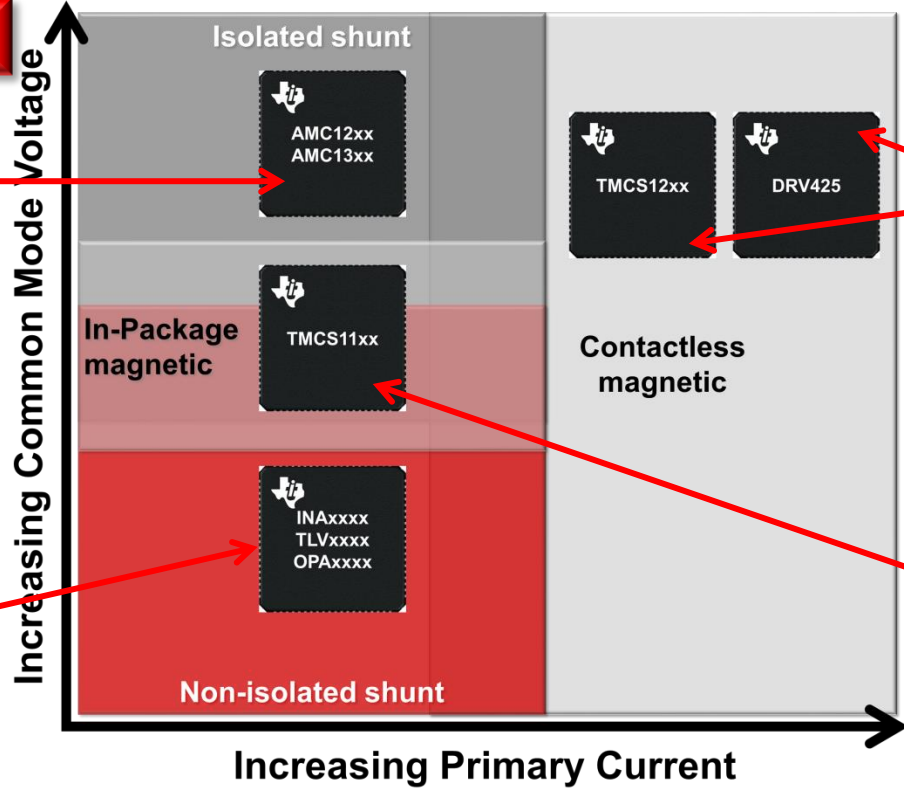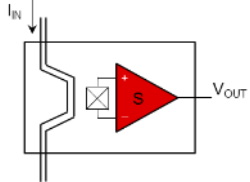Magnetic sensing indirectly measures the load current by measuring the magnetic field produced by a current running through a conductor.




Hybrid EV, Battery EV Current Sensing


DC-DC Converter	Battery Management	On-board Charging	Traction Inverter/ Motor Control	Starter / Generator
Power Stage Devices	State of Charge Devices	AC Current	Motor Current	Motor Current
<ul style="list-style-type: none"> 12V Rail: ⇒ INA190-Q1 48V Rail: ⇒ INA240-Q1 HV Rail: ⇒ DRV425-Q1 ⇒ AMC1302-Q1 Low-side monitoring: ⇒ INA181-Q1 ⇒ INA381-Q1 (OC) 	<ul style="list-style-type: none"> Bottom of Stack: ⇒ INA229-Q1 ⇒ INA226-Q1 12V Battery Top of Stack: ⇒ INA190-Q1 ⇒ INA226-Q1 48V Battery Top of Stack: ⇒ INA240-Q1 ⇒ INA229-Q1 HV Battery Top of Stack: ⇒ AMC1302-Q1 ⇒ DRV425-Q1 	<ul style="list-style-type: none"> In-package Hall current sensor ⇒ TMCS1100-Q1 	<ul style="list-style-type: none"> In-line phase current requires the ability to negate high dV/dT V_{CM}: 48V ⇒ INA240-Q1 HV ⇒ AMC1302-Q1 Low-side phase may require negative V_{CM} survivability: ⇒ INA181-Q1 ⇒ INA303-Q1 ⇒ INA281-Q1 	<ul style="list-style-type: none"> In-line phase current requires the ability to negate high dV/dT V_{CM}: ⇒ INA240-Q1 Low-side phase may require negative V_{CM} survivability: ⇒ INA181-Q1 ⇒ INA303-Q1 ⇒ INA281-Q1
Diagnostic Devices	Diagnostic Devices	PFC Current	Diagnostic Devices	Diagnostic Devices
<ul style="list-style-type: none"> 12V Systems: ⇒ INA186-Q1 48V Systems: ⇒ INA281-Q1 HV Systems: ⇒ DRV425-Q1 ⇒ AMC1302-Q1 Low-side monitoring: ⇒ INA181-Q1 ⇒ INA381-Q1 (OC) 	<ul style="list-style-type: none"> Low-side: ⇒ INA181-Q1 ⇒ INA381-Q1 (OC) 12V High-side: ⇒ INA186-Q1 48V High-side: ⇒ INA281-Q1 HV High-side: ⇒ AMC1302-Q1 ⇒ DRV425-Q1 	<ul style="list-style-type: none"> High-side In-package Hall current sensor ⇒ TMCS1100-Q1 Shunt monitoring ⇒ AMC1302-Q1 Low-side Shunt monitoring: ⇒ INA181-Q1 ⇒ INA381-Q1 (OC) 	<ul style="list-style-type: none"> Low-side DC-Link: ⇒ INA181-Q1 ⇒ INA381-Q1 (OC) 48V High-Side DC-Link: ⇒ INA281-Q1 High-side DC-Link requiring isolation: ⇒ AMC1302-Q1 ⇒ DRV425-Q1 	<ul style="list-style-type: none"> Low-side DC-Link: ⇒ INA181-Q1 ⇒ INA381-Q1 (OC) 12V High-side DC-Link: ⇒ INA186-Q1 48V High-Side DC-Link: ⇒ INA281-Q1 48V Isolated Systems ⇒ AMC1302-Q1
		DC/DC Current		
		<ul style="list-style-type: none"> HV Monitoring: In-package Hall current sensor ⇒ TMCS1100-Q1 Shunt monitoring ⇒ AMC1302-Q1 Low-side monitoring: ⇒ INA181-Q1 ⇒ INA381-Q1 (OC) 		

48V current sensing options: architecture


Current sense amplifier

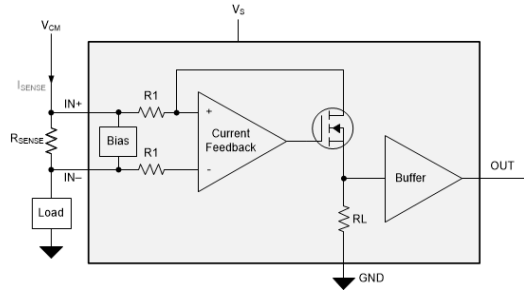


Difference amplifier

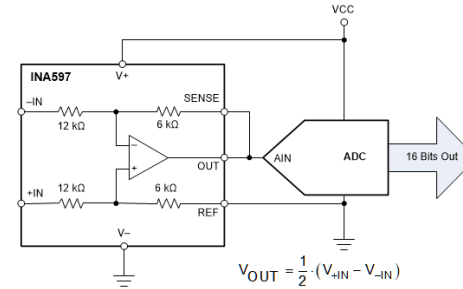

Isolated current sense amplifier

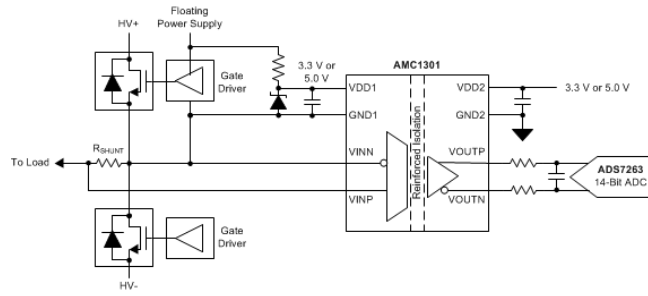

In-package Hall-effect current sensor

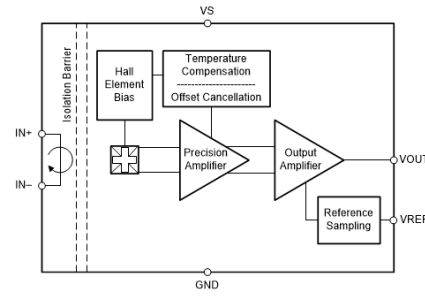

48V current sensing options: pros & cons

Current sense amplifier

Pros

- Unique floating input stage topology allows for V_{CM} to exceed and be independent of V_S
- Precision integrated gain network maximizes accuracy and minimizes drift
- Low offset enables use of low ohmic shunt resistors enabling higher current measurements and minimizing power dissipations

Cons

- Usually only offered at fixed gain options

Difference amplifier

Pros

- Tolerates large common-mode voltages (up to $\pm 275V$ with $\pm 15V$ supply)

Cons

- Resistor network loads the system; Must ensure system impedance is significantly smaller than diff amp input impedances
- Typically low gain requires additional amplifier stage to keep P_{DIS} in shunt reasonable
- Output must be managed to limit output dynamic range to protect downstream circuitry when supporting high V_{CM}

Isolated current sense amplifier

Pros

- Extends common mode capability by galvanically isolating the input stage from the output
- Enables galvanic isolation even in low voltage ($< 100V$) applications where transients exist that may require isolation
- Low offset and integrated precision gain network on input stage enable high accuracy

Cons

- Limited gain options limit shunt resistor options

In-package Hall-effect current sensor

Pros

- Extends common mode capability by galvanically isolating the input stage from the output
- Enables galvanic isolation even in low voltage ($< 100V$) applications where transients exist that may require isolation

Cons

- Current handling capability limited to 30A at 25°C
- Sensitive to stray magnetic fields that can degrade measurement accuracy


Errors in current sensing circuits

1. Offset error $\longrightarrow e_{Offset} (\%) \approx e_{V_{OS}} + e_{CMRR} + e_{PSRR}$

2. Gain error $\longrightarrow e_{Gain} (\%) \approx e_{Gain_error} + e_{Linearity} + e_{Shunt_tolerance}$

3. Application error $\longrightarrow e_{Application} (\%) \approx e_{Bias_current} + e_{Other}$

**For more info
Click to visit**

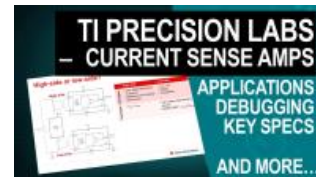



Worst-case total error – more conservative

$$\zeta_{Worst}(\%) \approx e_{V_{OS}} + e_{CMRR} + e_{PSRR} + e_{Gain_error} + e_{Linearity} + e_{Shunt_tolerance} + e_{Bias_current} + e_{Other}$$

Root-sum-square (RSS) total error – more realistic



$$\zeta_{RSS}(\%) \approx \sqrt{e_{V_{OS}}^2 + e_{CMRR}^2 + e_{PSRR}^2 + e_{Gain_error}^2 + e_{Linearity}^2 + e_{Shunt_tolerance}^2 + e_{Bias_current}^2 + e_{Other}^2}$$

Current sense amplifier option – INA293

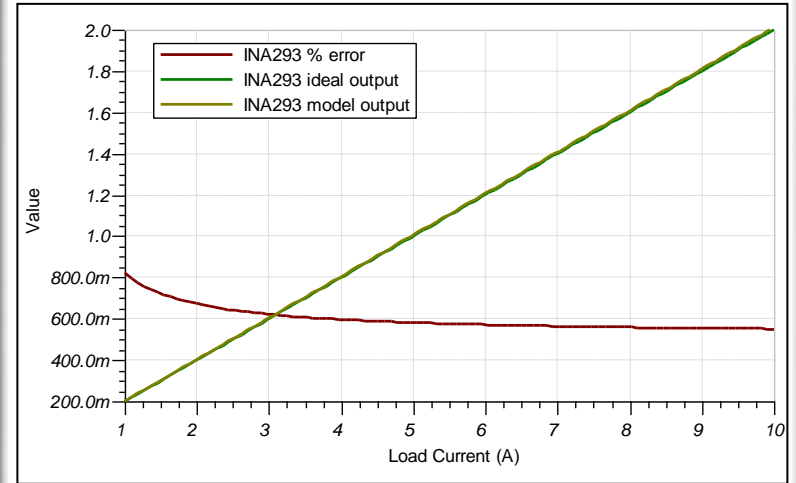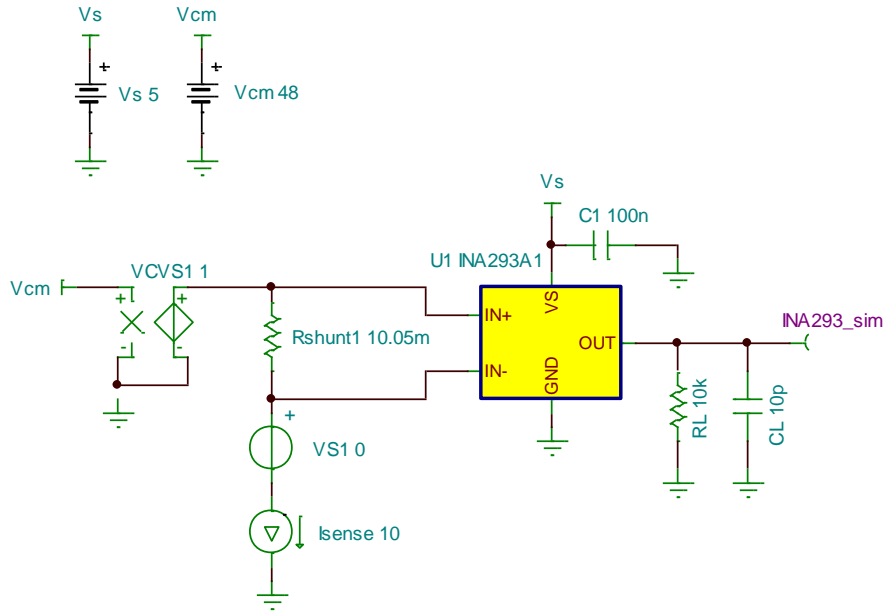



BOM Estimate		INA293
Device		\$1.05
Shunt resistor		\$0.73
Total cost with 0.5% shunt:		\$1.78
Item	Price source	
TI devices	ti.com 1k price	
Shunt resistor: 10mΩ, 0.5%, 50 PPM, 1W 2412	Digi-Key 1Ku T&R price	

Difference amplifier option – INA597

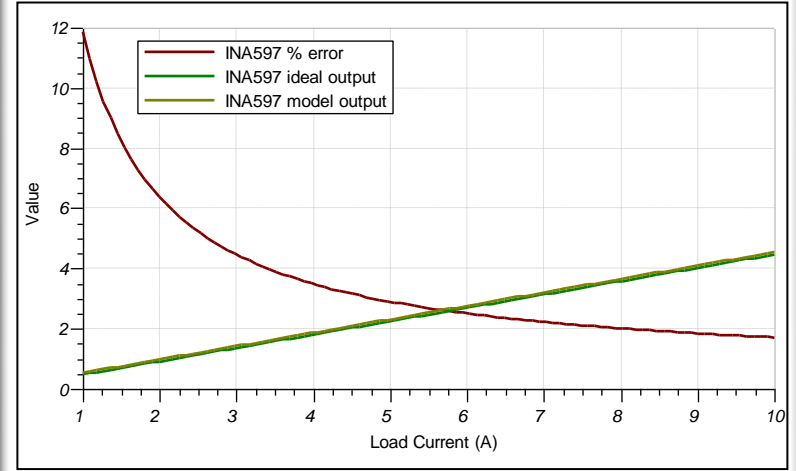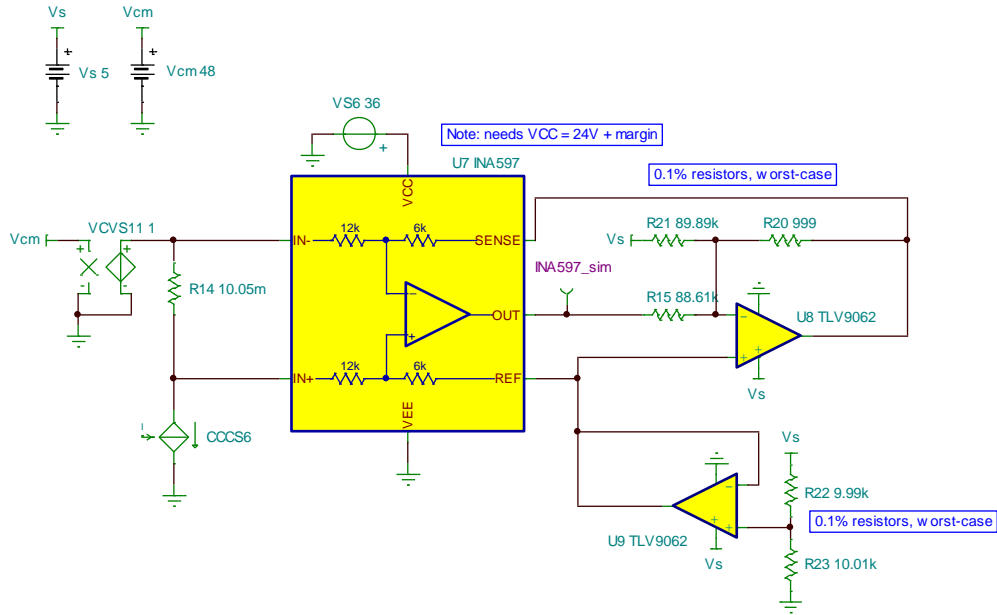



BOM Estimate		INA597		
Device		\$0.84		
Shunt resistor		\$0.73		
Increase gain stage: TLV9062		\$0.25		
		1%	0.5%	0.1%
Total for five of these resistors		\$0.08	\$0.13	\$0.18
Total cost with 0.5% shunt:		\$1.90	\$1.95	\$2.00
Item	Price source			
TI devices	ti.com 1k price			
Shunt resistor: 10mΩ, 0.5%, 50 PPM, 1W 2412	Digi-Key 1Ku T&R price			
1%, 100 PPM, 0.25W resistor	Digi-Key 1Ku T&R price			
0.5%, 50 PPM, 0603 resistor	Digi-Key 1Ku T&R price			
0.1%, 10 PPM, 0.25W resistor	Digi-Key 1Ku T&R price			

Isolated amplifier option – AMC1301

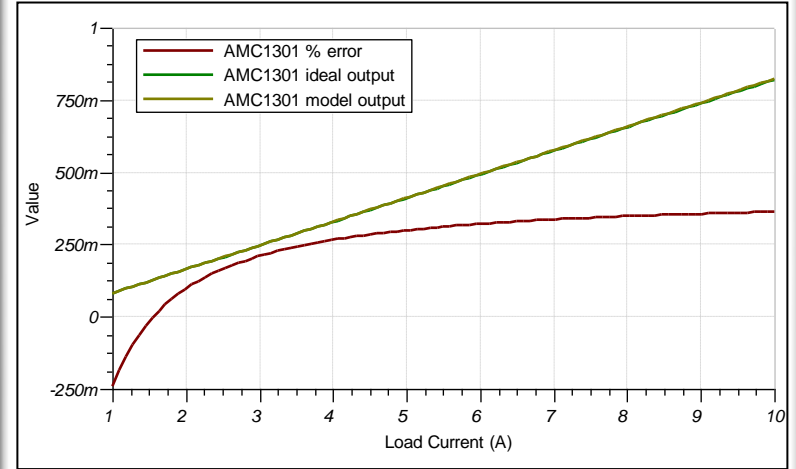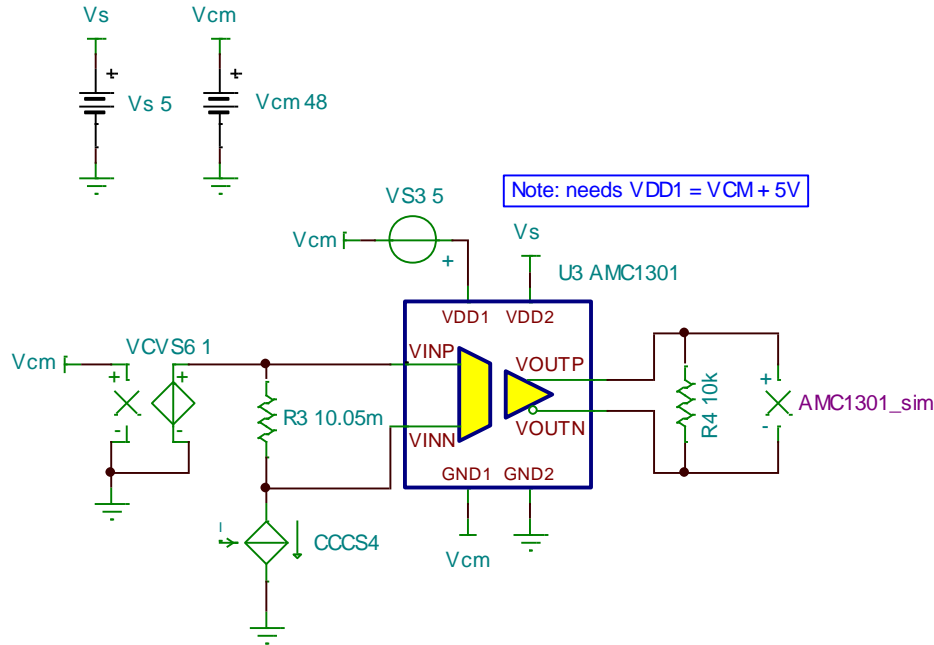


BOM Estimate		AMC1301
Device		\$2.55
Shunt resistor		\$0.73
Total cost with 0.5% shunt:		\$3.28
Item	Price source	
TI devices	ti.com 1k price	
Shunt resistor: 10mΩ, 0.5%, 50 PPM, 1W 2412	Digi-Key 1Ku T&R price	

In-package Hall sensor option – TMCS1100

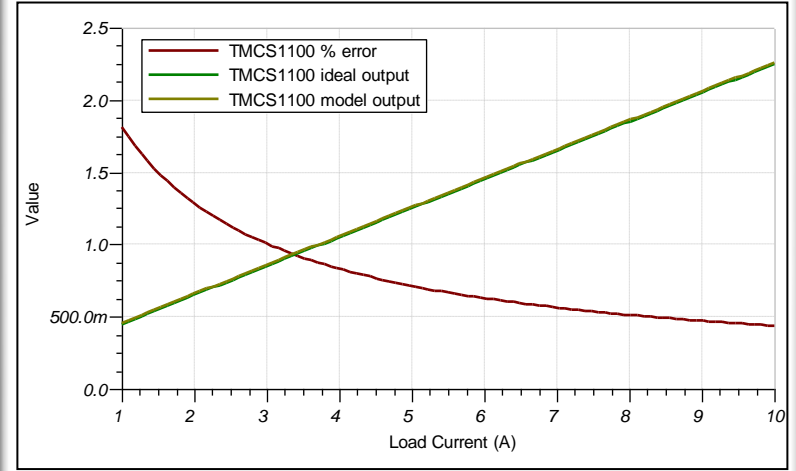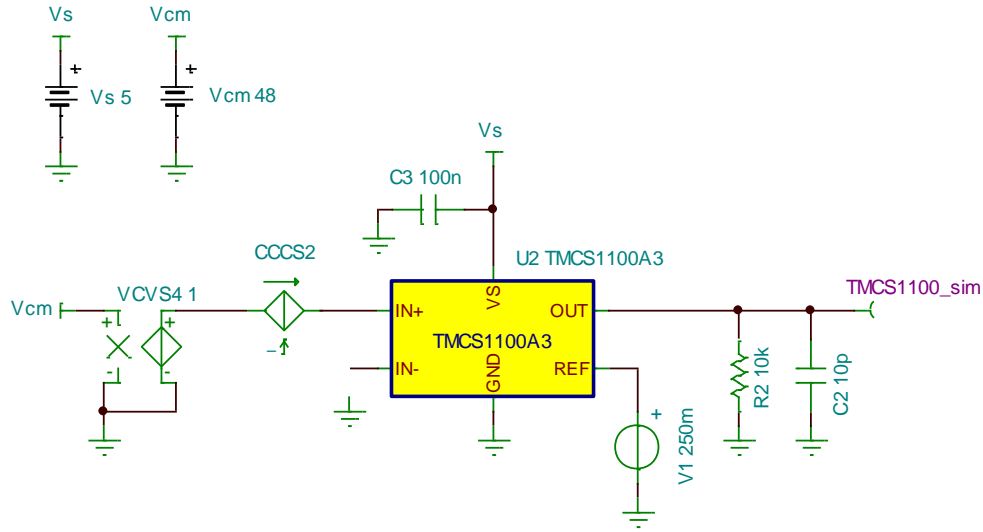

BOM Estimate		TMCS1100
Device		\$1.50
Shunt resistor		\$0.00
Total cost with 0.5% shunt:		\$1.50
Item		Price source
TI devices		ti.com 1k price

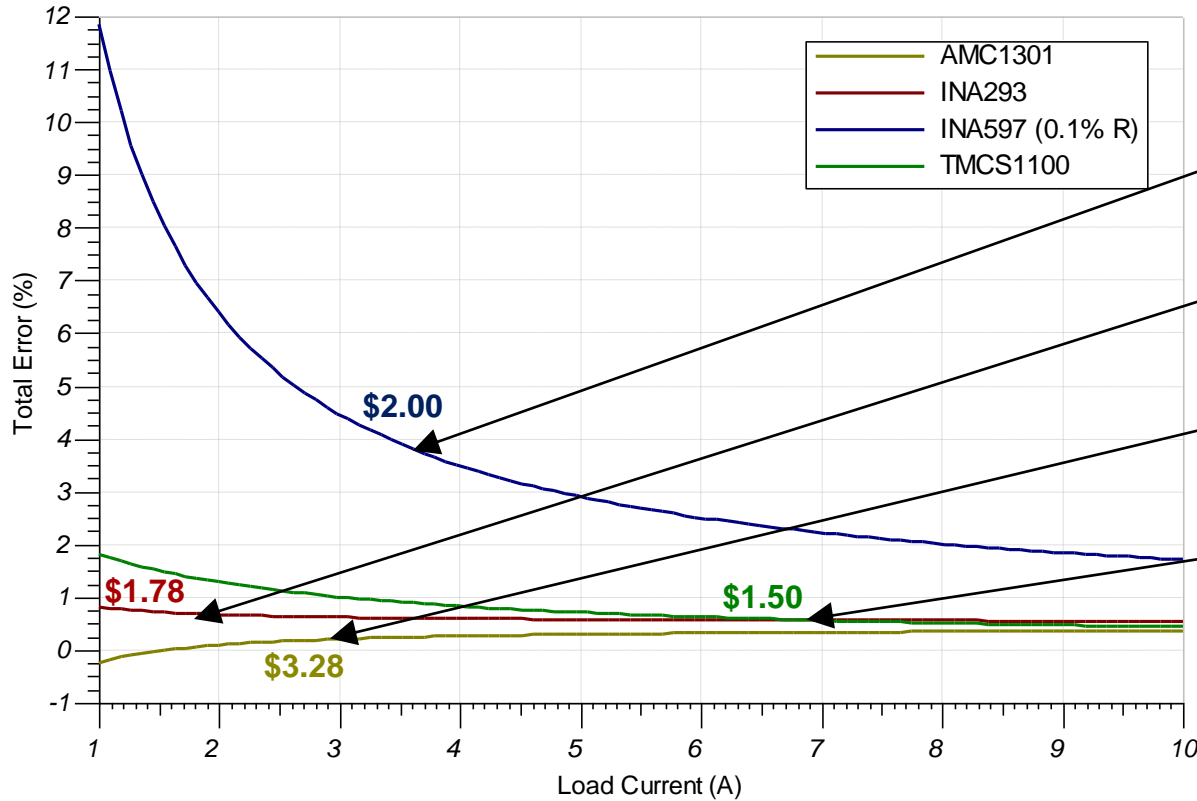48V current sensing options: DC error analysis



Note: TI SPICE models are usually designed to typical specs

DA = poor performance versus price, 2-chip solution

CSA = best overall value and simplest implementation

ISO = good performance, but at a higher cost

MCS = good value, but sensitive to magnetic/mechanical design


Error tool on ti.com

Current sense amplifier error analysis INA229-Q1 ?

	Min	Max	Range
Ideal shunt resistor		<input type="text" value="2"/> mΩ	0.001 to 100 mΩ
Sensed current range	<input type="text" value="1"/>	- <input type="text" value="100"/> A	0.0001 to 100 A
Supply voltage		<input type="text" value="5"/> V	2.7 to 5.5 V
Common-mode voltage		<input type="text" value="48"/> V	-0.3 to 85 V
Operating temperature		<input type="text" value="125"/> °C	-40 to 125 °C

Update

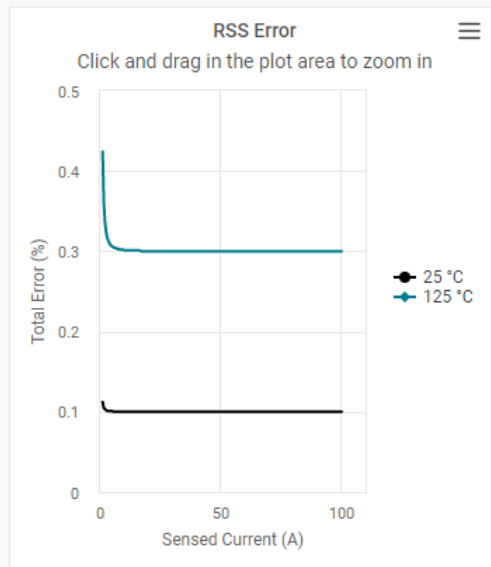Note: The error tool uses *RSS* (root-sum-of-squares) error of *worst-case specs*




X scale:

- Linear
 Logarithmic

Export to Excel

AUTOMOTIVE 48-V APPLICATIONS


48-V battery management (BMS)

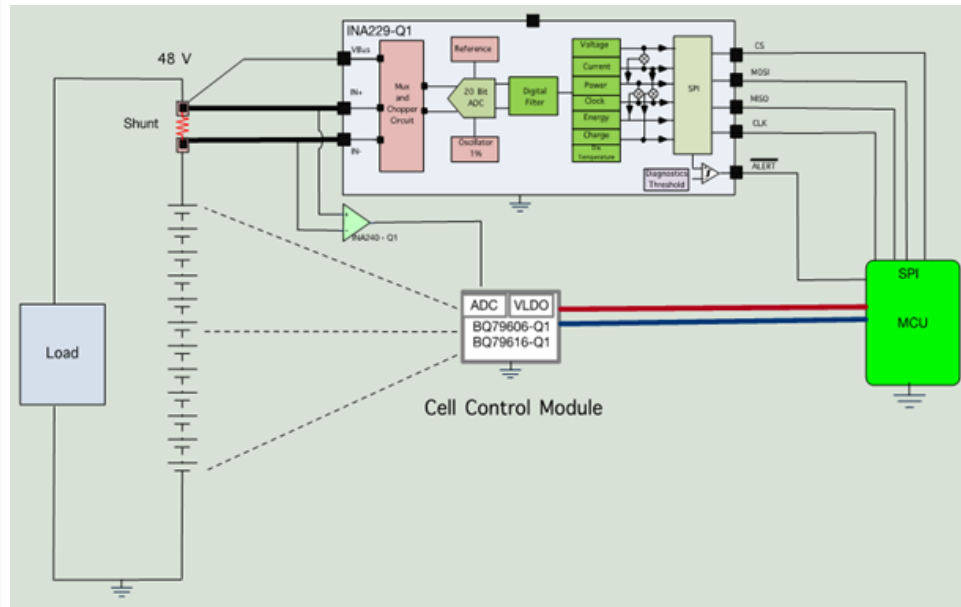

V_{CM}	48V	Error at 1600A Current:	0.10%
V_{SUPPLY}	5V	Error at 100A Current:	0.10%
Full Scale Input	$\pm 160\text{mV}$	Error at 10A Current:	0.22%
Max Current	$\pm 1600\text{A}$	Error at 1A Current:	2.0%
Ideal Shunt Resistor	$100\mu\Omega$	Error at 0.1A Current:	20%

- BMS presents unique challenge of measuring bi-directional current for up to 5+ decades of dynamic range: **$\pm 100\text{'s of mA to } \pm 1000\text{'s of amps}$**
 - 1000s of amps requires sub- $100\mu\Omega$ shunt resistor
 - Low value shunt drives extremely low offset requirement to measure small currents.
- INA229-Q1**
 - $1\mu\text{V}$ offset to allow use of low value shunts needed for high current
 - ENOB=20 with 160mV full scale input extends dynamic range achievable
 - Alert diagnostics can be used to detect Over Currents using GPIO
- INA240-Q1** could be used as a parallel path across shunt to improve system diagnostics and to reduce failure analysis of the shunt


48V-12V bi-directional DC/DC

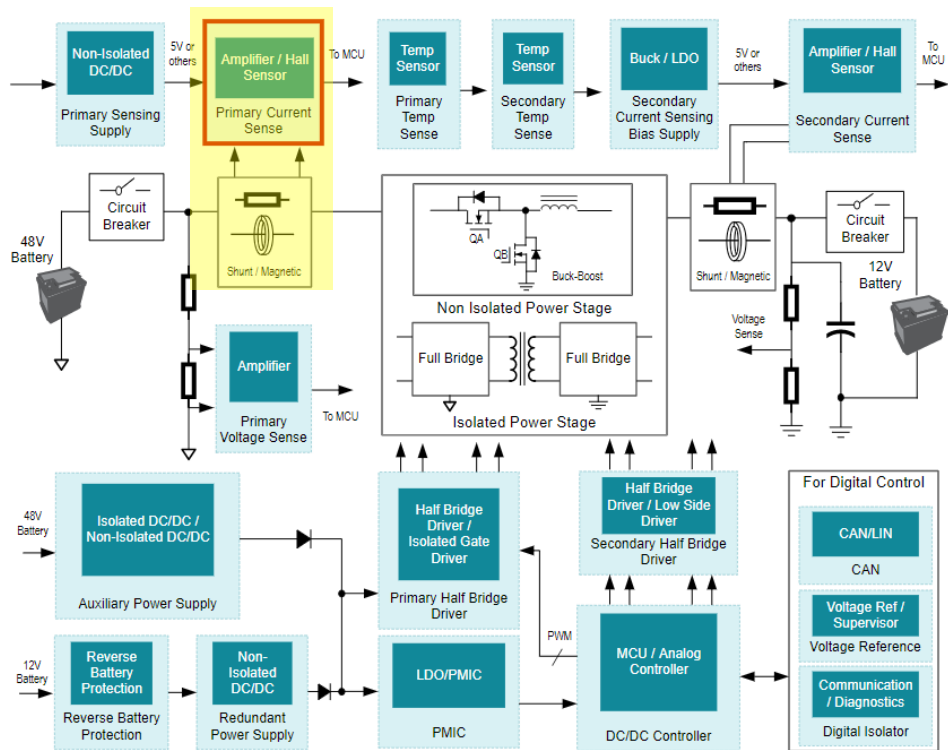


- The 48V supplies large loads such as traction motor, air-conditioning, and starters.
- Common mode range must survive up to 90V minimum and preferred to survive up to >100V
- [INA240-Q1](#) or [INA293-Q1](#) offer enhanced performance with industry leading:
 - Survivable common mode voltage up to 120V
 - Offset voltages less than 50 μ V enable the use of lower ohmage shunt resistors enabling more power efficient designs
 - Gain error of less than 0.2% with zero-drift to enable stable measurements regardless of operating environment

48V DC motor drive


Half-bridge

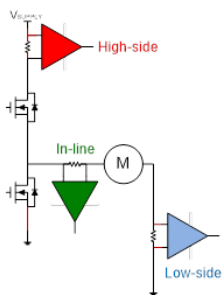

H-bridge


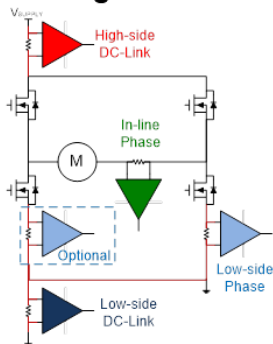


3-phase

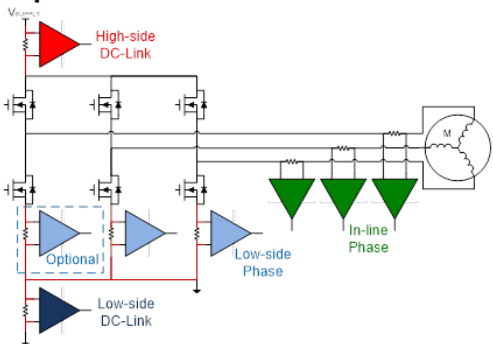

- High-side DC-Link: [INA290-Q1](#), [INA293-Q1](#)
 - Stable V_{CM}
 - Enables ability to detect load shorts to ground
 - Uni-directional current
 - High common-mode voltage amplifier
 - Driver current is not equal to phase current
- In-line phase: [INA240-Q1](#)
 - True phase current at all times, NO guess work
 - Best for maximizing motor control efficiency
 - PWM common-mode voltage seen by amplifier
 - High common-mode voltage combined with high dV/dT poses steep challenge to amplifier
- Signal's frequency contents
 - The differential signal (useful information) is relatively narrow-band, and small;
 - The common mode PWM signal (not useful) is wide-band and BIG.
- **An ideal inline sensor amplifies only differential signal and is "blind" to common mode signal → INA240-Q1!**

48V solenoid

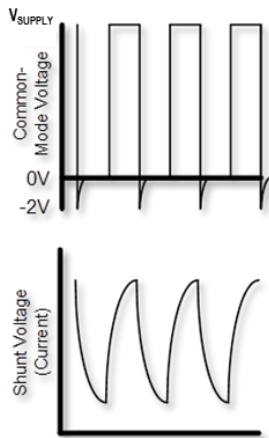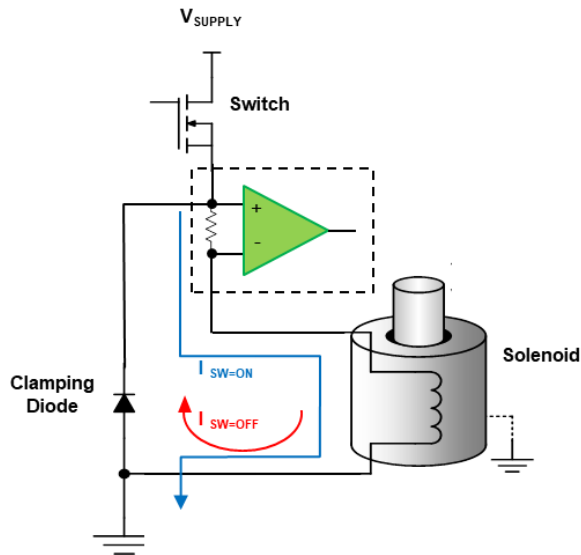

- High side drive, high side sense
- High side drive disconnects solenoid from high voltage power to extend solenoid lifetime
- High side sense avoids ground bouncing and allows for short to GND fault detect.
- **Challenges: a fast switching PWM common mode voltage between 48V and negative voltage**
- **INA293-Q1, INA240-Q1, and INA253-Q1 address both challenges well with high bandwidth and wide CMV range**


KEY 48V AUTOMOTIVE PRODUCTS

AEC-Q100 Portfolio $\geq 48V$


Existing	Q100 Option Available	Q100 in Development
New Release		

High Precision:


- $VOS \leq 100\mu V$
- Gain Err $\leq 0.5\%$

 **INA240**

-4.0V to 80V CMR
25uV Offset, 0.2% Gain Error
 Gains: 20, 50, 100 V/V
Enhanced PWM Rejection
AEC-Q100 Grade 0 In SOIC
 TSSOP & SOIC

 **INA293**


-4V to 110V CMR
-20V to 120V Survivability
 20uV Offset, 0.15% Gain Error
1.3MHz BW & 2.5V/ μ s slew rate
 Gains: 20, 50, 100, 200, 500V/V
 SOT-23 Dual Pinouts

 **INA290**


2.7V to 110V CMR
-20V to 120V Survivability
 25uV Offset, 0.25% Gain Error
800KHz BW & 3V/ μ s slew rate
 Gains: 20, 50, 100, 200, 500V/V
 SC-70

Mid-Performance:


- $VOS \leq 1mV$
- Gain Err $\leq 1.5\%$

 **LMP8601 Family**

-22V to +60V CMR
 1mV Offset, 0.5% Gain Error
 Gains: 20, 50, 100V/V
Split Stage for Filtering
AEC-Q100 Grade 0 (Gain=20)
 SOIC-8


 **LMP8480 - 8481**

4.5V to +76V CMR
 265uV Offset, 0.8% Gain Error
 Gains: 20, 50, 60, 100V/V
 MSOP-8


 **INA282 Family**

-14V to +80V CMR
70uV Offset, 1.4% Gain Error
 Gains: 50, 100, 200, 500, 1000
CMRR: 140dB Minimum
 SOIC-8 & MSOP-8


High Bandwidth

 **INA193 Family**


-16V to +80V CMR
 2mV Offset, 2.5% Gain Error
 Gain Options: 20, 50, 100V/V
 SOT-23 Dual Pinouts

 **INA270 - 271**

-16V to +80V CMR
 2.5mV Offset, 2.5% Gain Error
 Gain Options: 14, 20V/V
Split Stage for Filtering
 SOIC


 **INA281**

-4V to 110V CMR
-20V to 120V Survivability
 500uV Offset, 0.5% Gain Error
1.3MHz BW & 2.5V/ μ s slew rate
 Gains: 20, 50, 100, 200, 500V/V
 SOT-23 Dual Pinouts


 **INA280**

2.7V to 110V CMR
-20V to 120V Survivability
 500uV Offset, 0.5% Gain Error
800kHz BW & 3V/ μ s slew rate
 Gains: 20, 50, 100, 200, 500V/V
 SC-70

Digital Output Current/Voltage/Power Monitors

 **INA228/INA229**

0V to +85V CMR
1uV Offset & 0.1% Gain Error
20-bit ADC
 SPI (229) and I2C (228) Outputs
 VSSOP-10

 **INA238/INA239**

0V to +85V CMR
10uV Offset & 0.25% Gain Error
16-bit ADC
 SPI (239) and I2C (238) Outputs
 VSSOP-10

INA240

-4 to 80V, Bi-directional, Ultra-Precise Current Sense Amplifier w/ Enhanced PWM Rejection

Features

- Enhanced PWM Rejection minimizes impact of high dV/dt common mode voltage transitions
- Wide Common-Mode : -4V to 80V
- High AC CMRR: 93dB @ 50kHz
- High Accuracy
 - Input Offset Voltage: $\pm 25\mu\text{V}$ (Max) with $0.25\mu\text{V}/^\circ\text{C}$ Max Drift
 - Gain Error: $\pm 0.25\%$ (Max) with $2.5\text{ppm}/^\circ\text{C}$ Max Drift
 - AC CMRR: $\geq 93\text{dB}$ @ 50kHz
 - DC CMRR: $\geq 120\text{dB}$
 - PSRR: $\leq \pm 10 \mu\text{V}/\text{V}$
- Available Gains: 20, 50, 100, 200V/V
- Bi-Directional current sensing
- Packages: TSSOP-8, SOIC-8
- Functional-safety capable AEC-Q100 Grade 1 & Grade 0 (SOIC)


Applications

- Motor Control
- Solenoid/Valve Control
- Pressure Regulator
- Power Management



Benefits

- Enhanced PWM Rejection allows for direct in-line motor current sensing
- Large input range to integrate into increasing common-mode voltage applications
- High accuracy minimizes system margins

Ex: In-line Motor Current Sensing

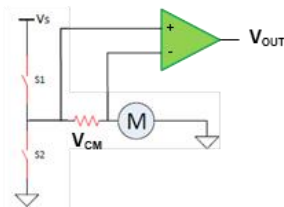

Ex: High-side DC-DC Current Sensing

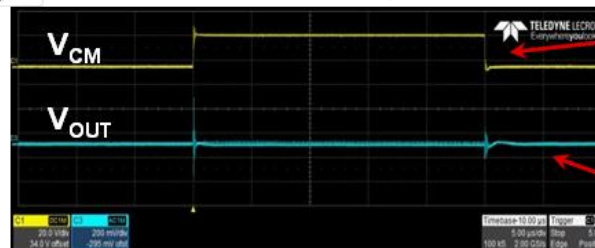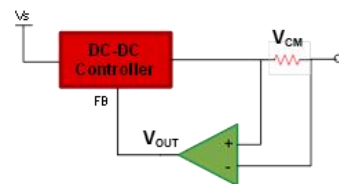

Large, high
slew rate input
 V_{CM}

Stable V_{OUT} !

INA290 family

110V High Voltage, High-Side, High Bandwidth, Unidirectional Current Sense Amplifier in SC-70 Package

Features


- 2.7V to 110V Common-Mode Range
 - -20V to 120V Survivability
- DC Accuracy:
 - Offset: 25 μ V (MAX) with 0.5 μ V/ $^{\circ}$ C drift
 - Gain Error: 0.25% (MAX) with 10 ppm/ $^{\circ}$ C drift
- High Speed: 800KHz 3dB bandwidth and 3V/ μ s slew rate
- Gain options: 20V/V, 50V/V, 100V/V, 200 V/V, 500V/V
- DC Supply: 2.7V to 20V
- Available in SC-70 (2mm x 1mm) Package
- AEC-Q100 Grade 1 Option Planned in 4Q20

Applications

- 48V Automotive BMS
- Solenoid Control
- 48V Server
- 54V Telecom
- 60V Industrial Auto Transport
- 54V PA Biasing & Monitoring

Benefits

- Wide common mode range supports 12V,24V,48V,60V,72V rails
 - Support negative transients survivability in harsh Inductive loads
- Low offset and Low gain error enables
 - improves system accuracy over temperature (-40 $^{\circ}$ C to 125 $^{\circ}$ C)
 - accurate lower current measurements
 - smaller shunt values (< 1m Ω)
- High Bandwidth and slew rate supports faster signal throughput
 - Ripple current measurement
 - Faster current throughput for protection
- Multiple Gain options increase design flexibility
- SC-70-5 package enables industry's smallest amplifier with least board

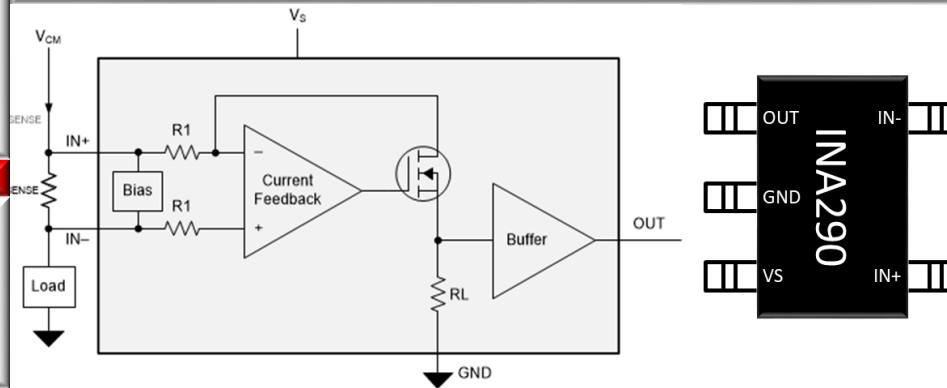

INA293 family

110V High Voltage, High Bandwidth, Unidirectional Current Sense Amplifier

Features


- -4V to 110V Common-Mode Range
 - -20V to 120V Survivability
- DC Accuracy:
 - Offset: 20 μ V (MAX) with 0.25 μ V/ $^{\circ}$ C drift
 - Gain Error: 0.15% (MAX) with 10 ppm/ $^{\circ}$ C drift
- High Speed: 1.3MHz 3dB bandwidth and 2.5V/ μ s slew rate
- Gain options: 20V/V, 50V/V, 100V/V, 200 V/V, 500V/V
- DC Supply: 2.7V to 20V
- Available in two SOT23-5 pin-out configurations
- AEC Q100 Option Planned in 3Q20

Applications

- 48V Automotive
- Solenoid Control
- 48V Server
- 48V Telecom
- 60V Industrial Auto Transport
- PLC Digital Output Control

Benefits

- Wide common mode range supports 12V,24V,48V,60V,72V rails
 - -20V common mode survivability supports large inductive kick backs.
- Low offset and Low gain error enables
 - improves system accuracy over temperature (-40 $^{\circ}$ C to 125 $^{\circ}$ C)
 - accurate lower current measurements
 - smaller shunt values (< 1m Ω)
- High Bandwidth and slew rate supports faster signal throughput
 - Ripple current measurement
 - Faster current throughput for protection
 - Reduces blanking times in PWM applications
- Multiple Gain options increase design flexibility
- Wide supply range to support high voltage analog PID feedback systems.

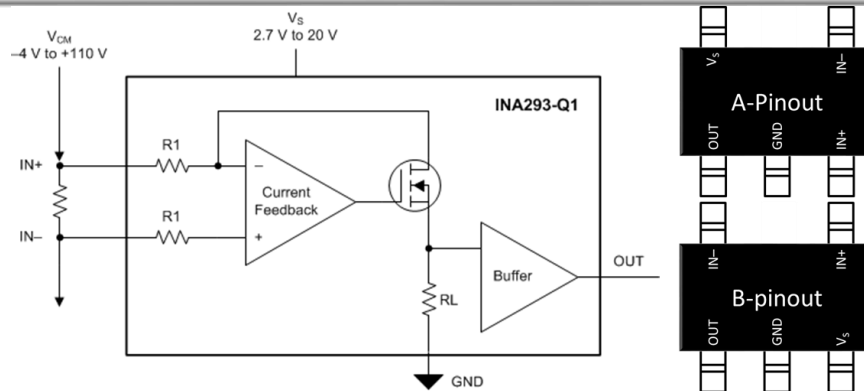

INA229

85V 20-bit, Bi-directional, SPI Power/Energy/Charge Monitor

Features


- -0.3V to 85V Common Mode Voltage
- Shunt Voltage ADC Specifications
 - Full Scale Range (+/-160mV or +/-40mV) with 20-bit Resolution (300nV/LSB or 70nV/LSB)
 - High Common Mode Rejection Ratio of 126dB (Min)
 - Offset: 1uV (Max at VCM=0V) with 0.05uV/°C (Max) Drift
 - Gain Error : 0.10% (Max) with 20ppm/°C (Max) Drift
 - Internal 1% Oscillator for Precision Energy/Charge Measurement
- Telemetry
 - Voltage, Current: <0.2% Error
 - Power, Time, Energy, Charge: <1% Error
 - Internal Temperature: ±3°C
- AC Specifications
 - Programmable conversion time/ Sampling Average
 - 50uS – 14bits
 - 1mS to 64mS– 20 bits
 - Fastest Over Current Alert threshold: 50uS
- DC Supply: 2.7V – 5.5V with Iq Operation < 1mA
- AEC-Q100 Option

Applications

- 48V Automotive BMS
- 48V Servers
- AISG Modem Control
- Renewable Energy Monitoring
- PA Bias Control
- 48V PoE systems

Benefits

- Wide common mode range supports low-side, 24V,48V,60V Power Rail systems.
- 20Bit ADC resolution,
 - 120dB of dynamic range measurements
 - Low offset and Gain error enables low ohmic shunts, ($\mu\Omega$)
 - Low temperature drift eliminates over temperature calibration
- Accurate Power/Energy and Charge estimation
- Programmable Conversion time to maximize system noise measurement
- Multi alert system that can detect
 - Over current, Under current
 - Under Voltage, Over Voltage
- SPI output mode to support high speed data throughput

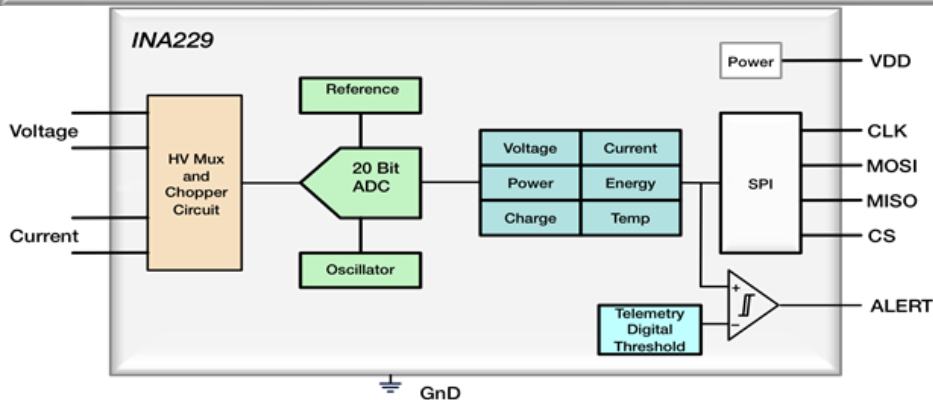

TMCS1100

Precision, Bi-directional, Galvanically Isolated Current Sensor with External Reference

Features


- 80 kHz signal bandwidth
- 1% Accuracy (-40 to 125°C)
- ± 600 V Working Voltage, 3 kV Dielectric Isolation (IEC 60950-1)
- Operating voltage: 3.0 V to 5.5 V
- 20 A max continuous DC/RMS current (thermally limited)
- Multiple sensitivities for wide linear measurement ranges
 - TMCS1100A1: 50 mV/A – TMCS1100A2: 100 mV/A
 - TMCS1100A3: 200 mV/A – TMCS1100A4: 400 mV/A
- 8-pin SOIC package
- AEC-Q100 Grade 1 Option

Applications

- Motor Control
- PV String Inverters
- Switching Converters
- Overcurrent Protection
- Power Monitoring
- On-Board Charger PFC

Benefits

- Ability to measure an isolated ac or dc current
- In-package sensing simplifies PCB and application design
- Highest accuracy Hall current sensing device in the industry
- Highest working voltage isolation (600 V) in 8-pin SOIC
- Ability to precisely set the reference voltage (V_{REF}) independent of V_{CC} enables higher accuracy.
- V_{REF} can be shared with ADC for increased system accuracy.
- Fixed sensitivity eliminates ratiometry errors and improves supply noise rejection

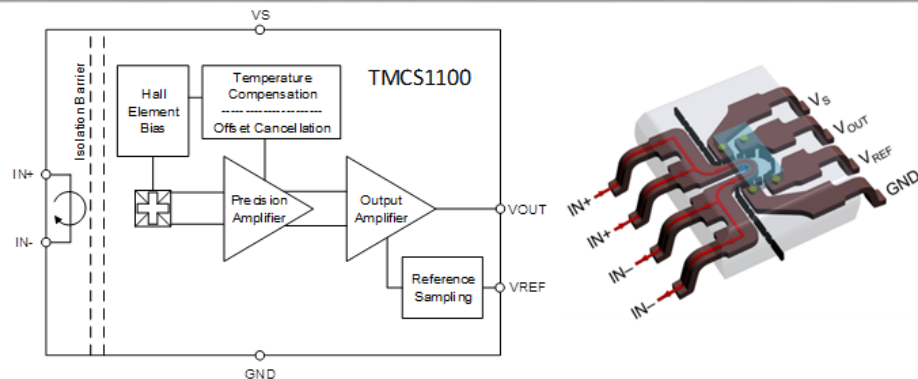

QUIZ TIME!

Quiz

- Which of the following is not an advantage of using isolated amplifiers (such as AMC1301) for current sensing?
 - Supports up to kV of common-mode range
 - Wide variety of gain options
 - High measurement accuracy
 - Still provides isolated sensing at low voltages

- Which of the following is an advantage of using current sense amplifiers (such as INA293) for current sensing?
 - High performance vs. cost
 - Simple to implement in a system
 - Floating input stage allows $V_{CM} > V_S$
 - All of the above


Quiz, cont.

- A device SPICE model is usually designed to _____ datasheet specs.
 - Min/max
 - Worst-case
 - RSS of worst-case
 - Typical

- The ti.com CSA error tool plots _____ error.
 - Min/max
 - Worst-case
 - RSS of worst-case
 - Typical

Quiz, cont.

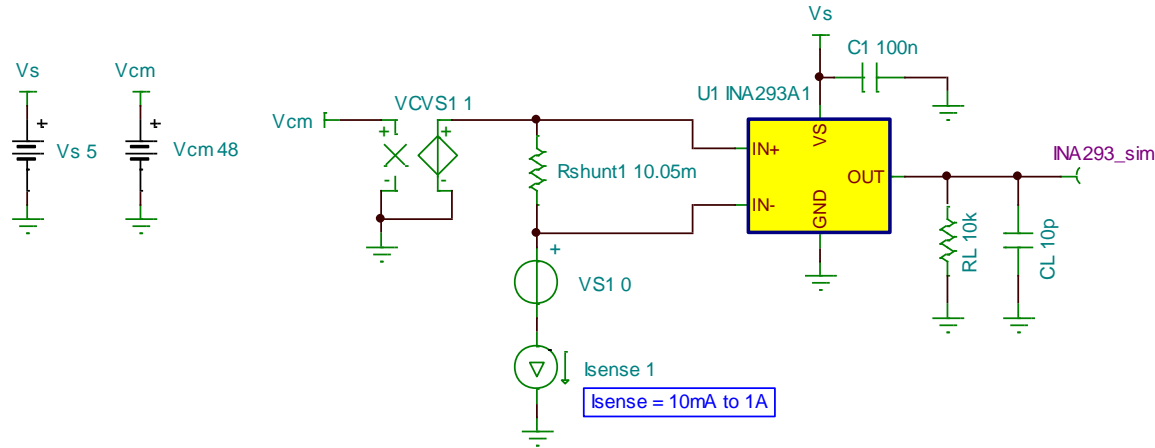
- For the circuit simulating INA293-Q1 shown?
 - What is the current that will produce the worst DC error?
 - What is the dominant error source in this worst case?
 - How can the error be reduced without changing amplifiers?
 - What is the max power dissipation if $R_{SHUNT} = 100m\Omega$?



Quiz, cont.


- For the circuit simulating INA293-Q1 shown?
 - What is the current that will produce the worst DC error?
 - 1A
 - 500mA
 - 10mA

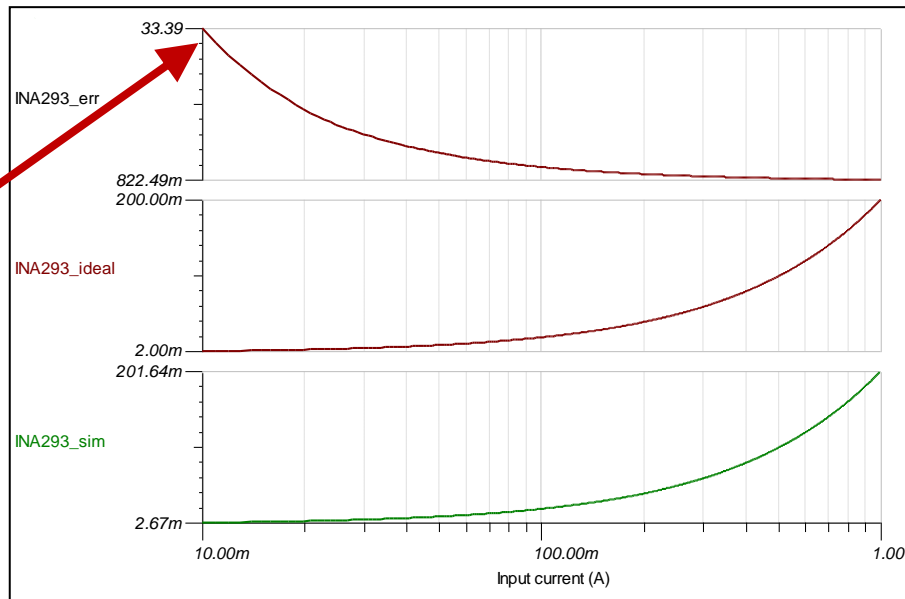Worst error occurs at minimum current, ~33.4%



Quiz, cont.

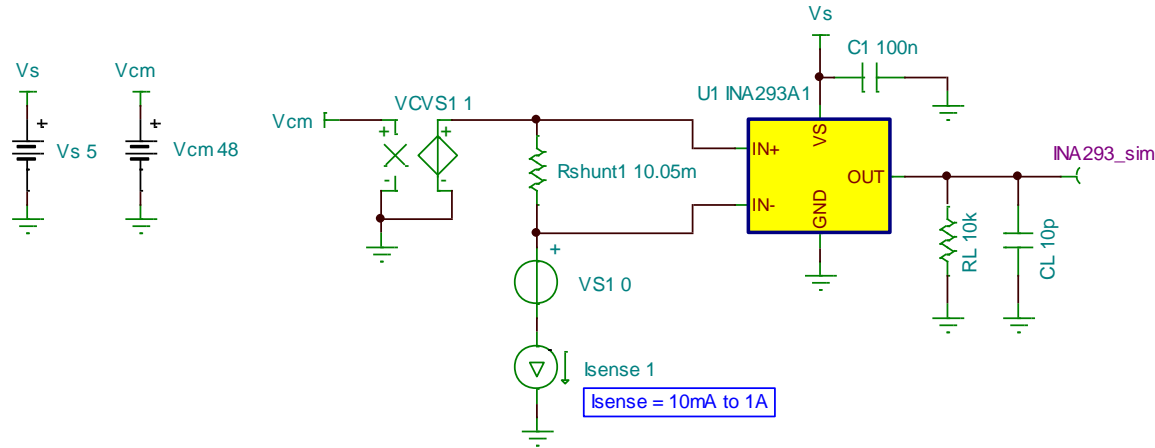
- For the circuit simulating INA293-Q1 shown?
 - What is the dominant error source in this worst case?
 - INA293-Q1 gain error
 - Shunt tolerance
 - INA293-Q1 V_{OFFSET}
 - INA293-Q1 CMRR



Quiz, cont.

- For the circuit simulating INA293-Q1 shown?
 - How can the error be reduced without changing amplifiers?
 - Add a filter to input
 - Increase shunt resistor value
 - Change output filter values


At 100mΩ, error drops to 3.2%

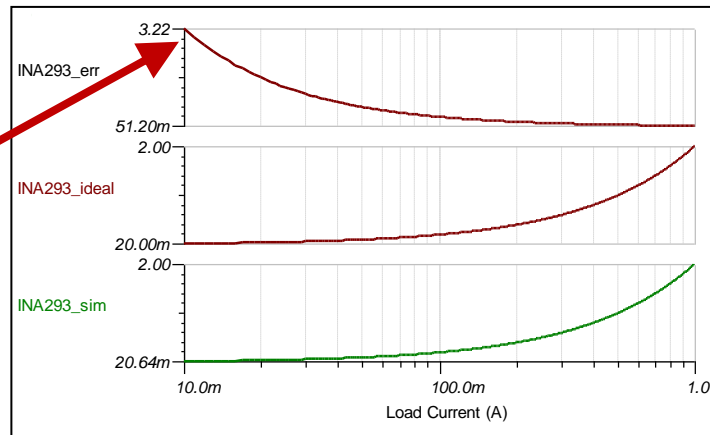

Quiz, cont.

- For the circuit simulating INA293-Q1 shown?
 - What is the max power dissipation if $R_{shunt} = 100\text{m}\Omega$?
 - 1W
 - 500mW
 - 100mW
 - 10mW
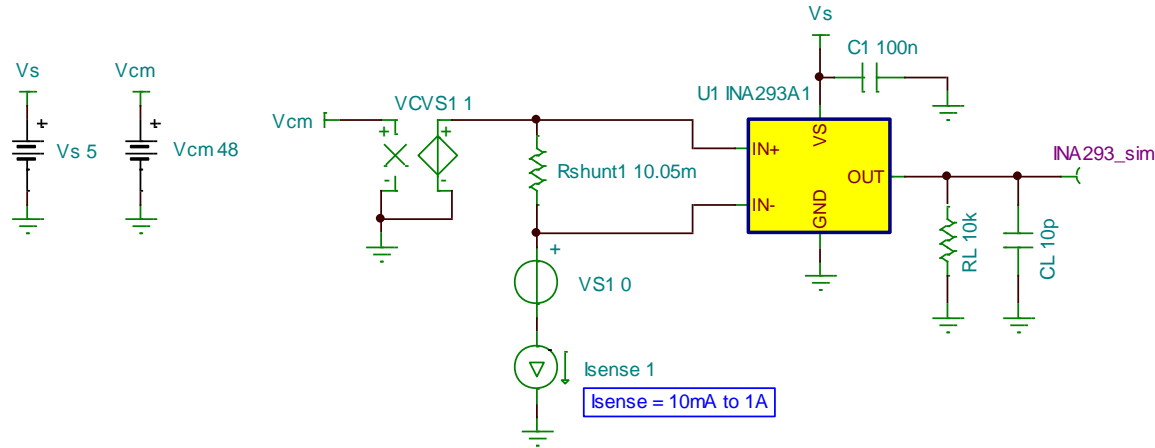
$$P_{DIS} = I^2 * R = (1A)^2 * 100\text{m}\Omega = 100\text{mW}$$



THANK YOU!



©2020 Texas Instruments Incorporated. All rights reserved.

The material is provided strictly "as-is" for informational purposes only and without any warranty.
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated