

Breaking down accuracy errors in a precision high-speed ADC signal chain

By Rob Reeder

Applications Engineer, High-Speed Data Converters

Introduction

Data converters, amplifiers, professional athletes—they all have accuracy errors. As it relates to electronics, however, an accuracy error is the sum of numerous fluctuations that move the DC conditions within each part in a signal chain. These errors can eat up the useful signal dynamic range of the system in different ways.

This article examines error-producing conditions in the signal chain where the fully differential amplifier (FDA) meets the high-speed analog-to-digital (ADC) converter in a receiver system.

Signal-chain overview and resistor errors

Figure 1 gives an overview of the signal-chain subset. Here, the analog input signal connects to the primary of the balun, which converts the input signal to a differential signal. In this example, the FDA gains up the signal by 4 or 12 dB; the signal then moves through a matching network to eventually interface to the high-speed ADC for sampling of the analog signal.

Table 1 separates the high-level signal-chain specifications in a spreadsheet, a good starting point for keeping all of the specifications in order.

For the following analysis, assume that there are no errors associated with the balun. See References 7 through 9 for descriptions of balun and transformer nuances.


Table 1. Signal-chain specifications

Overall Signal Chain Specifications	Value	Unit
Input Signal	0.3	V
Temp. Range (–40 to +85°C) ⇒ 1 = 26°C at Room Temp.	1	
Kelvin (Room Temp.)	299.15	K
Boltzmann's Constant	13.8×10^{-24}	W-s/K
LDO Reg Line Regulation	0.05	%/V
ADC Supply Voltage-VA19	1.9	V
ADC Supply Voltage-VA11	1.1	V
ADC Supply Voltage-VD11	1.1	V
DIFF Amp Supply Voltage	5	V
BW	1	GHz
Noise BW—1st Order System	1.57	GHz
Noise BW—2nd Order System	1.22	GHz

There are three significant contributors to resistor errors:

- Resistor tolerance (R_{tol}) is the value tolerance, usually specified in percent.
- Resistor temperature coefficient (R_{tempco}) is the value's drift, usually specified in parts per million per degrees Celsius.
- Resistor life (R_{life}) or qualification is the value's drift over thousands of hours, usually specified in percent.

Figure 1. Subset of a receiver signal chain

 

For example, a simple 50- Ω resistor with a 5% tolerance, 1,000 ppm/ $^{\circ}\text{C}$ over a -40°C to $+85^{\circ}\text{C}$ temperature range (125 $^{\circ}$) and a life drift of 2% over 1,000 hours would yield a resistance error of $\pm 9.75 \Omega$.

Or, using Equation 1, where the total resistor tolerance is equal to:

$$R_{\text{value}} \pm (R_{\text{tol}} + R_{\text{tempco}} + R_{\text{life}}) \quad (1)$$

Therefore,

$$\begin{aligned} \text{Total Tolerance} &= R_{\text{value}} \pm \left(\frac{R_{\text{tol}}}{100} \times R_{\text{value}} \right) \\ &+ \left[\left(\frac{R_{\text{tempco}}}{10^6} \times \text{TempRange} \right) \times R_{\text{value}} \right] \\ &+ \left(\frac{R_{\text{life}}}{100} \times R_{\text{value}} \right) \quad (2) \\ &= 50 \pm (2.5 + 6.25 + 1) \\ &= 40.25 \Omega \text{ to } 59.75 \Omega \end{aligned}$$

Initially, 40.25 Ω to 59.75 Ω looks like a big range of resistance variability, especially for a 50- Ω resistor. However, this is over the resistor's entire temperature range and life. For simplicity, it is best to understand the tolerance at room temperature, or 25 $^{\circ}\text{C}$; in this case, setting the TempRange = 1 in the example. This setting tightens up the resistor's error range, yielding 46.45 Ω to 53.55 Ω , which is a bit more realistic for a lab setting. Tighter tolerance resistors can also have a dramatic effect in cleaning up the error range as well.

Table 2 captures all of the resistor values in the spreadsheet and organizes them neatly. Eventually, the errors and tolerances can be factored in for each resistor throughout the signal chain. A table at the end of this article includes a minimum and maximum value for each resistor and how it influences the signal chain.

Amplifier errors

There are two types of amplifier errors:

- Inherent errors like bias current, offset voltage and common-mode error.
- Environmental-type errors like power-supply rejection ratio (PSRR) and temperature. These errors are more dependent on or influenced by outside parameters at the system level.

Table 2. Resistor error specifications

Diff Amp Circuit & Resistor Specs	Value	Unit
Amp Gain (A_v), [Calculated]	4	
Amp Gain (dB), [Calculated]	12.04	dB
R _g	50	Ω
R _f	175	Ω
R _{fint} [DS] ¹	25	Ω
R _{s1} and R _{s2}	8.66	Ω
R _t	282	Ω
Characteristic Impedance (Z)	50	Ω
Resistor Coefficient	1000	ppm/ $^{\circ}\text{C}$
Resistor Tolerance	5	%
Resistor Life Tolerance, 1000 hours	2	%

¹[DS]—Value from datasheet

References 3 and 4 provide a fully functional model on amplifier errors and how they are manifested. Both documents go into great detail on the derivations of amplifier model errors. For simplicity, Figure 2 and Table 3 offer a breakdown of these errors.

The equations in Table 3 yield a referred-to-output (RTO) summary of errors that can be root-sum-squared (RSS) to achieve a total cumulative error for the amplifier as well as an output signal level in the signal chain.

With all resistor errors captured and organized, to start the amplifier analysis, it is best to solve the feedback factors, coefficients and equivalent resistances defined in Table 3. Each of these will provide a minimum and maximum, based on the minimum and maximum resistance values previously defined in Table 2.

Solving for the feedback factors, coefficients and equivalent resistances is the first step in understanding the output signal-level error or gain error based on the qualitative factors shown in Table 3. Next, calculate through all of the other errors listed in the amplifier error

Figure 2. Simple amplifier error model

 


Table 3. Amplifier error equations (referred to output)

Quantity	Symbol	General Expression
Feedback Factors	β_1, β_2	$\beta_1 = \frac{R_3}{R_3 + R_4}, \beta_2 = \frac{R_1}{R_1 + R_2}$
Coefficients	b1, b2	$b_1 = 1 + \frac{1}{2 \times \text{CMRR}}, b_2 = 1 - \frac{1}{2 \times \text{CMRR}}$
Equivalent Resistances	R_{EQ1}, R_{EQ2}	$R_{EQ1} = R_1 \parallel R_2, R_{EQ2} = R_3 \parallel R_4$
Applied Input Common Mode	V_{ICM}	$V_{ICM} = \frac{V_{IN-} + V_{IN+}}{2}$
Desired Output	$V_{OD, \text{Desired}}$	$V_{id} \frac{2 - (\beta_1 + \beta_2) - \frac{1}{2 \times \text{CMRR}} \times (\beta_1 - \beta_2)}{(\beta_1 + \beta_2) + \frac{1}{2 \times \text{CMRR}} \times (\beta_1 - \beta_2) + \frac{2}{a}}$
Output Error Due to Input Offset Voltage	$\Delta V_{OD}(V_{IO})$	$\frac{2V_{IO}}{(\beta_1 + \beta_2) + \frac{1}{2 \times \text{CMRR}} \times (\beta_1 - \beta_2) + \frac{2}{a}}$
Output Error Due to Input Bias Currents	$\Delta V_{OD}(I_{IB})$	$2I_{IB} \frac{(R_{EQ1} - R_{EQ2}) + \frac{1}{2 \times \text{CMRR}} \times (R_{EQ1} - R_{EQ2})}{(\beta_1 + \beta_2) + \frac{1}{2 \times \text{CMRR}} \times (\beta_1 - \beta_2) + \frac{2}{a}}$
Output Error Due to Input Offset Current	$\Delta V_{OD}(I_{IO})$	$I_{IO} \frac{(R_{EQ1} + R_{EQ2}) + \frac{1}{2 \times \text{CMRR}} \times (R_{EQ1} - R_{EQ2})}{(\beta_1 + \beta_2) + \frac{1}{2 \times \text{CMRR}} \times (\beta_1 - \beta_2) + \frac{2}{a}}$
Output Error Due to Common Mode Mismatch	$\Delta V_{OD}(V_{OCM} - V_{ICM})$	$\frac{2(V_{OCM} - V_{ICM})(b_1\beta_1 - b_2\beta_2)}{(\beta_1 + \beta_2) + \frac{1}{2 \times \text{CMRR}} \times (\beta_1 - \beta_2) + \frac{2}{a}}$
Output Error Due to Input Common Mode	$\Delta V_{OD}(V_{ICM})$	$\frac{2V_{ICM} / \text{CMRR}}{(\beta_1 + \beta_2) + \frac{1}{2 \times \text{CMRR}} \times (\beta_1 - \beta_2) + \frac{2}{a}}$
Output Error Due Power Supply Variations	$\Delta V_{OD}(\Delta V_S)$	$\frac{2\Delta V_S / \text{PSRR}}{(\beta_1 + \beta_2) + \frac{1}{2 \times \text{CMRR}} \times (\beta_1 - \beta_2) + \frac{2}{a}}$

equation table and collect them in a spreadsheet: input offset error, input bias current error, common-mode mismatch, PSRR, etc. See Table 4.

Once completed, subtotal the simple RSS summation of the errors and add that total to the output signal level to obtain the total RTO error.

Interface errors

An anti-aliasing filter helps minimize the noise bandwidth coming from the amplifier. Even simple resistor-capacitor-type low-pass filters will wiggle and ripple through the pass band because of tolerances, parasitics and frequency mismatches. However, for simplicity in this signal-chain design, bandwidth is key, so a simple matching pad will interface between the output of the amplifier and the input of the ADC.

As previously described in the *Signal-chain overview and resistor errors* section, first calculate the values used to create the matching pad. Next, calculate the K-ratio errors based on standard 3-dB pad calculations found in most radio-frequency (RF) cookbooks or even an internet search. See Figure 3.

After obtaining the variance in loss of the pad (in this case, 3 dB nominal), it is possible to then determine the signal loss through this portion of the signal chain coming from the output of the amplifier, and what signal level the ADC will actually sample.

Table 4. Amplifier error specifications

Amplifier Specs	Design Spec.	Unit
Input Offset Voltage Drift	10	mV
Input Bias Current Drift	150	μA
Input Bias Current	70	μA
Input Offset Current	2	μA
PSRR	-80	dB
Input Offset Voltage	1	mV
Open Loop Gain (Av)	60	
Amp CMRR	72	dBc
Input CM	0.4	mV
Output CM	-27.0	mV
Input Voltage Noise	1.25	nV
Input Noise Current	3.5	pA

Figure 3. X-dB, T-attenuator pad calculations


 


Figure 4. DC errors: gain, offset, DNL and INL

 

Data converter errors

Finally, the signal hits the ADC, but it has errors as well; see References 1 and 6 for more information. Figure 4 illustrates four types of ADC errors: gain, offset, differential nonlinearity (DNL) and integral nonlinearity (INL). To get a better sense of the errors that affect the ADC's accuracy, PSRR should be included as well. While this spec can be difficult to find in some data sheets, the reasoning for including this particular error in Table 5 is that the headroom on data converter supplies is decreasing, largely driven by today's speed and bandwidth demands, which in turn, this drives the designs of these data converters into smaller process geometries. Table 5 sums these errors.

Like amplifier errors, calculating the RSS of these errors together will provide the total accumulation of error given by the data converter.

Table 5. ADC error specifications

ADC Specs.	Datasheet Spec.	Design Spec.	Unit
ADC Number of Bits		12	bits
ADC Input Full Scale (Differential)		800	mV _{PP}
ADC LSB Size, [Calculated]		195.31	μV _{PP}
Linearity (INL)	±2	4	LSB
Offset Error	±2	10	mV
Gain Error	±50	100	mV _{PP}
Offset Drift	23	30	μV/°C, LSB
Gain Drift	-0.01	40	%/°C, LSB
PSRR	5 LSB	-60	5 LSB, V
Clock Rate (fs)		10.4	GSPS
Ideal 12 bit SNR, [Calculated]		74	dB
SNR	55 at 1 GHz	55	dBFS
SINAD	53.4 at 1 GHz	53.4	dBFS
ENOB, [Calculated]		8.58	bits

Final analysis

It is now possible to RSS each subtotal error to get an understanding of the full accuracy error throughout the entire signal chain on the input signal, and what that difference is relative to the full-scale range of the ADC. Table 6 shows the final analysis.

The RSS approach is a popular way to properly sum errors throughout the signal chain because it isn't as pessimistic as a straight summation, also known as a worst-case analysis. There will always be some random variation of these errors, as some errors can cancel or move in opposite directions. Self-heating, temperature and other environmental factors also have an effect. Another approach is to assign a weighting factor into a particular error or set of errors, which helps to understand the sensitivity within a certain part of the signal chain that is critical to the design.

References

1. "What Designers Should Know About Data Converter Drift," Burr-Brown application bulletin (SBAA046), September 1986.
2. "Worst-case circuit design includes component tolerances," EDN, April 15, 2004.
3. James Karki, "Fully Differential Amplifiers," Texas Instruments (TI) application report (SLOA054E), September 2016.
4. John Miller, "DC Output Errors in a Fully-Differential Amplifier," TI application report (SLVA417), May 2010.
5. "Understanding Data Converters," TI application report (SLAA013), 1995.
6. Shridhar Atmaram More, "ADC Performance Parameters – Convert the Units Correctly!," TI application report (SLAA587), May 2013.
7. Doug Jorgesen and Christopher Marki, "Balun Basics Primer: A Tutorial on Baluns, Balun Transformers, Magic-Ts, and 180° Hybrids," Marki Microwave, 2014.
8. Rob Reeder and Ramya Ramachandran, "Wideband A/D Converter Front-End Design Considerations: When to Use a Double Transformer Configuration," AnalogDialogue, VOL 40: July 2006.
9. David Brandon and Rob Reeder. "High Speed Amplifier Testing Involves Enough Math to Make Your Balun Spin!," AnalogDialogue, VOL 52: June 2018.

Table 6. Full signal-chain error accumulation

Signal Chain Calculations	Min	Max	Unit
Amp Resistor Errors			
Total Tolerance (R _g +R _{tol} +R _{tempco} +R _{life})	46.45	53.55	Ω
Total Tolerance (R _f +R _{tol} +R _{tempco} +R _{life})	162.58	187.43	Ω
Feedback Factors 1 & 2	0.22	0.18	
Coefficients 1 & 2	1.0001	0.9999	
Equivalent Resistances 1 & 2	36.13	41.65	Ω
Total Tolerance (Gain/Loss)	3.5	4.57	Gain
Output Signal Level	1.10277	1.10281	V
Amp Errors			
Input Offset Voltage Error, [RTO] ¹	4.5993	4.5994	mV
Input Bias Current Error, [RTO]	-1.77	1.78	mV
Input Offset Current Error, [RTO]	0.358	0.358	mV
CM Mismatch, [RTO]	-5.38	5.38	mV
Input CM, [RTO]	115.53	115.53	nV
PSRR, [RTO]	23	23	μV
Amp Total Accuracy Error, [RSS] ²	7.307	7.309	mV
Amp Output Signal Level, [RSS]	1.1101	1.1101	V
Network Errors			
Total Tolerance (Rs1 & Rs2+R _{tol} +R _{tempco} +R _{life})	8.05	9.27	Ω
Total Tolerance (R _t +R _{tol} +R _{tempco} +R _{life})	261.98	302.02	Ω
K Ratio Tolerance (Rs)	1.38	1.46	
K Ratio Tolerance (R _t)	1.45	1.38	
Average Network Loss	2.82	3.25	dB
Amp & Network Output Signal Level	0.80208	0.7636	V
ADC Errors			
ADC Linearity, INL (LSB), [DS] ³ = ±2.0		781.25	μV
ADC Offset Error, [DS] = ±2.0		1.9531	mV
ADC Gain Error, [DS] = ±50		800	μV _{pp}
ADC Offset Drift, [DS] = 23		24	μV
ADC Gain Drift, [DS] = -0.01 %		32	μV
ADC PSRR, [DS] = 5 LSB		550	5 LSB, nV
ADC Total Accuracy Error		2.2509	mV
Amp & ADC Total Accuracy Error [RSS]			
Amp & ADC Total Accuracy Error [RSS]	7.6459	7.6475	mV
ADC Input Signal Level [RSS]	804.3306	765.8546	mV
DC Accuracy-FS	4.81		%

¹[RTO] = Referred to Output,

²[RSS] = Errors are Root Sum Squared,

³[DS] = Datasheet Spec.

TI Worldwide Technical Support

TI Support

Thank you for your business. Find the answer to your support need or get in touch with our support center at

www.ti.com/support

China: <http://www.ti.com.cn/guidedsupport/cn/docs/supporthome.tsp>

Japan: <http://www.tij.co.jp/guidedsupport/jp/docs/supporthome.tsp>

Technical support forums

Search through millions of technical questions and answers at TI's E2E™ Community (engineer-to-engineer) at

e2e.ti.com

China: <http://www.deyisupport.com/>

Japan: <http://e2e.ti.com/group/jp/>

TI Training

From technology fundamentals to advanced implementation, we offer on-demand and live training to help bring your next-generation designs to life. Get started now at

training.ti.com

China: <http://www.ti.com.cn/general/cn/docs/gencontent.tsp?contentId=71968>

Japan: <https://training.ti.com/jp>

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011617

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

© 2020 Texas Instruments Incorporated.
All rights reserved.



SLYT798

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated