

# **The Offset DAC**

## **ABSTRACT**

Several of TI’s high-resolution delta-sigma Analog-to-Digital Converters <sup>(1)</sup> (ADCs) include an analog offset Digital-to-Analog Converter (DAC) for helping extend the input range. This application note provides additional insight into how the offset DAC works, discusses its performance, and also shows how to use it as a signal generator for a self-test.

### **Contents**

1	How It Works .....	2
2	Use And Performance.....	3
3	Self-Test .....	4

### **List of Figures**

1	Offset Block Diagram.....	2
2	ADC Output Noise vs Offset DAC Setting.....	4
3	ADC Output vs Offset DAC Setting .....	4
4	DNL vs Offset DAC Setting.....	5
5	INL vs Offset DAC Setting.....	5

### **List of Tables**

1	Offset DAC Output.....	2
2	Offset DAC Output, Input-Referred.....	2
3	Offset DAC Output for ADS1240, ADS1243 with RANGE Bit = 1 and PGA = 128 .....	3
4	Offset DAC Output, Input-Referred for ADS1240, ADS1243 with RANGE Bit = 1 and PGA = 128 .....	3

<sup>(1)</sup> ADS1216, ADS1217, ADS1218, ADS1240, ADS1241, ADS1242, ADS1243, MSC1210.

## 1 How It Works

Figure 1 shows the block diagram for the offset DAC and associated circuitry. Conceptually, the offset DAC is a programmable voltage source. The input voltage, after being amplified by the Programmable Gain Amplifier (PGA), sums with the offset DAC voltage. The resultant voltage is measured by the delta-sigma ADC.

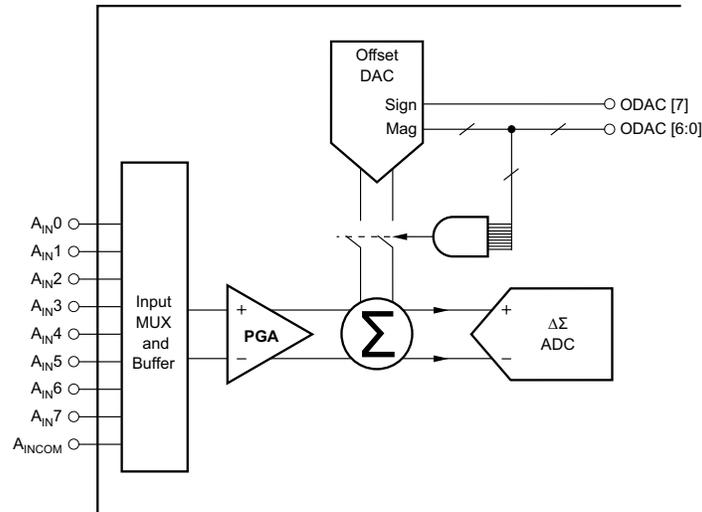


Figure 1. Offset Block Diagram

The offset DAC ODAC register sets the value of the offset DAC voltage. Bit 8 of the ODAC register sets the sign, whether the output voltage is negative or positive. The lower 7 bits set the magnitude as a percentage of the full-scale input range. When the magnitude is set to 0, the offset DAC is disabled. When the magnitude is set to all ones (127), the offset DAC outputs a value of 50% of the full-scale input range. Table 1 shows the offset DAC output for different ODAC values.

Table 1. Offset DAC Output

ODAC REGISTER VALUE	OFFSET DAC OUTPUT <sup>(1)</sup> (% OF FS INPUT)
0 000000 (00 <sub>H</sub> )	0%
0 000001 (01 <sub>H</sub> )	0.4%
0 111111 (0F <sub>H</sub> )	50%
1 000000 (80 <sub>H</sub> )	0%
1 000001 (81 <sub>H</sub> )	-0.4%
1 111111 (FF <sub>H</sub> )	-50%

<sup>(1)</sup> For the ADS1240, ADS1241, ADS1242, and ADS1243, the output voltage of the offset DAC has a different magnitude when the RANGE bit within the ACR register = 1 and PGA = 128. See Table 3 and Table 4 for the values in this case.

To refer the offset DAC output voltage back to the input, use the full-scale input range. Table 2 shows the “input-referred” offset DAC voltages for full-scale input ranges of 2.5 V, 0.625 V and 156 mV. It doesn’t matter how the full-scale input range is set. For example, the offset DAC will produce the same input-referred voltages for an ADS1216 with ( $V_{REF} = 2.5V$ ,  $PGA = 1$ ) or ( $V_{REF} = 1.25V$ ,  $PGA = 2$ ).

Table 2. Offset DAC Output, Input-Referred

ODAC REGISTER VALUE	OFFSET DAC VOLTAGE, INPUT-REFERRED		
	FS INPUT = 2.5 V	FS INPUT = 0.625 V	FS INPUT = 156 mV
0 000000 (00 <sub>H</sub> )	0	0	0
0 000001 (01 <sub>H</sub> )	0.0098	0.002461	0.615
0 111111 (0F <sub>H</sub> )	1.25	0.3125	78.125

**Table 2. Offset DAC Output, Input-Referred (continued)**

ODAC REGISTER VALUE	OFFSET DAC VOLTAGE, INPUT-REFERRED		
	FS INPUT = 2.5 V	FS INPUT = 0.625 V	FS INPUT = 156 mV
1 000000 (80 <sub>H</sub> )	0	0	0
1 000001 (81 <sub>H</sub> )	-0.0098	-0.002461	-0.615
1 111111 (FF <sub>H</sub> )	-1.25	-0.3125	-78.125

**Table 3. Offset DAC Output for ADS1240, ADS1243 with RANGE Bit = 1 and PGA = 128**

ODAC REGISTER VALUE	OFFSET DAC OUTPUT (% OF FS INPUT)
0 000000 (00 <sub>H</sub> )	0%
0 000001 (01 <sub>H</sub> )	0.8%
0 111111 (0F <sub>H</sub> )	100%
1 000000 (80 <sub>H</sub> )	0%
1 000001 (81 <sub>H</sub> )	-0.8%
1 111111 (FF <sub>H</sub> )	-100%

**Table 4. Offset DAC Output, Input-Referred for ADS1240, ADS1243 with RANGE Bit = 1 and PGA = 128**


ODAC REGISTER VALUE	OFFSET DAC VOLTAGE, INPUT-REFERRED	
	FS INPUT = 19.5 mV	FS INPUT = 9.77 mV
0 000000 (00 <sub>H</sub> )	0	0
0 000001 (01 <sub>H</sub> )	0.154	0.077
0 111111 (0F <sub>H</sub> )	19.531	9.765
1 000000 (80 <sub>H</sub> )	0	0
1 000001 (81 <sub>H</sub> )	-0.154	-0.077
1 111111 (FF <sub>H</sub> )	-19.531	-9.765

## 2 Use And Performance

The offset DAC can correct positive or negative input offsets up to 50% of the full-scale input range. To see its benefit, consider the following application: Using an ADS1216 with a reference voltage of 2.5 V, measure a 0 to 50 mV signal. With a 2.5-V reference, the ADS1216 has a full-scale input range of  $\pm 78$  mV for PGA = 32, or  $\pm 39$  mV for PGA = 64. Without the offset DAC, the PGA must be set to 32 or lower to avoid overloading the ADC. However, by using the offset DAC set to -20 mV, the input shifts from 0 to 50 mV down to -20 mV to 30 mV. A PGA of 64 can now be used, allowing a higher resolution measurement.

System- or self-calibration commands do not affect the offset DAC. When doing self-calibrations (SELFCAL, SELFOCAL, or SELFGCAL), be sure to turn off the offset DAC by setting ODAC = 00<sub>H</sub>. Otherwise, the calibration will be affected by the offset DAC output voltage.

Figure 2 shows the rms noise in ppm of full-scale versus offset DAC setting. The noise gets markedly better when using the offset DAC. The noise is lowest when the offset DAC's output is maximum. The ADC's integral nonlinearity error, when is unaffected by the offset DAC and the gain error drift of the offset DAC output voltage, is typically 1ppm/°C.

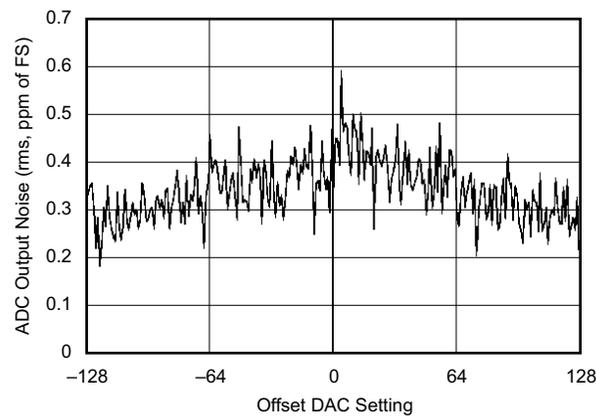


**Figure 2. ADC Output Noise vs Offset DAC Setting**
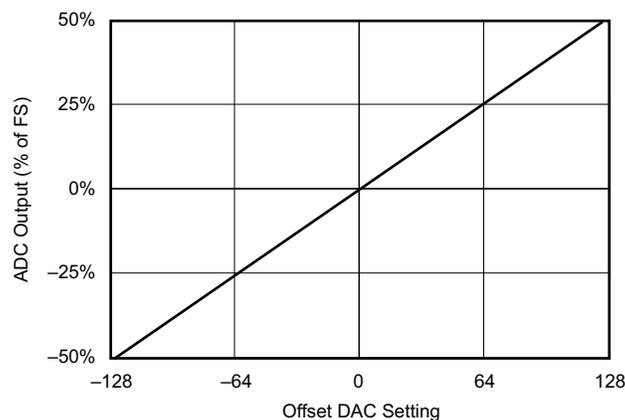
### 3 Self-Test

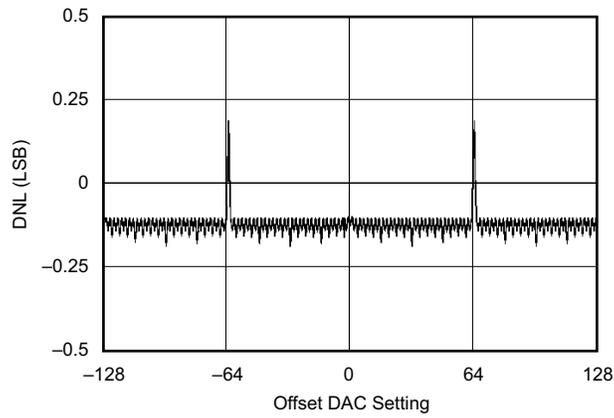
The offset DAC is basically a second input source to the ADC. As a result, it can also serve as a signal generator for a self-test function. To do this, program the MUX so as to disconnect the normal inputs and sweep the ADC's input using the offset DAC. The host controlling the ADC will then collect this data and perform the necessary checks to insure proper functionality.

Figure 3 shows ADC data collected with the normal inputs disconnected and the offset DAC stepped from its most negative to its most positive setting. The inputs were disconnected by setting the MUX register to  $88_{\text{H}}$ ; this connects both MUX outputs to  $A_{\text{INCOM}}$ . Then, the ODAC register was decremented from  $\text{FF}_{\text{H}}$  to  $00_{\text{H}}$ , collecting data at each step. At  $00_{\text{H}}$ , ODAC was incremented up to  $7\text{F}_{\text{H}}$ , again collecting data after each step.




**Figure 3. ADC Output vs Offset DAC Setting**

To measure the quality of the offset DAC as an input source, the data in Figure 3 was fit with a line going through the end points. The differential nonlinearity (DNL) and integral nonlinearity (INL) of intermediate points were then measured in units of offset DAC LSBs against this line. Figure 4 shows the DNL error versus offset DAC setting. Figure 5 shows the INL error versus offset DAC setting.



**Figure 4. DNL vs Offset DAC Setting**

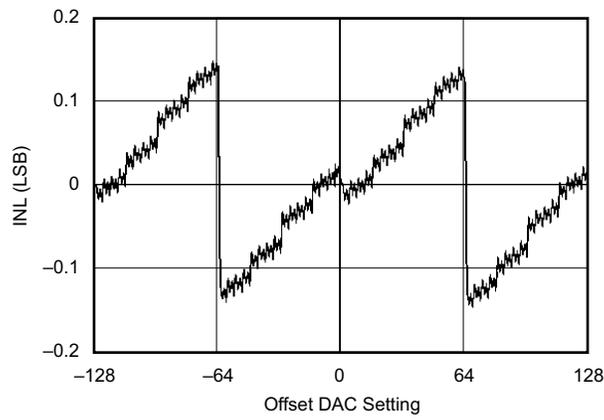

**Figure 5. INL vs Offset DAC Setting**

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)