

Applying the Current DAC on the TSC2000, TSC2200, TSC2300, and TSC2301 Touch Screen Controllers

Rick Downs

Data Acquisition Products

ABSTRACT


The TSC2000, TSC2200, TSC2300, and TSC2301 touch screen controllers all feature an 8-bit current-output DAC, which was intended for use as an LCD contrast adjustment. Some of the parametric limitations on the DAC may make it seem that it would not be useful for some applications; this application note shows some simple ways to overcome these apparent “limitations.”

Basic DAC Configuration

Pullup Voltage Less Than or Equal To the TSC Power Supply

The TSC2000, TSC2200, TSC2300, and TSC2301 touch screen controllers (hereafter referred to as the “TSCs”) have an on-board 8-bit D/A converter (DAC), outlined in Figure 1. This configuration yields a current sink (A_{OUT}) controlled by the value of a resistor connected between the ARNG pin and ground. The eight-bit data is written to the D/A converter through the DAC data register in these devices.

Figure 1. D/A Converter Configuration

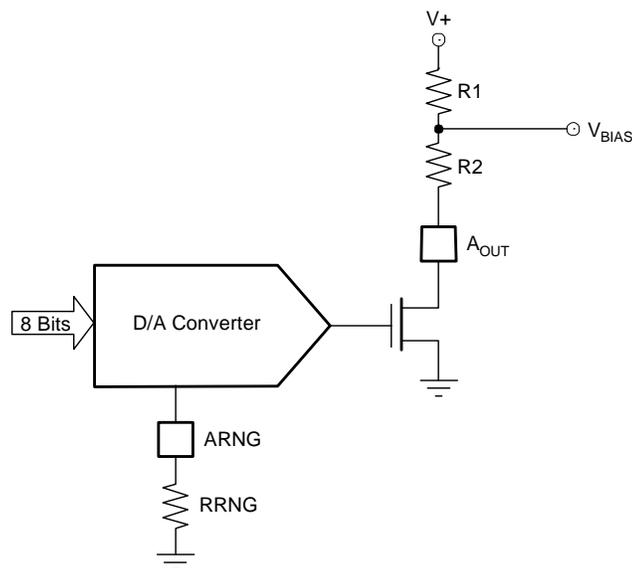


This circuit is designed for flexibility in the output voltage at the V_{bias} point shown in Figure 1 to accommodate the widely varying requirements for LCD contrast control bias. V_+ can be a higher voltage than the supply voltage for the TSCs. The only restriction is that the voltage on the AOUT pin can never go above the absolute maximum rating for the device, and should stay above 1.5V for linear operation.

The DAC has an output sink range that is limited to 1mA. This range can be adjusted by changing the value of RRNG, shown in Figure 1. As this DAC is not designed to be a precision device, the actual initial value of the output current range can vary as much as $\pm 20\%$. Furthermore, the current output will change due to variations in temperature; the DAC has a temperature coefficient of approximately $-2\mu A/^\circ C$.

To set the full-scale current, RRNG can be determined from the graph shown in Figure 2.

Figure 2. DAC Output Current Range vs ARNG Resistor Value

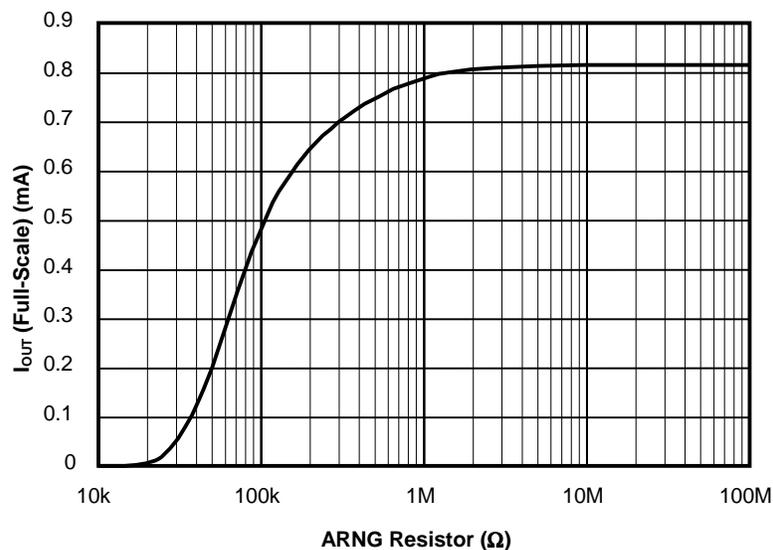

For example, consider an LCD that has a contrast control voltage V_{BIAS} which can range from 2V to 4V, and draws $400\mu A$ when used, with an available +5V supply. Note that this is higher than the TSC 3V supply voltage, but within the absolute maximum rating.

The maximum V_{BIAS} voltage is 4V, which occurs when the DAC current is 0. Thus, only the $400\mu A$ load current I_{LOAD} will be flowing from 5V to V_{BIAS} . This means 1V will be dropped across R_1 , so $R_1 = 1V/400\mu A = 2.5K\Omega$.

The minimum V_{BIAS} is 2V, which occurs when the DAC current is at its full-scale value, I_{MAX} . In this case, $5V - 2V = 3V$ will be dropped across R_1 , so the current through R_1 will be $3V/2.5K = 1.2mA$. This current is $I_{MAX} + I_{LOAD} = I_{MAX} + 400\mu A$, so I_{MAX} must be set to $800\mu A$. According to Figure 2, this means that RRNG should be around 1MΩ.

Since the voltage at the AOUT pin should not go below 1.5V, this limits the voltage at the bottom of R2 to be 1.5V minimum; this occurs when the DAC is providing its maximum current, I_{MAX} . In this case, $I_{MAX} + I_{LOAD}$ flows through R1, and I_{MAX} flows through R2. Thus,


$$R_2 I_{MAX} + R_1 (I_{MAX} + I_{LOAD}) = 5V - 1.5V = 3.5V \quad \text{Equation 1}$$

We already have found $R1=2.5K$, $I_{MAX} = 800\mu A$, $I_{LOAD} = 400\mu A$; we can now solve Equation 1 for R2 and find that it should be 625Ω.

Pullup Voltage Greater Than the TSC Power Supply

In the previous example, when the DAC current is zero, the voltage on the AOUT pin will rise above the TSC supply voltage. This is not a problem, however, since $V+$ was within the absolute maximum rating of the device; no special precautions are necessary. Many LCD displays require voltages much higher than the absolute maximum ratings of the TSCs. In this case, the addition of an NPN transistor, as shown in Figure 3, will protect the AOUT pin from damage.


Figure 3. DAC Circuit when Using $V+$ Higher than V_{supply} .

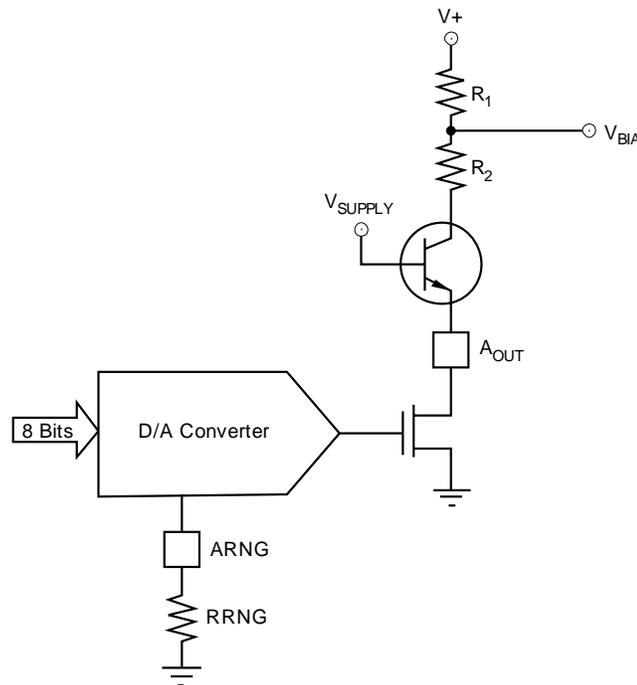

Extending the Output Voltage Range Below 1.5V

The addition of a differential amplifier eliminates the problem of having to have at least 1.5V on the AOUT pin, allowing the adjustable voltage from the DAC for LCD contrast control to go to 0V, if a bipolar or rail-to-rail op amp is used. The circuit connection is shown in Figure 4.

Figure 4. Adding a Differential Amplifier

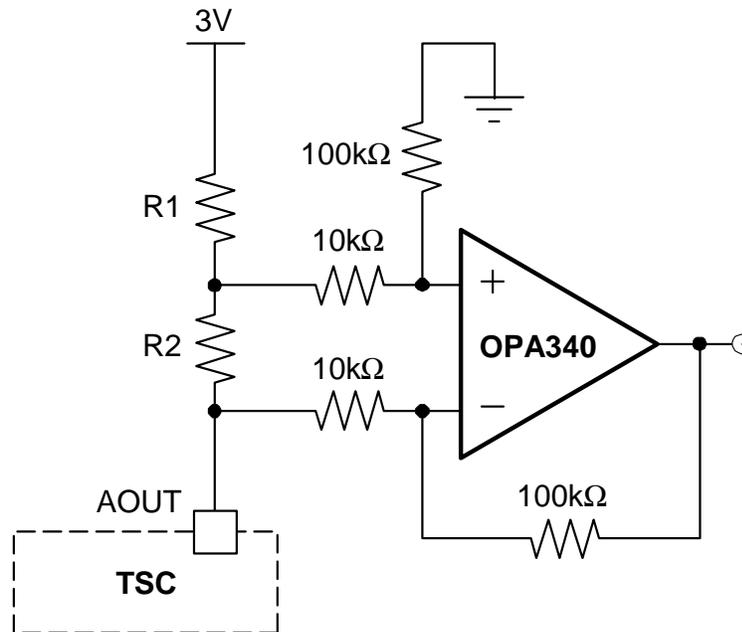

R1 and R2 must be chosen so that at the maximum DAC current, the desired output voltage, divided by the gain of the differential amplifier, is present across R2. In this example, we will assume that the maximum DAC current is 700 μ A, and that the desired output swing is 0V to 1.6V. Note that the gain in this example is 10.

With a 3V supply voltage, and with AOUT being at least 1.5V, 1.5V is dropped across R1+R2. Thus,

$$1.5V = 700\mu A(R_1 + R_2) \quad \text{Equation 2}$$

Solving Equation 2 shows that R1+R2 should be 2.1k Ω . Now, at 700 μ A, we want 1.6V/10 = 0.16V dropped across R2. Solving for this, we find that R2 should be 228 Ω . If we were to use easily available standard values, setting R2 = 270 Ω and R1 = 1.8K, we would have a system that would provide an output swing of 0 to 1.89V. If the output must be limited to 1.6V, then a value closer to the 228 Ω should be found for R2, and R1 adjusted accordingly.

References

1. *TSC2200 datasheet* (SBAS191)

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products & application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265